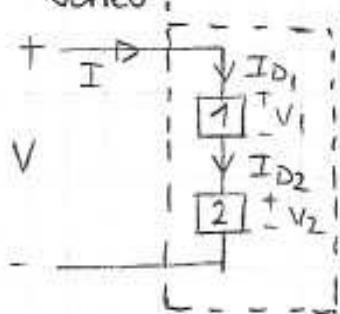


## Series & Parallel Combinations Of Circuit Components


Series:



$$\begin{aligned} I_1 &= I_2 = I && \left. \right\} \text{Due to Series connection} \\ V &= V_1 + V_2 \end{aligned}$$


$$V = f_1(I_1) + f_2(I_2)$$

$$V = f_1(I) + f_2(I)$$

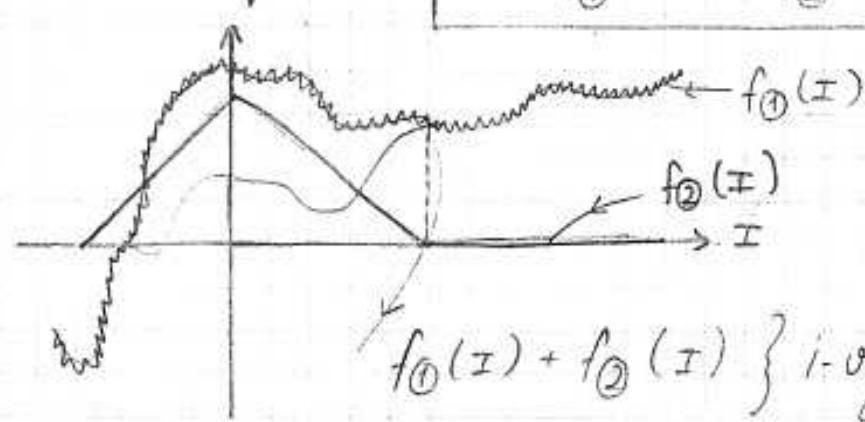

$f_1(I) + f_2(I)$  } i-v characteristic of  
combined component

Parallel:



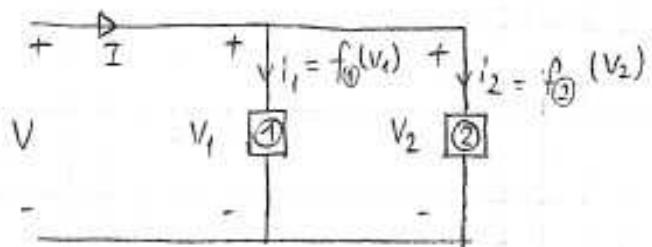



$$V_1 = V_2 = V$$

$$I = i_1 + i_2$$



$$= f_1(V_1) + f_2(V_2)$$

$$\boxed{I = f_1(v) + f_2(v)}$$

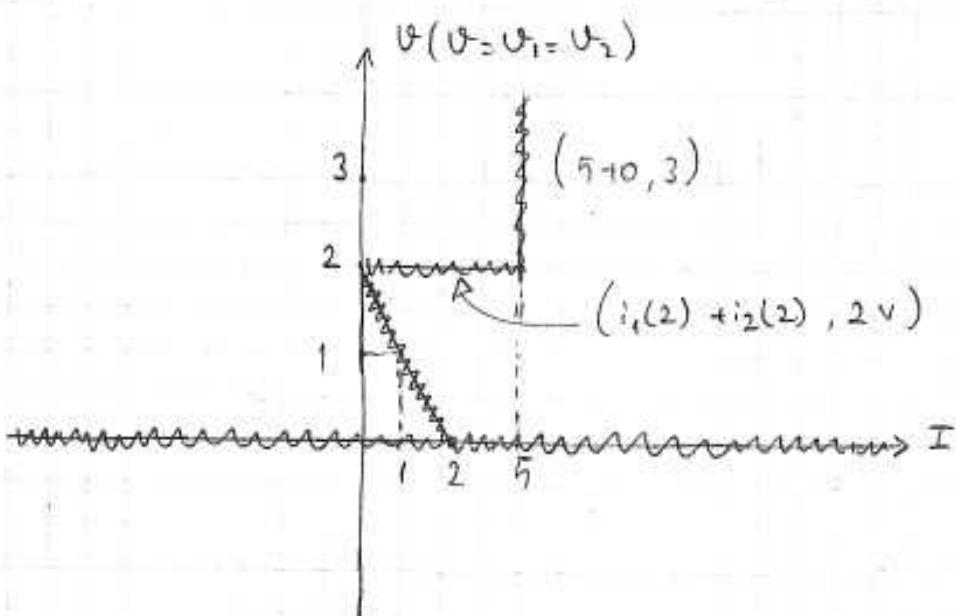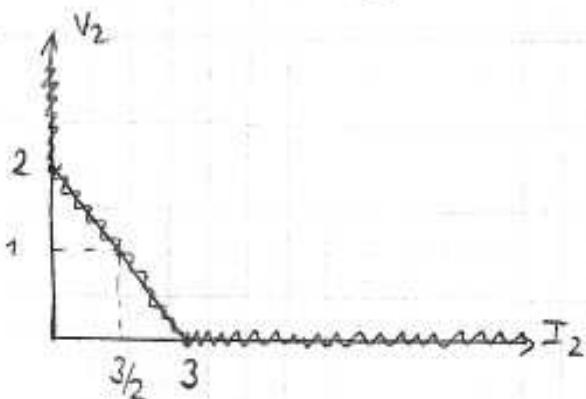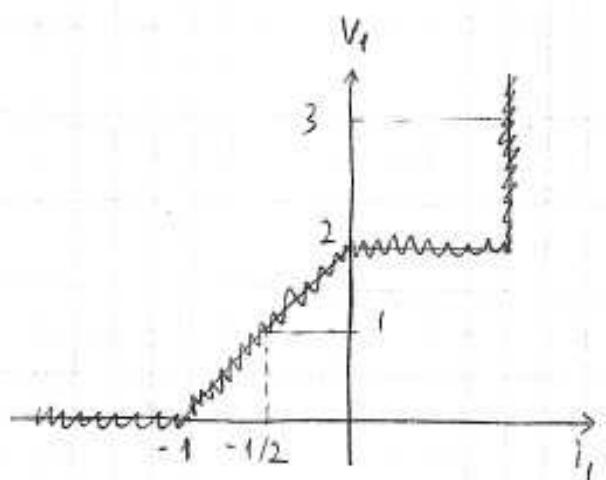


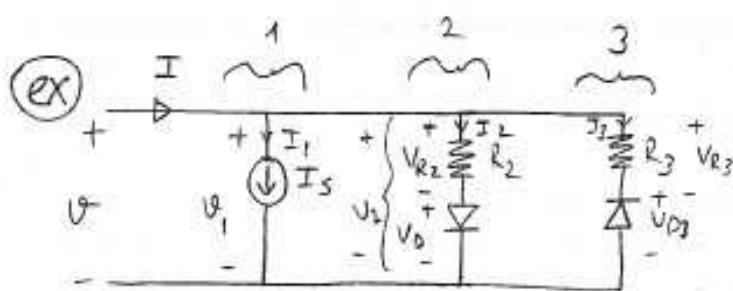

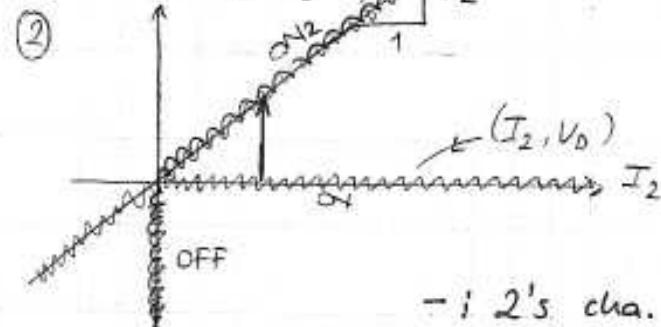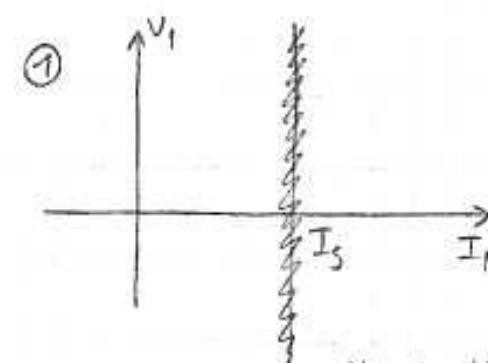$\rightarrow 1 \parallel 2 \parallel 3$   $(I_2, V_{R2})$




- i 2's cha.

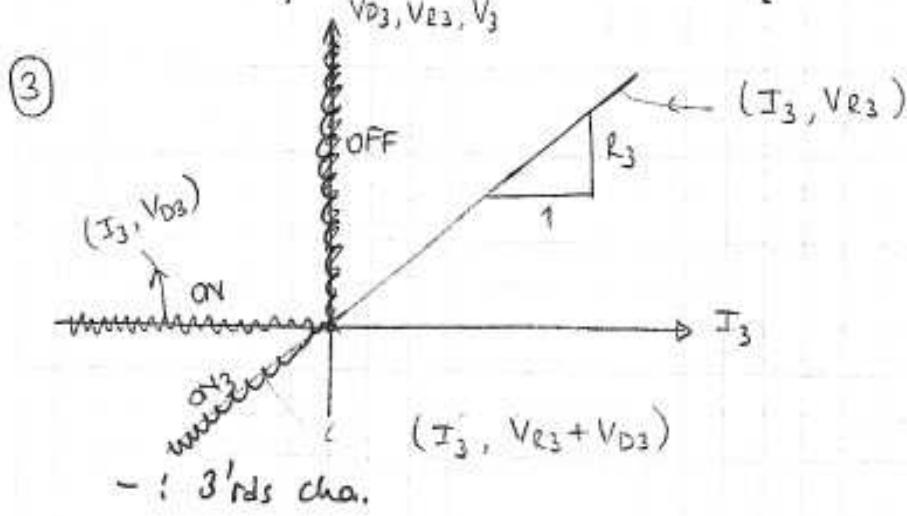

- i 3'rd's cha.


↓

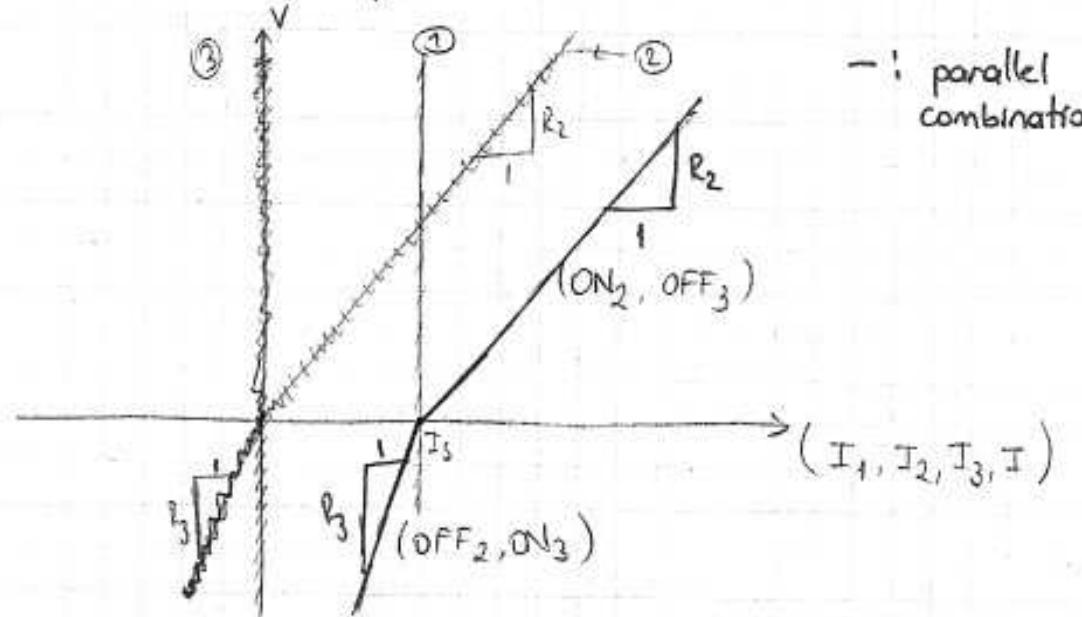

-: parallel combination



$(I_1, I_2, I_3, I)$

$(OFF_2, ON_3)$

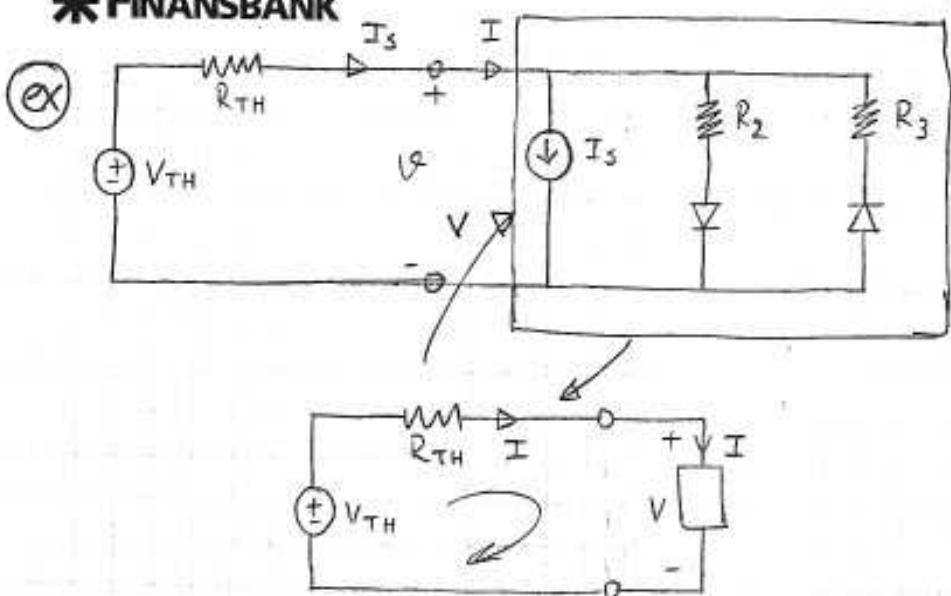


$$-V_{TH} + R_{TH} \cdot I + V = 0$$
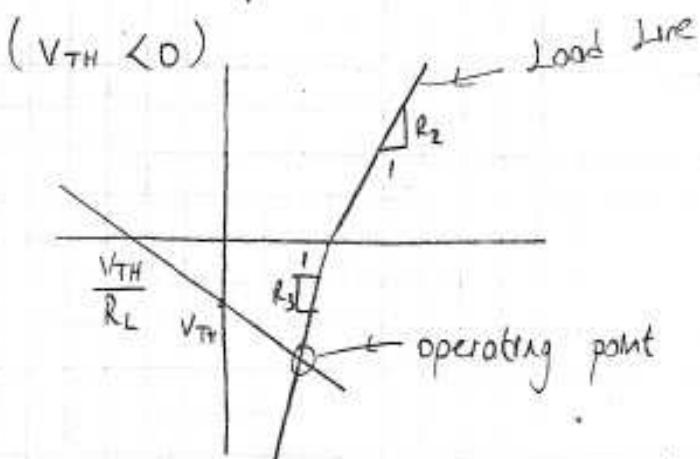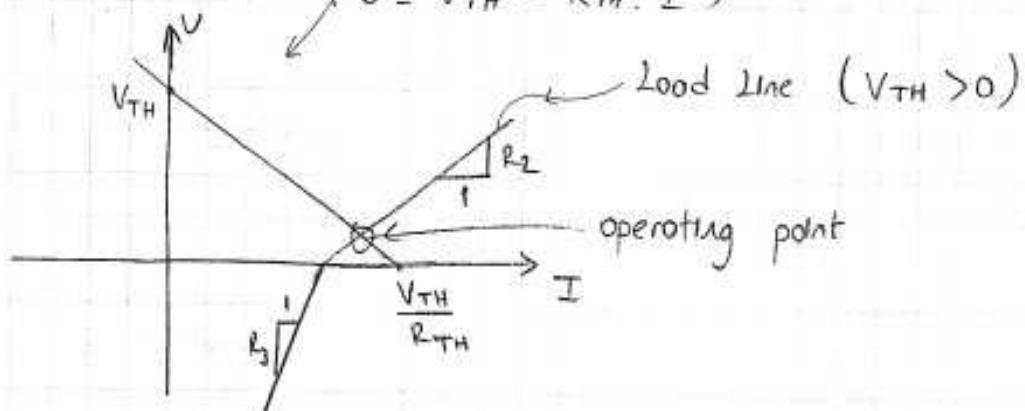
$$\{ \theta = V_{TH} - R_{TH} \cdot I \}$$




(ex)

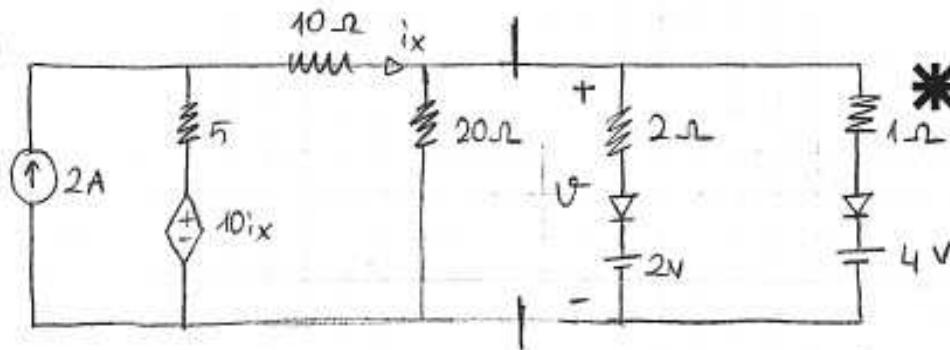

Find  $i_x$ .   
 → State Guessing  
 → Graphical Method

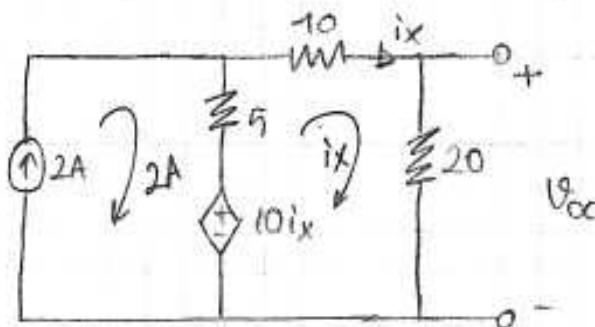Let's find Thévenin eq. of left hand side of "0+" branch.




$$\cancel{OC \text{ Voltage}} \quad -10ix + 5(ix-2) + 10ix + 20ix = 0$$

$$25ix = 10 \quad ix = \frac{2}{5} = 0.4 \text{ A}$$

$$V_{OC} = 20ix = 20 \cdot \frac{2}{5} = 8 \text{ V}$$


SC Current

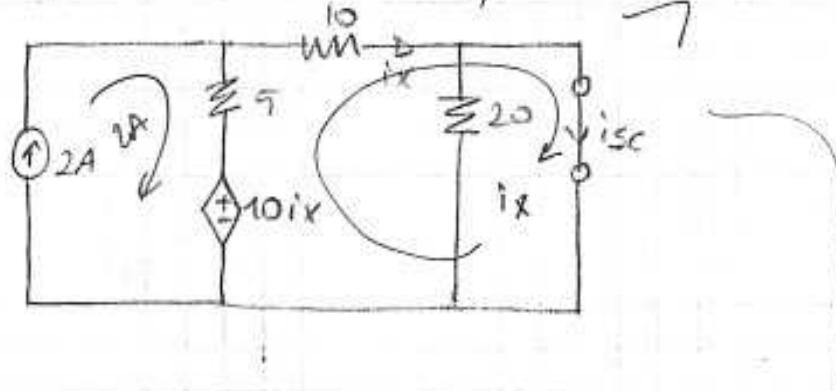


$$R_{TH} = \frac{V_T}{I_{SC}} = 4\Omega$$

$$-10ix + 5(ix-2) + 10ix = 0$$
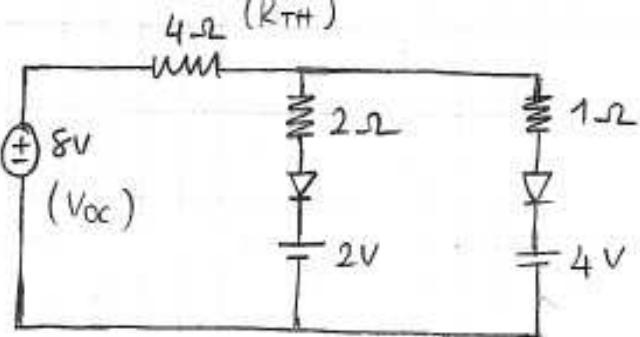
$$\underline{ix = 2 \text{ A}} \quad i_x = i_{SC} = 2 \text{ A}$$







Graphical

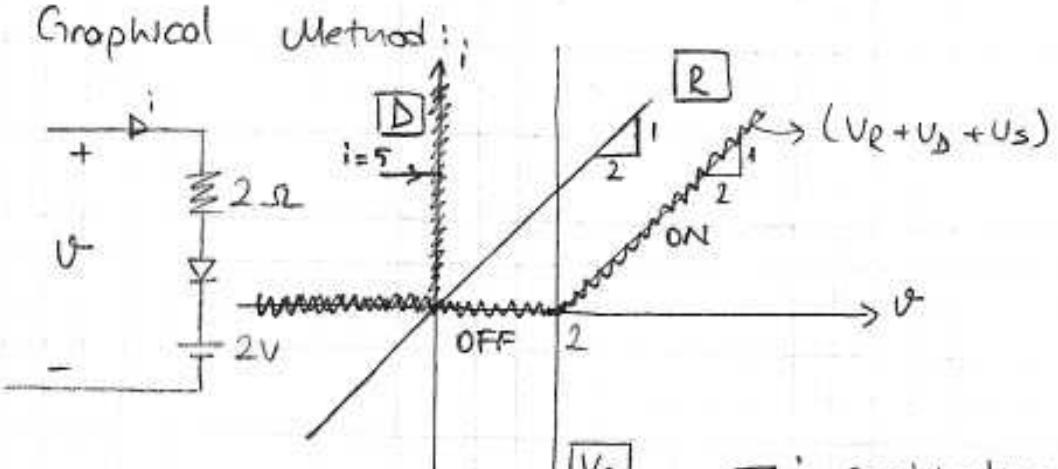



Method:

—: combination of three components

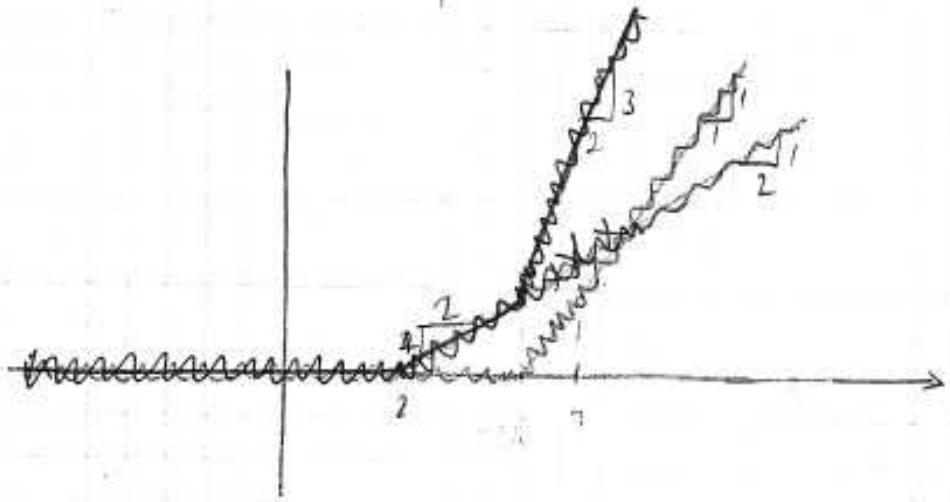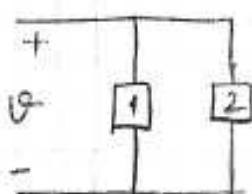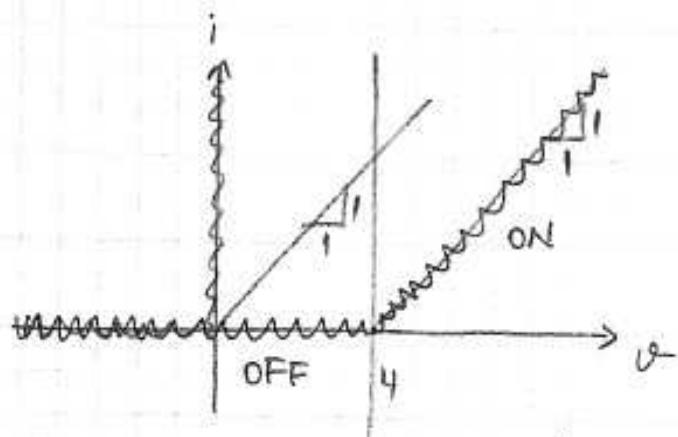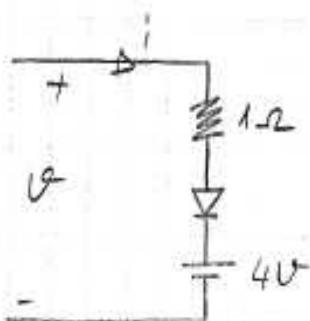✓ Diode does not allow a negative current.




—: combination 1-2 ✓

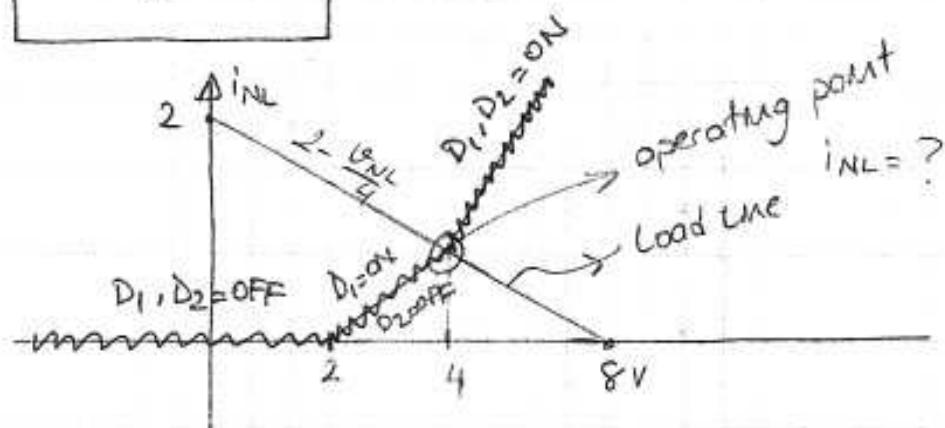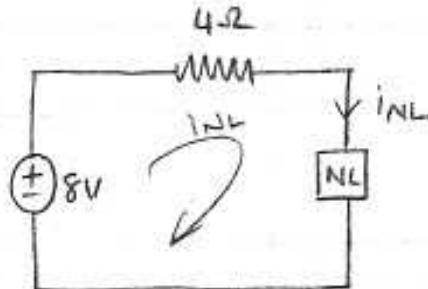

$$-8 + 4 \cdot i_{NL} + V_{NL} = 0$$


$$\boxed{i_{NL} = 2 - \frac{V_{NL}}{4}} \quad \leftarrow \text{KVL constraint}$$




(ex)

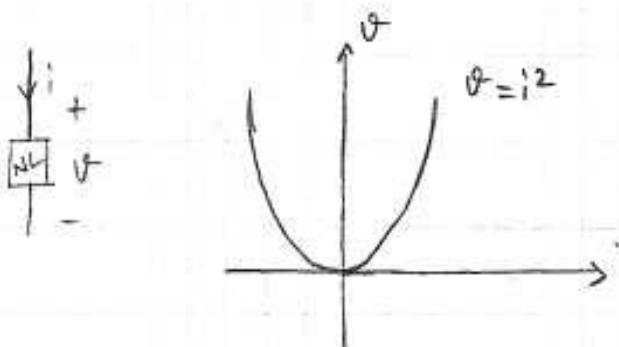

5.03.2010



Then find (1)

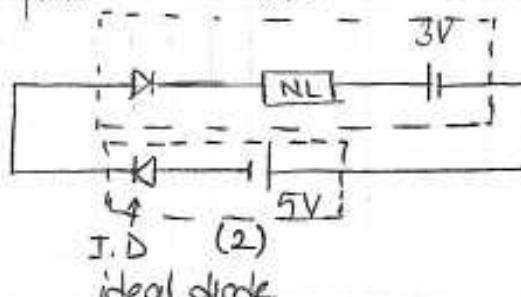

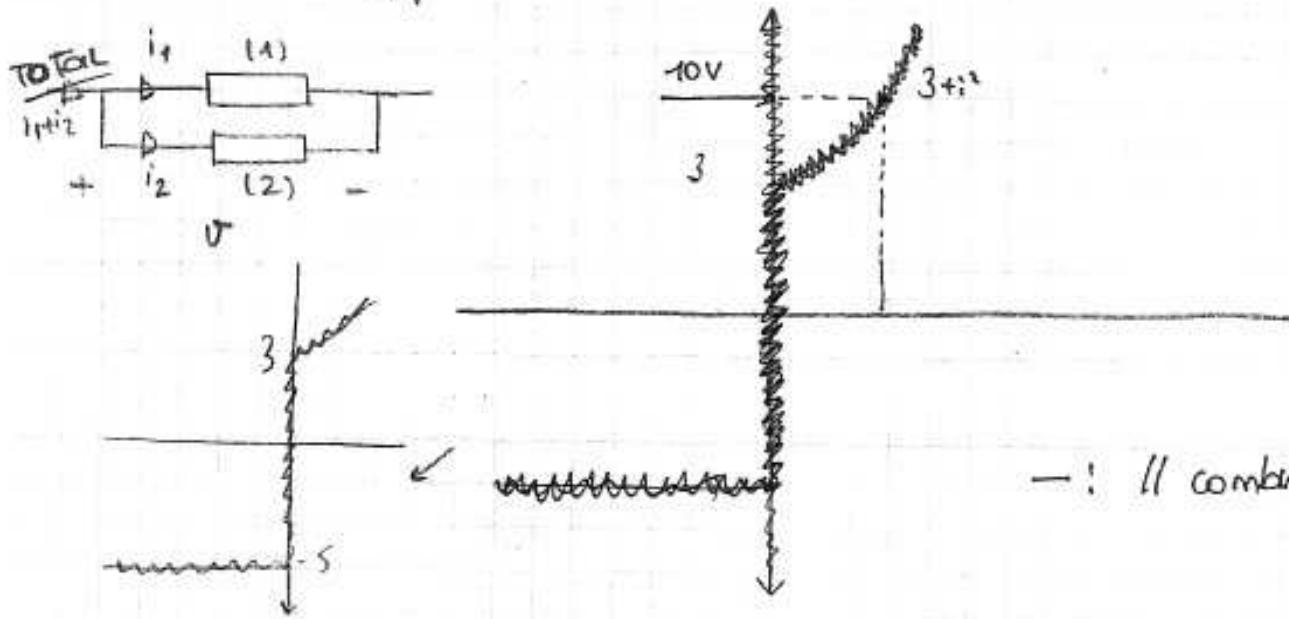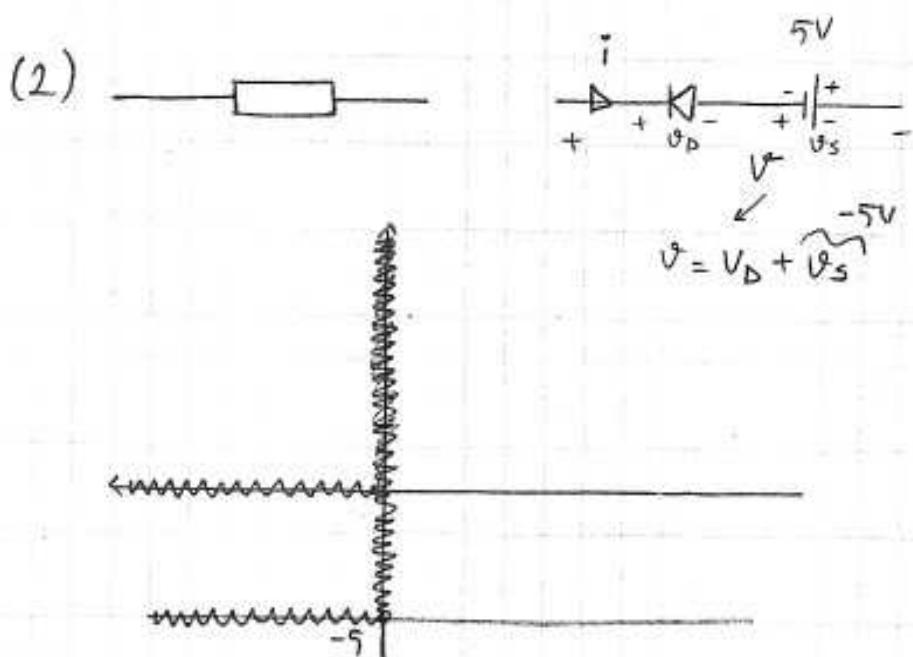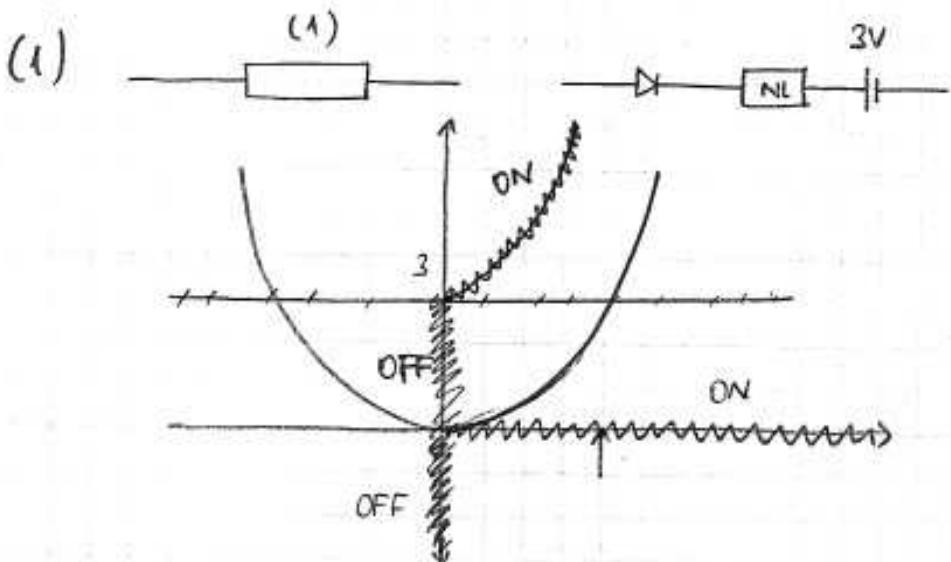

# Diode Applications:

## ① Half-Wave Rectifier:

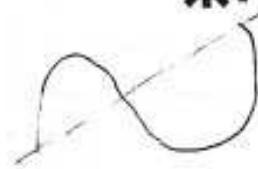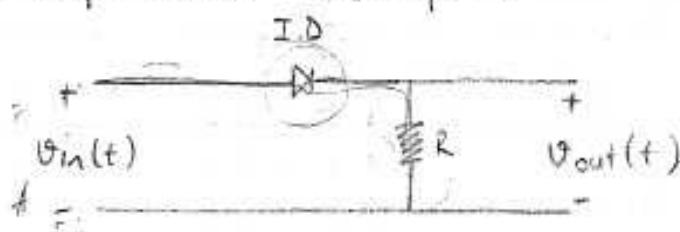


$$V_{out}(t) = \begin{cases} V_{in}(t) & V_{in}(t) > 0 \\ 0 & V_{in}(t) < 0 \end{cases}$$


Check:  $V_{in}(t) = A$

①  $A > 0$ , Diode ON,  $V_{out}(t) = V_{in}(t)$

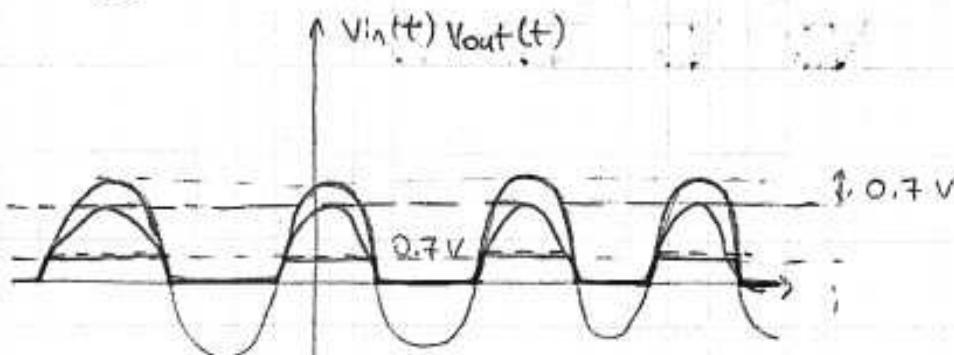②  $A < 0$ , Diode OFF,  $V_{out}(t) = 0$




→ Not Ideal

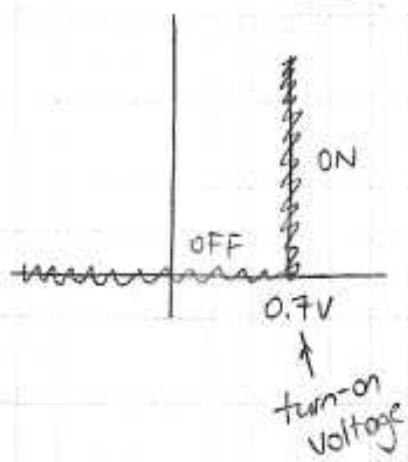


ON →

OFF →

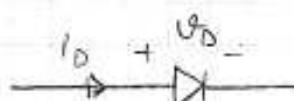


→ : this model

## ② Full-Wave Rectifier

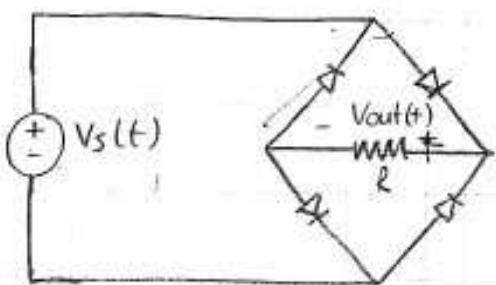

Diodes are ideal


$$V_{out}(t) = |V_{in}(t)|$$

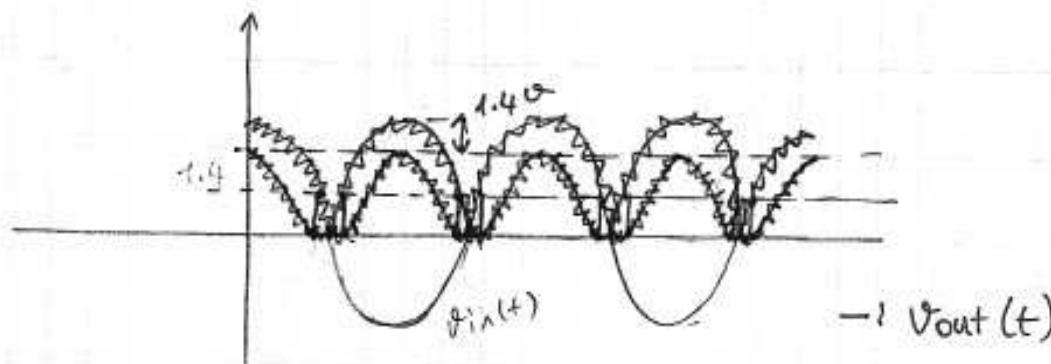

Check:

$$V_{in}(t) = A$$

$$\textcircled{1} \quad A > 0$$

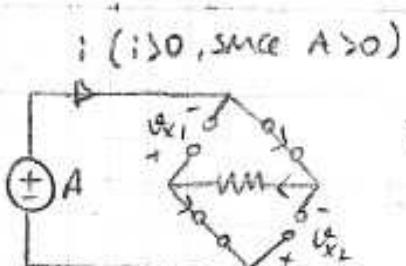


$$V_{x1} = V_{x2} = -A \quad \text{OFF}$$

$$V_{out}(+) = A$$

-: not-ideal model  
Vout(t)

$$\textcircled{2} \quad A < 0$$

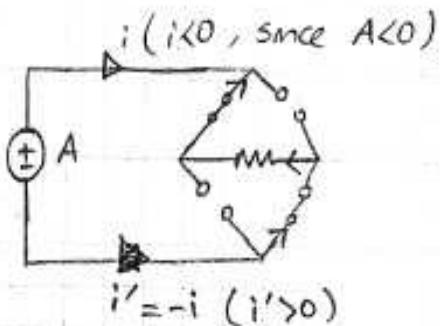

$$\begin{aligned} V_{out} &= i'R \\ &= -A \end{aligned}$$