

Nth Order Dynamic Circuits lecture Notes of Kamil Nar (Spring 2010)

Generalized branch:



Graph theoretical node analysis

↓
we use generalized branches for voltage sources.


① $\underline{A} \cdot \underline{J} = 0$ KCL
 ② $\underline{J} = \underline{G} \cdot \underline{v}$ Terminal eq } \underline{J} better be \underline{i}

③ $\underline{v} = \underline{A}^T \underline{e}$ → Auxiliary equation from graph
 ↓
 Branch voltages → node voltages (e_1, e_3)


Inserting ③ into ②

$\underline{J} = \underline{G} \cdot \underline{A}^T \underline{e}$
 $\underline{A} \cdot \underline{J} = \underline{A} \cdot \underline{G} \cdot \underline{A}^T \underline{e} = 0$
 known matrix ↓ unknown vector

Ex

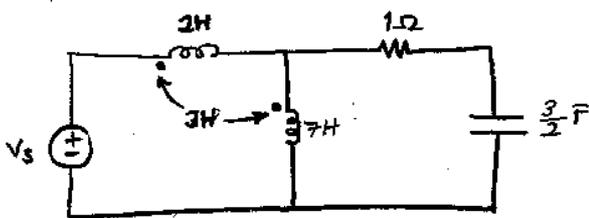

Graph theoretical node analysis:

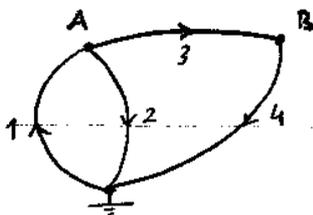

$$A = \begin{bmatrix} 1 & 2 & 3 & 4 \\ -1 & 1 & 1 & 0 \\ 0 & 0 & -1 & 1 \end{bmatrix}$$

$J_3 = \frac{v_3}{1\Omega} = v_3$

$J_4 = \frac{3}{2} \frac{d}{dt} v_4(t)$

$$\begin{bmatrix} v_{2H}(t) \\ v_{3H}(t) \end{bmatrix} = \begin{bmatrix} 2 & 3 \\ 3 & 7 \end{bmatrix} \begin{bmatrix} \frac{d}{dt} i_{2H}(t) \\ \frac{d}{dt} i_{3H}(t) \end{bmatrix}$$

$J_1 = i_{2H}(t)$

$J_2 = i_{3H}(t)$

$$\begin{bmatrix} D & i_{2H}(t) \\ D & i_{7H}(t) \end{bmatrix} = \frac{1}{5} \begin{bmatrix} 7 & -3 \\ -3 & 2 \end{bmatrix} \begin{bmatrix} v_{2H}(t) \\ v_{7H}(t) \end{bmatrix}$$

$$\begin{bmatrix} i_{2H}(t) - i_{2H}(0) \\ i_{7H}(t) - i_{7H}(0) \end{bmatrix} = \frac{1}{5} \begin{bmatrix} 7 & -3 \\ -3 & 2 \end{bmatrix} \begin{bmatrix} \int_0^t v_{2H}(\tau) d\tau \\ \int_0^t v_{7H}(\tau) d\tau \end{bmatrix}$$

$$J_1 = i_{2H}(0) + \frac{7}{5} D^{-1} v_{2H}(t) - \frac{3}{5} D^{-1} v_{7H}(t)$$

$$J_2 = i_{7H}(0) - \frac{3}{5} D^{-1} v_{2H}(t) + \frac{2}{5} D^{-1} v_{7H}(t)$$

$$v_{2H} = v_1 + v_5$$

$$v_{7H} = v_2$$

$$\begin{bmatrix} J_1 \\ J_2 \\ J_3 \\ J_4 \end{bmatrix} = \begin{bmatrix} \frac{7}{5} D^{-1} & -\frac{3}{5} D^{-1} & 0 & 0 \\ -\frac{3}{5} D^{-1} & \frac{2}{5} D^{-1} & 0 & 0 \\ 0 & 0 & 1 & 0 \\ 0 & 0 & 0 & \frac{3}{2} D \end{bmatrix} \begin{bmatrix} v_1 \\ v_2 \\ v_3 \\ v_4 \end{bmatrix} + \begin{bmatrix} i_{2H}(0) \\ i_{7H}(0) \\ 0 \\ 0 \end{bmatrix} + \begin{bmatrix} \frac{7}{5} D^{-1} \\ -\frac{3}{5} D^{-1} \\ 0 \\ 0 \end{bmatrix} v_5$$

$$J = \underline{G} \cdot \underline{v} + \underline{i}(0) + \underline{v}_5$$

$$\underline{A} \cdot J = \underline{A} \cdot \underline{G} \cdot \underline{v} + \underline{A} \cdot \underline{i}(0) + \underline{A} \cdot \underline{v}_5 = 0$$

$$\underline{A} \cdot \underline{G} \cdot \underline{A}^T \cdot \underline{e} + \underline{A} \cdot \underline{i}(0) + \underline{A} \cdot \underline{v}_5 = 0$$

$$A = \begin{bmatrix} -1 & 1 & 1 & 0 \\ 0 & 0 & -1 & 1 \end{bmatrix}$$

$$\left(\underline{A} \underline{G} \underline{A}^T \right) \begin{bmatrix} e_A \\ e_B \end{bmatrix} = - \begin{bmatrix} i_{7H}(0) - i_{2H}(0) - 2 D^{-1} v_5(t) \\ 0 \end{bmatrix}$$


$$\left[\begin{array}{c|c} 3D^{-1} + 1 & -1 \\ -1 & 1 + \frac{3}{2}D \end{array} \right] \begin{bmatrix} e_A \\ e_B \end{bmatrix} = \begin{bmatrix} i_{2H}(0) - i_{7H}(0) + 2D^{-1} v_5(t) \\ 0 \end{bmatrix}$$

↳ integro-differential equation

Initial conditions for the solution of differential equation:

$$i_{2H}(0) = i_{2H} \quad ; \quad i_{7H}(0^-) = i_{7H} \quad ; \quad V_{\frac{3}{2}F}(0^-) = V_{\frac{3}{2}F}$$

At $t = 0^+$

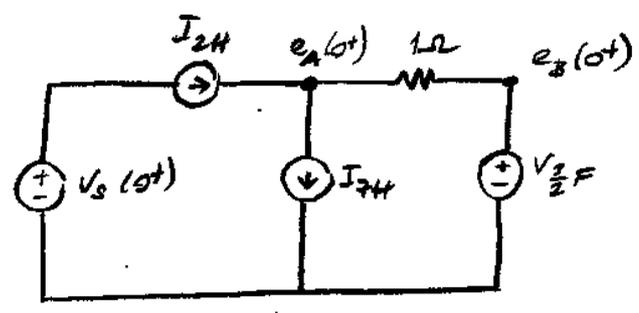

$$e_B(t) = V_{\frac{3}{2}F}(0^-)$$

$$e_A(t) = e_B(t) + i_{2H}(0^-) - i_{7H}(0^-)$$

KCL at e_B :

$$\frac{e_B - e_A}{1} + \frac{3}{2} \frac{d}{dt} e_B(t) = 0 \quad \checkmark$$

KCL at e_A :


$$\frac{e_A - e_B}{1} + i_{7H}(t) - i_{2H}(t) = 0 \quad \dots (*)$$

$$\begin{bmatrix} i_{2H}(t) \\ i_{7H}(t) \end{bmatrix} = \begin{bmatrix} 7/5 D^{-1} & -3/5 D^{-1} \\ -3/5 D^{-1} & 2/5 D^{-1} \end{bmatrix} \begin{bmatrix} v_{2H}(t) \\ v_{7H}(t) \end{bmatrix} + \begin{bmatrix} i_{2H}(0^-) \\ i_{7H}(0^-) \end{bmatrix}$$

$$i_{7H}(t) - i_{2H}(t) = \underbrace{-2D^{-1} v_{2H}(t)}_{v_s(t) - e_A(t)} + \underbrace{D^{-1} v_{7H}(t)}_{e_A(t)} + i_{7H}(0^-) - i_{2H}(0^-)$$

$$= 3D^{-1} e_A - 2D^{-1} v_s(t) - i_{2H}(0) + i_{7H}(0) \rightarrow \text{into } (*)$$

Ex: (Mesh Analysis)

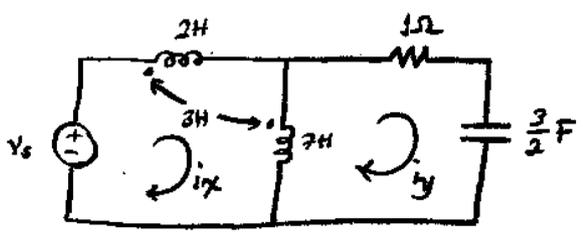

$$\begin{bmatrix} v_{2H} \\ v_{7H} \end{bmatrix} = \begin{bmatrix} 2 & 3 \\ 3 & 7 \end{bmatrix} \begin{bmatrix} \dot{i}_{2H} \\ \dot{i}_{7H} \end{bmatrix}$$

KVL around i_x :

$$-V_s + V_{2H}(t) + V_{7H}(t) = 0$$

$$i_{2H} = i_x$$

$$i_{7H} = i_x - i_y$$

$$-V_s + 5 \dot{i}_x + 10 \dot{i}_x - 10 \dot{i}_y = 0$$

$$15 D i_x - 10 D i_y = V_s$$

KVL around i_y :

$$-V_{7H}(t) + 1 \cdot \dot{i}_y(t) + V_C(t) = 0$$

$$\downarrow$$

$$V_C(0^-) + \frac{1}{C} \int_0^t i_C(\tau) d\tau$$

$$\downarrow$$

$$i_y(\tau)$$


$$-10 D i_x + 7 D i_y + i_y + V_C(0^-) + \frac{2}{3} D^{-1} i_y(t) = 0$$

$$\begin{bmatrix} 15 D & -10 D \\ -10 D & 7 D + 1 + \frac{2}{3} D^{-1} \end{bmatrix} \begin{bmatrix} i_x(t) \\ i_y(t) \end{bmatrix} = \begin{bmatrix} V_s(t) \\ -V_C(0^-) \end{bmatrix}$$


$$i_x(0^+) = i_{2H}(0^-)$$

$$i_y(0^+) = i_{2H}(0^-) - i_{7H}(0^-)$$

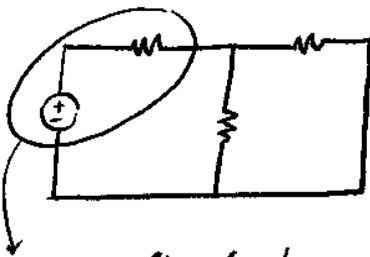Generalized Branch: (when graph theoretical node / mesh is written)



Generalized branch for node analysis

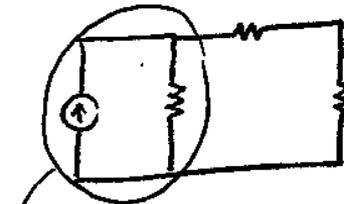


Generalized branch for mesh analysis.

Modified Node Analysis (MNA)

In MNA, we write equations such that we end up with a differential equation instead of an integro-differential eqn. To do that:

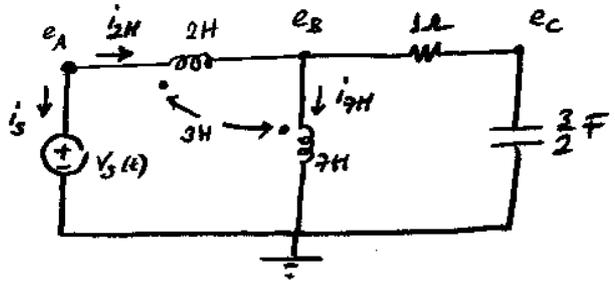- ① Assign auxiliary variables (other than node voltage variables) for inductors, voltage sources
- ② Write the KCL equations as in node analysis, use auxiliary variables where necessary
- ③ Write additional equations for auxiliary variables




KCL @ eA:

$$\begin{bmatrix} 0 & 0 & 0 & 1 & 1 & 0 \\ 0 & 1 & -1 & 0 & -1 & 1 \\ 0 & -1 & 1 + \frac{3}{2}D & 0 & 0 & 0 \\ 1 & 0 & 0 & 0 & 0 & 0 \\ 1 & -1 & 0 & 0 & -2D & -3D \\ 0 & 1 & 0 & 0 & -3D & -3D \end{bmatrix} \begin{bmatrix} e_A \\ e_B \\ e_C \\ i_{2H} \\ i_{7H} \\ i_{7H} \end{bmatrix} = \begin{bmatrix} 0 \\ 0 \\ 0 \\ V_s \\ 0 \\ 0 \end{bmatrix}$$

$$\begin{bmatrix} V_{2H} \\ V_{7H} \end{bmatrix} = \begin{bmatrix} e_A - e_B \\ e_B \end{bmatrix} = \begin{bmatrix} 2 & 3 \\ 3 & 7 \end{bmatrix} \begin{bmatrix} D i_{2H} \\ D i_{7H} \end{bmatrix}$$

At $t = 0^+$

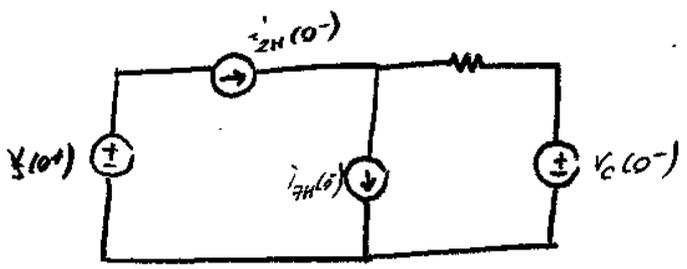

$$\begin{aligned} e_A(0^+) &= V_s(0^+) \\ e_B(0^+) &= V_c(0^+) + I_{2H}(0^+) - I_{7H}(0^+) \\ e_C(0^+) &= V_c(0^+) \\ i_{2H}(0^+) &= i_{2H}(0^-) \\ i_{7H}(0^+) &= i_{7H}(0^-) \\ i_s(0^+) &= -i_{2H}(0^-) \end{aligned}$$

State Equations

$$\dot{\underline{x}}(t) = \underline{A} \cdot \underline{x}(t) + \underline{B} \cdot \underline{u}(t)$$

Ex:

$$\begin{bmatrix} \dot{x}_1(t) \\ \dot{x}_2(t) \end{bmatrix} = \begin{bmatrix} 1 & 2 \\ 5 & 6 \end{bmatrix} \begin{bmatrix} x_1(t) \\ x_2(t) \end{bmatrix} + \underbrace{\begin{bmatrix} 1 \\ 0 \end{bmatrix} v_s(t) + \begin{bmatrix} 0 \\ 2 \end{bmatrix} i_s(t)}_{\begin{bmatrix} 1 & 0 \\ 0 & 2 \end{bmatrix} \begin{bmatrix} v_s(t) \\ i_s(t) \end{bmatrix}}$$

1st order matrix differential equation!

Solution is by Laplace transform, or eigen-decomposition of \underline{A} , or through state-transition matrices, series expansion.

State variables: { Capacitor voltages, Inductor current }

Steps: ① Include all voltage sources in tree, all current sources in co-tree



② Put maximum number of possible capacitors in tree, minimum number of possible inductors

③ If there is a transformer, put only one - but one - branch of transformer in tree.

Writing the equations:

State variables: All capacitor voltages in the tree and all inductor currents in co-tree are state variables.

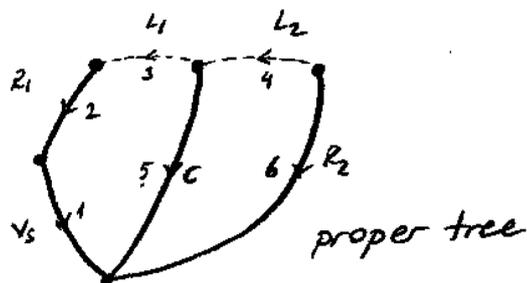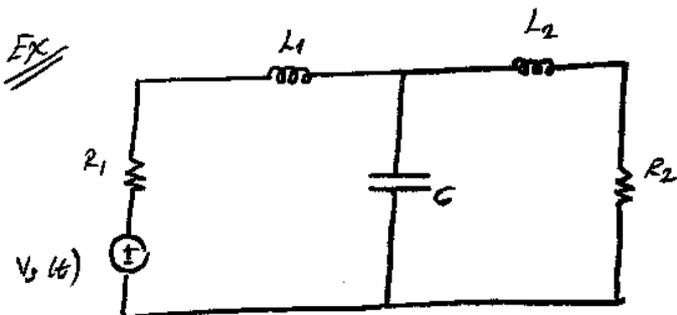- 1) write fundamental-loop (KVL) for each inductor current in the co-tree.
- 2) write fundamental cut-set (KCL) for each capacitor voltage in the tree



state variables = { $v_C(t)$, $i_{L_1}(t)$ + $i_{L_2}(t)$ }

Order of = # of state = 3

For L_1 , KVL:

$$v_3 + v_2 + v_1 - v_5 = 0 \text{ (Fundamental loop for } L_1 \text{ branch)}$$

$$L_1 \dot{i}_{L_1} + R_1 i_{L_1} + v_5 - \mathcal{J}_C = 0$$

\hookrightarrow not a state var. \rightarrow express in terms of state var.

\Rightarrow write fund. cut-set for i_{L_1} branch *

$$i_{L_1} = i_{L_1}$$

$$\dot{i}_{L_1}(t) = -\frac{R_1}{L_1} i_{L_1}(t) + \frac{1}{L_1} v_C(t) - \frac{\mathcal{J}_S(t)}{L_1}$$

For L_2 , KVL:

$$v_{L_2} + v_C - \mathcal{J}_C = 0$$

$$L_2 \dot{i}_{L_2} + \mathcal{J}_C - R_2 i_{L_2} = 0$$

\downarrow
 $-i_{L_2}$ from fundamental cut-set

$$\dot{i}_{L_2}(t) = -\frac{R_2}{L_2} i_{L_2}(t) - \frac{1}{L_2} v_C(t)$$


For C, KCL:

$$i_C - i_{L_2} + i_{L_1} = 0$$

$$\dot{v}_C = -\frac{1}{C} i_{L_1} + \frac{1}{C} i_{L_2}$$

$$\begin{bmatrix} \dot{v}_C(t) \\ \dot{i}_{L_1}(t) \\ \dot{i}_{L_2}(t) \end{bmatrix} = \begin{bmatrix} 0 & -1/C & 1/C \\ 1/L_1 & -R_1/L_1 & 0 \\ -1/L_2 & 0 & -R_2/L_2 \end{bmatrix} \begin{bmatrix} v_C(t) \\ i_{L_1}(t) \\ i_{L_2}(t) \end{bmatrix} + \begin{bmatrix} 0 \\ -1/L_1 \\ 0 \end{bmatrix} \mathcal{J}_S(t)$$

EX

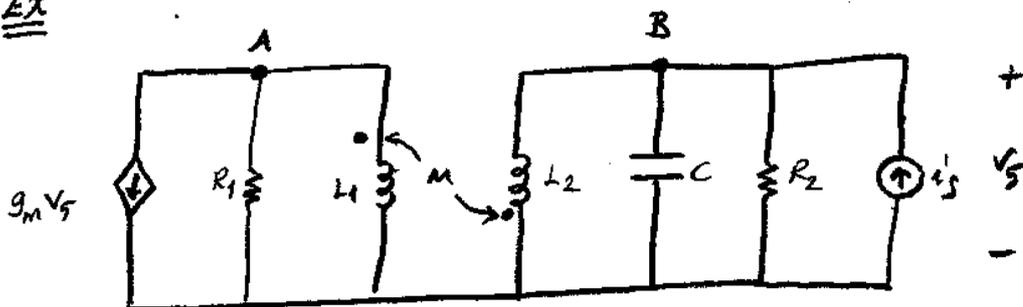


+
 v_S
-

$$v_C(0^-) = J_0$$

$$i_{L_1}(0^-) = I_0^{L_1}$$

$$i_{L_2}(0^-) = I_0^{L_2}$$

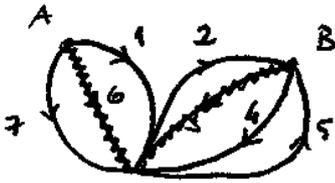

Current sources (dependent ones too) are not included in tree.

State Eqn:

Fund. cut-set of capacitor branches:

$$i_3 + i_4 - i_5 - i_2 = 0$$

$$C \cdot \dot{v}_C + \frac{v_4}{R_2} - i_5 - \frac{i_{L_2}}{\sqrt{}} = 0$$

Fund. loop $\rightarrow v_4 = v_C$

$$\dot{v}_C(t) = \frac{1}{C} i_{L_2}(t) - \frac{1}{R_2 \cdot C} v_C(t) + \frac{i_5(t)}{C}$$

$$\begin{bmatrix} v_{L_1}(t) \\ v_{L_2}(t) \end{bmatrix} = \begin{bmatrix} L_1 & M \\ M & L_2 \end{bmatrix} \begin{bmatrix} \frac{d}{dt} i_{L_1}(t) \\ \frac{d}{dt} i_{L_2}(t) \end{bmatrix}$$

things we are looking for!



$$\begin{bmatrix} \frac{d}{dt} i_{L_1}(t) \\ \frac{d}{dt} i_{L_2}(t) \end{bmatrix} = \frac{1}{L_1 L_2 - M^2} \begin{bmatrix} L_2 & -M \\ -M & L_1 \end{bmatrix} \begin{bmatrix} v_{L_1}(t) \\ v_{L_2}(t) \end{bmatrix}$$

$$v_{L_1}(t) \xrightarrow{\text{fund. loop}} v_{R_1} \xrightarrow{\text{term. eqn.}} i_{R_1} \cdot R_1 \xrightarrow{\text{fund. cutset}} R_1 (-g_m v_5 - i_{L_1})$$

$$\xrightarrow{\text{fund. loop}} R_1 (-g_m \dot{v}_C - \frac{i_{L_1}}{\sqrt{}})$$

$$v_{L_2}(t) \xrightarrow{\text{fund. loop}} -\dot{v}_C$$

Ex

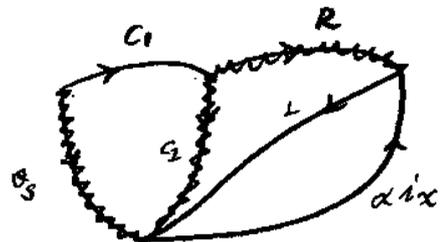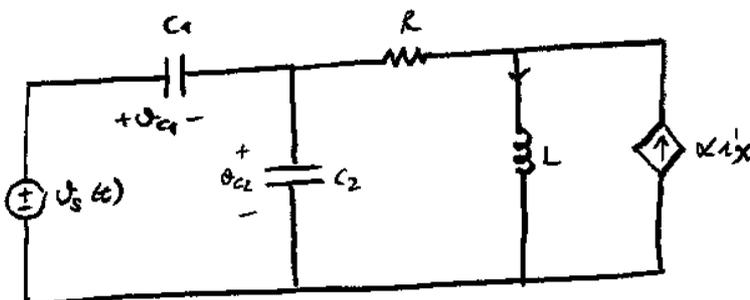

State variables: $\{ v_{c2}, i_L \}$ *

\swarrow capacitors on tree \searrow inductors on co-tree

→ Fund. cut-set of C_2 branch:

$$-i_{c1} + i_{c2} + i_L - \alpha i_x = 0$$

$$\downarrow \qquad \downarrow$$

$$-C_1 \dot{v}_{c1} + C_2 \dot{v}_{c2} + i_L - \alpha C_2 \dot{v}_{c2} = 0$$

$$\downarrow$$

$$-C_1 (\dot{v}_s - \dot{v}_{c2}) + C_2 (1-\alpha) \dot{v}_{c2} + i_L = 0$$

$$\dot{v}_{c2}(t) = \frac{-1}{C_1 + C_2(1-\alpha)} i_L + \frac{C_1}{C_1 + C_2(1-\alpha)} \dot{v}_s(t)$$

→ Fund Loop for L branch:

$$v_L = -v_R + v_{c2}$$


$$L \cdot \dot{i}_L \xrightarrow{\text{F.L.}} i_L \cdot R = (i_L - \alpha i_x) R = (i_L - \alpha C_2 \dot{v}_{c2}) R$$

↓
from 1st state eqn.


$$L \cdot \dot{i}_L = -R \cdot i_L + R \cdot C_2 \cdot \alpha \left(\frac{-i_L}{C_1 + C_2(1-\alpha)} + \frac{C_1}{C_1 + C_2(1-\alpha)} \dot{v}_s(t) \right) + v_{c2}$$

Note: 3 dynamic elements but 2 state variables!

Exo

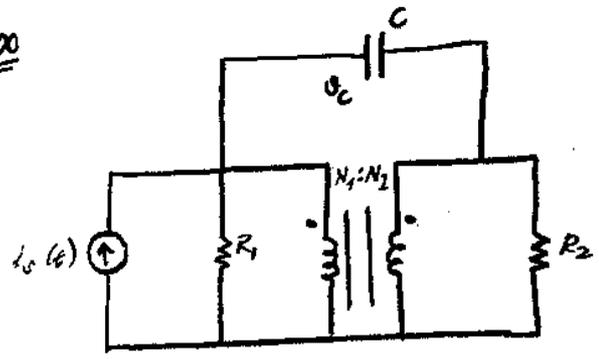

$$v_c(0^-) = v_0$$

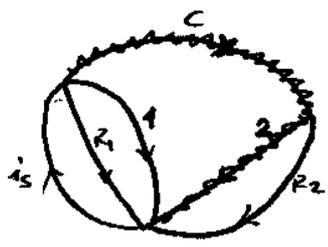

$$\frac{v_1}{v_2} = \frac{N_1}{N_2} \quad ; \quad \frac{i_1}{i_2} = \frac{-N_2}{N_1}$$

$$i_c + i_1 + i_2 - i_s = 0$$

$$C \dot{v}_c - \frac{N_2}{N_1} i_2 + \frac{\mathcal{P}R_1}{R_1} - i_s = 0$$

$$\text{F.L. } v_c + v_2 = v_c + v_1 \cdot \frac{N_2}{N_1} = v_1 \rightarrow v_1 = \frac{v_c}{1 - N_2/N_1} = \frac{N_1 v_c}{N_1 - N_2}$$

$$v_2 = \frac{N_2 v_c}{N_1 - N_2}$$

$$\text{F.C. } i_2 = -i_2 - i_1 - i_2 + i_s = -\frac{\mathcal{P}R_2}{R_2} + \frac{N_2}{N_1} i_2 - \frac{\mathcal{P}R_1}{R_1} + i_s \dots$$

2nd try

$$C \dot{v}_c = i_s - i_2 - i_1$$

State var = $\{v_c\}$

$$v_1 = \frac{v_c \cdot N_1}{N_1 - N_2}$$

Fund. cut-set for 2:


$$i_2 = i_s - i_2 - i_1 - i_2$$

$$i_2 = i_s - \frac{v_1}{R_1} - i_1 - \frac{v_2}{R_2}$$

$$-\frac{N_1}{N_2} i_1 = i_s - \frac{v_2}{R_1} \cdot \frac{N_1}{N_1 - N_2} - i_1 - \frac{v_c N_2}{R_2 \cdot (N_1 - N_2)}$$

$$i_1 = \frac{i_s - \frac{v_c}{N_1 - N_2} \left(\frac{N_1}{R_1} + \frac{N_2}{R_2} \right)}{1 - N_1/N_2}$$


EX

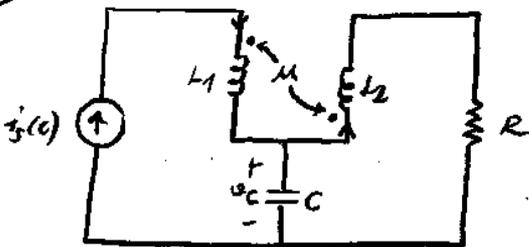

Solution:

$$\begin{bmatrix} \dot{v}_c \\ i_{L2} \end{bmatrix} = \begin{bmatrix} 0 & 1/C \\ -1/L_2 & -R/L_2 \end{bmatrix} \begin{bmatrix} v_c \\ i_{L2} \end{bmatrix} + \begin{bmatrix} 1/C \\ 0 \end{bmatrix} i_s + \begin{bmatrix} 0 \\ M/L_2 \end{bmatrix} i_s$$

Ex

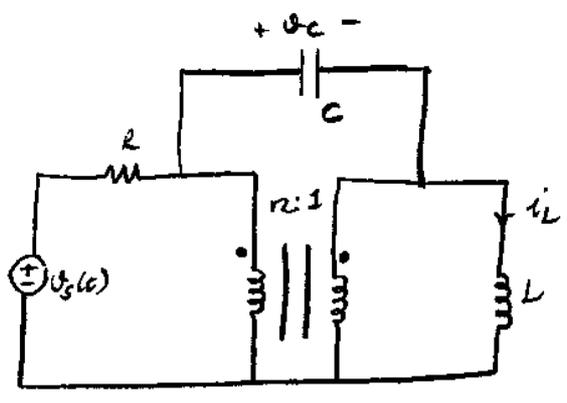


$$\begin{bmatrix} \dot{v}_c \\ \dot{I}_L \end{bmatrix} = \begin{bmatrix} \frac{-n^2}{(n-1)^2 RC} & \frac{-1}{(n-1)C} \\ \frac{1}{(n-1)L} & 0 \end{bmatrix} \begin{bmatrix} v_c \\ I_L \end{bmatrix} + \begin{bmatrix} \frac{1}{(n-1)RC} + \frac{1}{RC} \\ 0 \end{bmatrix} v_s(t)$$

Time-Invariance

When input is shifted in time, if output is also shifted system is time-invariant

Application: R, L, C
 ↓
 multiple $R, \frac{1}{R}$
 $\int/dt, \int_{-\infty}^t$

Solution of Nth order Dif Eqn:

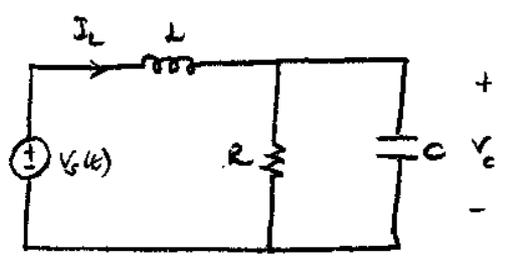

$$\begin{aligned} v_c(0^-) &= v_0 \\ I_L(0^-) &= I_0 \end{aligned}$$

Node analysis:

$$C \cdot \dot{v}_c + \frac{v_c}{R} - I_L = 0$$

↓



$$I_L(0^-) + \frac{1}{L} \int_0^t [v_s(\tau) - v_c(\tau)] d\tau$$

$$C \cdot \ddot{v}_c + \frac{\dot{v}_c}{R} + \frac{v_c - v_s(t)}{L} = 0 \rightarrow \left(D^2 + \frac{1}{RC} D + \frac{1}{LC} \right) v_c(t) = \frac{v_s(t)}{LC}$$

$$v_c(0^-) = v_0$$

$$i_L(0^-) = I_0 = \left[I_L - \frac{v_c}{L} \right] \cdot \frac{1}{-}$$

State Eqn:

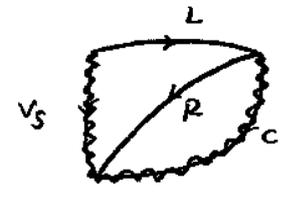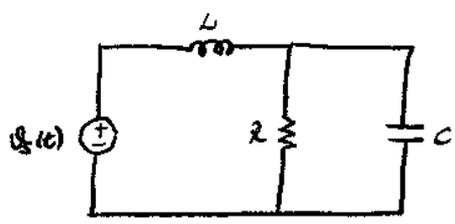

Cut-set for cap. branch: $C \dot{v}_c = -\frac{v_c}{R} + I_L$

Fund. loop for ind. branch: $L \dot{I}_L = v_s(t) - v_c$

$$\begin{bmatrix} \dot{v}_c(t) \\ \dot{I}_L(t) \end{bmatrix} = \begin{bmatrix} -1/RC & 1/C \\ -1/L & 0 \end{bmatrix} \begin{bmatrix} v_c(t) \\ I_L(t) \end{bmatrix} + \begin{bmatrix} 0 \\ 1/L \end{bmatrix} v_s(t)$$

1st order matrix diff eqn = 2nd order scalar diff eqn

Take another derivative of $v_c(t)$ equation:

$$\ddot{v}_c(t) = -\frac{1}{RC} \dot{v}_c(t) + \frac{1}{C} \dot{I}_L(t)$$

$$D^2 v_c(t) = -\frac{1}{RC} D v_c - \frac{1}{LC} v_c + \frac{1}{LC} v_s(t)$$

$$\left(D^2 + \frac{1}{RC} D + \frac{1}{LC} \right) v_c(t) = \frac{1}{LC} v_s(t) \rightarrow \text{same eqn. with the one gotten by node analysis}$$

Using state eqn., initial conditions are already given!
No need for ot analysis.

Solution of 2nd order scalar Diff. eqn

$$R = 1/3; C = 1; L = 1/2$$

$$(D^2 + 3D + 2) v_c(t) = 0$$

$$v_c(0) = v_0$$

$$\dot{v}_c(0) = I_0 - 3v_0$$

$$\lambda_{1,2} = \{-1, -2\} \rightarrow \text{modes of the system}$$

$$v_c(t) = \alpha \cdot e^{-t} + \beta e^{-2t}$$

zero-input response:
superposition of 2 modes

a mode of the circuit

2nd mode of the circuit.

How do you excite only 1 mode?

$$V_c(0) = V_0$$

$$I_c(0) = I_0 - 3V_0$$

$$V_c(t) \Big|_{t=0} = \alpha e^{-t} + \beta e^{-2t} \Big|_{t=0} = \alpha + \beta = V_0$$

$$I_c(t) \Big|_{t=0} = -\alpha e^{-t} - 2\beta e^{-2t} \Big|_{t=0} = -\alpha - 2\beta = I_0 - 3V_0$$

Two single modes $\alpha \neq 0, \beta = 0 \rightarrow V_0 = \alpha$

$$I_0 - 3V_0 = -\alpha \rightarrow I_0 = 2\alpha$$

$$V_0 = 1V$$

$$I_0 = 2A$$

$$V_c(t) = e^{-t} (\alpha = 1, \beta = 0)$$

$$\alpha = 0, \beta \neq 0 \quad \left. \begin{array}{l} V_0 = \beta \\ I_0 = \beta \end{array} \right\} V_c(t) = \beta \cdot e^{-2t}$$

Natural frequencies: Roots of characteristic equation (λ_1, λ_2)

Natural response: When we have zero input response \rightarrow natural response

Mode: Individual components of natural response

Solution by State Eqn

$$\begin{bmatrix} \dot{V}_c(t) \\ \dot{I}_L(t) \end{bmatrix} = \begin{bmatrix} -3 & 1 \\ -2 & 0 \end{bmatrix} \begin{bmatrix} V_c(t) \\ I_L(t) \end{bmatrix} \quad \begin{array}{l} V_c(0) = V_0 \\ I_L(0) = I_0 \end{array}$$

$$\dot{\underline{x}}(t) = \underline{A} \cdot \underline{x}(t) \quad ; \quad \underline{x}(0) = \underline{x}_0$$

$$\text{Let } \underline{x}(t) = \begin{bmatrix} c_1 \\ c_2 \end{bmatrix} e^{\lambda t}$$

$$\lambda \begin{bmatrix} c_1 \\ c_2 \end{bmatrix} e^{\lambda t} = \underline{A} \begin{bmatrix} c_1 \\ c_2 \end{bmatrix} e^{\lambda t}$$

$$(\lambda I - A) \begin{bmatrix} c_1 \\ c_2 \end{bmatrix} = \begin{bmatrix} 0 \\ 0 \end{bmatrix} \quad \begin{bmatrix} c_1 \\ c_2 \end{bmatrix} \neq \begin{bmatrix} 0 \\ 0 \end{bmatrix} \rightarrow \det(\lambda I - A) = 0$$

$\det(\lambda I - A)$ is called characteristic polynomial

roots of $|\lambda I - A| = 0$ are the eigenvalues of \underline{A} matrix.

$$|\lambda I - A| = \begin{vmatrix} \lambda+3 & -1 \\ 2 & \lambda \end{vmatrix} = \lambda(\lambda+3)+2 = \lambda^2 + 3\lambda + 2 \rightarrow \text{charac eqn.}$$

Then natural frequencies are the roots of

$$\lambda^2 + 3\lambda + 2 = 0 \quad \lambda = \{-1, -2\}$$

$$\underline{x}(t) = \left\{ \begin{bmatrix} c_1 \\ c_2 \end{bmatrix} e^{-t}, \begin{bmatrix} d_1 \\ d_2 \end{bmatrix} e^{-2t} \right\}$$

$$\underline{x}(t) = \underline{c} \cdot e^{-t} + \underline{d} \cdot e^{-2t}$$

$$\dot{\underline{x}}(t) = \underline{A} \cdot \underline{x}(t)$$

$$\dot{\underline{x}}(t) = \lambda_1 \cdot e^{\lambda_1 t} \cdot \underline{c} + \lambda_2 \cdot e^{\lambda_2 t} \cdot \underline{d} = \underline{A} (e^{\lambda_1 t} \underline{c} + e^{\lambda_2 t} \underline{d})$$

To excite $e^{\lambda_1 t}$ mode, $\underline{d} = 0$.

$$\hookrightarrow \underline{c} \cdot \lambda_1 \cdot e^{\lambda_1 t} = \underline{A} \cdot \underline{c} \cdot e^{\lambda_1 t}$$

$$\underline{A} \cdot \underline{c} = \lambda_1 \cdot \underline{c}$$

To excite a single mode or mode with natural frequency, λ_1

$\underline{v}_c(0^-)$, $\underline{I}_L(0^-)$ should be the eigenvector of \underline{A} corresponding

to λ_1 .

\underline{A} matrix of state eqn. is fundamental for analysis; since its eigenvalues are the natural frequencies, the eigenvectors of \underline{A} are the required initial conditions to excite a mode.

To excite $\lambda_1 = -1$ natural freq:

$$\begin{bmatrix} -3 & 1 \\ -2 & 0 \end{bmatrix} \underline{e}_1 = \lambda_1 \cdot \underline{e}_1$$

$$(\lambda_1 \underline{I} - \underline{A}) \underline{e}_1 = 0$$

$$\begin{bmatrix} \lambda+3 & -1 \\ 2 & \lambda \end{bmatrix} \begin{bmatrix} \alpha \\ \beta \end{bmatrix} = 0$$

$$\lambda = -1 \rightarrow \begin{bmatrix} 2 & -1 \\ 2 & -1 \end{bmatrix} \begin{bmatrix} \alpha \\ \beta \end{bmatrix} = 0$$

$$\begin{bmatrix} \alpha \\ \beta \end{bmatrix} = \begin{bmatrix} 1 \\ 2 \end{bmatrix} k$$


$$\begin{bmatrix} \underline{v}_c(0^-) \\ \underline{I}_L(0^-) \end{bmatrix} = \begin{bmatrix} 1 \\ 2 \end{bmatrix} k \rightarrow \text{excites } e^{-t} \text{ mode.}$$

$$\lambda = -2$$

$$\begin{bmatrix} 1 & -1 \\ 2 & -2 \end{bmatrix} \begin{bmatrix} x \\ y \end{bmatrix} = \begin{bmatrix} 0 \\ 0 \end{bmatrix}$$

$$\text{eigen vector} = \left\{ \begin{bmatrix} 1 \\ 1 \end{bmatrix} \right\}$$
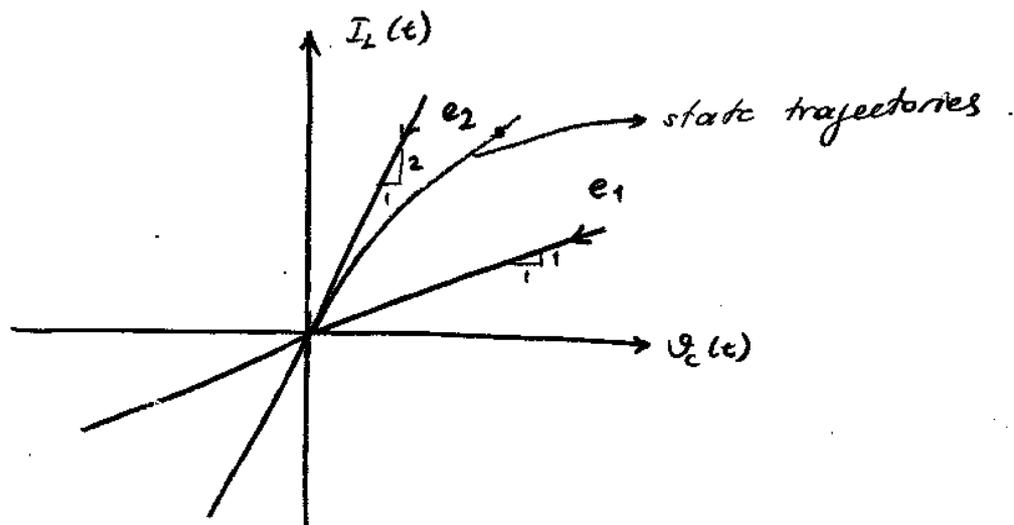
$$\begin{bmatrix} I_1(0^-) \\ I_2(0^-) \end{bmatrix} = \begin{bmatrix} 1 \\ 1 \end{bmatrix} k \rightarrow \text{excites } e^{-2t} \text{ mode.}$$




On Complex Exponential Function

$$f(x) = e^x = \sum_{k=0}^{\infty} \frac{x^k}{k!} \quad x \in \mathbb{R}$$

$z \in \mathbb{C} \rightarrow$ complex field

$$z = z_r + j \cdot z_i, \quad z_r, z_i \in \mathbb{R}, \quad j = \sqrt{-1}$$
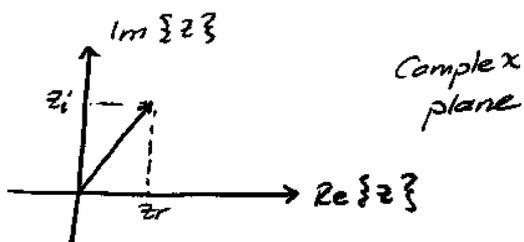
$$\underline{z} = \begin{bmatrix} z_r \\ z_i \end{bmatrix}$$




$$f(z) = e^z = \sum_{k=0}^{\infty} \frac{z^k}{k!}$$

$f(z)$: z : purely real and positive ($z=2$)
negative ($z=-2$)


imaginary ($z=2j$)

complex valued ($z=1+2j$)

1) Purely real, positive valued

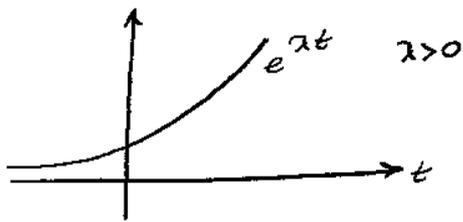

2) Purely real, negative valued

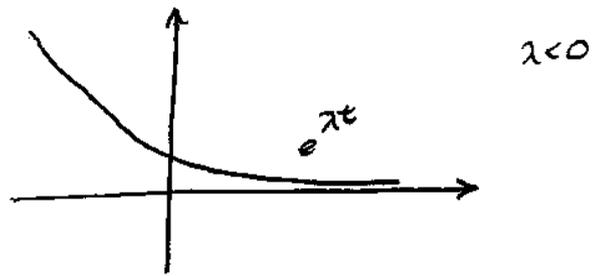

3) Purely imaginary

$$f(t) = e^{j\omega t} \quad \omega \in \mathbb{R}, t \in \mathbb{R}$$

$$e^{j\phi} = \sum_{k=0}^{\infty} \frac{(j\phi)^k}{k!} = \sum_{n=0}^{\infty} \frac{(j\phi)^{2n}}{2n!} + \sum_{n=0}^{\infty} \frac{(j\phi)^{2n+1}}{(2n+1)!}$$

$$= \sum_{n=0}^{\infty} \frac{(-1)^n \phi^{2n}}{2n!} + j \sum_{n=0}^{\infty} \frac{(-1)^n \phi^{2n+1}}{(2n+1)!}$$

$$= \cos \phi + j \cdot \sin \phi$$

$$e^{j\phi} = \cos \phi + j \cdot \sin \phi \quad \text{Euler's formula}$$

$$e^{jA} \cdot e^{jB} = e^{j(A+B)}$$


$$(\cos A + j \sin A)(\cos B + j \sin B) = \cos(A+B) + j \sin(A+B)$$

$$\cos(A+B) = \cos A \cdot \cos B - \sin A \cdot \sin B$$


$$\sin(A+B) = \sin A \cdot \cos B + \cos A \cdot \sin B$$

HW $\sum_{k=0}^{N-1} \cos(\omega k) \Rightarrow \cos(\omega N)$

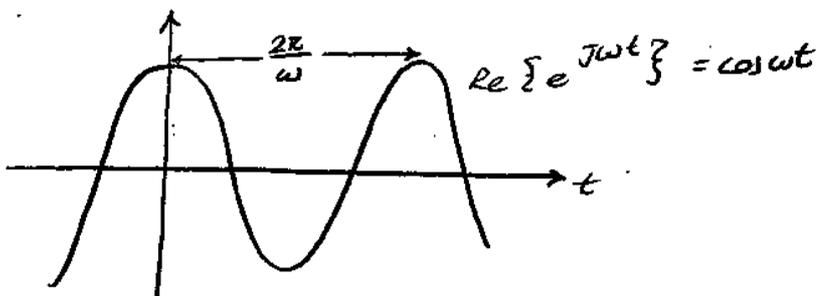Hint: $\cos(\omega k) = \text{Re} \{ e^{j\omega k} \}$



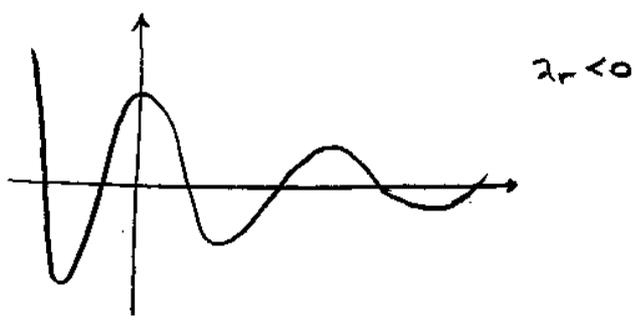4) $\lambda \in \mathbb{C}$
 $f(t) = e^{\lambda t} = e^{\lambda_r \cdot t} \cdot e^{-j \lambda_i t}$



Stability of LTI systems


stability refers to keeping current and voltage of each branch bounded (finite) through circuit components.

- 1) zero-input
- 2) stability concept with inputs


Given any initial condition, if each state goes to zero as $t \rightarrow \infty$, then such a system is called asymptotically stable

Note: There are more than one stability definition, such as, exponentially stable, asymptotically stable, Lyapunov stability etc.

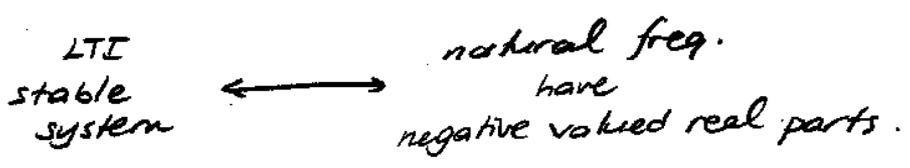For LTI systems, all stability definitions converge to the same condition.



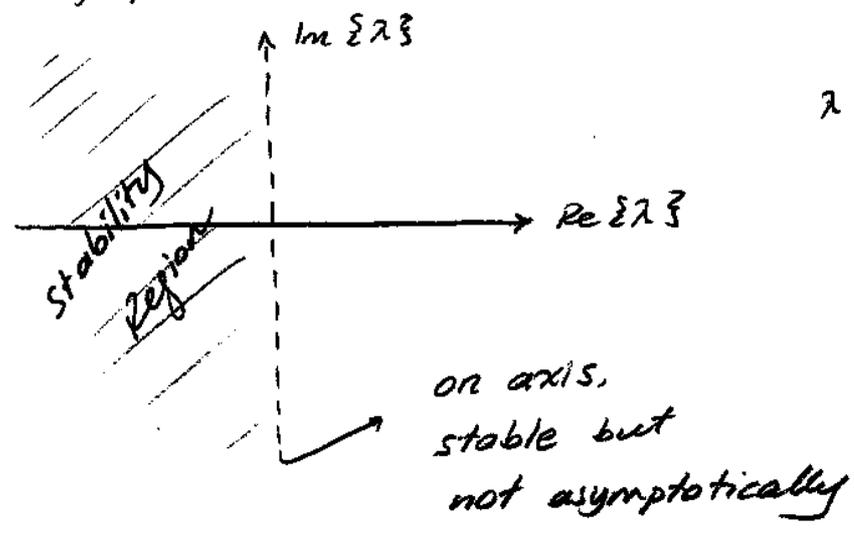natural freq: roots of char. eq. (eigenvalues of A)



Solution of Dynamic System with Inputs

Particular Solution of Diff. Eqn.

$$(D^2 + 3D + 2) x(t) = f(t) \quad \hookrightarrow \text{forcing term (external input)}$$

$$f(t) = e^{st} \quad \left(\begin{array}{l} \text{we limit our interest to exponential inputs.} \\ \text{later we will use more powerful techniques} \\ \text{covering more function types} \end{array} \right)$$

Ex

$$(D^2 + 3D + 2) x(t) = e^{st}$$

$$x_p = A e^{st}$$

$$A(s^2 + 3s + 2) e^{st} = e^{st}$$

$$A = \frac{1}{s^2 + 3s + 2}, \text{ provided that } s^2 + 3s + 2 \neq 0 \text{ (} s \neq \text{natural freq.)}$$


Important Remark:

For stable systems, as $t \rightarrow \infty$, the zero-input solution goes to zero and we are left with zero-state solution. Then if the input is in the form of e^{st} , for LTI systems, the particular solution is also a complex exponential with the same exponent.

State eqns are favourite tool for analysis.

MNA, NA, MA require more number of eqns and initial conditions of the equations have to be found and integro differential

8.3.2010

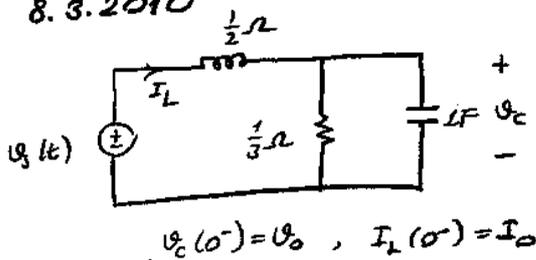

$$(D^2 + 3D + 2) v_c(t) = 2 v_s(t)$$

$$v_c^{\text{complete}}(t) = v_c^h(t) + v_c^p(t)$$

↓

system determined, natural freq. → input dependent

Homogeneous: $(D^2 + 3D + 2) v_c(t) = 0 \rightarrow \lambda_{1,2} = \{-1, -2\}$
natural freq.

Particular solution :

Let $U_s(t) = e^{-5t} \rightarrow$ case ①

Assume $U_p(t) = A \cdot e^{-5t}$

$(s^2 + 3s + 2) A e^{st} = 2 e^{st} \rightarrow A = \frac{2}{s^2 + 3s + 2}, s \notin \{-1, -2\}$

For $U_s(t) = e^{-5t}, A = \frac{2}{12} = \frac{1}{6}$

$U_{complete}(t) = \underbrace{c_1 \cdot e^{-t} + c_2 \cdot e^{-2t}}_{\text{homogeneous (natural resp.)}} + \underbrace{\frac{1}{6} \cdot e^{-5t}}_{\text{particular}}$

steady state: part of complete response as $t \rightarrow \infty$
transient: the remaining part in the complete response apart from steady state.

No steady state $\rightarrow U^{ss}(t) = 0!$

Case ② : $U_s(t) = 1V = e^{st} \downarrow_{s=0}$

$U_c^p(t) = A$

$(D^2 + 3D + 2) U_c^p(t) = 2 \quad A = 1 \rightarrow U_c^p(t) = 1V$

$U^{ss}(t) = 1 \rightarrow$ steady state solution.

Method: For exponential inputs, to find particular solution, we make the guess of $A \cdot e^{st}$ then find A.

Case ③ : $U_s(t) = \cos(5t)$

$(D^2 + 3D + 2) U_c^p(t) = 2 \cdot \cos(5t)$

$U_c^p(t) = A \cdot \cos(5t) + B \sin(5t)$

$U_s(t) = \cos 5t = \text{Re} \{ e^{j5t} \}$

$(D^2 + 3D + 2) U_c^p(t) = 2 \text{Re} \{ e^{j5t} \}$

$U_c^p(t) = \text{Re} \{ A_c \cdot e^{j5t} \}, A_c \in \mathbb{C}$

$\frac{d}{dt} U_c^p(t) = \text{Re} \{ \frac{d}{dt} A_c e^{j5t} \} = \text{Re} \{ j5 \cdot A_c \cdot e^{j5t} \}$

$\frac{d^2}{dt^2} U_c^p(t) = \text{Re} \{ -25 \cdot A_c \cdot e^{j5t} \}$

Do the substitution

$$D^2 \vartheta_c P(t) + 3D \cdot \vartheta_c P(t) + 2 \vartheta_c P(t) = \operatorname{Re} \{ 2e^{j5t} \}$$

$$\operatorname{Re} \{ -25 A_c e^{j5t} \} + \operatorname{Re} \{ j15 A_c \cdot e^{j5t} \} + \operatorname{Re} \{ 2 A_c e^{j5t} \} = \operatorname{Re} \{ 2e^{j5t} \}$$

$$\operatorname{Re} \{ A_c (-23 + j15) e^{j5t} \} = \operatorname{Re} \{ 2 e^{j5t} \}$$

$$A_c = \frac{2}{-23 + j15} = \frac{2(-23 - j15)}{23^2 + 15^2}$$

$$\vartheta_c P(t) = \operatorname{Re} \left\{ \frac{-46 - j15}{23^2 + 15^2} e^{j5t} \right\}$$

$$= -\frac{2}{23^2 + 15^2} \cdot \operatorname{Re} \{ (23 + j15) (\cos 5t + j \sin 5t) \}$$

$$= -\frac{2}{23^2 + 15^2} [23 \cos(5t) - 15 \sin(5t)]$$

$$\cos(5t) = \operatorname{Re} \{ e^{j5t} \}$$

$$\sin(5t) = \cos(5t - 90^\circ)$$

Exponential functions are the eigenfunction of an LTI dynamic system.

Stability

$$[D^2 - (\lambda_1 + \lambda_2) D + \lambda_1 \lambda_2] \vartheta_c(t) = \vartheta_s(t)$$

λ_1, λ_2 : natural freq.

1) Asymptotically stable ($\operatorname{Re} \{ \lambda_1 \} < 0$ & $\operatorname{Re} \{ \lambda_2 \} < 0$)

$$\vartheta_s(t) = e^{st}$$

$$s = 0 \text{ (DC)}$$

↓

$$\vartheta_c(t) = \text{natural resp.}$$

+

A

BIBO stability

seems to be OK.

$$s = 1$$

$$\vartheta_c(t) = \text{nat. resp.}$$

+

$$A \cdot e^t$$

$$s = j2 \text{ (AC)}$$

$$\vartheta_c(t) = \text{nat. resp.}$$

+

$$A_c \cdot e^{j2t}$$

BIBO is OK


for real (imaginary) part of the solution

BIBO stability:


All bounded inputs \rightarrow Bounded outputs

Bounded func: $|x(t)| < \mu, \exists M$

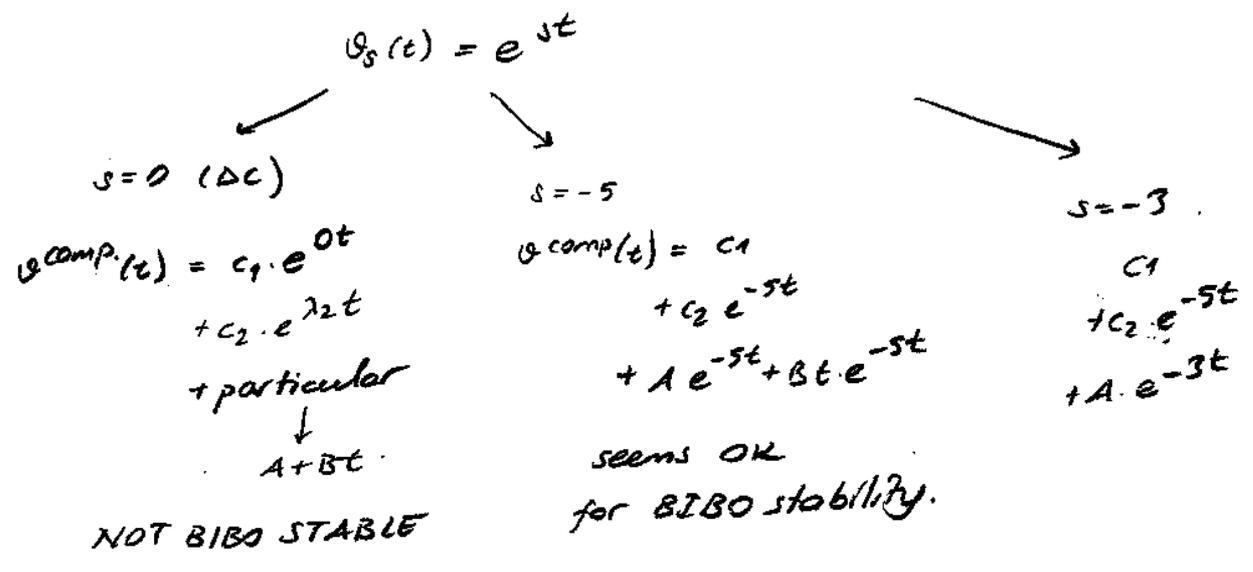② stable $\rightarrow \operatorname{Re}\{\lambda_1\} \leq 0, \operatorname{Re}\{\lambda_2\} \leq 0$



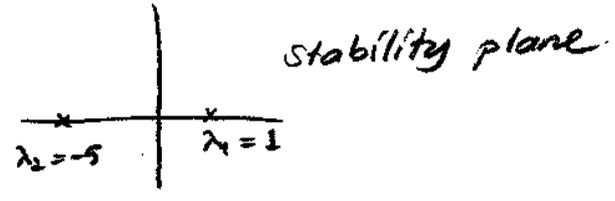③ Unstable $\rightarrow \operatorname{Re}\{\lambda_1\} > 0$ or $\operatorname{Re}\{\lambda_2\} > 0$




Ex/

$$\begin{bmatrix} D+1 & D+2 & 0 \\ 3 & D-1 & 2 \\ 1 & 5 & D \end{bmatrix} \begin{bmatrix} x_1(t) \\ x_2(t) \\ x_3(t) \end{bmatrix} = \begin{bmatrix} 2D \\ L \\ 0 \end{bmatrix} v_3(t)$$

$$\begin{vmatrix} s+1 & s+2 & 0 \\ 3 & s-1 & 2 \\ 1 & 5 & s \end{vmatrix} \rightarrow \text{gives char. eqn.}$$

PHASORS

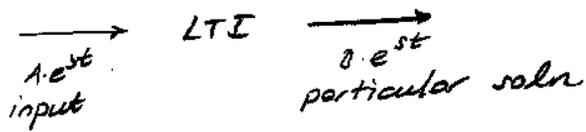

We know that exponential family of signals (Ae^{st}) at the input of a N th order dynamic system produces an output (particular soln, soln in the forcing term, i.e. input) in the form $B \cdot e^{st}$. So exponential family, the output is determined by finding B .

Then the coefficient of the exponent is called the phasor. In general A, B are complex numbers.

Specific for A.C. inputs, that is $f(t) = M \cdot \cos(\omega t + \phi)$; we have the following phasor definition

$$\begin{aligned} f(t) = M \cdot \cos(\omega t + \phi) &= \text{Re} \{ M \cdot e^{j(\omega t + \phi)} \} \quad [M, \phi, \omega \in \mathbb{R}] \\ &= \text{Re} \{ \underbrace{M \cdot e^{j\phi}}_A \cdot e^{j\omega t} \} \\ &= \text{Re} \{ A \cdot e^{j\omega t} \} \\ &\quad \left(\begin{array}{l} \text{complex valued;} \\ \text{phasor, coefficient of } e^{j\omega t} \end{array} \right) \end{aligned}$$

Then,

$$\begin{array}{ccc} * \quad 2 \cos\left(\omega t + \frac{\pi}{6}\right) & \xrightarrow{\text{phasor}} & 2 e^{j\frac{\pi}{6}} \\ \left[= \text{Re} \{ 2 e^{j\frac{\pi}{6}} \cdot e^{j\omega t} \} \right] & \xleftarrow{\text{form}} & (2 \angle 30^\circ) \end{array}$$

$$\begin{array}{ccc} * \quad (1 \angle 45^\circ) & \xrightarrow{\text{time}} & \text{Re} \{ \underbrace{1 \angle 45^\circ}_{e^{j\pi/4}} e^{j2t} \} \\ \omega = 2 & & = \cos\left(2t + \frac{\pi}{4}\right) \end{array}$$

$$\text{Ex } \underbrace{\cos(4t+30^\circ)}_A + \underbrace{\cos(4t+60^\circ)}_B = 2 \cos\left(\frac{A+B}{2}\right) \cos\left(\frac{A-B}{2}\right)$$

$$= \text{Re} \left\{ e^{J30^\circ} e^{J4t} \right\} + \text{Re} \left\{ e^{J60^\circ} e^{J4t} \right\}$$

$$= \text{Re} \left\{ e^{J4t} (e^{J30^\circ} + e^{J60^\circ}) \right\}$$

$$= \text{Re} \left\{ e^{J4t} \left(\begin{bmatrix} \cos 30^\circ \\ J \sin 30^\circ \end{bmatrix} + \begin{bmatrix} \cos 60^\circ \\ J \sin 60^\circ \end{bmatrix} \right) \right\}$$

$$= \text{Re} \left\{ e^{J4t} \left(\frac{\sqrt{3}+1}{2} + J \frac{\sqrt{3}+1}{2} \right) \right\} = \text{Re} \left\{ e^{J4t} \underbrace{(1+J)}_{\sqrt{2} \cdot e^{J\frac{\pi}{4}}} \left(\frac{\sqrt{3}+1}{2} \right) \right\}$$

polar coord. representation

$$= \text{Re} \left\{ \left(\frac{1+\sqrt{3}}{2} \right) \cdot \sqrt{2} \cdot e^{J(4t + \frac{\pi}{4})} \right\} = \frac{1+\sqrt{3}}{\sqrt{2}} \cdot \cos\left(4t + \frac{\pi}{4}\right)$$

In the previous example, we have repeatedly used $\text{Re} \{ e^{J4t} (\dots) \}$ at every step. We do not write this at every step, but prefer to write the phasor instead.

That is,


$$\cos(4t+30^\circ) + \cos(4t+60^\circ) \xrightarrow{\text{phasor}} \overset{\omega=4}{1 \angle 30^\circ} + 1 \angle 60^\circ$$

$$= \left(\frac{\sqrt{3}+J}{2} \right) + \left(\frac{1+J\sqrt{3}}{2} \right) \leftarrow \text{resulting phasor}$$

$$= \frac{1+\sqrt{3}}{\sqrt{2}} e^{J\pi/4}$$

$$= \frac{1+\sqrt{3}}{2} \cos(4t+45^\circ) \quad \text{time domain}$$
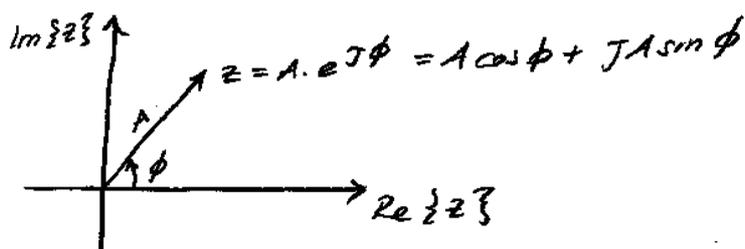
$$A \angle \phi = A \cdot e^{J\phi} = A(\cos \phi + J \sin \phi)$$



Note:

NA \rightarrow some of natural frequencies at zero can be missing due to D, D^{-1} cancellation



MNA \rightarrow used to find natural freq. (has only Δ 's)

State Eqn \rightarrow used for natural freq. (has only Δ 's)

natural freq. can be complex number.

if λ is complex valued, its conjugate is also a natural freq.

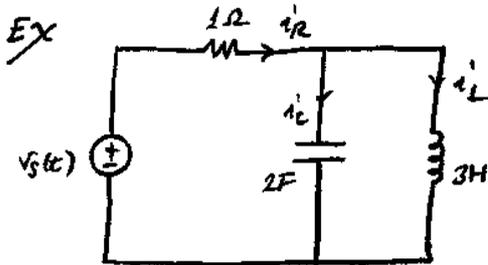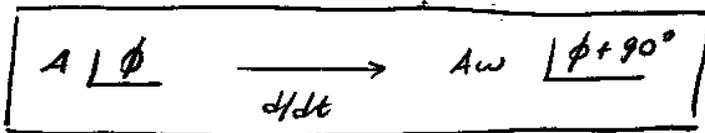Ex $\frac{d}{dt} A \cos(\omega t + \phi) = -A\omega \sin(\omega t + \phi)$
 $= A\omega \cos(\omega t + \phi + 90^\circ)$




$$i_L(t) = \cos(t)$$

$$v_L(t) = v_C(t) = -3\sin(t)$$

$$i_C(t) = -6\cos(t)$$

$$i_R = i_C + i_L = -5\cos(t)$$
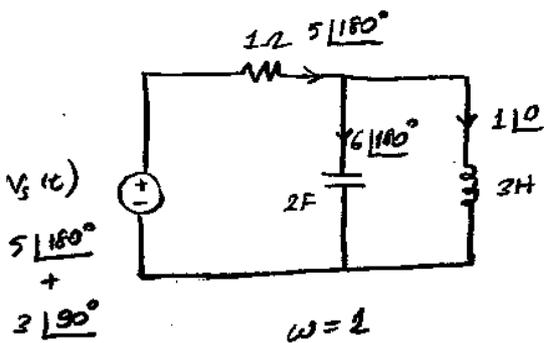
$$v_s(t) = R \cdot i_R + v_L(t) = -5\cos(t) - 3\sin(t)$$



$$v_s(t) = 5 \angle 180^\circ + 3 \angle 90^\circ$$

$$= -5 + j3$$

$$= \sqrt{25+9} e^{j(\tan^{-1} \frac{3}{-5})}$$

$$v_s(t) = \sqrt{34} \cos\left(t - \tan^{-1} \frac{3}{5}\right)$$


$$= \sqrt{34} \cdot e^{\left\{ e^{j(\omega t - \tan^{-1} \frac{3}{5})} \right\}}$$

Phasors allow us

- 1) Add cosines (with the same frequency)
- 2) Differentiate cosines

So adding differentiated and scaled many cosine terms is possible with phasors.


Ex

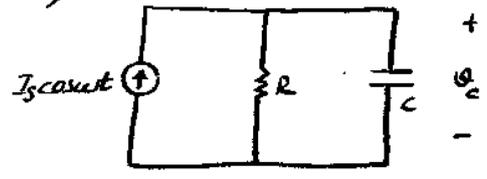

$$\left(D + \frac{1}{RC}\right) v_c(t) = \frac{i_s(t)}{C} = \frac{I_s \cos \omega t}{C}$$

$$v_c(0^-) = v_0$$
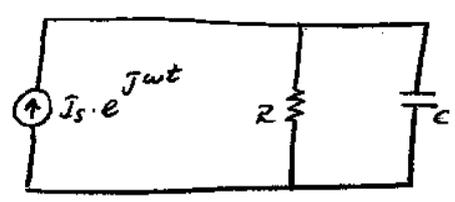
$$\textcircled{i} v_c^{\text{complete}}(t) = q \cdot e^{-t/RC} + A \cos \omega t + B \sin \omega t$$



$$\left(D + \frac{1}{RC}\right) v_c(t) = \frac{I_s \cdot e^{j\omega t}}{C}$$

$$\textcircled{ii} v_c^{\text{complete}}(t) = d_1 \cdot e^{-t/RC} + D \cdot e^{j\omega t}$$

↘ can be complex number

$$\textcircled{iii} v_c^{\text{complete}}(t) = \text{Re} \left\{ \textcircled{ii} v_c^{\text{complete}}(t) \right\}$$


$I_s \cdot e^{j\omega t} \rightarrow$ complex excitation

$$\textcircled{i} v_c^{\text{complete}}(t) = d_1 \cdot e^{-t/RC} + \frac{I_s \cdot R}{1 + (\omega RC)^2} \cos \omega t + \frac{I_s \omega R^2 C}{1 + (\omega RC)^2} \sin \omega t$$

$$d_1 + \frac{I_s \cdot R}{1 + (\omega RC)^2} = v_0 \leftarrow d_1 \text{ is found.}$$

If we are only interested in particular solution for A.C. excitation; we have some simplifications.

Phasor Circuit Analysis

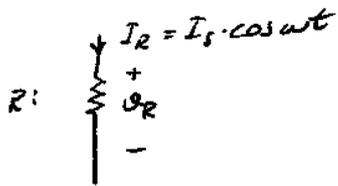

Time-domain




$$I_R(t) = I_s \cdot \cos \omega t$$

$$V_R(t) = R \cdot I_s \cdot \cos \omega t$$

Phasor

$$i_R = I_s \angle 0$$

$$V_R = R I_s \angle 0$$

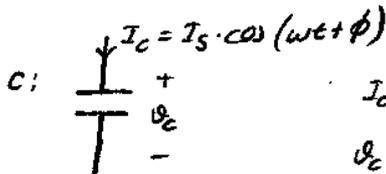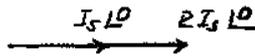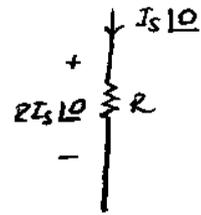



$$I_C(t) = I_s \cdot \cos(\omega t + \phi)$$

$$V_C(t) = \frac{I_s}{\omega C} \sin(\omega t + \phi)$$


$$I_C = I_s \angle \phi$$

$$V_C = \frac{I_s}{\omega C} \angle \phi - 90^\circ$$

$$= \frac{1}{\omega C} I_s \angle \phi$$

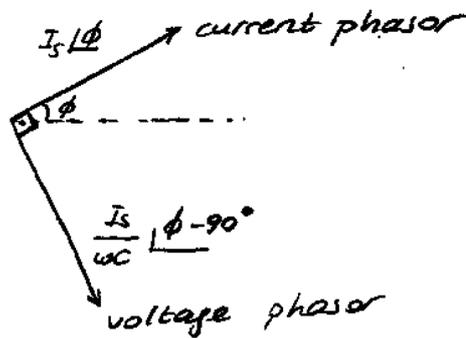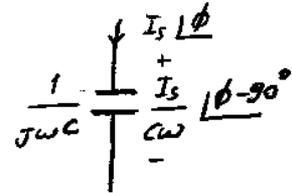

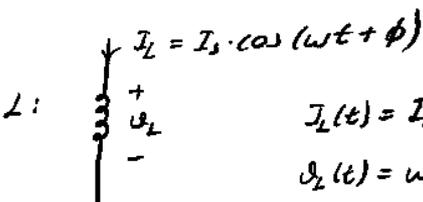Capacitor voltage (phasor) lags the current (phasor) by 90° .
 capacitor current leads the voltage by 90° .





$$I_L(t) = I_s \cos(\omega t + \phi)$$


$$V_L(t) = \omega L I_s \cdot \cos(\omega t + \phi + \frac{\pi}{2})$$

$$I_L = I_s \angle \phi$$

$$V_L = \omega L I_s \angle \phi + 90^\circ$$

$$V_L = j\omega L I_s \angle \phi$$

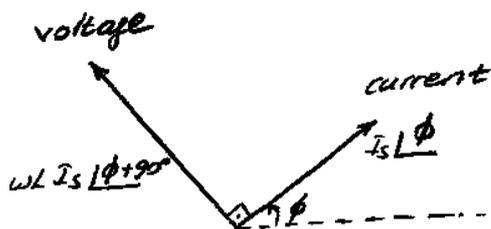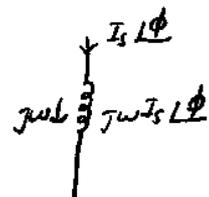


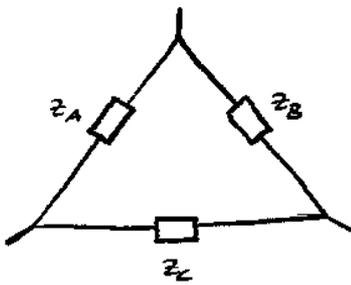

$$z_1 = \frac{z_B z_C}{z_A + z_B + z_C}$$

$$z_2 = \frac{z_A z_C}{z_A + z_B + z_C}$$
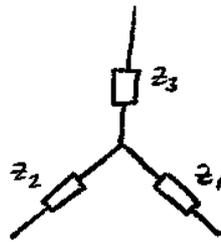
$$z_3 = \frac{z_A z_B}{z_A + z_B + z_C}$$



$$z_A = \frac{z_1 z_2 + z_1 z_3 + z_2 z_3}{z_1}$$

$$z_B = \frac{z_1 z_2 + z_1 z_3 + z_2 z_3}{z_2}$$

$$z_C = \frac{z_1 z_2 + z_1 z_3 + z_2 z_3}{z_3}$$


General AC Circuit Analysis

AC steady state analysis (particular soln. due to AC excitation)

- 1) Node
- 2) Mesh
- 3) Thevenin - Norton
- 4) other simplification methods


} AC analysis.

ex Node Analysis

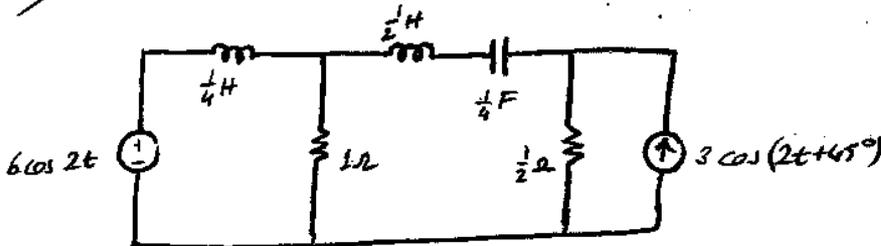

Find AC steady-state branch current & voltages.

Phasor Domain

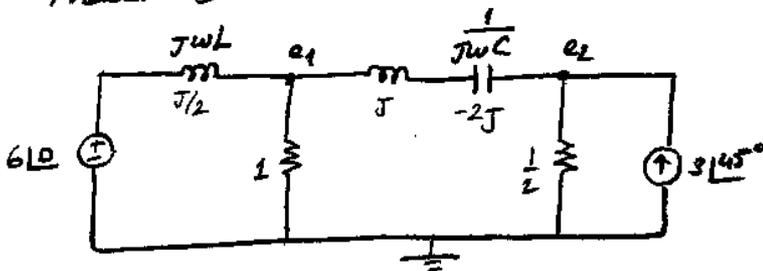

$$\omega = 2$$


$$\text{KCL at } e_1: \frac{e_1}{1} + \frac{e_1 - 6 \angle 0}{j/2} + \frac{e_1 - e_2}{-j} = 0$$

$$\text{KCL at } e_2: \frac{e_2}{1/2} + \frac{e_2 - e_1}{-j} - 3 \angle 45^\circ = 0$$

$$\begin{bmatrix} 1-j & -j \\ -j & 2+j \end{bmatrix} \begin{bmatrix} e_1 \\ e_2 \end{bmatrix} = \begin{bmatrix} -12j \\ 3 \angle 45^\circ \end{bmatrix} \rightarrow \begin{bmatrix} e_1 \\ e_2 \end{bmatrix} = \begin{bmatrix} ? \\ 3.63 \angle 14^\circ \end{bmatrix}$$


$$e_2(t) = 3.63 \cos(2t + 14^\circ)$$

Ex

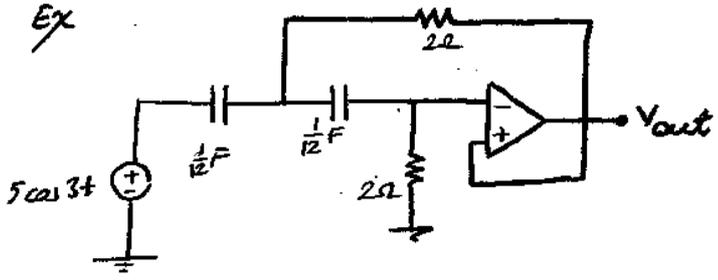

Assume op-amp is in linear region. Find V_{out} .

Phasor domain

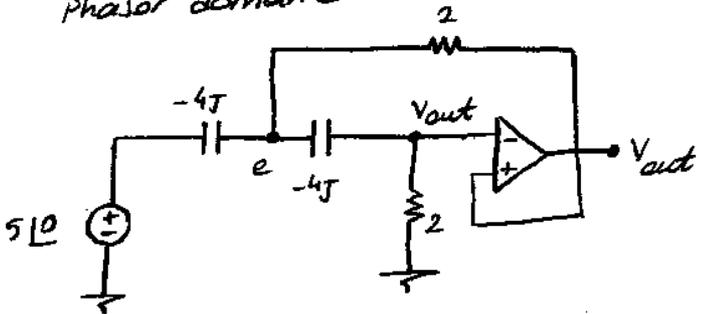

$$\omega = 3$$

KCL at e : $\frac{e-5}{-4j} + \frac{e-V_{out}}{2} + \frac{e-V_{out}}{-4j} = 0 \dots \textcircled{1}$



KCL at V_- : $e = V_{out} + \frac{V_{out}}{2}(-4j) = V_{out}(1-2j)$

$\textcircled{1} \rightarrow e(2+2j) + V_{out}(-2-j) = 5j$

$V_{out}[(1-2j)(2+2j) - 2-j] = 5j$

$V_{out} = \frac{5j}{4-3j} = \frac{5j}{5 \angle -37^\circ} = 1 \angle 127^\circ \rightarrow V_{out} = \cos(3t + 127^\circ) \text{ V}$

Ex Mesh Analysis

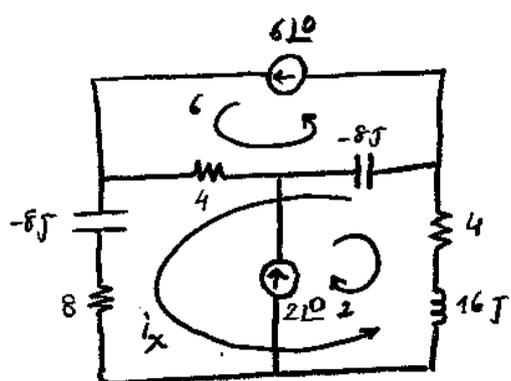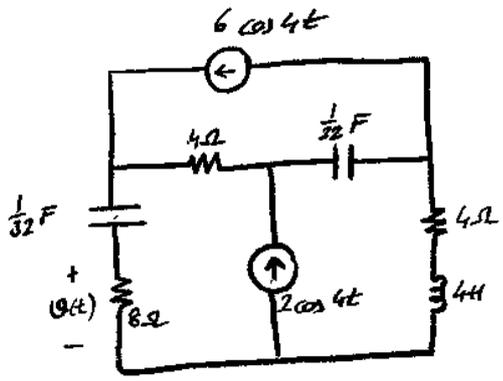

$$\omega = 4$$

KVL around i_x loop:

$$4(i_x - 6) + (8 - 8j)i_x + (4 + 16j)(i_x - 2) - 8j(i_x - 2 - 6) = 0$$


$$i_x = \frac{24 + 8(4j + 1) - 64j}{4 + 8 - 8j + 16j + 4 - 8j} = \frac{8(4 - 4j)}{16} = \frac{1}{2} 5 \angle -45^\circ$$

$$v = i_x \cdot 8 = 20 \angle -45^\circ$$

$$v(t) = 20 \cos(4t - 45^\circ) \text{ V}$$

Sources with different Frequencies (ω)

↳ angular frequency (rad/s)

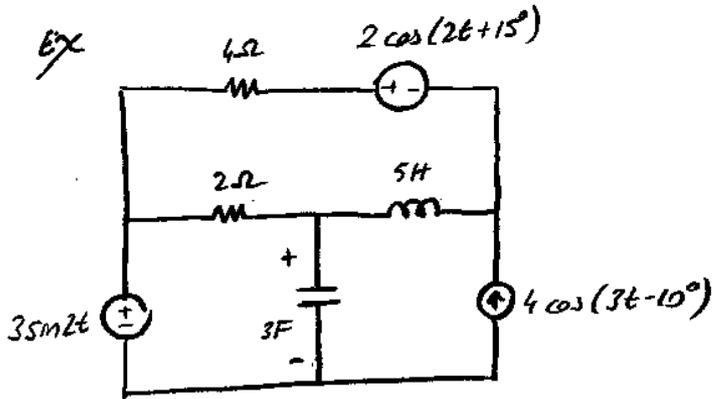


$$v_{3F}(t) = ?$$

$$\sin(t) = \cos(t - 90^\circ)$$

$$1 \angle -90^\circ$$

Superpose:

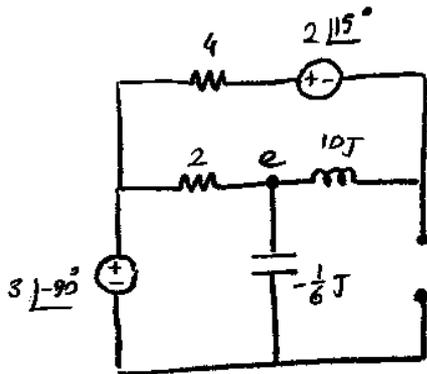


$$\omega = 2$$

$$\frac{e}{-j/6} + \frac{e - (3 \angle -90 - 2 \angle 15^\circ)}{4 + 10j} + \frac{e - 2 \angle 30}{2} = 0$$

$$e = v_{3F} \text{ (A)} \angle \theta \text{ (A)}$$
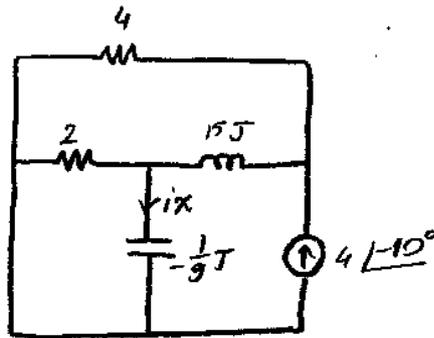
$$v_{3F} \text{ (A)}(t) = v_{3F} \text{ (A)} \cos(2t + \theta \text{ (A)})$$



$$\omega = 3$$


$$i_x = 4 \angle -10^\circ \cdot \frac{4}{4 + (15j + 2 \parallel (-j/9))} \cdot \frac{2}{2 - 9j}$$

$$v_{3F} = -\frac{j}{9} i_x = v_{3F} \text{ (B)} \angle \theta \text{ (B)}$$


$$v_{3F} \text{ (B)}(t) = v_{3F} \text{ (B)} \cos(3t + \theta \text{ (B)})$$

$$v_{3F}(t) = v_{3F} \text{ (A)}(t) + v_{3F} \text{ (B)}(t)$$

Ex

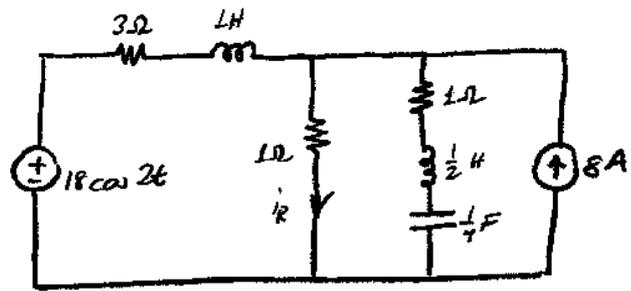


$i_e^{ss}(t) = ?$
 $\omega = \{2, 0\}$

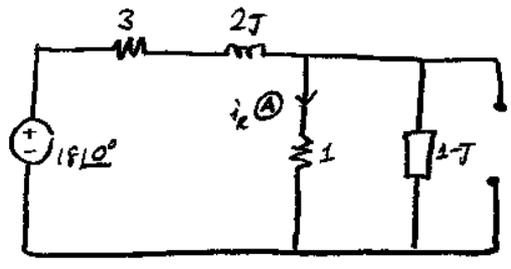

$i_R \textcircled{A} = \frac{18}{3+2j} \cdot \frac{1}{\frac{1}{1} + \frac{1}{1-j} + \frac{1}{3+2j}} = 2(1-j)$
 $= 2\sqrt{2} \angle -45^\circ$
 $i_R \textcircled{A}(t) = 2\sqrt{2} \cos(2t - 45^\circ)$

$\omega = 2$

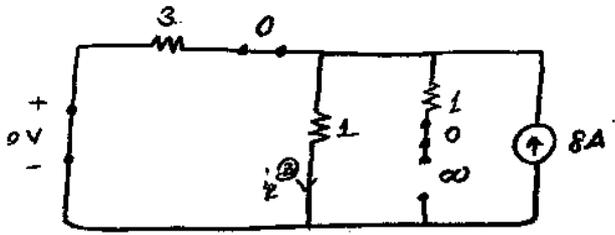


$i_R \textcircled{B} = 8 \cdot \frac{3}{3+1} = 6A$

$\omega = 0$


$\Rightarrow i_R(t) = 6 + 2\sqrt{2} \cos(2t - 45^\circ) A$

Thevenin - Norton

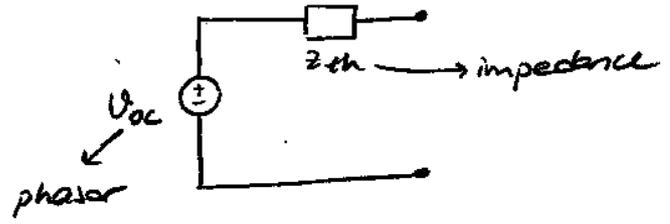
Exactly as in resistive circuits with phasor domain!



Coupled Inductor

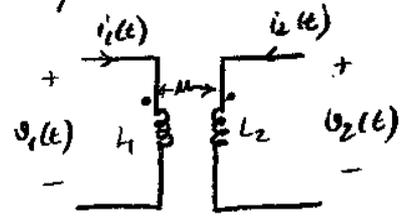


phasor

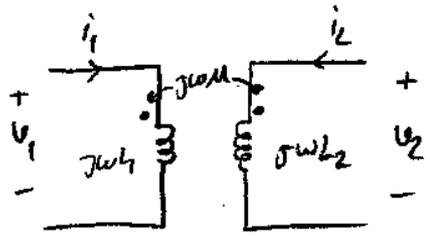

$$\begin{bmatrix} v_1(t) \\ v_2(t) \end{bmatrix} = \begin{bmatrix} L_1 & M \\ M & L_2 \end{bmatrix} \begin{bmatrix} D i_1(t) \\ D i_2(t) \end{bmatrix}$$

$$\begin{bmatrix} v_1 \\ v_2 \end{bmatrix} = \begin{bmatrix} j\omega L_1 & j\omega M \\ j\omega M & j\omega L_2 \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \end{bmatrix}$$

Ideal Transformer

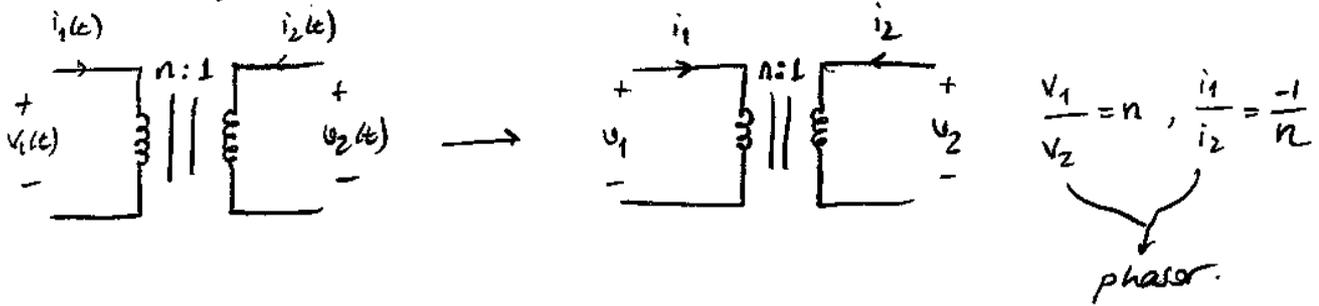

Ex (Prev. Unit)

$$(D^2 + 4) u_c(t) = \cos 2t = \operatorname{Re} \{ e^{j2t} \}$$


$$(D^2 + 4) u_c(t) = 0$$

$$\lambda^2 + 4 = 0 \rightarrow \lambda_{1,2} = \{ \pm 2j \}$$

$$u_c^{\text{comp}}(t) = c_1 e^{\lambda_1 t} + c_2 e^{\lambda_2 t} + A t \cdot e^{j2t}$$

↓
particular soln.
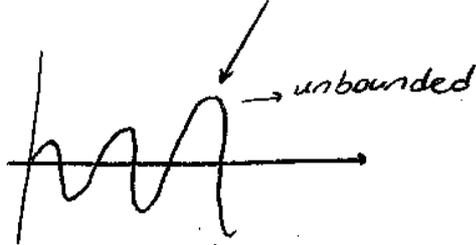
$$\cos(2t) + \dots (\dots) t \cos(2t + \phi)$$



AC Power Analysis

RMS or Effective Values

$x(t)$: periodic function $[\exists T, T \neq 0 \rightarrow x(t-T) = x(t) \forall t]$

Root mean square \Rightarrow
$$RMS = \sqrt{\frac{1}{T} \int_{t_0}^{t_0+T} [x(t)]^2 dt}$$


integrate over a full period.

$$RMS = \sqrt{\frac{1}{T} \int_0^T [x(t)]^2 dt}$$

① $x(t) = A \cdot \cos(\omega t + \phi)$


$$RMS \rightarrow \sqrt{\frac{1}{T} \int_0^T A^2 \cos^2(\omega t + \phi) dt} = \sqrt{\frac{A^2}{T} \int_0^T \frac{1 + \cos(2\omega t + 2\phi)}{2} dt} = \frac{A}{\sqrt{2}}$$

② $x(t)$: triangular (saw-tooth)

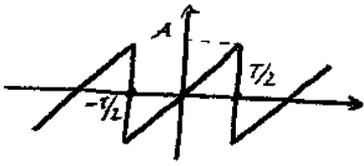


$$\begin{aligned} \text{RMS} &= \sqrt{\frac{1}{T} \int_{-T/2}^{T/2} \left(\frac{2A}{T}t\right)^2 dt} \\ &= \sqrt{\frac{2 \cdot 4A^2}{T^3} \int_0^{T/2} t^2 dt} = \boxed{\frac{A}{\sqrt{3}}} \end{aligned}$$

③ Rectangular

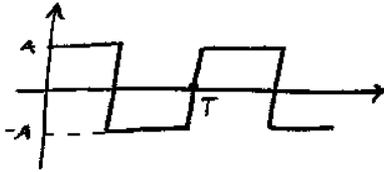

$$\text{RMS} \{x(t)\} = A \text{ (effective)}$$

Why RMS?

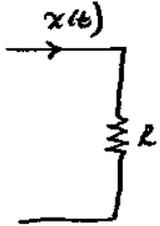


$$p(t) = R [x(t)]^2$$

$$E(\text{absorbed by } R) = \int_0^T p(t) dt = \int_0^T R [x(t)]^2 dt$$

$$= R \cdot T \cdot \frac{1}{T} \int_0^T x^2(t) dt$$

$$= 2T \cdot (x_{\text{RMS}})^2 = (R \cdot x_{\text{RMS}}^2) T \rightarrow \text{energy calculation}$$

Average Power

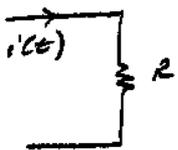


$$P_{\text{AV}} = \frac{1}{T} \int_0^T p(t) dt \text{ or } P_{\text{AV}} = \lim_{T \rightarrow \infty} \frac{1}{T} \int_0^T p(t) dt$$

$$= R \cdot \frac{1}{T} \int_0^T i^2(t) dt = \boxed{(i_{\text{RMS}})^2 \cdot R}$$

E consumed in 5 periods $\rightarrow P_{\text{AV}} \cdot 5T$

Average and Instantaneous Power

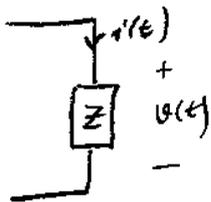

$$\left. \begin{aligned} v(t) &= U_m \cdot \cos(\omega t + \theta_v) \rightarrow v = U_m \angle \theta_v \\ i(t) &= I_m \cdot \cos(\omega t + \theta_i) \rightarrow i = I_m \angle \theta_i \end{aligned} \right\} z = \frac{U_m}{I_m} \angle \theta_v - \theta_i$$

$$p(t) = v(t) i(t) = U_m \cdot I_m \cdot \cos(\omega t + \theta_v) \cos(\omega t + \theta_i)$$

$$= \frac{U_m I_m}{2} \left[\underbrace{\cos(\theta_v - \theta_i)}_{\theta_2} + \underbrace{\cos(2\omega t + \theta_v + \theta_i)}_{2\theta_1 + \theta_2} \right]$$

$$p(t) = \frac{V_m I_m}{2} \left[\cos \theta_2 + \cos(2\omega t + 2\theta_1) \cos(\theta_2) - \sin(2\omega t + 2\theta_1) \sin(\theta_2) \right]$$

$$= \frac{V_m I_m}{2} \cos(\theta_2) \left\{ 1 + \cos(2\omega t + 2\theta_1) \right\} - \frac{V_m I_m}{2} \sin(\theta_2) \sin(2\omega t + 2\theta_1)$$

$$P_{AV} = \frac{1}{T} \int_0^T p(t) dt = \frac{V_m I_m}{2} \cos(\theta_2)$$


$$= \boxed{V_{RMS} \cdot I_{RMS} \cdot \cos(\theta_2)}$$

$$p(t) = P_{AV} \left\{ 1 + \cos(2(\omega t + \theta_1)) \right\} - Q \cdot \sin(2(\omega t + \theta_1))$$

$$Q = \frac{V_m I_m}{2} \sin(\theta_2)$$

$$p(t) = P_{AV} + P_{AV} \cdot \cos(2\omega t + 2\theta_1) - Q \sin(2\omega t + 2\theta_1)$$
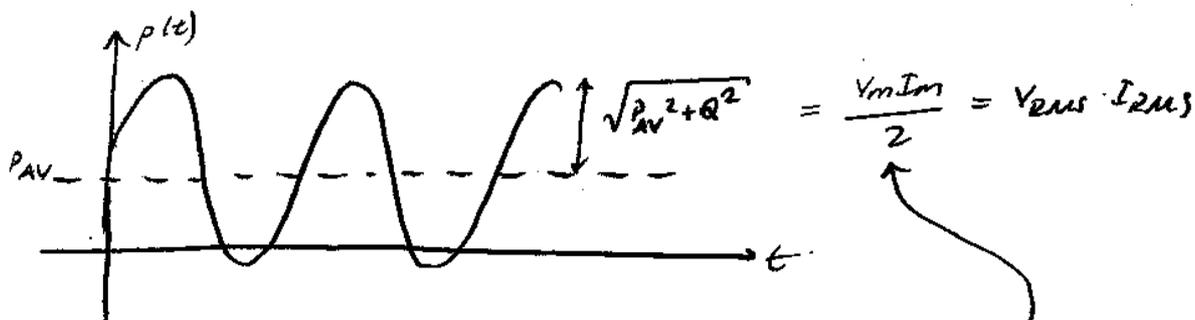
$$= P_{AV} + \sqrt{P_{AV}^2 + Q^2} \cos(2\omega t + 2\theta_1 + \tan^{-1} \frac{Q}{P_{AV}})$$




$$\sqrt{P_{AV}^2 + Q^2} = \sqrt{\left[\frac{V_m I_m}{2} \cos(\theta_2) \right]^2 + \left[\frac{V_m I_m}{2} \sin(\theta_2) \right]^2} = \frac{V_m I_m}{2}$$

$V_{RMS} \cdot I_{RMS}$: apparent power

$$A \cos \omega t + B \sin \omega t = \sqrt{A^2 + B^2} \cos(\omega t - \tan^{-1} \frac{B}{A})$$

Special Cases

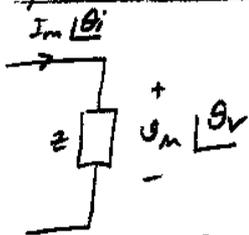

$$1) z = R \rightarrow \theta_2 = 0$$

$$P_{AV} = \frac{V_m I_m}{2} = V_{RMS} I_{RMS}$$

$$p(t) = P_{AV} \left\{ 1 + \cos(2\omega t + 2\theta_1) \right\}$$

$$z = \frac{V_m}{I_m} \angle \theta_2 - \theta_1$$

② z : inductor

$$\theta_z = 90^\circ$$

$$P_{AV} = 0$$

$$p(t) = -\frac{V_m I_m}{2} \sin(2\omega t + 2\theta_i)$$

$$Q = \frac{V_m I_m}{2}$$

Q: Reactive Power (unit VAR)

↳ volt-ampere reactive

$$Q = \frac{V_m I_m}{2} \sin(\theta_z)$$

25.3.2010

$$p(t) = P_{AV} \{ 1 + \cos(2\omega t + 2\theta_i) \} - Q \cdot \sin(2\omega t + 2\theta_i)$$

$$P_{AV} = V_{RMS} \cdot I_{RMS} \cdot \cos(\theta_z)$$


$$Q = V_{RMS} \cdot I_{RMS} \cdot \sin(\theta_z)$$

↓
 V_{eff}

$$\frac{1}{T} \int_0^T p(t) dt = P_{AV} \text{ in watts (time average of } p(t))$$

Work done in T_s secs. = $P_{AV} \cdot T_s \rightarrow$ Joules


Let's check:

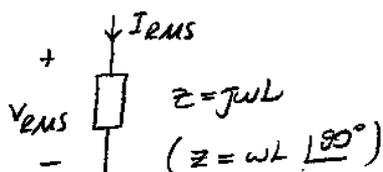

$$p(t) = -V_{RMS} \cdot I_{RMS} \sin(2\omega t + 2\theta_i)$$

$$P_{AV} = V_{RMS} \cdot I_{RMS} \cos(90^\circ) = 0$$
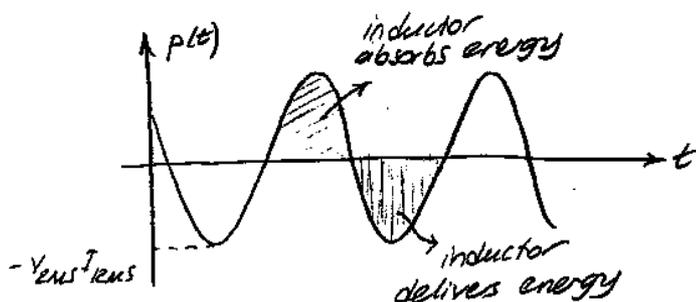
$$Q = V_{RMS} \cdot I_{RMS} \sin(90^\circ) = V_{RMS} I_{RMS}$$



Inductor does not do any work!

$$\langle p(t) \rangle = \frac{1}{T} \int_0^T p(t) dt = 0$$


Average Stored Energy:

$$\textcircled{1} \text{ Capacitor: } E_C(t) = \frac{1}{2} C V_C^2(t)$$

$$E_C^{AVG} = \frac{1}{T} \int_0^T (E_C(t)) dt = \frac{1}{2} C (V_C^{RMS})^2$$

② Inductor:
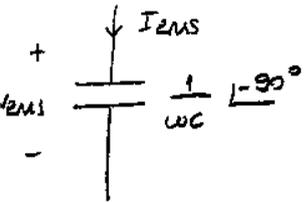
$$E_L^{AVG} = \frac{1}{2} \cdot L \cdot (I_L^{RMS})^2$$



$$Q = V_{RMS} \cdot I_{RMS} \sin(\theta_z) = -V_{RMS} \cdot I_{RMS}$$

$$P_{AV} = 0$$

$$= -V_{RMS} \cdot \frac{V_{RMS}}{|Z|}$$


$$= -\omega C V_{RMS}^2$$

$$= -2\omega \cdot \left(\frac{1}{2} C V_{RMS}^2 \right)$$

$$= -2\omega \cdot E_C^{AVG}$$

$$\frac{V_{phasor}}{I_{phasor}} = Z = \frac{1}{j\omega C}$$

$$\frac{V_{RMS}}{I_{RMS}} = |Z| = \frac{1}{\omega C}$$

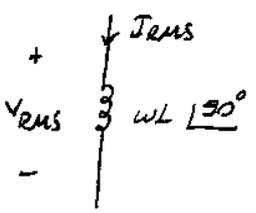



$$Q = V_{RMS} \cdot I_{RMS} \sin(90^\circ) = V_{RMS} I_{RMS}$$

$$= \omega L I_{RMS}^2$$

$$= 2\omega \left(\frac{1}{2} \cdot L I_{RMS}^2 \right)$$

$$= 2\omega E_L^{AVG}$$

conservation of P_AVG and Q:

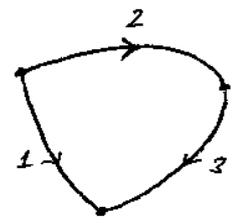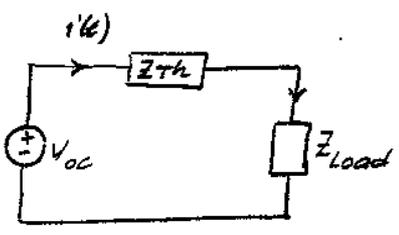

$$i_k(t) = I_m^k \cos(\omega t + \theta_i^k)$$

$$v_k(t) = V_m^k \cos(\omega t + \theta_v^k)$$

Tellegen's Theorem:

$$\sum_{k=1}^3 P_k(t) = 0$$

$$P_{AV2} \left\{ 1 + \cos(2\omega t + 2\theta_{i2}) \right\}$$

$$- Q_2 \sin(2\omega t + 2\theta_{i2})$$

$$P_{AV3} \left\{ 1 + \cos(2\omega t + 2\theta_{i3}) \right\}$$

$$- Q_3 \sin(2\omega t + 2\theta_{i3})$$

$$P_{AVS} \left\{ 1 + \cos(2\omega t + 2\theta_{iS}) \right\}$$

$$- Q_S \sin(2\omega t + 2\theta_{iS})$$

$$P_2(t) + P_3(t) = -P_1(t) = P_S(t)$$

power supplied by v_OC

Due to validity for all t

$$\sum P_{AV} \text{ absorbed} = \sum P_{AV} \text{ supplied}$$

$$\sum Q \text{ absorbed} = \sum Q \text{ supplied}$$

Complex Power

$$S = P + jQ = V_{RMS} I_{RMS} \cos(\theta_2) + j V_{RMS} I_{RMS} \sin(\theta_2)$$


complex power

Note:

$$p(t) = P_{AV} + P_{AV} \cos(2\omega t + 2\theta_i) - Q \sin(2\omega t + 2\theta_i)$$

$$= P_{AV} + \operatorname{Re} \left\{ (P_{AV} + jQ) e^{j2(\omega t + \theta_i)} \right\}$$

Ex

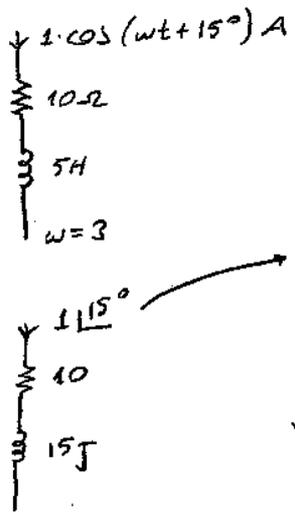

Find P_{AV} , Q , S for the component.

$$I_{RMS} = 1/\sqrt{2}$$

$$V = (1 \angle 15^\circ)(10 + j15) = (1 \angle 15^\circ) (5\sqrt{13} \angle \tan^{-1} 3/2)$$

$$= 5\sqrt{13} \angle 15^\circ + \tan^{-1} 3/2$$


$$V_{RMS} = \frac{5\sqrt{13}}{\sqrt{2}}$$

$$P_{AV} = I_{RMS} V_{RMS} \cos(\theta_2) = \frac{5\sqrt{13}}{2} \cdot \frac{10}{5\sqrt{13}} = 5 \text{ Watts}$$

$$Q = I_{RMS} \cdot V_{RMS} \cdot \sin(\theta_2) = \frac{5\sqrt{13}}{2} \cdot \frac{15}{5\sqrt{13}} = \frac{15}{2} \text{ VAR}$$

2nd Method

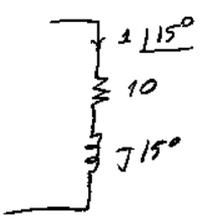P_{AV} of $(10 + j15)$ is only due to 10Ω



$$I_{RMS} = 1/\sqrt{2}$$

$$P_{AV}^{10\Omega} = V_{RMS} \cdot I_{RMS} \cdot \cos(\theta_2)$$


$$= I_{RMS}^2 R = \frac{1}{2} \cdot 10 = 5 \text{ Watts}$$

$$Q^{j15} = V_{RMS} \cdot I_{RMS} \sin(\theta_2)$$

$$= |Z_{j15}| \cdot I_{RMS} I_{RMS} = 15 \cdot I_{RMS}^2 = \frac{15}{2} \text{ VAR}$$

$\rightarrow 0$ for a resistor.


So in general

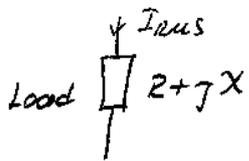

$$P_{Load} = I_{rms}^2 R$$

$$Q_{Load} = I_{rms}^2 X$$

3rd Method

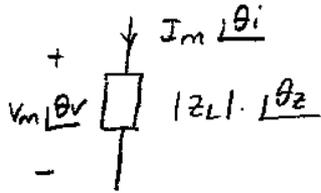

$$S = \frac{1}{2} \cdot V \cdot I^*$$

phasors


$$S = V_{rms} \cdot I_{rms} (\cos(\theta_z) + j \sin(\theta_z))$$

$$= \frac{|V|}{\sqrt{2}} \cdot \frac{|I|}{\sqrt{2}} e^{j\theta_z} \rightarrow \theta_v - \theta_i$$

$$= \frac{1}{2} (|V| \cdot e^{j\theta_v}) (|I| \cdot e^{-j\theta_i})$$

$$S_{Load} = \frac{1}{2} V \cdot I^*$$

Note! Inductive Load

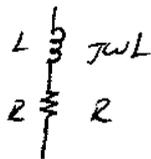


$$S = P + jQ$$

$$P = I_{rms}^2 \cdot R \quad \left. \begin{array}{l} P > 0 \\ Q > 0 \end{array} \right\}$$

$$Q_{ind} = I_{rms}^2 \cdot \omega L$$



Capacitive load

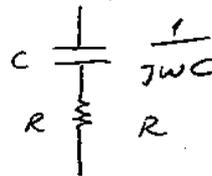

$$S = P + jQ$$

$$P = I_{rms}^2 \cdot R \quad \left. \begin{array}{l} P > 0 \\ Q < 0 \end{array} \right\}$$
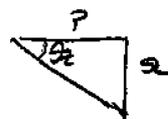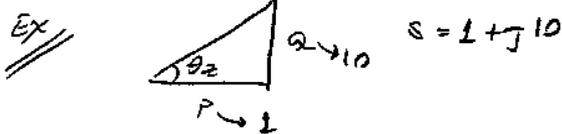
$$Q_{cap} = -I_{rms}^2 \cdot \frac{1}{\omega C}$$




power factor: $\cos(\theta_z)$
lagging (current lags)

leading (current leads)

29.3.2010

Review: AC steady-state power

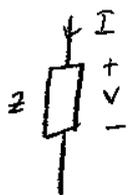

$$S = \frac{1}{2} V \cdot I^* = \frac{1}{2} |I|^2 Z = I_{rms}^2 \cdot Z$$

$$= I_{rms}^2 (R + jX)$$

$$\rightarrow I_{eff}^2$$


$$\Delta S = \Delta Z$$

pf = $\cos(\angle Z)$ lagging-leading

$$S = P + jQ$$

$$P = I_{rms}^2 R$$

$$Q = I_{rms}^2 X$$

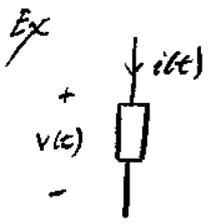

$v(t) = 3 \cos(4t + 30^\circ)$
 $i(t) = 6 \cos(4t - 20^\circ)$

1) Find real power (watts) and reactive power (VAR) of the component.

$S = \frac{1}{2} V \cdot I^* = \frac{1}{2} \cdot 3 \angle 30^\circ (6 \angle -20^\circ)^* = 9 \angle 50^\circ = 5.7 + j 6.8$


$P = 5.7 \text{ watts}$
 $Q = 6.8 \text{ VAR}$

2) Find pf of the component.

$\text{p.f.} = \cos(\Delta S) = \cos(50^\circ) = 0.64$ (lagging) (inductive)
 (current lags voltage)

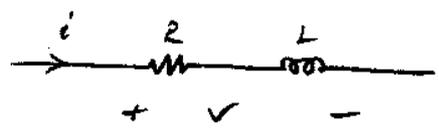
3) Assuming that the component is constructed from R, L, C, find suitable R, L, C to realize the component

$Z = \frac{V}{I} = \frac{3 \angle 30^\circ}{6 \angle -20^\circ} = \frac{1}{2} \angle 50^\circ = 0.32 + j 0.38$
 $= R + j \omega L \rightarrow L = \frac{0.38}{4} = 0.095 \text{ H}$



$V = 100 \text{ V (RMS)}$
 $P = 5 \text{ kW}$
 $\text{p.f.} = 0.8$ lagging

a) Find VAR (Reactive power)

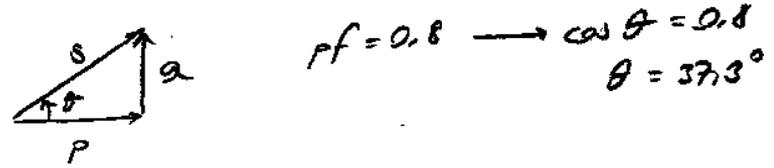

$Q = P \cdot \tan(37.3^\circ) = 5000 \cdot \frac{3}{4} = 3750 \text{ VAR}$

$S = P + jQ \rightarrow S = 5000 + j 3750$
 ↳ lagging

b) Apparent Power:

Apparent Power = $V_{\text{RMS}} \cdot I_{\text{RMS}}$
 $S = (5000 + j 3750) = I_{\text{RMS}}^2 (R + jX) = \frac{1}{2} |I|^2 Z = \frac{1}{2} \left| \frac{V}{Z} \right|^2 Z = \frac{1}{2} \frac{|V|^2}{Z^*}$
 $= \frac{V_{\text{RMS}}^2}{Z^*}$ ★ !

$$S = (5 + j 3,75) \text{ k} = \frac{V_{\text{RMS}}^2}{Z^*}$$

$$Z^* = \frac{1}{0,5 + j 0,375}$$

$$Z = \frac{1}{0,5 - j 0,375} = \frac{0,5 + j 0,375}{(0,5)^2 + (0,375)^2}$$


$$\text{Apparent power} = V_{\text{RMS}} \cdot I_{\text{RMS}} \quad \frac{V}{Z} = I \rightarrow I_{\text{RMS}} = \frac{V_{\text{RMS}}}{|Z|}$$

$$= 100 \cdot \frac{100}{121} = 10.000 \sqrt{(0,5)^2 + (0,375)^2}$$

$$\text{Apparent Power} = |S|$$

$$S = V_{\text{RMS}} I_{\text{RMS}} (\cos \theta_z + j \sin \theta_z)$$


$$|S| = V_{\text{RMS}} I_{\text{RMS}}$$

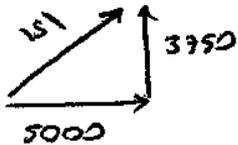

$$|S| = \frac{5000}{0,8} = 6250 \text{ VA}$$

Unit of S
is VA
(Volt-Ampere)

Ex

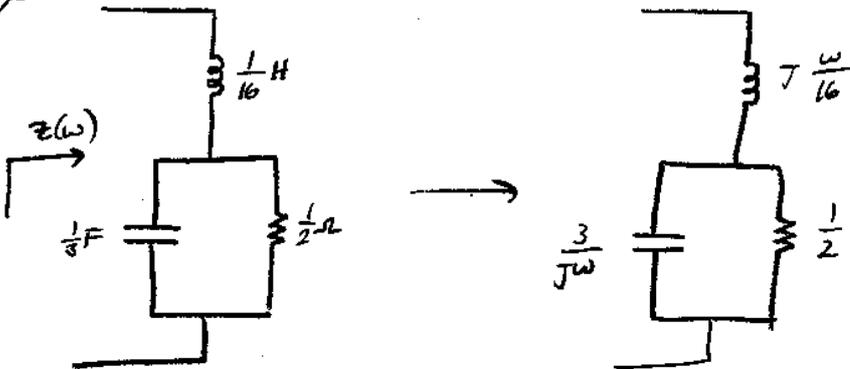


$$Z(\omega) = j \frac{\omega}{16} + \frac{\frac{3}{j\omega} \cdot \frac{1}{2}}{\frac{3}{j\omega} + \frac{1}{2}} = j \frac{\omega}{16} + \frac{3}{6 + j\omega} = \frac{j\omega}{16} + \frac{3(6 - j\omega)}{36 + \omega^2}$$

$$= \frac{j\omega^3 - 12j\omega + 288}{16(36 + \omega^2)} = \frac{288 + j\omega(\omega^2 - 12)}{16(36 + \omega^2)}$$

$$\textcircled{1} \omega = \sqrt{12} \rightarrow Z(\omega) \Big|_{\omega = \sqrt{12}} = \frac{288}{16 \cdot 48} \rightarrow \text{purely real}$$

$\textcircled{2} \omega > \sqrt{12} \rightarrow$ inductive load

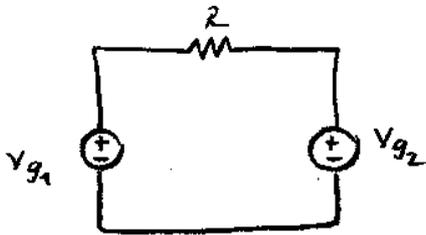$\textcircled{3} \omega < \sqrt{12} \rightarrow$ capacitive load



$$v_{g1} = V_1 \cos(\omega_1 t + \theta_1)$$

$$v_{g2} = V_2 \cos(\omega_2 t + \theta_2)$$


$$\boxed{\omega_1 \neq \omega_2!}$$

$$i_R(t) = I_1 \cos(\omega_1 t + \phi_1) + I_2 \cos(\omega_2 t + \phi_2) \text{ A (by superposition principle)}$$

$$P_{AV} = \frac{1}{T} \int_0^T (i_R(t))^2 R dt \rightarrow P_{AV} = \lim_{T \rightarrow \infty} \frac{1}{T} \int_0^T (i_R(t))^2 R dt$$

$$i_R^2(t) = I_1^2 \cos^2(\omega_1 t + \phi_1) + I_2^2 \cos^2(\omega_2 t + \phi_2) + 2I_1 I_2 \cos(\omega_1 t + \phi_1) \cos(\omega_2 t + \phi_2)$$

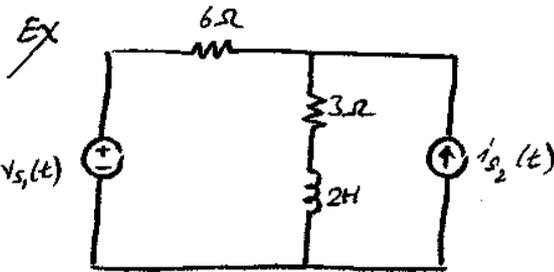
$$P_{AV} = (I_1^{RMS})^2 R + (I_2^{RMS})^2 R + \frac{2R}{T} I_1 I_2 \int_0^T \underbrace{\cos(\omega_1 t + \phi_1) \cos(\omega_2 t + \phi_2)}_{\frac{1}{2}(\cos((\omega_1 + \omega_2)t + \phi_1 + \phi_2) + \cos((\omega_1 - \omega_2)t + \phi_1 - \phi_2))} dt$$



$$v_s(t) = 6 \cos(3t) \text{ V}$$


$$i_{3\Omega}(t) = 2 \cos(4t + 30^\circ) \text{ A}$$

$$P_{3\Omega}^{AV} = ?$$

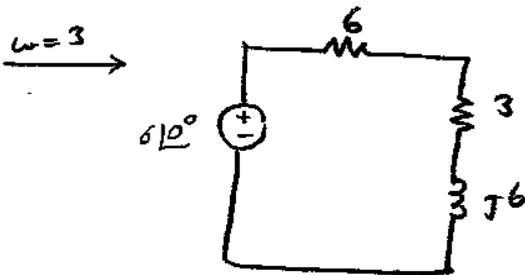

$$i_{3\Omega} = \frac{6 \angle 0^\circ}{3 + j6} = \frac{2}{3 + j2} = \frac{2}{\sqrt{13}} \angle \tan^{-1} \frac{2}{3} = 0.555 \angle -33.69^\circ$$
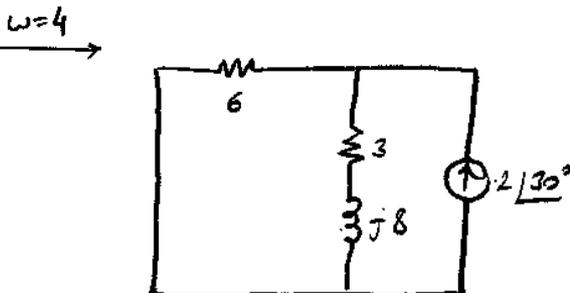
$$I_{3\Omega, RMS}^{\omega=3} = \frac{2}{\sqrt{13}} \cdot \frac{1}{\sqrt{2}} = \sqrt{\frac{2}{13}}$$




$$i_{3\Omega} = 2 \angle 30^\circ \cdot \frac{6}{9 + j8} = \frac{12 \angle 30^\circ}{\sqrt{145} \angle \tan^{-1} 8/9} = 0.997 \angle -11.634^\circ$$

$$I_{3\Omega, RMS}^{\omega=4} = \frac{6\sqrt{2}}{\sqrt{145}}$$

$$i_{3\Omega} = 0.555 \cos(3t - 33.69^\circ) + 0.997 \cos(4t - 11.634^\circ) \text{ A}$$

$$P_{AV} = P_{AV}^{\omega=3} + P_{AV}^{\omega=4} = (I_{RMS}^{\omega=3})^2 \cdot 3 + (I_{RMS}^{\omega=4})^2 \cdot 3 = 0.462 + 1.491 = 1.153 \text{ Watt}$$

Maximum Power Transfer

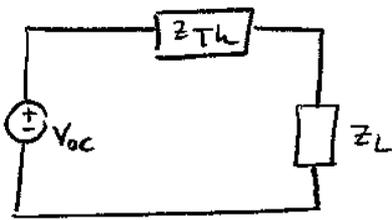

V_{oc}, Z_{TH} : fixed

What should the value of Z_L be such that P_{avg} of the load (Z_L) is maximized?

★ $Z_L = Z_{TH}^*$ ★

is the maximum transfer solution

Proof $P_{Load} = I_{RMS}^2 \cdot R_L$

$$P_{Load}(Z_L, X_L) = \frac{1}{2} \left| \frac{V_{oc}}{(Z_{TH} + Z_L) + j(X_{TH} + X_L)} \right|^2 \cdot R_L$$

$$\frac{\partial P_{Load}}{\partial R_L} = 0$$

$$\frac{\partial P_{Load}}{\partial X_L} = 0$$


Solve together

$$X_L = -X_{TH}$$

$$R_L = R_{TH}$$

$$Z_L = Z_{TH}^*$$

Ex

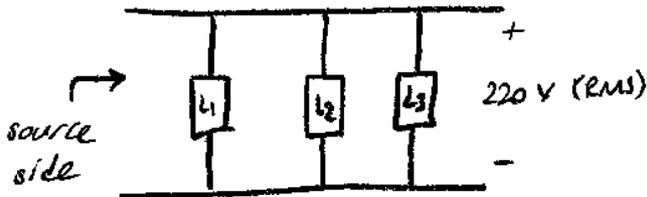

Load 1 : 16 kW , 18 kVAR

Load 2 : 10 kVA at 0.6 lead

Load 3 : 8 kW at unity pf

a) Find p.f. on the source side

b) Find the impedance seen by the source

$$S_1 = 16 + j18 \text{ kVA}$$

$$S_2 = 6 - j8 \text{ kVA}$$


$$S_3 = 8 \text{ kVA}$$

$$S_{source}^{supplied} = 30 + j10 \text{ kVA}$$

$$p.f. = \cos(\theta_2)$$

$$S_{total} = I_{RMS}^2 Z_{combined} \rightarrow 4S = 4Z$$

$$S_{total} = 30 + j10 \text{ kVA}$$

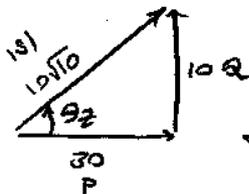

$$p.f = \cos(\theta_2) = \frac{30}{10\sqrt{10}} = \frac{3\sqrt{10}}{10} \text{ lagging}$$

always state leading or lagging with pf.

b) $S = \bar{I}_{RMS}^2 Z_{comb.}$; $|S| = V_{RMS} \cdot I_{RMS}$ ($S = \frac{1}{2} V \cdot I^*$)

$30 + j10$ $220 V$

$$I_{RMS} = \frac{10\sqrt{10} \times 10^3}{220} = 143,74 \text{ A (RMS)}$$

$$Z_{comb} = \frac{S}{\bar{I}_{RMS}^2} = \frac{(30 + j10) \times 10^3}{(143,74)^2} = 1,45 + j0,48$$

Power Factor Compensation

Ex/ A mill consumes 100 kW from 220 V RMS line, at pf 0,85 lagging.

a) Find the current (RMS) supplied by the source

b) Find the current (RMS) " if pf were 0,95 lagging


a) $S_L = 100 + j 100 \tan(31,7^\circ)$ $|S_L| = V_{RMS} \cdot I_{RMS}$

$$|S_L| = \frac{100}{0,85} = 117,66 \text{ kVA} \quad I_{RMS} = \frac{|S_L|}{V_{RMS}} = 534,8 \text{ A}$$

b) $S_L = 100 + j \tan(18^\circ)$

$$|S_L| = \frac{100}{0,95} = 105,3 \text{ kVA} \rightarrow I_{RMS} = \frac{|S_L|}{220 V} = 478 \text{ A}$$

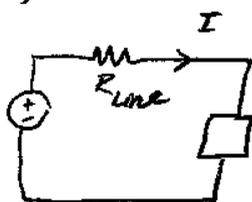c) If there is a line connecting generator to the load and $R_{line} = 0,1$; Find the power loss over the line for $pf = 0,85$, $pf = 0,95$.



i) $pf = 0,85$ $P_{line} = (0,1) \cdot I_{RMS}^2 = 0,1 \cdot (534,8)^2$
 $= 28,6 \text{ kW}$

ii) $pf = 0,95$ $P_{line} = 0,1 \cdot (478)^2 = 22,9 \text{ kW}$

d) Define efficiency:

$$\text{efficiency} = \frac{\text{Real power supplied to load}}{\text{Real power generated by source}}$$


$$pf = 0.85 \rightarrow \text{eff} = \frac{100}{100 + 28.6} = 77\%$$

$$pf = 0.95 \rightarrow \text{eff} = \frac{100}{100 + 22} = 82\%$$


Ex) Load requires 2kW at 0.75 pf lagging at 220 V rms.
Calculate the reactive power supplied by the compensating capacitor to make pf 0.9 and find the impedance and assuming 50 Hz, 220 V (RMS) system find the capacitor value in terms of Farads.

Before:

$$S_{\text{before}} = 2000 + j1764$$

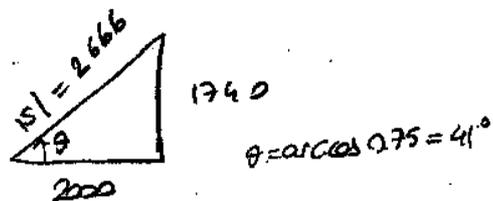


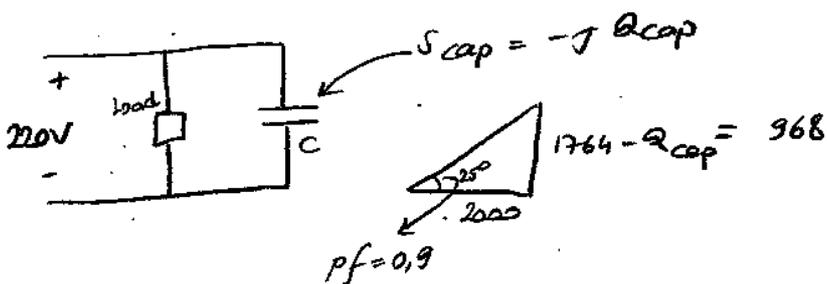We assume that load & compensating element always operate at 220 V (RMS)



$$Q_{\text{cap}} = 796$$

$$S_{\text{cap}} = -j 796 \text{ VAR}$$

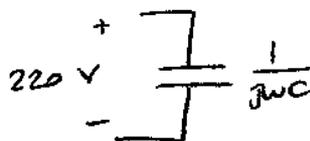

$$I_{\text{rms}} = \frac{|S_{\text{cap}}|}{220} = 3.61 \text{ A (rms)}$$

$$S_{\text{cap}} = I_{\text{rms}}^2 \cdot Z_{\text{cap}} = -j 796$$

$$Z_{\text{cap}} = \frac{-j 796}{(3.61)^2} = -j 61.07$$


$$-j \frac{1}{\omega C} = -j 61.07 \rightarrow C = \frac{1}{100\pi \cdot 61.07} = 52 \mu\text{F}$$

Volt-Ampere Method

We make use of conservation of complex power in the Volt-Ampere method.

$$\sum_k S_k^{supplied} = \sum_k S_k^{absorbed}$$

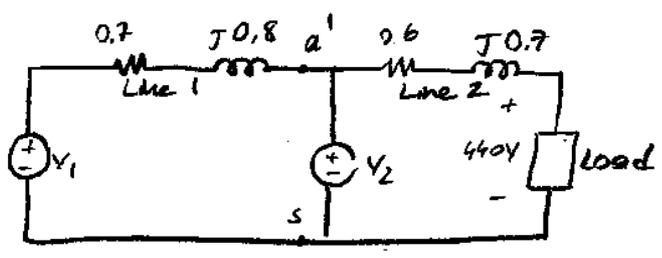Ex Two generators supply 10 kW load at 0.8 pf lagging.
 The generator-2 supplies 5 kW at 0.6 pf lagging
 Find the voltages of V_1 & V_2 (RMS), the apparent power of generator 1 and pf of generator 1.



$$S_{G2}^{supplied} = 5000 + j6666 \text{ VA}$$

$$S_L = 10000 + j7500 \text{ VA}$$

$$I_{RMS}^{load} = \frac{|S_{Load}|}{V_{RMS}} = \frac{10000/0.8}{440} = 28.4 \text{ A RMS}$$

$$S_{Line-2} = (I_{load}^{RMS})^2 \cdot (0.6 + j0.7) = 484 + j565$$

$$S_{Load} + S_{Line-2} = 10484 + j8065 \text{ VA}$$

$$|S_{Load+Line-2}| = I_{load}^{RMS} \cdot V_2^{RMS}$$

$$(0.484^2 + 8065^2)^{1/2} = 28.4 V_2^{RMS} \rightarrow V_2^{RMS} = 466 \text{ V RMS}$$

$$S_{right \text{ of } a-a'} = S_{Load+Line-2} - S_{G2}^{sup} = 5484 + j1400$$

$$|S_{right \text{ of } a-a'}| = I_{Line-1}^{RMS} \cdot V_{a-a'}^{RMS}$$

$$(5484^2 + 1400^2)^{1/2} = I_{Line-1}^{RMS} \cdot 466$$

$$I_{Line-1}^{RMS} = 12.14 \text{ A}$$

$$S_{Line-1} = (I_{Line-1}^{RMS})^2 \cdot (0.7 + j0.8) = 103 + j118$$


$$S_{G1}^{sup} = S_{Line-1} + S_{right \text{ of } a-a'} = 5587 + j1516$$

$$|C_{sup}| = V_1 \cdot I_1 \Rightarrow V_1^{RMS} = \frac{(5587^2 + 1516^2)^{1/2}}{12.14} = 477 \text{ V}$$

$$pf = \cos^{-1} \frac{5587}{(5587^2 + 1516^2)^{1/2}} = 0.965$$

3-Phase Balanced Circuits


Y-Connection

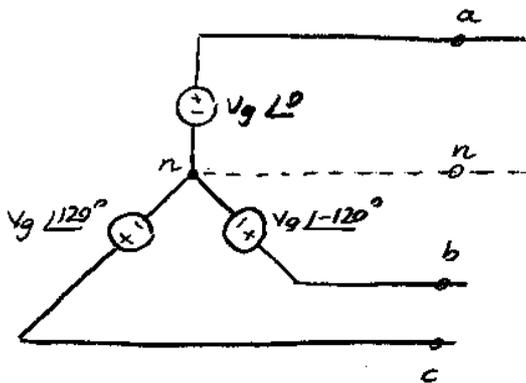


$$V_{an} = V_g L^0$$

$$V_{bn} = V_g L^{-120^\circ}$$

$$V_{cn} = V_g L^{120^\circ}$$

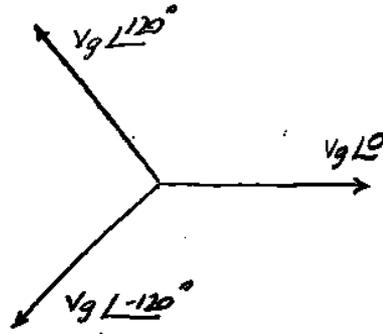


Balanced 3- ϕ systems.

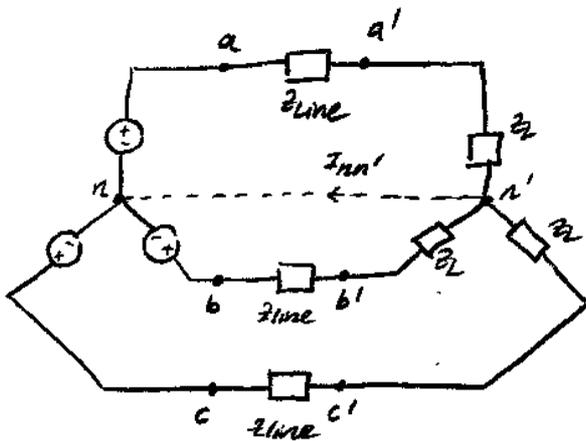


Note:

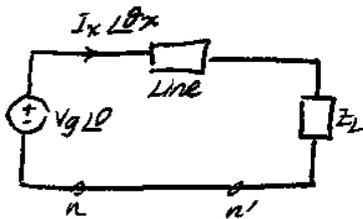Solving only phase a is equivalent to solving all phases since




Then
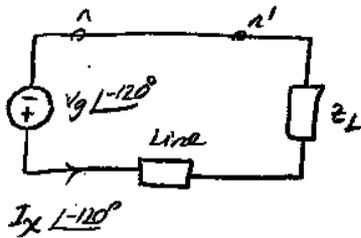
$$I_{nn'} = I_x L^{0x} + I_x L^{0x-120^\circ} + I_x L^{0x+120^\circ}$$



Phase-Line Current / Voltages

Y-Connection:

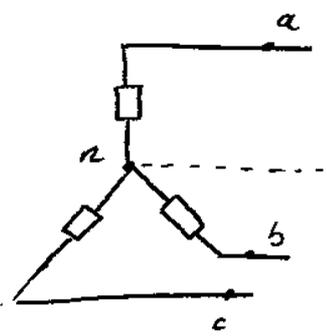

V_{an}, V_{bn}, V_{cn} : Phase voltages


V_{ab}, V_{ac}, V_{bc} : Line voltages
(line to line)

$V_{ab} = V_a - V_b = V_{an} + V_{nb}$

I_{an} : phase current
 $I_{aa'}$: Line current
 $I_{aa'} = I_{an}$


Phase voltage \neq Line voltage
 Phase current = Line current
 } For Y-connection

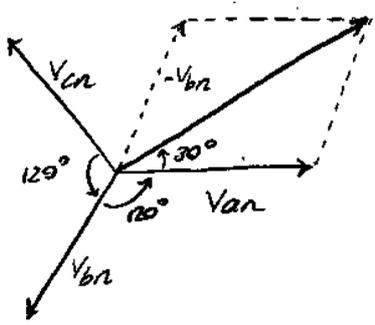Line-voltage, phase-voltage relation for Y-connection




$V_{ab} = \sqrt{3} V_g \angle 30^\circ$
 $V_{ac} = \sqrt{3} V_g \angle -30^\circ$
 $V_{bc} = \sqrt{3} V_g \angle -90^\circ$

08.04.2010

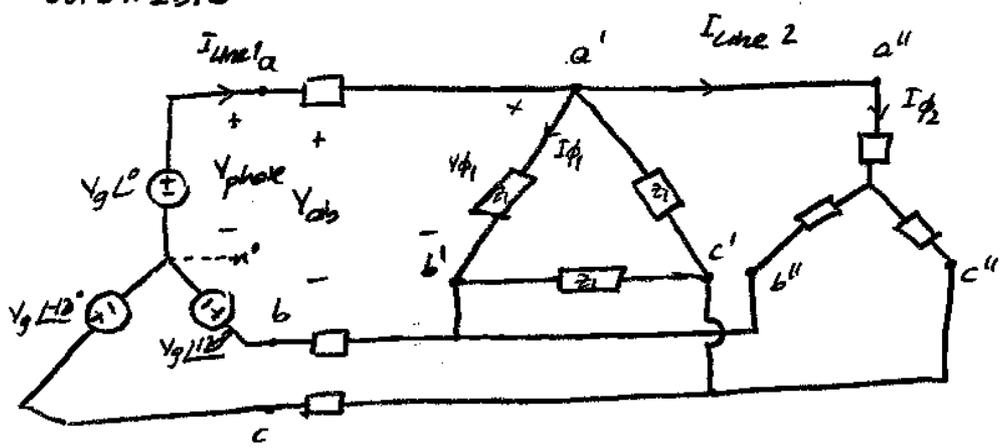

V_p : phase voltage
 I_p : phase current
 (current in a single phase of the component)

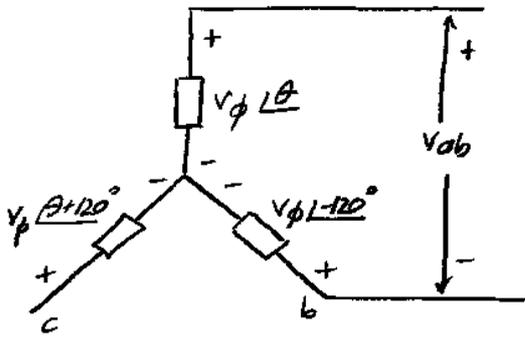V_{line} : Line voltage (V_{ab}, V_{ac}, V_{bc})
 I_{line} : Current passing thru the line
 (2 line)



$$\begin{aligned}
 V_{ab} &= V_{\phi} \angle \theta - V_{\phi} \angle \theta - 120^\circ \\
 &= V_{\phi} \angle \theta (1 - \angle -120^\circ) \\
 &= V_{\phi} \angle \theta (1 + \angle 60^\circ) \\
 &= V_{\phi} \angle \theta \left(1 + \frac{1}{2} + j\frac{\sqrt{3}}{2}\right) \\
 &= \sqrt{3} V_{\phi} \angle \theta \left(\frac{\sqrt{3}}{2} + j\frac{1}{2}\right) = \sqrt{3} V_{\phi} \angle \theta + 30^\circ
 \end{aligned}$$

(Line voltage in RMS) = $\sqrt{3} \times$ (Phase voltage in RMS)

(Line current in RMS) = (Phase current in RMS)

Power Relations for Y-Connection

$$P_{Tot} = 3 \cdot P_{\phi} \rightarrow \text{per phase}$$

$$P_{\phi} = |I_{\phi, RMS}|^2 R_{\phi}$$

$$S_{Tot} = 3 S_{\phi}$$

$$S_{\phi} = |I_{\phi, RMS}|^2 (R_{\phi} + jX_{\phi})$$

$$P_{Tot} = \text{Re} \{ S_{Tot} \} = 3 \text{Re} \{ S_{\phi} \} = 3 \text{Re} \left\{ |I_{\phi, RMS}|^2 |Z_{\phi}| e^{j\angle Z_{\phi}} \right\}$$


$$= 3 \text{Re} \left\{ I_{\phi, RMS} \cdot V_{\phi, RMS} \cdot e^{j\angle Z_{\phi}} \right\}$$

$$= 3 \cdot I_{\phi, RMS} \cdot V_{\phi, RMS} \cdot \cos(\angle Z_{\phi})$$


$$\underbrace{I_{LINE}} \quad \underbrace{\frac{V_{LINE}}{\sqrt{3}}}$$

$$= \sqrt{3} \cdot V_{LINE, RMS} \cdot I_{LINE, RMS} \cdot \cos(\angle Z_{\phi})$$

P_{Total} for Y-Load

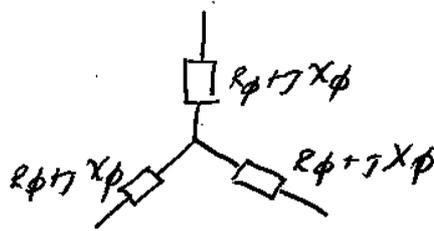


Δ- Connection

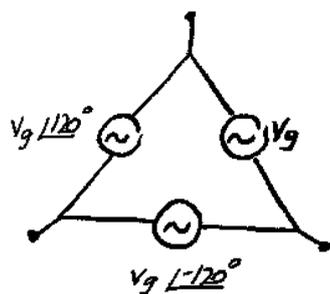

No neutral line

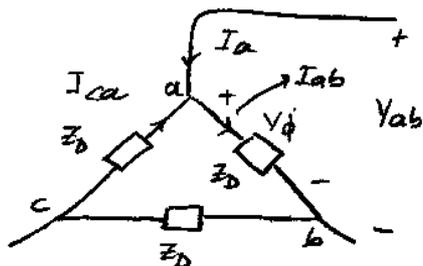Generators are Y connected in general, not Δ connected.



For Δ-Load

$$V_{line, RMS} = V_{\phi, RMS}$$

$$I_{line, RMS} = \sqrt{3} \cdot I_{\phi, RMS}$$

$$I_a = I_{ab} - I_{ca} = \frac{V_{ab}}{z_{\Delta}} - \frac{V_{ca}}{z_{\Delta}} = \frac{V_{\phi} \angle 0^\circ}{z_{\Delta}} - \frac{V_{\phi} \angle -120^\circ}{z_{\Delta}}$$

$$= I_{\phi} - I_{\phi} \angle -120^\circ$$

$$I_a = \sqrt{3} I_{\phi} \angle 30^\circ$$

↓
Line current

Power Calculation for Δ-Load


$$P_{Tot} = 3 P_{\phi} = 3 Re \left\{ V_{\phi, RMS}^{\Delta} \cdot I_{\phi, RMS}^{\Delta} \cdot e^{j \Delta z_{\Delta}} \right\}$$

$$= 3 Re \left\{ V_{line, RMS}^{\Delta} \cdot \frac{I_{line, RMS}^{\Delta}}{\sqrt{3}} \cdot e^{j \Delta z_{\Delta}} \right\}$$

$$= \sqrt{3} \cdot V_{line, RMS}^{\Delta} \cdot I_{line, RMS}^{\Delta} \cdot \cos(\Delta z_{\Delta})$$

same formula for both Δ and Y Loads!

Ex

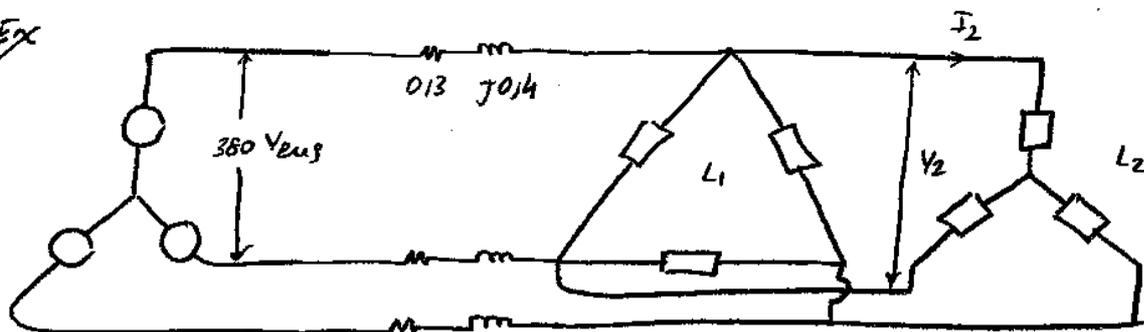


Generator produces 380V-rms line to line voltage
produces 9 kW and 9 k-VAR

Load 1 6kW at 0.6 p.f. Lagging

Find V_2 , I_2 and power absorbed by Load₂.

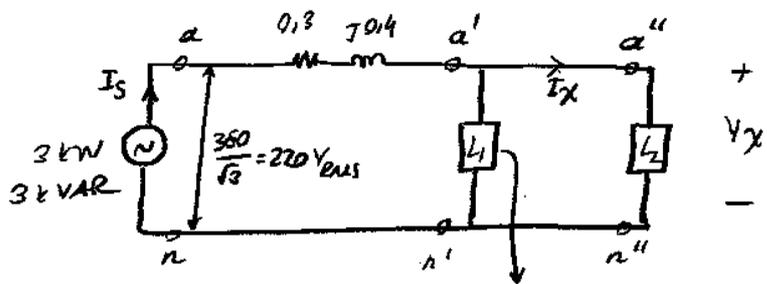Soln 1: Using single phase equivalent circuit.



converted to an Y-load
by $\Delta \rightarrow Y$ transformation

$$S_G = 3 + j3 \text{ kVA} \quad |S_G| = 3\sqrt{2} \text{ kVA} = 220 \cdot I_{S-rms}$$

$$I_{S-rms} = 19.3 \text{ A}$$

$$S_{LINE} = I_{S,rms}^2 (0.3 + j0.4) = 112 + j149$$

$$S_{L1} + S_{L2} = 3000 + j3000 - (112 + j149) \\ = 2888 + j2851$$

$$|S_{L1+L2}| = |V_{x-rms}| |I_{S-rms}|$$

$$4,058 \text{ kVA} = V_{x-rms} \cdot 19.3 \rightarrow V_{x-rms} = 210,3$$

$$V_2 = \sqrt{3} \cdot V_x = 364 \text{ V}_{rms}$$


$$S_{L2} = S_{L1+L2} - S_{L1} = 2888 + j2851 - \left(\frac{6000 + j6000}{3} \right) \\ = 888 + j187$$

$$|S_{L2}| = V_{x-rms} \cdot I_{x-rms} \rightarrow I_{x-rms} = 4,31 \text{ A}_{rms} = \bar{I}_2$$

Power absorbed by Load 2

$$S_{L2}^{tot} = 3 S_{L2} = 2664 + j561$$

Soln 2: Single Line diagram

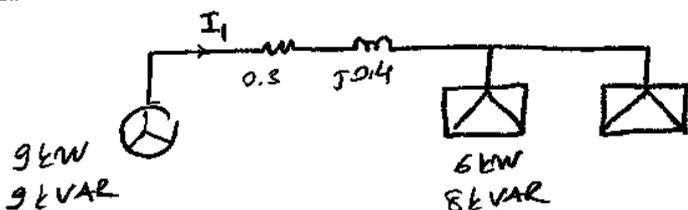

For both loads

$$P_{load} = \sqrt{3} V_{line} \cdot I_{line} \cdot \cos(\angle Z_{load})$$

$$Q_{load} = \sqrt{3} V_{line} \cdot I_{line} \cdot \sin(\angle Z_{load})$$

$$S_{load} = P_{load} + j Q_{load}$$

} 3p total
power
quantities

① Find $I_L \rightarrow |S_{gen}| = \sqrt{3} \cdot \underbrace{V_{Line}^{gen}}_{380} \cdot I_{Line}^{gen}$
 $9000\sqrt{2} \qquad \qquad \qquad I_{Line} = 19.3 \text{ A}$

② Line Losses $S_{Line} = 3(19.3)^2(0.3 + j0.4) = 336 + j447$

③ Power left to loads
 $S_{L1+L2} = 8664 + j8553$

④ $|S_{L1+L2}| = \sqrt{3} |V_{L1+L2}^{RMS}| \cdot I_{Line}$
 $V_{L1+L2}^{RMS} = 364 \text{ V}_{RMS}$


⑤ $S_{L2} = 8664 - 6000 + j(8553 - 8000) = 2664 + j561 \text{ VA}$

12.04.2010

3- ϕ Systems

Y-Connection


Δ -Connection

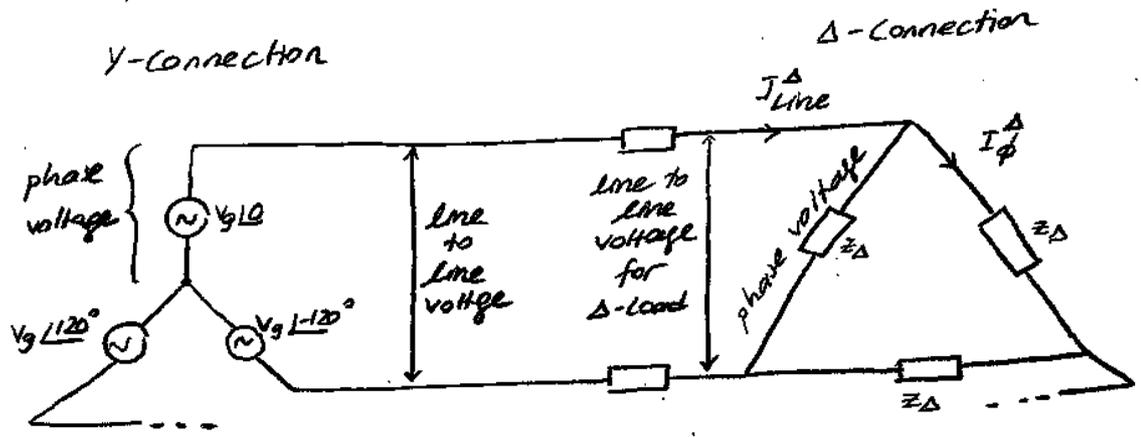

phase voltage: V_g (RMS)
 Line to Line voltage = $\sqrt{3} V_g$

$V_{phase} = V_{Line}$
 $\sqrt{3} \cdot I_{\phi}^{\Delta} = I_{Line}$

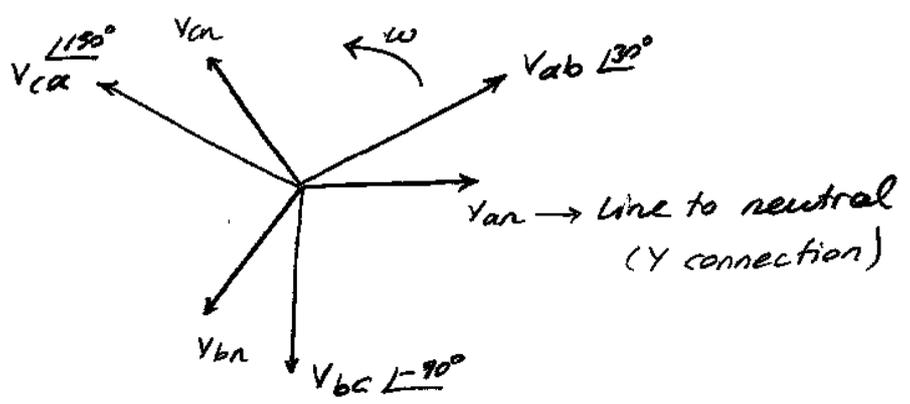
$P_{Load}^{Tot, VA} = \sqrt{3} \cdot V_{Load, RMS} \cdot I_{Load, RMS} \cdot \underbrace{\cos(\angle \theta_z)}_{\text{p.f of load.}}$
 $Q_{Load}^{Tot, VA} = \dots \cdot \sin(\angle \theta_z)$




a b c (positive sequence) (a at 0° , then b at 120° , c at 240°)

a c b (negative sequence)

Δ -Y

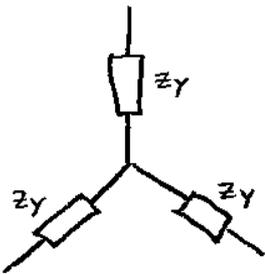


\equiv

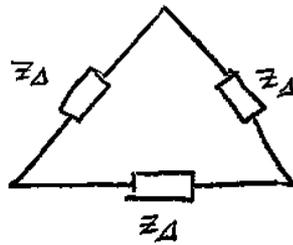

$$Z_{\Delta} = 3 Z_Y$$

ZPS IV

Prob ⑥

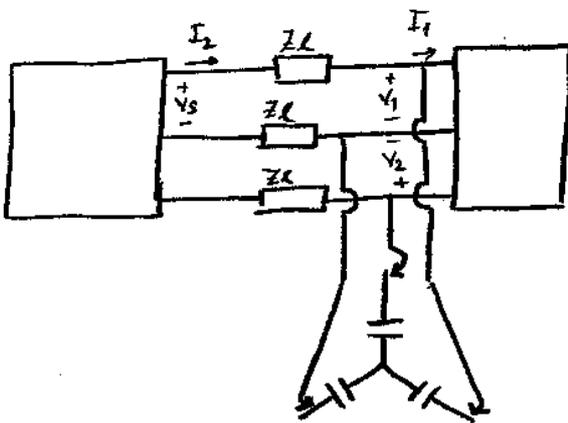

A balanced 3- ϕ

Load: 400 kW, $pf = \frac{1}{\sqrt{2}}$ lagging

$$V_1 = 400 \angle 30^\circ \quad V_2 = 400 \angle -30^\circ \text{ V}_{\text{RMS}}$$

$$Z_L = 0.07 + j0.16 \quad \text{RMS phase}$$

a) switches are open. Find I_1 , V_{self} , the complex power supplied by source, and efficiency.

3 ϕ Problems:

- ① By default, given powers are 3 ϕ
- ② By default, given voltages are line-to-line.

$$a) P_{\text{tot}} = 400 \text{ kW} = \sqrt{3} V_{\text{line}} \cdot I_{\text{line}} \cdot \cos(\angle \theta_2) \rightarrow I_1 = 816.7 \text{ A (RMS)}$$


$$S_{\text{line tot}} = 3 I_{1, \text{RMS}}^2 \cdot (2\lambda) = 140 + j 320 \text{ kVA}$$

$$S_{\text{sup tot}} = 540 + j(320 + 400) = 540 + j 720 \text{ kVA}$$

$$\text{Eff} = \frac{400}{540} = 74\%$$


b) switches are closed, and pf of the compensated load becomes 0.8 lagging. Find the susceptance of the capacitors in the bank, I_1 , I_2 , V_{self} , complex power supplied by the load.

Before comp.

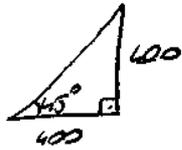

After comp.

$p = 400 \text{ kW}$ $pf = 0.8$

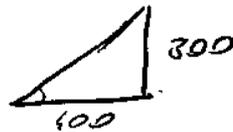

$|S_{tot}| = \sqrt{3} \cdot V_{Line} \cdot I_{Line}$

$500 \text{ kVA} = \sqrt{3} \cdot 400 \cdot I_{Line} \rightarrow I_{Line} = I_2 = 721.6 \text{ A}$

$S_{Line}^{tot} = 3 \cdot (I_{RMS})^2 \cdot Z_2 = 109 + j 250 \text{ kVA}$

$S_{tot}^{sup} = 509 + j 550 \text{ kVA}$

$Eff = \frac{400}{509} = 78 \%$

$V_{Line}^{sup} = \frac{|S_{tot}^{sup}|}{\sqrt{3} |I_{Line}^{sup}|} = 600 \text{ V}_{RMS}$
 $\rightarrow I_2 = 721.6$


$S_{cap-bank} = -100 j \text{ kVAR}$

$S_{cap} = -j \frac{100}{3} \text{ kVAR}$
 per phase


$-j \frac{100}{3} = \frac{|V_{RMS}^{cap}|^2}{Z_{cap}^*} \rightarrow \frac{1}{Z_{cap}^*} = \frac{-j \frac{100}{3} \text{ kVA}}{(\frac{400}{\sqrt{3}})^2}$

$Z_{cap} = -j \frac{16}{10}$

3- ϕ Power measurement

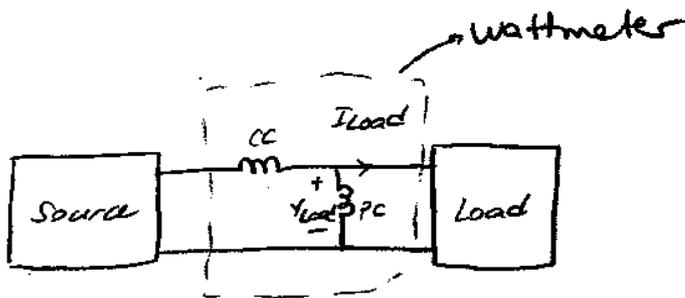

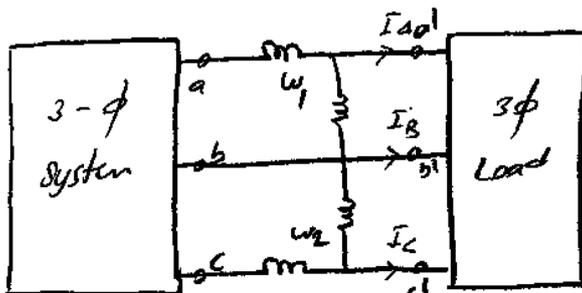cc : current coil (low impedance)
 pc : Potential coil (high impedance)



Measurement of W_1 : $\text{Re} \{ V_{a'b'} \cdot I_A^* \}$

" W_2 : $\text{Re} \{ V_{c'b'} \cdot I_C^* \}$

$$V_{a'b'} = V_{L\text{ine}} \angle 30^\circ$$

$$V_{b'c'} = V_{L\text{ine}} \angle -90^\circ$$

$$I_A = I_{L\text{ine}} \angle -\theta$$


$$I_C = I_{L\text{ine}} \angle -\theta + 120^\circ$$

$$W_1 = \text{Re} \{ V_{L\text{ine}} \angle 30^\circ \cdot I_{L\text{ine}} \angle -\theta \} = V_{L\text{ine}} \cdot I_{L\text{ine}} \cos(\theta + 30^\circ)$$

$$W_2 = \text{Re} \{ V_{L\text{ine}} \angle -90^\circ \cdot I_{L\text{ine}} \angle -\theta + 120^\circ \} = V_{L\text{ine}} \cdot I_{L\text{ine}} \cos(\theta - 30^\circ)$$

$$W_1 + W_2 = V_{L\text{ine}} \cdot I_{L\text{ine}} (2 \cos \theta \cdot \cos(30^\circ)) = \sqrt{3} \cdot V_{L\text{ine}} \cdot I_{L\text{ine}} \cos \theta$$

total power absorbed
by the load.

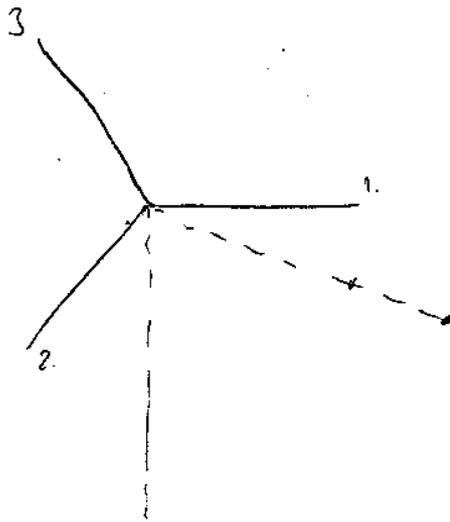

$$V_{L\text{ine}} \angle -30^\circ \cdot I_{L\text{ine}} \angle \theta$$

$$V_{L\text{ine}} I_{L\text{ine}} \cos(\theta - 30^\circ)$$

$$V_{L\text{ine}} \angle -90^\circ \cdot I_{L\text{ine}} \angle \theta + 120^\circ$$


$$V_{L\text{ine}} I_{L\text{ine}} \cos(\theta + 150^\circ)$$

$$2 \cos(\theta - 60^\circ) \cos(90^\circ)$$

Z

a) LTI dyn. circuit

i) formulation ii) solution

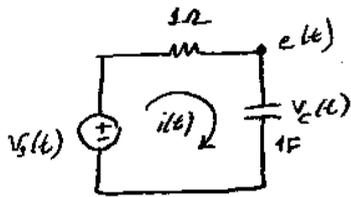

$v_c(0^-) = v_0$

$(D+1) \cdot e(t) = v_s(t)$

$e(0^-) = v_0$

planar circuit: $(1+D^{-1}) i(t) = v_s(t) - v_0$

t-domain

$d(s) = s+1=0 \rightarrow s=-1$

$v_{ch} = a \cdot e^{-t}$

$v_s(t) = 0 : \begin{cases} v_{c21}(t) = a \cdot e^{-t} \\ v_{c21}(0^-) = v_0 \end{cases} \rightarrow a = v_0$

$v_0 = 0 : v_{c25}(t)$

$v_{c25}(0^-) = 0$

$v_c(t) = v_{c21}(t) + v_{c25}(t)$

$v_s(t) = \delta(t)$

$\dot{h}(t) = -h(t) + \delta(t)$

\uparrow
 $v_{c21}(t) \quad h(0^-) = 0$

$h(t) = v_{ch}(t) \cdot u(t) \rightarrow a \cdot e^{-t}$

$h(0^+) = 1 \rightarrow a = 1 \rightarrow h(t) = e^{-t} \cdot u(t)$

Note:

$h(t) = a \cdot e^{-t} u(t)$

$\dot{h}(t) = -a \cdot e^{-t} u(t) + \underbrace{a \cdot e^{-t} \delta(t)}_{a \cdot \delta(t)}$

$-a \cdot e^{-t} u(t) + a \cdot \delta(t) = -a \cdot e^{-t} u(t) + \delta(t)$

$a = 1$

$v_{c25}(t) = h(t) * u_s(t)$

$= \int_0^t h(t-t') u_s(t') dt'$

$= e^{-t} \int_0^t e^{t'} u_s(t') dt', t \geq 0$

$v_s(t) = u(t) : v_{c25}(t) = 1 - e^{-t} \quad v, t \geq 0$

$t - 1 + e^{-t} \quad v, t \geq 0$

$t u(t) :$

$\frac{1}{2} (e^t - e^{-t}) \quad v, t \geq 0$

$e^t u(t) :$

$t \cdot e^{-t} \quad v, t \geq 0$

$e^{-t} u(t) :$

for $\cos(t) \cdot u(t) :$

$\int_0^t e^{t'} \cos(t') dt' = \operatorname{Re} \left\{ \int_0^t e^{t'} e^{j t'} dt' \right\}$

$= \operatorname{Re} \left\{ \frac{1}{1+j} e^{(1+j)t'} \Big|_0^t \right\} = \operatorname{Re} \left\{ \frac{1}{1+j} e^{(1+j)t} - \frac{1}{1+j} \right\}$

$1 - 545^\circ \quad 1 - 135^\circ$

$$= \frac{1}{\sqrt{2}} e^{t} (\cos t - 45^\circ) - \frac{1}{2}$$

$$\cos(t) \cdot u(t) : \frac{1}{\sqrt{2}} (\cos t - 45^\circ) - \frac{1}{2} e^{-t} \quad v, t \geq 0$$

$$\underline{\text{If}} \quad v_s(t) = v_s \cdot e^{s_0 t}$$

$$\text{let } v_{cp}(t) = v_c \cdot e^{s_0 t}$$

$$v_c = \frac{1}{s_0 + 1} v_s$$

$$v_{c_{zs}}(t) = \underbrace{a \cdot e^{-t}}_{v_{ch}(t)} + v_{cp}(t)$$

$$v_{c_{zs}}(0) = 0 = a + v_{cp}(0) \Rightarrow a = -v_{cp}(0)$$

$$v_s(t) = 1, t \geq 0$$

$$v_s = 0, s = 0 \Rightarrow v_c = 1 \quad v_{cp}(t) = 1$$

$$v_{c_{zs}}(t) = a \cdot e^{-t} + 1$$

$$\downarrow$$

$$-1$$

$$e^{Jt}: v_s = 1, s_0 = J$$

$$v_c = \frac{1}{J+1} = \frac{1}{\sqrt{2}} e^{-J45^\circ}$$

$$v_{cp}(t) = \text{Re} \{ v_c \cdot e^{Jt} \}$$

$$= \frac{1}{\sqrt{2}} \cos(t - 45^\circ)$$

$$v_{c_{zs}}(t) = a e^{-t} + \frac{1}{\sqrt{2}} \cos(t - 45^\circ)$$

$$a + \frac{1}{\sqrt{2}} \cos(-45^\circ) = 0 \rightarrow a = -\frac{1}{2}$$

$$\dot{v}_c(t) = -v_c(t) + v_s(t)$$

$$v_c(0^-) = v_0$$

s-domain


$$\mathcal{L} \{ \dot{v}_c(t) \} = \mathcal{L} \{ -v_c(t) + v_s(t) \}$$

$$s v_c(s) - \frac{v_c(0^-)}{v_0} = -v_c(s) + v_s(s)$$

$$(s+1) v_c(s) = v_0 + v_s(s) \longrightarrow$$

$$v_s(t) = \delta(t) \Rightarrow v_s(s) = 1$$
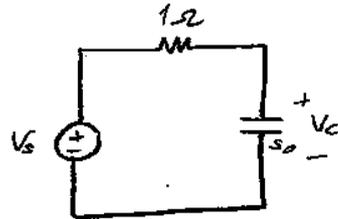
$$\Rightarrow v_{c_{zs}}(s) = \frac{1}{s+1}$$



$$v_c = \frac{\frac{1}{s_0}}{\frac{1}{s_0} + 1} v_s$$

$$= \frac{1}{s_0 + 1} v_s$$

$$v_c(s) = \underbrace{\frac{1}{s+1} v_s(s)}_{v_{c_{zs}}(s)} + \underbrace{\frac{v_0}{s+1}}_{v_{c_{zi}}(s)}$$

$$v_c(t) = v_{c_{zs}}(t) + v_0 \cdot e^{-t}$$

z

$$u(t) \rightarrow \frac{1}{s}$$

$$V_{C2S}(s) = \frac{1}{s+1} \cdot \frac{1}{s} = \frac{1}{s} - \frac{1}{s+1}$$

$$\frac{1}{s} \cdot \frac{1}{s+1} = \frac{a}{s+1} + \frac{b}{s}$$

$$\frac{1}{s} \Big|_{s=-1} = a + b \frac{s+1}{s} \Big|_{s=-1}$$

$$a = -1, b = 1$$

$$t u(t) \rightarrow \frac{1}{s^2}$$

$$V_{C2S}(s) = \frac{1}{s+1} \cdot \frac{1}{s^2} = \frac{a}{s+1} + \frac{b}{s} + \frac{c}{s^2}$$

$$a = -1, c = 1$$

to find b, differentiate

$$\frac{1}{s+1} = a \cdot \frac{s^2}{s+1} + bs + c \rightarrow -\frac{1}{(s+1)^2} \Big|_{s=0} = a \frac{2s(s+1) - s^2}{(s+1)^2} + b + 0 \Big|_{s=0}$$

$$b = -1$$

$$V_{C2S}(t) = 1 \cdot e^{-t} - 1 + 1 \cdot t \quad v, t \geq 0.$$

$$e^t u(t) \rightarrow \frac{1}{s-1}$$

$$V_{C2S}(s) = \frac{1}{(s+1)(s-1)} = \frac{1/2}{s-1} - \frac{1/2}{s+1}$$

$$V_{C2S}(t) = -\frac{1}{2} e^{-t} + \frac{1}{2} \cdot e^t \quad v, t \geq 0$$

$$e^{-t} u(t) \rightarrow \frac{1}{s+1}$$

$$V_{C2S}(s) = \frac{1}{(s+1)^2}$$

$$V_{C2S}(t) = t \cdot e^{-t} \quad v, t \geq 0$$

$$\cos t u(t) \rightarrow \frac{s}{s^2+1}$$

$$V_{C2S}(s) = \frac{s}{(s+1)(s^2+1)} = \frac{a}{s+1} + \frac{b+c}{s^2+1}$$

$$a = \frac{-1}{1+1} = -\frac{1}{2}$$

$$-\frac{1}{2}(s^2+1) + bs^2 + bs + cs + c = s$$

$$(b - \frac{1}{2})s^2 + (b+c)s + (c - \frac{1}{2}) = s$$

$$b = \frac{1}{2} \quad c = \frac{1}{2}$$

$$V_{C2S}(t) = -\frac{1}{2} e^{-t} + \frac{1}{2} \cos t + \frac{1}{2} \sin t \quad v, t \geq 0$$

$$\frac{1}{\sqrt{2}} \cos(t - 45^\circ)$$

$$\cos t u(t) \rightarrow \frac{1}{s^2+1}$$

$$V_{C2S}(s) = \frac{a}{s+1} + \frac{b}{s-j} + \frac{c}{s+j}$$

$$a = -\frac{1}{2}$$

$$b = \frac{s}{(s+1)(s+j)} \Big|_{s=j} = \frac{j}{(j+1)2j} = \frac{1}{2} \cdot \frac{1}{j+1} = \frac{1-j}{4}$$

$$c = \frac{s}{(s+1)(s-j)} \Big|_{s=-j} = \frac{1+j}{4} = b^*$$

$$V_{C2S}(t) = -\frac{1}{2} \cdot e^{-t} + \underbrace{b \cdot e^{jt} + b^* \cdot e^{-jt}}_{2 \operatorname{Re} \{ b e^{jt} \}} = 2 \operatorname{Re} \left\{ \frac{1-j}{2\sqrt{2}} e^{-j45^\circ} e^{jt} \right\} = \frac{1}{\sqrt{2}} \cos(t - 45^\circ)$$

$$e^{Tt} \cdot u(t) \rightarrow \frac{1}{s-T}$$

$$V_{C2S}(s) = \frac{1}{(s+1)(s-T)} = \frac{a}{s+1} + \frac{b}{s-T}$$

$$a = \frac{1}{-1-T} = -\frac{1-T}{2}$$

$$b = \frac{1}{T+1} = \frac{1}{\sqrt{2}} e^{-j45^\circ}$$

$$V_{C2S}(t) = -\frac{1-T}{2} e^{-t} + \frac{1}{\sqrt{2}} e^{-j45^\circ} e^{Tt} \quad v, t \geq 0$$

$$\cos(t) \cdot u(t) = \text{Re} \{ V_{C2S}(t) \} \quad u(t)$$

$$V_R(t) = R \cdot i_2(t)$$

$$V_R(s) = 2 \cdot I_2(s)$$

$$V_L(t) = L \cdot D \cdot i_2(t)$$

$$V_L(s) = L (s I_2(s) - I_0)$$

$$= sL I_2(s) - L I_0$$


$$i_c(t) = C \cdot D V_C(t)$$

$$I_C(s) = C (s V_C(s) - V_0)$$

$$= sC V_C(s) - C V_0$$

$$V_C(s) = \frac{1}{sC} I_C(s) + \frac{V_0}{s}$$

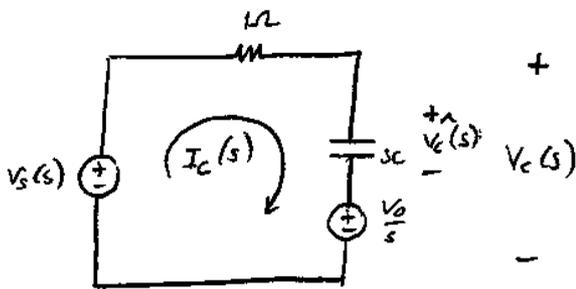
$$\underbrace{\hspace{1cm}}_{\hat{V}_C(s)}$$




$$V_C(s) = \frac{V_0}{s} + \frac{1}{\frac{1}{s} + 1} (V_S(s) - \frac{V_0}{s})$$

$$H(s) = \frac{1}{s+1} \leftarrow \text{a system function}$$

pole / zero diagram

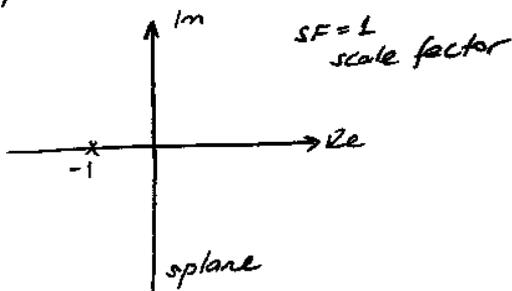

$$H(s) = \frac{3s(s+1)}{s^2+1}$$

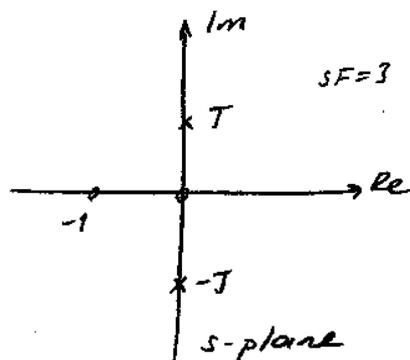


$$H(s) = \frac{P(s)}{Q(s)} \text{ rational function.}$$


real rational function.

$$\text{deg } H = \max \{ \text{deg } P, \text{deg } Q \}$$


$$H(s) = \frac{-4s^2}{(s+2)(s^2+2s+3)}$$

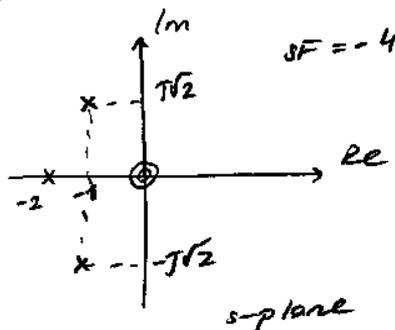

Z

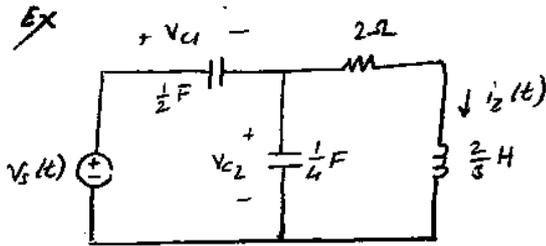

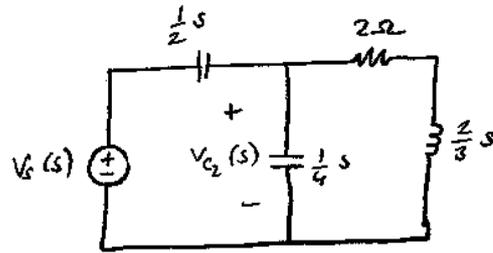at zero-initial state
 $v_s(t) = 4 \cos(2t - 15^\circ)$




$$Z_0 = \frac{4}{s} \parallel \left(2 + \frac{2}{3}s\right)$$

$$V_{c2}(s) = \frac{Z_0}{Z_0 + \frac{2}{s}} v_s(s)$$

$$Z_0 = \frac{\frac{8}{s} + \frac{8}{3}}{\frac{4}{s} + 2 + \frac{2}{3}s}$$

$$= \frac{8 \left(\frac{s}{3} + 1\right)}{4 + 2s + \frac{2s^2}{3}} = \frac{4(s+3)}{s^2 + 3s + 6}$$
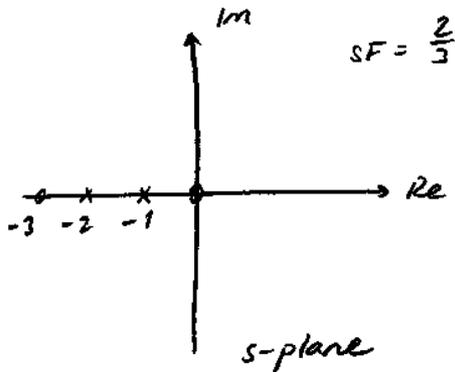
$$V_{c2}(s) = \frac{4(s+3)}{s^2 + 3s + 6} v_s(s) = \underbrace{\frac{2}{3} \frac{s(s+3)}{(s+1)(s+2)}}_{H(s)} v_s(s)$$



$$\frac{s(s+3)}{s^2 + 3s + 2} = 1 - \frac{2}{s^2 + 3s + 2}$$

$$H(s) = \frac{2}{3} - \frac{4}{3} \frac{1}{(s+1)(s+2)}$$

$$= \frac{2}{3} - \frac{4}{3} \frac{1}{s+1} + \frac{4}{3} \frac{1}{s+2}$$

$$h(t) = \frac{2}{3} \delta(t) - \frac{4}{3} e^{-t} + \frac{4}{3} e^{-2t}$$

19.04.2010

Brief Review of Laplace Transform and s-domain Analysis

$$(D^2 + 3D + 2) x(t) = f(t)$$

$$\Downarrow$$

$$\begin{bmatrix} \dot{x}_1(t) \\ \dot{x}_2(t) \end{bmatrix} = \begin{bmatrix} \cdot \\ \cdot \end{bmatrix}_{2 \times 2} \begin{bmatrix} x_1(t) \\ x_2(t) \end{bmatrix} + \begin{bmatrix} \cdot \\ \cdot \end{bmatrix} f(t)$$

$$F(s) = \int_{-\infty}^{\infty} f(t) e^{-st} dt, \quad s \in \text{R.O.C. (for which Laplace transform integral converges)}$$

↳ $s \in C$

$$\mathcal{L}\{f(t)\} = F(s)$$

$$f(t) = \frac{1}{2\pi j} \int_{\sigma-j\infty}^{\sigma+j\infty} F(s) e^{st} ds \quad (s \in \text{ROC})$$

$$\mathcal{L}\{u(t)\} = \int_{-\infty}^{\infty} u(t) e^{-st} dt = \int_0^{\infty} e^{-st} dt = \frac{e^{-st}}{s} \Big|_{t=\infty}^{t=0} = \frac{1}{s}, \quad s > 0$$

$\text{Re}\{s\} > 0$

Two types of Laplace transforms:

① Unilateral

$$F(s) = \int_{0^-}^{\infty} f(t) e^{-st} dt$$

② Bilateral

$$F(s) = \int_{-\infty}^{\infty} f(t) e^{-st} dt$$

↳ more of interest, since we have initial value problems.

$$\mathcal{L}\{f'(t)\} = \int_{0^-}^{\infty} f'(t) e^{-st} dt = \underbrace{e^{-st} f(t) \Big|_{t=0^-}^{\infty}}_{-f(0^-)} + \underbrace{\int_0^{\infty} f(t) s e^{-st} dt}_{sF(s)}$$

$$= sF(s) - f(0)$$

$$\mathcal{L}\{f''(t)\} = s \mathcal{L}\{f'(t)\} - f'(0) = s^2 \mathcal{L}\{f(t)\} - s f(0) - f'(0)$$

$$(D^2 + 3D + 2) v_c(t) = f(t) \longrightarrow u(t)$$

$$v_c(0^-) = v_0$$

$$\dot{v}_c(0^-) = \dot{v}_0$$

Let there be a solution,

$$v_c(t) \iff v_c(s)$$

$$\dot{v}_c(t) \iff s v_c(s) - v_0$$

$$\dot{v}_c'(t) \iff s^2 v_c(s) - s v_0 - \dot{v}_0$$

$$\mathcal{L}\{\alpha f_1(t) + \beta f_2(t)\} = \alpha \mathcal{L}\{f_1(t)\} + \beta \mathcal{L}\{f_2(t)\}$$

$$(D^2 + 3D + 2) v_c(t) \iff v_c(s) [s^2 + 3s + 2] - v_0(s+3) - \dot{v}_0$$

$$= u(t)$$

$$= \frac{1}{s}$$

$$v_c(s) [s^2 + 3s + 2] - v_0(s+3) - \dot{v}_0 = \frac{1}{s}$$

$$v_c(s) = \frac{s(s+3)v_0 + s\dot{v}_0 + 1}{s(s^2 + 3s + 2)}$$

$$2 \{ u(t) \} = \frac{1}{s}$$

$$2 \{ s(t) \} = 1$$

$$2 \{ e^{at} \} = \frac{1}{s-a}$$

$$2 \{ \cos(at) \} = \frac{s}{s^2+a^2}$$

$$2 \{ \sin(at) \} = \frac{a}{s^2+a^2}$$

$$V_c(s) = \frac{s(s+3)V_0 + s\dot{V}_0 + 1}{s(s+1)(s+2)}$$

$$= \frac{A}{s} + \frac{B}{s+1} + \frac{C}{s+2}$$

partial fraction expansion

$$s=0 \rightarrow A = \frac{1}{2}$$

$$s=-1 \rightarrow B = \frac{-2V_0 - \dot{V}_0 + 1}{-1}$$

$$s=-2 \rightarrow C = \frac{-2V_0 - 2\dot{V}_0 + 1}{2}$$

$2^{-1} \{ \}$ of RHS / LHS

$$v_c(t) = \frac{1}{2}u(t) + (2V_0 + \dot{V}_0 - 1)e^{-t} + (-V_0 - \dot{V}_0 + \frac{1}{2})e^{-2t}, t \geq 0$$

Ex

$$F(s) = \frac{s-2}{s(s+1)^2} = \frac{A}{s} + \frac{B}{s+1} + \frac{C}{(s+1)^2}$$

$$2 \{ V_0 \} = \frac{V_0}{s}$$

$$s=0 \rightarrow A = -2$$


$$s=-1 \rightarrow C = 3$$

$$F(s) \cdot (s+1)^2 = \frac{s-2}{s(s+1)^2} (s+1)^2 = \frac{A}{s} (s+1)^2 + B(s+1) + C$$

$$\frac{d}{ds} \left(\frac{2}{s^2} = A \left(1 - \frac{1}{s^2} \right) + B \rightarrow s=-1 \rightarrow B=2 \right)$$

Circuit Response Using s-Domain Methods

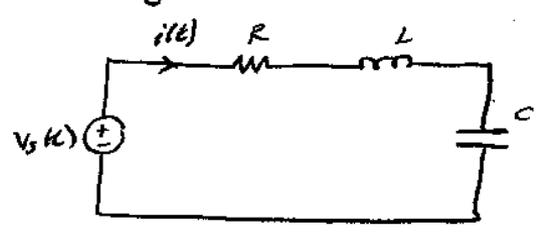① Taking Laplace Transform of Time-Domain Relation:



$$v_c(0^-) = V_0$$

$$i_L(0^-) = I_0$$

$$\text{KVL: } -v_s(t) + R i(t) + L \frac{d}{dt} i(t) + v_c(0^-) + \frac{1}{C} \int_0^t i(\tau) d\tau = 0$$

(LST)

$$-V_s(s) + R \cdot I(s) + L(sI(s) - I_0) + \frac{V_0}{s} + \frac{1}{C} \cdot \frac{I(s)}{s} = 0$$

$$I(s) = \frac{Cs V_s(s) + sLC I_0 - CV_0}{s^2 LC + RCs + 1}$$




$$I(s) = \frac{\frac{sV_s(s)}{L}}{s^2 + \frac{R}{L}s + \frac{1}{LC}} + \frac{sI_0 - \frac{1}{L}V_0}{s^2 + \frac{R}{L}s + \frac{1}{LC}}$$

$i(t)$: complete solution. = $i^{zs}(t) + i^{zi}(t)$

22.04.2010

Circuit Response using Laplace Transform

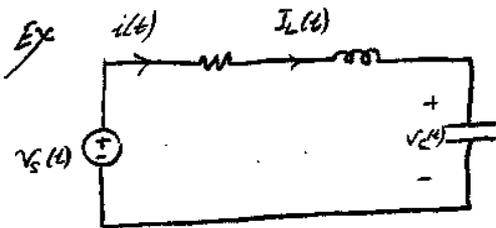

$$v_C(0^-) = V_0$$

$$i_L(0^-) = I_0$$

$$I(s) = \underbrace{\frac{sI_0 - V_0/L}{s^2 + \frac{R}{L}s + \frac{1}{LC}}}_{zi} + \underbrace{\frac{sV_s(s)/L}{s^2 + \frac{R}{L}s + \frac{1}{LC}}}_{zs}$$

① Let $L = 4H$; $R = 6\Omega$; $C = 0.04F$
 $I_0 = 5A$; $V_0 = 1V$

$$I(s) = \frac{sV_s(s)}{s^2 + 6s + 25} + \frac{5s - 1}{s^2 + 6s + 25} \quad (*)$$

Also let $v_s(t) = 12 \sin(5t)$ $t \geq 0$

$$\rightarrow v_s(s) = 2 \{ 12 \sin(5t) \} = \frac{60}{s^2 + 25}$$

$$I(s) = \frac{60s}{(s^2 + 6s + 25)(s^2 + 25)} + \frac{5s - 1}{s^2 + 6s + 25}$$

$$\hookrightarrow (s+3)^2 + 16 = (s+3+j4)(s+3-j4)$$

$$I^{zs}(s) = \frac{60s}{(s^2 + 6s + 25)(s^2 + 25)}$$

$$= \frac{K_1}{s+3+j4} + \frac{K_1^*}{s+3-j4} + \frac{K_2}{s+j5} + \frac{K_2^*}{s-j5}$$

$$K_1 = \frac{60s}{(s+3-j4)(s+j5)(s-j5)} \Big|_{s=-3-j4} = -j1.25$$

$$K_2 = I^{zs}(s) \cdot (s+j5) \Big|_{s=-j5} = j$$

$$I^{zs}(s) = \frac{J_{1,25}}{s+3-j4} + \frac{-j_{1,25}}{s+3+j4} + \frac{-j}{s-j5} + \frac{j}{s+j5}$$

$$I^{zs}(s) = \frac{-10}{(s+3)^2+16} + \frac{10}{s^2+25}$$

$$\mathcal{L}^{-1}\{I^{zs}(s)\} = i^{zs}(t) = \underbrace{-\frac{5}{2} e^{-3t} \sin(4t)}_{\text{transient part for z.s. solution}} + \underbrace{2 \sin(5t)}_{\text{steady state part of zero state response}}$$

transient part for z.s. solution

steady state part of zero state response

$$\mathcal{L}^{-1}\{I^{zs}(s)\} = i^{zs}(t) = j_{1,25} e^{-(3-j4)t} - j_{1,25} e^{-(3+j4)t} - j e^{j5t} + j e^{-j5t}$$

$$= 2 \operatorname{Re} \left\{ j_{1,25} e^{-(3-j4)t} \right\} + 2 \operatorname{Re} \left\{ -j e^{j5t} \right\}$$

$$= \frac{j_{1,25}^*}{2} \operatorname{Re} \left\{ e^{j(4t+90^\circ)} \right\} - 2 \operatorname{Re} \left\{ e^{j(5t+90^\circ)} \right\}$$

$\cos(4t+90^\circ)$ $\cos(5t+90^\circ)$

$$I^{zi}(s) = \frac{5s-1}{(s+3)^2+4^2} = \frac{k_1}{s+3+j4} + \frac{k_1^*}{s+3-j4}$$

$$k_1 = \frac{5s-1}{s+3-j4} \Big|_{s=-3-j4} = \frac{-16-j20}{-j8} = \frac{20-j16}{8} = \frac{5}{2} - j2$$

$$i^{zi}(t) = 2 \operatorname{Re} \left\{ k_1 e^{-(3+j4)t} \right\} = 2 e^{-3t} \operatorname{Re} \left\{ \left(\frac{5}{2} - j2 \right) (\cos 4t - j \sin 4t) \right\}$$

$$= 2 e^{-3t} \left[\frac{5}{2} \cos(4t) - 2 \sin(4t) \right]$$

$$= 2 e^{-3t} \sqrt{\frac{25}{4} + 4} \cos \left(4t - \tan^{-1} \frac{-2}{5/2} \right)$$

② Step response: (Zero-state response for $u(t)$ input)

Same values for R, L, C etc.

$$I^{zs}(s) = \frac{s V_s(s)}{s^2+6s+25} \leftarrow 2 \{u(t)\} = 1/s = V_s(s)$$

$$I^{zs}(s) = \frac{1}{(s+3)^2+4^2} = \frac{1}{4} e^{-3t} \sin(4t)$$

③ Impulse response:

$$I^{zs}(s) = \frac{s V_s(s)}{s^2+6s+25} \xrightarrow{2 \{ \delta(t) \} = 1}$$

$$= \frac{s}{(s+3)^2+4^2} = \frac{s+3}{(s+3)^2+4^2} + \frac{-3}{(s+3)^2+4^2} = e^{-3t} \cos(4t) - \frac{3}{4} e^{-3t} \sin(4t)$$


Poles and zeros in S-domain

$$I^{zs}(s) = K \cdot \frac{\prod_{k=1}^Z (s - z_k)}{\prod_{k=1}^P (s - p_k)}$$



a ratio of two polynomials
in "s domain" $\{ I^{zs}(t) \}$

p_k : Poles of $I^{zs}(s)$ (singularities)







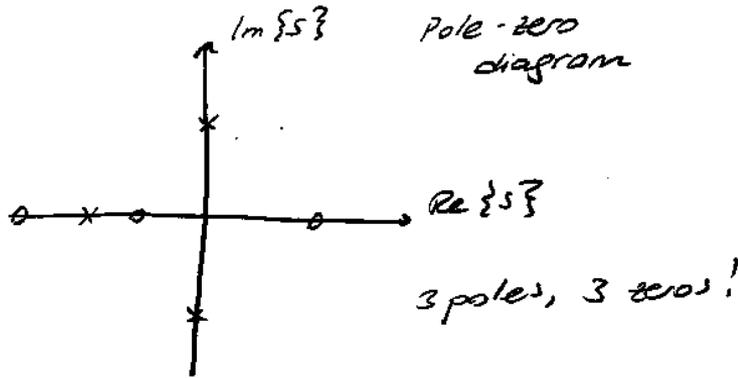
z_k : zeros of $I^{zs}(s)$ ($I^{zs}(z_k) = 0$)



Ex

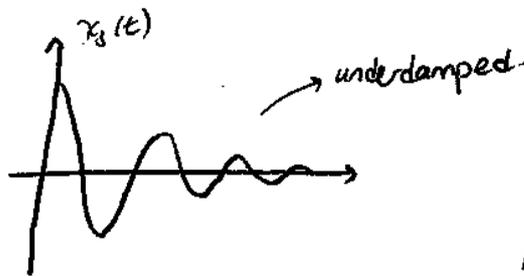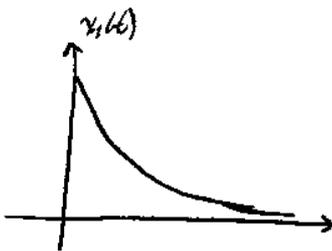

monomert
monomert

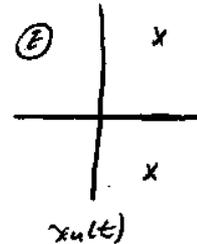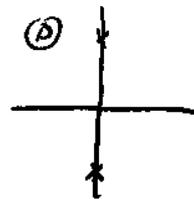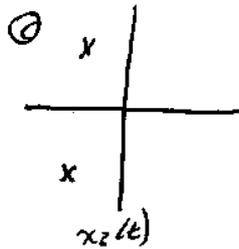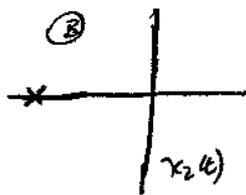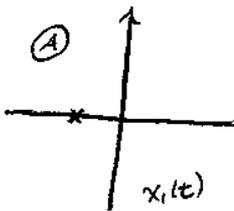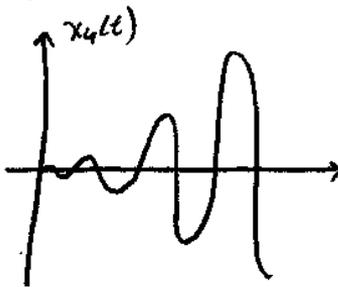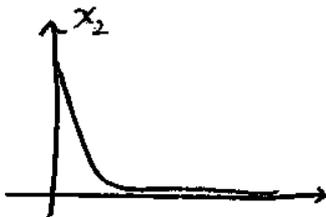

distance to $\text{Im}\{s\}$ determines how fast it decay and distance to $\text{Re}\{z\}$ its frequency.

Initial and Final Value Theorems

Initial Value: $\lim_{t \rightarrow 0^+} f(t) = \lim_{s \rightarrow \infty} s F(s)$

Final Value: $\lim_{t \rightarrow \infty} f(t) = \lim_{s \rightarrow 0} s F(s)$

Exo Step response:

$i^{zs}(t) = \frac{1}{4} e^{-3t} \sin 4t \xrightarrow{\mathcal{L}\{ \cdot \}} I^{zs}(s) = \frac{1}{s^2 + 6s + 25}$

$i^{zs}(0^+) = 0 \quad \lim_{s \rightarrow \infty} s I^{zs}(s) = 0 \quad \rightarrow$ initial value theorem

$i^{zs}(\infty) = 0 \quad \lim_{s \rightarrow 0} s I^{zs}(s) = 0 \quad \rightarrow$ final value theorem

Some important details

To use initial value theorem $s = \infty$ should be in R.O.C.


Final value theorem $s = 0$

$2 \{ \cos(\beta t) \} = \frac{s}{s^2 + \beta^2} \xrightarrow{\text{final value theorem}} \lim_{s \rightarrow 0} s \frac{s}{s^2 + \beta^2} = 0$

but $\lim_{t \rightarrow \infty} \cos \beta t$ does not exist.


do not never forget R.O.C. when I_s is discussed.

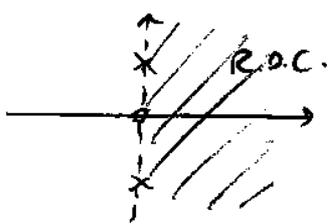$2 \{ \cos \beta t \} = \int_0^{\infty} \cos \beta t \cdot e^{-st} dt$ has R.O.C.



Circuit Components in s-domain

Capacitor:


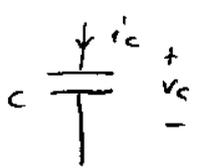



time domain
 $i_c(t) = C \frac{dv_c(t)}{dt}$

s-domain

$I_c(s) = Cs V_c(s) - C V_c(0^-)$

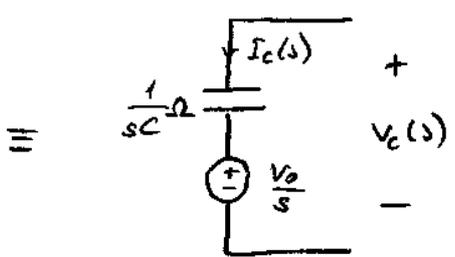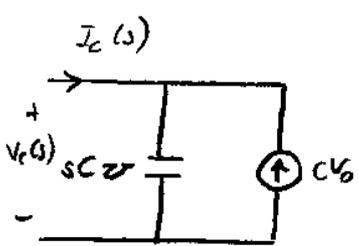$V_c(s) = \frac{I_c(s)}{Cs} + \frac{V_0}{s}$




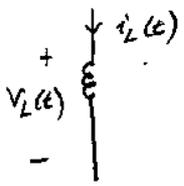


$$V_L(t) = L \cdot \frac{di_L(t)}{dt}$$

$$i_L(0^-) = I_0$$


$$V_L(s) = sL I_L(s) - L \cdot I_0$$

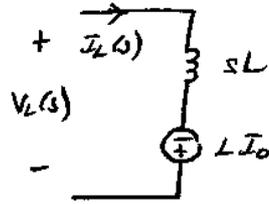
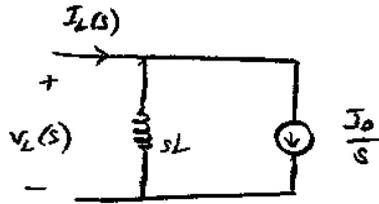
$$I_L(s) = \frac{V_L(s)}{sL} + \frac{I_0}{s}$$




Ex

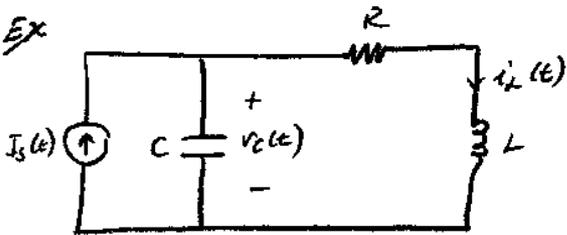


$$V_C(0^-) = V_0$$

$$I_L(0^-) = I_0$$

↓ s domain

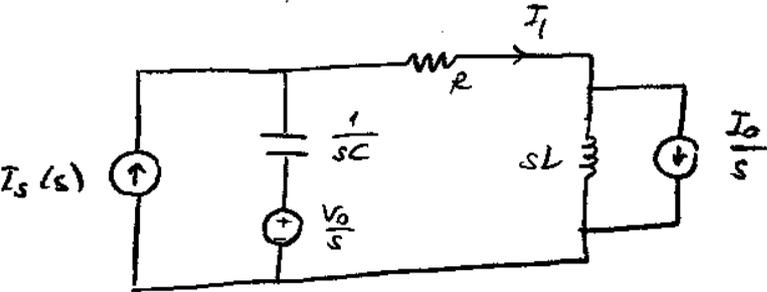

zero-state:

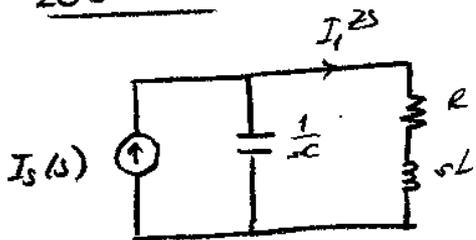


$$I_1^{zs}(s) = I_S(s) \frac{\frac{1}{sC}}{\frac{1}{sC} + sL + R}$$

$$= \frac{1}{LCs^2 + sRC + 1} I_S(s)$$

$$= \frac{1/LC}{s^2 + \frac{R}{L}s + \frac{1}{LC}} I_S(s)$$

zero-input

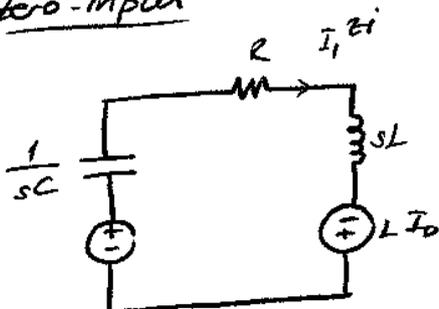

$$I_1^{zi}(s) = \frac{\frac{V_0}{s} + L I_0}{\frac{1}{sC} + R + sL} = \frac{\frac{V_0}{L} + s I_0}{s^2 + \frac{R}{L}s + \frac{1}{LC}}$$

Zero-state:

$$I_1(s) = \frac{1/LC}{s^2 + \frac{R}{L}s + \frac{1}{LC}} I_s(s) \rightarrow (s^2 + \frac{R}{L}s + \frac{1}{LC}) I_1(s) = \frac{I_s(s)}{LC}$$

(L⁻¹?)


$$(D^2 + \frac{R}{L}D + \frac{1}{LC}) i_1^{zs}(t) = \frac{i_s(t)}{LC}$$

$$i_1^{zs}(0^-) = 0 ; \frac{d}{dt} i_1^{zs}(0) = 0$$


natural freq: roots of char. polynomial.

poles of $I_1^{zs}(s)$ solution $I_1^{zs}(s) = \frac{1/LC I_s(s)}{s^2 + \frac{R}{L}s + \frac{1}{LC}}$

Ex Mesh Analysis in S-domain

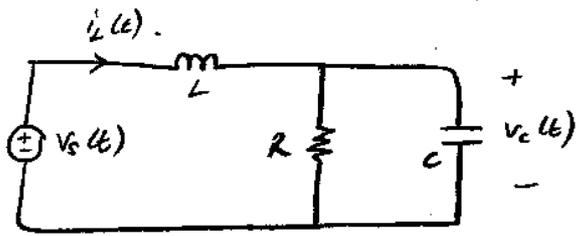

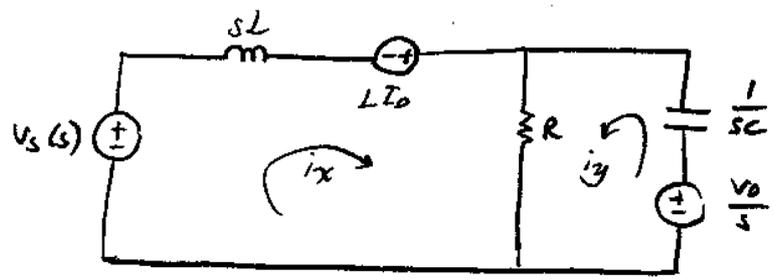S domain $\left\{ \begin{array}{l} i_L(0^-) = I_0 \\ v_C(0^-) = V_0 \end{array} \right.$



$$\begin{bmatrix} sL + R & R \\ sCR & 1 + sRC \end{bmatrix} \begin{bmatrix} i_x(s) \\ i_y(s) \end{bmatrix} = \begin{bmatrix} V_s(s) + LI_0 \\ CV_0 \end{bmatrix}$$

$$i_x(s) = \frac{\begin{vmatrix} V_s(s) + LI_0 & R \\ CV_0 & 1 + sRC \end{vmatrix}}{\begin{vmatrix} sL + R & R \\ sRC & 1 + sRC \end{vmatrix}} = \frac{(V_s(s) + LI_0)(1 + sRC) - RCV_0}{s^2 RLC + sL + R}$$

$$= \frac{\frac{V_s(s)}{RCL} (1 + sRC) + \left(\frac{LI_0}{RC} - \frac{RCV_0}{L} \right) + sRC I_0}{s^2 RLC + \frac{sL}{RC} + \frac{R}{LC}}$$

$$I_X(s) = \frac{\left(\frac{1}{RC} + \frac{s}{L}\right)}{s^2 + \frac{1}{RC}s + \frac{1}{LC}} V_S(s) + \frac{\frac{I_0}{RC} - \frac{V_0}{L} + sI_0}{s^2 + \frac{1}{RC}s + \frac{1}{LC}}$$

Let $R = 8\Omega$, $L = 6H$, $C = \frac{1}{48}F$

$$I_X(s) = \frac{1 + s/6}{s^2 + 6s + 8} V_S(s) + \frac{6I_0 - \frac{V_0}{6} + sI_0}{s^2 + 6s + 8}$$

↓

$$-\frac{1}{2} \left(2I_0 - \frac{V_0}{6} \right) \frac{1}{s+4} + \frac{1}{2} \left(4I_0 - \frac{V_0}{6} \right) \frac{1}{s+2}$$

$$I_X^{21}(s) = \frac{\frac{V_0}{12} - I_0}{s+4} + \frac{2I_0 - \frac{V_0}{12}}{s+2}$$

$$I_X^{25}(s) = \frac{1 + s/6}{s^2 + 6s + 8} V_S(s)$$

→ Assume we have zero input case, find initial conditions to excite the mode with $\lambda = -2$.

$$i_X^{21}(t) = \left[\left(\frac{V_0}{12} - I_0 \right) e^{-4t} + \left(2I_0 - \frac{V_0}{12} \right) e^{-2t} \right] u(t)$$

then $V_0 = 12I_0$ $\begin{bmatrix} V_0 \\ I_0 \end{bmatrix} = \alpha \begin{bmatrix} 12 \\ 1 \end{bmatrix} \rightarrow$ excites $\lambda = -2$ mode only.

→ Assume $V_S(t) = 16 \cos 2t u(t)$ find $i_X^{25}(t)$.

$$I_X^{25}(s) = \frac{1 + s/6}{s^2 + 6s + 8} \cdot \frac{16s}{s^2 + 4}$$

$$= \frac{\frac{2/3(-32)}{2 \cdot 8}}{s+2} + \frac{\frac{1/3 \cdot 16(-4)}{-2 \cdot 20}}{s+4} + \frac{As+B}{s^2+4}$$


$$s=0 \rightarrow 0 = -\frac{2}{3} + \frac{2}{15} + \frac{B}{4} \rightarrow B = \frac{32}{15}$$

$$\frac{8}{3} = \frac{-16}{3} + \frac{16}{5} + B + 6A \rightarrow A = \frac{16}{3}$$

$$I_X^{25}(s) = \frac{-4/3}{s+2} + \frac{8/15}{s+4} + \frac{16/3 s + 32/15}{s^2+4}$$

$$i_X^{25}(t) = -\frac{4}{3} e^{-2t} + \frac{8}{15} e^{-4t} + \frac{16}{3} \cos(2t) + \frac{16}{15} \sin(2t)$$

Coupled Inductor

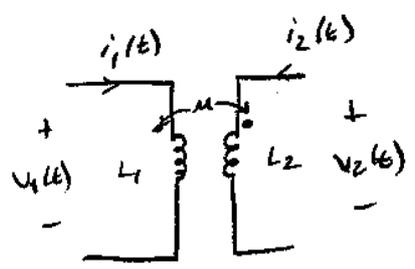


$$\begin{bmatrix} v_1(t) \\ v_2(t) \end{bmatrix} = \begin{bmatrix} L_1 & M \\ M & L_2 \end{bmatrix} \begin{bmatrix} \dot{i}_1(t) \\ \dot{i}_2(t) \end{bmatrix}$$

$$i_1(0^-) = I_1$$

$$i_2(0^-) = I_2$$

$$\begin{bmatrix} v_1(s) \\ v_2(s) \end{bmatrix} = \begin{bmatrix} L_1 & M \\ M & L_2 \end{bmatrix} \begin{bmatrix} s I_1(s) - I_1 \\ s I_2(s) - I_2 \end{bmatrix}$$

Transformer:

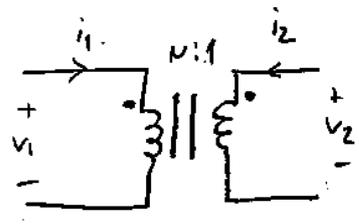

$$\frac{i_1(t)}{i_2(t)} = -\frac{1}{N} \quad \frac{v_1(t)}{v_2(t)} = N$$

$$\frac{I_1(s)}{I_2(s)} = -\frac{1}{N} \quad \frac{V_1(s)}{V_2(s)} = N$$

Network Functions



$$H(s) = \frac{\mathcal{L}\{y^{zs}(t)\}}{\mathcal{L}\{x(t)\}}$$

output at zero-state

network function

input

Let $\frac{I_L^{zs}(s)}{V_s(s)} = \frac{s}{s+1} \rightarrow (s+1) I_L^{zs}(s) = V_s(s) \cdot s$

} $z^{-1}\{ \}$?

$(D+1) i_L^{zs}(t) = \frac{d}{dt} v_s(t)$

output (unknown)

input




$$\frac{\mathcal{L}\{y_3^{zs}(t)\}}{\mathcal{L}\{x_3(t)\}} = H(s)$$

$$\begin{aligned} \mathcal{L}\{y_3^{zs}(t)\} &= H(s) \mathcal{L}\{x_3(t)\} \\ &= H(s) \cdot \mathcal{L}\{\alpha x_1(t)\} + H(s) \mathcal{L}\{\beta x_2(t)\} \\ &= \mathcal{L}\{y_1^{zs}(t) + y_2^{zs}(t)\} \end{aligned}$$

The ZS solutions obey the superposition principle so ZS solution can be found by superposition method.

If initial conditions are non-zero, they should be treated separately by ZI solution.

Ex

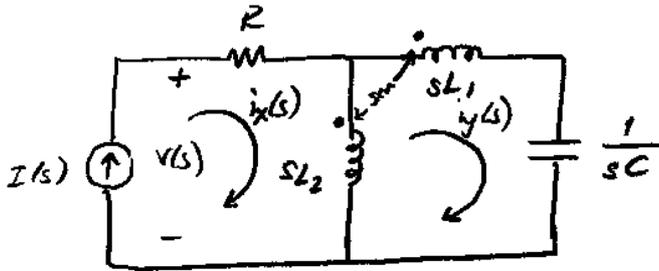

Note that no initial conditions since network functions are always expressed in ZS.

$$Z(s) = \frac{V(s)}{I(s)}$$

$$I_x(s) = I(s)$$

$$V(s) = R \cdot I(s) + sL_2 (I(s) - I_y(s)) + sM \cdot I_y(s)$$

KVL: $-V_{L2} + V_{L1} + I_y(s) \cdot \frac{1}{sC} = 0$

$$- (sL_2 (I(s) - I_y(s)) + sM I_y(s))$$


$$+ (sL_1 I_y(s) + sM (I(s) - I_y(s))) + \frac{I_y(s)}{sC} = 0$$

Find $I_y(s)$ in terms of $I(s)$.

Replace $I_y(s)$ in the output relation and express output in terms of $I(s)$ (input)





$$Z(s) = \frac{V(s)}{I(s)} = \frac{R + s^2 2C(L_1 + L_2 - 2M) - s^3 \dots}{s^2 C(L_1 + L_2 - 2M) + 1}$$

Network Functions

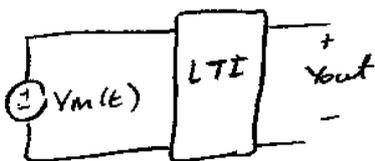

$$H_V(s) = \frac{V_{out}(s)}{V_{in}(s)}$$

↓
voltage transfer function.

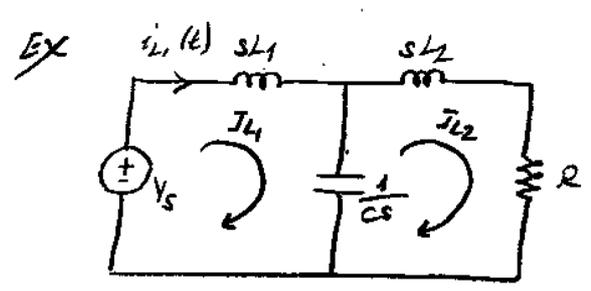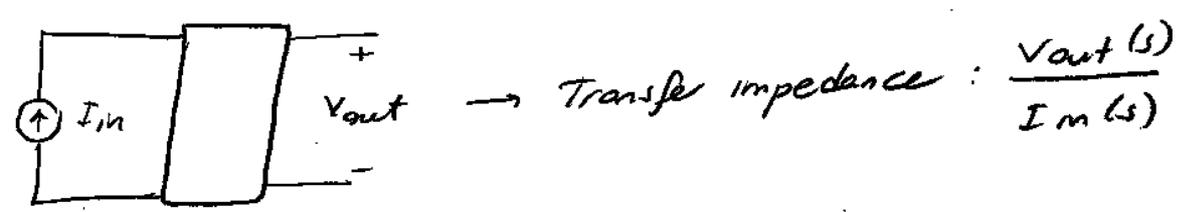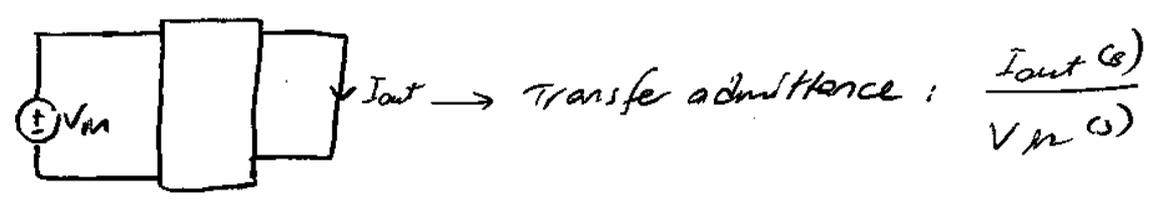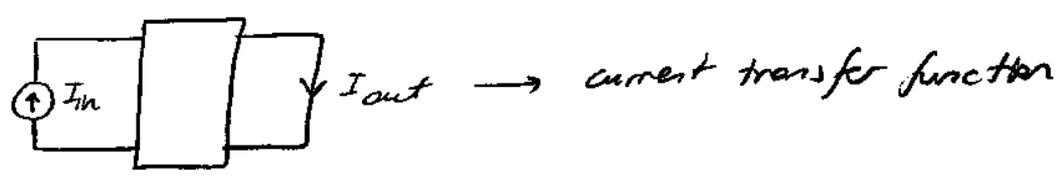


Find $\frac{I_{L1}(s)}{V_s(s)}$

KVL: $-V_s(s) + I_{L1}(s) \left(sL_1 + \frac{1}{sC} \right) - I_{L2} \frac{1}{sC} = 0$
 $-I_{L1}(s) \cdot \frac{1}{sC} + I_{L2}(s) \left(sL_2 + R + \frac{1}{sC} \right) = 0$

$$\begin{bmatrix} sL_1 + \frac{1}{sC} & -\frac{1}{sC} \\ -\frac{1}{sC} & \frac{1}{sC} + sL_2 + R \end{bmatrix} \begin{bmatrix} I_{L1} \\ I_{L2} \end{bmatrix} = \begin{bmatrix} V_s(s) \\ 0 \end{bmatrix}$$

$$I_{L1}(s) = \frac{V_s(s) \cdot \left(\frac{1}{sC} + sL_2 + R \right)}{\frac{L_1}{C} + s^2 L_1 L_2 + s R L_1 + \frac{L_2}{C} + \frac{R}{sC}}$$


Network Functions and Impulse Response:

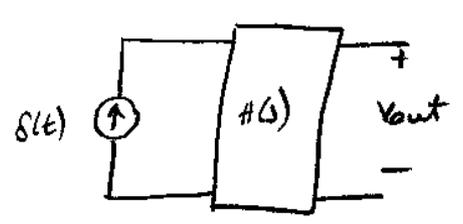

$V_{out}(s) = H(s) \cdot \mathcal{L}\{s(t)\}$

$V_{out}(s) = H(s)$

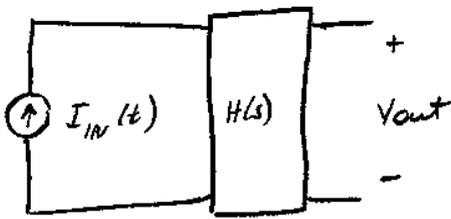$H(s) = \mathcal{L}\{V_{out}(t) \text{ for } s(t) \text{ input}\}$
 ↓
 impulse response



$$V_{out}(s) = H(s) \cdot I_{in}(s)$$


$\mathcal{L}^{-1}\{\}$
 ↓
 impulse response in s domain.

$$V_{out}(t) = \int_{-\infty}^{\infty} h(\tau) \cdot I_{in}(t-\tau) d\tau \quad \leftarrow \text{convolution}$$

$$V_{out}(t) = h(t) * I_{in}(t)$$

↓
convolution

About the integral:

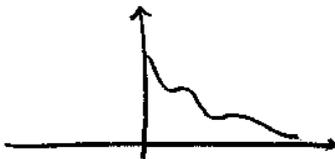

$$h(t) = 0 \quad t < 0$$

$I_{in}(t)$ is given for $t > 0$.


$$I_{in}(t) = 0 \quad t < 0$$

$$V_{out}(t) = \int_{-\infty}^{\infty} h(\tau) I_{in}(t-\tau) d\tau = \int_{-\infty}^0 \dots + \int_0^t \dots + \int_t^{\infty} \dots$$

\swarrow $h(\tau) = 0$ \searrow $I_{in}(t-\tau) = 0$

$$V_{out}(t) = \int_0^t h(\tau) I_{in}(t-\tau) d\tau \quad \left(\text{for causal systems} \right)$$

Step Response

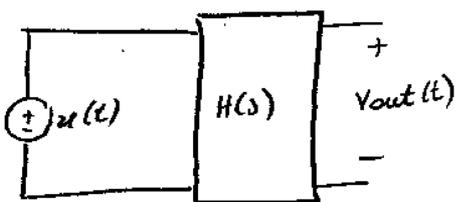

$$V_{out}(s) = H(s) \cdot V_{in}(s)$$

$$\mathcal{L}\{u(t)\} = \frac{1}{s}$$

$$V_{out}(s) = H(s) \cdot \frac{1}{s}$$

$$\mathcal{L}^{-1}\{\} \rightarrow V_{out}^{step}(t) = \mathcal{L}^{-1}\left\{ \frac{H(s)}{s} \right\} = \int_0^t h(\tau) d\tau$$

↓
impulse response


or by convolution:

$$V_{out}^{step} = \int_{-\infty}^{\infty} h(\tau) v_{in}(t-\tau) d\tau = \int_0^t h(\tau) u(t-\tau) d\tau$$

\swarrow $u(t-\tau) = 1$

$$= \int_0^t h(\tau) d\tau$$

Ex

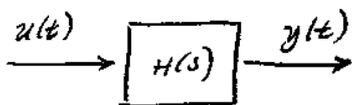

$$H(s) = \frac{1}{(s+2)(s+3)} = \frac{V_{out}^{zs}(s)}{V_{in}(s)}$$

$$(s+2)(s+3) V_{out}^{zs}(s) = V_{in}(s)$$

$$(D+2)(D+3) V_{out}^{zs}(t) = V_{in}(t)$$


$$V_{out}^{step}(s) = H(s) \cdot \frac{1}{s}$$

$$= \frac{1}{(s+2)(s+3) \cdot s} = \frac{-1/2}{s+2} + \frac{+1/3}{s+3} + \frac{1/6}{s}$$


response due to natural frequencies

response due to external input
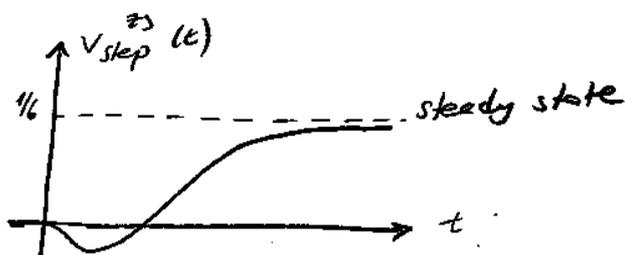
$$V_{out}(t) = -\frac{1}{2} e^{-2t} + \frac{1}{3} e^{-3t} + \frac{1}{6}$$



Sinusoidal Steady State Response

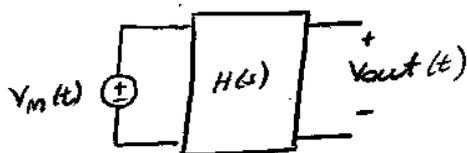

$$V_{in}(t) = A \cdot \cos(\omega t + \phi)$$

$$H(s) = \frac{V_{out}(s)}{V_{in}(s)}$$

$$2 \{ V_{in}(t) \} = 2 \{ A \cdot \cos(\omega t + \phi) \}$$

$$= A \cdot \cos \phi \cdot 2 \{ \cos \omega t \} - A \sin \phi \cdot 2 \{ \sin \omega t \}$$

$$= A \cos \phi \frac{s}{s^2 + \omega^2} - A \sin \phi \frac{\omega}{s^2 + \omega^2} = \frac{A}{s^2 + \omega^2} (s \cos \phi - \omega \sin \phi)$$

$$V_{out}(s) = H(s) \cdot V_{in}(s) = H(s) \cdot \left[A \cdot \frac{s \cos \phi - \omega \sin \phi}{s^2 + \omega^2} \right]$$

$$= \underbrace{\frac{K}{s - j\omega} + \frac{K^*}{s + j\omega}}_{\text{due to sinusoidal input}} + \underbrace{\frac{A_1}{s - \lambda_1} + \frac{A_2}{s - \lambda_2} + \dots + \frac{A_N}{s - \lambda_N}}_{\text{resp. of nat. freq.}}$$

due to sinusoidal input.

λ_i are the poles of $H(s)$; they are natural frequencies

Let's focus on the response due to sinusoidal input : $K = ?$

$$K = \left(H(s) A \cdot \frac{s \cos \phi - \omega \sin \phi}{s + j\omega} \right) \Bigg|_{s=j\omega}$$


$$K = H(j\omega) \cdot A \cdot \frac{j\omega \cos \phi - \omega \sin \phi}{2j\omega}$$

$$= H(j\omega) \frac{A}{2} [\cos \phi + j \sin \phi] = H(j\omega) \cdot \frac{A}{2} e^{j\phi}$$


$$\begin{aligned} \mathcal{L}^{-1} \left\{ \frac{K}{s-j\omega} + \frac{K^*}{s+j\omega} \right\} &= K \cdot e^{j\omega t} + K^* \cdot e^{-j\omega t} = 2 \operatorname{Re} \left\{ K e^{j\omega t} \right\} \\ &= 2 \operatorname{Re} \left\{ |K| \cdot e^{j(\omega t + \angle K)} \right\} \\ &= 2|K| \cdot \cos(\omega t + \angle K) \end{aligned}$$

$$\mathcal{L}^{-1} \left\{ \frac{K}{s-j\omega} + \frac{K}{s+j\omega} \right\} = A \cdot |H(j\omega)| \cdot \cos(\omega t + \phi + \angle H(j\omega))$$


the output at steady state
(free of natural response terms)

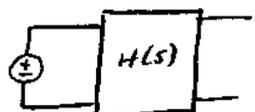$A \cos(\omega t + \phi)$  $v_{out}^{ss} = A \cdot |H(j\omega)| \cos(\omega t + \phi + \angle H(j\omega))$

Ex/

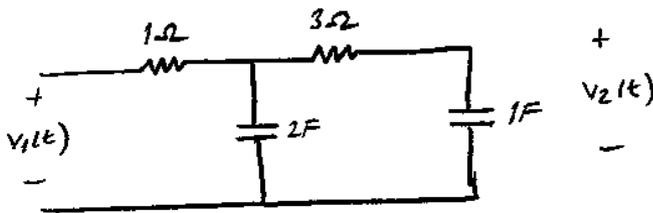

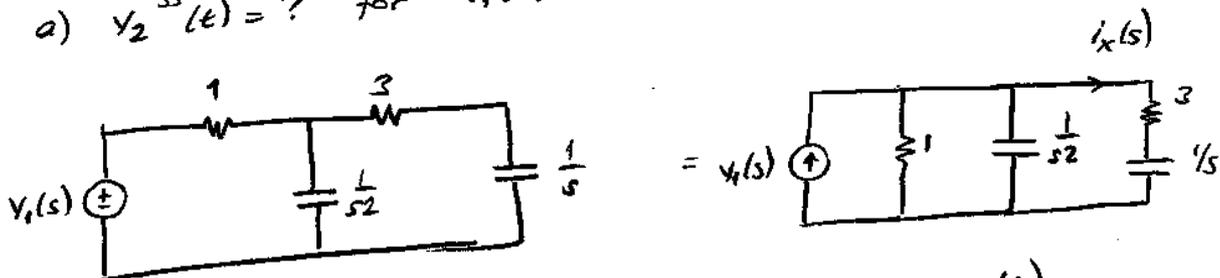a) $v_2^{ss}(t) = ?$ for $v_1(t) = 4 \cos\left(\frac{1}{2}t + 30^\circ\right)$



$$i_x(s) = \frac{1 / \frac{1}{s} + 3}{1 + s^2 + \frac{1}{\frac{1}{s} + 3}} \cdot v_1(s) = \frac{s}{(3s+2)(2s+1) + s} \cdot v_1(s)$$


$$v_2(s) = i_x(s) \cdot \frac{1}{s} = \frac{v_1(s)}{6s^2 + 6s + 1} = \underbrace{\frac{1/6}{s^2 + 3s + \frac{1}{6}}}_{H(s)} v_1(s)$$

a) If input is $4 \cos(\frac{1}{2}t + 30^\circ) \rightarrow v_{out} = 4 |H(j\frac{1}{2})| \cos(\frac{1}{2}t + 30^\circ + \angle H(j\frac{1}{2}))$ 75

$$H(j\frac{1}{2}) = \frac{1/6}{-\frac{1}{4} + j\frac{1}{2} + \frac{1}{6}} = \frac{1}{-\frac{1}{2} + j3} = \frac{1}{\sqrt{9 + \frac{1}{4}}} e^{j(180^\circ + \tan^{-1} 3/0.5)}$$

If $1 \cos(\frac{1}{2}t + 30^\circ) \rightarrow \boxed{H(s)} \rightarrow \frac{8}{\sqrt{37}} \cos(\frac{1}{2}t - 150^\circ + \tan^{-1} 6)$

FREQUENCY RESPONSE

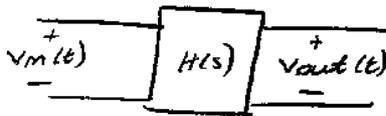





$$v_{in}(t) = A_{in} \cos(\omega t + \phi_{in})$$

$$v_{out}(t) = A_{in} |H(j\omega)| \cos(\omega t + \phi_{in} + \angle H(j\omega))$$


at the output, magnitude is multiplied by $|H(j\omega)|$

Gain function: $|H(j\omega)|$ (Magnitude Response)

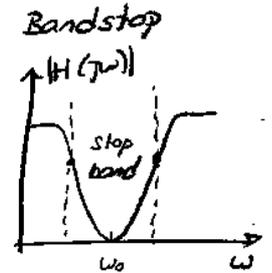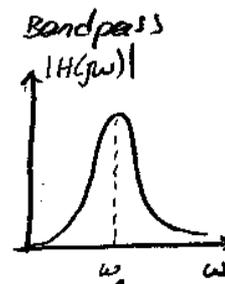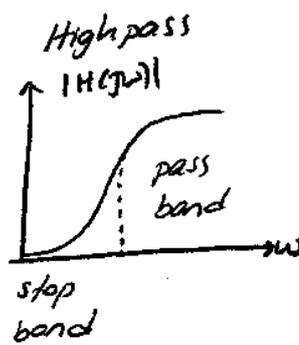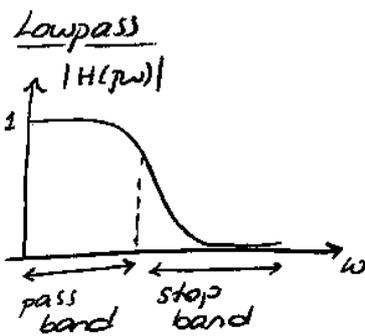Phase function: $\angle H(j\omega)$ (Phase Response)




Decibel

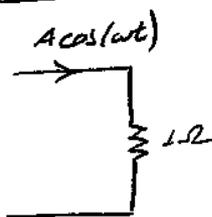

$$P_{1\Omega}^{AVG} = \frac{A^2}{2} R \quad R = 1\Omega$$

square of RMS of $A(\cos \omega t)$

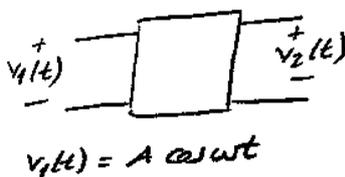


The avg. power at the input is $A^2/2$.
= AVG power dissipated over 1Ω resistor.

Decibel: $10 \log_{10} \left(\frac{\text{Power at the output}}{\text{Power at the input}} \right)$

$$10 \log_{10} \left(\frac{|A(H(j\omega))|^2 \cdot R}{\frac{A^2}{2} \cdot R} \right) = 10 \log_{10} (|H(j\omega)|^2) \text{ dB}$$

Low-pass

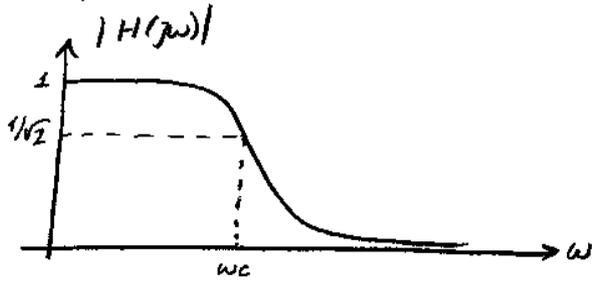

dB: ded Bell
↳ Graham Bell

↳ cut-off, half power, critical, -3dB
freq freq freq freq

$ H(j\omega) ^2$	dB ($10 \log_{10} H(j\omega) ^2$)
1	0
2	3
3	4.77
4	6
5	7
7	8.45
8	9
9	9.54
10	10

$$10 \log_{10} 3 = \frac{10}{4} \log_{10} 3^4$$

$$\approx \frac{10}{4} \log_{10} 80 \approx 8 \times 10$$

dB: $10 \log_{10} |H(j\omega)|^2 = 20 \log_{10} |H(j\omega)|$

Remember that dB is related to power quantities.

Frequency response of 1st order circuits


a) Lowpass

$$H(s) = \frac{K}{s + \alpha}$$

$$\frac{Y(s)}{X(s)} = \frac{K}{s + \alpha}$$

$$sY(s) + \alpha Y(s) = K X(s)$$
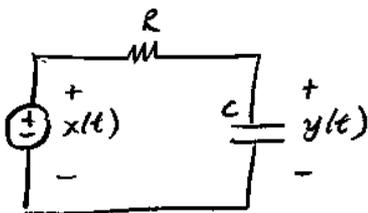
$$\frac{d}{dt} y(t) + \alpha y(t) = K x(t)$$



$$-x(t) + (C \cdot y(t))' R + y(t) = 0$$

$$y(t) + \frac{1}{RC} y(t) = \frac{1}{RC} x(t)$$


$$|H(j\omega)| = \left| \frac{K}{\alpha + j\omega} \right| = \frac{|K|}{\sqrt{\alpha^2 + \omega^2}}$$

$$\angle H(j\omega) = \angle \left(\frac{K}{\alpha + j\omega} \right) = \angle K - \tan^{-1} \frac{\omega}{\alpha}$$

K is real number, but when $K < 0 \rightarrow \angle K = 180^\circ$

$$|H(j\omega)| = \frac{|K|}{\omega \sqrt{1 + (\frac{\alpha}{\omega})^2}} = \frac{|K|}{|\alpha| \sqrt{1 + (\frac{\omega}{\alpha})^2}}$$

$$|H(j\omega)| \approx \begin{cases} \frac{|K|}{|\alpha|} & \omega \ll |\alpha| \\ \frac{|K|}{\omega} & \omega \gg |\alpha| \end{cases} \quad (\omega = 10\alpha) \rightarrow \text{an order of magnitude more than } \alpha.$$

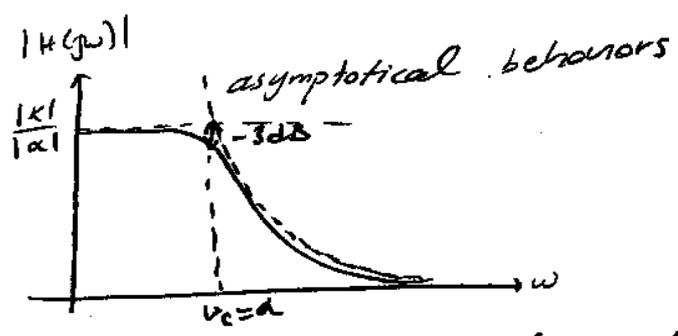

-3dB freq: A special freq at which $|H(j\omega)|$ is $1/\sqrt{2}$ times $|H(j\omega)|_{max}$.

$$\max |H(j\omega)| = \frac{|K|}{|\alpha|} \quad (\omega = 0)$$

$$\frac{\max |H(j\omega)|}{\sqrt{2}} = \frac{|K|}{|\alpha| \sqrt{1 + (\frac{\alpha}{\alpha})^2}} = \frac{|K|}{|\alpha| \sqrt{2}} \rightarrow \omega_c = \alpha$$


Interestingly the point where two graphs meet is the critical frequency


low frequency asymptote: $\frac{|K|}{|\alpha|}$
 high frequency asymptote: $\frac{|K|}{\omega}$
 } They are equal for $\omega = \alpha$

In magnitude response plots, we use dB scale and that changes the plot with linear scale that follows.

dB scale \rightarrow Matlab notation loglog scale


$$H(s) = \frac{100}{s+20}$$

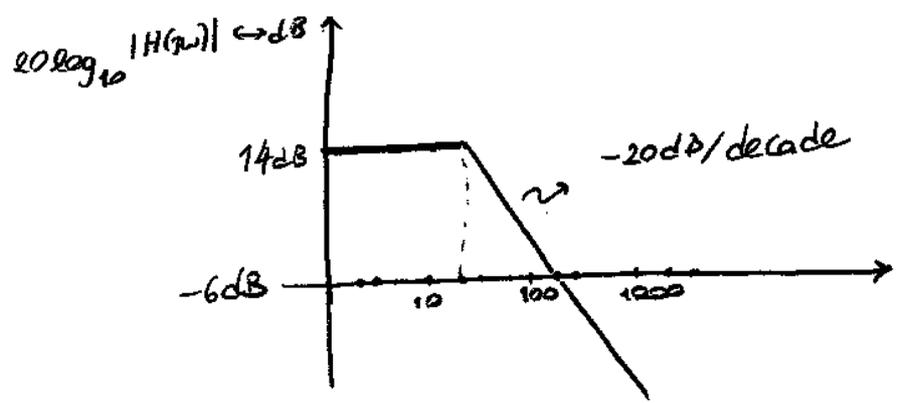

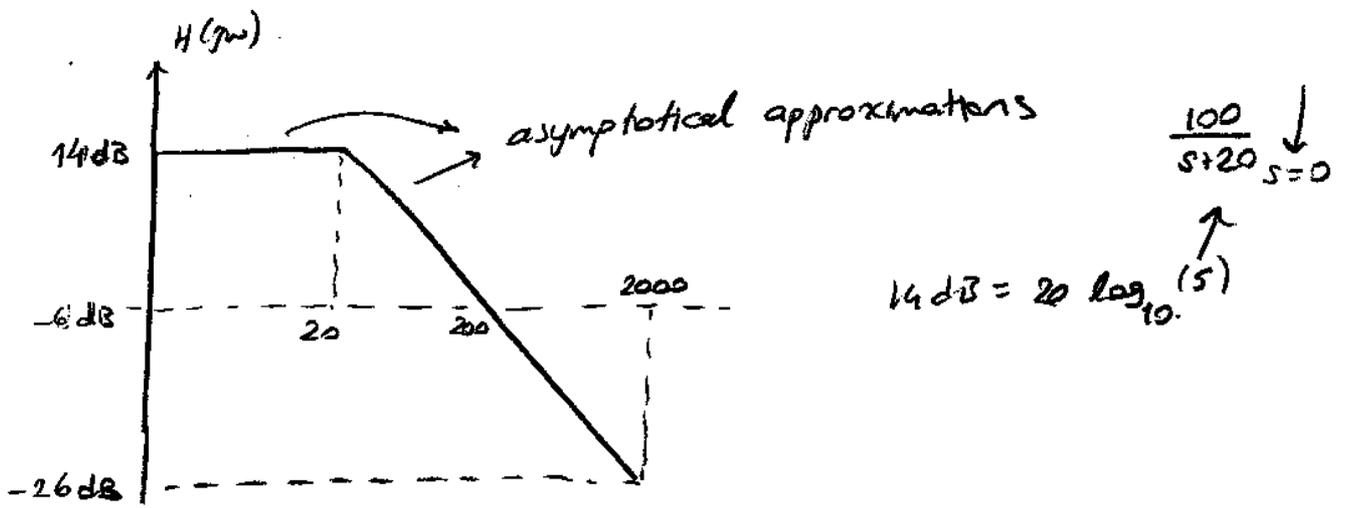


Phase Response:
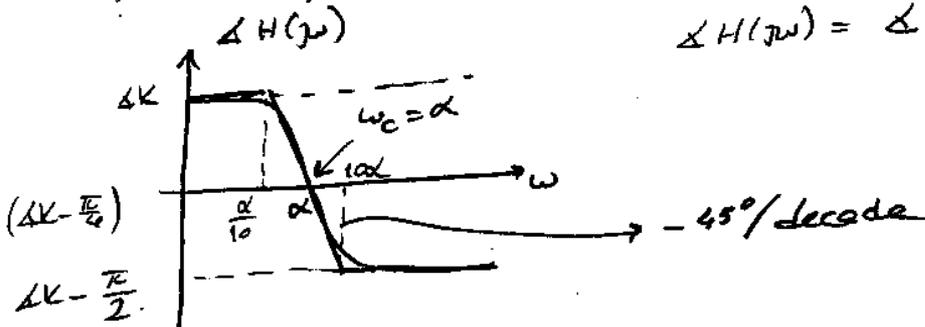
$$\angle H(j\omega) = \angle K - \tan^{-1}\left(\frac{\omega}{\alpha}\right)$$




10.5.2010 - Z

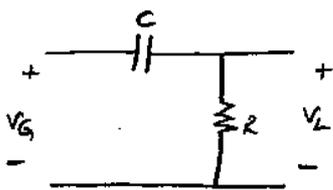


$$H(s) \triangleq \frac{V_L(s)}{V_G(s)} = \frac{R}{R + \frac{1}{sC}} = \frac{sRC}{sRC + 1}$$

$$\tau \triangleq RC, \quad \alpha \triangleq \frac{1}{\tau}$$

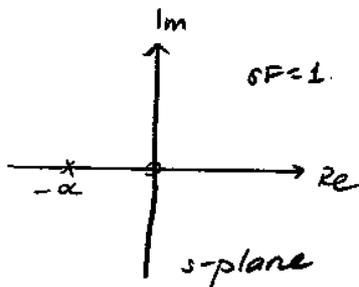
$$H(s) = \frac{s\tau}{s\tau + 1} = \frac{s/\alpha}{1 + s/\alpha} = \frac{1}{1 + \frac{\alpha}{s}} = \frac{s}{s + \alpha}$$


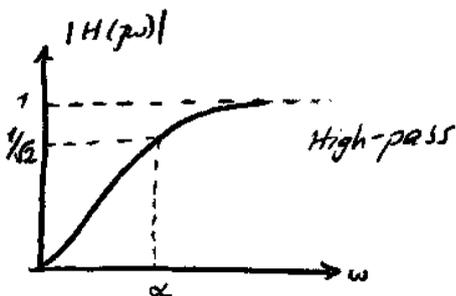
$$\begin{aligned}
 H(j\omega) &= \frac{j\omega\tau}{1 + j\omega\tau} \\
 &= \frac{j\omega}{\alpha + j\omega} \\
 &= \frac{j\omega/\alpha}{1 + j\omega/\alpha}
 \end{aligned}$$





$$= \frac{\left|\frac{j\omega}{\alpha}\right|}{\sqrt{1 + \left(\frac{j\omega}{\alpha}\right)^2}} e^{j\left(\frac{\pi}{2} \text{sign}(\omega) - \tan^{-1} \frac{\omega}{\alpha}\right)}$$

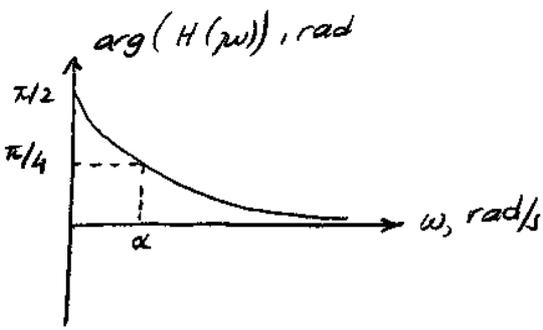

$$|H(jw)| = \frac{w}{P} e^{-T(\frac{\pi}{2} - \theta)}$$

$$\frac{w}{\sqrt{a^2 + w^2}}$$

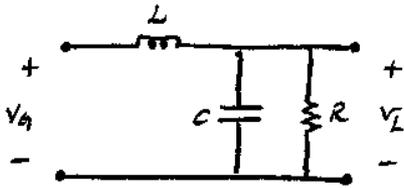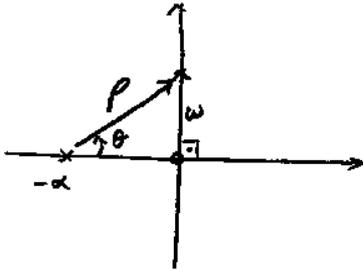

$$R \parallel \frac{1}{sC} = \frac{\frac{R}{sC}}{R + \frac{1}{sC}} = \frac{R}{1 + sRC}$$

$$H(s) = \frac{\frac{R}{1 + sRC}}{\frac{R}{1 + sRC} + sL} = \frac{R}{s^2 RC + sL + R}$$

$$= \frac{1}{LC} \frac{1}{s^2 + \frac{s}{RC} + \frac{1}{LC}}$$

$$\omega_0 \triangleq \frac{1}{\sqrt{LC}}$$

$$2\alpha \triangleq \frac{1}{RC}$$

$$Q \triangleq \frac{\omega_0}{2\alpha} = \omega_0 RC$$

$$= \frac{\omega_0^2 RC}{\omega_0} = \frac{\frac{RC}{LC}}{\omega_0} = \frac{1}{\omega_0 \frac{L}{R}}$$


$$H(s) = \frac{\omega_0^2}{s^2 + 2\alpha s + \omega_0^2} = \frac{1}{\left(\frac{s}{\omega_0}\right)^2 + \left(\frac{2\alpha}{\omega_0}\right) \frac{s}{\omega_0} + 1}$$

$\frac{2\alpha}{\omega_0} \rightarrow \frac{1}{Q}$


$$s^2 + 2\alpha s + \omega_0^2 = 0 \rightarrow s_{1,2} = -\alpha \pm \sqrt{\alpha^2 - \omega_0^2}$$

$$Q < \frac{1}{2} : \alpha > \omega_0 : \alpha_d \triangleq \sqrt{\alpha^2 - \omega_0^2}$$
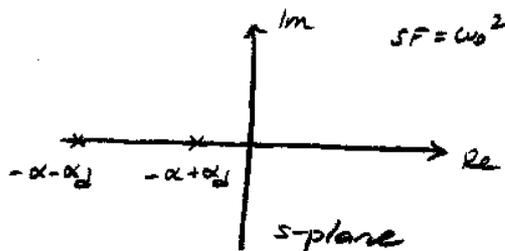
$$s_1 = -\alpha + \alpha_d \quad s_2 = -\alpha - \alpha_d \quad OD \rightarrow \text{overdamped}$$




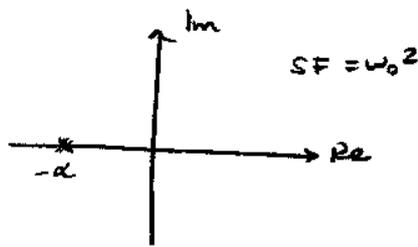$Q = \frac{1}{2}$: $\alpha = \omega_0$ C.D. critically damped



$Q > \frac{1}{2}$: $\omega_0 > \alpha$, $\omega_d \triangleq \sqrt{\omega_0^2 - \alpha^2}$

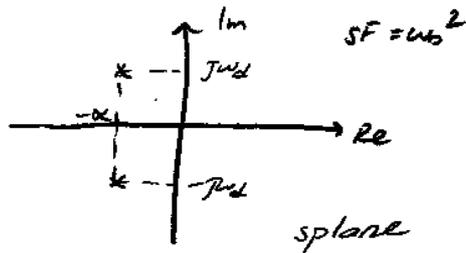$s_{1,2} = -\alpha \pm j\omega_d$ U.D. under damped



$Q < \frac{1}{2}$: $H(s) = \frac{\omega_0^2}{(s-\alpha_1)(s-\alpha_2)} = \frac{1}{(1-\frac{s}{\alpha_1})(1-\frac{s}{\alpha_2})}$

$$H(j\omega) = \frac{1}{(1+j\frac{\omega}{\alpha_1})(1+j\frac{\omega}{\alpha_2})}$$

$$= \frac{1}{\sqrt{1+(\frac{\omega}{\alpha_1})^2} \sqrt{1+(\frac{\omega}{\alpha_2})^2}} e^{-j(\tan^{-1} \frac{\omega}{\alpha_1} + \tan^{-1} \frac{\omega}{\alpha_2})}$$

$Q = \frac{1}{2}$: $H(s) = \frac{1}{(1+\frac{s}{Q})^2} \rightarrow H(j\omega) = \frac{1}{(1+j\frac{\omega}{Q})^2}$

$$= \frac{1}{1+(\frac{\omega}{Q})^2} e^{-j2 \tan^{-1} \frac{\omega}{Q}}$$

$Q > \frac{1}{2}$: $H(j\omega) = \frac{1}{[1-(\frac{\omega}{\omega_0})^2] + j\frac{1}{Q}(\frac{\omega}{\omega_0})}$

$$= \frac{1}{\left\{ [1-(\frac{\omega}{\omega_0})^2]^2 + \frac{1}{Q^2} (\frac{\omega}{\omega_0})^2 \right\}^{\frac{1}{2}}} e^{-j \tan^{-1} \frac{\frac{1}{Q} \frac{\omega}{\omega_0}}{1-(\frac{\omega}{\omega_0})^2}}$$

$x \triangleq \frac{\omega}{\omega_0}$, $P(x) \triangleq (1-x^2)^2 + \frac{1}{Q^2} x^2$

$y \triangleq x^2$, $R(y) = (1-y)^2 + \frac{1}{Q^2} y$

$R(0) = 1, |H(j0)| = 1$

$R(\infty) = 0, |H(j\infty)| = 0$

$R(1) = \frac{1}{a^2}, |H(j\omega_0)| = a$

$\frac{dR(y)}{dy} = 2y - 2 + \frac{1}{a^2} \stackrel{?}{=} 0 \quad y = 1 - \frac{1}{2a^2}$

if $1 - \frac{1}{2a^2} \geq 0 \Rightarrow 1 \geq \frac{1}{2a^2}$




$\Rightarrow a \geq \frac{1}{\sqrt{2}}$

$\omega_p = \omega_0 \sqrt{1 - \frac{1}{2a^2}}, a \geq \frac{1}{\sqrt{2}}$

peak freq.

$R(y_p) = \frac{1}{a^2} (1 - \frac{1}{4a^4})$

$|H(j\omega_p)| = \frac{a}{\sqrt{1 - \frac{1}{4a^4}}}$

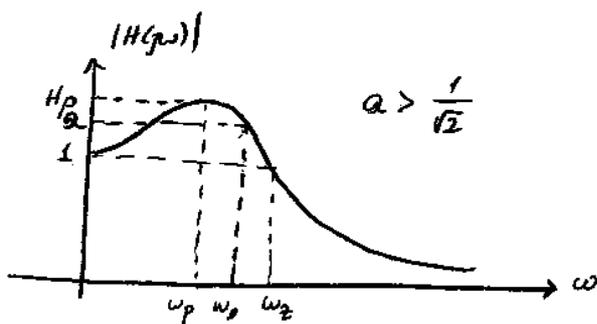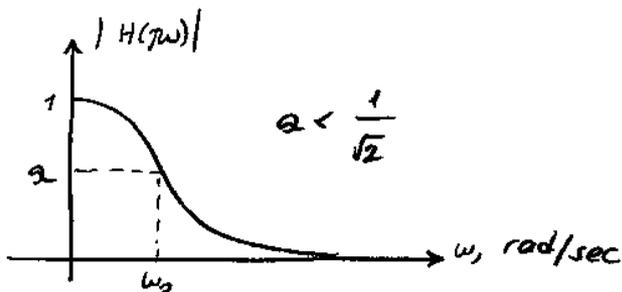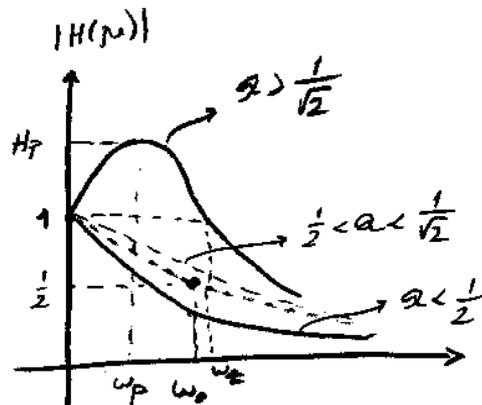

$T(x) = \tan^{-1} \frac{\frac{1}{a}x}{1-x^2}$

$T(0) = 0$

$T(1) = \frac{\pi}{2}$

$T(\infty) = \pi$

$1-x^2 = \pm \frac{1}{a}x \rightarrow \begin{matrix} 3\pi/4 \\ \pi/4 \end{matrix}$

$x^2 \pm \frac{1}{a}x - 1 = 0$

$x_{1,2} = \mp \frac{1}{2a} \pm \sqrt{\frac{1}{4a^2} + 1}$


$\omega_{1,2} = \omega_0 x_{1,2} = \mp \frac{\omega_0}{2a} \pm \sqrt{\frac{\omega_0^2}{4a^2} + \omega_0^2}$
 $= \mp \alpha \pm \sqrt{\alpha^2 + \omega_0^2}$


$\omega_1 = -\alpha + \sqrt{\alpha^2 + \omega_0^2} \Rightarrow \pi/4$

$\omega_2 - \omega_1 = 2\alpha$

$\omega_2 = \alpha + \sqrt{\alpha^2 + \omega_0^2} \Rightarrow 3\pi/4$


$\omega_1 \omega_2 = \omega_0^2$

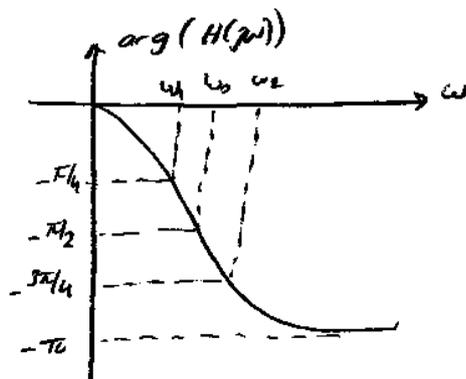

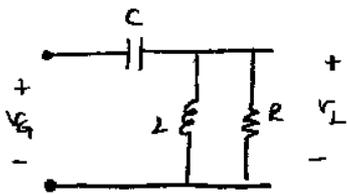




$$H(s) = \frac{s^2}{s^2 + \frac{1}{RC}s + \frac{1}{LC}} = \frac{s^2}{s^2 + 2\alpha s + \omega_0^2}$$
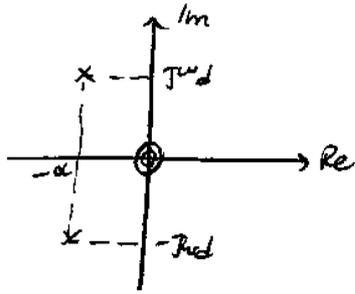
$$= \frac{(s/\omega_0)^2}{(s/\omega_0)^2 + 1/Q(s/\omega_0) + 1}$$



$$\arg(H(j\omega)) = \pi - \tan^{-1} \frac{1/Q \cdot \omega/\omega_0}{1 - (\omega/\omega_0)^2}$$


↳ π + low pass

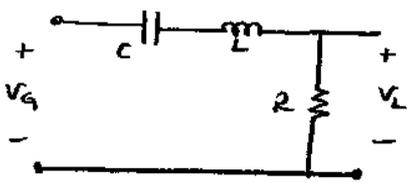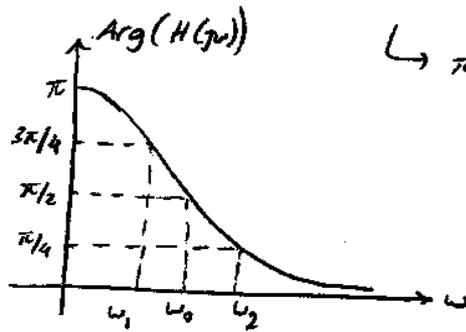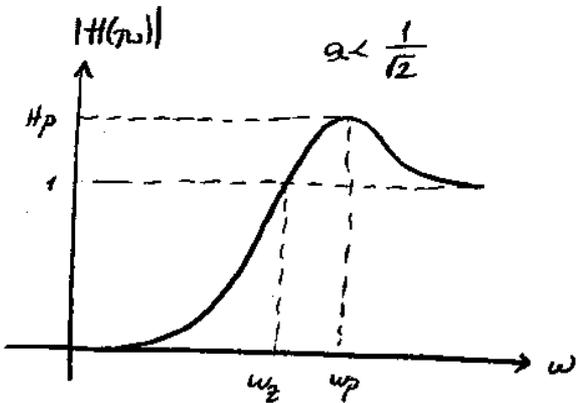

$$H(s) = \frac{R}{R + sL + \frac{1}{sC}} = \frac{R}{L} \frac{s}{s^2 + s\frac{R}{L} + \frac{1}{LC}} = \frac{2\alpha s}{s^2 + 2\alpha s + \omega_0^2}$$

$$Q = \frac{\omega_0 L}{R} = \frac{1}{\omega_0 RC}$$

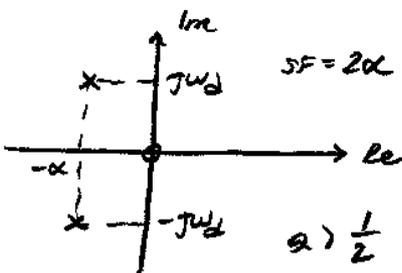
$$H(s) = \frac{1/Q (s/\omega_0)}{(s/\omega_0)^2 + 1/Q (s/\omega_0) + 1} = \frac{1}{1 + Q \frac{(s/\omega_0)^2 + 1}{(s/\omega_0)}}$$




$$H(j\omega) = \frac{1}{1 + jQ \frac{1 - (\omega/\omega_0)^2}{\omega/\omega_0}}$$

$$\arg(H(j\omega)) = \frac{\pi}{2} \text{sign}(\omega) - \tan^{-1} \frac{1/Q \cdot \omega/\omega_0}{1 - (\omega/\omega_0)^2}$$


$\frac{\pi}{2}$ + Low pass

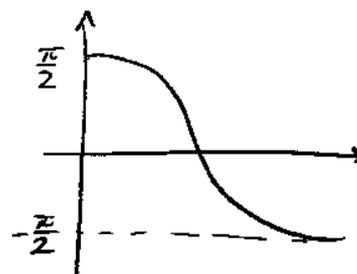

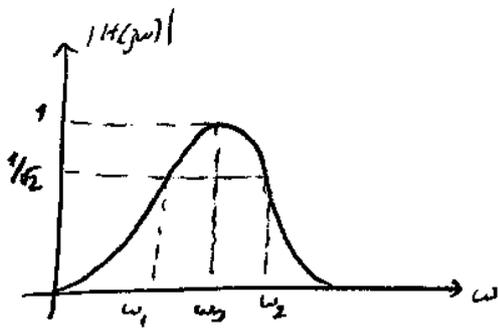

$\omega_2 - \omega_1 = 2\alpha \rightarrow$ half power bandwidth

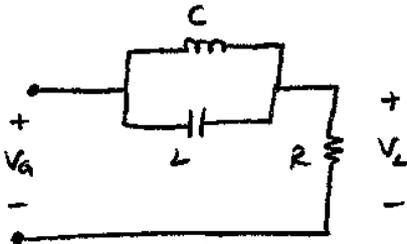$\omega_0 = \sqrt{\omega_1 \omega_2} \rightarrow$ center freq.



$$H(s) = \frac{R}{R + \frac{1}{sC + \frac{1}{sL}}} = \frac{s^2 + \frac{1}{LC}}{s^2 + s \frac{1}{RC} + \frac{1}{LC}}$$




$$= \frac{s^2 + \omega_0^2}{s^2 + 2\alpha s + \omega_0^2}$$

$$= \frac{(s/\omega_0)^2 + 1}{(s/\omega_0)^2 + \frac{1}{Q}(s/\omega_0) + 1}$$

$$Y(j\omega_0) = j\omega_0 C + \frac{1}{j\omega_0 L}$$


$$= 0$$

↳ no conductance

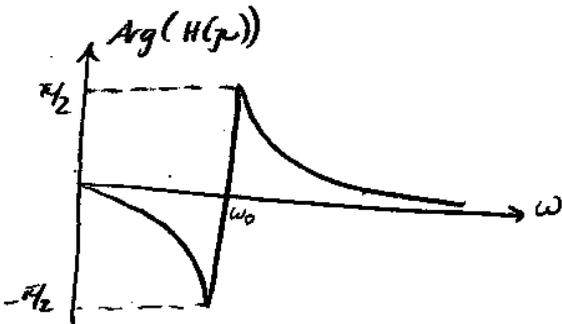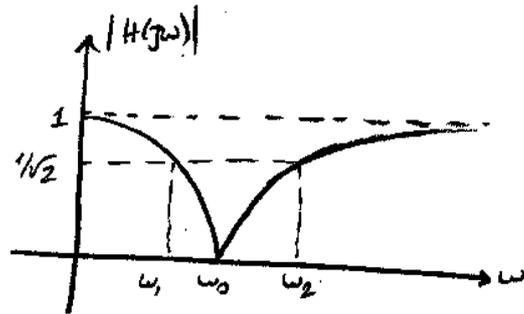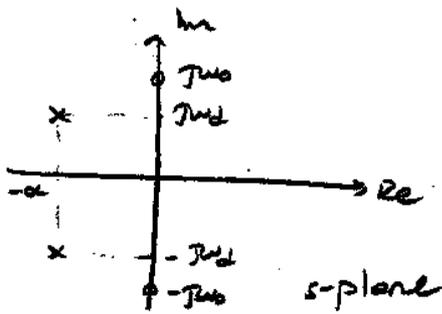

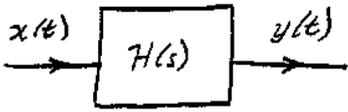13.05.2010


Band-pass - Band-stop Filters using 1st order Circuits






$$H_1(s) = \frac{s}{s + \alpha_1} k_1 \rightarrow \text{high pass system}$$

$$H_2(s) = \frac{k_2}{s + \alpha_2} \rightarrow \text{low pass system}$$



Band pass system

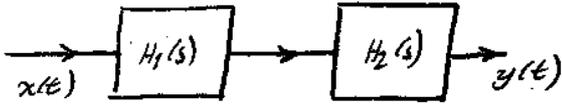

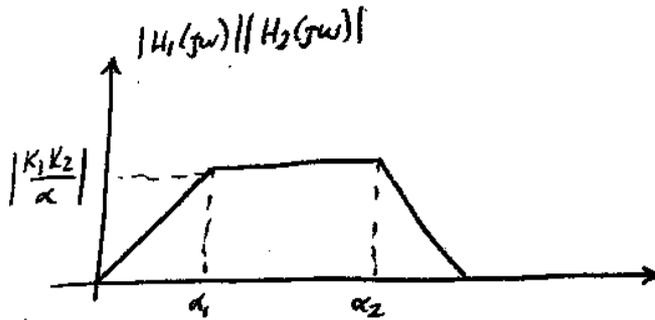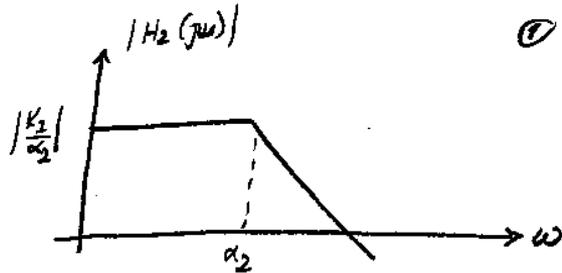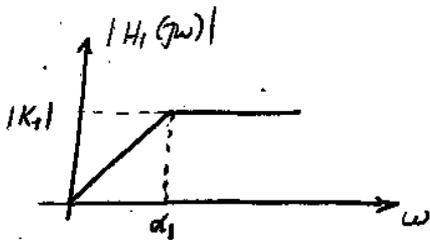
$$H(s) = H_1(s) H_2(s) \rightarrow \text{No loading effects between systems ① and ②}$$




Parallel Combination

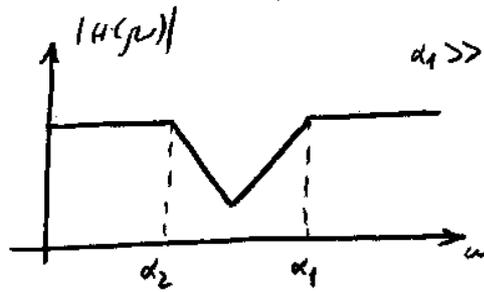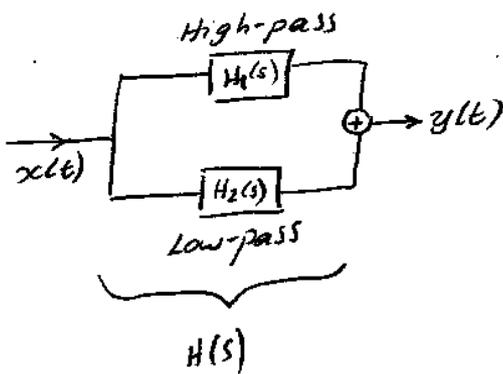

Band-stop filter

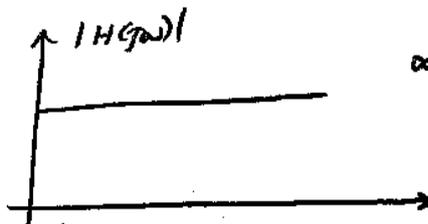

All-pass filter

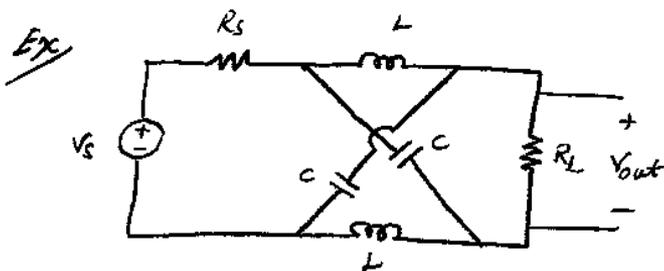

$$\frac{L}{C} = R_L^2$$

$$H(j\omega) = \frac{R_L}{R_L + R_s} \frac{1 - j\omega C R_L}{1 + j\omega C R_L}$$

$$|H(j\omega)| = \frac{R_L}{R_L + R_s} ; \angle H(j\omega) = 2 \tan^{-1}(-\omega C R_L)$$

Second Order Circuits

(A) Band-Pass System

$$H(s) = K \frac{s}{s^2 + 2\delta\omega_0 s + \omega_0^2}$$

$s^2 + 2\delta\omega_0 s + \omega_0^2$: char. polynomials

↳ distinct and real roots $\lambda_1 \neq \lambda_2$

identical roots

$$\lambda_1 = \lambda_2 \longrightarrow H(s) = \frac{Ks}{(s-\lambda_0)^2}$$

complex conjugate roots

$$\lambda_1 = \lambda_2^*$$

2nd order system with complex poles requires some special interest

$$H(s) = K \frac{s}{(s-\lambda_1)} \cdot \frac{1}{(s-\lambda_2)}$$

\uparrow high-pass \uparrow low-pass

$$H(s) \downarrow_{s=j\omega} = K \frac{j\omega}{-\omega^2 + 2\delta\omega_0 j\omega + \omega_0^2} = K \frac{1}{\frac{\omega_0^2 - \omega^2}{j\omega} + 2\delta\omega_0}$$

$$= K \frac{1}{\omega_0 \left(2\delta + j \left[\frac{\omega}{\omega_0} - \frac{\omega_0}{\omega} \right] \right)}$$

$$|H(j\omega)| = \frac{|K|}{\omega_0} \cdot \frac{1}{\sqrt{(2\delta)^2 + \left(\frac{\omega}{\omega_0} - \frac{\omega_0}{\omega} \right)^2}}$$

$$\angle H(j\omega) = \angle K - \tan^{-1} \left[\left(\frac{\omega}{\omega_0} - \frac{\omega_0}{\omega} \right) / 2\delta \right]$$

$$s^2 + 2\delta\omega_0 s + \omega_0^2 = 0$$

$$s_{1,2} = \left\{ -\delta\omega_0 \pm \omega_0 \sqrt{\delta^2 - 1} \right\}$$

(1) $\delta = 1 \longrightarrow s_{1,2} = \left\{ -\omega_0 \right\}$ double roots, critically damped


$$x_{1,2} = -\omega_0$$

② $\gamma > 1 \rightarrow$ distinct roots (overdamped)

③ $\gamma = 0 \rightarrow s_{1,2} = \{ \pm j\omega_n \}$

④ $|\gamma| < 1$: complex roots


Pole-zero Plot for $H(s)$

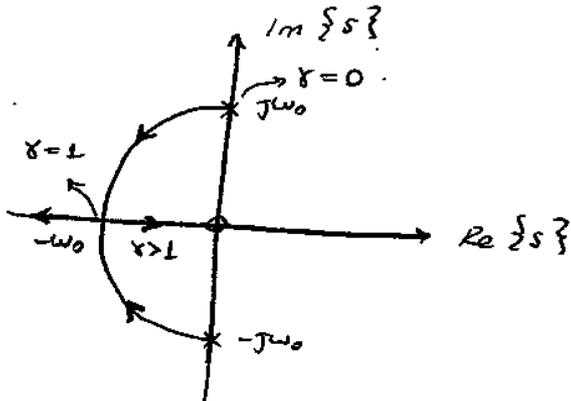

$$H(s) = \frac{Ks}{s^2 + 2\gamma\omega_n s + \omega_n^2}$$

γ : damping coefficient
 ω_n : resonant frequency (rad/sec)

$$H(s) = \frac{Ks}{(s-p_1)(s-p_2)}$$

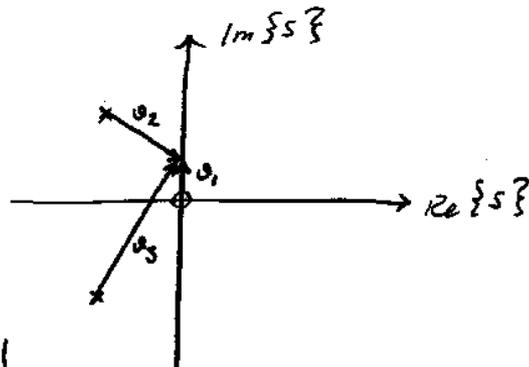

$$|H(j\omega)| = \frac{|K| \cdot |j\omega|}{|j\omega - p_1| \cdot |j\omega - p_2|} = \frac{|K| \cdot \omega}{\omega_2 \omega_3}$$

Returning to Algebraic Discussion


$$H(j\omega) = \frac{K/\omega_n}{2\gamma + j\left(\frac{\omega}{\omega_n} - \frac{\omega_n}{\omega}\right)}$$

$$\arg \max_{\omega} (|H(j\omega)|) = \omega_n$$


$$|H(j\omega_n)| = \max_{\omega} |H(j\omega)| = \frac{|K|}{2\gamma\omega_n}$$

$$\begin{aligned} \textcircled{1} \omega \ll \omega_n \rightarrow H(j\omega) &= \frac{K/\omega_n}{2\gamma + j\left(\frac{\omega}{\omega_n} - \frac{\omega_n}{\omega}\right)} \approx \frac{K/\omega_n}{2\gamma + j\left(-\frac{\omega_n}{\omega}\right)} \approx \frac{K/\omega_n}{-j\omega_n/\omega} \\ &\approx j \frac{K\omega}{\omega_n^2} \end{aligned}$$
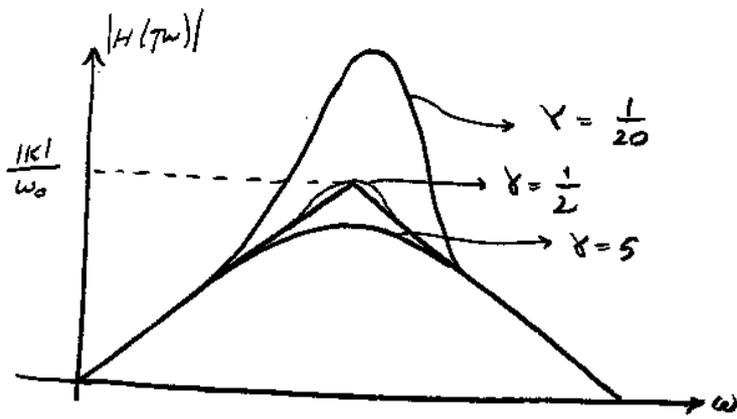
$$\textcircled{2} \omega \gg \omega_n \rightarrow H(j\omega) \approx \frac{K/\omega_n}{2\gamma + j\omega/\omega_n} \approx -j \frac{K}{\omega}$$



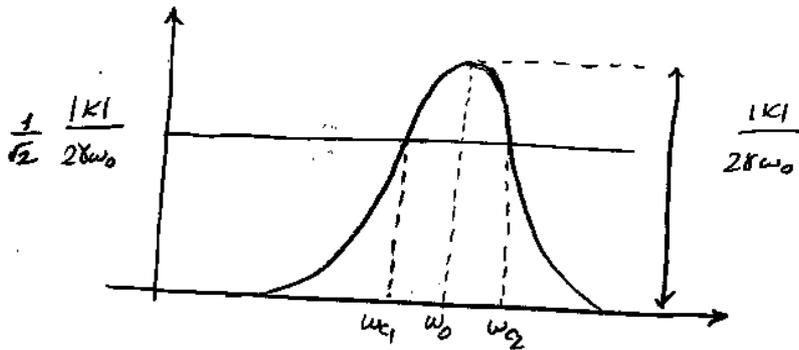Less damping (γ smaller) results in peaking freq. response.



ω_1, ω_2 : cut off frequencies

$$|H(j\omega)| = \left| \frac{K/\omega_0}{2\delta + j\left(\frac{\omega}{\omega_0} - \frac{\omega_0}{\omega}\right)} \right| \Bigg|_{\omega=\omega_1, \omega_2} = \frac{|K|/\omega_0}{\sqrt{2} \cdot 2\delta}$$

$\pm 2\delta$

one of the

Then cut-off frequencies satisfy the following property:

$$\left(\frac{\omega}{\omega_0} - \frac{\omega_0}{\omega}\right) = 2\delta$$


$$\omega^2 - 2\delta\omega_0\omega - \omega_0^2 = 0 \rightarrow \text{solution gives cut-off freq.}$$

$$\text{then } \omega_{1,2} = \omega_0 \left(\delta \pm \sqrt{1+\delta^2} \right) \rightarrow \omega_2 = \omega_0 \left(\delta + \sqrt{1+\delta^2} \right)$$

For ω_1 : we repeat the same calculation for $\left(\frac{\omega}{\omega_0} - \frac{\omega_0}{\omega}\right) = -2\delta$

$$\text{and get } \omega_1 = \omega_0 \left(-\delta + \sqrt{1+\delta^2} \right)$$
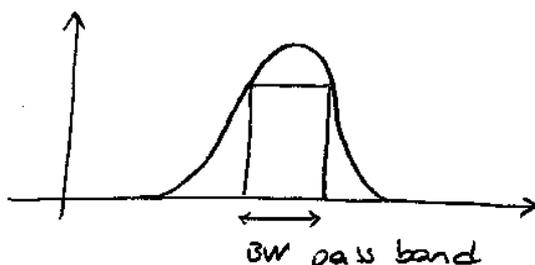
$$\underline{\text{Bandwidth of the system}} = \omega_2 - \omega_1 = 2\delta\omega_0$$




Q : quality Factor

$$Q = \frac{\omega_0}{BW} = \frac{1}{2\delta}$$

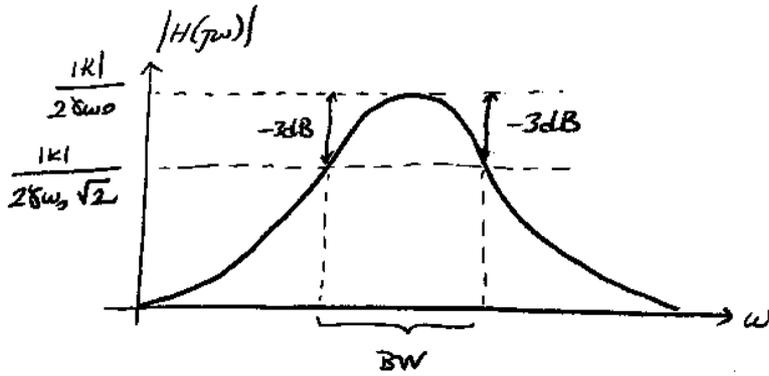17.09.2010

Second order Band-Pass Response:

$$H(s) = \frac{Ks}{s^2 + 2\zeta\omega_0 s + \omega_0^2} \rightarrow \text{2nd order band-pass system}$$



$H(j\omega) \rightarrow$ ① $|H(j\omega)|$ has a peak at $(\omega_0, \frac{|K|}{2\zeta\omega_0})$


② $|H(j\omega_0)| = 70\%$ of the peak

$$\omega_{c1} = \omega_0 (-\zeta + \sqrt{1 + \zeta^2})$$

$$\omega_{c2} = \omega_0 (\zeta + \sqrt{1 + \zeta^2})$$

③ $BW = \omega_{c2} - \omega_{c1} = 2\zeta\omega_0$

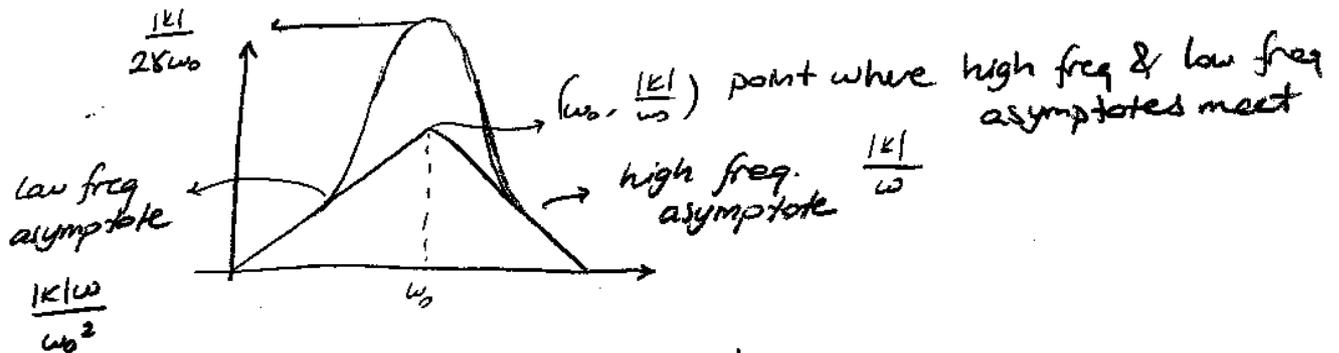④ $Q = \frac{\omega_0}{BW} = \frac{1}{2\zeta}$ (Q : quality factor)




1) ζ small: peaky response $\rightarrow Q$: high
 high Q filters \rightarrow narrow band filters

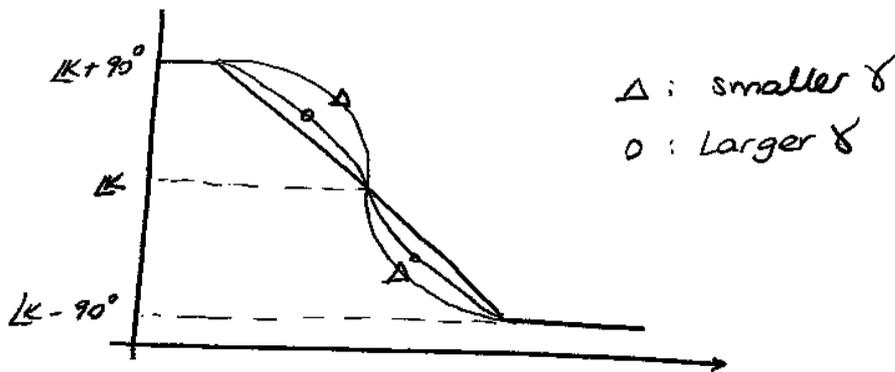2) ζ large: broad response $\rightarrow Q$: low
 low Q filter \rightarrow wide band filters

Phase Response (2nd order Bandpass Systems)

$$\angle H(j\omega) = \angle K - \tan^{-1} \left(\frac{\omega/\omega_0 - \omega_0/\omega}{2\gamma} \right)$$



Second order Low Pass Systems

$$H(s) = \frac{K}{s^2 + 2\gamma\omega_0 s + \omega_0^2}$$

$$H(j\omega) = \frac{K}{\omega_0^2 - \omega^2 + j 2\gamma\omega_0\omega}$$


$$|H(j\omega)| = \frac{|K|}{\sqrt{(\omega_0^2 - \omega^2)^2 + (2\gamma\omega_0\omega)^2}}$$

$$\angle H(j\omega) = \angle K - \tan^{-1} \left(\frac{2\gamma\omega_0\omega}{\omega_0^2 - \omega^2} \right)$$

$$H(j\omega) = \frac{K}{\omega_0^2 \left(1 - \left(\frac{\omega}{\omega_0}\right)^2 + j 2\gamma \frac{\omega}{\omega_0} \right)}$$

$$\textcircled{1} \quad \omega \ll \omega_0 \longrightarrow |H(j\omega)| = \frac{|K|}{\omega_0^2}$$


$$\textcircled{2} \quad \omega \gg \omega_0 \longrightarrow |H(j\omega)| = \frac{|K|}{\omega^2}$$

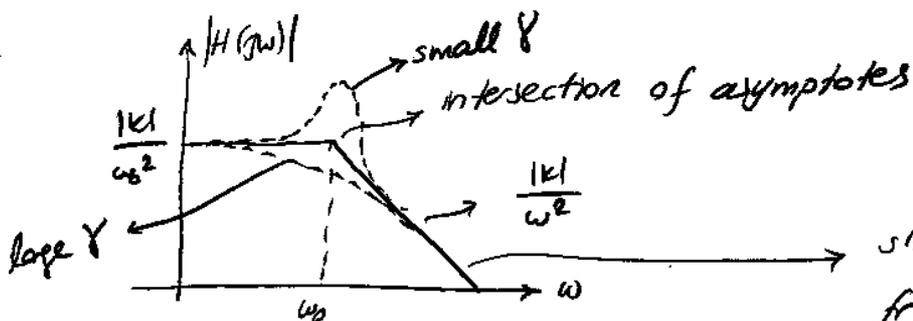

$$\textcircled{3} \quad |H(j\omega_0)| = \frac{|K|}{2\gamma\omega_0^2}$$

Second order High Pass Systems
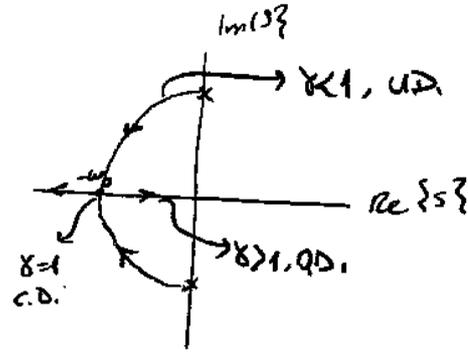
$$H(s) = \frac{Ks^2}{s^2 + 2\zeta\omega_0 s + \omega_0^2}$$





$$\begin{aligned} \textcircled{1} H(j\omega) &= \frac{-K\omega^2}{\omega_0^2 - \omega^2 + j2\zeta\omega\omega_0} \\ &= \frac{-K\omega^2}{\omega_0^2 \left(1 - \left(\frac{\omega}{\omega_0}\right)^2 + j2\zeta\frac{\omega}{\omega_0} \right)} \end{aligned}$$


$$\textcircled{2} \angle H(j\omega) = 180^\circ + \angle K - \tan^{-1} \frac{2\zeta\omega/\omega_0}{1 - (\omega/\omega_0)^2}$$

$$\textcircled{1} \omega \ll \omega_0 \rightarrow H(j\omega) = \frac{-K\omega^2}{\omega_0^2}, \quad |H(j\omega)| = \frac{|K|\omega^2}{\omega_0^2}$$

$$\textcircled{2} \omega \gg \omega_0 \rightarrow H(j\omega) = -K, \quad |H(j\omega)| = |K|$$

$$\textcircled{3} |H(j\omega_0)| = \frac{|K|}{2\zeta}$$

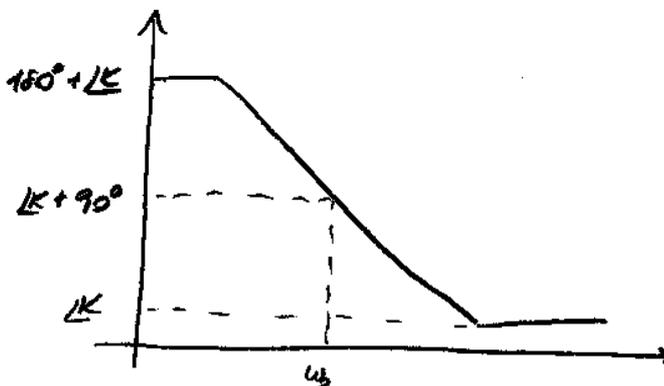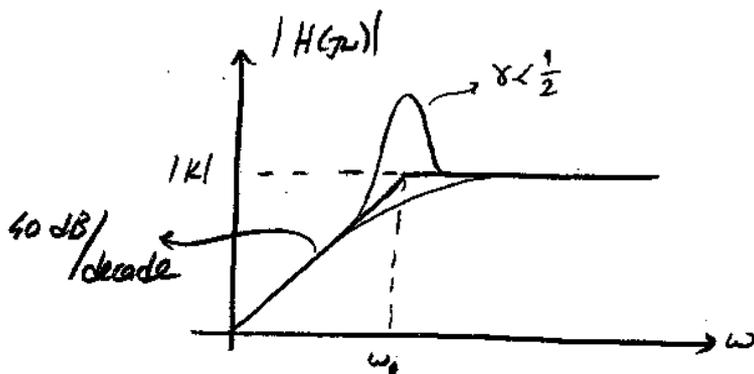

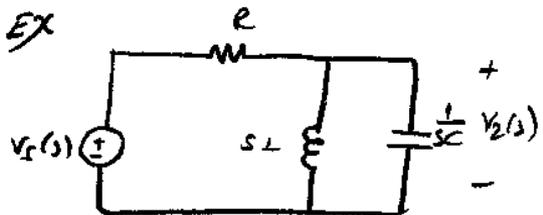

$$H(s) = \frac{V_2(s)}{V_1(s)} = \frac{s/RC}{s^2 + \frac{s}{RC} + \frac{1}{LC}}$$

$$= K \frac{s}{s^2 + 2\delta\omega_0 s + \omega_0^2}$$

$L = 0.25 \text{ H}, R = 1 \text{ k}\Omega, C = 1 \mu\text{F}$


$\omega_0 = \frac{1}{\sqrt{LC}} = 2 \text{ k rad/sec}$

$\text{BW} = 2\omega_0 \delta = \frac{1}{RC} = 1 \text{ k rad/sec}$

$Q = \frac{\omega_0}{\text{BW}} = 2 \text{ (unitless)}$

$Q = \frac{1}{2} \rightarrow$ critically damped (?)
 $Q > \frac{1}{2} \rightarrow$ underdamped.

Exo Active Filter

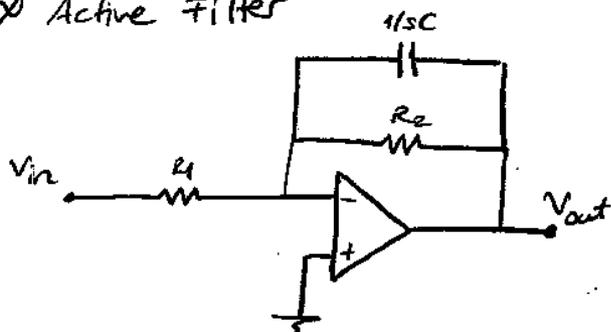

$$H(s) = \frac{-R_2}{R_1} \frac{1}{1 + sR_2C}$$


Scaling

24.05.2010

used to modify a given filter to

- i) realizable filter (with components on the shelf)
- ii) changing (scaling) gain-phase response

① magnitude scaling

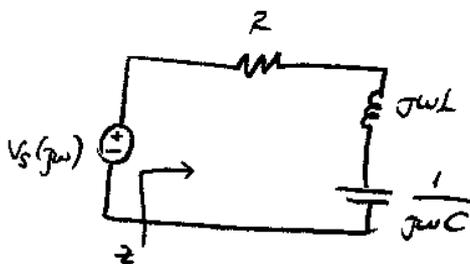


$$Z(j\omega) = R + j\omega L + \frac{1}{j\omega C}$$

$$I_s(j\omega) = \frac{V_s(j\omega)}{R + j\omega L + \frac{1}{j\omega C}}$$

$$\frac{V_{out}(j\omega)}{V_s(j\omega)} = \frac{j\omega L + \frac{1}{j\omega C}}{R + j\omega L + \frac{1}{j\omega C}} \quad (*)$$

Replace $R \rightarrow k_m R$
 $L \rightarrow k_m L$
 $C \rightarrow C/k_m$ } After replacement no change in the transfer function

② Frequency Scaling

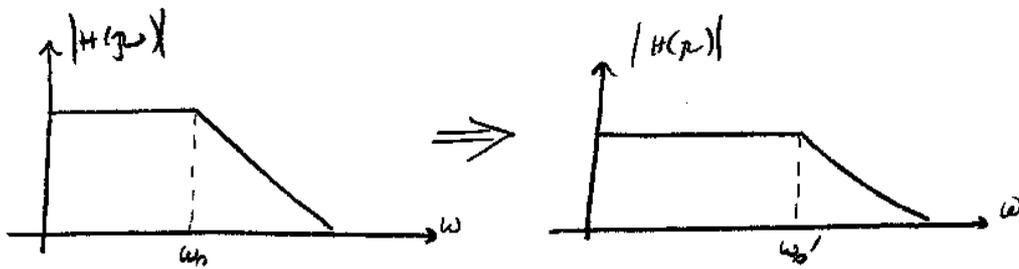

$$H(j\omega) = \frac{j\omega L + \frac{1}{j\omega C}}{R + j\omega L + \frac{1}{j\omega C}}$$

$|H(j\omega)|$ is the value at cut-off

$$R \rightarrow R$$

$$L \rightarrow \frac{L}{k_f}$$


$$C \rightarrow \frac{C}{k_f}$$

after
 $H(j\omega)$

$$\frac{j \frac{\omega}{k_f} L + \frac{1}{j \frac{\omega}{k_f} C}}{R + j \frac{\omega}{k_f} L + \frac{1}{j \frac{\omega}{k_f} C}} = H(j \frac{\omega}{k_f})$$

select $k_f = \frac{\omega_0'}{\omega_0}$ (?)

Ex

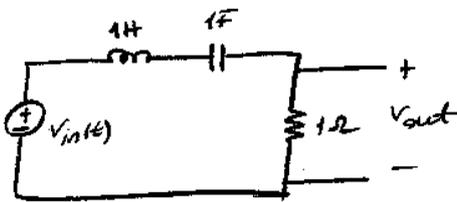

$$\omega_0 = \sqrt{1/LC} = 1 \text{ rad/s}$$

$$BW = 28\omega_0 = \frac{R}{L} = 1 \text{ rad/s}$$

$$Q = \frac{\omega_0}{BW} = 1$$

Scale the circuit such that the resonant frequency is at 500 Hz and use a 2 μF capacitor.

$$R \xrightarrow{k_f} R \xrightarrow{k_m} R k_m \longrightarrow 160 \Omega$$



$$L \xrightarrow{k_f} L/k_f \xrightarrow{k_m} L \frac{k_m}{k_f} \longrightarrow 50 \text{ mH}$$

$$C \xrightarrow{k_f} C/k_f \xrightarrow{k_m} \frac{C}{k_f k_m} \longrightarrow 2 \mu\text{F}$$

$$\omega_0' = 2\pi \cdot 500 = 1000\pi \text{ rad/sec}$$

$$k_f = \frac{\omega_0'}{\omega_0} = 1000\pi \quad k_m = \frac{1\text{F}}{2\mu\text{F} \cdot 1000\pi} \approx 160$$

Q does not change !!

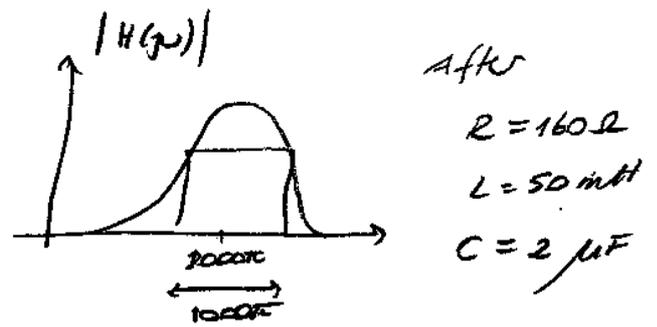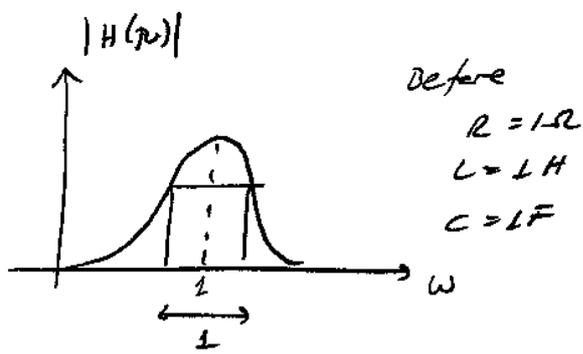

Bode Plots

Ex $H(s) = 12500 \frac{(s+10)}{(s+50)(s+500)}$

① Bring $H(s)$ into standard form

$$H^{std}(s) = K \frac{(1 + \frac{s}{\alpha_1})}{(1 + \frac{s}{\alpha_2})(1 + \frac{s}{\alpha_3})}$$

$$H(s) = 5 \frac{(1 + \frac{s}{10})}{(1 + \frac{s}{50})(1 + \frac{s}{500})}$$


② Find critical frequencies:

$$\omega_{critical} = \{10, 50, 500\}$$

③ $|H(j\omega)| = 5 \frac{|1 + j\omega/10|}{|1 + j\omega/50| |1 + j\omega/500|}$


dB ↓

$$20 \log_{10} |H(j\omega)| = |H(j\omega)|_{dB} = 20 \log_{10}(5) + 20 \log_{10} |1 + j\omega/10| - 20 \log_{10} |1 + j\omega/50| - 20 \log_{10} |1 + j\omega/500|$$

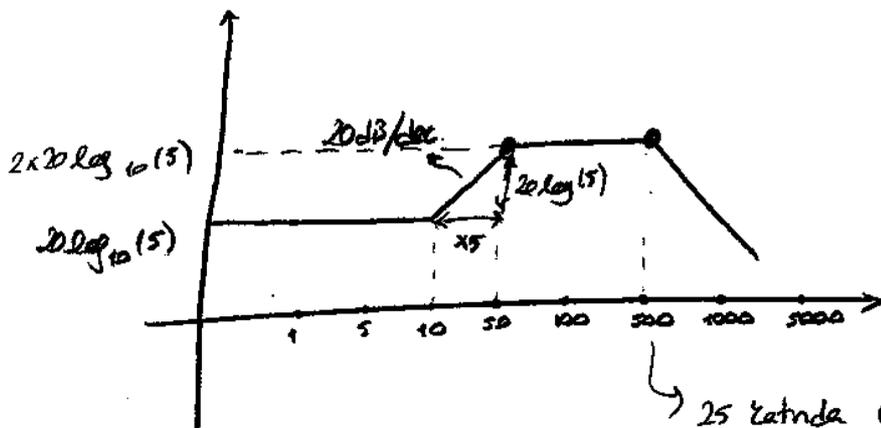


Phase Plot

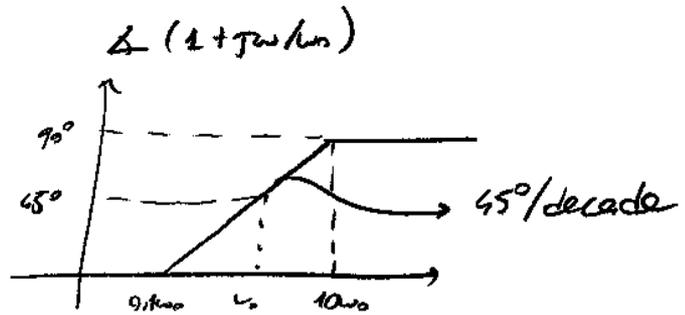- ① $\angle 5$
- ② $\angle (1 + j\omega/10)$
- ③ $-\angle (1 + j\omega/50)$
- ④ $-\angle (1 + j\omega/5000)$



Edge points for graph drawing are at $\left\{ \frac{\omega_0}{10}, \omega_0, 10\omega_0 \right\}$

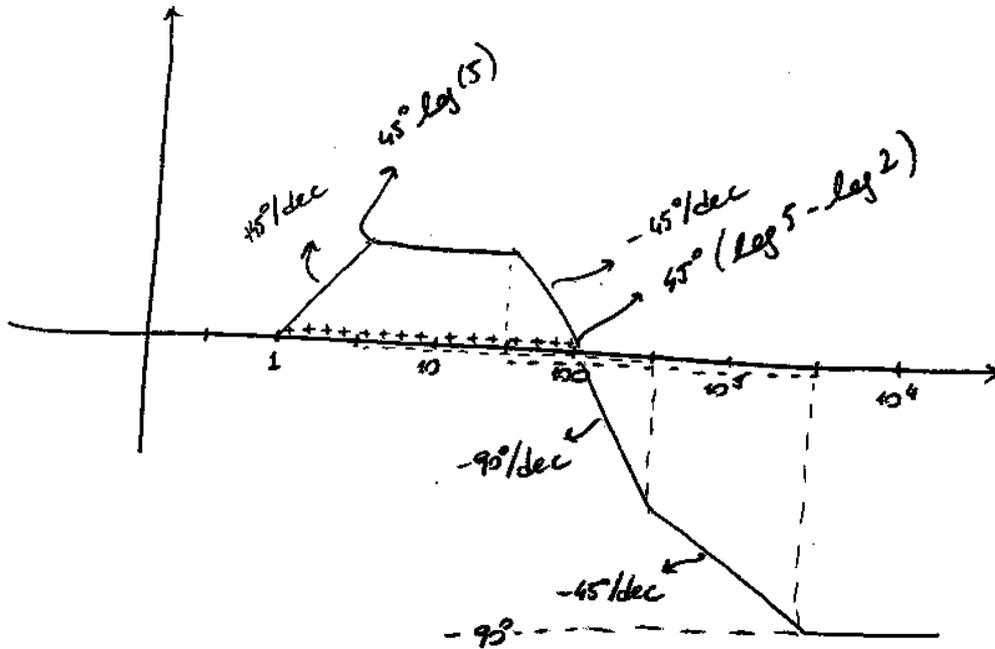- ① 0
- ② +45°/dec btw [1, 100]
- ③ -45°/dec [1, 500]
- ④ -45°/dec btw [50, 5000]



27.05.2010

$$H(s) = \frac{ks}{s^2 + 2\zeta\omega_0 s + \omega_0^2}$$


$$BW = 2\zeta\omega_0$$

$$Q = \frac{\omega_0}{BW} = \frac{1}{2\zeta}$$

$\zeta = \frac{1}{2}$; ($Q=1$) $\rightarrow (s + \omega_0)^2 \rightarrow$ critically damped $\lambda_1 = \lambda_2 = -\omega_0$

$\zeta > \frac{1}{2} \rightarrow$ overdamped λ_1, λ_2 : real distinct

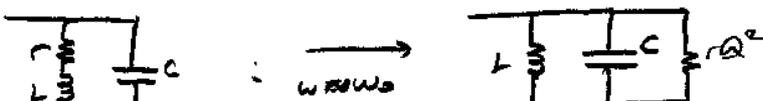$\zeta < \frac{1}{2} \rightarrow$ underdamped



Bode Plots with 2nd Order Systems

Let's examine the following term:

$$A(s) = s^2 + 2\zeta\omega_0 s + \omega_0^2$$

Note: $A(s)$ can be factorized as $(s + \alpha_1)(s + \alpha_2)$ where α_1, α_2 real when $\zeta > 1$ and $\zeta > 1$ then reduces $A(s)$ to the multiplication of 1st order systems.

Then assume $\zeta < 1$; roots are imaginary

To start to analyze, write $A(s)$ in the standard form

$$A(s) = \omega_0^2 \left(1 + \frac{2\zeta}{\omega_0} s + \frac{s^2}{\omega_0^2} \right)$$


$$A^{std}(s) = 1 + \frac{2\zeta}{\omega_0} s + \frac{s^2}{\omega_0^2}$$

$s = j\omega$

$\xrightarrow{1..1}$
 $\sqrt{\left(1 - \frac{\omega^2}{\omega_0^2}\right)^2 + \left(\frac{2\zeta\omega}{\omega_0}\right)^2}$

$\xrightarrow{\Delta}$
 $\tan^{-1} \left(\frac{2\zeta \omega/\omega_0}{1 - \left(\frac{\omega}{\omega_0}\right)^2} \right)$

$20 \log_{10} \sqrt{\left(1 - \frac{\omega^2}{\omega_0^2}\right)^2 + \left(\frac{2\zeta\omega}{\omega_0}\right)^2}$

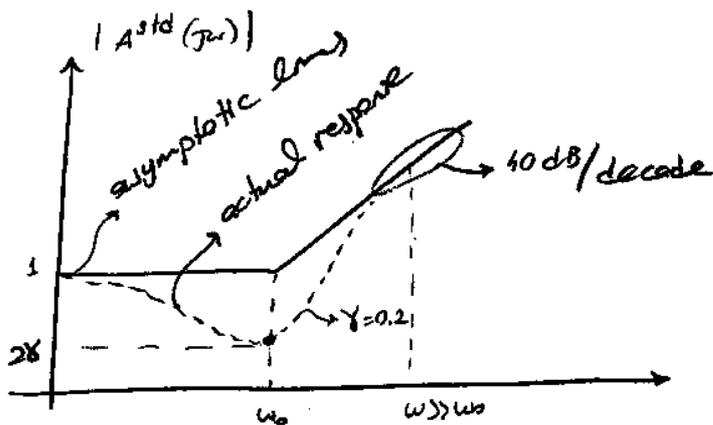

Case 1: $\omega \ll \omega_0$

Case 2: $\omega \gg \omega_0$

$$|A^{std}(j\omega)|_{dB} = 20 \log_{10} \sqrt{\left(\frac{\omega}{\omega_0}\right)^4 + \frac{4\zeta^2}{\omega_0^2} + \left(\frac{\omega}{\omega_0}\right)^2}$$

$$= 20 \log_{10} \left(\frac{\omega}{\omega_0}\right)^2$$


Case 3: $\omega = \omega_0$

$$|A^{std}(j\omega_0)| = 2\zeta$$

$\zeta < 1 \rightarrow$ for imaginary roots or underdamped systems



$$Q = \frac{1}{2\zeta}; \text{ High } Q: \text{ small } \zeta$$

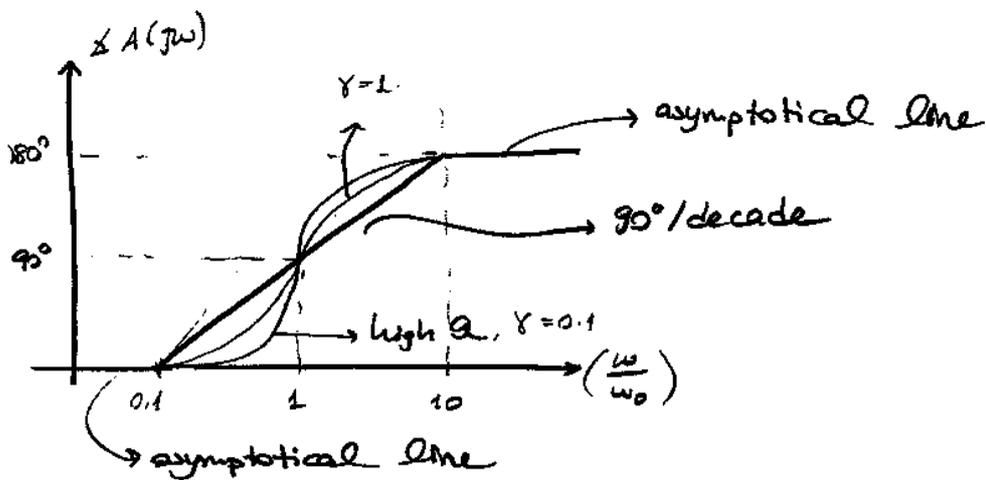Note: $\zeta = \frac{1}{2}; 2\zeta = 1$ actual curve passes through the intersection of asymptotes.



Ex $H(s) = \frac{5000(s+100)}{s^2+400s+(500)^2} = \frac{5000 \cdot 100 (1 + s/100)}{500^2 (1 + \frac{400s}{500^2} + \frac{s^2}{500^2})}$
 \downarrow \downarrow
 $28\omega_0$ ω_0^2
 \downarrow \downarrow
 $\gamma = 0.4$
 \downarrow
 underdamped
 2nd order system model
 $= \frac{2(1 + s/100)}{1 + \frac{16}{10000}s + (\frac{s}{500})^2}$
 $\rightarrow \omega_0 = 500$

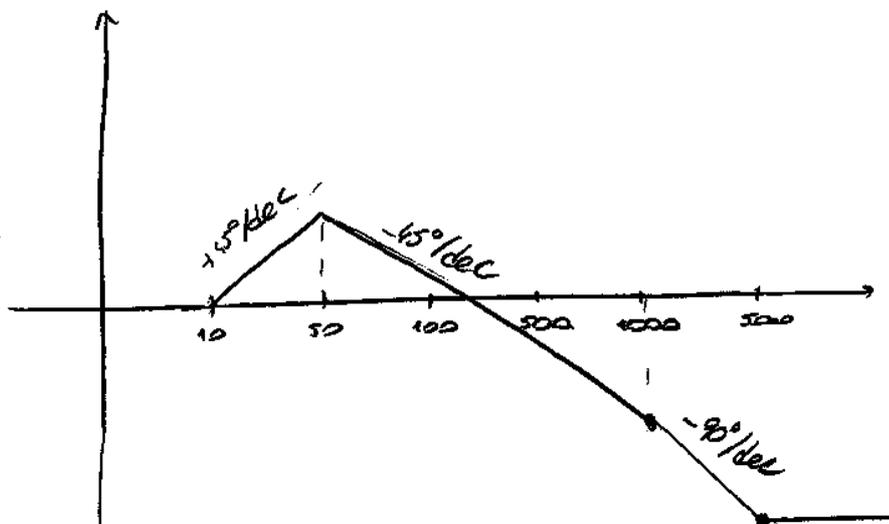
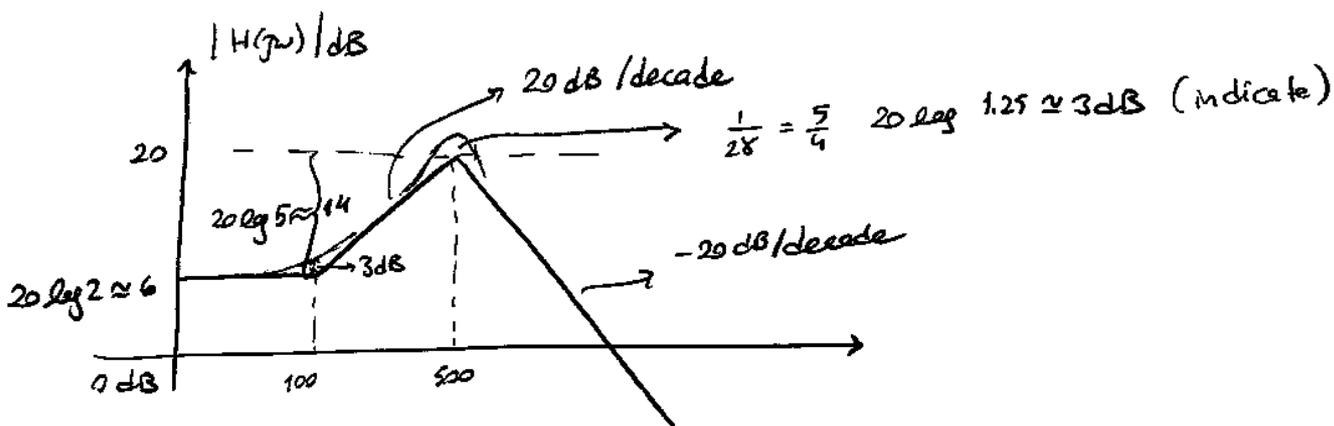
$\omega_{\text{critical}} = \{100, 500\}$
 \downarrow
 zero location $\rightarrow \omega_0$ (2nd order system)



State Equations with non-linear elements

If an element is non-linear we would like to express the current in the state equation form, we can do the following.

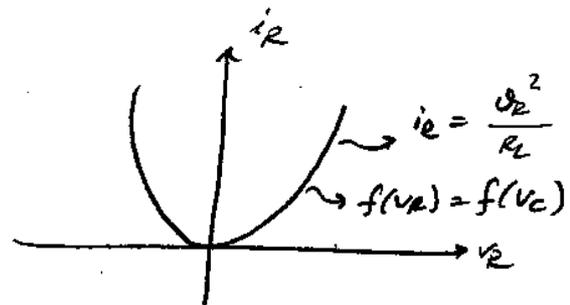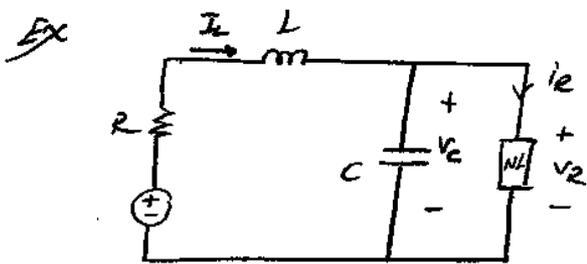- ① Check whether the component is voltage / current controlled.
- ② Try to include the current of the nonlinear component if it is current controlled (or its voltage otherwise)
- ③ Include variables of dynamic components as state variables
- ④ Try to combine ② and ③



$$\text{KCL: } C \cdot \dot{v}_C(t) = -i_R + i_L$$

$$\quad \quad \quad \hookrightarrow -\frac{v_C^2(t)}{R_L}$$

$$\dot{v}_C(t) = -\frac{1}{C \cdot R_L} v_C^2(t) + \frac{1}{C} i_L(t)$$

$$\text{KVL} \quad -v_C(t) + R \cdot i_L(t) + L \dot{i}_L(t) + v_C(t) = 0$$

$$\dot{i}_L(t) = -\frac{1}{L} v_C(t) - \frac{R}{L} i_L(t) + \frac{1}{L} v_S(t)$$

zero input:

$$\dot{v}_C(t) = -\frac{v_C^2(t)}{R_L \cdot C} + \frac{i_L(t)}{C}$$

$$v_C(0^-) = v_0$$

$$i_L(0^-) = I_0$$

$$\dot{i}_L(t) = -\frac{v_C(t)}{L} - \frac{R}{L} i_L(t)$$


$$v_C(t) \triangleq v_C \quad i_L(t) \triangleq i_L$$

$$v_C^{\cdot}(t) = 0 \rightarrow -\frac{v_C^2}{R_L C} + \frac{i_L}{C} = 0$$

$$i_L^{\cdot}(t) = 0 \rightarrow -\frac{v_C}{L} - \frac{R}{L} i_L = 0$$

$$V_c = -2 I_L$$

$$V_c^2 = R_L I_L$$

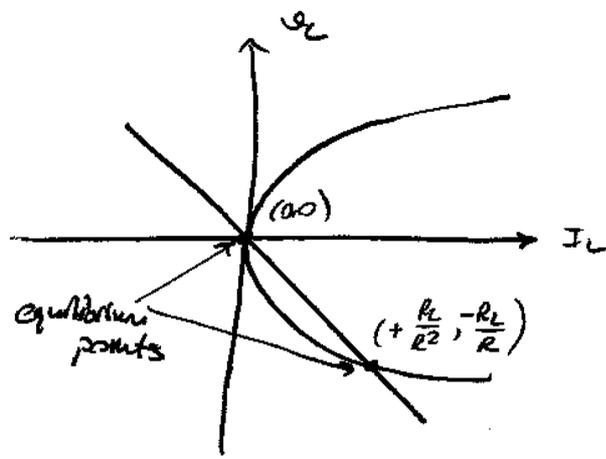

① In the following circuit $|V_L| = 240$ V (RMS) at all times. The following information about the loads are given:


d_1 : absorbs 180 Watts and 240 VARs.

d_2 : absorbs 600 VA at 0.6 pf lagging


a) Assume there is no capacitor connected between a-b terminals. Find input impedance at the load side, source voltage $|V_S|$ (in RMS) and p.f. on source side.

b) Now, the capacitor is connected between a-b terminals. Find value of C such that average power absorbed by 5 ohm resistor is minimum. Find $|V_S|$ with the compensation capacitor.

c) Find value of C such that load side p.f. is 0.9 lagging. Find $|V_S|$ with compensation capacitor.

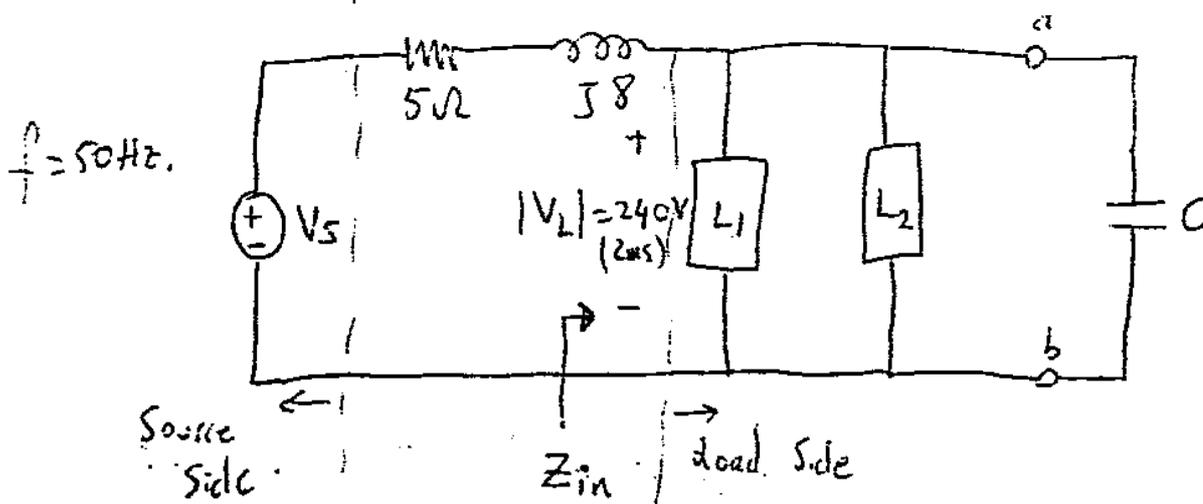

1

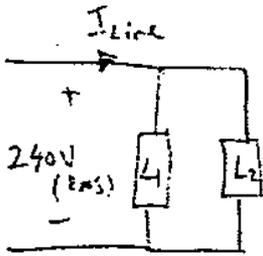

$$S_{L1} = 180 + j240$$


$$+ S_{L2} = 600 \frac{1}{\cos^{-1}(0.6)} = 360 + j480$$

$$S_{total} = 540 + j720$$

a)

$$|I_{line}| = \frac{|S_{total}|}{240} = \frac{900}{240} = 3.75 \text{ A (RMS)}$$

$$S_{total} = |I_{line}|^2 Z \rightarrow Z = \frac{540 + j720}{(3.75)^2} = 38.4 + j51.2 = 64 \angle 53.1^\circ$$

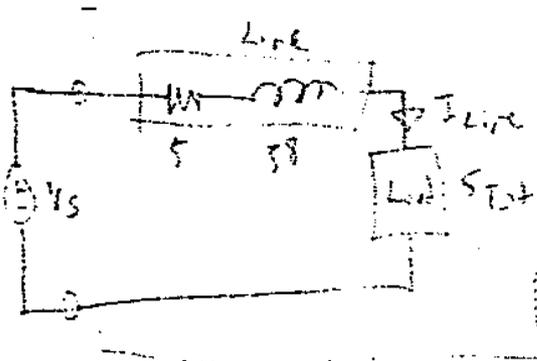

$$S_{line} = |I_{line}|^2 (5 + j8)$$

$$= 70.3125 + j112.5$$

$$S_{source} = S_{line} + S_{total}$$

$$= 610.31 + j832.5$$

$$|S_{source}| = |I_{line}| |V_s| \rightarrow |V_s| = \frac{|610.31 + j832.5|}{3.75} = 275.26 \text{ V RMS}$$

p.f. on source side $\cos(\tan^{-1} \frac{832.5}{610.31}) = 0.59$ lagging.

b) $S_{before} = 540 + j720$

$I_{line}^{before} = 3.75 \text{ A}$

$S_{after} = 540 + j720 - j720 = 540$

$I_{line}^{after} = \frac{540}{240} = 2.25 \text{ A}$

↑
compensation

$$S_{line} = (2.25)^2 (5 + j8) = 25.31 + j40.5$$

$$S_{source} = 540 + 25.31 + j40.5 \Rightarrow$$

$$S_{\text{source}} = 565.31 + j40.5 \quad (3)$$

$$|S_{\text{source}}| = 566.75 = |V_s| \cdot |I_{\text{line}}| \rightarrow$$

$$\rightarrow |V_s| = 251.89 \text{ V (RMS)}$$

$$S_{\text{compensator}} = -j720$$

$$S_{\text{compensator}} = \frac{|V_{\text{cap}}|^2}{X_C^*}$$


$$X_C = \frac{|V_{\text{cap}}|^2}{S_{\text{comp}}^*} = \frac{(240)^2}{j720} = -j80$$

$$X_C = \frac{-j}{\omega C}$$

$$X_C = -j80 \rightarrow C = \frac{1}{(2\pi \cdot 50)80} = 39.8 \mu\text{F}$$

(In this problem, to minimize power loss on line resistor, the current through the resistor should be minimized. Therefore load side pf should be 1.0 after compensation. to minimize loss)

c) After

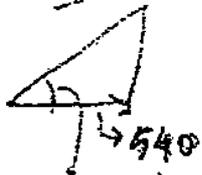

$$\cos^{-1}(0.9) = 25.84$$

$$S^{\text{After}} = 540 + j \tan(25.84^\circ) 540 = 540 + j261$$

$$S^{\text{After}} \equiv S^{\text{before}} + S^{\text{compensation}}$$

$$S^{\text{compensation}} = -j458.5$$

$$X_C = -j \frac{(240)^2}{458.5} = -j125.63; C = \frac{1}{(100\pi)125.6} = 25.3 \mu\text{F}$$

$$|I_{line}|^{after} = \frac{|S^{after}|}{240} = \frac{590/0.9}{240} = 2.5 \text{ A.} \quad (4)$$

$$S_{line} = (2.5)^2 (5 + j8) = 31.25 + j50$$

$$S_{source} = 571.25 + j301.1 \text{ (supplied)}$$


$$|S_{source}| = |V_s| \cdot |I_{line}| \rightarrow V_s = 258.27 \text{ V} \quad (RMS)$$

\uparrow 645 \uparrow 2.5


$$|S_{source}| = |V_s| \cdot |I_{line}| \rightarrow V_s = 258.27 \text{ V,} \quad (RMS)$$

\uparrow 645 \uparrow 2.5


2nd Order All-Pass Circuit:

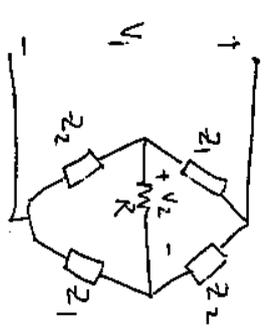

i) Z_{Th} seen by $R \rightarrow (Z_1 || Z_2) 2$.

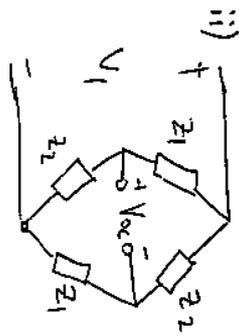
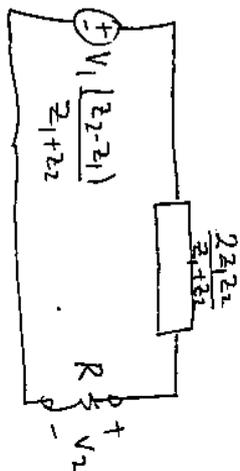
$$V_{oc} = V_1 \left(\frac{Z_2 - Z_1}{Z_1 + Z_2} \right)$$



$$\frac{V_2(s)}{V_1(s)} = ?$$

$$\frac{V_2(s)}{V_1(s)} = \frac{\left(\frac{Z_1^2 - Z_2^2}{Z_1 + Z_2} \right) R}{Z_1 + 2Z_2} \cdot \frac{R}{R(Z_1 + Z_2) + 2Z_1 Z_2}$$

$$\det Z_1 Z_2 = R^2$$

$$\frac{(Z_2 - Z_1)}{(Z_1 + Z_2) + 2R}$$

$$= \frac{Z_2(Z_2 - Z_1)}{Z_2(Z_1 + Z_2) + 2R}$$

$$H(s) = \frac{Z_2 - R}{Z_2 + R}$$

$$= \frac{Z_2 - R}{Z_2 + R}$$


$$|H(s)| = \frac{Z_2(s) - R}{Z_2(s) + R} \quad V_A(s) = \frac{sL - R}{sL + R} V_E(s)$$

then $Z_2(s)$: purely real $\rightarrow H(s) = \frac{R_2 - R}{R_2 + R}$, $Z_2 = R_2$

$\rightarrow |H(s)|$ is not function of $\omega \rightarrow$ but system does not contain any dynamic elements. Therefore it is just a voltage divider, not a filter.

② $Z_2(s)$: purely imaginary $\rightarrow H(s) = \frac{sX_2 - R}{sX_2 + R}$, $Z_2 = sX_2$


$\rightarrow |H(s)| = 1 \rightarrow$ we have dynamic system with an all-pass structure.

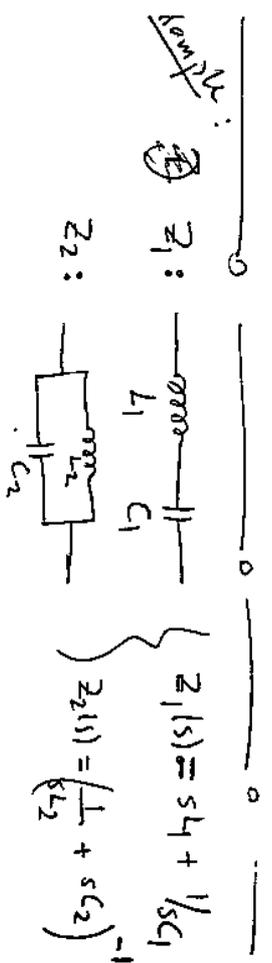

$Z_1: sL_1 + 1/sC_1$
 $Z_2: \frac{1}{sL_2 + sC_2}$
 $Z_1 \cdot Z_2 = R^2 \rightarrow Z_1 = \frac{R^2}{Z_2} \rightarrow sL_1 + \frac{1}{sC_1} = R^2 \left(\frac{1}{sL_2} + sC_2 \right)$

det $L_1 = R^2 C_2$
 $C_1 = L_2 / R^2$

Series RLC Band-Stop Filter

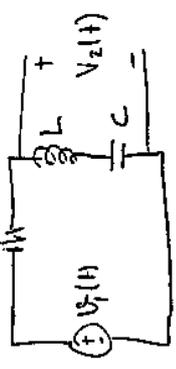


$$H(s) = \frac{V_2(s)}{V_1(s)} = \frac{sL + 1/sC}{sL + 1/sC + R} = \frac{s^2 + 1/LC}{s^2 + \frac{R}{L}s + 1/LC}$$


$$H(s) = \frac{(1/LC - \omega^2)}{(1/LC - \omega^2) + j\omega R/L}$$

Note: $|H(j\omega)| = 0$ for $\omega = \sqrt{1/LC}$

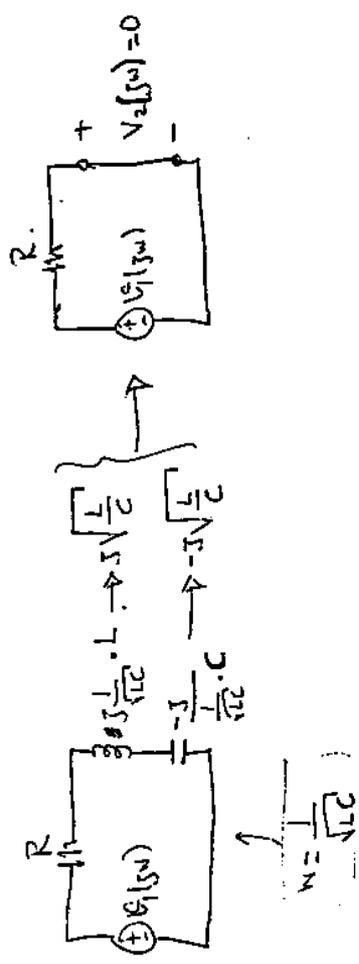Let's redraw the circuit at $\omega = 1/\sqrt{LC}$



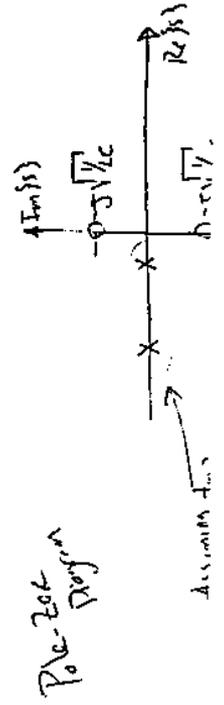Note that $V_2(s)$ source sees purely resistive circuit at $\omega = 1/\sqrt{LC}$. This phenomena is called resonance. (more on this later).



Then $H(s) = \frac{Z_2 - R}{Z_2 + R} = \frac{1 - RY_2}{1 + RY_2}$

$$= \frac{1 - \frac{R}{sL_2} - sRC_2}{1 + \frac{R}{sL_2} + sRC_2}$$


$$= - \frac{s^2 - \frac{1}{RC_2}s + \frac{1}{L_2C_2}}{s^2 + \frac{1}{RC_2}s + \frac{1}{L_2C_2}}$$

$$H(s) = - \frac{s^2 - 2\alpha\omega_0 s + \omega_0^2}{s^2 + 2\alpha\omega_0 s + \omega_0^2}$$

Note: If s_1, s_2 are roots of $s^2 + 2\alpha\omega_0 s + \omega_0^2 = 0$. Then $-s_1 - s_2$ are the roots of $s^2 - 2\alpha\omega_0 s + \omega_0^2 = 0$. (Why? $\sum \text{roots} = \text{sum of roots}$; ω_0^2 : product of roots)

Then $H(s) = - \frac{(s-p_1)(s-p_2)}{(s+p_1)(s+p_2)}$

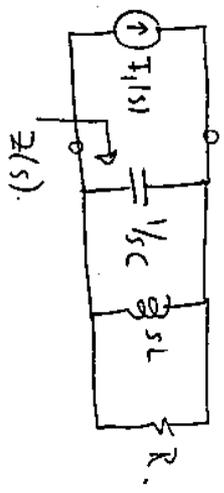Note: This picture shows that system is all-pass.



$$Z(s) = \frac{1}{1/sC + sL + R} = \frac{s/C}{s^2 + \frac{1}{RC}s + 1/LC}$$

Definition: The frequency for which $Z(s)$ is purely real is called the resonance frequency.

$$Z(s) = \frac{s/C}{-w^2 + 1/LC + s/C + w/LC} = \frac{w/C}{j(w^2 - 1/LC) + w/LC}$$


(We have studied this system under the title of 2nd order Band-Pass circuit)

is zero when $w = 1/\sqrt{LC}$


$$s^2 + \frac{1}{RC}s + \frac{1}{LC} \xrightarrow{w_0} \text{BW} = w_2 - w_1 = 2\sigma w_0 = 1/RC$$

$$w_0 = \sqrt{1/LC}, \quad 2\sigma = \frac{1}{R}\sqrt{\frac{L}{C}}$$

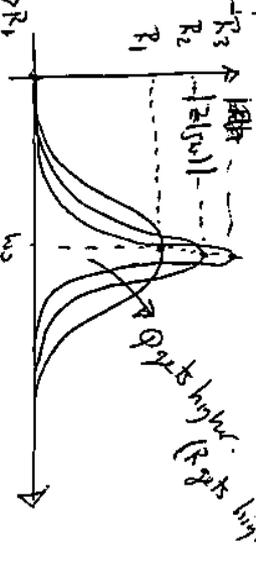Practice shows the impedance seen by the source for 3 parallel RLC circuits with $R_3 \gg R_2 \gg R_1$



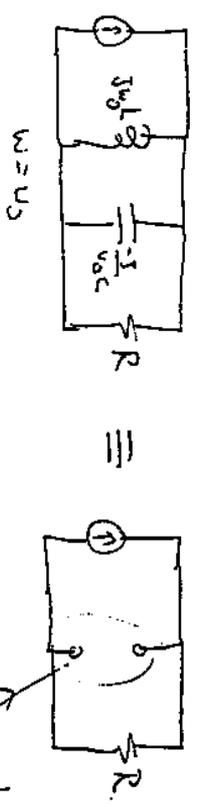3) The maximum impedance is seen at resonance freq. (6) (for parallel RLC) and it is equal to R. Note that



Another Interpretation for Q : Quality factor.

For parallel RLC circuit, the average energy stored in capacitor is $E_C = \frac{1}{2} C V_{eff}^2$; similarly the average magnetic energy stored in inductor is $E_L = \frac{1}{2} L I_{eff}^2$. Let's calculate the total energy stored in L and C.

$$E_T = E_C + E_L = \frac{1}{2} C V_{eff}^2 + \frac{1}{2} L \left(\frac{V_{eff}}{wL}\right)^2$$

$$= \frac{1}{2} \left(C + \frac{1}{w^2 L}\right) V_{eff}^2$$

$$= \frac{1}{2} C \left(1 + \frac{1}{w^2 LC}\right) V_{eff}^2$$

$$= \frac{1}{2} C \left(1 + \frac{w_0^2}{w^2}\right) V_{eff}^2$$


$$= \frac{1}{2} C w_0 \left(\frac{w}{w_0} + \frac{w_0}{w}\right) V_{eff}^2$$

Finite Q capacitors and Inductors.

In practice, it is not possible to have inductors which does not have any internal resistance. (Remember inductor \equiv coil)

Then any resonance circuit, that is containing both capacitors and inductors are effected by the internal resistance value.

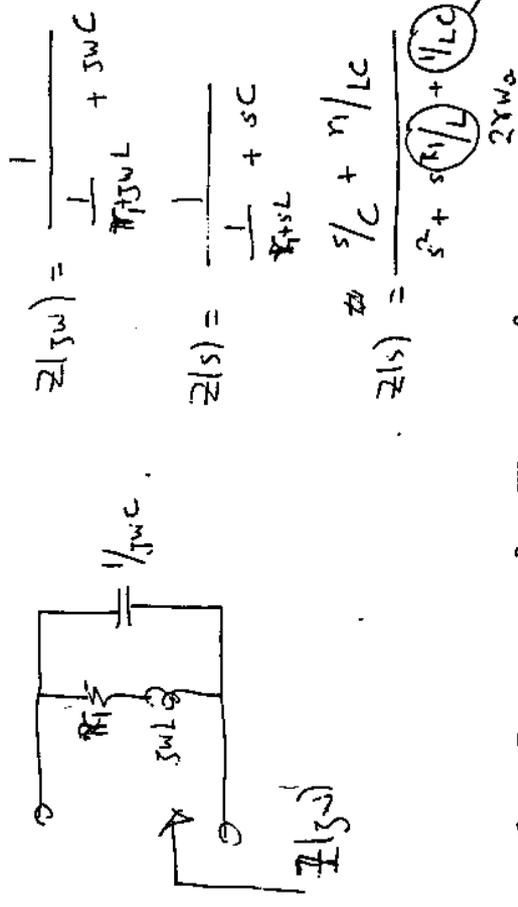Since resonance circuits are operated around the resonant freq, our analysis is focused on the behaviour around resonant freq.



$$Z(s) = \frac{1}{\frac{1}{R} + \frac{1}{sL} + sC}$$

$$Z(s) = \frac{1}{\frac{1}{R} + sC}$$


$$Z(s) = \frac{1}{s^2 + s\left(\frac{1}{L}\right) + \frac{1}{LC}}$$

$$s^2 + s\frac{R}{L} + \frac{1}{LC} = s^2 + 2\gamma\omega_0 s + \omega_0^2$$

ω_0 is not the resonance freq. or the frequency for which $|Z(s)|$ has a maxima.

$\gamma = \frac{R}{2L}$

7

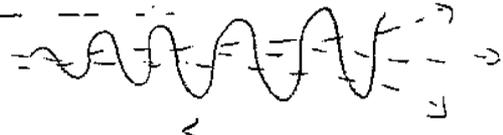

We will now show that at $\omega = \omega_0$

$$Q = 2\pi \cdot \frac{E T}{T P_R} \quad \left(\frac{Q}{\text{unitless}} \right) \text{ where } T = \frac{2\pi}{\omega_0}$$

where P_R is the average power consumed by R and $T \cdot P_R$ is the energy dissipated over R in a period.

$$\frac{2\pi E T}{T \cdot P_R} = \frac{\omega E T}{P_R} = \frac{\frac{1}{2} C \omega_0 \left(\frac{\omega}{\omega_0} + \frac{\omega_0}{\omega} \right) V_{eff}^2}{\frac{V_{eff}^2}{R}}$$

$$= \frac{RC\omega_0}{2} \left(\frac{\omega}{\omega_0} + \frac{\omega_0}{\omega} \right)$$

$$= R\sqrt{\frac{C}{L}} \left(\frac{\omega}{\omega_0} + \frac{\omega_0}{\omega} \right)$$

$$= \frac{Q}{2} \left(\frac{\omega}{\omega_0} + \frac{\omega_0}{\omega} \right)$$

for $\omega = \omega_0 \rightarrow \frac{2\pi E T}{T \cdot P_R} = Q, \quad T = \frac{2\pi}{\omega_0}$

Note: Resonant freq. is the freq. where maximum of $|Z(s)|$ for parallel RLC circuit; BUT this is not ω_0 . $T \cdot P_R$ is the energy of maximum of $|Z(s)|$.

there

$$Z(s) = \frac{5s/c + r/lc}{s^2 + r/lc} = \frac{1}{c} \frac{(r/lc)}{(w_a^2 - w^2) + jw r/lc}$$

$$= \frac{1}{c} \frac{(r/lc)}{(w_a^2 - w^2) + jw w_a/q}$$

$$= \frac{1}{c} \frac{(r/lc)}{(w_a^2 - w^2) + jw w_a/q}$$

for $Z(s)$ to be purely real, angle of numerator and denominator of $Z(s)$ should be same \rightarrow so

$$\frac{w_a/q}{w_a/c} = \frac{r w_a/q}{w_a^2 - w^2}$$

$$\left(\frac{w_a}{q}\right)^2 = w_a^2 - w^2$$

$$w^2 = w_a^2 \left(1 - \frac{1}{q^2}\right)$$

$$w = w_a \sqrt{1 - \frac{1}{q^2}}$$

then $w_0 = w_a \sqrt{1 - 1/q^2}$ is the resonant freq.

$$Z(jw_0) = \frac{1}{c} \frac{(r/lc)}{(w_0^2 - w_0^2) + jw_0 r/lc}$$

$$= \frac{1}{c} \frac{r/lc}{jw_0 r/lc} = \frac{r/lc}{c w_0 r/lc} = \frac{1}{c w_0}$$

$$= \frac{1}{c w_0} = \frac{1}{c w_a \sqrt{1 - 1/q^2}}$$

$$= \frac{1}{c w_a} \frac{1}{\sqrt{1 - 1/q^2}}$$

$$= \frac{1}{c w_a} \frac{q}{\sqrt{q^2 - 1}}$$

$$= \frac{q}{c w_a \sqrt{q^2 - 1}}$$

Ex: a) $r = 50 \Omega$, $L = 10 \text{ mH}$, $C = 4 \mu\text{F}$


then $w_a = 1/\sqrt{LC} = 10^4 \text{ rad/sec}$

$$Q = \frac{w_a}{r/L} = 2 \text{ (unitless)}$$

$$w_0 = w_a \sqrt{1 - 1/Q^2} = 10^4 \sqrt{1 - 1/4} = 8.66 \text{ k rad/sec}$$


$$Z(j0) = 50 \Omega, \quad Z(jw_0) = Q^2 r = 200 \Omega; \quad Z(jw_a) = 223.606 \angle 23.1^\circ$$

$$Z(jw_m) = 223.89 \angle 23.1^\circ$$


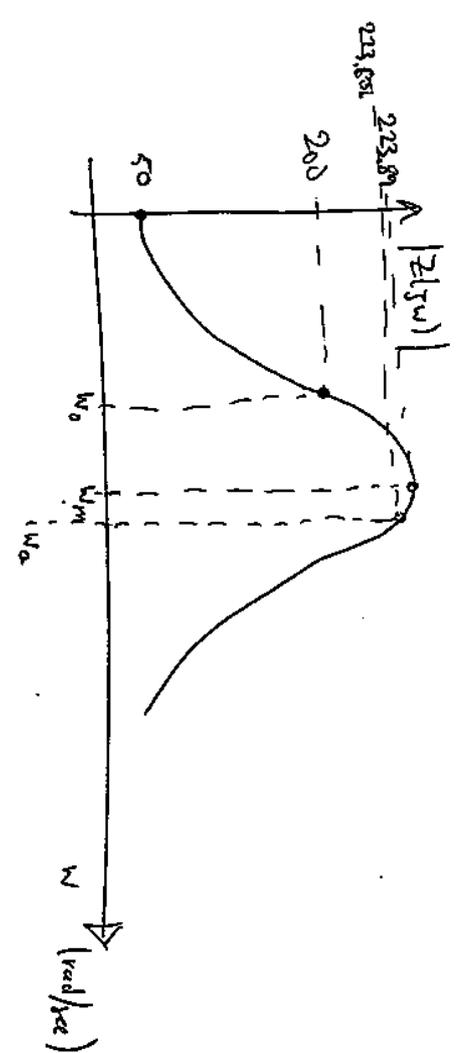


$w_a = \sqrt{1/LC}$
 w_m : should be found by taking derivative of $|Z(jw)|$ wrt. w .
 $w_0 = w_a \sqrt{1 - 1/Q^2}$ \leftarrow resonant freq. of frack-circuit.

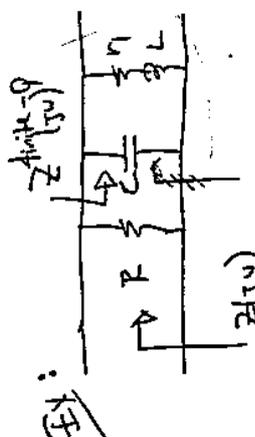close to ω_m . As $Q \rightarrow \infty$, ω_0 and ω_m approaches ω_0 . But note that $Q=2$ is close enough for many purposes in this example.



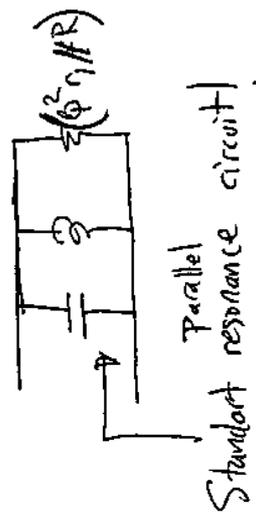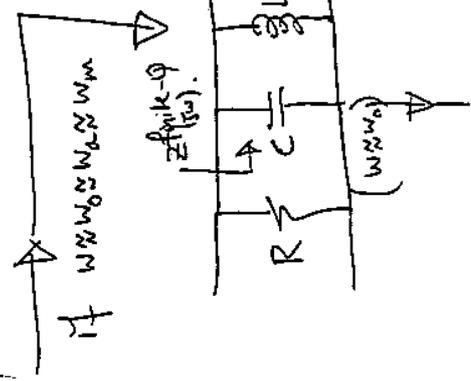Find $Z(s)$, and assume that ω_0 is resonant frequency of this system.



$$\omega_p = \omega_0 \sqrt{1 - \frac{1}{2Q^2}}$$

$Q > \frac{1}{\sqrt{2}}$

