

Question 1 (20 pts) For some lumped circuit N , made of single branch elements, a fundamental loop matrix B is given below.




$$B = \begin{bmatrix} 1 & 2 & 3 & 4 & 5 & 6 & 7 \\ 0 & 0 & -1 & 1 & 1 & 0 & 0 \\ -1 & -1 & 0 & 1 & 0 & 1 & 0 \\ 0 & -1 & 0 & 1 & 0 & 0 & 1 \end{bmatrix} \xrightarrow{\text{F}} \xrightarrow{\text{I}}$$

branch numbers

- Obtain a possible graph of circuit N .
- Write the corresponding fundamental cutset matrix Q .
- Let \hat{N} be the dual circuit of N . Some of the branch currents (in Amps) and voltages (in Volts) of dual circuit \hat{N} are given below. Find the missing currents and voltages.

$\hat{i}_1 = ?$	$\hat{i}_2 = 3$	$\hat{i}_3 = ?$	$\hat{i}_4 = 1$	$\hat{i}_5 = 1$	$\hat{i}_6 = 6$	$\hat{i}_7 = ?$
$\hat{v}_1 = ?$	$\hat{v}_2 = -5$	$\hat{v}_3 = -1$	$\hat{v}_4 = ?$	$\hat{v}_5 = ?$	$\hat{v}_6 = ?$	$\hat{v}_7 = 3$

a)

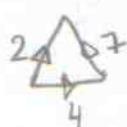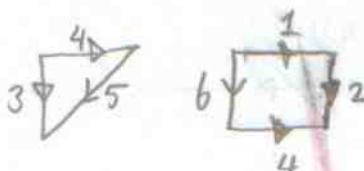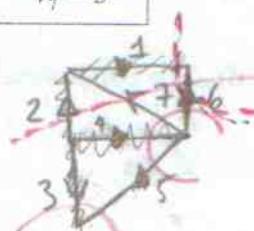 \rightarrow 

b)

$$Q = \left[\begin{array}{ccccccc}
1 & 2 & 3 & 4 & 5 & 6 & 7 \\
1 & 0 & 0 & 0 & 1 & 0 & 0 \\
0 & 1 & 0 & 0 & 0 & +1 & 0 \\
0 & 0 & 1 & 0 & +1 & 0 & 0 \\
0 & 0 & 0 & 1 & -1 & -1 & -1
\end{array} \right] \xrightarrow{\text{-F}^T}$$

c) Then N satisfies

$v_1 = 2$	$v_2 = 3$	$v_3 = -1$	$v_4 = 1$	$v_5 = 1$	$v_6 = 6$	$v_7 = -3$
$i_1 = -$	$i_2 = -5$	$i_3 = -1$	$i_4 = -$	$i_5 = -$	$i_6 = -$	$i_7 = 3$

From graph $\rightarrow v_1 = -v_2 + v_4 + v_6 = 4V \rightarrow \hat{i}_1 = 4A$
 $v_3 = v_4 + v_5 = 2V \rightarrow \hat{i}_3 = 2A$
 $v_7 = +v_2 - v_4 = +2V \rightarrow \hat{i}_7 = +2A$

From graph $\rightarrow i_1 = i_2 + i_7 = -2A \rightarrow \hat{v}_1 = -2V$



$i_4 = -i_2 - i_3 = 6A \rightarrow \hat{v}_4 = 6V$

$i_5 = -i_3 = 1A \rightarrow \hat{v}_5 = 1V$

$i_6 = -i_1 = +2A \rightarrow \hat{v}_6 = 2V$

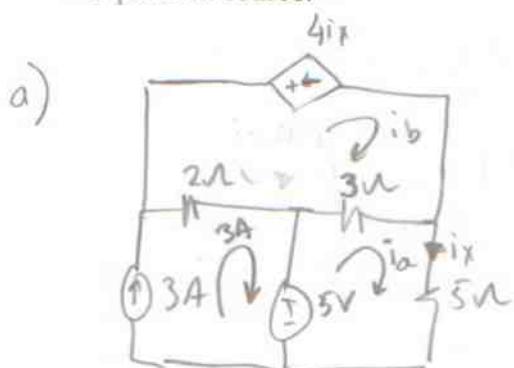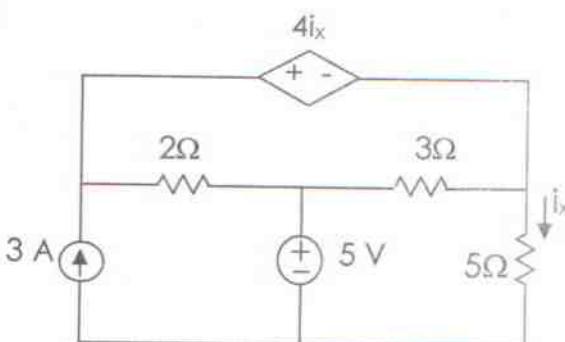
Question 2 (20 pts) Given the following circuit,

- Obtain the mesh equation(s) and put into the matrix form.
- Obtain the node equation(s).
- Find the power supplied / absorbed by the dependent source.



$$\begin{aligned} \text{KVL } i_b &\rightarrow +4i_x + 2(i_b - 3) + 3(i_b - i_a) = 0 \\ \text{KVL } i_a &\rightarrow 5i_a - 5 + 3(i_a - i_b) = 0 \end{aligned}$$

$$\left[\begin{array}{c|c} 1 & 5 \\ 8 & -3 \end{array} \right] \begin{bmatrix} i_a \\ i_b \end{bmatrix} = \begin{bmatrix} 6 \\ 5 \end{bmatrix}$$

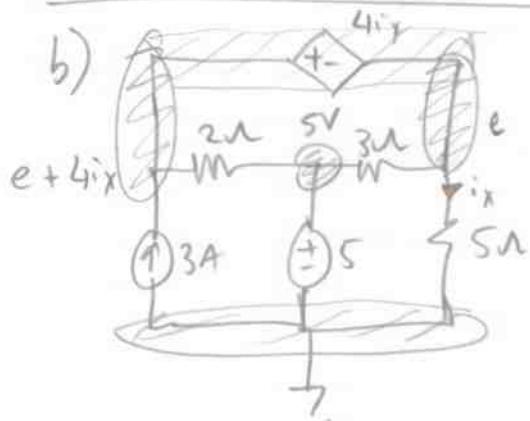


$$\begin{aligned} \text{KCL supernode} &\rightarrow \\ \frac{e}{5} + \frac{e-5}{3} + \frac{e+4i_x - 5}{2} - 3 &= 0 \end{aligned}$$

$$\left(\frac{1}{5} + \frac{1}{3} + \frac{9}{10} \right) e = \frac{5}{3} + \frac{5}{2} + 3$$

$$e = \frac{50 + 75 + 90}{6 + 10 + 27} = \frac{215}{43}$$




$$e = 5V$$

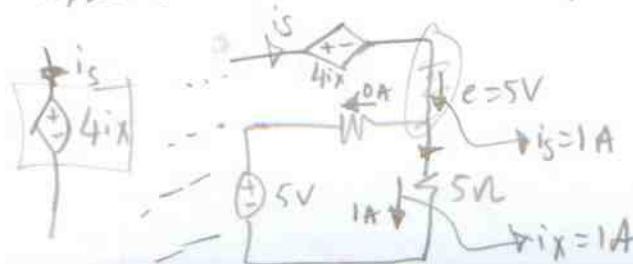c) $P_{4ix\text{source}} = i_s \cdot 4i_x \rightarrow P_{4ix\text{Source}} = 1 \cdot (4 \cdot 1) = 4W \text{ absorbed.}$



Question 3 (20 pts)

Find the Thevenin equivalent circuit to the left of terminals a and b.

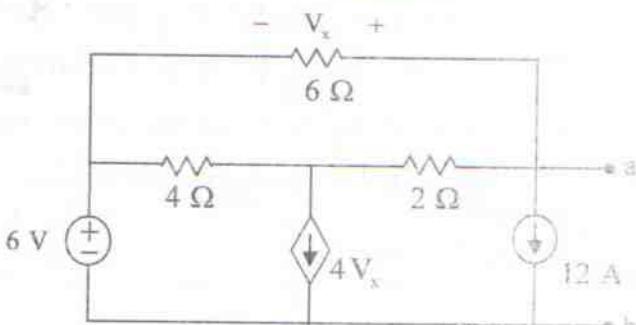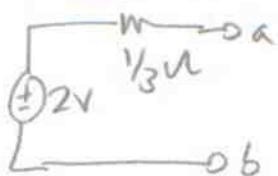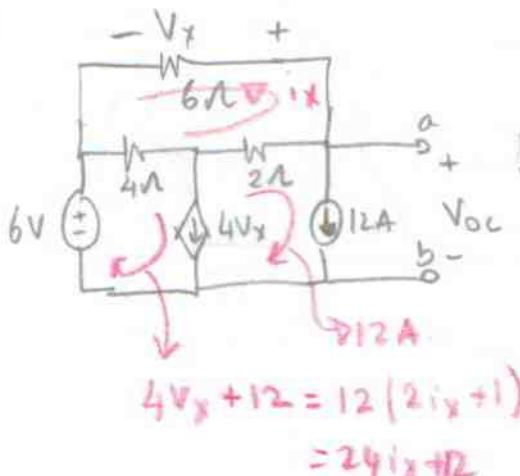Answer:a) V_{oc} :


$$V_x = 6ix$$

KVL ix loop:

$$6ix + 4(4ix + 24ix + 12) + 2(2ix + 12) = 0$$

$$ix = \frac{-48 - 24}{100 + 6 + 2} = \frac{-72}{108} = -\frac{2}{3}$$

$$\boxed{V_x = -4V} \rightarrow \boxed{V_{oc} = 6 + V_x = 2V}$$

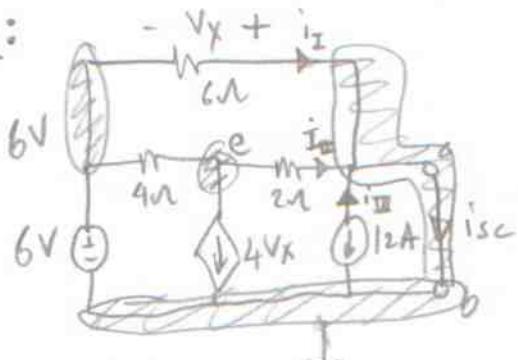 i_{sc} :


$$R_{Th} = \frac{V_{oc}}{i_{sc}} = \frac{2}{6} = \frac{1}{3} \Omega$$

 $KCL @ e$:

$$\frac{e - 6}{4} + \frac{e}{2} + 4V_x = 0 \rightarrow e = \frac{24 + 3/2}{3/4} = 34V$$

$$e = 34V$$

$$\boxed{i_{sc} = i_I + i_{II} + i_{III}} \\ = 1 + 17 + (-12) = 6A$$

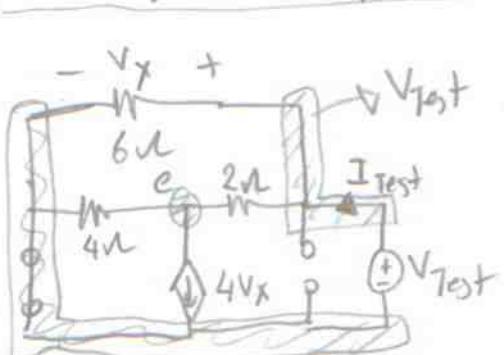Test Voltage Method for R_{Th} :

$$V_x = V_{test}$$

$$\frac{e}{4} + \frac{e - V_{test}}{2} + 4V_x = 0 \rightarrow e = -\frac{3.5}{0.75} V_{test}$$


$$e = -\frac{14}{3} V_{test}$$

$$I_{test} = \frac{V_x + V_{test} - e}{2} = V_{test} \left(\frac{1}{6} + \frac{1}{2} + \frac{14}{6} \right) = \frac{3}{3} V_{test}$$

$$\frac{V_{test}}{I_{test}} = \frac{1}{3} \rightarrow \boxed{R_{Th} = \frac{1}{3} \Omega}$$


Question 4 (20 pts)

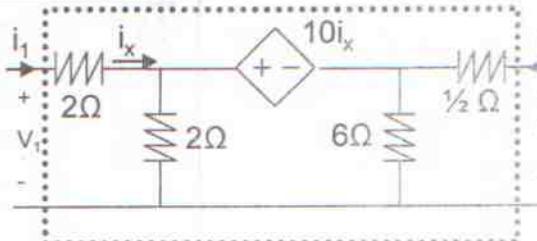- a) Find the *resistance (open circuit) parameters* of the following two port.




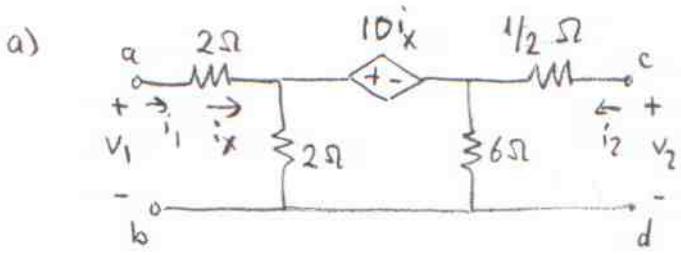- b) The two port shown in part (a) is used in the following configuration. Determine R_L so that it absorbs maximum power. Also compute this power.





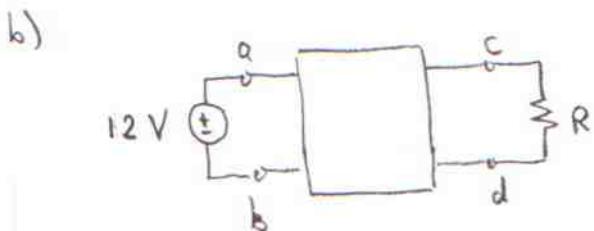
Find the resistance (open circuit) parameters.



Determine R so that it absorbs the maximum power.

Also compute this power.

Solution

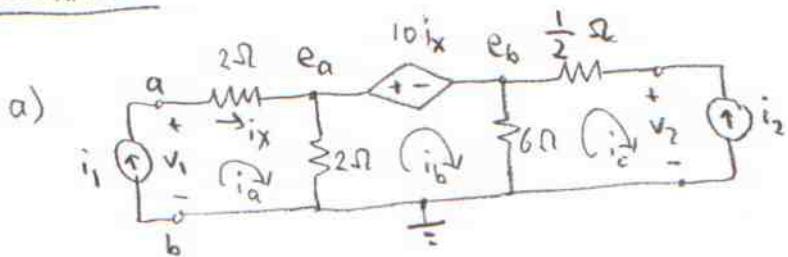

$$i_x = i_1$$

$$e_a = e_b + 10i_x = e_b + 10i_1$$

$$-i_1 + \frac{1}{2}e_a + \frac{1}{6}e_b - i_2 = 0 \Rightarrow \frac{2}{3}e_b = -4i_1 + i_2 \Rightarrow e_b = -6i_1 + \frac{3}{2}i_2$$


$$e_a = 4i_1 + \frac{3}{2}i_2$$

\uparrow
 $e_b + 10i_1$

$$v_1 = 2i_1 + e_a = 6i_1 + \frac{3}{2}i_2$$

$$v_2 = e_b + \frac{1}{2}i_2 = -6i_1 + \frac{3}{2}i_2 + \frac{1}{2}i_2 = -6i_1 + 2i_2$$

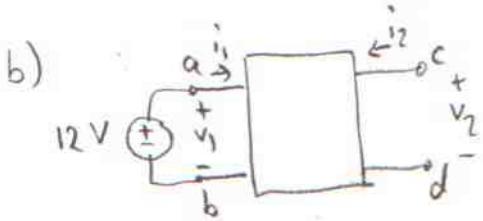
$$\begin{bmatrix} v_1 \\ v_2 \end{bmatrix} = \begin{bmatrix} 6 & 3/2 \\ -6 & 2 \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \end{bmatrix}$$



$$v_1 = 12 \text{ V}$$

$$6i_1 + \frac{3}{2}i_2 = 12 \Rightarrow i_1 = 2 - \frac{1}{4}i_2$$
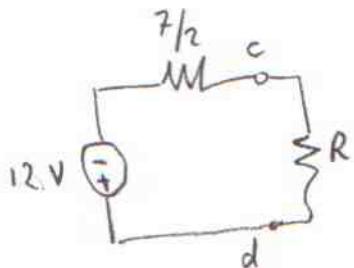
$$v_2 = -6\left(2 - \frac{1}{4}i_2\right) + 2i_2 = -12 + \frac{3}{2}i_2 + 2i_2 = -12 + \frac{7}{2}i_2$$



$$R = \frac{7}{2} \Omega$$

$$P = \frac{144}{4 \times \frac{7}{2}} = \frac{72}{7} \text{ W}$$

$$i_a = i_1, \quad i_c = -i_2, \quad i_x = i_a = i_1$$

$$10i_x + 6(i_b - i_c) + 2(i_b - i_a) = 0 \Rightarrow 10i_1 + 8i_b + 6i_2 - 2i_1 = 0$$

$\uparrow \quad \uparrow \quad \uparrow$
 $i_1 \quad -i_2 \quad i_1$

$$8i_b = -8i_1 - 6i_2$$

$$i_b = -i_1 - \frac{3}{4}i_2$$

$$v_1 = 2i_a + 2(i_a - i_b) = 4i_1 + 2i_1 + \frac{3}{2}i_2 = 6i_1 + \frac{3}{2}i_2$$

$$v_2 = 6(i_b - i_c) - \frac{1}{2}i_c = -6i_1 - \frac{9}{2}i_2 + \frac{13}{2}i_2 = -6i_1 + 2i_2$$

Question 5 (10 pts) Using the voltage and current values indicated on the circuit of Figure 1, find the power supplied/absorbed by the independent current source of the circuit of Figure 2.

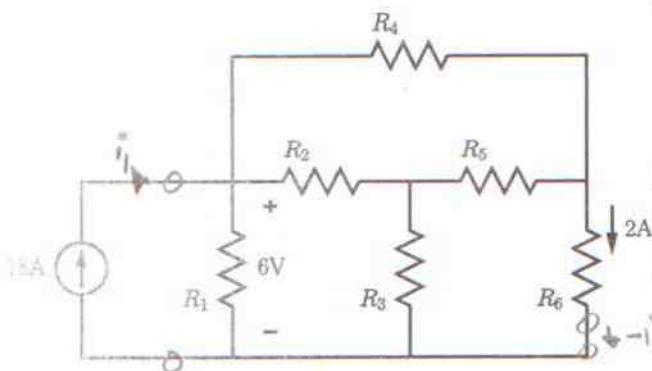


Figure 1


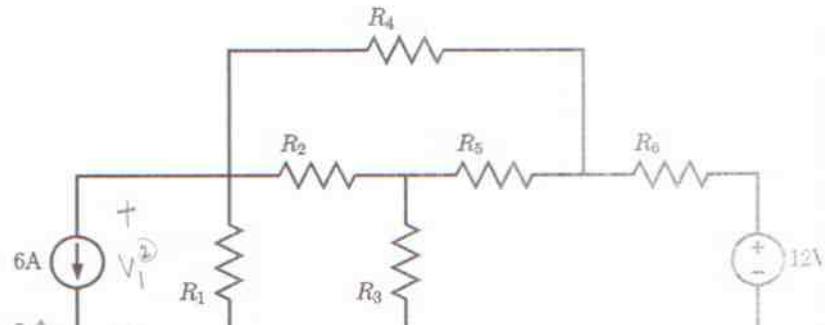


Figure 2

Find $V_1^{(2)}$ then power of 6A source

A: Kill 12V source first →


(A):

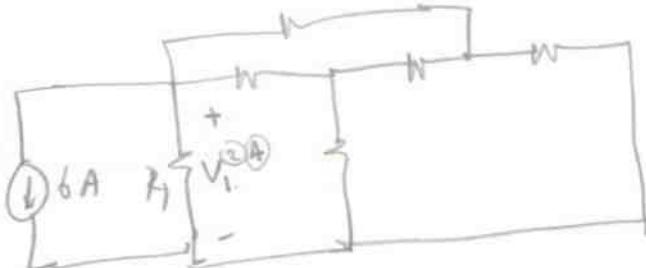

$$\text{Then } V_1^{(2A)} = 6 \cdot \frac{-6}{18} = -2 \text{ V (by linearity)}$$

B: Kill 6A source then →

(B):

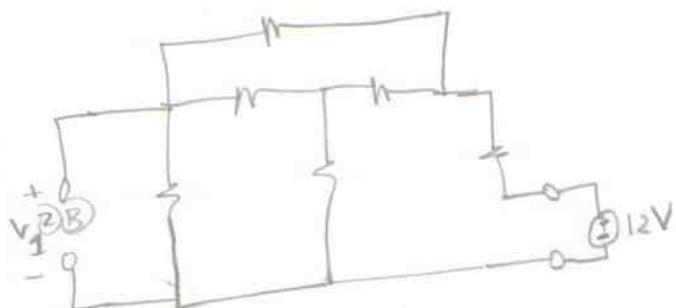

$$V_1^{(2B)} = h_{12} 12 \quad \left(\text{due to reciprocity} \right)$$

$$h_{12} = -h_{21} = -\frac{2}{18}$$


$$= \frac{4}{3} V_1^{(2A)}$$

$$V_1^{(2)} = V_1^{(2A)} + V_1^{(2B)} = -2 + \frac{4}{3} = -\frac{2}{3}$$

$$P_{\text{absorbed}} = V_1^{(2)} \cdot 6 = -4 \text{ W} \rightarrow \boxed{4 \text{ W supplied}}$$

Name:

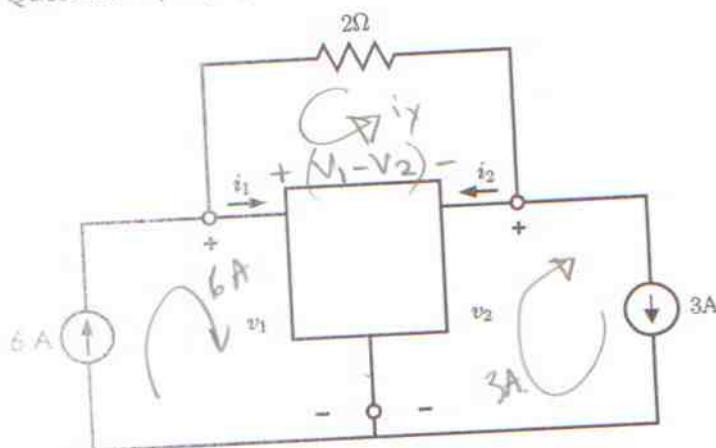Question 6 (10 pts) Find the powers delivered to the resistor and to the three-terminal element.



$$\begin{bmatrix} v_1 \\ v_2 \end{bmatrix} = \begin{bmatrix} 0 & 4 \\ -4 & 0 \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \end{bmatrix}$$

meshes - # current sources
 $\Rightarrow 3 - 2 = 1$ unknown

KVL in i_x loop:


$$2i_x + v_1 - v_2 = 0 \rightarrow 2i_x + 4(i_1 + i_2) = 0$$

3

$$i_x = -6$$

$$i_1 = i_x + 6 = 0 \text{ A}, \quad v_1 = 12 \text{ V}$$
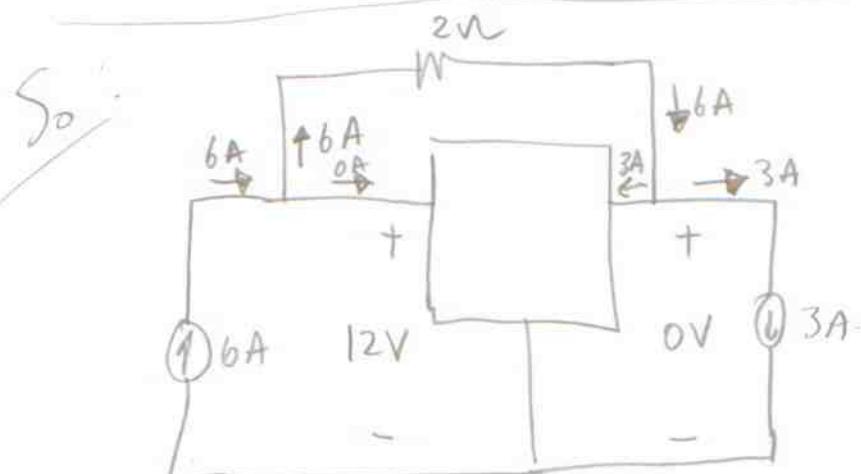
$$i_2 = -i_x - 3 = 3 \text{ A}, \quad v_2 = 0 \text{ V}$$



$$P_{2\Omega} = 6^2 \cdot 2 = 72 \text{ W}$$

$$P_{\text{comp}} = i_1 v_1 + i_2 v_2 \\ = 0 \cdot 12 + 3 \cdot 0 \\ = 0 \text{ W.}$$