
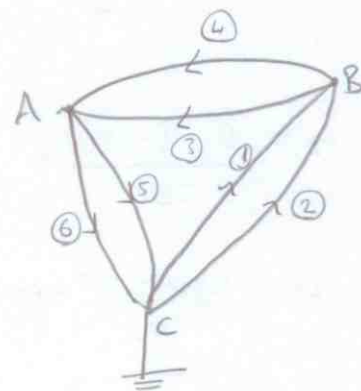


1)

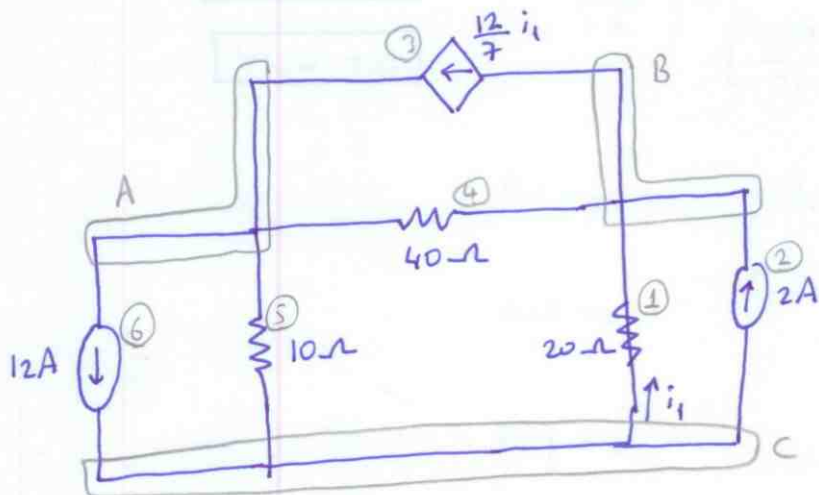

a) $A = \begin{bmatrix} 0 & 0 & -1 & -1 & 1 & 1 \\ -1 & -1 & 1 & 1 & 0 & 0 \end{bmatrix}$

$J = \begin{bmatrix} J_1 \\ J_2 \\ J_3 \\ J_4 \\ J_5 \\ J_6 \end{bmatrix}$

① $A \cdot J = \begin{bmatrix} 0 \\ 0 \end{bmatrix}$ (KCL)

② $V = A^T \cdot e = \begin{bmatrix} 0 & -1 \\ 0 & -1 \\ -1 & 1 \\ -1 & 1 \\ 1 & 0 \\ 1 & 0 \end{bmatrix} \begin{bmatrix} e_A \\ e_B \end{bmatrix} = \begin{bmatrix} V_1 \\ V_2 \\ V_3 \\ V_4 \\ V_5 \\ V_6 \end{bmatrix} \Rightarrow \begin{matrix} V_1 = -e_B \\ V_2 = -e_B \\ V_3 = e_B - e_A \\ V_4 = e_B - e_A \\ V_5 = e_A \\ V_6 = e_A \end{matrix}$

③ $J = G \cdot V + J_s \xrightarrow{\text{multiply by } A} A \cdot J = A \cdot G \cdot V + A \cdot J_s$

using ② and ③ $A \cdot J = A \cdot G \cdot A^T \cdot e + A \cdot J_s = 0$ (by # ①)

so; $e = -(AGA^T)^{-1} \cdot A \cdot J_s$

$$e = - \left(\begin{bmatrix} 0 & 0 & -1 & -1 & 1 & 1 \\ -1 & -1 & 1 & 1 & 0 & 0 \end{bmatrix} \begin{bmatrix} 1/20 & 0 & 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 & 0 & 0 \\ 0 & 0 & 1/40 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 & 1/10 & 0 \\ 0 & 0 & 0 & 0 & 0 & 0 \end{bmatrix} \begin{bmatrix} 0 & -1 \\ 0 & -1 \\ -1 & 1 \\ -1 & 1 \\ 1 & 0 \\ 1 & 0 \end{bmatrix} \right) \cdot A \cdot J_s$$

$$-\left(\frac{1}{40} \begin{bmatrix} 5 & -1 \\ -1 & 3 \end{bmatrix}\right)^{-1} \cdot A \cdot J_s = -\frac{20}{7} \begin{bmatrix} 3 & 1 \\ 1 & 5 \end{bmatrix} \begin{bmatrix} 0 & 0 & -1 & -1 & 1 & 1 \\ -1 & -1 & 1 & 1 & 0 & 0 \end{bmatrix} \begin{bmatrix} 0 \\ 2 \\ 0 \\ -\frac{3e_B}{35} \\ 0 \\ 12 \end{bmatrix}$$

$$e = \begin{bmatrix} e_A \\ e_B \end{bmatrix} = \begin{bmatrix} 34 + \frac{6e_B}{35} \\ 2 - \frac{12e_B}{35} \end{bmatrix} \cdot \left(\frac{-20}{7}\right)$$


$e_B = -280V$

$e_A = 40V$


$$i_1 = \frac{0 - (-280)}{20} = 14A$$

$$i_3 = \frac{-280 - 40}{40} = -8A$$


$$i_5 = \frac{40 - 0}{10} = 4A$$

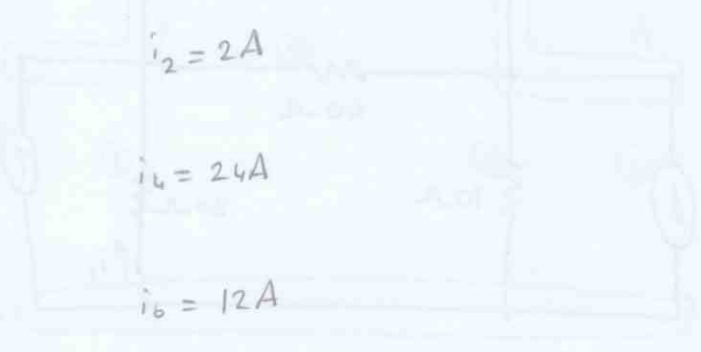

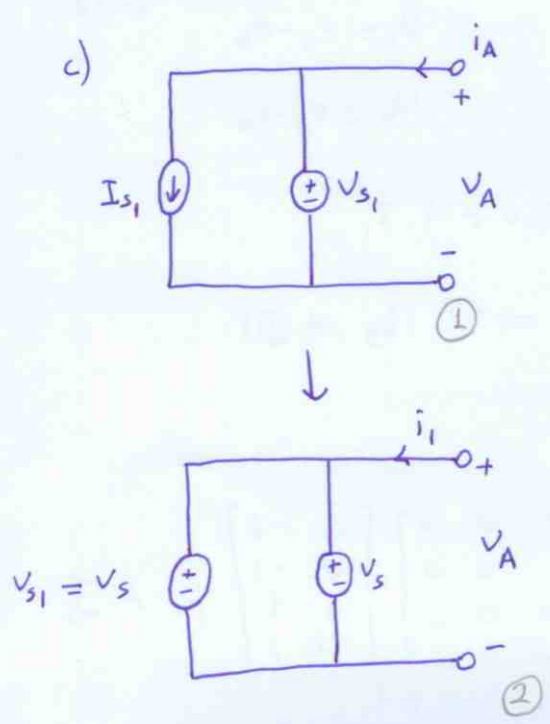
b) Since the circuit in part a has a unique soln., we may change any of the circuit element with an appropriate one. In part A since $V_A - V_B = 40V$, if we change the 10Ω resistance with $40V$ voltage source, there will not any change for other values. Therefore; i_1 is still 14A.



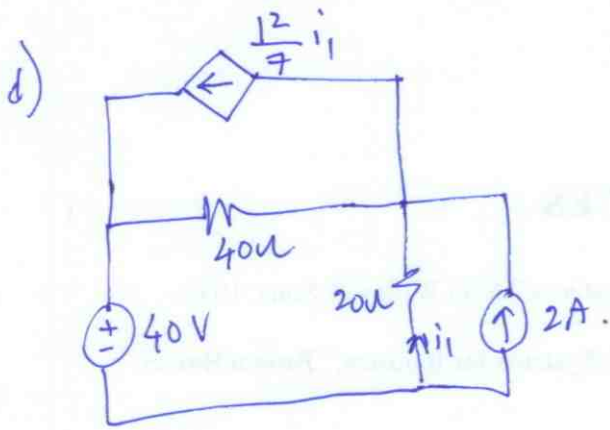Like part b, we can use substitution theorem for this part. We can change current source with a voltage source without affecting other circuit elements. (figure 2). After changing it, we have two parallel voltage sources. The final voltage source is equal to both of them (because they are parallel)




Mesh Analysis:

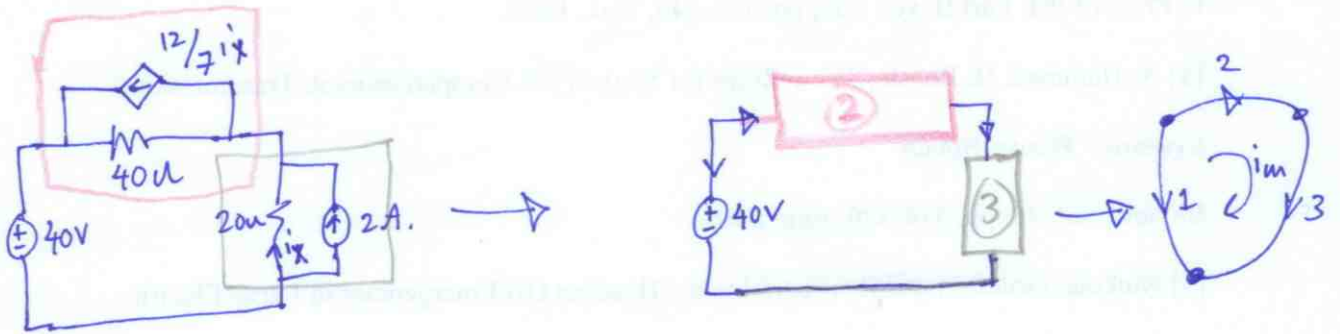

① $-v_1 + v_2 + v_3 = 0 \rightarrow [-1 \ 1 \ 1] \underline{v} = 0 \rightarrow \underline{M} = [-1 \ 1 \ 1]$


② $\underline{J} = \underline{M}^T \underline{i}_m$ (i_m : mesh current, the unknown)

③ Branch eq. ① $v_1 = 40$ ✓

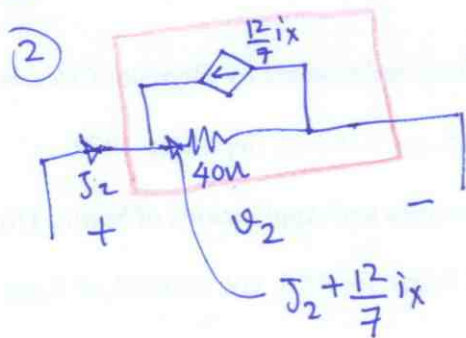

$v_2 = 40 (J_2 + \frac{12}{7} i_x)$ ✗

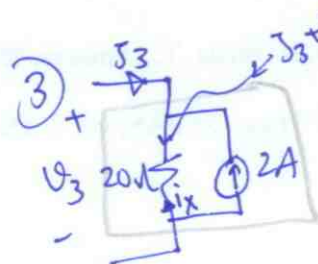i_x (should be expressed in terms of J_k 's)



$v_3 = (J_3 + 2) 20$ ✓

$i_x = -(J_3 + 2)$

$v_2 = \frac{40}{7} (J_2 + \frac{12}{7} (J_3 + 2))$ ✓

Then
$$\begin{bmatrix} v_1 \\ v_2 \\ v_3 \end{bmatrix} = \begin{bmatrix} 0 & 0 & 0 \\ 0 & 40 & -480/7 \\ 0 & 0 & 20 \end{bmatrix} \begin{bmatrix} J_1 \\ J_2 \\ J_3 \end{bmatrix} + \begin{bmatrix} 40 \\ -960/7 \\ 40 \end{bmatrix}; \underline{v} = \underline{R} \underline{J} + \underline{v}_s$$

$$\left. \begin{array}{l} \textcircled{1} \underline{M} \underline{v} = 0 \\ \textcircled{2} \underline{J} = \underline{M}^T \underline{i}_m \\ \textcircled{3} \underline{v} = \underline{R} \underline{J} + \underline{v}_s \end{array} \right\} \rightarrow \underline{M} \underline{v} = 0 = \left(\underline{M} \underline{R} \underline{M}^T \right) \underline{i}_m + \underline{M} \underline{v}_s$$

$$\left(\underline{M} \underline{R} \underline{M}^T \right) = [-1 \ 1 \ 1] \begin{bmatrix} 0 & 0 & 0 \\ 0 & 40 & -480/7 \\ 0 & 0 & 20 \end{bmatrix} \begin{bmatrix} -1 \\ 1 \\ 1 \end{bmatrix} = 60 - \frac{480}{7}$$

$$\underline{M} \underline{v}_s = [-1 \ 1 \ 1] \begin{bmatrix} 40 \\ -960/7 \\ 40 \end{bmatrix} = \frac{-960}{7}$$

$$\left(\underline{M} \underline{R} \underline{M}^T \right) \underline{i}_m = -\underline{M} \underline{v}_s \rightarrow \left(60 - \frac{480}{7} \right) \underline{i}_m = \frac{960}{7}$$

$$\underline{i}_m = -16 \text{ A.}$$


Then $\textcircled{2} \underline{J} = \underline{M}^T \underline{i}_m = \begin{bmatrix} -1 \\ 1 \\ 1 \end{bmatrix} 16 \text{ A.} = \begin{bmatrix} +16 \\ -16 \\ -16 \end{bmatrix} \text{ A.}$

$$\textcircled{3} \underline{v} = \underline{R} \underline{J} + \underline{v}_s = \begin{bmatrix} 40 \\ \frac{40 \cdot (-16) - 960}{7} \\ 20(-16) + 40 \end{bmatrix}$$

$\frac{40 \cdot (-16) - 960}{7} \rightarrow \frac{-1280 - 960}{7} = \frac{-2240}{7} = -320 \text{ V}$
 $20(-16) + 40 = -320 + 40 = -280 \text{ V}$

$$i_x = -(i_3 + 2) = 14 \text{ A.}$$

S₀

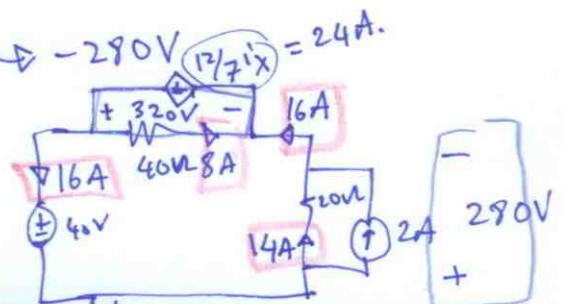

All satisfied!