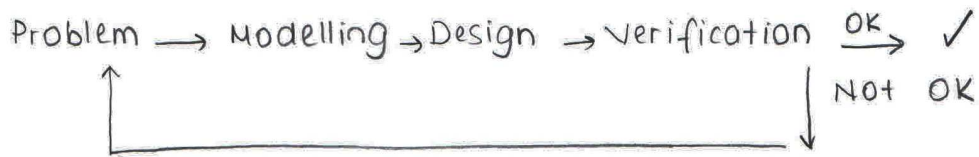


EE 201 Circuit Theory I  
Instructor : Çağatay Candan



Introduce :

- ① Models of electric components
- ② Relations for physical principles
- ③ Analysis Methods
- ④ Design principles/ examples


charge, current, voltage, power, energy, flux  
q: coulombs (c)

①  
②  
charge/sec : charge transferred per second is current

$$i(t) = \frac{dQ(t)}{dt} \approx \frac{Q(t+\Delta) - Q(t)}{\Delta} = \frac{\text{Coulomb}}{\text{seconds}}$$



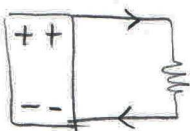Current direction shows the direction of moving (+) charges (sign and direction)



Units: Voltage

$$\begin{array}{ccc}
 + \bullet A & & - \bullet A \\
 5V & = & -5V \\
 - \bullet B & & + \bullet B \\
 V_A = V_B + 5 & & V_A = V_B - (-5)
 \end{array}$$


energy : Joule's

$$W = q \cdot \Delta V$$

Power : Rate of energy changes (in watts)

$$P(t) = \frac{dW(t)}{dt}$$

Components have mathematical models

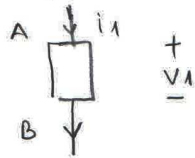


$$v_1(t) = R \cdot i_1(t) \quad \text{or} \quad i_1(t) = C \frac{dv_1(t)}{dt} \dots$$


### Electrical components

Resistance :

Node, Branch, Network

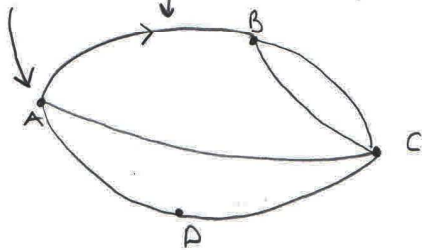


Resistance  
 $R (\Omega)$

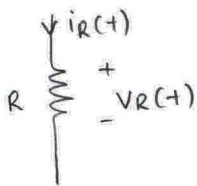


$$v_R(t) = R \cdot i_R(t)$$

Capacitor  
 $C (F)$

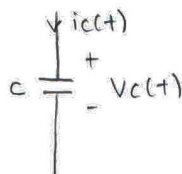


$$i_C(t) = C \frac{dv_C(t)}{dt}$$

Inductor  
 $L (H)$

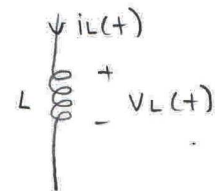


$$v_L(t) = L \frac{di_L(t)}{dt}$$

Passive sign convention:

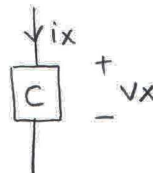


Lumped components, Lumped circuits

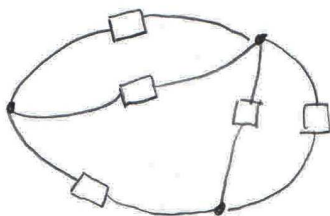


High frequency circuits, wires can act as inductors  
 $\lambda = c/f$  (circuit sizes) much smaller ( $\lambda$ )  
 ↑  
 wavelength


More components ;

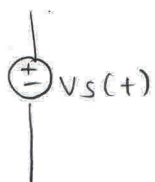

Independent voltage source

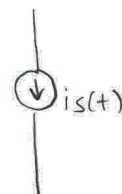


Independent current source


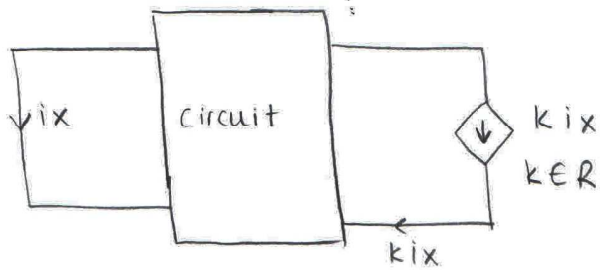


Dependent current source  
current controlled current source



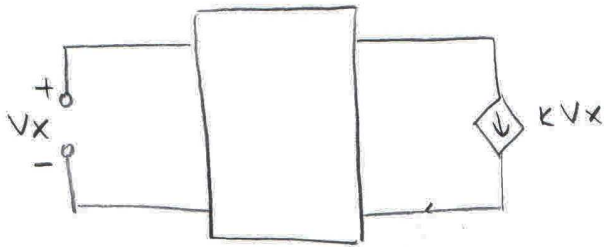
if  $i_x = 1A$        $k i_x = k \cdot 1 = k A$



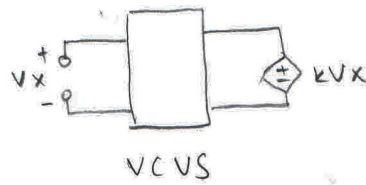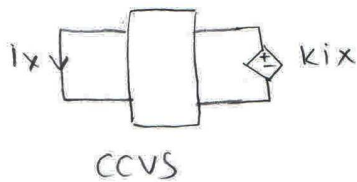Dependent current source  
voltage controlled current source



Terminals, Branches

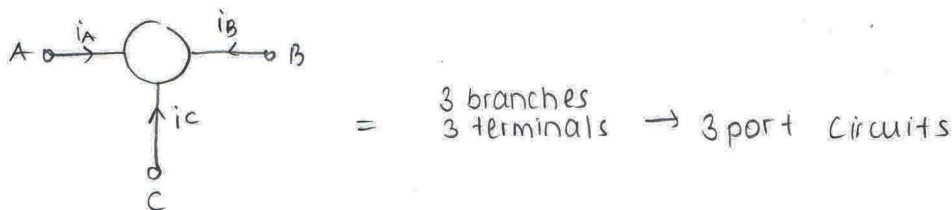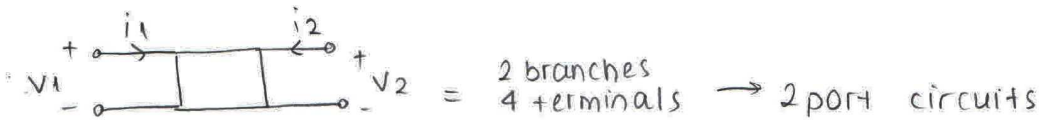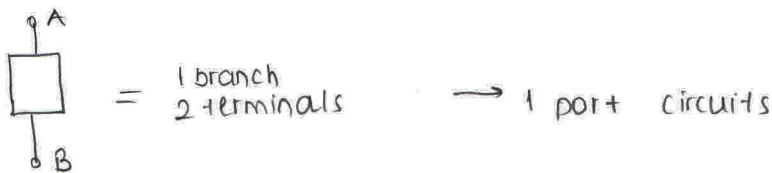

} multiport circuits



## Kirchoff's Laws

### 1-) Kirchoff's Current Law (KCL)

principle: conservation of charge

$$\underbrace{\sum_{k=1}^N i_k}_{\text{Entering charge per sec}} = \underbrace{\sum_{l=1}^L i'_l}_{\text{leaving charge per sec}}$$

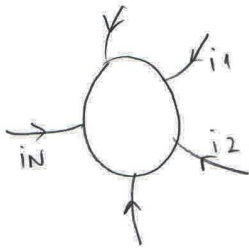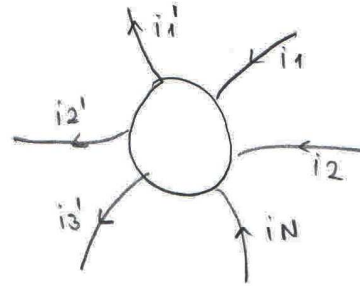Entering charge per sec      leaving charge per sec




$$\sum_{k=1}^N i_k = 0 \quad \text{All entering currents sum to zero}$$

Similarly summation of all leaving currents = 0

### 2-) Kirchoff's voltage Law (KVL)

principle: conservation of energy

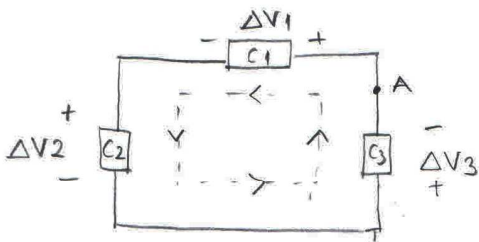


$$W_A \rightarrow A = q \Delta V_1 + q \Delta V_2 + q \Delta V_3 = 0$$

number of the branches in the loop

$$\sum_{k=1}^3 \Delta V_k = 0$$

k: branch index in the loop

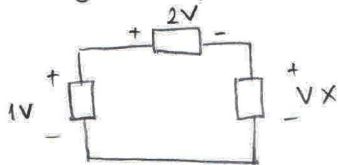
\* voltage drops across a loop is equal to zero




$$V_x = ?$$

$$+2 - 1 + V_x = 0 \quad \text{then } V_x = -1 \text{ V}$$

\*

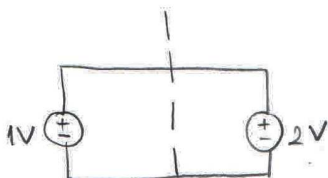

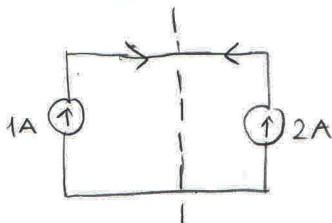Idealized circuit models do not cover this



idealized models do not apply

## Passive and Active components

- Active components (voltage sources, current sources)

Components procedure net energy

- Passive components do not procedure net energy (resistor)

$$V(t) = R \cdot i(t)$$

$$P(t) = V(t) i(t)$$

$$W(t) = \int_{-\infty}^t P(z) dz$$

$$\left. \begin{array}{l} P(t) = V(t) i(t) \\ W(t) = \int_{-\infty}^t P(z) dz \end{array} \right\} \begin{array}{l} P(t) = (i(t))^2 R \\ \text{for resistor} \end{array}$$

So  $P(t) > 0 \quad \forall t$  (if  $R > 0$ )



$$W(t) = \int_{-\infty}^t P_R(z) dz > 0 \quad \rightarrow \quad W_R(t) : \text{Energy absorbed by a resistor is always positive}$$

$\downarrow$   
 positive function ( $R > 0$ )

Then  $W_R(t) > 0 \quad \forall t \leftarrow$  if component is passive

Capacitors have  $P(t)$  which can be positive or negative

$$P_c(t) = V_c(t) i_c(t)$$

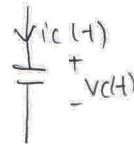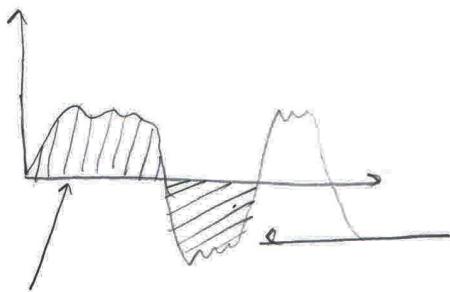

$P(t) < 0$  Capacity delivery energy outside the work

$$P(t) > 0$$


Capacitor is absorbing power like a resistor

$$W_c(t) = \int_{-\infty}^t P_c(z) dz = \int_{-\infty}^t C \frac{dV_c(z)}{dz} \cdot Q_c(z) dz = \int_{V=V_c(-\infty)}^{V=V_c(t)} C \cdot u \cdot du$$

$$= C \frac{u^2}{2} \Big|_{u=V_c(-\infty)}^{u=V_c(t)} = \frac{1}{2} C V_c^2(t) > 0 \quad \rightarrow \text{Therefore, capacitor is passive component}$$


(by taking  $V_c(t) = 0$  at infinity)
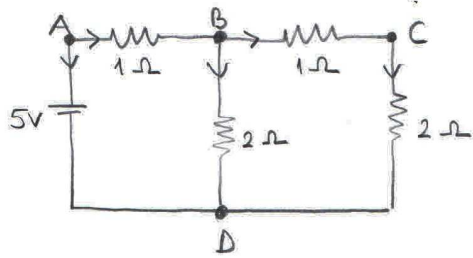
# Graph Theoretical Methods for Circuit Analysis



Conditions:

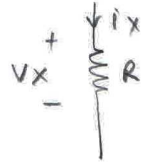1- All Ohm's law equations, that is terminal equations for resistor, to be satisfied



$$V_x = i_x \cdot R$$


4 equations for resistors

1 equation for voltage source

2- KCL (so many of them = nodes)

3- KVL (LOOPS  $\rightarrow$  3)

Graph ;

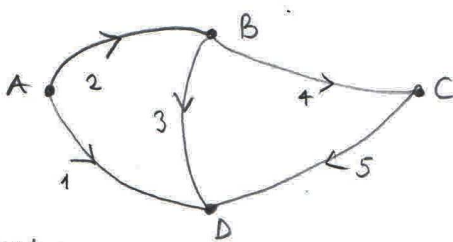

Incidence Matrix:

$$A_a = \begin{matrix} A \rightarrow \\ B \rightarrow \\ C \rightarrow \\ D \rightarrow \end{matrix} \begin{bmatrix} 1 & 1 & 0 & 0 & 0 \\ 0 & -1 & 1 & 1 & 0 \\ 0 & 0 & 0 & -1 & 1 \\ -1 & 0 & -1 & 0 & -1 \end{bmatrix}$$

branches = 1 2 3 4 5


Mesh

Loop

Directed graph


Mesh matrix
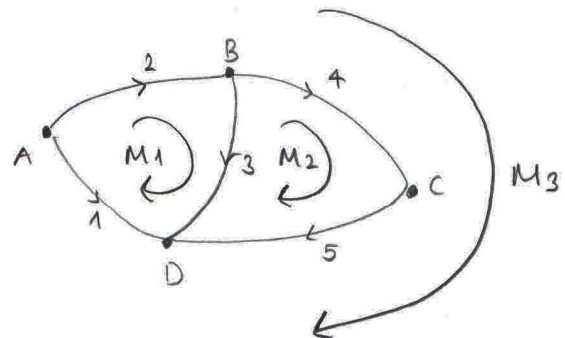
$$M_a = \begin{matrix} M_1 \\ M_2 \\ M_3 \end{matrix} \begin{bmatrix} 1 & 2 & 3 & 4 & 5 \\ -1 & 1 & 1 & 0 & 0 \\ 0 & 0 & -1 & 1 & 1 \\ -1 & 1 & 0 & 1 & 1 \end{bmatrix}$$



Mesh Equation in Matrix form

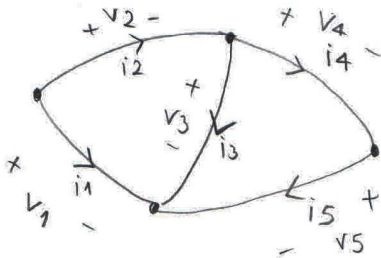Let  $v_1, v_2, \dots, v_5$  be branch voltages



To satisfy KVL ;

$$M_a \times \begin{bmatrix} v_1 \\ v_2 \\ v_3 \\ v_4 \\ v_5 \end{bmatrix} = 0$$

Then  $\begin{bmatrix} -1 & 1 & 1 & 0 & 0 \\ 0 & 0 & -1 & 1 & 1 \\ -1 & 1 & 0 & 1 & 1 \end{bmatrix} \begin{bmatrix} v_1 \\ v_2 \\ v_3 \\ v_4 \\ v_5 \end{bmatrix} = 0$ ,  $M = \begin{bmatrix} -1 & 1 & 1 & 0 & 0 \\ 0 & 0 & -1 & 1 & 1 \end{bmatrix}$

Reduced mesh matrix  
(only write equations for inner meshes)

Steps for mesh analysis;

1. Write reduced mesh matrix and form KVL constraints.

$$M \cdot V = 0$$

$$V = \begin{bmatrix} V_1 \\ V_2 \\ V_3 \\ V_4 \\ V_5 \end{bmatrix}$$


branch voltage  
vector

$$J = \begin{bmatrix} J_1 \\ J_2 \\ J_3 \\ J_4 \\ J_5 \end{bmatrix}$$

branch current vector

2. Introduce mesh currents ( $i_1, i_2, \dots$ ) and express branch currents via mesh currents

$$J = M^T \cdot i$$

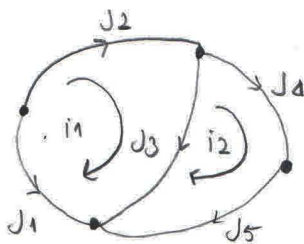

$$J_1 = -i_1$$

$$J_2 = i_1$$

$$J_3 = i_1 - i_2$$

$$J_4 = i_2$$


$$J_5 = i_2$$

$$J = M^T \cdot i$$

$$\begin{bmatrix} -1 & 0 \\ 1 & 0 \\ 1 & -1 \\ 0 & 1 \\ 0 & 1 \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \end{bmatrix}$$

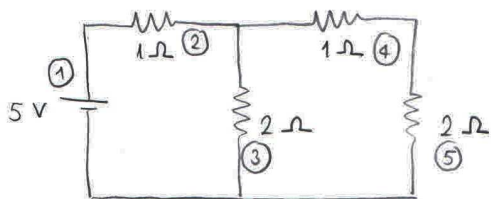3. Write terminal equations

$$\underline{V} = R \cdot \underline{J} + \underline{V}_c$$



$$V_1 = 5 \text{ V}$$

$$V_2 = J_2 \cdot 1$$

$$V_3 = J_3 \cdot 2$$

$$V_4 = J_4 \cdot 1$$

$$V_5 = J_5 \cdot 2$$

$$V = \begin{bmatrix} 0 & 0 & 0 & 0 & 0 \\ 0 & 1 & 0 & 0 & 0 \\ 0 & 0 & 2 & 0 & 0 \\ 0 & 0 & 0 & 1 & 0 \\ 0 & 0 & 0 & 0 & 2 \end{bmatrix} \begin{bmatrix} J_1 \\ J_2 \\ J_3 \\ J_4 \\ J_5 \end{bmatrix} + \begin{bmatrix} 5 \\ 0 \\ 0 \\ 0 \\ 0 \end{bmatrix}$$

resistance matrix

voltage source vector

$$1 - \underline{M} \underline{V} = 0$$

$$2 - \underline{J} = \underline{M}^T \cdot \underline{i}$$

$$3 - \underline{V} = \underline{R} \underline{J} + \underline{V}_s$$

In mesh analysis, mesh currents ( $i$ ) are unknowns  
 combine 2 and 3 and get

$$\underline{V} = \underline{R} \underline{M}^T \underline{i} + \underline{V}_s$$

Then multiply from left by  $\underline{M}$

$$0 = \underline{M} \underline{V} = (\underline{M} \underline{R} \underline{M}^T) \underline{i} + \underline{M} \underline{V}_s ; (\underline{M} \underline{R} \underline{M}^T) \underline{i} = -\underline{M} \underline{V}_s$$

$$\underline{M} \underline{R} \underline{M}^T = \begin{bmatrix} -1 & 1 & 1 & 0 & 0 \\ 0 & 0 & -1 & 1 & 1 \end{bmatrix} \begin{bmatrix} 0 & 0 \\ 1 & 0 \\ 2 & -2 \\ 0 & 1 \\ 0 & 2 \end{bmatrix} = \begin{bmatrix} 3 & -2 \\ -2 & 5 \end{bmatrix}$$

$$\underline{M} \cdot \underline{V}_s = \begin{bmatrix} -5 \\ 0 \end{bmatrix} \quad (\underline{M} \underline{R} \underline{M}^T) \begin{bmatrix} i_1 \\ i_2 \end{bmatrix} = -\underline{M} \underline{V}_s \iff \begin{bmatrix} 3 & -2 \\ -2 & 5 \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \end{bmatrix} = \begin{bmatrix} 5 \\ 0 \end{bmatrix}$$



$$\begin{bmatrix} i_1 \\ i_2 \end{bmatrix} = \frac{1}{11} \begin{bmatrix} 5 & 2 \\ 2 & 3 \end{bmatrix} \begin{bmatrix} 5 \\ 0 \end{bmatrix} = \begin{bmatrix} 25/11 \\ 10/11 \end{bmatrix}$$

↓

mesh currents (unknowns)

$$\underline{J} = \underline{M}^T \underline{i} \quad \underline{V} = \underline{R} \underline{J} + \underline{V}_s$$

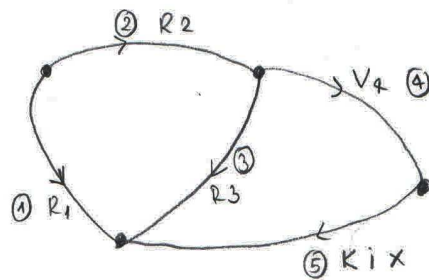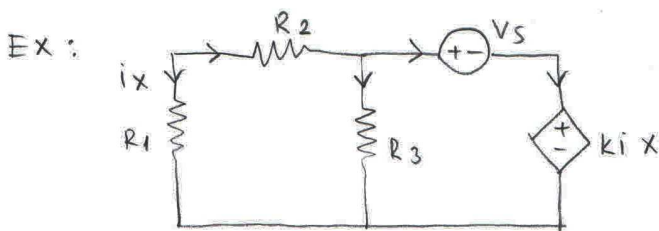branch currents                      branch voltages



$$1 - \underline{M} = \begin{bmatrix} -1 & 1 & 1 & 0 & 0 \\ 0 & 0 & -1 & 1 & 1 \end{bmatrix}$$

$$2 - \underline{J} = \underline{M}^T \underline{i} \quad \text{mesh current unknowns}$$

$$3 - V_1 = R_1 J_1$$

$$V_2 = R_2 J_2$$

$$V_3 = R_3 J_3$$

$$V_4 = V_s$$


$$V_5 = kix = k J_1$$

$$\underline{V} = \begin{bmatrix} R_1 & 0 & 0 & 0 & 0 \\ 0 & R_2 & 0 & 0 & 0 \\ 0 & 0 & R_3 & 0 & 0 \\ 0 & 0 & 0 & 0 & 0 \\ k & 0 & 0 & 0 & 0 \end{bmatrix} \begin{bmatrix} J_1 \\ J_2 \\ J_3 \\ J_4 \\ J_5 \end{bmatrix} + \begin{bmatrix} 0 \\ 0 \\ 0 \\ V_s \\ 0 \end{bmatrix}$$


$\underline{R} \quad \underline{J} \quad \underline{V}_s$



## Node Analysis

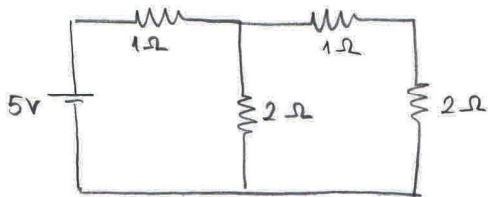


source transformation

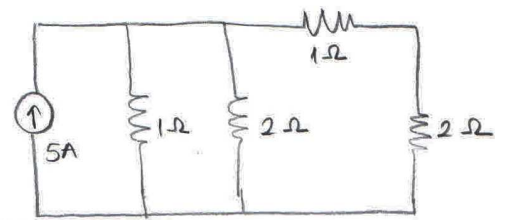

(same example used for mesh analysis)

solve this using node analysis

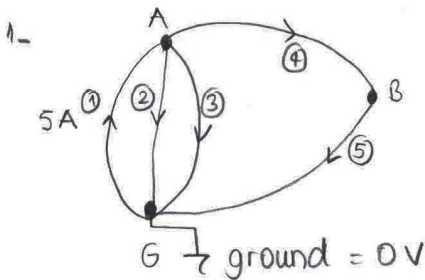

2- Write KCL's for every node

$$Aa \begin{bmatrix} J_1 \\ J_2 \\ J_3 \\ J_4 \\ J_5 \end{bmatrix} = \underline{0} + \begin{bmatrix} -1 & 1 & 1 & 1 & 0 \\ 0 & 0 & 0 & -1 & 1 \\ 1 & -1 & -1 & 0 & -1 \end{bmatrix} \begin{bmatrix} J_1 \\ J_2 \\ J_3 \\ J_4 \\ J_5 \end{bmatrix} = \begin{bmatrix} 0 \\ 0 \\ 0 \end{bmatrix}$$

incidence matrix

$$\underline{A} \underline{J} = \underline{0} \longrightarrow \begin{bmatrix} -1 & 1 & 1 & 1 & 0 \\ 0 & 0 & 0 & -1 & 1 \end{bmatrix} \begin{bmatrix} J_1 \\ J_2 \\ J_3 \\ J_4 \\ J_5 \end{bmatrix} = \begin{bmatrix} 0 \\ 0 \end{bmatrix}$$

reduced incidence matrix

3- Introduce Node voltages (e<sub>k</sub>'s)

Assume G is at 0V level.

G is ground assign e<sub>A</sub>, e<sub>B</sub> volts wrt ground to each node

$$\begin{bmatrix} V_1 \\ V_2 \\ V_3 \\ V_4 \\ V_5 \end{bmatrix} = \underline{V} = \underline{A}^T \underline{e} = \begin{bmatrix} -1 & 0 \\ 1 & 0 \\ 1 & 0 \\ 1 & -1 \\ 0 & 1 \end{bmatrix} \begin{bmatrix} e_A \\ e_B \end{bmatrix} = \begin{bmatrix} -e_A \\ e_A \\ e_A \\ e_A - e_B \\ e_B \end{bmatrix}$$

$$4- \underline{J} = \underline{G} \underline{V} + \underline{J}_s$$

$$\begin{bmatrix} J_1 \\ J_2 \\ J_3 \\ J_4 \\ J_5 \end{bmatrix} = \begin{bmatrix} 0 & 0 & 0 & 0 & 0 \\ 0 & 1/1\Omega & 0 & 0 & 0 \\ 0 & 0 & 1/2\Omega & 0 & 0 \\ 0 & 0 & 0 & 1/1\Omega & 0 \\ 0 & 0 & 0 & 0 & 1/2\Omega \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \\ V_3 \\ V_4 \\ V_5 \end{bmatrix} + \begin{bmatrix} 5 \\ 0 \\ 0 \\ 0 \\ 0 \end{bmatrix}$$

$$\underline{A} \underline{J} = \underline{0} \text{ (KCL)} \longrightarrow \underline{V} = \underline{A}^T \underline{e} \longrightarrow \underline{J} = \underline{G} \underline{V} + \underline{J}_s$$

↳ e: node voltages

$$\underline{A} \underline{J} = 0 = \underline{A} \underline{G} \underline{V} + \underline{A} \underline{J}_s \quad \underline{V} = \underline{A}^T \underline{e}$$

$(\underline{A} \underline{G} \underline{A}^T) \underline{e} = -\underline{A} \underline{J}_s$

we get node voltages

Duality: (Dual components, dual variables, dual circuits)

Dual Variables ( $\hat{\quad}$ )

$$\begin{aligned} v &\longrightarrow \hat{i} \\ i &\longrightarrow \hat{v} \\ q &\longrightarrow \hat{\phi} \rightarrow \text{flux} \\ \phi &\longrightarrow \hat{q} \end{aligned}$$

Dual components:

Resistor ( $R \ \Omega$ )			$\hat{R}$ Resistor ( $R \ \hat{\Omega}, \frac{1}{R} \ \Omega$ ) <span style="font-size: small; margin-left: 10px;">↗ siemens, mho</span>
i.e. $2 \ \Omega$	→		$1/2 \ \Omega$
$V = R i$	→		$\hat{i} = \hat{V} \hat{R}$
Capacitor ( $C$ Farad)	→		Inductors ( $L$ Henry)
Inductor ( $L$ Henry)	→		Capacitor ( $C$ Farads)


Other Dual Variables

node → mesh.


outer mesh → reference node / ground node

cutset → loop


Dual Circuits:

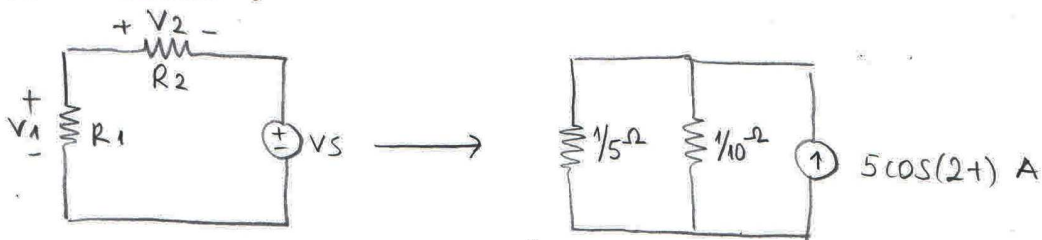
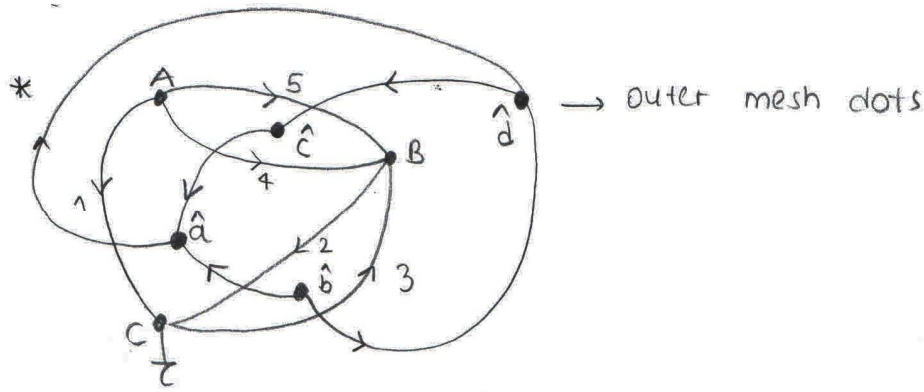
$$\begin{aligned} R_1 = 5 \ \Omega &\quad R_1 \longrightarrow \hat{R}_1 \\ R_2 = 10 \ \Omega &\quad R_2 \longrightarrow \hat{R}_2 \\ V_s = 5 \cos(2t) \ \text{V} &\quad V_s \longrightarrow I_s \\ \text{if } v_1 = 3 \ \text{V} \text{ then} &\quad J_1 = 3 \ \text{A} \end{aligned}$$




Dual Graph :

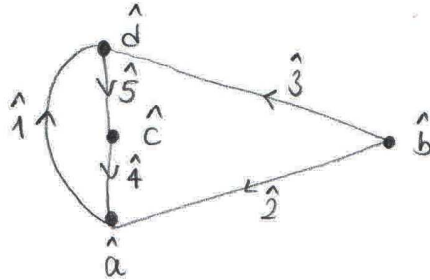

\* Draw the circuit

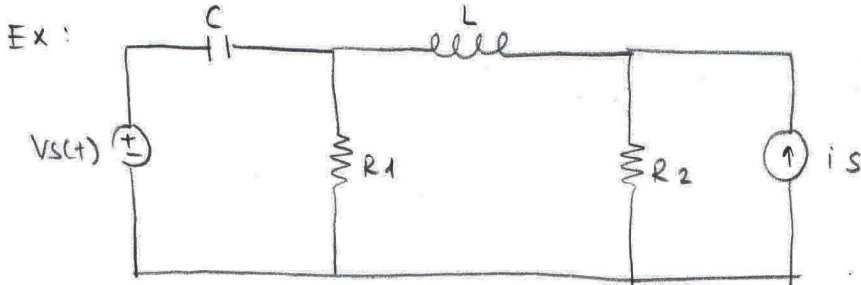And replace every branch of the dual circuit with a dual component  
 90° clockwise rotation to find dual graph directions  
 Every branch is in between 2 dots (two meshes)  
 find a dual branch for every branch




$$V_s(t) = 2 \cos t \text{ V} \quad \phi_L = \tan^{-1}(13)$$

$$C = 10 \mu\text{F} \quad R_1 = 10 \Omega$$

$$i_s(t) = 2 \text{ A} \quad R_2(t) = 2 + \cos t$$

Dual Circuit :

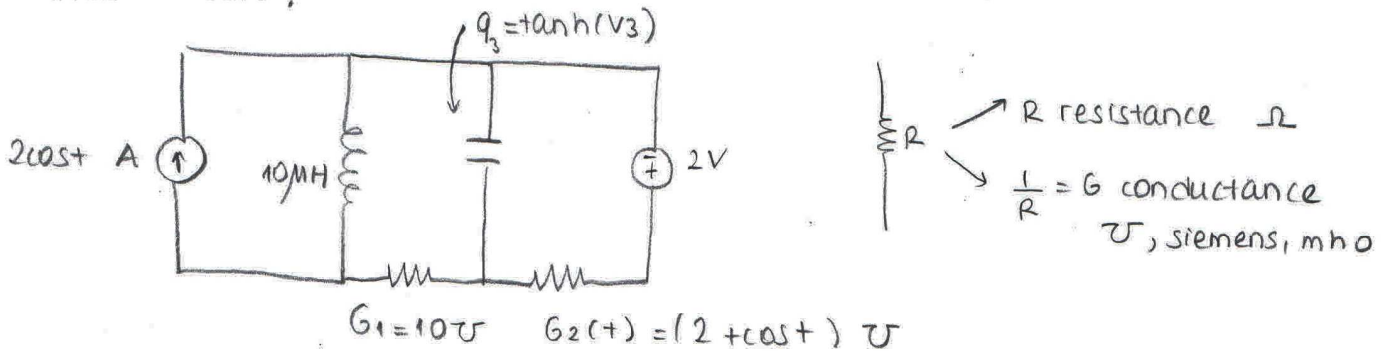

## Classification of Circuits

\* Resistive (memoryless) / Dynamics


Linear / Non-linear

Time invariant / time-varying

Passive / Active


Generalized Branch :

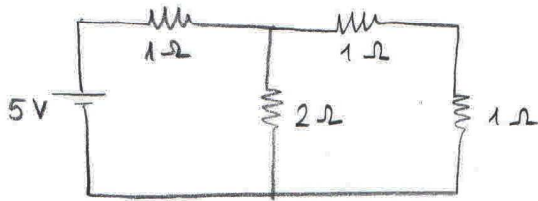For Graph theoretical Node/Mesh analysis, we may need to form generalized branches



Solve this using mesh analysis



A

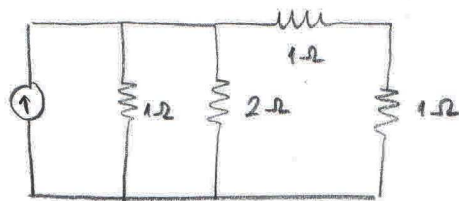

Solve this using node analysis

B

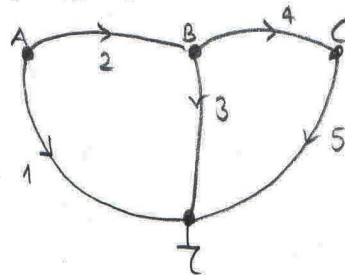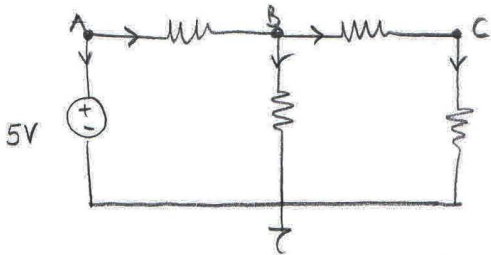$A \equiv B$  Let's apply node analysis to A



$$\underline{A} \underline{J} = 0$$

$$\begin{bmatrix} 1 & 1 & 0 & 0 & 0 \\ 0 & -1 & 1 & 1 & 0 \\ 0 & 0 & 0 & -1 & 1 \end{bmatrix} \begin{bmatrix} J_1 \\ J_2 \\ J_3 \\ J_4 \\ J_5 \end{bmatrix} = 0$$

$$J_1 = \underline{5V} + J_5$$

$$J_2 = V_2 / 1$$

$$J_3 = V_3 / 2$$

$$J_4 = V_4 / 1$$

$$J_5 = V_5 / 1$$

$J_1$  can be any scalar


Generalized branch  
Node Analysis



a branch

generalized branch

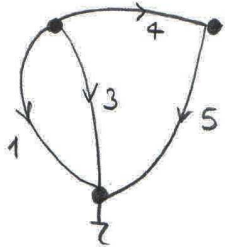
If we use generalized branch, then graph becomes ;




$$\begin{bmatrix} 1 & 1 & 1 & 0 \\ 0 & 0 & -1 & 1 \end{bmatrix} \begin{bmatrix} J_1 \\ J_3 \\ J_4 \\ J_5 \end{bmatrix} = \begin{bmatrix} 0 \\ 0 \end{bmatrix}$$

$$\begin{bmatrix} J_1 \\ J_3 \\ J_4 \\ J_5 \end{bmatrix} = \begin{bmatrix} 1 & 0 & 0 & 0 \\ 0 & 1/2 & 0 & 0 \\ 0 & 0 & 1 & 0 \\ 0 & 0 & 0 & 1 \end{bmatrix} \begin{bmatrix} V_1 \\ V_3 \\ V_4 \\ V_5 \end{bmatrix} + \begin{bmatrix} -5 \\ 0 \\ 0 \\ 0 \end{bmatrix} \quad \text{since } J_1 = \frac{V_1 - 5}{1-\Omega}$$

Mesh Analysis

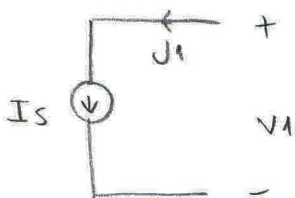

A relation between \$J\_1\$ and \$V\_1\$

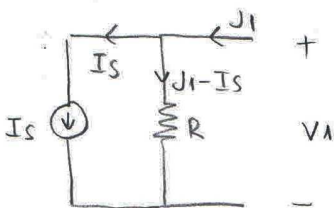

$$V_1 = R(J_1 - I_s) = RJ_1 - RI_s$$


equation expressing \$V\_1\$ in terms of \$J\_1\$

Tellegen's Theorem

2 forms

Form 1



Graph

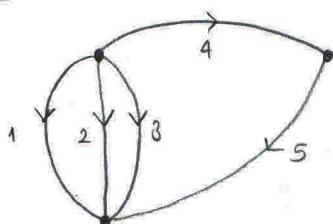

# of branches

$$\sum_{k=1}^n v_k i_k = 0$$

Form 2:

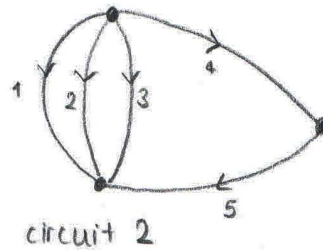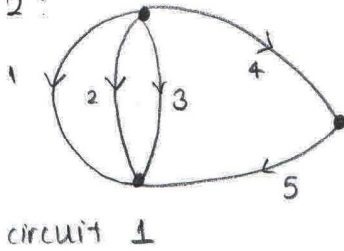

$\hat{V}_k, \hat{J}_k$  branch variables

$$\sum_{k=1}^{\# \text{branches}} V_k \hat{J}_k = \sum_{k=1}^{\# \text{branches}} \hat{V}_k J_k = 0$$

Note: Graphs of circuits are identical

Circuit 1

$$\underline{A} \underline{J} = 0$$

$$\underline{V} = \underline{A}^T \underline{e}$$

Circuit 2

$$\underline{A} \hat{\underline{J}} = 0$$

$$\hat{\underline{V}} = \underline{A}^T \hat{\underline{e}}$$

Node analysis  
for 2 circuits

$$\sum_{k=1}^{\# \text{branches}} V_k \hat{J}_k = \underline{V}^T \hat{\underline{J}} = (\underline{A}^T \underline{e})^T \hat{\underline{J}} = \underline{e}^T (\underline{A} \hat{\underline{J}}) = 0$$

$$[V_1 \ V_2 \ V_3 \ \dots \ V_N] \begin{bmatrix} J_1 \\ J_2 \\ J_3 \\ \vdots \\ J_N \end{bmatrix} = \sum_{k=1}^N V_k J_k$$

1.  $\underline{J}$  (branch currents) are in the nullspace of  $\underline{A}$


$$\underline{A} \underline{x} = 0$$

2.  $\underline{V}$  is the range space of  $\underline{A}^T$

$$\underline{A} = [C_1 \ C_2 \ \dots \ C_N] \text{ of column space}$$

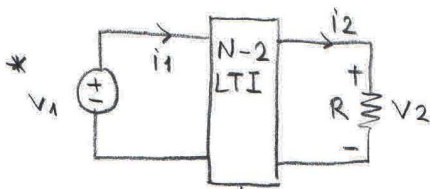3. So  $\underline{J}$  and  $\underline{V}$  vectors are in orthogonal spaces of  $\underline{A}$  matrix

Tellegen's theorem Application (also related the concept of reciprocity)



resistors obeying Ohm's Law

Circuit 1

$$R = 1 \Omega$$

$$V_1 = 4 \text{ V}$$

$$i_1 = 1 \text{ A}$$

$$V_2 = 1 \text{ V}$$

$$i_2 = 1 \text{ A}$$

Circuit 2

$$R = 2 \Omega$$

$$\hat{V}_1 = 6 \text{ V}$$

$$\hat{i}_1 = 1.2 \text{ A}$$

$$\hat{V}_2 = ?$$

$$1 - \underline{V}^T \underline{J} = 0 \longrightarrow \sum_{k=1}^N V_k \hat{J}_k = 0$$


$$2 - \underline{\hat{V}}^T \cdot \underline{J} = 0 \longrightarrow \sum \hat{V}_k J_k = 0$$

$$V_1 \hat{J}_1 + V_2 \hat{J}_2 + \sum_{k=3}^N V_k \hat{J}_k = 0$$

$$\frac{4V}{4V} \cdot \frac{-1.2A}{-1.2A} + \frac{1V}{1V} \frac{\hat{V}_2}{R_2} + \sum_{k=3}^N V_k \hat{J}_k = 0$$

$$\hat{V}_1 J_1 + \hat{V}_2 J_2 + \sum_{k=3}^N \hat{V}_k J_k = 0$$
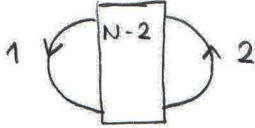
$$\frac{6V}{6V} \cdot \frac{-1A}{-1A} + \frac{1A}{1A} \hat{V}_2 + \sum_{k=3}^N \hat{V}_k J_k = 0$$




$$1 - 4(-1.2) + \frac{\hat{V}_2}{2} \cdot 1 + \sum R_k J_k \hat{J}_k = 0$$

$$2 - 6(-1) + \hat{V}_2 \cdot 1 + \sum R_k J_k J_k = 0$$

$$\hat{V}_2 = 2.4 \text{ V}$$
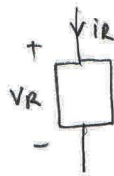
### Linear Time-varying Resistance Circuits



$$V_R = f(i_R)$$

Some special cases have important consequences

1) Linearity




$$L \{ x_1(t) \} = y_1(t)$$

$$L \{ x_2(t) \} = y_2(t)$$



$$L \{ x_1(t) + x_2(t) \} = y_1(t) + y_2(t)$$

2)  $L \{ \alpha x_1(t) \} = \alpha y_1(t)$  Linear system

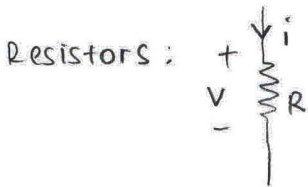Question;  $L \{ 0 \}$  should be 0 (since  $L \{ x_1(t) - x_1(t) \} = y_1(t) - y_1(t) = 0$ )




If  $V = R i$  (Ohm's Law)

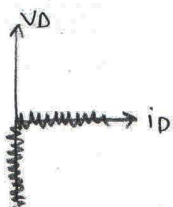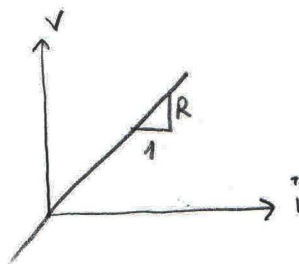

Diode: nonlinear component

## 2 - Time Invariance

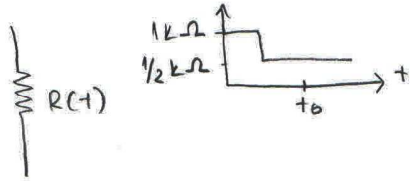

resistance value is not constant

it is time varying

$$V_R(t) = R(t) I_R(t)$$

LTI Resistor  $V(t) = R i(t) \quad \forall t \quad R = \text{constant}$

combinational Sources and resistors (Circuit Simplification)


Series combination of resistors:




$$V = V_1 + V_2 \quad \text{by KVL}$$

$$= iR_1 + iR_2$$

$$= i(R_1 + R_2)$$

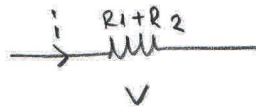


Voltage sources:

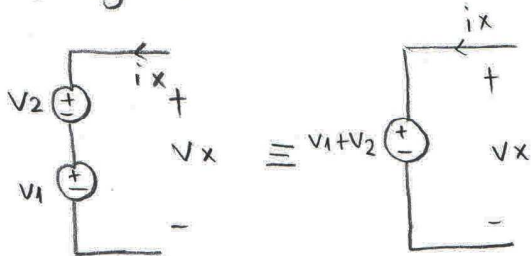

$$V_x = V_1 + V_2 \quad i_x \in R$$

Parallel combinations

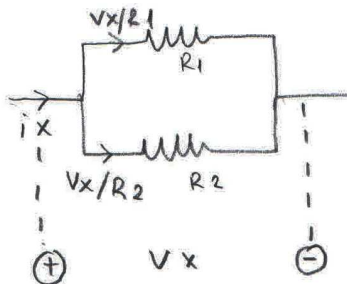

$$i_x = \frac{V_x}{R_1} + \frac{V_x}{R_2}$$

$$i_x = V_x \left( \frac{1}{R_1} + \frac{1}{R_2} \right)$$



$$\text{then } V_x = i_x \left( \frac{1}{R_1} + \frac{1}{R_2} \right)^{-1}$$

current sources (parallel)





Source Transformation

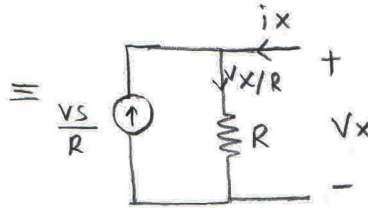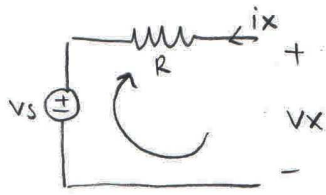


for 1<sup>st</sup> circuit;  $-V_x + R i_x + V_s = 0$  KVL


$$i_x = \frac{V_x - V_s}{R} = \frac{V_x}{R} - \frac{V_s}{R}$$

for 2<sup>nd</sup> circuit;  $i_x = V_x/R - V_s/R$

} equality

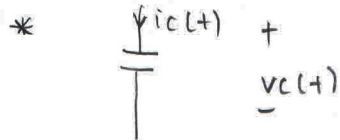


$$i_c(t) = C \frac{dv_c(t)}{dt}$$


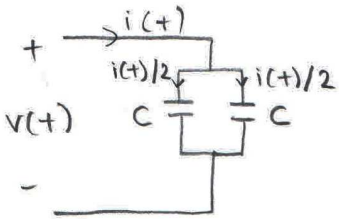


$$i_c(t) = \frac{i(t)}{2} = C \frac{dv_c(t)}{dt}$$

$$i(t) = 2C \frac{dv_c(t)}{dt}$$

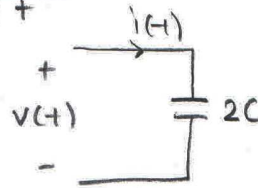


Ex: (source transformation)

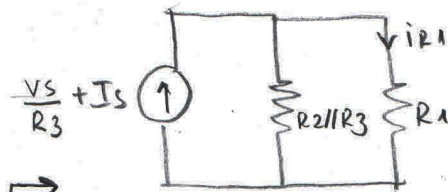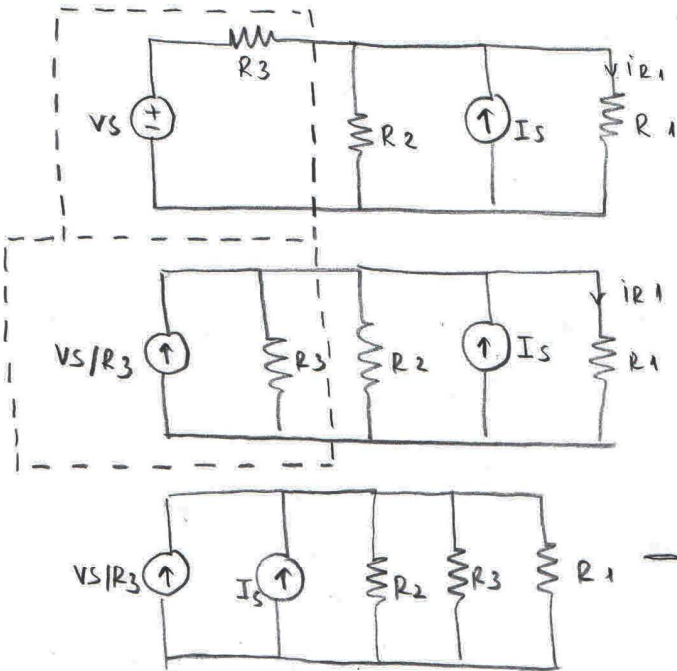

$$i_{R1} = \frac{\left(\frac{V_s}{R_3} + I_s\right) (R_2 // R_3 // R_1)}{R_1}$$

## Node-Mesh Analysis

### Node Analysis

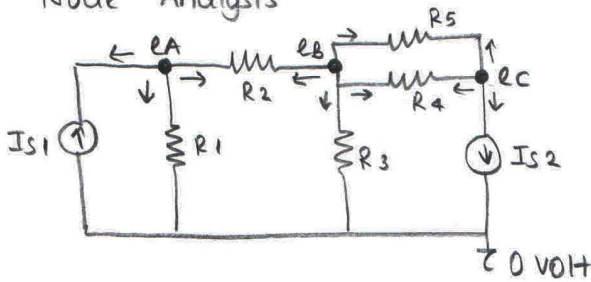

- Steps:
1. Select a Datum (Ground) node
  2. Assign node voltage variables to the remaining nodes
  3. Write KCL at every node and solve for node voltages


\* KCL at EA:  $-I_{s1} + \frac{e_A}{R_1} + \frac{e_A - e_B}{R_2} = 0$

KCL at EB:  $\frac{e_B - e_A}{R_2} + \frac{e_B}{R_3} + \frac{e_B - e_C}{R_4 // R_5} = 0$

KCL at EC:  $I_{s2} + \frac{e_C - e_B}{R_4 // R_5} = 0$

$$\begin{bmatrix} 1/R_1 + 1/R_2 & -1/R_2 & 0 \\ -1/R_2 & 1/R_2 + 1/R_3 + 1/R_4 + 1/R_5 & -1/R_4 - 1/R_5 \\ 0 & -1/R_4 - 1/R_5 & 1/R_4 + 1/R_5 \end{bmatrix} \begin{bmatrix} e_A \\ e_B \\ e_C \end{bmatrix} = \begin{bmatrix} I_{s1} \\ 0 \\ -I_{s2} \end{bmatrix}$$

### Node Analysis with Voltage Sources

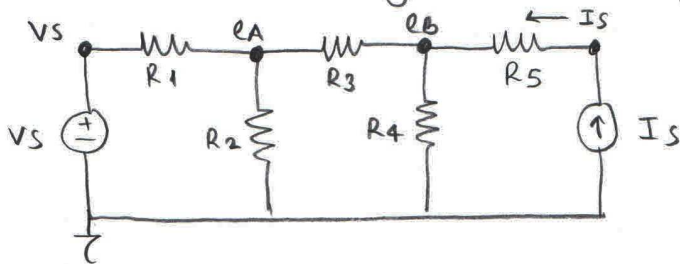

KCL @ EA:  $\frac{e_A}{R_2} + \frac{e_A - V_S}{R_1} + \frac{e_A - e_B}{R_3} = 0$


@ EB:  $\frac{e_B - e_A}{R_3} + \frac{e_B}{R_4} - I_S = 0$

} can find  $e_A$  and  $e_B$

KCL @ EA:  $\frac{e_A - e_C}{R_1} + \frac{e_A}{R_2} + \frac{e_A - e_B}{R_3} = 0$


KCL @ EB:  $\frac{e_B - e_A}{R_3} + \frac{e_B}{R_4} - I_S = 0$

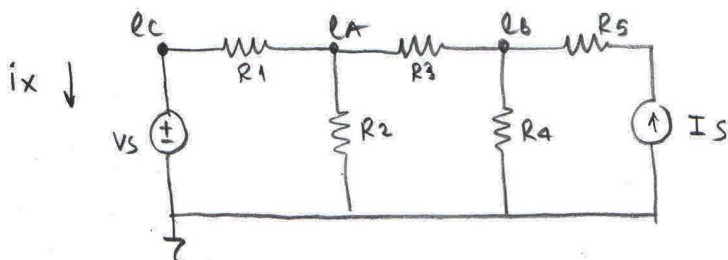KCL @ EC:  $i_x + \frac{e_C - e_A}{R_1} = 0$



4 equations, 4 unknowns

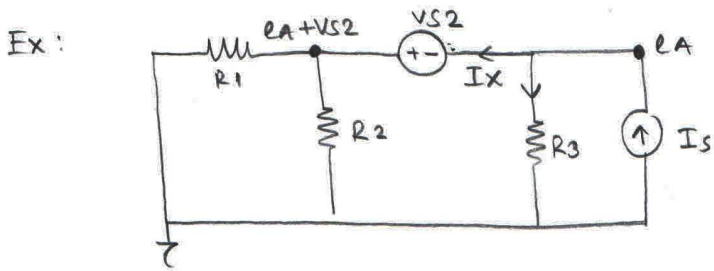
$\{e_A, e_B, e_C, i_x\}$   $e_C = V_S(+)$



KCL @ eA:  $\frac{eA}{R_3} - I_S + I_X = 0$

@ eA+VS2:  $\frac{eA+VS2}{R_2} + \frac{eA+VS2}{R_1} - I_X = 0$


2 equations  
2 unknowns

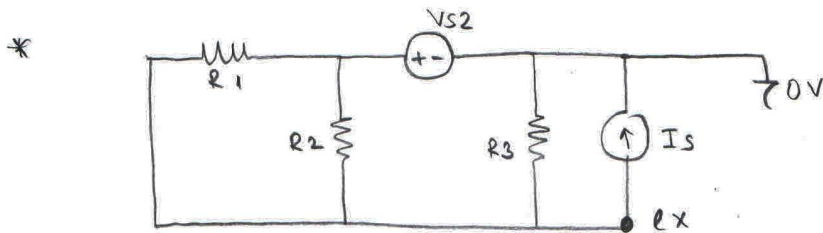




KCL @ ex;  $I_S + \frac{eX}{R_3} + \frac{eX-VS2}{R_1} + \frac{eX-VS2}{R_2} = 0$

$$\left( \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \right) eX = \left( \frac{VS2}{R_1} + \frac{VS2}{R_2} - I_S \right)$$
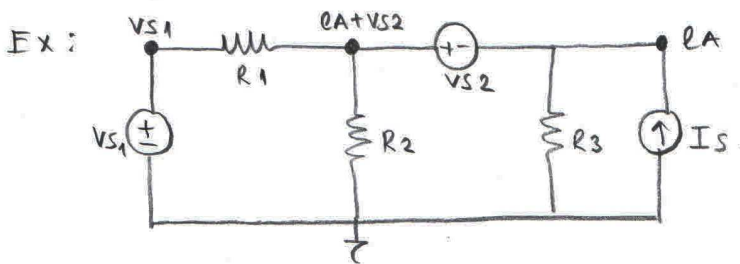
$$eX = \frac{VS2/R_1 + VS2/R_2 - I_S}{\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}}$$



2 equations, 2 unknowns

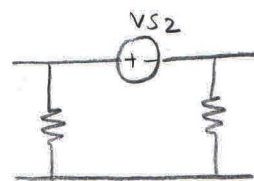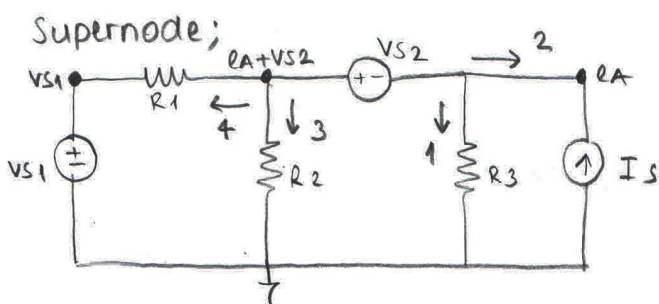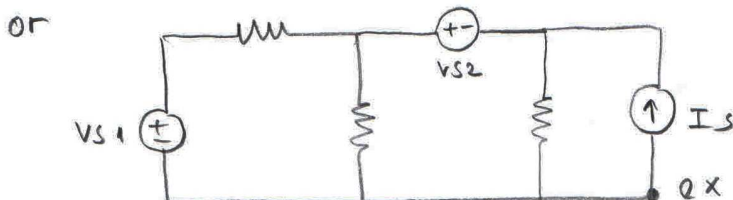


Supernode (Always contain a voltage source)

KCL @ Supernode;  $\frac{e_A}{R_3} - I_S + \frac{e_A + V_{S2}}{R_2} + \frac{e_A + V_{S2} - V_{S1}}{R_1} = 0$

$$e_A = \frac{I_S - V_{S2}/R_2 + (-V_{S2} + V_{S1})/R_1}{1/R_1 + 1/R_2 + 1/R_3}$$

Without a Super-node

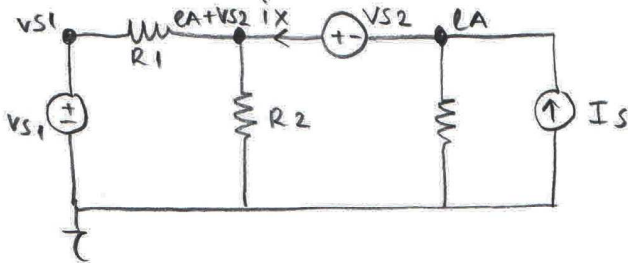

KCL @ eA =  $\frac{e_A}{R_3} - I_S + i_x = 0$

@ eA+VS2 =  $\frac{e_A + V_{S2} - V_{S1}}{R_1} - i_x + \frac{e_A + V_{S2}}{R_2} = 0$


2 equations, 2 unknowns

### Node Analysis

Select a ground node



Assign node voltages

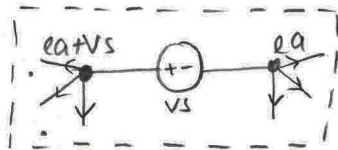write KCL equations at nodes (except ground)



supernode

### Mesh Analysis

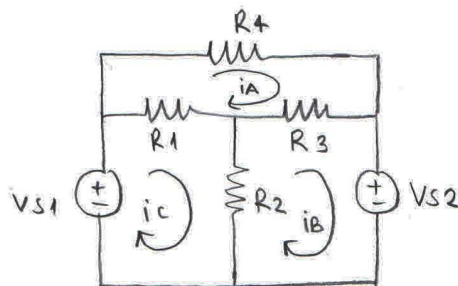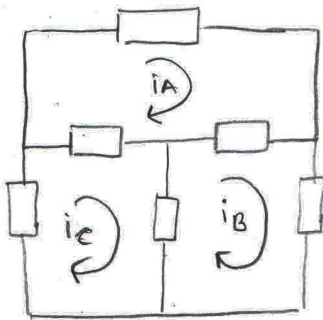

Assign mesh currents to each mesh.


Express branch currents in terms of mesh currents. write KVL around each mesh

Solve the resulting equation set for mesh currents

Mesh iA :  $R_4 \cdot i_A + R_3(i_A - i_B) + R_1(i_A - i_C) = 0$

Mesh iB :  $R_3(i_B - i_A) + V_{S2} + R_2(i_B - i_C) = 0$

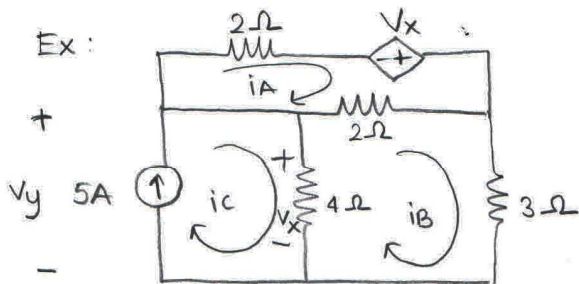Mesh iC :  $-V_{S1} + R_1(i_C - i_A) + R_2(i_C - i_B) = 0$



Mesh analysis is only applicable to planar circuits.

Node analysis is applicable to all

Mesh  $i_A$ :  $2i_A - V_x + 2(i_A - i_B) = 0$

Mesh  $i_B$ :  $2(i_B - i_A) + 3i_B + 4(i_B - i_C) = 0$

Mesh  $i_C$ :  $-V_y + 4(i_C - i_B) = 0$       $i_C = 5A$

$V_x = (i_C - i_B) \cdot 4$

by substituting 5A for  $i_C$ , we have

Mesh  $i_A$ :  $2i_A - \underbrace{4(5 - i_B)}_{V_x} + 2(i_A - i_B) = 0$

Mesh  $i_B$ :  $4(i_B - 5) + 2(i_B - i_A) + 3i_B = 0$


$$\begin{bmatrix} 2+2 & 4-2 \\ -2 & 9 \end{bmatrix} \begin{bmatrix} i_A \\ i_B \end{bmatrix} = \begin{bmatrix} 20 \\ 20 \end{bmatrix}$$

$$\begin{bmatrix} i_A \\ i_B \end{bmatrix} = \frac{1}{40} \begin{bmatrix} 9 & -2 \\ 2 & 4 \end{bmatrix} \begin{bmatrix} 20 \\ 20 \end{bmatrix} = \frac{1}{2} \begin{bmatrix} 9 & -2 \\ 2 & 4 \end{bmatrix} \begin{bmatrix} 1 \\ 1 \end{bmatrix} = \begin{bmatrix} 7/2 \\ 3 \end{bmatrix} A$$

$V_x = 8V$  then  $P_{5A} = -8 \cdot 5 = -40 W$  absorbed, 40 W delivered


Since it is a source absorbed power is negative

Note on Power calculations;

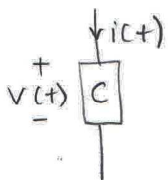

$P(t) = v(t) i(t)$

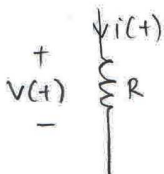
if  $P(t) > 0$  instantaneous power is absorbed at time  $t$




R is always absorbing power

$P(t) < 0$  delivering energy to other components at time  $t$ .

\*

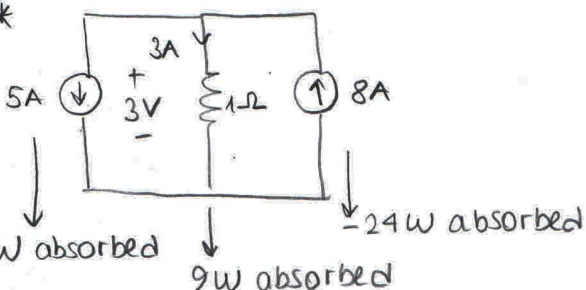

Ex:

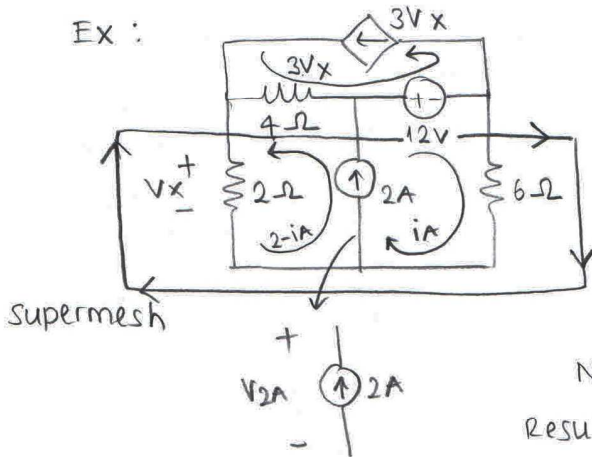

$$\text{Mesh } i_A: 12 + 6i_A - V_{2A} = 0$$

$$\text{Mesh } 2-i_A: -V_{2A} + 4(2-i_A - 3V_x) + 2(2-i_A) = 0$$

2 equations, 2 unknowns


KVL around supermesh

$$4(3V_x - (2-i_A)) + 12 + 6i_A - 2(2-i_A) = 0$$

Note: (Eqn in Mesh  $i_A$ ) minus (Eqn in  $(2-i_A)$ ) = 0

Results:  $i_A = 4A$   $V_x = -4V$

Ex:

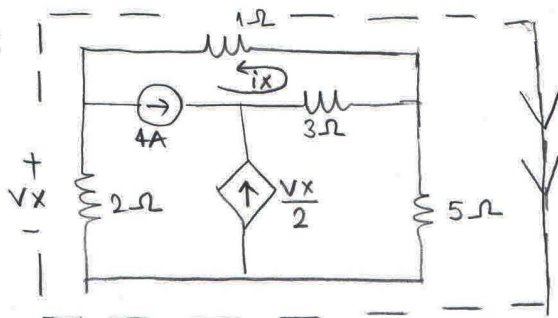

KVL around outer mesh;

$$1(-i_x) + 5\left(\frac{V_x}{2} + 4 - i_x\right) + 2(4 - i_x) = 0$$


$$-i_x + 5(i_x - 4 + 4 - i_x) + 2(4 - i_x) = 0$$

$$i_x = 8/3A \quad V_x = -8/3V$$

$$V_x = 2(i_x - 4)$$

This circuit requires 3 mesh currents, but it has 2 current sources. (one independent, one dependent) then  $3-2=1$  can be sufficient to solve for mesh currents.

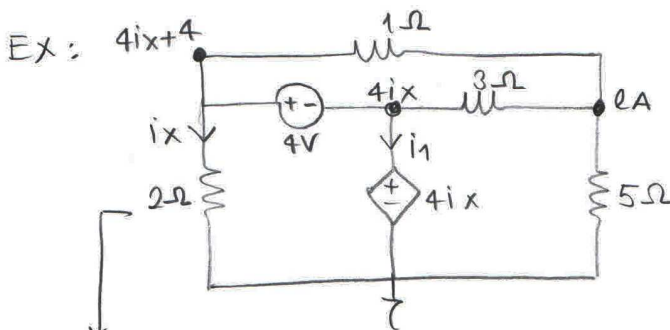For node analysis, same circuit requires 3 nodes and has no voltage sources, so "3-0" = 3 node equations should be solved together



KCL @  $e_A$ :

$$\frac{e_A}{5} + \frac{e_A - 4ix}{3} + \frac{e_A - (4ix + 4)}{1} = 0$$

KCL @  $4ix$ ;

$$\frac{4ix - e_A}{3} + i_1 + (5ix + 4 - e_A) = 0$$

KCL @  $4ix+4$ ;

$$-(5ix + 4 - e_A) + ix + \frac{4ix + 4 - e_A}{1} = 0$$

$$4ix + 4 = 2ix; \quad \boxed{ix = -2A}$$

$$\frac{e_A}{5} + \frac{e_A + 8}{3} + e_A + 4 = 0$$


$$\frac{23e_A}{15} + \frac{20}{3} = 0$$

$$\boxed{e_A = -80/23}$$

Fundamental loop Method: Similar to graph theoretical mesh analysis (but not equivalent)

- 1- Pick a tree
- 2- Write fun-loop eqns ( $\underline{B} \underline{V} = 0$ )
- 3- Express branch voltages in terms of branch currents ( $\underline{V} = \underline{R} \underline{J} + \underline{V}_s$ )
- 4- Use  $\underline{J} = \underline{B}^T \underline{i}$  relation expressing branch current in terms of fundamental loop currents (co-tree currents)

Graph

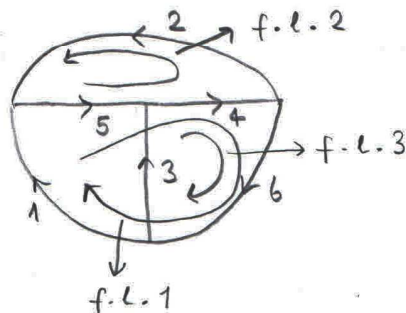

Tree: Set of connected branches of the graph such that

- 1- Branches do not form a loop
- 2- Every node is reached by a tree
- 3- Tree is connected

Tree branches  $\{4, 5, 6\}$

Co-tree branches  $\{1, 2, 3\}$

\* Every co-tree branch and whole-tree makes a loop (fund-loops - Union of a single co-tree branch and tree)

Step 2:

$$\begin{bmatrix} 1 & 0 & 0 \\ 0 & 1 & 0 \\ 0 & 0 & 1 \end{bmatrix} \begin{bmatrix} 1 & 1 & 1 \\ 1 & 1 & 0 \\ 1 & 0 & 1 \end{bmatrix} \begin{bmatrix} v_1 \\ v_2 \\ v_3 \\ v_4 \\ v_5 \\ v_6 \end{bmatrix} = \begin{bmatrix} 0 \\ 0 \\ 0 \end{bmatrix}$$

$\underline{I}$ 
 $\underline{F}$

fundamental loop

\* Fundamental loop directions are in the same directions with co-tree

Step 3:

$$\underline{J} = \underline{B}^T \underline{i}$$

$$\begin{bmatrix} j_1 \\ j_2 \\ j_3 \\ j_4 \\ j_5 \\ j_6 \end{bmatrix} = \begin{bmatrix} 1 & 0 & 0 \\ 0 & 1 & 0 \\ 0 & 0 & 1 \\ 1 & 1 & 1 \\ 1 & 1 & 0 \\ 1 & 0 & 1 \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \\ i_3 \end{bmatrix}$$

fundamental loop currents and currents of co-tree branches


Fundamental cut-set (Similar to graph node analysis (but not equivalent))

- 1- Draw graph
- 2- select tree

3- Write KCL at fundamental cut-set ( $\sum J = 0$ )

4- Write branch equations ( $J = GV + i_s$ )

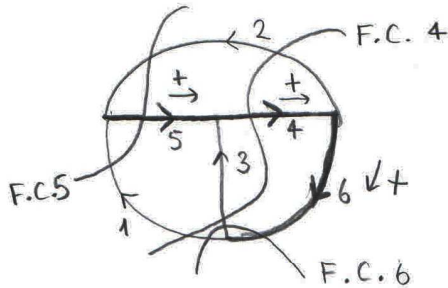5- Use  $\underline{v} = \underline{Q}^T \underline{e}$  expressing branch voltages in terms of tree branch voltages



Fundamental cut-set

Cut-set: partitions graph into 2 disjoint sets

1- should be cut-set

2- should intersect a single tree branch

Step 2  $\underline{Q} \underline{J} = \underline{0}$

$$F.C. \begin{bmatrix} 4 \\ 5 \\ 6 \end{bmatrix} \begin{bmatrix} -1 & -1 & -1 & | & 1 & 0 & 0 \\ -1 & -1 & 0 & | & 0 & 1 & 0 \\ -1 & 0 & -1 & | & 0 & 0 & 1 \end{bmatrix} \begin{bmatrix} J_1 \\ J_2 \\ J_3 \\ J_4 \\ J_5 \\ J_6 \end{bmatrix} = \begin{bmatrix} 0 \\ 0 \\ 0 \end{bmatrix}$$

$-F^T \quad \quad \quad I$

\* Note that +/- sign of cut-set is in the direction of related tree branch. Tree branch always enters to + side


$$\underline{B} = \begin{bmatrix} \underline{I} & | & \underline{F} \end{bmatrix}$$

for the same tree



$$\underline{Q} = \begin{bmatrix} -\underline{F}^T & | & \underline{I} \end{bmatrix}$$

$$\underline{B} \underline{Q}^T = \begin{bmatrix} \underline{I} & | & \underline{F} \end{bmatrix} \begin{bmatrix} -\underline{F} \\ \underline{I} \end{bmatrix} = \underline{F} - \underline{F} = \underline{0} \quad \text{Tellegen's theorem for cut-set thm}$$

Input i/v calculations

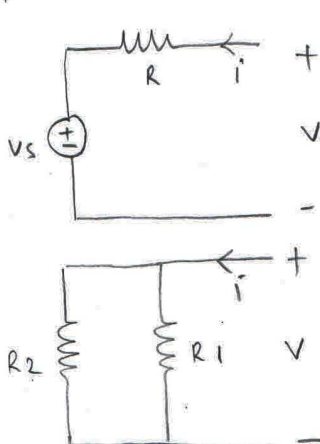


$$-V_s + R(-i) + V = 0$$

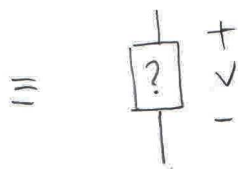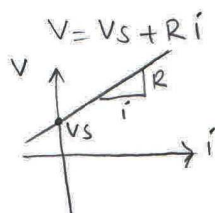


what is the mapping between i and v

$$i = \frac{V}{R_1} + \frac{V}{R_2}$$



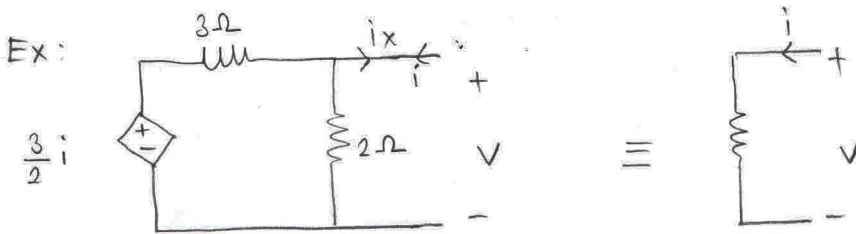


Let's assume that

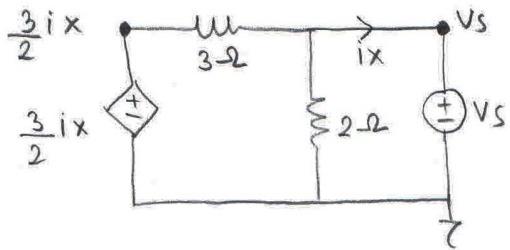

Find  $i_x$  in terms of  $v_s$




$$\frac{v_s}{2} + i_x = \left(\frac{3}{2}i_x - v_s\right) \frac{1}{3}$$

$$i_x = -\frac{5}{3}v_s$$

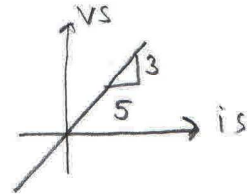


So I can use both independent voltage source and independent current source for  $i-v$  characteristic.

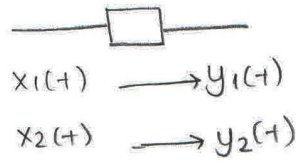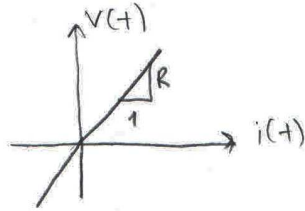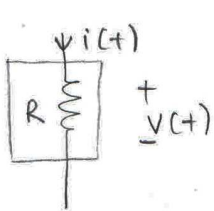Linearity: Linear components, linear relations  $\rightarrow$  linear systems



If linear  $L\{x_1(t) + x_2(t)\} = y_1(t) + y_2(t)$

$$L\{\alpha x_1(t)\} = \alpha y_1(t)$$

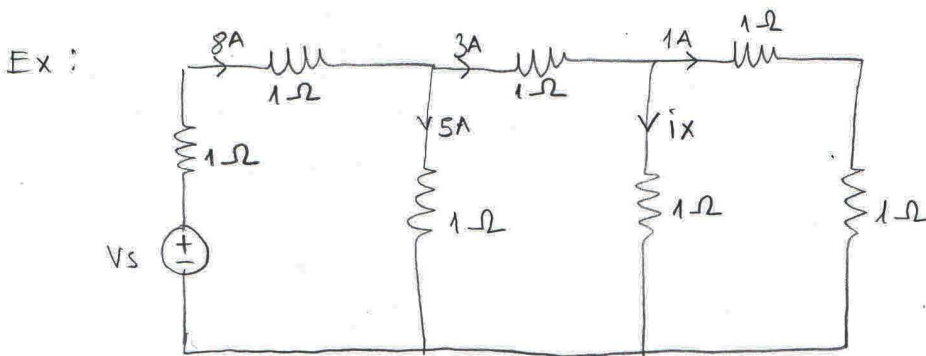


Ladder Network

Find  $i_x$

so let's apply the principle of linearity of soln

Assume  $i_x = 2A$   $v_s = 21V$

Circuits with Multiple Sources

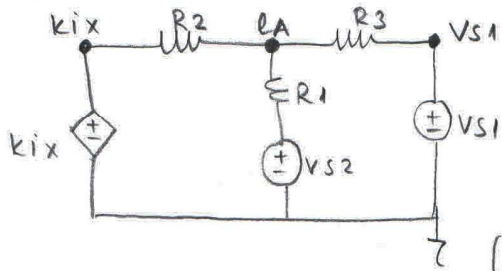

$$\frac{eA - V_{S2}}{R_1} + \frac{eA - kix}{R_2} + \frac{eA - V_{S1}}{R_3} = 0$$


$$ix = \frac{eA - V_{S1}}{R_3}$$

$$\left( \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} - \frac{k}{R_2 R_3} \right) eA = \frac{V_{S2}}{R_1} + \frac{V_{S1}}{R_3} - \frac{k V_{S1}}{R_2 R_3}$$

$eA$  can be solved from these equations.

Solution by Superposition Principle (Linearity Rule)

(I) Take  $V_{S2} = 0$   $V_{S1} \neq 0$

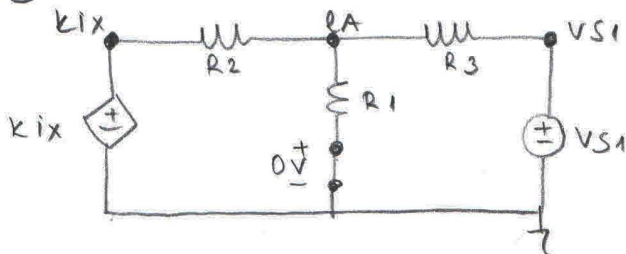


$$KCL; \frac{eA'}{R_1} + \frac{eA' - kix'}{R_2} + \frac{eA' - V_{S1}}{R_3} = 0$$

solution for  $V_{S2} = 0$

$$ix' = \frac{eA' - V_{S1}}{R_3}$$

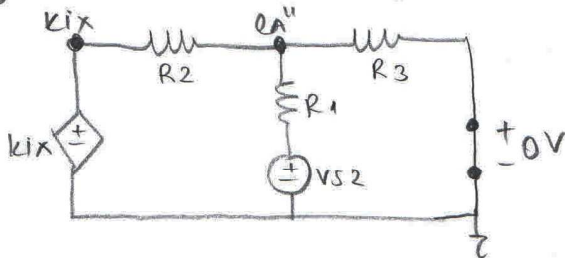(II) Take  $V_{S1} = 0$   $V_{S2} \neq 0$



$$KCL: \frac{eA'' - kix''}{R_2} + \frac{eA'' - V_{S2}}{R_1} + \frac{eA''}{R_3} = 0$$


$$ix'' = \frac{eA''}{R_3}$$

\* Claim:  $eA$  (solution when  $V_{S1} \neq 0$   $V_{S2} \neq 0$ ) can be written as


$eA = eA' + eA''$  superposition of two positions

\* If  $eA = eA' + eA''$  then  $ix = ix' + ix''$

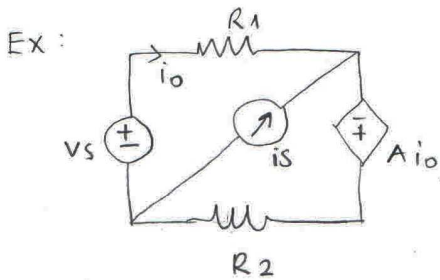★ Superposition is made only for independent sources -



Find  $i_o = ?$

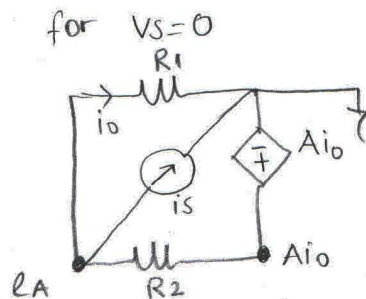


$$\frac{eA}{R_1} + I_S + \frac{eA - Aio}{R_2} = 0$$

$$\left( \frac{1}{R_1} + \frac{1}{R_2} - \frac{A}{R_1 R_2} \right) eA = -I_S$$

$$eA = \frac{-I_S}{\frac{1}{R_1} + \frac{1}{R_2} - \frac{A}{R_1 R_2}}$$

$$i_0' = \frac{eA}{R_1}$$

for  $i_s = 0$ ;

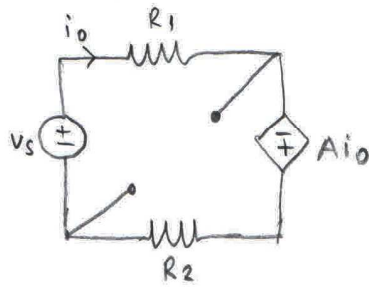


by KVL;

$$-V_s + R_1 i_0'' - A i_0'' + R_2 i_0'' = 0$$


$$i_0'' = \frac{V_s}{R_1 - A + R_2}$$

$$I_0 = i_0' + i_0''$$

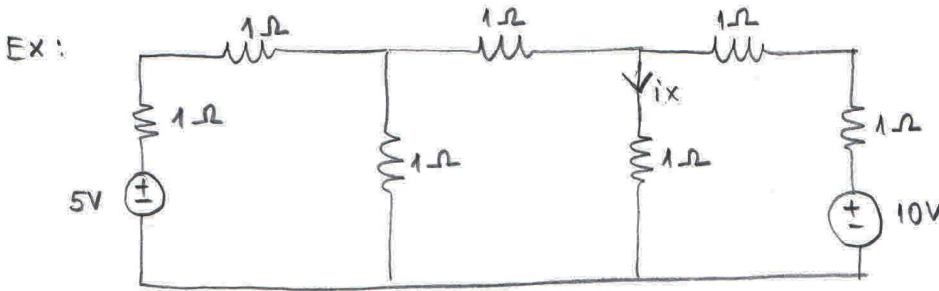


Find  $i_x$ ?

A - Kill (turn off) 10 V source.

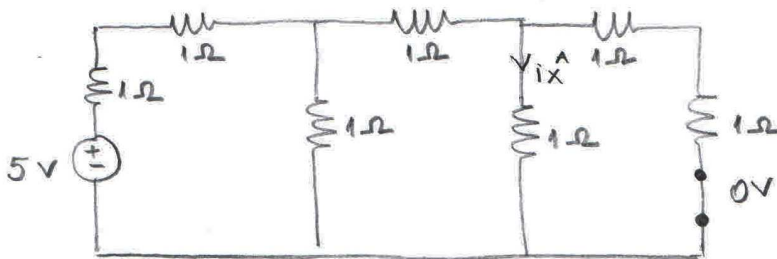


$$i_x^A = \frac{10}{21} \text{ A}$$

B - Kill (turn off) 5V source.

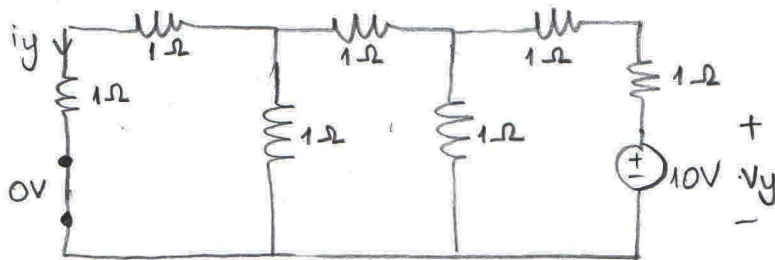

If  $i_y = 1 \text{ A}$  then  $V_y = 21 \text{ V}$   
 $i_y = ?$  if  $V_y = 10 \text{ V}$   
 $i_y = \frac{10}{21} \text{ A}$  if  $V_y = 10 \text{ V}$   
 $i_x^B = 5 i_y$ ;  $i_x^B = \frac{50}{21} \text{ A}$
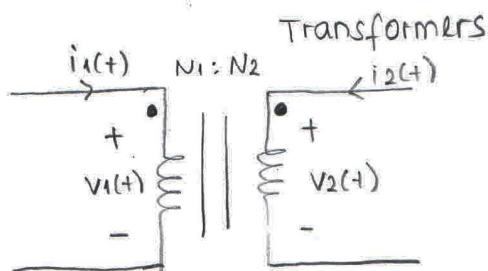
$$i_x = i_x^A + i_x^B = \frac{60}{21} = \frac{20}{7} \text{ A}$$



Dots are related to how turns are arranged in clockwise, counter-clockwise direction


Two port circuit component

$$\left[ \frac{v_1(t)}{v_2(t)} = \frac{N_1}{N_2} \right] \text{ voltage ratio is directly proportional to turn ratio.}$$

$$\left[ \frac{i_1(t)}{i_2(t)} = -\frac{N_2}{N_1} \right] \text{ current ratio is inversely proportional}$$

transformer relations

$N_1, N_2$  : Turn ratio of transformer

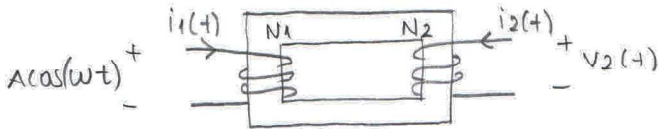


Power consumed by Ideal Transformer





$$P_{\text{consumed}}(t) = v_1(t) i_1(t) + v_2(t) i_2(t)$$

$$v_1(t) i_1(t) + \underbrace{\left( v_1(t) \frac{N_2}{N_1} \right)}_{v_2(t)} \underbrace{\left( -i_1(t) \frac{N_1}{N_2} \right)}_{i_2(t)} = 0 \text{ W}$$

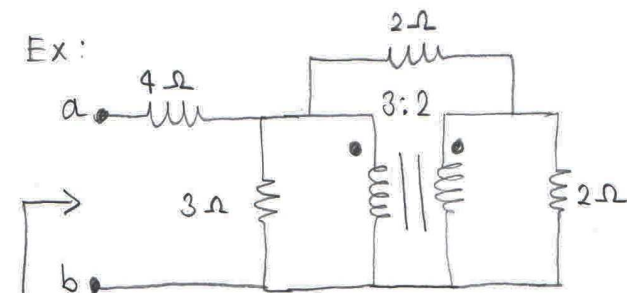\* Ideal Transformer do not consume any power



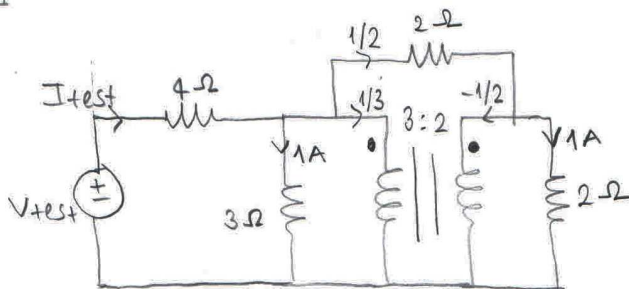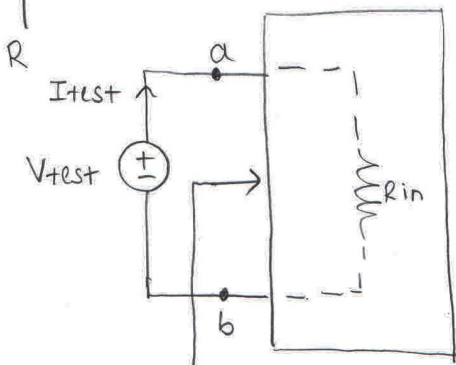Find input resistance seen from the a-b terminals




$$I_{\text{test}} = \frac{11}{6} \text{ A}$$

$$V_{\text{test}} = 4 \frac{11}{6} + 3 = \frac{62}{6}$$


$$R_{\text{IN}} = \frac{V_{\text{test}}}{I_{\text{test}}} = \frac{62}{11} \Omega$$

$$R_{\text{IN}} = \frac{V_{\text{test}}}{I_{\text{test}}}$$

### Δ-Y Transformation

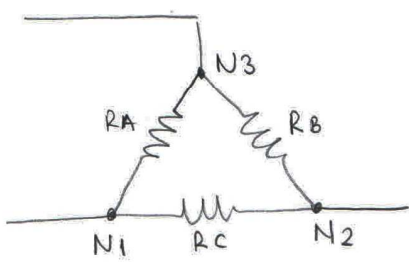

Δ  
Δ → Y

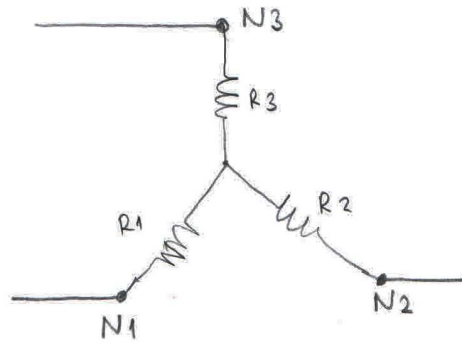

Y  
Δ → Y

$$R_A = \frac{R_1 R_2 + R_1 R_3 + R_2 R_3}{R_2}$$

$$R_1 = \frac{R_A R_C}{R_A + R_B + R_C}$$

$$R_B = \frac{R_1 R_2 + R_1 R_3 + R_2 R_3}{R_1}$$


$$R_2 = \frac{R_B R_C}{R_A + R_B + R_C}$$

$$R_C = \frac{R_1 R_2 + R_1 R_3 + R_2 R_3}{R_3}$$




$$R_3 = \frac{R_A R_B}{R_A + R_B + R_C}$$

If \$(R\_A, R\_B, R\_C)\$ & \$(R\_1, R\_2, R\_3)\$ satisfy the equations then Δ and Y networks are equivalent.

EX :

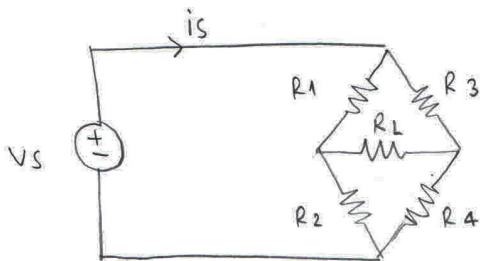

Find \$i\_s\$ in terms of \$V\_s\$

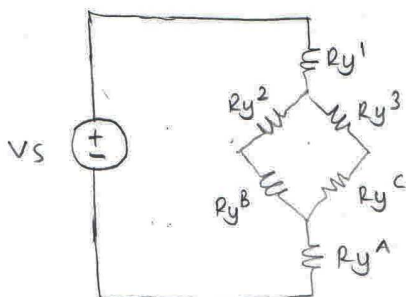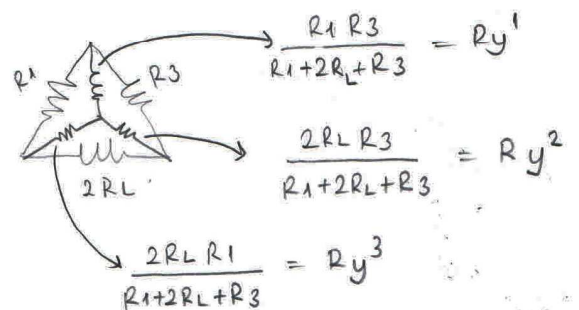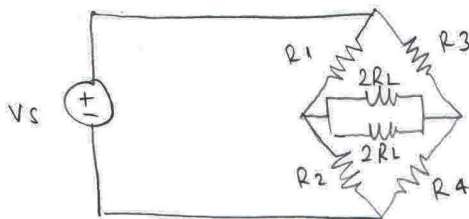

$$R_{y^A} = \frac{R_2 R_4}{R_2 + 2R_L + R_4}$$

$$R_{y^B} = \frac{2R_L R_2}{R_2 + 2R_L + R_4}$$


$$R_{y^C} = \frac{2R_L R_4}{R_2 + 2R_L + R_4}$$

$$R_{IN} = R_y^A + R_y^B + \left[ (R_y^2 + R_y^B) \parallel (R_y^3 + R_y^C) \right]$$


$$i_s = \frac{V_s}{R_{IN}}$$
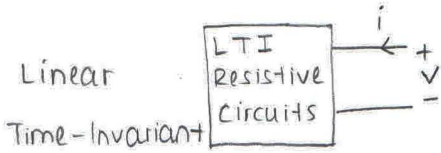
### Thevenin - Norton Equivalents

Finding (i-v) characteristic of a circuit  
(seen from two terminals)



### Thevenin Equivalent

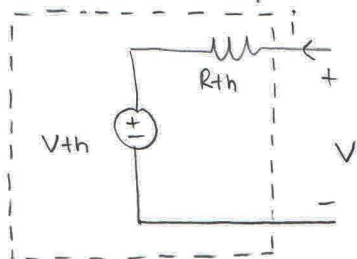

$V_{th}$  : Thevenin voltage


$R_{th}$  : Thevenin Resistance

$V_{th} = V_{oc}$  open circuit voltage

$R_{th} \Rightarrow$  Input resistance seen from two terminals

equivalent circuit = thevenin equivalent  
seen from two terminals



### Norton Equivalent

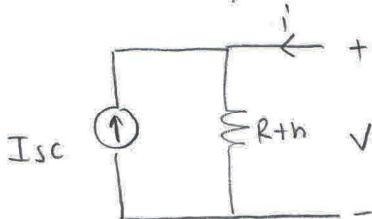

$I_{sc}$  : short circuit current

$R_{th}$  : thevenin resistance

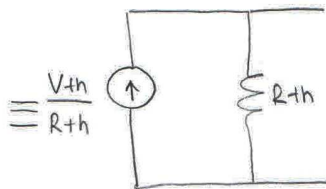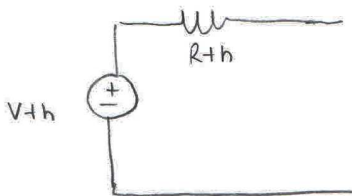Note : if source transformation is applied to Thevenin Equivalent ;



$$I_{sc} = \frac{V_{th}}{R_{th}}$$

### Procedure for finding Thevenin Equivalents


Procedure 1

(A) Find  $V_{oc}$

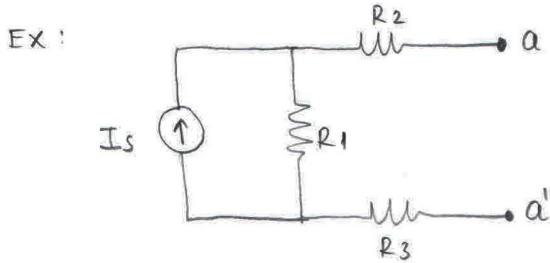(B) Find  $R_{th} \rightarrow$  Turn off all independent sources and find  $R_{IN}$  seen from two terminals


$\rightarrow$  Turn off all independent sources, apply  $V_{test}$  and measure  $I_{test}$  then  $R_{IN} = R_{th} = \frac{V_{test}}{I_{test}}$

- Procedure 2:
- Ⓐ Find  $V_{oc}$
  - Ⓑ Find  $I_{sc}$
  - Ⓒ Calculate  $R_{th}$  by  $\frac{V_{oc}}{I_{sc}}$



Find an equivalent circuit for the LHS of  $a a'$  terminals


Solution: Apply source transformation

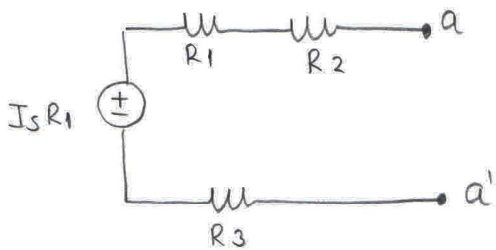


$$V_{th} = I_s R_1$$

$$R_{th} = R_1 + R_2 + R_3$$

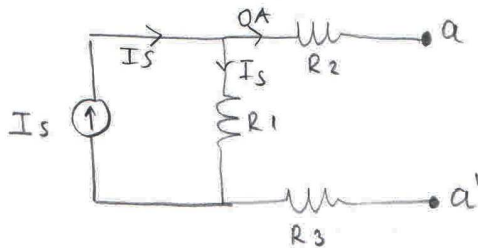
Procedure ① Ⓐ  $V_{oc} = ?$  (open circuit terminals)



$$V_{oc} = V_a - V_{a'} = I_s R_1$$

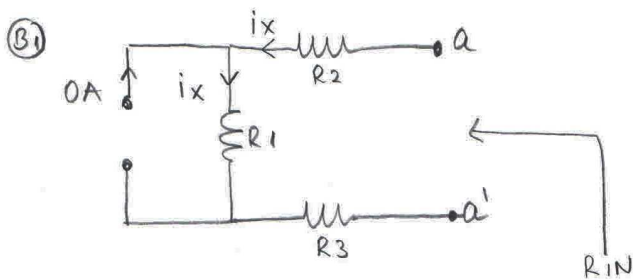

$$R_{IN} = R_1 + R_2 + R_3$$

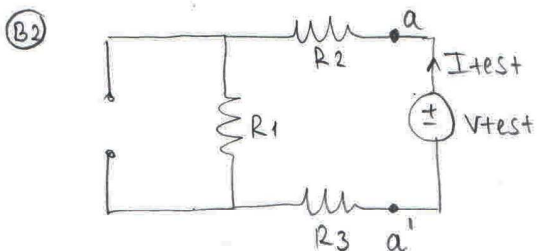


$$I_{test} = \frac{V_{test}}{R_1 + R_2 + R_3}$$

$$R_{IN} = \frac{V_{test}}{I_{test}} = R_1 + R_2 + R_3$$

Procedure ② Ⓐ  $V_{oc} = I_s R_1$

Ⓑ  $I_{sc} =$  Short Circuit Current (terminals are short-circuited)

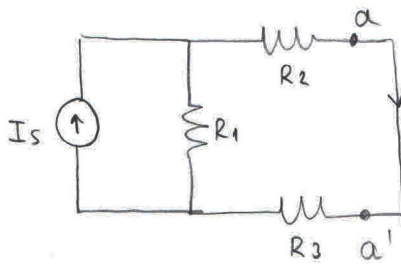
©  $R_{th} = \frac{V_{oc}}{I_{sc}} = R_1 + R_2 + R_3$




$$I_{sc} = I_s \cdot \frac{1/(R_2 + R_3)}{(1/R_1) + (1/(R_2 + R_3))} = I_s \frac{R_1}{R_1 + R_2 + R_3}$$

\* Dependent sources are named as sources but we should interpret dependent sources as dependent components but not sources such as independent sources. So do not apply — Source transformation — Do not turn off dependent sources during  $R_{in}$  calculations.


Remember

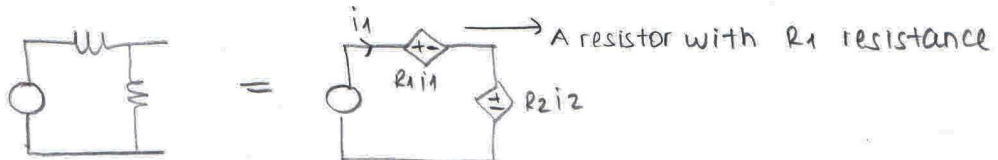

Ex:

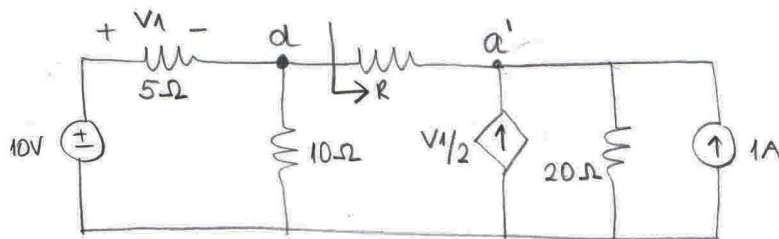

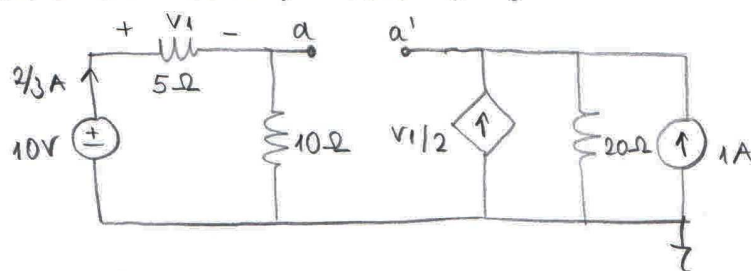Procedure 2:  $v_{oc} = ?$   $v_{oc} = v_a - v_b$




$$v_1 = \frac{10V}{(5+10)\Omega} \cdot 10\Omega = \frac{10}{3}V$$

$$v_{20\Omega} = 20\Omega \left(1 + \frac{v_1}{2}\right)A$$

$$v_{20\Omega} = \frac{160}{3}V$$

$$v_a = \frac{20}{3}V \quad v_{a'} = \frac{160}{3}V$$

$$v_{oc} = \frac{-140}{3}V$$

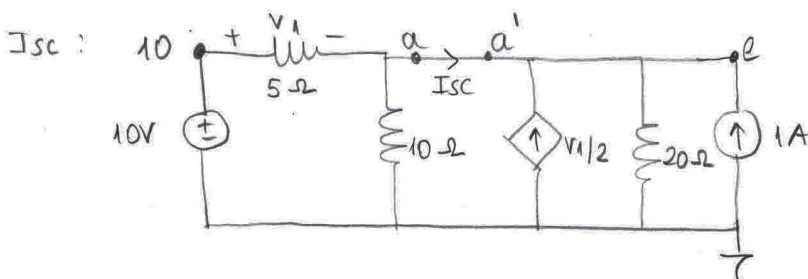

by KCL:  $\frac{e-10}{5} - 1 + \frac{e}{20} - \frac{e}{10}$


$$-\frac{v_1}{2} = 0$$



$$V_1 = 10 - e; \quad 17e = 160; \quad e = \frac{160}{7} \text{ V}$$


$$I_{SC} = \frac{10 - e}{5} - \frac{e}{10} = \frac{20 - 3e}{10} = \frac{-14}{17} \text{ A}$$
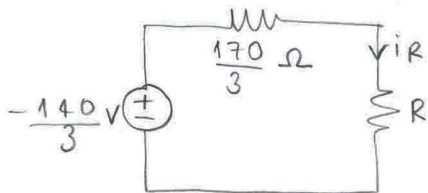
$$R_{th} = \frac{V_{OC}}{I_{SC}} = \frac{-140/3}{-14/17} = \frac{170}{3} \Omega$$



$$i_R = \frac{-140/3}{(170/3) + R} \quad \text{for any } R$$

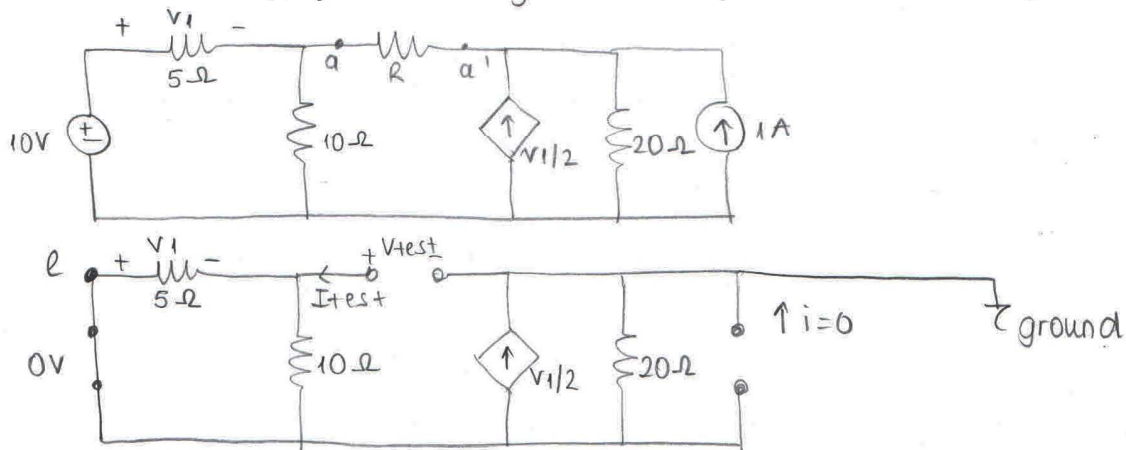Same Circuit: Apply test voltage method for  $R_{th}$  calculation.



by KCL  $\frac{e}{20} + \frac{v_1}{2} + \frac{e - V_{test}}{10} + \frac{e - V_{test}}{5} = 0$


$$17e = V_{test} \cdot 16$$


$$e = \frac{16}{17} V_{test}$$

$$i_{test} = \frac{v_1}{2} + \frac{e}{20} = \frac{11}{20} e - \frac{V_{test}}{2} = \frac{3}{170} V_{test}$$

$$R_{IN} = \frac{V_{test}}{I_{test}} = \frac{170}{3} \Omega$$


Maximum Power Transfer

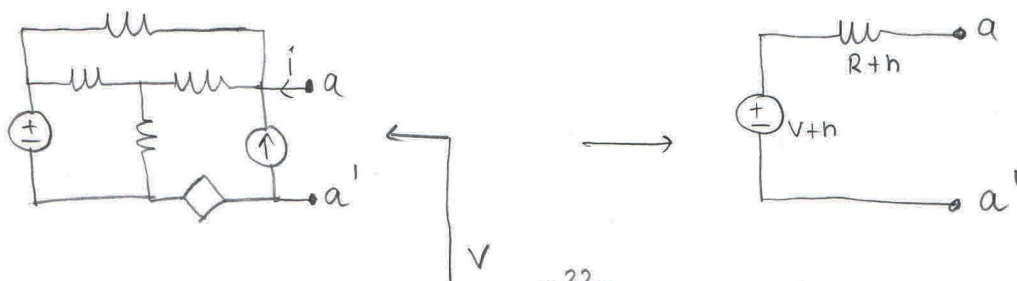

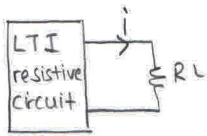

Max power transfer question: Select  $R_L$  such that power on  $R_L$  is maximum

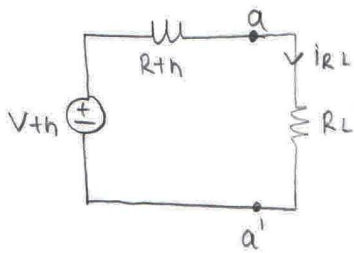Replace the equivalent circuit seen by  $R_L$



$$P_{RL} = i_{RL}^2 R_L = \left( \frac{V_{th}}{R_L + R_{th}} \right)^2 R_L$$


$$\frac{\partial P_{RL}}{\partial R_L} = 0 \rightarrow V_{th}^2 \left[ \frac{(R_{th} + R_L)^2 - 2(R_{th} + R_L)R_L}{(R_{th} + R_L)^4} \right]$$

$$(R_{th} + R_L)^2 = 2(R_{th} + R_L)R_L$$

$$(R_{th} + R_L) = 2R_L \quad R_{th} + R_L \neq 0$$


$$R_{th} + R_L = 0 \quad R_L = \{ R_{th}, -R_{th} \} \quad R_L = R_{th}$$

At maximum power transfer condition;

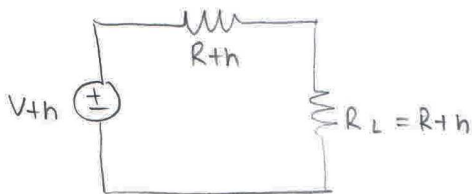

$$P_{max} = \left( \frac{V_{th}}{2R_{th}} \right)^2 R_{th} = \frac{V_{th}^2}{4R_{th}}$$

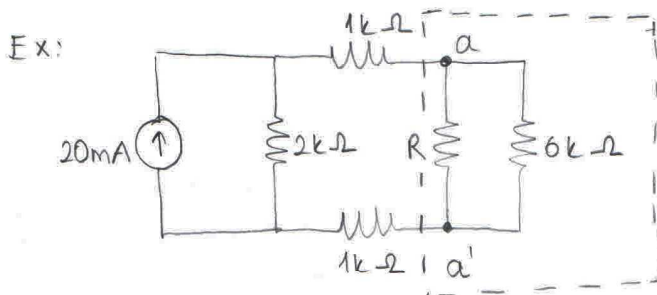Note: Power delivered  $R_L$  is equal to the power dissipated over  $R_{th}$   
so efficiency of max power transfer condition is 50%



Find  $R$  such that power delivered to load is maximized.

Thevenin equivalent of LHS of  $a-a'$

$$R_{th} = 4k\Omega$$


$$V_{oc} = 40V$$

→ for max power transfer

$$4k\Omega = R // 6k\Omega$$


$$R = 12k\Omega$$

Two-Ports

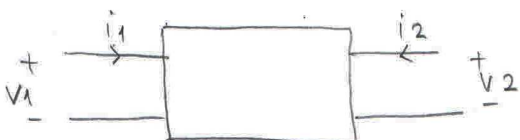

2 port circuit

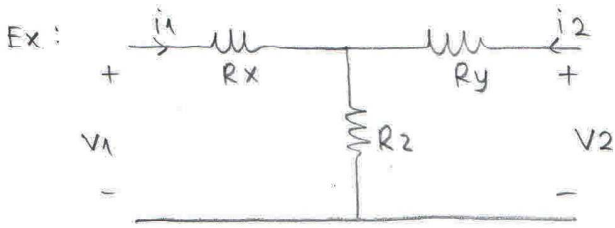
Goal: Represent two port circuit with some system parameters



R parameters

$$\begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} r_{11} & r_{12} \\ r_{21} & r_{22} \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \end{bmatrix}$$

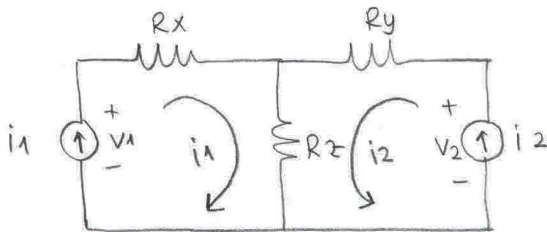output/unknown                      consider this part input



$$V_1 = i_1 R_x + R_z (i_1 + i_2)$$

$$V_2 = i_2 R_y + R_z (i_1 + i_2)$$

$$\begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} R_x + R_z & R_z \\ R_z & R_y + R_z \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \end{bmatrix}$$

G conductance parameters

$$\begin{bmatrix} i_1 \\ i_2 \end{bmatrix} = \begin{bmatrix} g_{11} & g_{12} \\ g_{21} & g_{22} \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix}$$

$$\underline{G} = \underline{R}^{-1}$$

Hybrid - I parameters


$$\begin{bmatrix} V_1 \\ i_2 \end{bmatrix} = \underbrace{\begin{bmatrix} h_{11} & h_{12} \\ h_{21} & h_{22} \end{bmatrix}}_H \begin{bmatrix} i_1 \\ V_2 \end{bmatrix}$$

Hybrid - II parameters

$$\begin{bmatrix} i_1 \\ V_2 \end{bmatrix} = \underbrace{H^{-1}}_{\text{hybrid II}} \begin{bmatrix} V_1 \\ i_2 \end{bmatrix}$$


Transfer parameters = ABCD parameters = Chain parameters
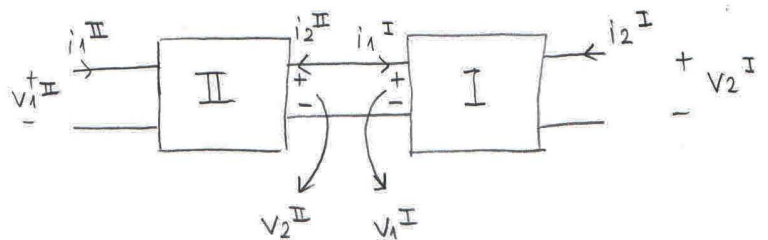
$$\begin{bmatrix} V_1 \\ i_1 \end{bmatrix} = \begin{bmatrix} A & B \\ C & D \end{bmatrix} \begin{bmatrix} V_2 \\ -i_2 \end{bmatrix}$$




(ABCD) cascade = (ABCD)<sub>II</sub> (ABCD)<sub>I</sub>

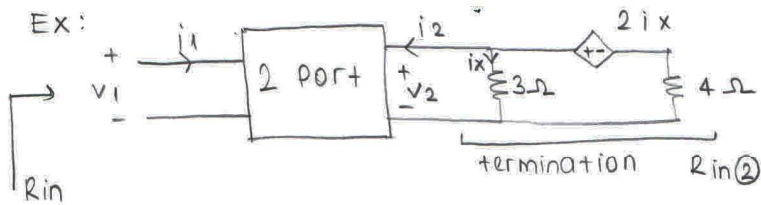\* ABCD parameters of the cascade is the matrix multiplication of two ports I & II



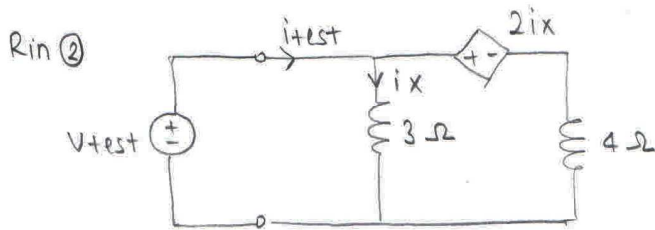
$$\begin{bmatrix} v_1 \\ v_2 \end{bmatrix} = \begin{bmatrix} 3 & 2 \\ 2 & 4 \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \end{bmatrix}$$



$$i_x = \frac{v_{test}}{3}$$

$$i_{test} = i_x + \frac{i_x}{4} = \frac{5}{4} i_x = \frac{5}{12} v_{test}$$
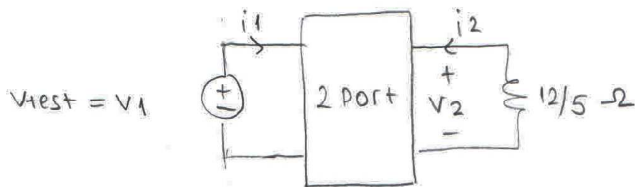
$$R_{in(2)} = \frac{v_{test}}{i_{test}} = \frac{12}{5} \Omega$$



Let's apply  $v_{test}$  and measure  $i_{test}$

$$\begin{bmatrix} v_1 \\ v_2 \end{bmatrix} = \begin{bmatrix} 3 & 2 \\ 2 & 4 \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \end{bmatrix} \quad \text{I need } \frac{v_1}{i_1}$$

$$v_1 = 3i_1 + 2i_2$$


$$v_2 = 2i_1 + 4i_2$$

$$v_2 = \frac{12}{5} (-i_2) = -\frac{12}{5} i_2 = 2i_1 + 4i_2 \quad ; \quad i_1 = -\frac{16}{5} i_2$$


$$v_1 = 3i_1 + 2i_2 = 3i_1 - \frac{5}{8} i_1 = \frac{19}{8} i_1$$

$$R_{in} = \frac{19}{8} \Omega$$

T network

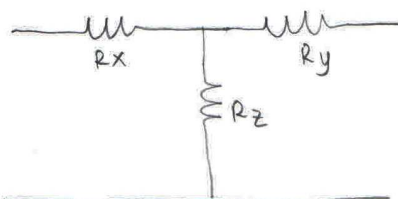

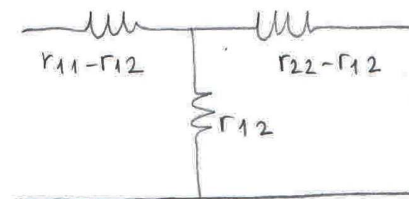
$$R = \begin{bmatrix} r_{11} & r_{12} \\ r_{21} & r_{22} \end{bmatrix} = \begin{bmatrix} R_x + R_y & R_y \\ R_y & R_y + R_z \end{bmatrix}$$




$$r_{12} = r_{21} \quad (\text{T network})$$

Let's go back previous problem

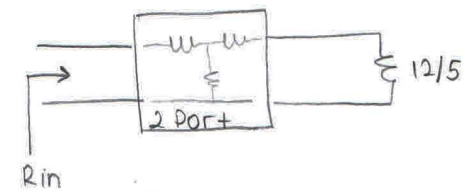

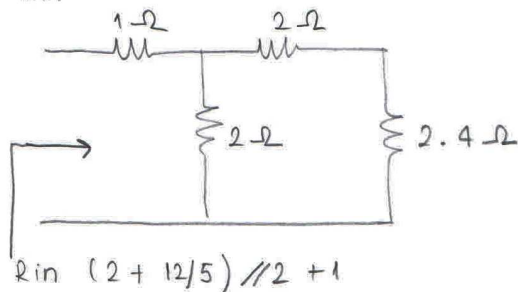
$$R = \begin{bmatrix} 3 & 2 \\ 2 & 4 \end{bmatrix}$$



Note: T network requires a symmetric R matrix

π Network

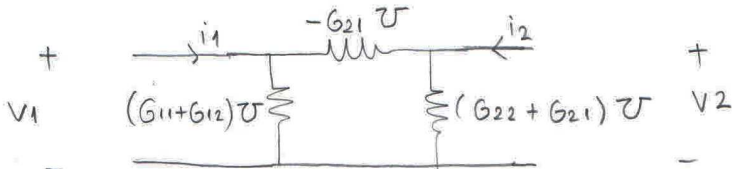


$$\begin{bmatrix} i_1 \\ i_2 \end{bmatrix} = \begin{bmatrix} G_{11} & G_{12} \\ G_{21} & G_{22} \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix}$$

conductance matrix

(requires symmetric  $\underline{G}$  matrix)


\*

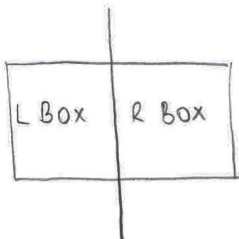

To apply Thevenin Equivalent, all circuit components in the port of the circuit whose equivalent is sought should be well defined, that is dependent sources should have their dependent variable branch in the port of the circuit where Thevenin is sought

Similarly, the both sides of the transformer should be in the same box.

Two Ports

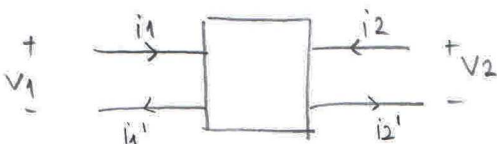


validity conditions:  $i_1 = i_1'$   
 $i_2 = i_2'$

Main assumption:  $\{ i_1, V_1, i_2, V_2 \}$  4 variables  
2 out of these 4 variables are inputs  
(Independent variable)

The rest is determined from the outputs (so a function of inputs)  
linear mapping of inputs

Π Parameters

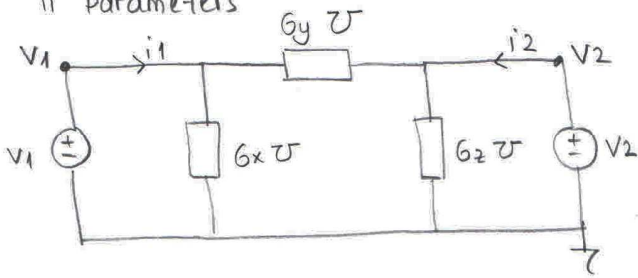

$$\begin{bmatrix} i_1 \\ i_2 \end{bmatrix} = \begin{bmatrix} G_{11} & G_{12} \\ G_{21} & G_{22} \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix}$$


$$i_1 = G_x V_1 + G_y (V_1 - V_2)$$

$$i_2 = G_z V_2 + G_y (V_2 - V_1)$$

$$\begin{bmatrix} i_1 \\ i_2 \end{bmatrix} = \begin{bmatrix} G_x + G_y & -G_y \\ -G_y & G_y + G_z \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix}$$

If you want to find only  $G_{22}$  then

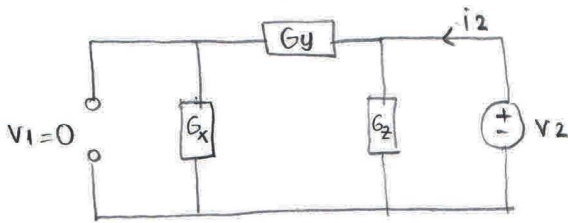
$$i_2 = G_{21} V_1 + G_{22} V_2 \quad \downarrow \quad V_1 = 0 \quad i_2 = G_{22} V_2$$



$$\frac{V_2}{i_2} = R_{in} = R_y // R_z$$

$$G_{22} = G_y + G_z$$

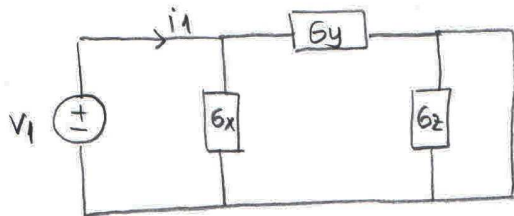
for  $G_{11}$ ;  $i_1 = G_{11} V_1 + G_{12} V_2 \quad \downarrow \quad V_2 = 0$



$$\frac{V_1}{i_1} = R_x // R_y$$

$$G_{11} = G_x + G_y$$


for  $G_{12}$ ;

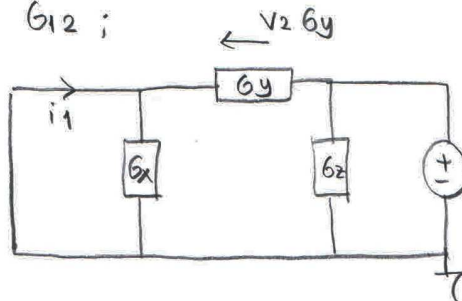

$$i_1 = -G_y V_2$$


$$G_{12} = -G_y$$

Interconnection of Two-ports

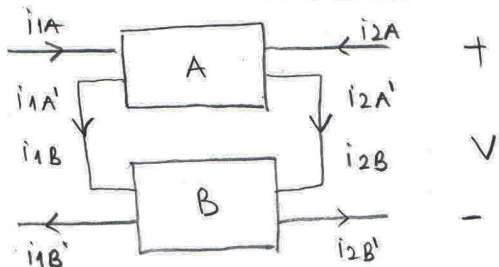


R parameters of the connected 2 ports;

$$R = R_A + R_B$$

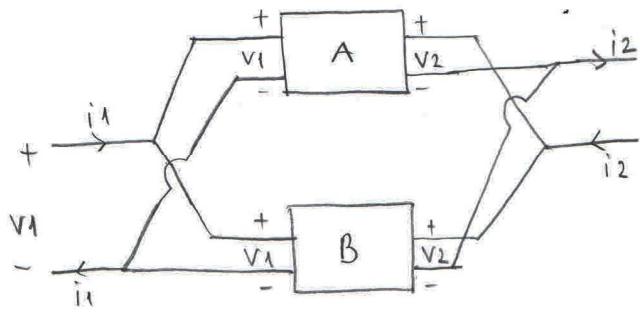

$$G_t = G_A + G_B$$


### Two-ports with Feedback

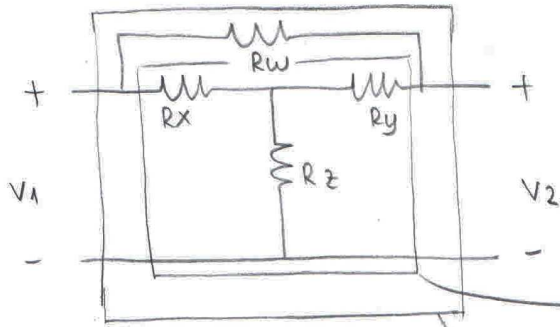

→ is not valid 2-port

→ is valid 2-port




### Transformers

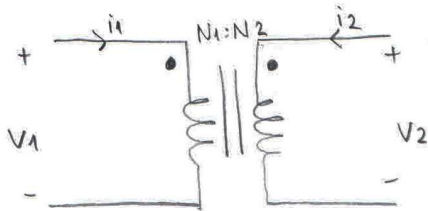


$$\frac{V_1}{V_2} = \frac{N_1}{N_2} = -\frac{i_2}{i_1}$$

$$\begin{bmatrix} V_1 \\ i_1 \end{bmatrix} = \begin{bmatrix} N_1/N_2 & 0 \\ 0 & N_2/N_1 \end{bmatrix} \begin{bmatrix} V_2 \\ -i_2 \end{bmatrix}$$

### ABCD parameters

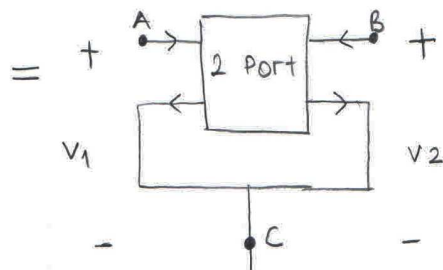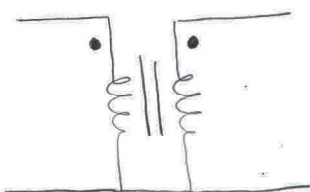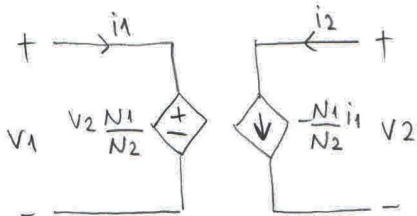

ABC, three terminal two port

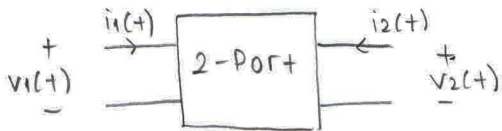

$$P_{2\text{port}} = v_1(t)i_1(t) + v_2(t)i_2(t) \quad (\text{Absorbed power by two port})$$

$$= 0$$

$P(t)$  of ideal transformer is zero (Lossless component)



### Reciprocity

If a 2port does not contain a dependent component (source), then  $\underline{R}$  &  $\underline{G}$  matrices are guaranteed to be symmetric ( $r_{12} = r_{21}$ ,  $g_{12} = g_{21}$ )

Under the same conditions; (no dependent source)



$$h_{12} = -h_{21} \quad (\text{skew symmetric})$$

1-)

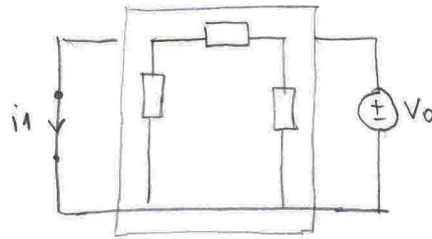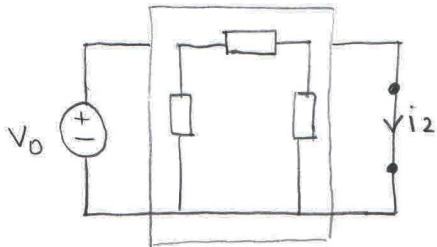

$$i_1 = i_2 \quad \text{since} \quad g_{12} = g_{21}$$



2-)

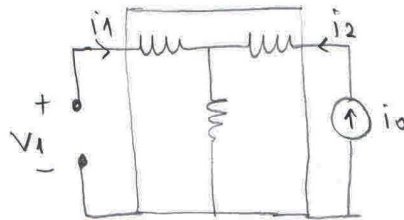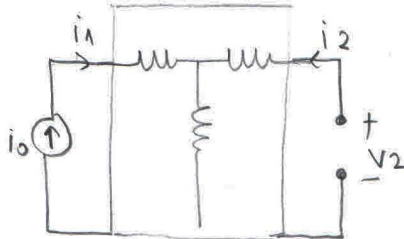

$$v_1 = v_2 \quad \text{since} \quad r_{12} = r_{21}$$

$$\begin{bmatrix} v_1 \\ v_2 \end{bmatrix} = \begin{bmatrix} r_{11} & r_{12} \\ r_{21} & r_{22} \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \end{bmatrix}$$

3-)

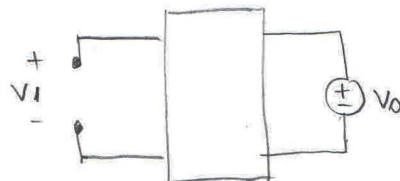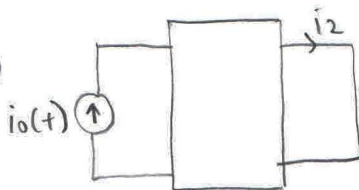

$$v_1 = i_2 \quad (\text{numerically}) \quad \text{since} \quad h_{21} = -h_{12}$$

Proof of 3<sup>rd</sup> case;

$$v_1 = i_2$$

$$\sum v_k i_k = \sum \hat{v}_k i_k \quad (\text{2 port contain resistors})$$


$$v_1 \hat{i}_1 + v_2 \hat{i}_2 + \underbrace{\sum_{k=3} v_k i_k}_{\text{for the branches in 2-port}} = \hat{v}_1 i_1 + \hat{v}_2 i_2 + \sum_{k=3} \hat{v}_k i_k$$

for the branches in 2-port



$$V_1 \hat{i}_1 + V_2 \hat{i}_2 = \hat{V}_1 i_1 + \hat{V}_2 i_2$$

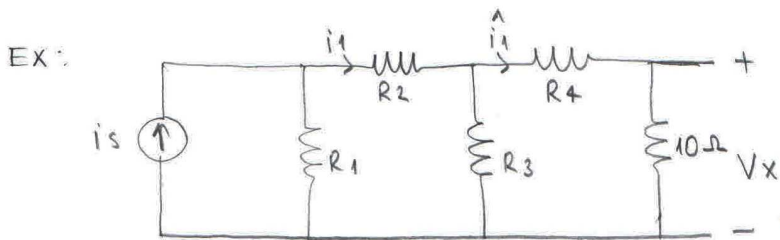
$$= \hat{V}_1 (-i_0) + (-i_2) i_0 ; \quad \hat{V}_1 = i_2$$



Calculate  $R_1$

$$i_1 = 0.6 i_s$$

$$\hat{i}_1 = 0.3 i_s$$

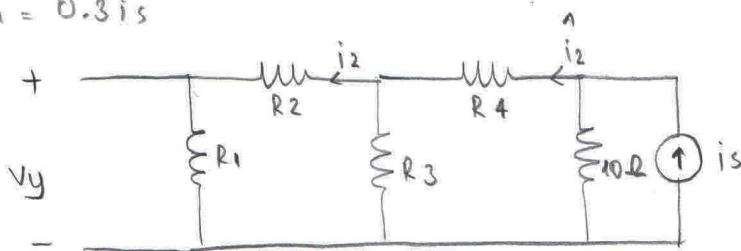




$$i_2 = 0.2 i_s$$

$$\hat{i}_2 = 0.5 i_s$$


$V_x = V_y$  from reciprocity  $10 \hat{i}_1 = R_1 i_2$   $R_1 = \frac{10 \hat{i}_1}{i_2} = 15 \Omega$

ZPS II ; 10-)
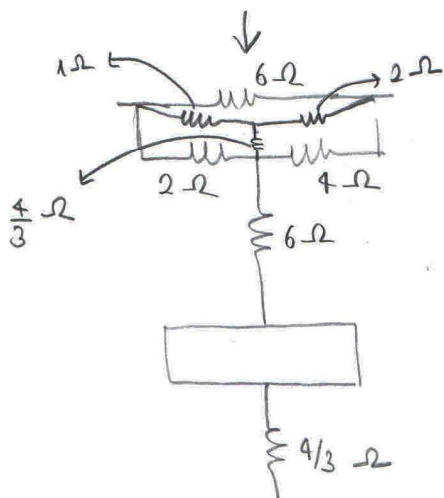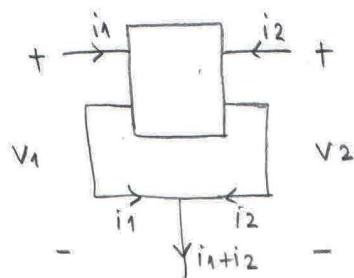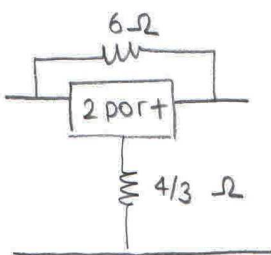
$$\begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} 8 & 6 \\ 6 & 10 \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \end{bmatrix}$$




$\equiv$

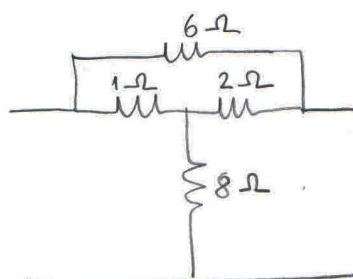


$$R = \begin{bmatrix} 9 & 8 \\ 8 & 10 \end{bmatrix}$$

### Symmetric Circuits


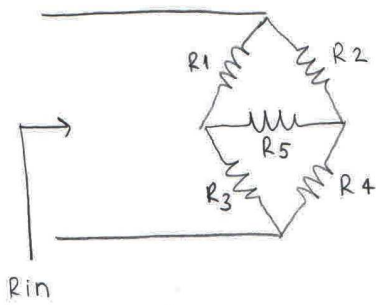


1.  $R_1 = R_2$  ;  
 $R_3 = R_4$

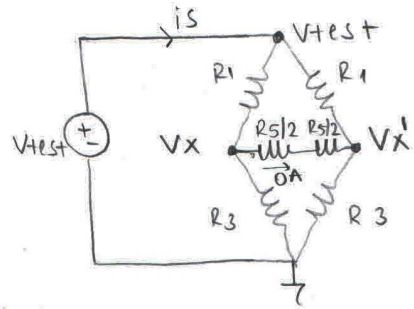


$$R_{in} = \left( \frac{R_1 + R_3}{2} \right)$$

2.  $R_1 = R_3$  ;  
 $R_2 = R_4$

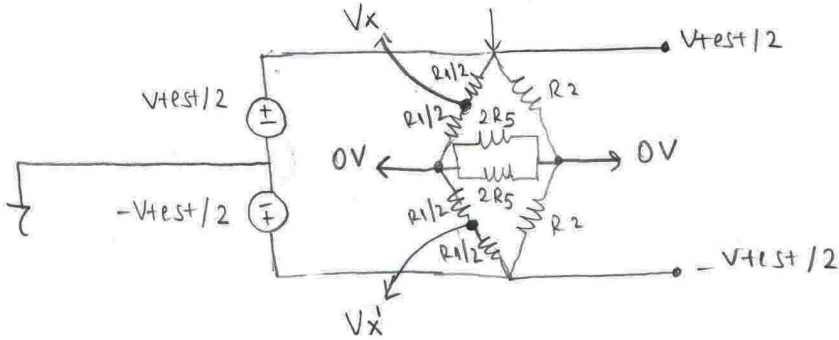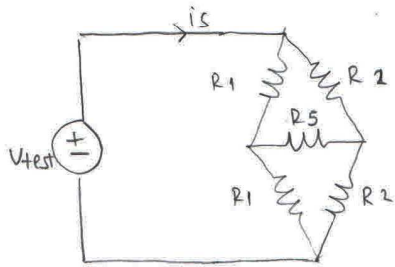


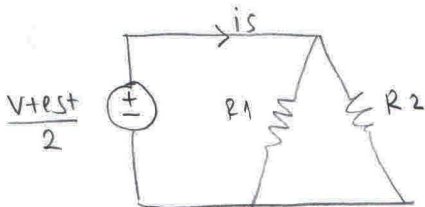Due to symmetry  $V_x = -V_x'$   
 So symmetry axis has 0V potential  
 due to symmetry




$$R_{in} = \frac{V_{test}}{i_s} = 2(R_1 // R_2) \quad \text{since} \quad i_s = \frac{V_{test}}{2(R_1 // R_2)}$$


EX :

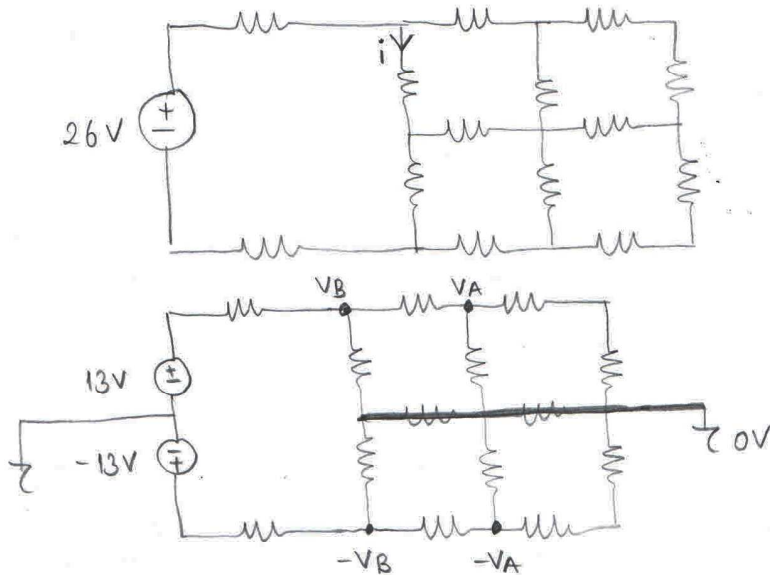

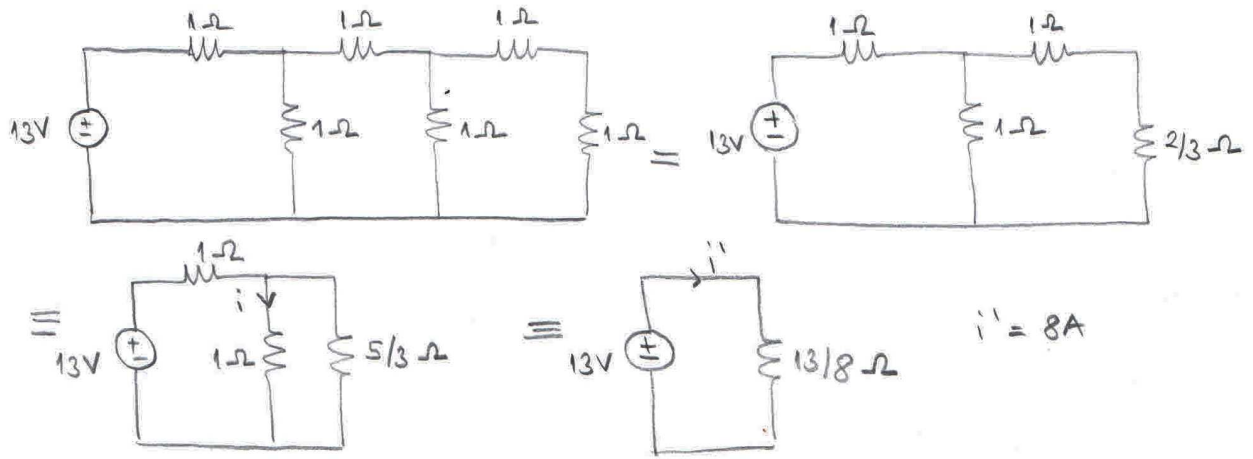All resistors are  $1\Omega$   
 Find  $i = ?$




$i = 5A$

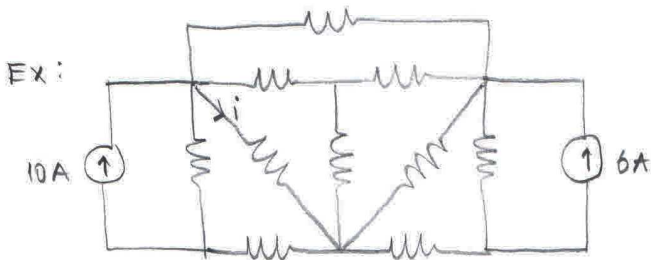


All resistors are  $1\Omega$  Find  $i = ?$

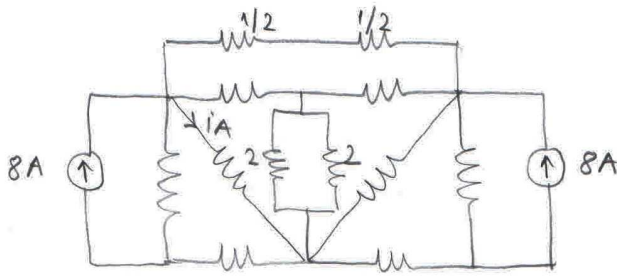$\begin{bmatrix} r_{11} & r_{12} \\ r_{21} & r_{22} \end{bmatrix}$  reciprocal





symmetric excitation


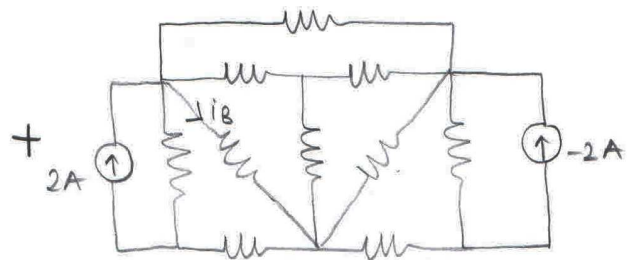


anti-symmetric excitation

$i = i_A + i_B$  (linearity rule)

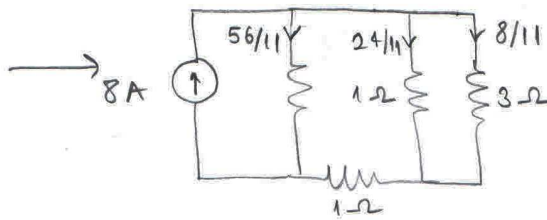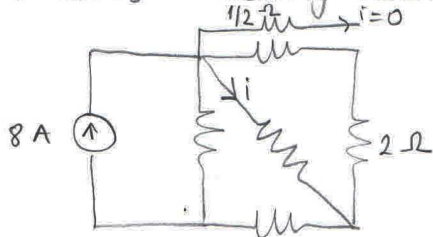

$i_A = 24/11$

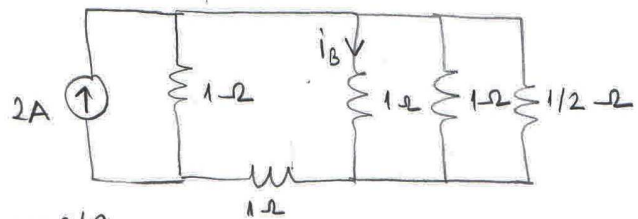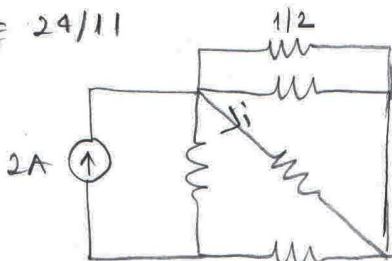


$i_B = 2/9$


$i = i_A + i_B$

Diodes  $\rightarrow$  Nonlinear resistors



current controlled component  $v_c = f(i_c)$

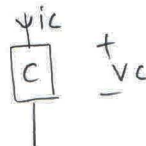voltage controlled component  $i_c = f(v_c)$




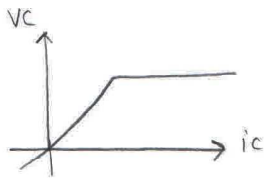

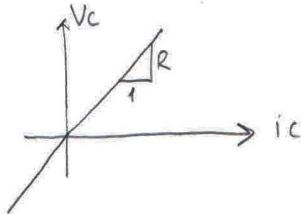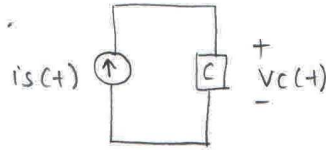Current controlled: every current value, there is a voltage value.




Both current and voltage controlled


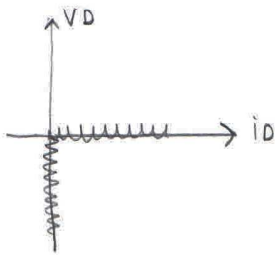


Neither current nor voltage controlled

Nonlinear

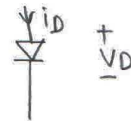


Operation Regions:

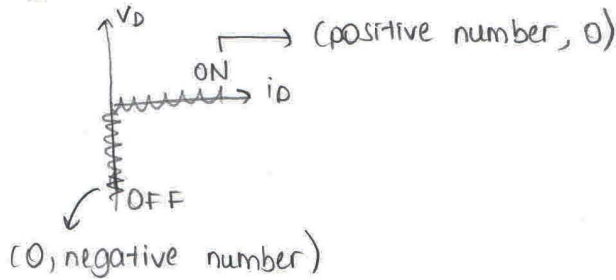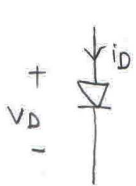


OFF  $\rightarrow i_D = 0$

ON  $\rightarrow V_D = 0$


for ideal diode

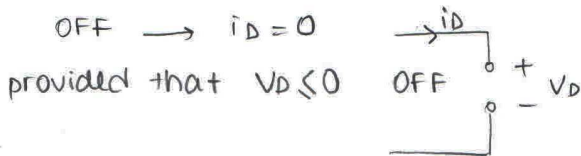

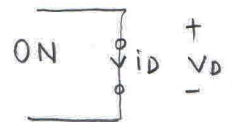
ON  $\rightarrow V_D = 0$   
provided that  $i_D > 0$



Ex:

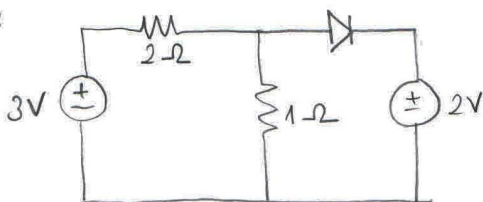


Assume OFF;

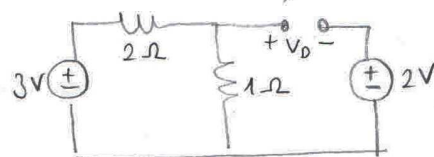

$V_D = -1 < 0$   
correct assumption


Assume ON;

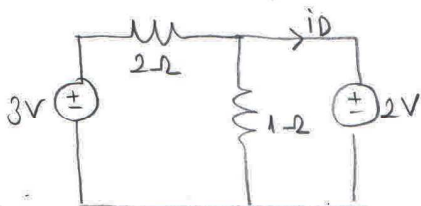

$i_D = -3/2 < 0$  Wrong assumption!

# Series and parallel combination


Series:

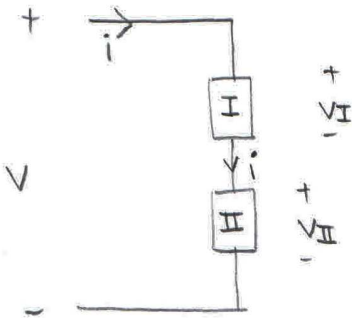

$$V = V_I + V_{II}$$


$$V_I = f_I(i)$$

$$V_{II} = f_{II}(i)$$

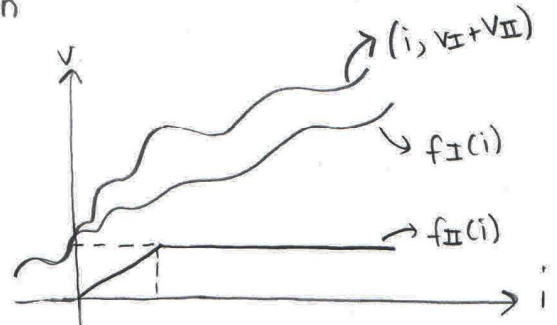


graphs are added vertically

Parallel:

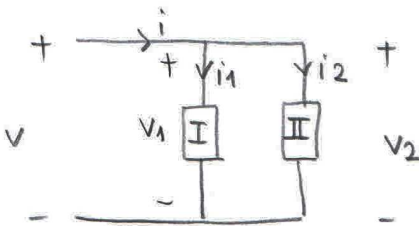


constraints:  $V = V_1 = V_2$

$$i = i_1 + i_2$$

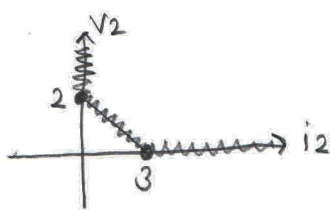




$$i_2 = g_2(V_2)$$

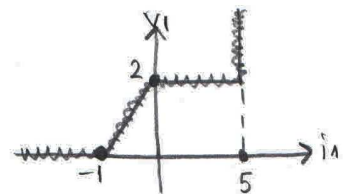



$$i_1 = g_1(V_1)$$

Graphs are added horizontally

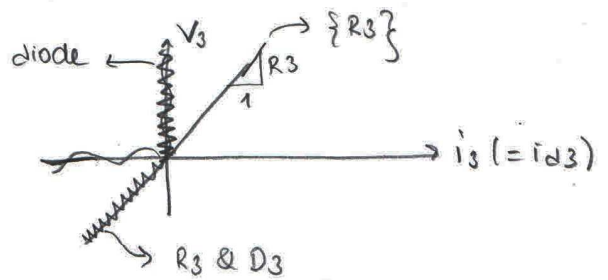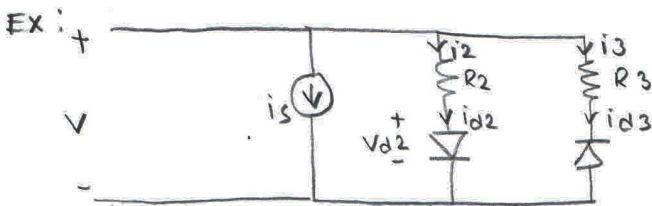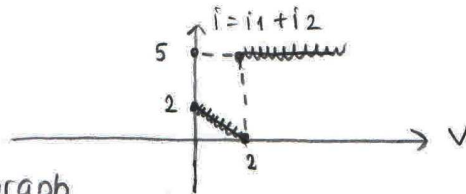Note: From these 2 graphs, this is parallel combination  $i-v$  is calculated by vertically adding the graph




Diodes are ideal

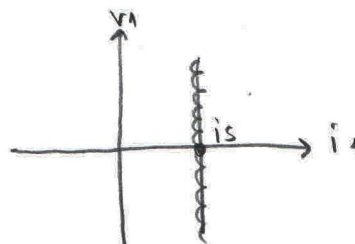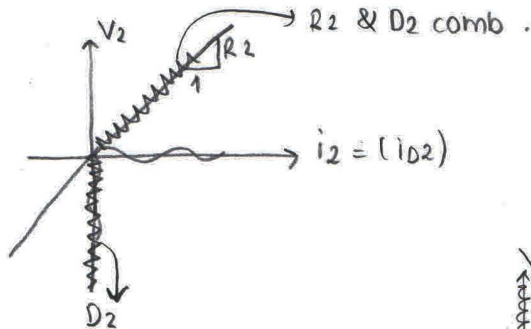


combine all.


$$V_1 = V_2 = V_3 = V$$

D2 OFF  
D3 ON




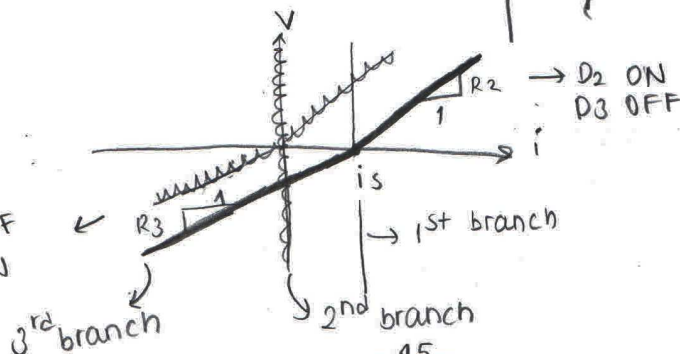


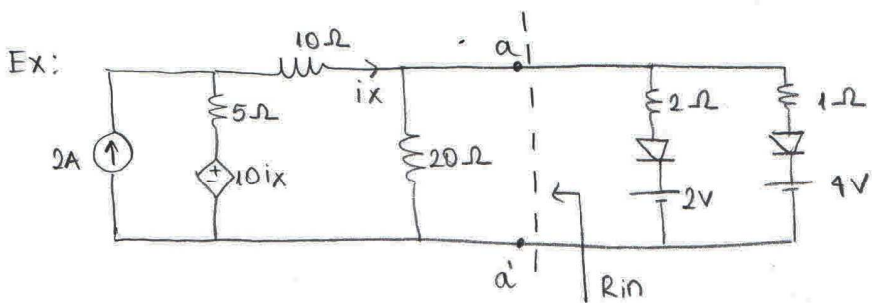

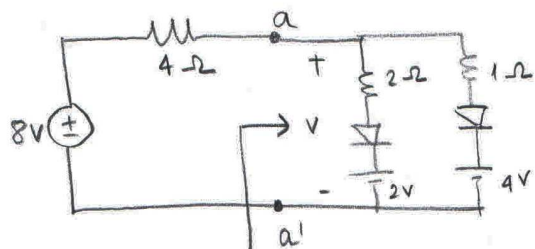Thevenin equivalent of the LHS of  $a-a'$



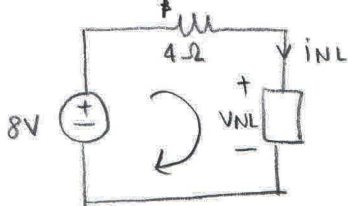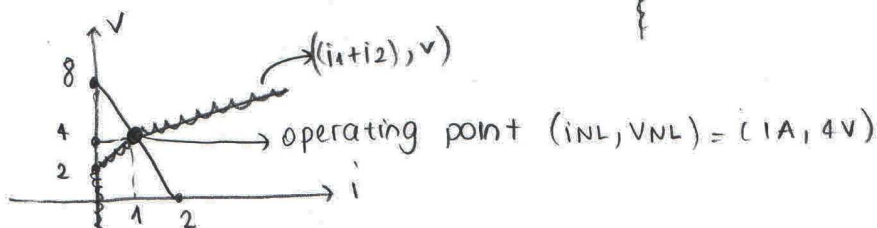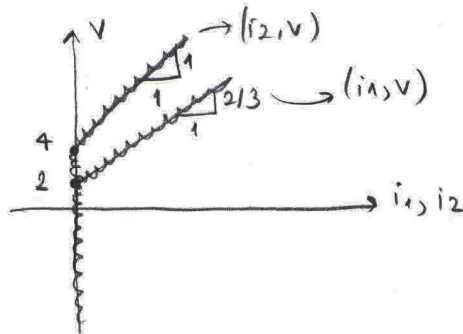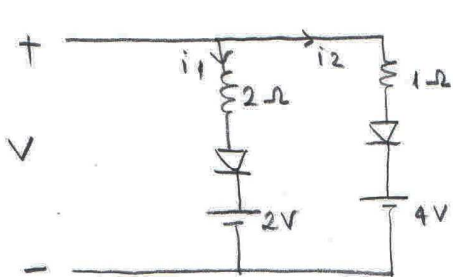So let's find  $i-v$  characteristic of RHS of  $a-a'$




$$-8 + 4i_{NL} + V_{NL} = 0$$

$$V_{NL} = 8 - 4i_{NL}$$

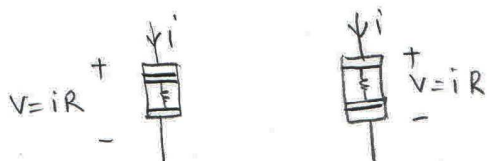
### Bilateral Component

Simple LTI resistors are bilateral. That is, if you flip the resistor, you get the same  $i-v$  characteristic









So if you change  $i \rightarrow -i$   
 $v \rightarrow -v$

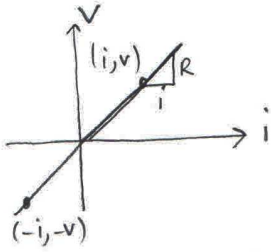In other words, both  $i-v$  and  $(-i) - (-v)$  should be on the  $i-v$  characteristics for bilateral component





So; bilateral components has symmetry across the origin



Practical Diode

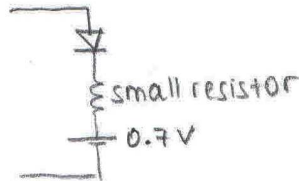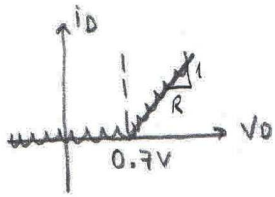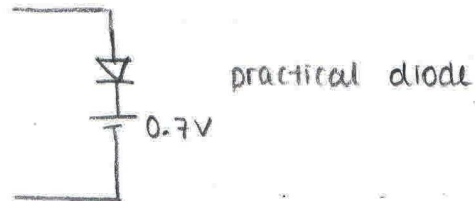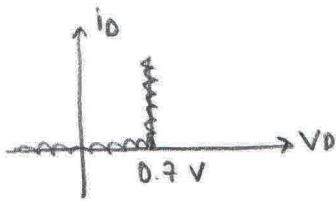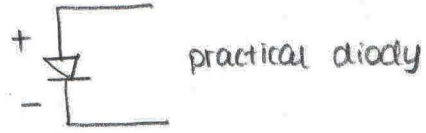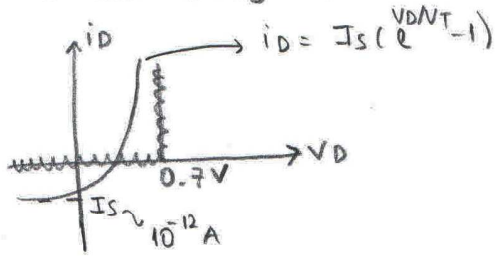

Another practical diode

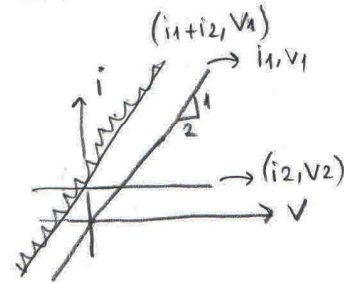
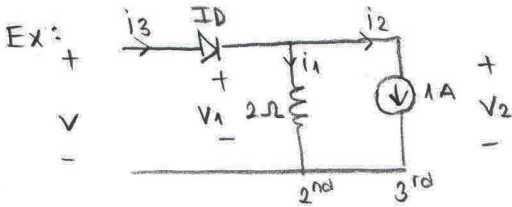


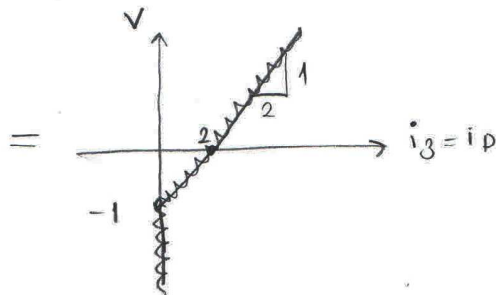
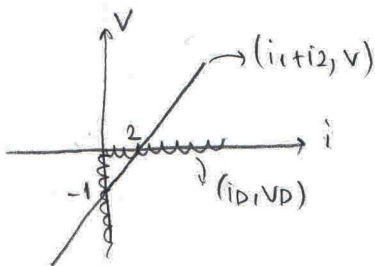
for 2<sup>nd</sup> and 3<sup>rd</sup> branches







Synthesis

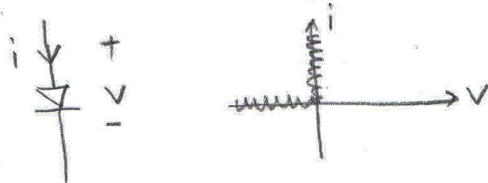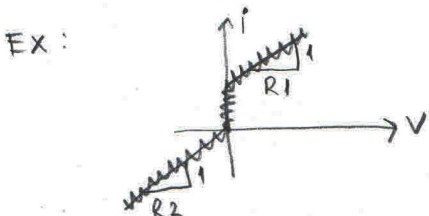Design a one port with R's and independent sources and ideal diodes such that we have the desired i-v characteristics.




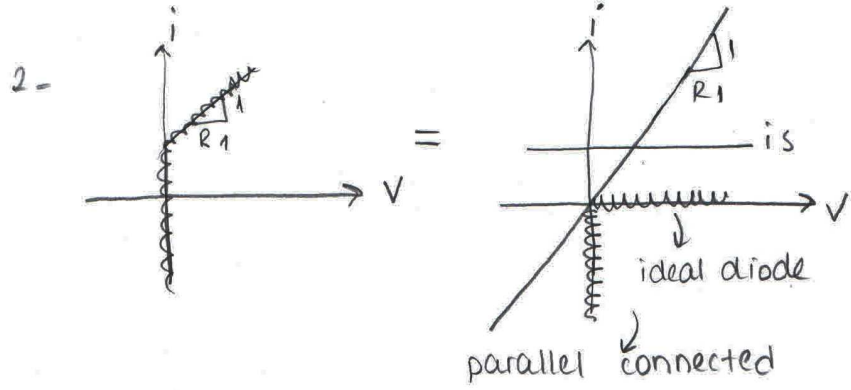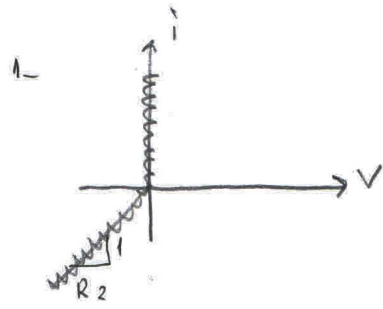


1 & 2 are connected in series.

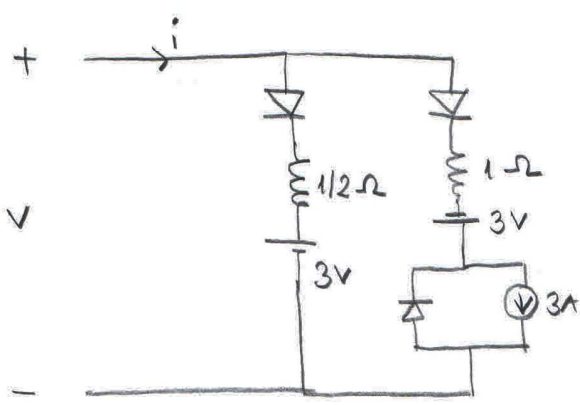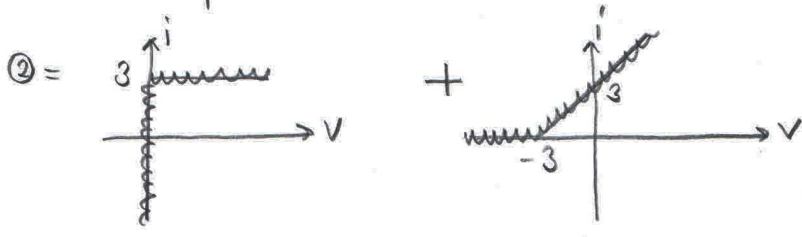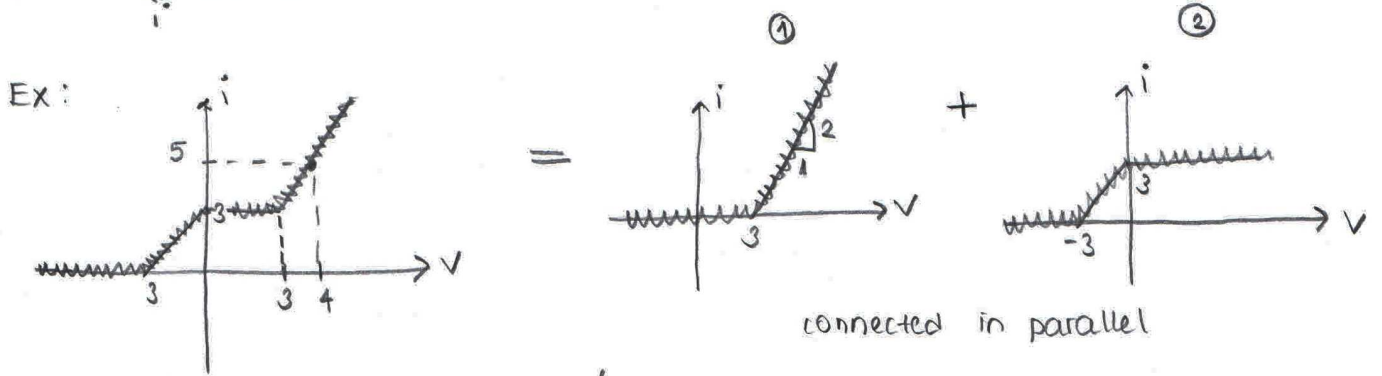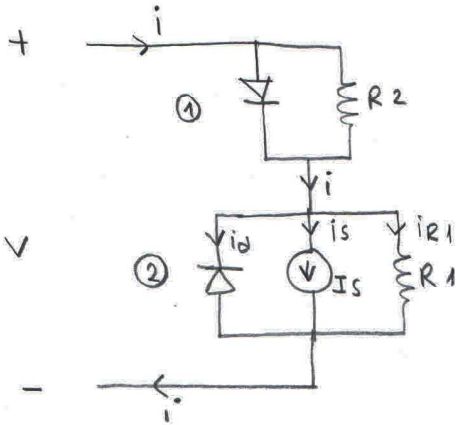



Diode Applications  
Half-Wave rectifier

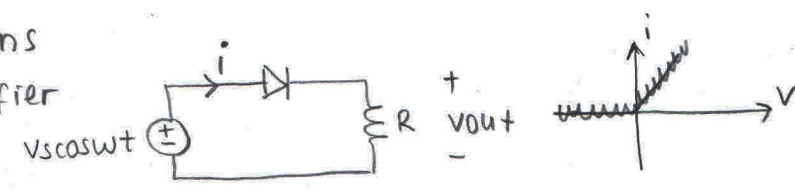




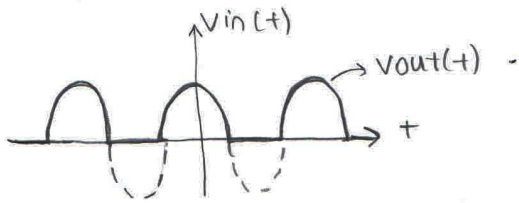

Full wave rectifier:

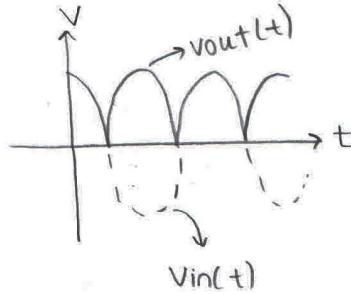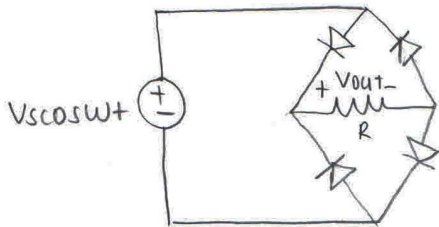


Ex:

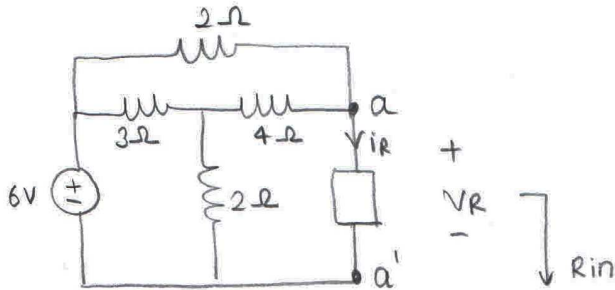


$$i_R = \begin{cases} 0.03 V_R^2, & V_R \geq 0 \\ 0, & V_R < 0 \end{cases}$$

Find Thevenin equivalent and then solve for  $i_R$  using load lines or algebraically.

Thevenin equivalent:

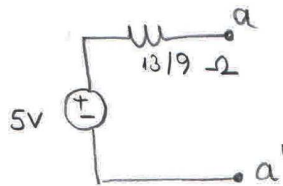

Algebraic method:

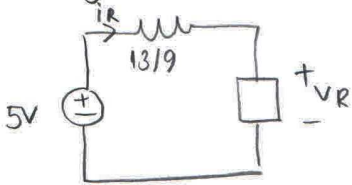

by KVL;  $-5 + 13/9 i_R + V_R = 0$

Let's assume  $V_R > 0$


$$-5 + 13/9 (0.03 V_R^2) + V_R = 0$$

$$V_R = \left\{ 4.22V, \text{ a negative number} \right\}$$

$V_R = 4.22V$  is a solution


$$i_R = 0.03 (4.22)^2$$

Load line method:

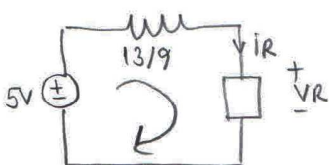


$-5 + (13/9) i_R + V_R = 0$  2 equations, 2 unknowns
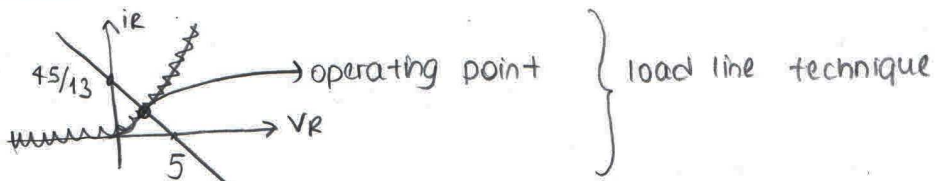
$$i_R = \begin{cases} 0.03 V_R^2, & V_R \geq 0 \\ 0, & V_R < 0 \end{cases}$$




## Small-Signal Analysis

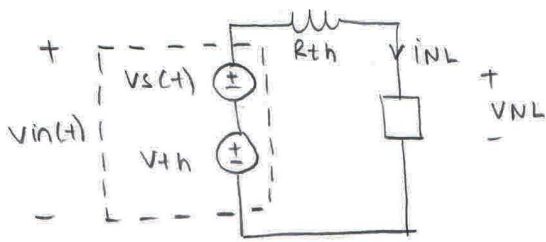


$V_{th}$  is a DC voltage  
 $v_s(t)$  is a time function

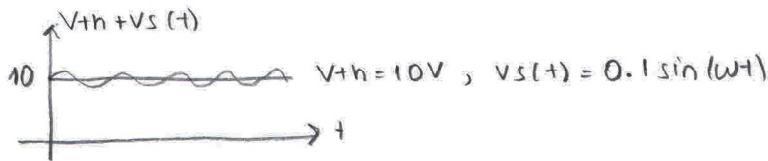We assume that  $V_{th} \gg v_s(t) \quad \forall t$




As in previous problem,

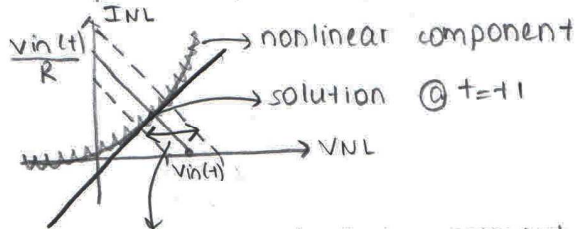

solution is surely in this segment  
 (since  $v_{in}$  changes over  $t$ )

approximation of NL component around DC operating point

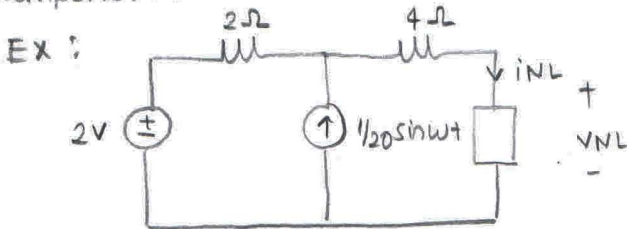- 1- Find DC operating point
- 2- Express Taylor series expansion of NL function around DC operating point and take the linear term only
- 3- Using the slope in the Taylor series expansion, find the solution for alternating component.




$$i_{NL}(t) = \begin{cases} V_{NL}^2, & V_{NL} \gg 0 \\ 0 & V_{NL} < 0 \end{cases} = f(V_{NL})$$

$$i_{NL}(t) = f(V_{NL}) = \sum_{k=0}^{\infty} \frac{f^{(k)}(t_0)}{k!} (t-t_0)^k$$


$$f(V_{NL}) = V_{NL}^2 = \begin{cases} 1 + \frac{2}{1!} (V_{NL}-1) + \frac{2}{2!} (V_{NL}-1)^2 & \text{expansion around } V_0=1 \end{cases}$$

$$4 + \frac{4}{1!} (V_{NL}-2) + \frac{4}{2!} (V_{NL}-2)^2 \quad \text{expansion around } V_0=2$$

1. Find DC operating point

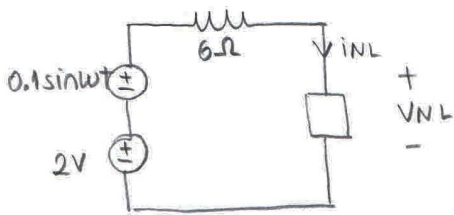

for DC operating point;

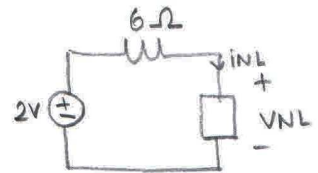


$$-2 + 6i_{NL} + V_{NL} = 0 \quad V_{NL}^2 = i_{NL} \text{ for } V_{NL} \gg 0$$

$$V_{NL} = \left\{ \frac{1}{2}, -\frac{2}{3} \right\} \text{ for } V_{NL} \gg 0$$


then  $V_{NL} = 1/2$  is the solution

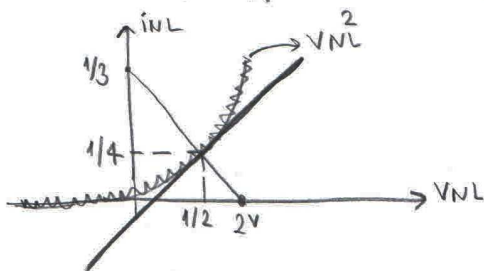2. Then expand nonlinearity around  $V_0 = 1/2$  (DC operating point)

$$V_{NL} = \frac{1}{4} + \frac{1}{1!} (V_{NL} - 1/2) + \frac{2}{2!} (V_{NL} - 1/2)^2$$




Then, small signal model;

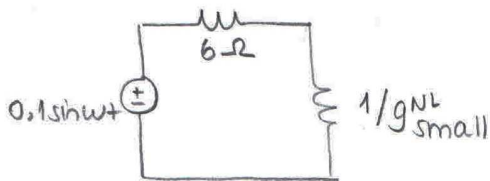

$$g_{NL}^{small} = f'(V_0) = 2V_0 \Big|_{V_0=1/2} = 1 \text{ } \Omega^{-1}$$

small signal conduction parameter


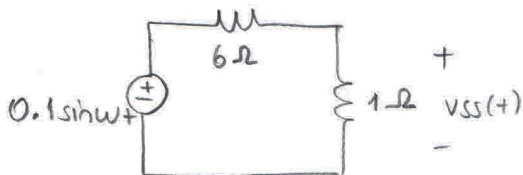


$$V^{SS}(+) = 1/7 (0.1 \sin \omega t)$$


$$V_{NL}(+) = 1/2 + 1/70 \sin \omega t \rightarrow \text{solution due to alternating input}$$

DC operating point


Operational Amplifier

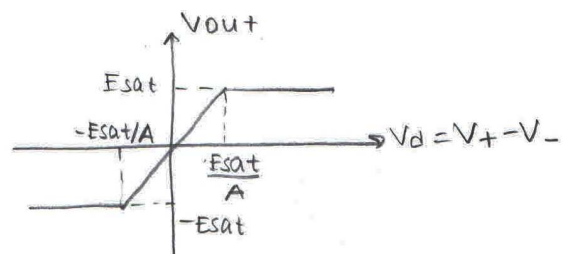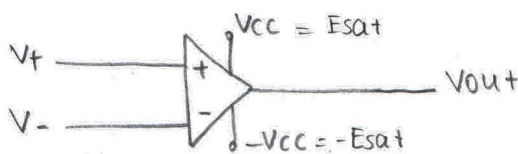

Ideal Op-Amp Model

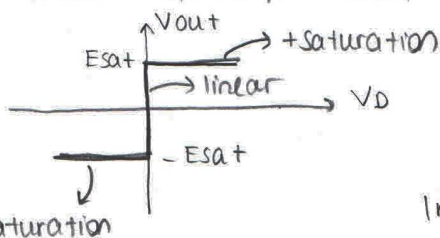


$A = \infty$

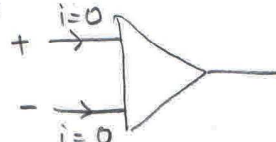

$$[R_{in} = \infty, r_{out} = 0]$$

In linear region;  $V_d = 0$ ,  $V_+ = V_-$  and  $|V_{out}| < E_{sat}$

### Inverting Amplifier

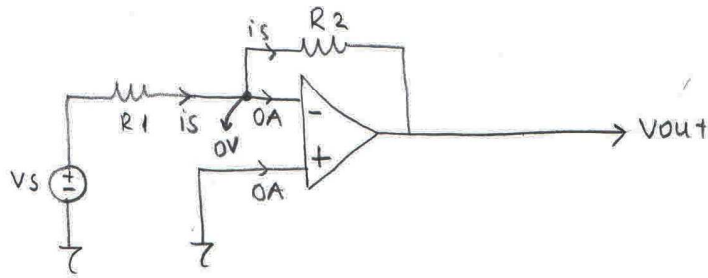


Assume that Op-Amp is in linear region.  $V_{out} = ?$

$$i_s = \frac{V_s - 0}{R_1} \quad V_{R_2} = i_s R_2 = \frac{R_2}{R_1} V_s$$


$$V_{out} = 0 - V_{R_2} = -\frac{R_2}{R_1} V_s$$
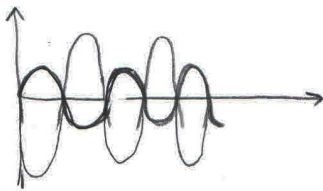
$$\frac{V_{out}}{V_s} = -\frac{R_2}{R_1} \text{ inverting } (R_2/R_1 = 2)$$



The analysis ( $V_{out}$ ) is correct if  $|V_{out}| < E_{sat} \frac{R_2}{R_1}$  (Validity condition)

### Noninverting Amplifier

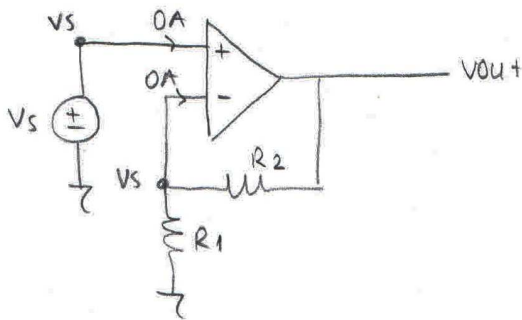


Assume that ideal Op-Amp in linear region

Find  $V_{out}$


$$\frac{-V_s}{R_1} = \frac{V_s - V_{out}}{R_2} \quad ; \quad V_{out} = \frac{R_1 + R_2}{R_1} V_s$$

noninverting amplifier

### Improved Model

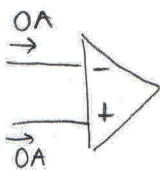

$$R_{in} = \infty \quad r_o = 0$$


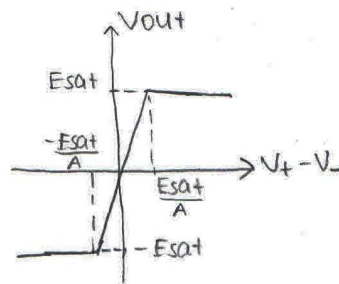


Finite gain ( $A$ ) model

$A$ : open loop gain

1- Assume Op-Amp in linear region

### Inverting Amplifier

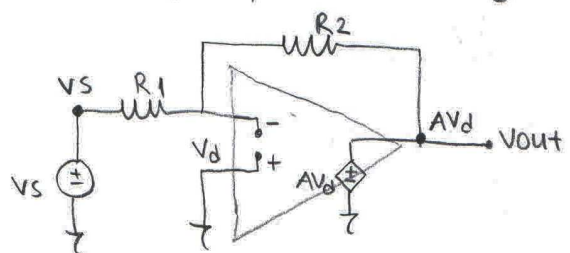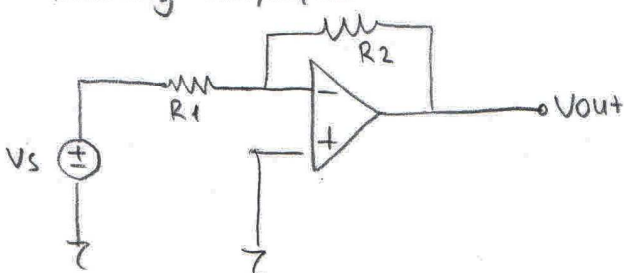

$$\frac{V_s + V_d}{R_1} = \frac{-V_d - AV_d}{R_2}, \quad R_2 V_s + R_2 V_d = -R_1 V_d - R_1 A V_d$$


$$(R_1 A + R_2 + R_1) V_d = -R_2 V_s; \quad V_d = \frac{-R_2}{R_1 A + R_1 + R_2} V_s \text{ in linear region}$$

$$V_{out} = AV_d = \frac{-AR_2}{R_1 A + R_1 + R_2} V_s$$

as  $A \rightarrow \infty$   $V_{out} \rightarrow -\frac{R_2}{R_1} V_s$  (as previously found)

Linear region assumption is valid.

$$|V_{out}| < E_{sat} \rightarrow |V_{in}| < \frac{R_2 + (1+A)R_1}{AR_2} E_{sat}$$

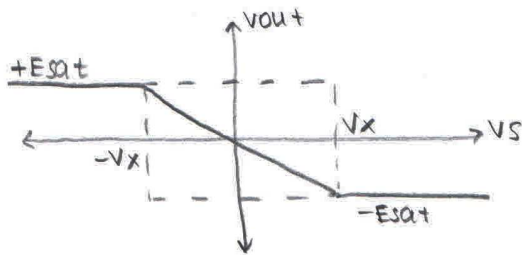


$$V_x = \frac{R_1(A+1) + R_2}{AR_2} E_{sat}$$

$$V_{out} = \frac{-AR_2}{R_1(A+1) + R_2} V_s$$


2. Assume  $-E_{sat}$ ;

$$V_{out} = -E_{sat}$$

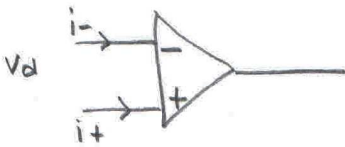


$$i_- = i_+ = 0 \text{ A}$$

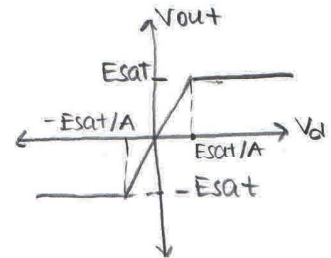Validity condition  $V_d < -\frac{E_{sat}}{A}$



Assume  $-E_{sat}$

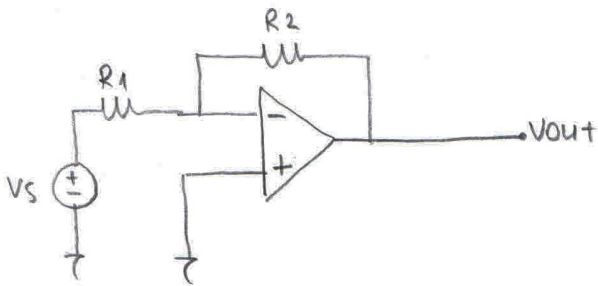

$$V_s - iR_1 = -V_d$$


$$i = \frac{V_s + E_{sat}}{R_1 + R_2}$$

$$V_d = \frac{R_1(V_s + E_{sat})}{R_1 + R_2} - V_s$$

So  $-E_{sat}$  region is valid when  $V_d < -\frac{E_{sat}}{A}$


$$\frac{R_1(V_s + E_{sat})}{R_1 + R_2} - V_s < -\frac{E_{sat}}{A} \Rightarrow AR_1(V_s + E_{sat}) - A(R_1 + R_2)V_s < -(R_1 + R_2)E_{sat}$$
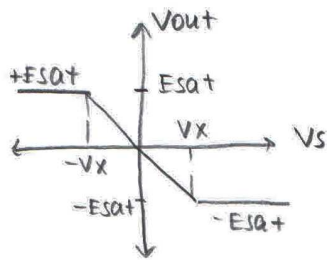
$$V_s > \frac{E_{sat} + (R_1 + R_2) + A R_1 E_{sat}}{A R_2} \quad - \quad V_s > \frac{R_1 (1+A) + R_2}{A R_2} E_{sat} \quad v_{out} = -E_{sat} \text{ if condition is satisfied}$$




Transfer (input-output) characteristic


Further improved model

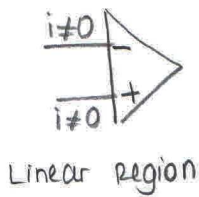


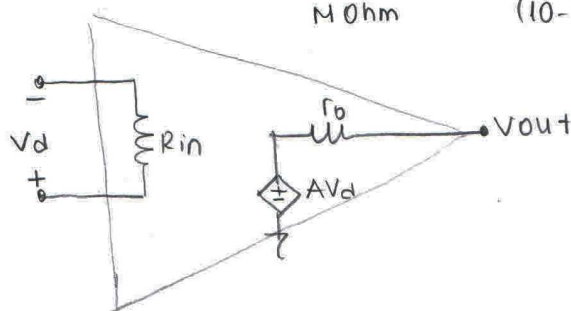
typical values:  $R_{in}$ : finite Mohm,  $r_o$ : finite (10-100  $\Omega$ ),  $A$ : finite  $10^6$



Inverting Amplifier (nonideal)

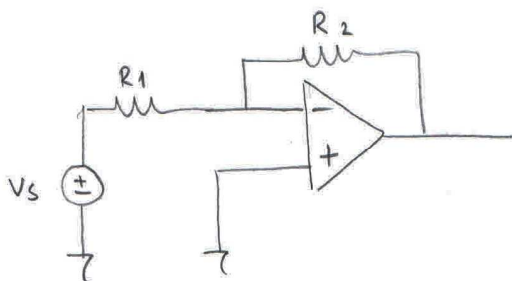

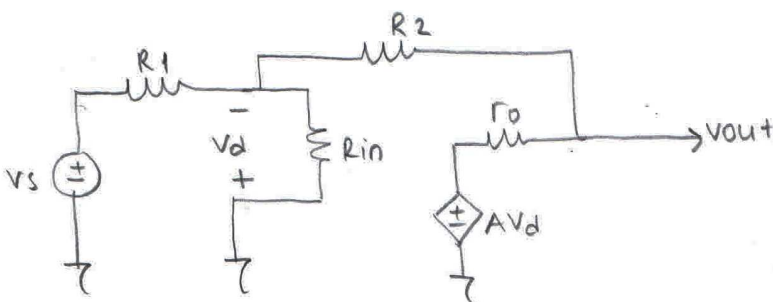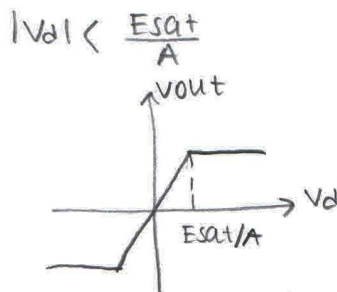Assume linear ( $R_{in}, r_o, A$ : finite) and



For no load condition that at the output of Op-Amp there is nothing connected  
Then  $i_{load} = 0$

Write KCL at  $-V_d$  node } solve for  $V_d, V_{out}$   
at  $V_{out}$  node

$$V_{out} = \frac{-A + r_o/R_2}{\frac{R_1}{R_2} (1+A + \frac{r_o}{R_{in}}) + (\frac{R_1}{R_{in}} + 1) + \frac{r_o}{R_2}} \cdot V_s \quad *$$


In (\*) as  $A \rightarrow \infty$   $V_{out} = -\frac{R_2}{R_1} V_s$ ,  $V_{out} = \frac{-A}{\frac{R_1}{R_2} (1+A) + 1}$  as  $A$  finite  $V$   
( $r_o = 0, R_{in} \rightarrow \infty$ ) result for 1<sup>st</sup> Model (result for 2<sup>nd</sup> Model)

So if  $R_1, R_2$  in the inverting amplifier  $\{R_1, R_2\} \gg r_o$   
 then  $\{R_1, R_2\} \ll R_{in}$


### Operational Amplifier Applications

Assume linear region for Op-Amp and take  $A \rightarrow \infty$  i.e. the ideal Op-Amp mode in the following circuits.


#### 1. Summer Amplifier

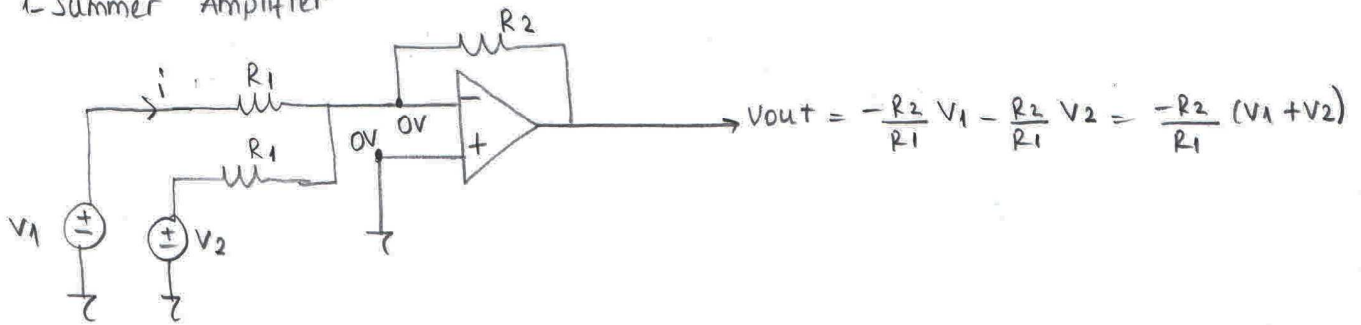

#### 2. Difference Amplifier

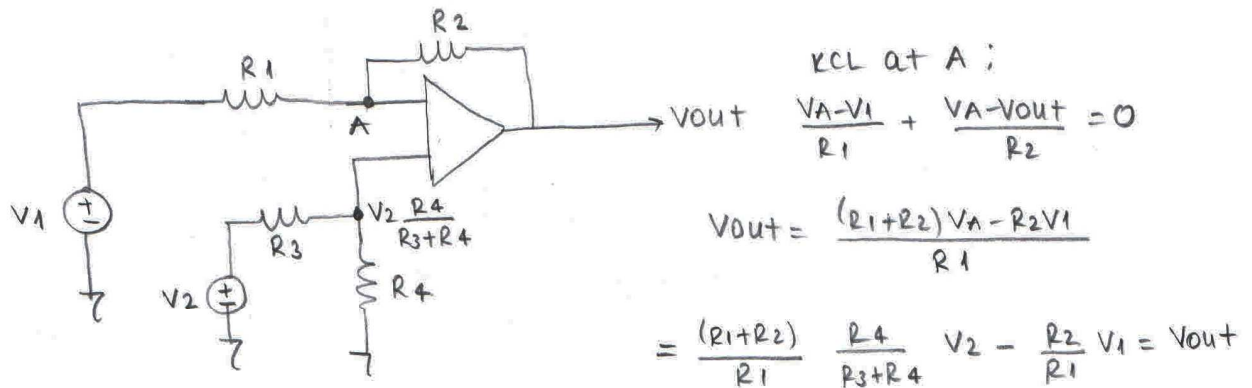

#### 3. Integrator Amplifier

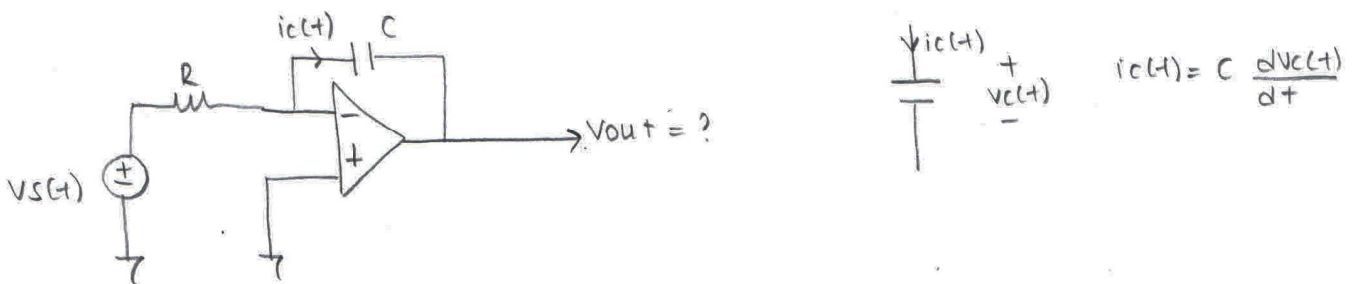

$i_c(t) = V_s/R$

$v_c(t) = -V_{out} ; \quad \frac{V_s(t)}{R} = C \frac{d}{dt} (-V_{out})$

$\frac{d}{dt} V_{out}(t) = -\frac{1}{RC} V_s(t)$

Integrate this equation to find  $V_{out}$

1. Assume  $V_c(0^-) = V_0$  is given

$\int_0^+ \frac{d}{dt} V_{out}(t) dt = -\frac{1}{RC} \int_0^+ V_s(\tau) d\tau ; \quad V_{out}(t) - V_{out}(0) = -\frac{1}{RC} \int_0^+ V_s(\tau) d\tau$

$$v_{out}(t) = v_{out}(0^-) - \frac{1}{RC} \int_0^+ v_s(\tau) d\tau \quad v_{out}(0^-) = -v_{cap}(0^-) = -V_0$$

2. An initial condition is not provided


$$v_{cap}(-\infty) = 0V$$

Integrate

between  $(-\infty)$  and  $(t)$

$$v_{out}(t) = v_{out}(-\infty) - \frac{1}{RC} \int_{-\infty}^+ v_s(\tau) d\tau = -\frac{1}{RC} \int_{-\infty}^+ v_s(\tau) d\tau$$

#### 4. Differentiator

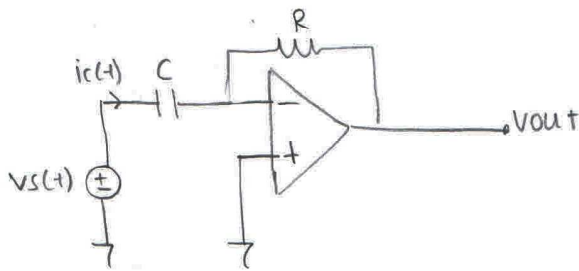

$$i_c(t) = C \frac{dV_C(t)}{dt} \rightarrow v_s(t)$$

$$v_{out} = -R i_c(t) = -RC \frac{dV_C(t)}{dt}$$


$$v_{out}(t) = -RC \frac{d}{dt} v_s(t)$$

#### Node Analysis with Op-Amps

Important notes: Never write a KCL equation at the output of the Op-Amp

$i_{out}(t)$  = Op-Amp's output current is an unknown, so KCL at  $v_{out}$  can't be written


1.

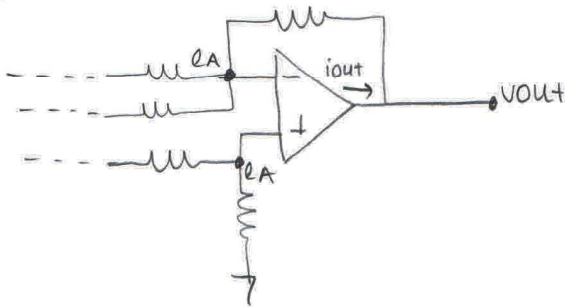


Linear region  $A \rightarrow \infty$

2. If  $A$  is finite and  $r_o$  is given

KCL at output can be written

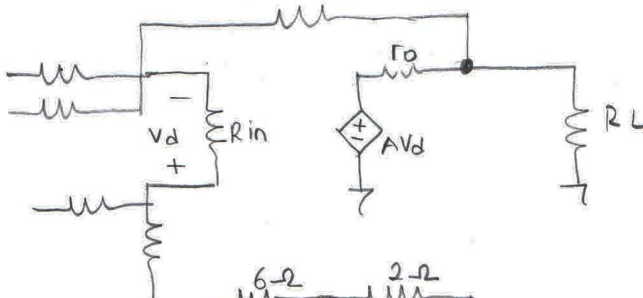

EX:

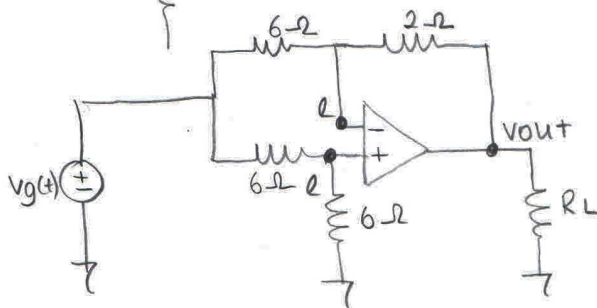

$r_{in}, r_o, A_{Vd}$  given


Find  $v_{out}$ . assume in linear region ( $A \rightarrow \infty$ )

$$KCL @ V_- = \frac{e - v_g(t)}{6} + \frac{e - v_{out}}{2} = 0$$



KCL at  $V_+$ ;  $\frac{e}{6} + \frac{e - Vg(t)}{6} = 0 \quad e = Vg(t)/2 \quad v_{out}(t) = 1/3 Vg(t)$

EX :

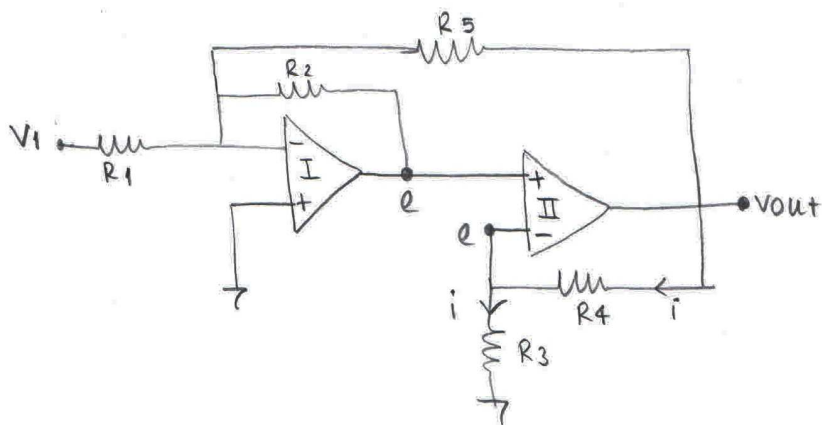

KCL @  $V_+$  of II :  $\frac{e}{R_3} + \frac{e - v_{out}}{R_4} = 0 \quad e = \frac{R_3}{R_3 + R_4} v_{out}$


KCL @  $V_+$  of I :  $-\frac{v_1}{R_1} - \frac{e}{R_2} - \frac{v_{out}}{R_5} = 0 \quad v_{out} = \frac{-R_5 R_2 (R_3 + R_4) v_1}{[R_2 (R_3 + R_4) + R_3 R_5] R_1}$

For the same problem; find input range (in volts) so that both Op-Amps guaranteed to be in linear region



Op-Amp I linear  $\rightarrow |e| < E_{sat} \quad |v_1| < Y$   
 Op-Amp II linear  $\rightarrow |v_{out}| < E_{sat} \quad |v_1| < X$  } number

That intersection of two intervals gives me the input range :  $|v_1| < \min(X, Y)$

EX: ZPS III, 4a;

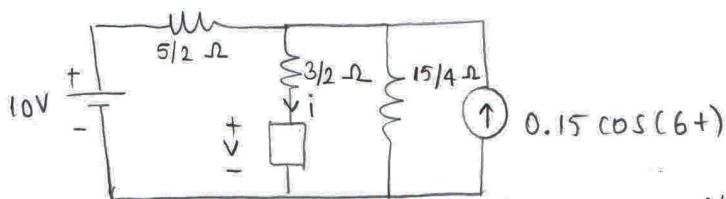

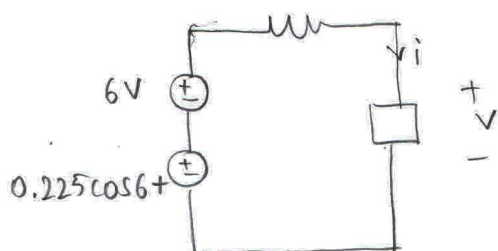
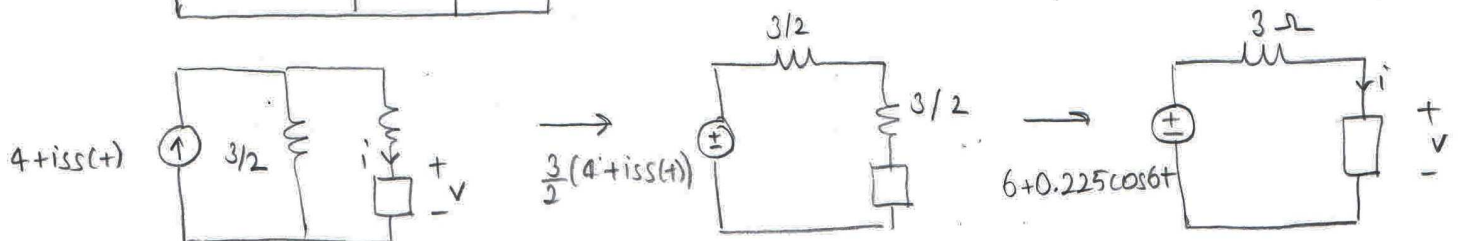
$$i = \begin{cases} \frac{1}{9} v^2 & v \geq 0 \\ 0 & \text{otherwise} \end{cases}$$





$-v_s(t) + 3i + v = 0$   
 $v = -6.3V$

AC component is sufficiently small in comparison the DC components



$$\frac{6}{0.225} \approx 30$$

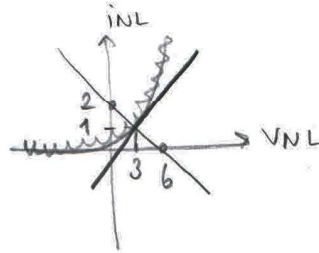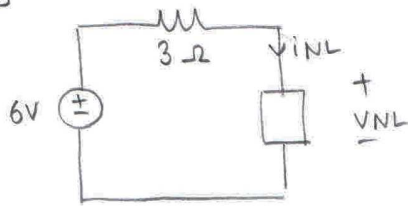

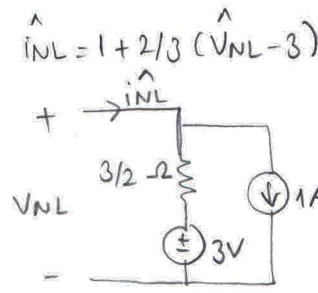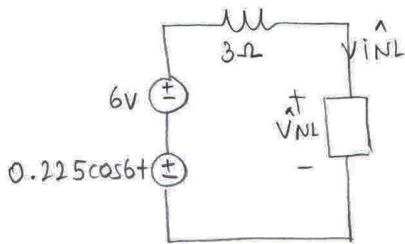slope = 2/3  
 $y = 1 + 2/3(x-3)$  eqn of this line  
 $i_N = 1 + 2/3(V_{NL}-3)$



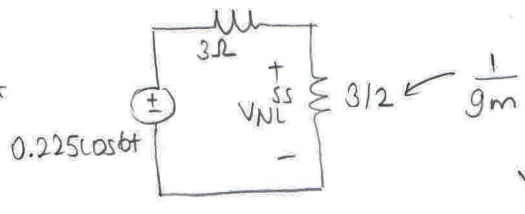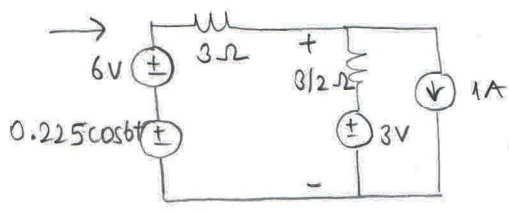
$$\hat{i}_{NL} = 1 + 2/3(\hat{V}_{NL}-3)$$



$$V_{NL}^{SS} = \frac{0.225 \cos 6t}{3}$$

slope at operating point  
 $\hat{V}_{NL} = \hat{V}_{NL}^{DC} + \hat{V}_{NL}^{SS}$

Op-Amps with nonlinear Components

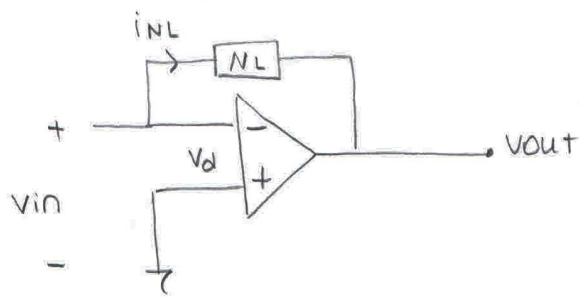


Assume Op-Amp in +sat  
 $V_{out} = E_{sat}$   $V_{NL} = V_- - E_{sat} \rightarrow V_{NL} < -E_{sat}$   
 $V_d > 0 \rightarrow V_- > 0 \rightarrow V_- < 0 \rightarrow V_{in} < 0$

Assume -Esat  
 $V_{out} = -E_{sat}$   $V_{NL} = V_- - (-E_{sat}); V_{NL} > E_{sat}$   
 $V_d < 0; V_- > 0 \rightarrow V_{in} > 0$

Assume linear region;

$$-E_{sat} < V_{out} < E_{sat} \quad V_{NL} = V_- - V_{out} \rightarrow -E_{sat} < V_{NL} < E_{sat}$$

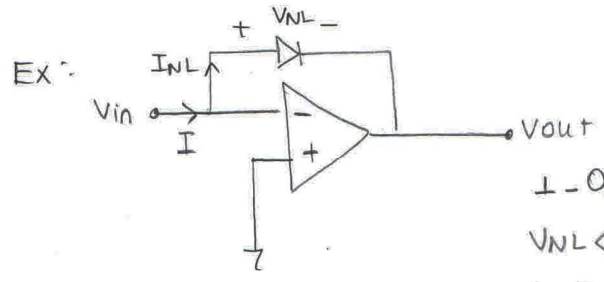
$$V_d = 0 \rightarrow V_- = 0 \quad V_{in} = 0$$



- a.) Find I vs Vin (input characteristic)
- b.) Find Vout vs Vin (transfer characteristic)

- 1- Op-Amp in +sat;  
 $V_{NL} < -E_{sat} \quad V_{in} < 0 \quad V_{out} = +E_{sat}$
- 2- Op-Amp in -sat;  $V_{NL} > E_{sat} \quad V_{in} > 0 \quad V_{out} = -E_{sat}$

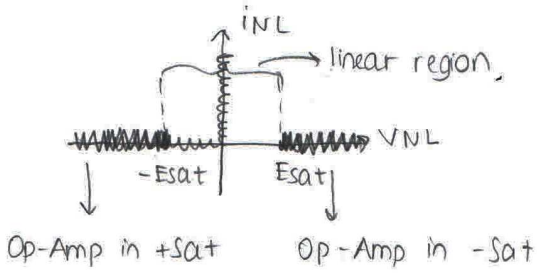Then, Op-Amp does not enter into -sat, since  $V_{NL}$  can not positive



3- Op-Amp in linear region?

$$-Esat \leq VNL \leq Esat$$

$$-Esat \leq Vout \leq Esat$$

$$Vin = 0 \quad 0 \leq VNL < Esat$$

$$-Esat \leq VNL \leq 0$$





only possible

$$VNL = 0$$

Diode: OFF

$$Vout = -VNL$$



Diode: ON

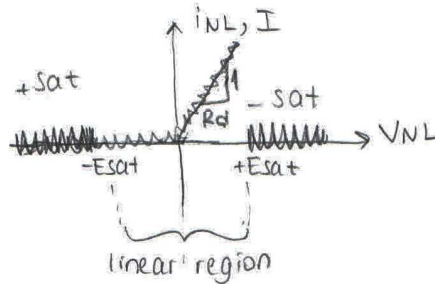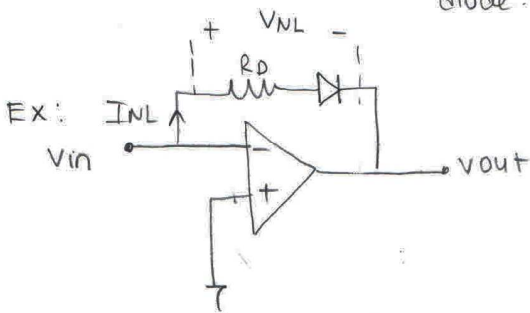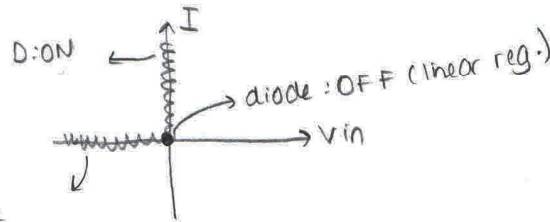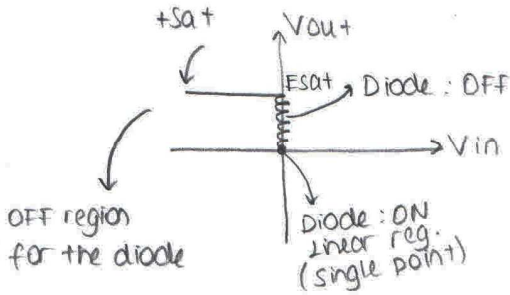

1- +sat;  $VNL < -Esat$

$$Vin < 0$$

$$Vout = +Esat$$

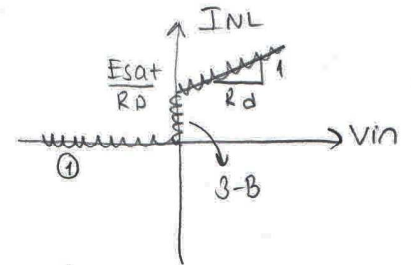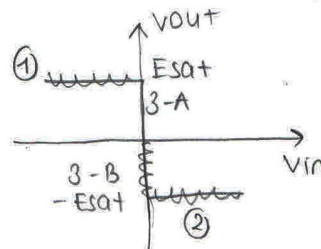

2- -sat;  $VNL > 0$ , diode: ON

$$Vout = -Esat$$

$$Vin > 0$$

3- In linear Region,

$$-Esat < VNL < +Esat$$

A-  $Vin = 0 \rightarrow -Esat < VNL < 0$


$$Vout = -VNL$$

$$0 < Vout < Esat$$

$I = 0$  since diode is OFF

B-  $0 < VNL < Esat$

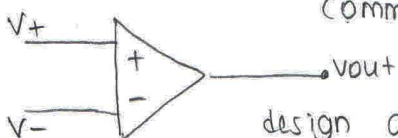-  $Esat < Vout < 0$  ;  $I = \frac{VNL}{RD}$  diode is ON [from  $(INL, VNL)$ ]



Common Mode Rejection Ratio

In linear region; "A" open loop gain can be due to design different for + and - terminals. So we have  $A+$  and  $A-$

by definition  
 Ideal case  $A_+ = A_- \triangleq A$

Practical case  $V_{out} = A_+ V_+ - A_- V_-$   
 $V_{common} \triangleq V_c = \frac{V_+ + V_-}{2}$   
 $V_d \triangleq V_+ - V_-$

$$\left. \begin{aligned} V_+ &= V_c + V_d/2 \\ V_- &= V_c - V_d/2 \end{aligned} \right\}$$


$$V_{out} = A_+ V_+ - A_- V_- = A_+ (V_c + V_d/2) - A_- (V_c - V_d/2)$$

$$= \underbrace{(A_+ - A_-)}_{A_c} V_c + \underbrace{\frac{A_+ + A_-}{2}}_{A_d} V_d$$

Ideally  $A_+ = A_- = A$   
 $V_{out} = A V_d$

$20 \log_{10} CMRR \triangleq (CMRR)_{dB}$  since  $CMRR \triangleq \left| \frac{A_d}{A_c} \right| \rightarrow$  Ideally  $CMRR \rightarrow \infty$   
 linear scale

Op-Amps with Positive Feedback

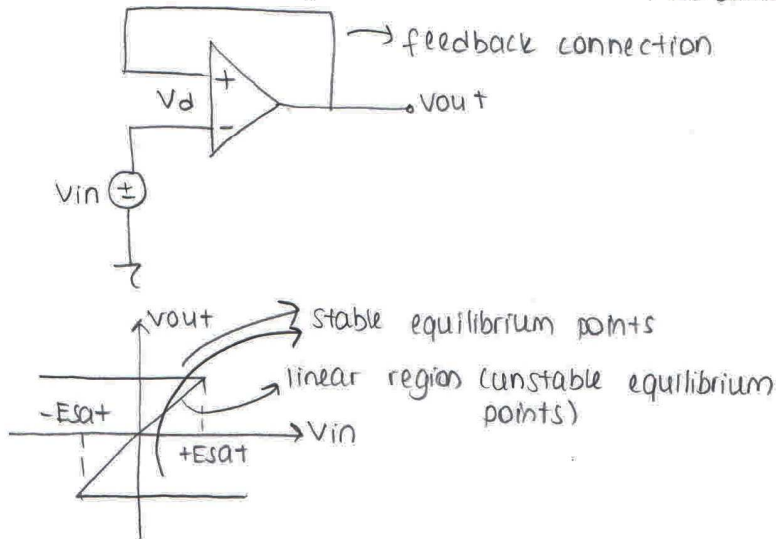

1 - Op-Amp in +sat;

$V_d > 0 \rightarrow V_{in} < E_{sat}$

$V_{out} = +E_{sat}$

$V_d = V_{out} - V_{in}$

2 - Op-Amp in -sat;


$V_d < 0$

$V_{out} = -E_{sat}$

$V_{in} > -E_{sat}$


Wave forms

1 - Unit-step function

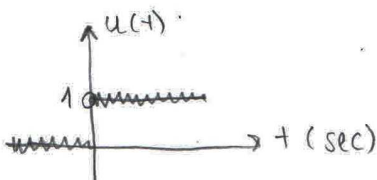

$$u(t) = \begin{cases} 1 & t > 0 \\ 0 & t < 0 \end{cases}$$


2 - Ramp function

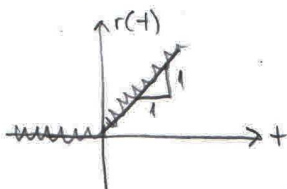


$$r(t) = \begin{cases} t & t > 0 \\ 0 & t < 0 \end{cases}$$

Superposition of  $u(t)$  and  $r(t)$



Ex:  $f(t) = 5u(t) - 5u(t-2)$

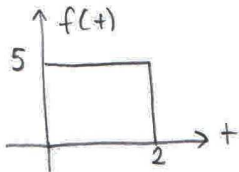

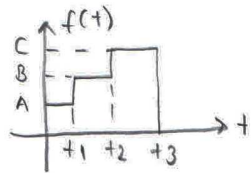Ex:  $f(t) = Au(t) + (B-A)u(t-t_1) + (C-B)u(t-t_2) - C(t-t_3)$





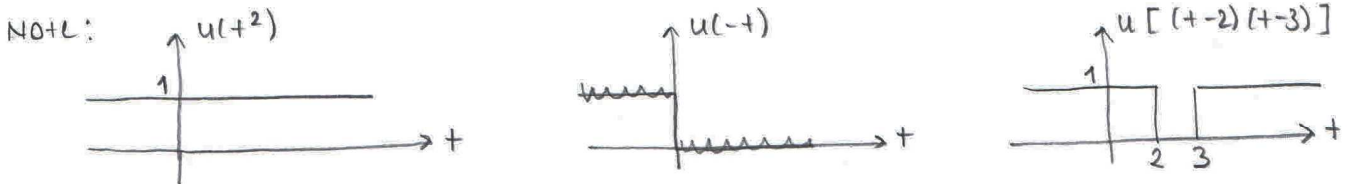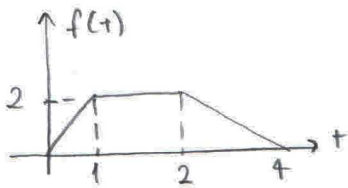Ex:  $f(t) = 2r(t) - 2r(t-1) - r(t-2) + r(t-4)$



Impulse Function (Generalized Function Distribution)

$\delta(t)$  = Impulse function

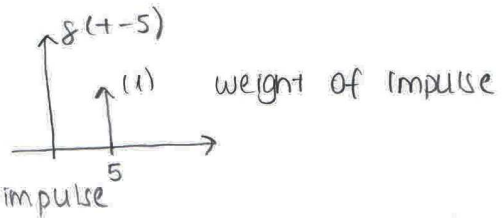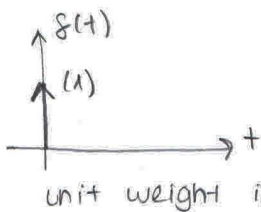

Properties:


1.  $\int_0^+ \delta(t) dt = 1$

2.  $u(t) = \int_{-\infty}^t \delta(z) dz$


3.  $\delta(t) = \frac{d}{dt} u(t)$

4.  $\int_0^+ f(z) \delta(z) dz = f(0) \int_0^+ \delta(z) dz = f(0) \cdot 1 = f(0)$

Summary:

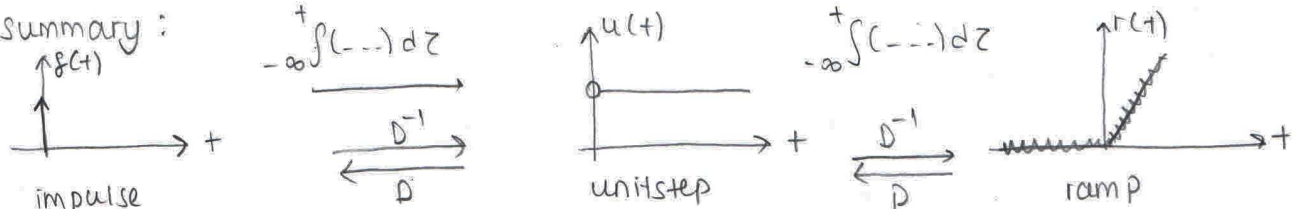

Definition of Impulse

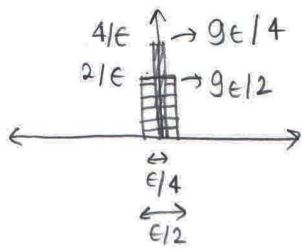

$$\int_{-\infty}^{\infty} g_{\epsilon}(t) dt = 1$$

$$g_{\epsilon}(t) \xrightarrow{\epsilon \rightarrow 0} \delta(t)$$

$$\int_{-\infty}^{\infty} g_{\epsilon/2}(t) dt = 1$$

$$\int_{-\infty}^{\infty} g_{\epsilon/4}(t) dt = 1$$

So property 1 follows the definition  $\int_0^t f(t) dt = 1$

### Sinusoidal Functions


$$f(t) = A \cos(\omega t + \phi)$$

A: amplitude

$\omega$ : radial frequency (rad/sec)

t: second


$\phi$ : phase

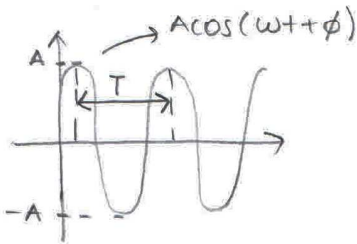

$$\omega = 2\pi f$$

f: frequency (1/sec, Hz): number of oscillations per second

T: 1/f time for one oscillation.

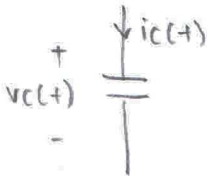

capacitors

$$Q(t) = C V(t)$$

C: capacitance (Farad)

$V(t)$ : voltage applied to capacitor

$Q(t)$ : charge stored in the capacitor

If capacitance is time varying;  $Q(t) = C(t) V(t)$

$$* \text{ If } Q(t) = C V(t); \quad \frac{d}{dt} Q(t) = i(t) = C \frac{d}{dt} V(t)$$

$$* \text{ If } Q(t) = C(t) V(t); \quad \frac{d}{dt} Q(t) = i(t) = \left[ \frac{d}{dt} C(t) \right] V(t) + C(t) \frac{d}{dt} V(t)$$

$$* P_{\text{cap}}(t) = V_c(t) i_c(t) \text{ Watts}$$

$$\text{Energy work done by capacitor} \quad \int_{-\infty}^t P_{\text{cap}}(\tau) d\tau = \Delta E$$

$$= \int_{-\infty}^t V_c(\tau) C \frac{dV_c(\tau)}{d\tau} d\tau = C \int_{-\infty}^t V_c(\tau) dV_c(\tau) = \frac{C}{2} [V_c(\tau)]_{-\infty}^t = \frac{C}{2} [V_c^2(t) - V_c^2(-\infty)]$$

$$= \Delta E$$

Assume that at  $t \rightarrow -\infty$  capacitor does not have any energy and  $V_{cap}(-\infty) = 0V$

$$E(t) = \frac{1}{2} C V_c^2(t)$$

$$* i_c(t) = C \frac{d}{dt} V_c(t)$$

$$\int_{-\infty}^{t_0} i_c(\tau) d\tau = C \int_{-\infty}^{t_0} \frac{dV_c(\tau)}{d\tau} d\tau = C [V_c(t_0) - V_c(-\infty)]$$

$$V_c(t_0) = \frac{1}{C} \int_{-\infty}^{t_0} i_c(\tau) d\tau + V_c(-\infty)$$

$$V_c(t_1) = \frac{1}{C} \int_{-\infty}^{t_1} i_c(\tau) d\tau = \frac{1}{C} \int_{-\infty}^{t_0} i_c(\tau) d\tau + \frac{1}{C} \int_{t_0}^{t_1} i_c(\tau) d\tau$$

$$V_c(t_1) = V_c(t_0) + \frac{1}{C} \int_{t_0}^{t_1} i_c(\tau) d\tau$$

Important Note:  $V_c(t)$ , capacitor voltage is a continuous function of time (unless its current contain impulses)

To show this note:

$$V_c(t+\epsilon) = V_c(t) + \frac{1}{C} \int_t^{t+\epsilon} i_c(\tau) d\tau$$

$$\text{as } \epsilon \rightarrow 0 \quad \lim_{\epsilon \rightarrow 0} V_c(t+\epsilon) = V_c(t) + \frac{1}{C} \lim_{\epsilon \rightarrow 0} \int_t^{t+\epsilon} i_c(\tau) d\tau$$



$$V_c(t^+) = V_c(t) \quad \text{continuous}$$

$$* D = \frac{d}{dt} \quad D^{-1} = \int_{-\infty}^t$$

$$V_c(t) = V_c(t_0) + \frac{1}{C} \int_{t_0}^t i_c(\tau) d\tau \quad t > t_0$$

↑  
initial condition

Initial Condition Models for Capacitor

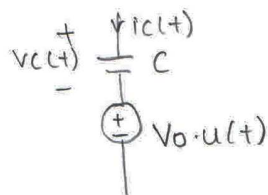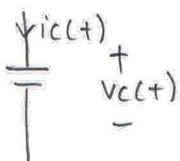


→ empty capacitor  
zero volts at  $t=0$   
zero energy

$$V_c(0^-) = V_0$$

$$V_c(t) = V_0 + \frac{1}{C} \int_0^t i_c(\tau) d\tau \quad t > 0$$
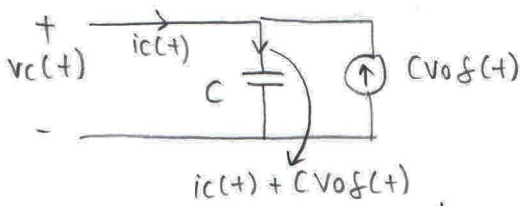
$$v_c(t) = v_c^{\text{empty}}(t) + V_0 u(t) = V_0 + \frac{1}{C} \int_0^+ i_c(z) dz = \frac{1}{C} \int_0^+ i(z) dz + V_0 \quad \text{for } t > 0$$




$$v_c^{\text{empty}}(t) = v_c(0^-) + \frac{1}{C} \int_0^+ i_c^{\text{empty}}(z) dz = \frac{1}{C} \int_0^+ i(z) dz + C \underbrace{\frac{V_0}{C} \int_0^+ \delta(z) dz}_1 \quad t > 0$$

$$= V_0 + \frac{1}{C} \int_0^+ i_c(z) dz$$

Series and Parallel Connection

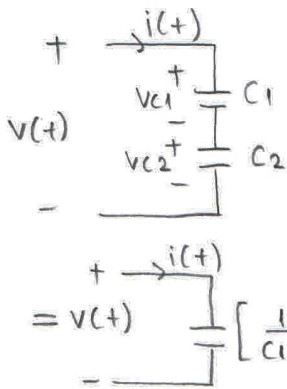
$C_1$  and  $C_2$  have any energy at  $t=0$



$$v(t) = v_{c1}(t) + v_{c2}(t) = \frac{1}{C_1} \int_0^+ i_{c1}(z) dz + \frac{1}{C_2} \int_0^+ i_{c2}(z) dz$$

$$= \left[ \frac{1}{C_1} + \frac{1}{C_2} \right] \int_0^+ i_c(z) dz$$


Parallel

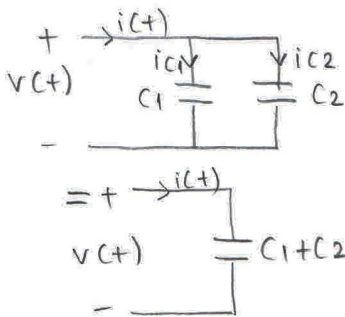

$$i(t) = i_{c1}(t) + i_{c2}(t)$$

$$= C_1 \frac{dv(t)}{dt} + C_2 \frac{dv(t)}{dt} = (C_1 + C_2) \frac{dv(t)}{dt}$$

Voltage Division for capacitors

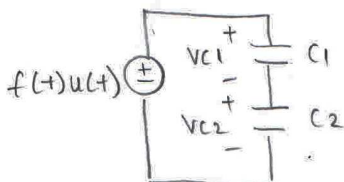

$$v_{c1}(0) = v_{c2}(0) = 0$$

they are connected in series


$$i(t) = \frac{C_1 C_2}{C_1 + C_2} \frac{d}{dt} \{ f(t) u(t) \} = \frac{C_1 C_2}{C_1 + C_2} \left[ \frac{df(t)}{dt} \cdot u(t) + \frac{du(t)}{dt} \cdot f(t) \right]$$

$$v_{c1} = \frac{1}{C_1} \int_0^+ i(z) dz = \frac{C_2}{C_1 + C_2} \left[ \int_0^+ f'(z) u(z) dz + f(0) \int_0^+ \delta(z) dz \right]$$


$$= \frac{C_2}{C_1 + C_2} [f(t) - f(0) + f(0) - 1]$$
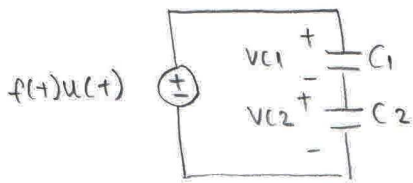
$$= \frac{C_2}{C_1 + C_2} f(t) = \frac{1/C_1}{1/C_1 + 1/C_2} f(t)$$






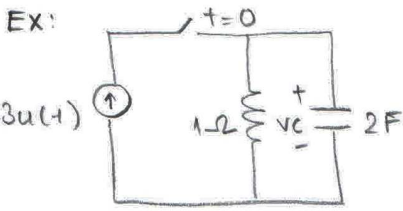
$v_{C1}$  and  $v_{C2}$  are proportional with  $\frac{1/C1}{1/C1+1/C2}$  and  $\frac{1/C2}{1/C1+1/C2}$



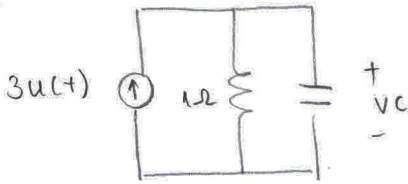$v_C(0^-) = 0$   
Find  $t=0^+$  solution  
what happened just after switching?




at  $t=0^-$

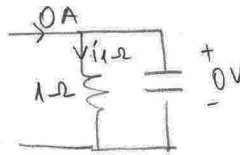

$i_{1\Omega}(0^-) = 0/1 = 0A$

at  $t=0^+$

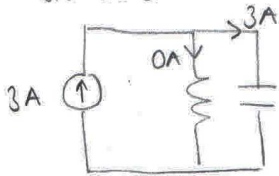


$v_C(0^-) = v_C(0^+) = 0$  [voltage is continuous if no impulses in the system]

$i_C(0^+) = 3A$


$$\left. \frac{dv_C(t)}{dt} \right|_{t=0^+}$$

$$2v_C'(0^+) = 3$$

$$v_C'(0^+) = 3/2$$

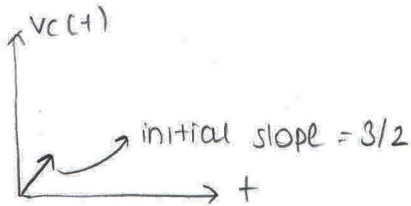

Ex:

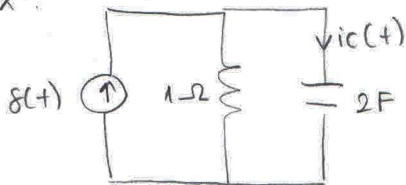


$v_C(0^-) = 0V$

at  $t=0^-$

$0^- < t < 0^+$


The same result of previous example

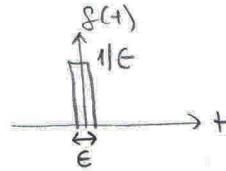

$$i_C(t) = 8(t)$$

$$v_C(0^+) = \frac{1}{2} \int_0^+ i_C(\tau) d\tau = 1/2 V$$

At  $t=0^+$

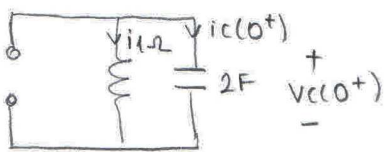


$$v_C(0^+) = 1/2 V$$


$$i_{1\Omega}(0^+) = 1/2 A$$

$$i_C(0^+) = -1/2 A = 2 v_C'(0^+);$$


$$v_C'(0^+) = -1/4$$

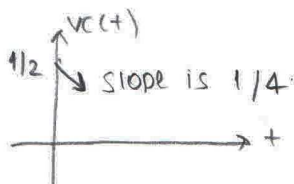

Inductors

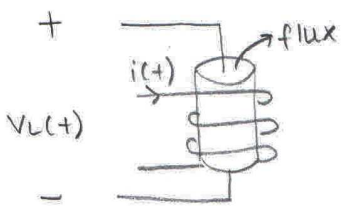

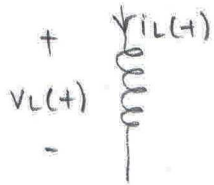$\phi(t) = L(t) i(t)$  similar ( $\phi = CV$ )  
 $v_L(t) = \frac{d\phi(t)}{dt} = \frac{d}{dt} \{ L(t) i(t) \}$




for LTI inductors  $v_L(t) = L \frac{d}{dt} i_L(t)$

$\int_{-\infty}^t v_L(\tau) d\tau = L \int_{-\infty}^t \frac{d}{d\tau} i_L(\tau) d\tau = L [i_L(t) - i_L(-\infty)]$


$i_L(t) = i_L(-\infty) + \frac{1}{L} \int_{-\infty}^t v_L(\tau) d\tau$  integral form

$v_L(t) = L \frac{di_L(t)}{dt}$  differential form


initial condition models

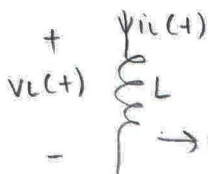

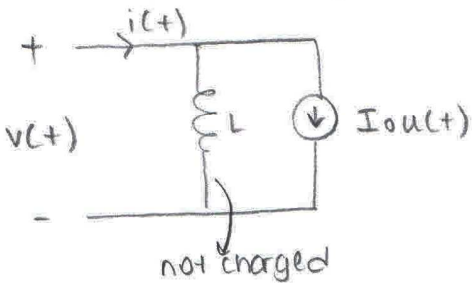$i_L(0^-) = I_0 \rightarrow i_L(t) = i_L(0^-) + \frac{1}{L} \int_{0^-}^t v_L(\tau) d\tau$  for  $t > 0$





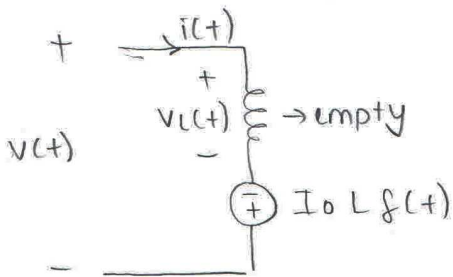$i(t) = I_0 + \frac{1}{L} \int_{0^-}^t v_L(\tau) d\tau \quad t > 0$



$v_L(t) = v(t) + I_0 L f(t)$   
 $i_L(t) = \frac{1}{L} \int_{0^-}^t [v_L(\tau) + I_0 L f(\tau)] d\tau$   
 $= I_0 + \frac{1}{L} \int_{0^-}^t v(\tau) d\tau \quad t > 0$

Inductors in Series and Parallel

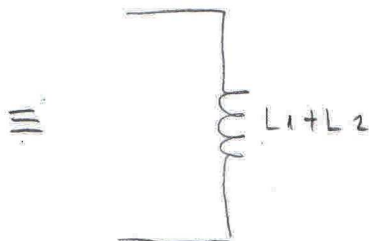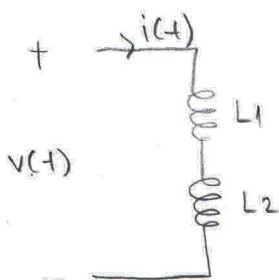



connected in series

$$V_{L1}(t) = L_1 \frac{di_1(t)}{dt}$$

$$V_{L2}(t) = L_2 \frac{di_2(t)}{dt}$$

$$V(t) = V_{L1}(t) + V_{L2}(t) = (L_1 + L_2) \frac{di(t)}{dt}$$

parallel

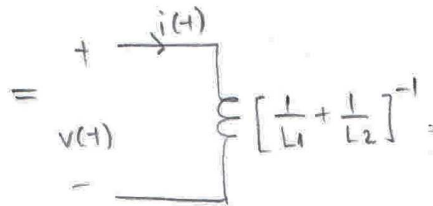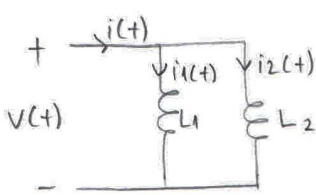

$$V(t) = L_1 \frac{di_1(t)}{dt} = L_2 \frac{di_2(t)}{dt}$$

$$i(t) = i_1(t) + i_2(t)$$

$$i_1 = \frac{1}{L_1} \int_0^+ v(z) dz$$

$$i_2 = \frac{1}{L_2} \int_0^+ v(z) dz$$

$$i = i_1 + i_2 = \left[ \frac{1}{L_1} + \frac{1}{L_2} \right] \int_0^+ v(z) dz = \frac{1}{L_{eq}} \int_0^+ v(z) dz$$

then  $L_{eq} = \left[ \frac{1}{L_1} + \frac{1}{L_2} \right]^{-1}$


$$* D^{-1} \{ v_L(t) \} = L D^{-1} D i_L(t)$$

$$\int_{-\infty}^+ v_L(z) dz = L i_L(t)$$

$$i_L(t) = \underbrace{\frac{1}{L} \int_{-\infty}^+ v_L(z) dz}_{i_L(t_0)} + \frac{1}{L} \int_{t_0}^+ v_L(z) dz$$


$$i_L(t) = i_L(t_0) + \frac{1}{L} \int_{t_0}^+ v_L(z) dz$$

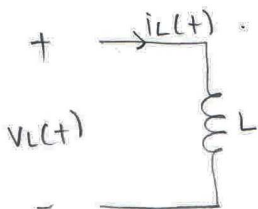Assume no initial energy for  $L_1, L_2$   
 $\frac{1}{2} L I_L^2(t) = E$ ;  $E(t) = 0$ ;  $i_L(t) = 0$




$$i_L(0^-) = I_0 \text{ A}$$
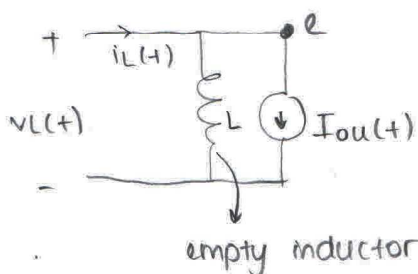
$$i_L(t) = i_L(0^-) + \frac{1}{L} \int_0^+ v_L(z) dz$$



$$i_L^{empty}(t) = \frac{1}{L} \int_0^+ v_L(z) dz \quad t > 0 \text{ then}$$
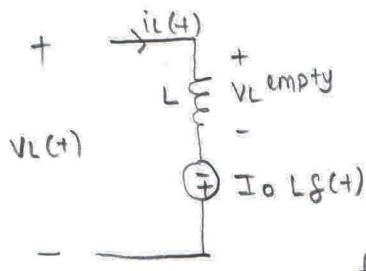
$$KCL \text{ at } a; \quad i_L(t) = i_L^{empty}(t) + I_{ou}(t) \\ = \frac{1}{L} \int_0^+ v_L(z) dz + I_0 u(t)$$



$$v_L^{empty}(t) = v_L(t) + I_0 L f(t)$$


$$i_L(t) = \frac{1}{L} \int_0^+ [v_L(\tau) + I_0 L f(\tau)] d\tau$$

empty inductor's voltage


for  $t > 0$   $i_L(t) = \frac{I_0 L}{L} \int_0^+ f(\tau) d\tau + \frac{1}{L} \int_0^+ v_L(\tau) d\tau$

NOTE: Inductor's current is a continuous function of time unless there is an impulse in the circuit or there is a pathological connection.

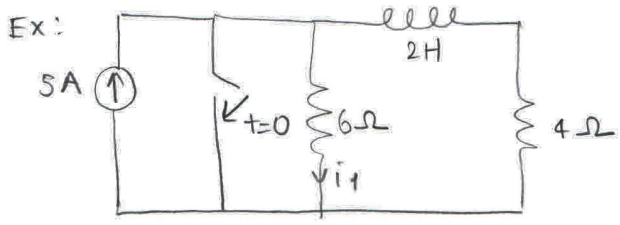
$$i_L(t_0^+) = i_L(t_0) + \frac{1}{L} \int_{t_0}^{t_0^+} v_L(\tau) d\tau \quad i_L(t_0^+) = i_L(t_0)$$




$i_1(0^-) = 2A$   
 Find  $i_L(0^+)$ ,  $i_1(0^+)$ ,  $\frac{d}{dt} i_L(t) \Big|_{t=0^+}$

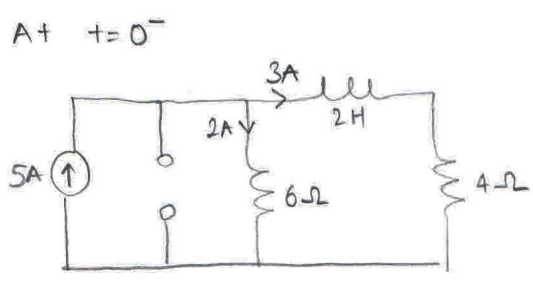


$i_L(0^-) = 3A$

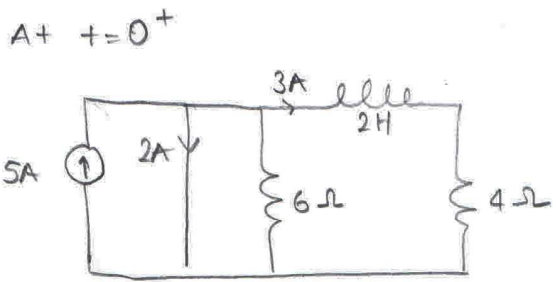

$i_1(0^+) = 0$   
 $v_L(0^+) = -12V = L \frac{di(t)}{dt}$   
 $\frac{di(t)}{dt} \Big|_{t=0^+} = -6$

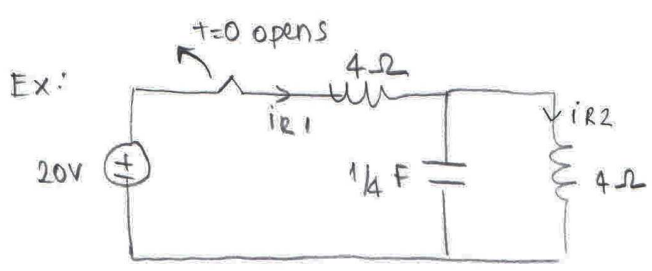

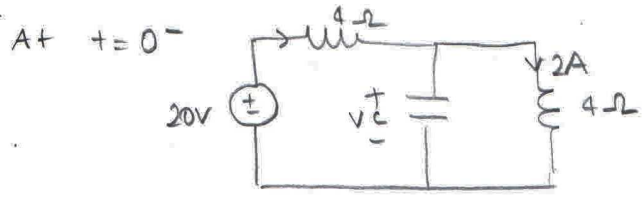$i_{r2}(0^-) = 2A$   
 Find  $Q(0^-)$  and  $Q(0^+)$   
 $i_{r2}(0^-)$  and  $i_{r1}(0^+)$   
 $i_C(0^-)$ ,  $i_C(0^+)$ ,  $v_C(0^+)$




$v_C(0^-) = 8V$   
 $Q(0^-) = 2 C$   
 $i_{r1}(0^-) = 3A$   
 $i_C(0^-) = 1A$

Capacitors: Voltage is continuous

Inductors: Current is continuous

At  $t = 0^+$

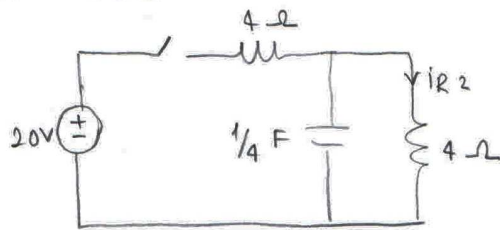


$$v_C(0^+) = 8V \quad Q(0^+) = 2C$$

$$i_{R2}(0^+) = 8/4 = 2A \quad i_R(0^+) = 0A$$

$$i_C(0^+) = -2A = C \dot{v}_C(t)$$

$$\dot{v}_C(t) = -8$$

Some Pathological Circuits

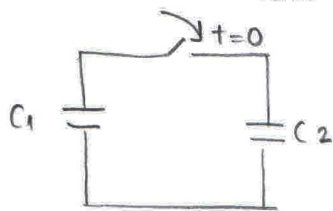


$$v_{C1}(0^-) = V1 \quad v_{C2}(0^-) = V2$$

$$Q_{C1}(0^-) = C1V1 \quad Q_{C2}(0^-) = C2V2$$

$$Q^{total}(0^-) = C1V1 + C2V2$$

$$Q^{total}(0^+) = C1V1 + C2V2$$

At  $t = 0^+$ ; switch is closed

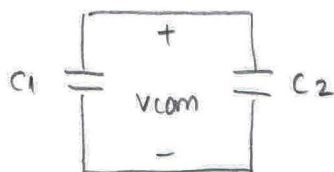

After switching the capacitance changes to  $C1 // C2 = C1 + C2$

$$Q_1(0^+) = C1 v_{com}$$

$$Q_2(0^+) = C2 v_{com}$$

$$Q(0^+) = Q_1 + Q_2 = v_{com} (C1 + C2)$$

$$v_{com}(0^+) = \frac{C1V1 + C2V2}{C1 + C2}$$


Energy at  $t = 0^-$ ;  $E_{total}(0^-) = \frac{1}{2} C1V1^2 + \frac{1}{2} C2V2^2$

$$E_{total}(0^+) = \frac{1}{2} (C1 + C2) \frac{(C1V1 + C2V2)^2}{(C1 + C2)^2}$$

$$E_{total}(0^-) > E_{total}(0^+)$$

In EE201, we say that energy is lost during switching (More on this provided EM courses)



At  $t = 0^-$

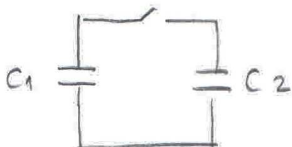


$$v_{C1}(0^-) = V1$$

$$v_{C2}(0^-) = V2$$

At  $t = 0^+$

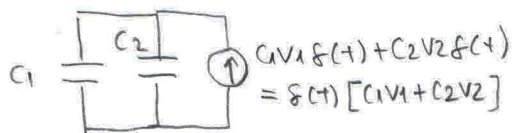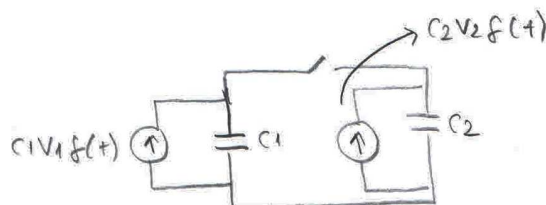

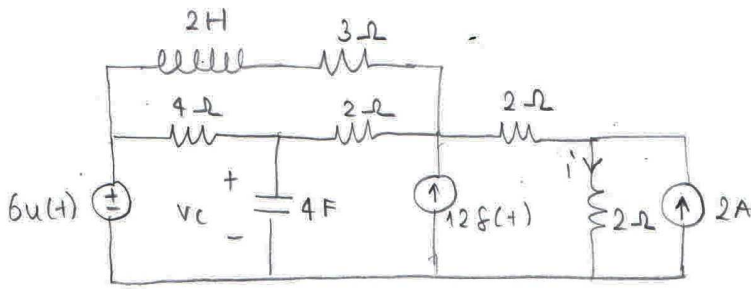
$$v_{eq}(0^+) = \frac{C1V1 + C2V2}{C1 + C2}$$




$v_C(0^-) = 10V$   
 $i_L(0^-) = 5A$   
 Find  $v_C(0^+)$   $i_L(0^+)$

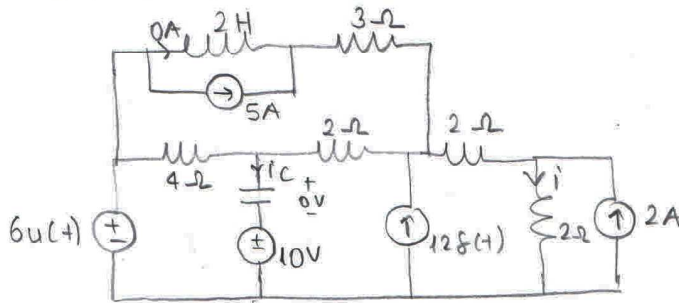$0^- < t < 0^+$  during the application of impulse  
 $0 - \epsilon < t < 0 + \epsilon$



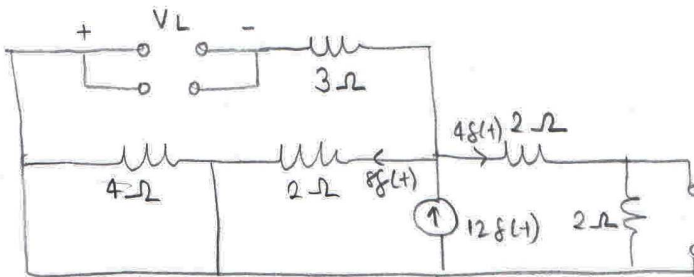
I'd like to find  $i_C(t)$  &  $v_L(t)$   
 during  $0^- < t < 0^+$   
 $v_C(0^+) = v_C(0^-) + \frac{1}{C} \int_0^+ i_C(z) dz$   
 $i_L(0^+) = i_L(0^-) + \frac{1}{L} \int_0^+ v_L(z) dz$



then  $i_{C1} = 8\delta(t)$   
 $v_{L1} = -16\delta(t)$   
 Then  $v_C(0^+) = 10 + \frac{1}{C} \int_0^+ (8\delta(t') + k) dt'$   
 $= 12V$

$i_L(0^+) = 5 + \frac{1}{L} \int_0^+ (-16\delta(t') + k) dt' = -3A$


Mutual Inductor

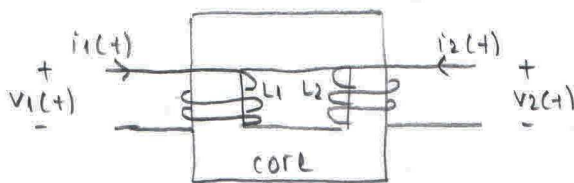

$$\begin{bmatrix} \phi_1(t) \\ \phi_2(t) \end{bmatrix} = \begin{bmatrix} L_1 & M \\ M & L_2 \end{bmatrix} \begin{bmatrix} i_1(t) \\ i_2(t) \end{bmatrix}$$


Special cases:

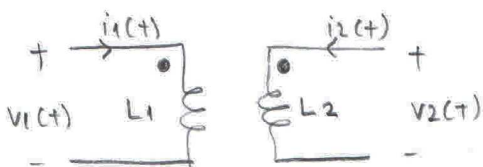- $M=0 \rightarrow L_1, L_2$  two regular inductance, (only self inductance)
- $M = \sqrt{L_1 L_2}$   $k = \frac{M}{\sqrt{L_1 L_2}} = 1$  coupling coefficient = 1 No loss ideal transformer



with dot convention following terminal equation results
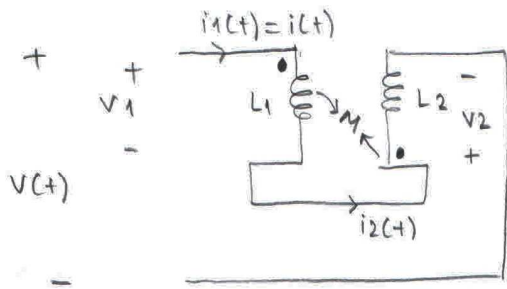
$$\begin{bmatrix} v_1(t) \\ v_2(t) \end{bmatrix} = \begin{bmatrix} L_1 & M \\ M & L_2 \end{bmatrix} \begin{bmatrix} d/dt i_1(t) \\ d/dt i_2(t) \end{bmatrix}$$



$$\begin{bmatrix} v_1(t) \\ v_2(t) \end{bmatrix} = \begin{bmatrix} L_1 & M \\ M & L_2 \end{bmatrix} \begin{bmatrix} di_1(t)/dt \\ di_2(t)/dt \end{bmatrix}$$

$$\begin{bmatrix} i_1(t) = i_1(t) \\ i_1(t) = i_2(t) \end{bmatrix} \Rightarrow i_1(t) = i_2(t)$$

$$v_1(t) + v_2(t) = v(t)$$

$$\left. \begin{aligned} v_1(t) &= L_1 di/dt + M di/dt \\ v_2(t) &= L_2 di/dt + M di/dt \end{aligned} \right\} v(t) = di/dt (L_1 + L_2 + 2M)$$

### First Order Circuits

$(D + \gamma)x(t) = f(t)$  satisfies I.C. and differential equation for  $t > 0$

$f(t)$ : forcing term - external input


$x(t)$ : scalar unknown function  $x(0^-) = x_0$  initial condition

$D$ :  $d/dt$

### Types of solutions

1. Homogenous - Particular solution
2. zero input - zero state solution
3. Transient - Steady State solution
4. Complete solution

### First Order RC, RL Circuits

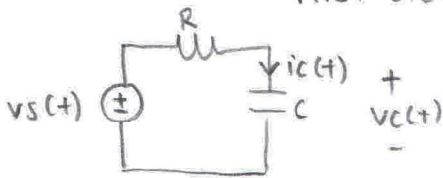


$$-v_S(t) + i_C(t) \cdot R + v_C(t) = 0$$

$$RC \dot{v}_C(t) + v_C(t) = v_S(t)$$

$$\left(D + \frac{1}{RC}\right) v_C(t) = \frac{v_S(t)}{RC} \quad v_C(0^-) = V_0$$

↓ dual

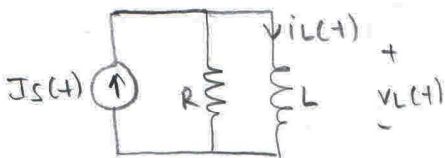

$$\frac{v_L}{R} + i_L - i_S(t) = 0$$

$$\frac{L}{R} \dot{i}_L(t) + i_L(t) = i_S(t)$$

$$\left(D + \frac{R}{L}\right) i_L(t) = \frac{R}{L} i_S(t) \quad i_L(0^-) = I_0$$

### 1- Homogenous - Particular solutions

$$\left(D + \frac{1}{RC}\right) v_C(t) = \frac{v_S(t)}{RC} \quad v_C(0^-) = V_0$$

homogenous soh.

$$\left(D + \frac{1}{RC}\right) v_C^h(t) = 0$$

particular soh.

$$\left(D + \frac{1}{RC}\right) v_C^p(t) = \frac{v_S(t)}{RC}$$

CCDE (Constant Coefficient Differential Equation)

$$v_c^h(t) = a e^{\lambda t} \quad a, \lambda: \text{generic unknowns}$$

Substitute  $v_c^h(t)$  in D.E.  $(D + \frac{1}{RC}) a e^{\lambda t} = 0 \rightarrow (D + \frac{1}{RC}) a = 0$

Then  $\rightarrow a = 0$ ,  $v_c^h(t) = 0$  trivial and not useful solution

$$\rightarrow \lambda = -\frac{1}{RC} \quad v_c^h(t) = d e^{-t/RC} \quad \text{solution is valid for any } d \in \mathbb{R}$$

Particular Solution

1.  $v_s(t) = B u(t) \rightarrow (D + \frac{1}{RC}) v_c(t) = \frac{v_s(t)}{RC}$  case 1



$$(D + \frac{1}{RC}) v_c(t) = \frac{B}{RC} \quad t > 0$$

Guess  $v_c^p(t) = A \rightarrow (D + \frac{1}{RC}) A = B/RC \quad t > 0$  then  $A = B$

$$v_c^p(t) = B \rightarrow \text{particular solution } v_s(t) = B u(t) \rightarrow v_c(t) \stackrel{\text{complete}}{=} \underbrace{d e^{-t/RC}}_{v_c^h(t)} + \underbrace{B}_{v_c^p(t)} \quad t > 0$$

$d$ : unknown: will be found using initial condition

2. Case 2

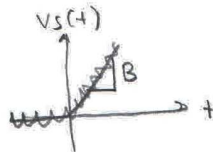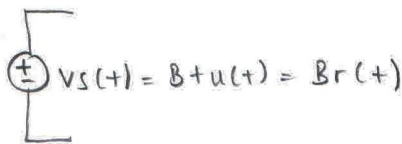

$$(D + \frac{1}{RC}) v_c^p(t) = \frac{B + t}{RC} \quad t > 0$$

Guess  $v_c^p(t) = A_0 + A_1 t + A_2 t^2 \quad (D + \frac{1}{RC}) v_c^p(t) = \frac{B + t}{RC} \quad t > 0$


$$A_1 + \frac{A_0 + A_1 t}{RC} = \frac{B + t}{RC} \quad A_1 = B \quad A_0 = -BRC \quad v_c^p(t) = -BRC + Bt \quad t > 0$$

$$v_c^{\text{complete}}(t) = d e^{-t/RC} - BRC + Bt \quad t > 0$$

$d$  is adjusted so that  $V_0 = v_c(0^-) = v_c(0^+)$


2. zero input / zero state solutions

zero input solution

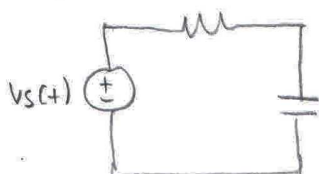

$$v_c(0^-) = V_0$$

$v_s(t) > 0$   
zero input

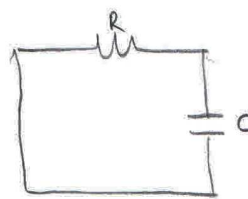

$$v_c(0^-) = V_0$$

$$v_c(0^-) = V_0$$


$$(D + \frac{1}{RC}) v_c^{zi}(t) = 0 \quad v_c^{zi}(0) = V_0$$

$$v_c^{zi}(t) = d e^{-t/RC} \quad t > 0$$

$$\boxed{v_c(0^-) = v_c(0^+) = V_0}$$

$$\boxed{v_c^{zi}(t) = V_0 e^{-t/RC}}$$



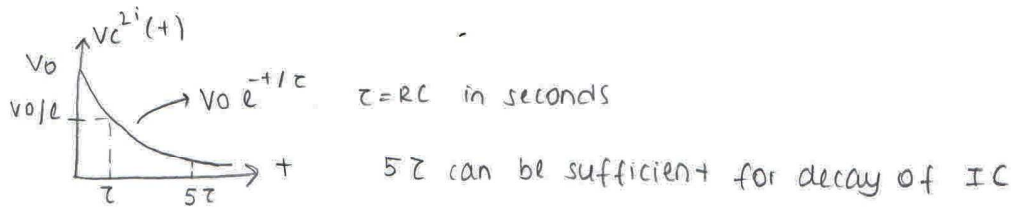

$$\frac{V}{I} \cdot \frac{Q}{V} = \frac{Q}{\Delta t} = \Delta t \text{ seconds} \quad \Omega \cdot F = \text{sec}$$

zero state solutions

State concept, states describe the dynamics system completely and sufficient to determine the output from input and the states

Circuit theory states are  $V_{cap}(t)$  and  $I_L(t)$

$V_c(0^-), I_L(0^-)$  external input  $f(0^-) = f_0$

$V_c(0^+), I_L(0^+)$  can be found

$$\left(D + \frac{1}{RC}\right) V_c^{zs}(t) = \frac{V_s(t)}{RC} \quad V_{cap}(0^-) = 0 \text{ volts}$$

Case 1:  $V_s(t) = B u(t)$

$$\left(D + \frac{1}{RC}\right) V_c^{zs}(t) = \frac{B}{RC} \quad t > 0 \quad V_c^{zs}(0^-) = 0 \quad V_c^{zs}(t) = d e^{-t/RC} + B \text{ from earlier results}$$

$$V_c^{zs}(0^-) = V_c^{zs}(0^+) = 0 \quad d = -B$$

$$V_c^{zs}(t) = B(1 - e^{-t/RC}) \quad t > 0$$

$$V_c^{com}(t) = V_c^{zi}(t) + V_c^{zs}(t) = V_0 e^{-t/RC} + B(1 - e^{-t/RC}) \quad t > 0$$

$\downarrow$   
 zero input

Case 2:  $V_s(t) = B \delta(t)$


$$\left(D + \frac{1}{RC}\right) V_c^{zs}(t) = \frac{B}{RC} \delta(t) \quad t > 0 \quad V_c^{zs}(0^-) = 0$$

$$V_c^{zs}(t) = BRC e^{-t/RC} + B + -BRC$$


$$V_c^{comp}(t) = \underbrace{V_0 e^{-t/RC}}_{\text{due to I.C.}} + \underbrace{(BRC e^{-t/RC} + B + -BRC)}_{\text{zero state}}$$

Sketching the curves


Case 1:

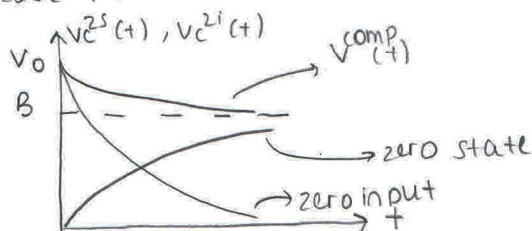

Case 2:

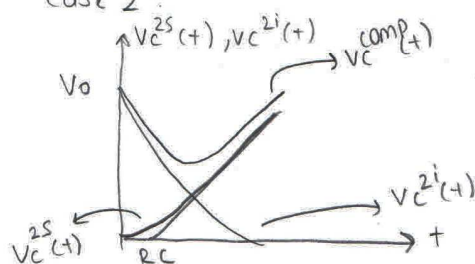


### 3: Transient and steady state

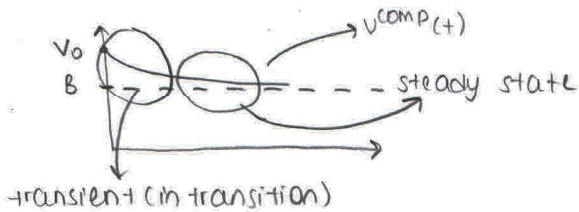

In transient part, the component of the solution due to IC dominates the complete solutions. For RC/RL circuits ( $\tau$ ) can be considered as the external of transient region  $\tau = RC$  or  $\tau = L/R$  sec

Steady state soln is the part which is free of initial conditions. Initial conditions are decayed to zero.


#### Circuits with DC inputs

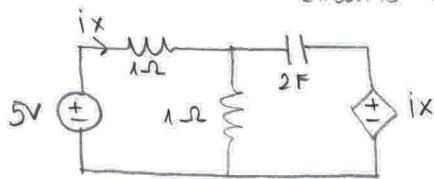

$v_c(0^-) = 5V$  Find  $v_c(t)$   $i_x = 5 - e$   
 $\frac{e-5}{1} + \frac{e}{1} + C \frac{dv}{dt} + 2e - 5 + 2(e - (5-e)) = 0$




$2e(t) - 5 + 4e'(t) = 0 ; (4D+2)e(t) = 5 ;$

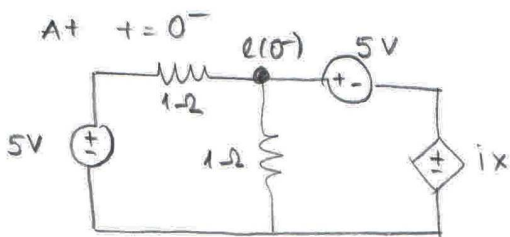$(D+1/2)e(t) = 5/4 \quad e(t) = d e^{-t/2} + 5/2$




$i_x = 0$   
 $e(t) = 5/2(1 + e^{-t/2})$   
 $v_c(t) = e(t) - (5 - e) = 2e(t) - 5$   
 $v_c(t) = e(t) = 5e^{-t/2} \rightarrow 0$
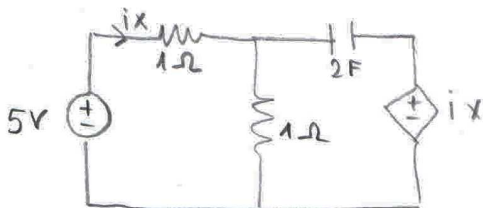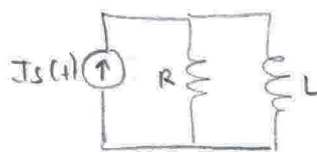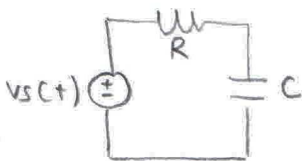
#### First (1<sup>st</sup>) Order circuits with DC inputs



$v_c(0^-) = 5V$   
 $v_c(t) = 5 e^{-t/2} u(t) \rightarrow 0$

#### DC Input case:

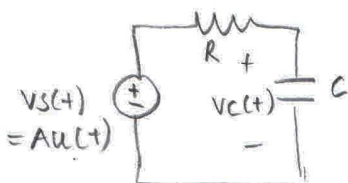


$v_c(0^-) = V_0 \quad v_s(t) = v_R + v_C = iR + v_C = RC v_C'(t) + v_C$   
 $= (RCD+1)v_C(t)$

$(D + \frac{1}{RC})v_C(t) = \frac{v_s(t)}{RC} = \frac{Au(t)}{RC}, \quad v_c(0^-) = V_0$

$v_{cap}(t) = v_{cap}^p(t) + v_{cap}^h(t) = A + d e^{-t/RC} u(t) = A + (V_0 - A) e^{-t/RC} u(t)$   
 Algebraic solution

So that the initial condition is satisfied  $v_{cap}(t) = A + (V_0 - A)e^{-t/RC} u(t)$   
 as  $t \rightarrow \infty$  capacitor gets fully charged

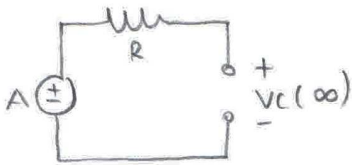For DC input capacitors will be eventually charged and its current will be zero  
 So capacitor acts like open circuit as  $t \rightarrow \infty$




$$v_c(\infty) = A$$

$$v_c(0^-) = V_0 \quad v_c(0^+) = V_0$$




$$v_c(t) = v_c(\infty) + [v_c(0^+) - v_c(\infty)] e^{-t/\tau} u(t)$$

First Order RC Circuits with DC inputs

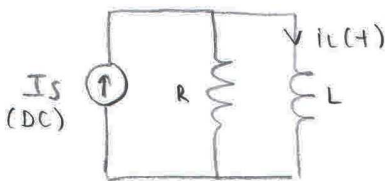


as  $t \rightarrow \infty$

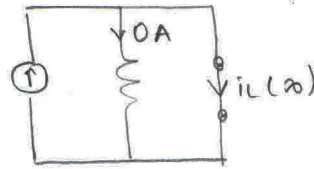

L acts as short circuit  
 $i_L(\infty) = I_s$

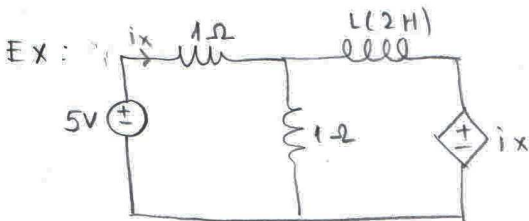
$$i_L(t) = I_L(\infty) + (I_0 - I_L(\infty)) e^{-t/\tau} u(t) \quad \tau = L/R$$



$R_{seen} \text{ by inductor} = 1 \Omega$


$\tau = L/R = 2 \text{ sec's}$

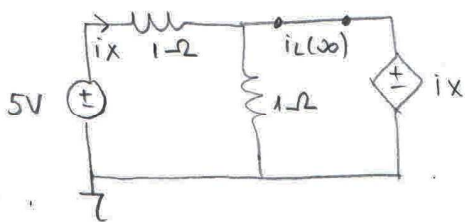$I_L(\infty) = ? \quad I_0 = 5A \quad I_L(t) = ?$



$i_L(\infty) = 0A$

$i_L(t) = 5e^{-t/2} u(t)$

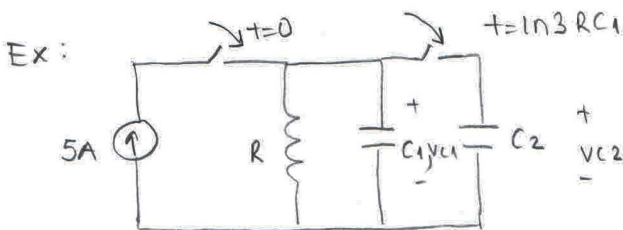


$v_{c1}(0^-) = 2R \quad v_{c2}(0^-) = 6R$

At  $t=0$  switch 1 closes

At  $t=ln3RC1$  switch 2 closes

Find  $v_{c1}(t)$  and  $v_{c2}(t)$

$0 < t < ln3RC1$

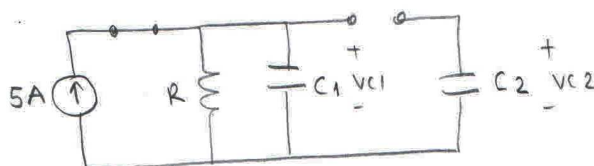


$v_{c2}(t) = v_{c2}(0^+) = v_{c2}(0^-) = 6R$

$v_{c1}(t) = v_{c1}(\infty) + [v_{c1}(0^+) - v_{c1}(\infty)] e^{-t/\tau}$

$v_{c1} = 5R - 3R e^{-t/\tau} u(t)$

$$V_{C1}(RC_1 \ln 3) = 5R - 3R e^{-\ln 3} = 4R$$

$$\ln 3 RC_1 < + < \ln 3 RC_1^+$$

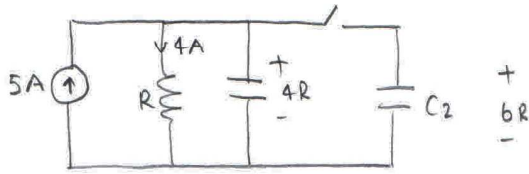

$$V_{C1}(\text{before}) = 4R$$

$$V_{C2}(\text{before}) = 6R$$

$$t = \ln 3 RC_1^-$$

$V_{com}(\text{after})$  they are in parallel


$$Q_{\text{before}} = C_1 V_{C1}^{\text{before}} + C_2 V_{C2}^{\text{before}} = 4RC_1 + 6RC_2$$

$$Q_{\text{after}} = Q_{\text{before}} = (C_1 + C_2) V_{com} = \frac{4RC_1 + 6RC_2}{C_1 + C_2}$$

$$V_{com} \text{ is after } t = \ln 3 RC_1^+$$

for  $t > \ln 3 RC_1^+$

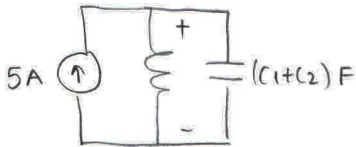
$$V_{C1}(\ln 3 RC_1^+) = V_{C2}(\ln 3 RC_1^+) = V_{com}$$




$$V_{com}(\ln 3 RC_1^+) = \frac{4RC_1 + 6RC_2}{C_1 + C_2}$$

$$V_{com}(t) = V_C(\infty) - [V_C(\infty) - V_{com}(\ln 3 RC_1^+)] e^{-(t - \ln 3 RC_1)/\tau} \quad t > \ln 3 RC_1$$
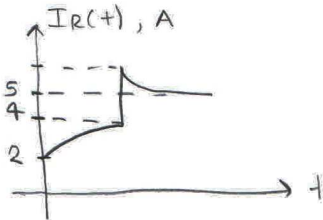
$$V_{com}(t) = 5R - (5R - R \frac{4C_1 + 6C_2}{C_1 + C_2}) e^{-(t - \ln 3 RC_1)/RC_1(C_1 + C_2)} \quad t > \ln 3 RC_1$$




EX: ZPS VI, 1-

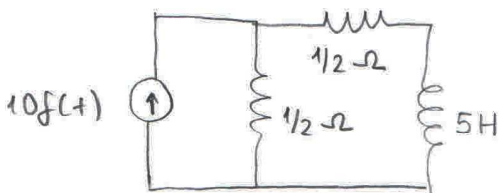

$$i_L(0^-) = -2A$$

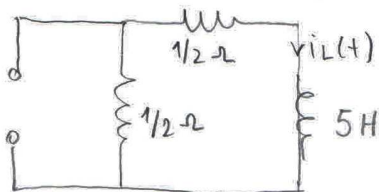
$$i_L(0^+) = ? \quad \text{for } t > 0^+$$



$$i_L(0^+) = I_0 \quad i_L(t) = I_0 e^{-t/\tau} u(t) \quad t > 0^+$$

$$\tau = L/R_{\text{seen}} = 5/1 = 5 \text{ secs}$$


for  $0 < t < 0^+$

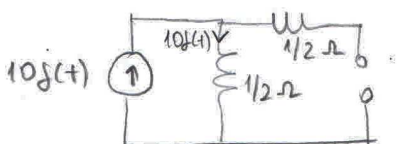

$$I_0 = i_L(0^-) + \frac{1}{L} \int_0^{0^+} v_L(z) dz = -2 + \frac{1}{5} \int_0^{0^+} 5f(t') dt' = -1A$$

a-) Unit Step Response

b-) Ramp Response

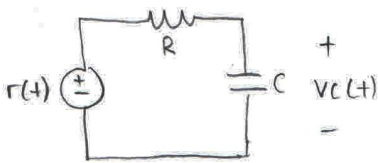


$$(D + \frac{1}{RC}) v^{\text{ramp}}(t) = \frac{t}{RC} \quad t \gg 0 \quad v^{\text{ramp}}(0^-) = 0V$$


$$v^{\text{ramp}}(t) = \underbrace{A + Bt}_{\text{particular}} + \underbrace{d e^{-t/RC}}_{\text{homogenous}} \quad t \gg 0$$

$$v^{\text{ramp}}(t) = \left\{ t - RC(1 - e^{-t/RC}) \right\} u(t) \quad t \gg 0$$
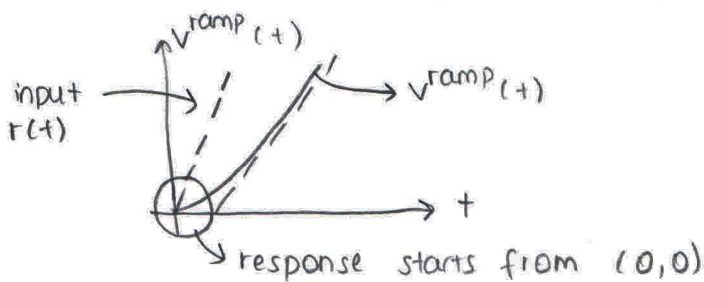
$$v^{\text{ramp}}(0^-) = v^{\text{ramp}}(0^+) = -RC + d = 0 \quad ; \quad d = RC$$



c-) Sinusoidal Response

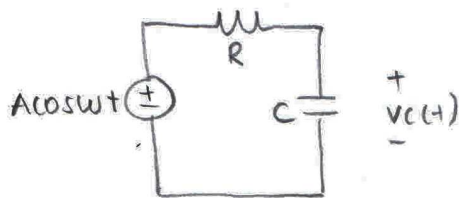

$$v_c(0^-) = 0V$$

$$(D + \frac{1}{RC}) v_c^{\text{sin}} = \frac{A \cos wt}{RC}$$

$$v_c^{\text{sin}}(t) = \underbrace{B_1 \cos wt + B_2 \sin wt}_{\text{particular}} + \underbrace{d e^{-t/RC}}_{\text{homogenous}}$$

$$(D + \frac{1}{RC}) (B_1 \cos wt + B_2 \sin wt) = \frac{A}{RC} \cos wt$$

$$\cos wt \left( \frac{B_1}{RC} + B_2 \right) + \sin wt \left( -\omega B_1 + \frac{B_2}{RC} \right) = \frac{A}{RC} \cos wt \quad \forall t \gg 0$$


$$\frac{B_1}{RC} + B_2 = \frac{A}{RC} \quad -\omega B_1 + B_2/RC = 0 \quad B_2 = \omega RC B_1$$

$$\begin{bmatrix} 1/RC & \omega \\ -\omega & 1/RC \end{bmatrix} \begin{bmatrix} B_1 \\ B_2 \end{bmatrix} = \begin{bmatrix} A/RC \\ 0 \end{bmatrix} \rightarrow \begin{bmatrix} B_1 \\ B_2 \end{bmatrix} = \frac{1}{(RC)^2 \omega^2} \begin{bmatrix} A/(RC)^2 \\ \frac{A}{RC} \omega \end{bmatrix}$$

$$v^{sin}(t) = \underbrace{\frac{A/RC}{(RC)^2 + \omega^2} \left[ \frac{1}{RC} \cos \omega t + \omega \sin \omega t \right]}_{\text{particular}} + d e^{-t/RC}$$

$v^{sin}(0^+) = 0V$   
 $d = \frac{-A/(RC)^2}{(RC)^2 + \omega^2} = -B_1$

d-Impulse Response

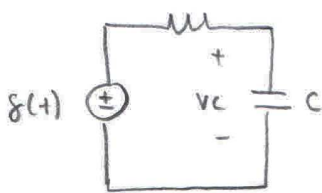

$$v_c(0^-) = 0V$$


$$\left(D + \frac{1}{RC}\right) v_c^{imp}(t) = \frac{\delta(t)}{RC} \quad t \gg 0$$

$$\left(D + \frac{1}{RC}\right) v_c^{imp}(t) = 0 \quad t \gg 0$$

$$v_c^{imp}(0^+) = ?$$

$$v_c^{imp}(t) = v_c(0^+) e^{-t/RC}$$


$$0 < t < 0^+$$

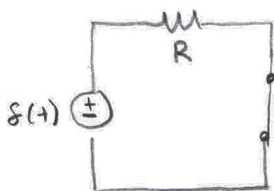

$$i_c(t) = \frac{\delta(t)}{R} = C \dot{v}_c(t)$$


$$v_c(0^+) = v_c(0^-) + \frac{1}{C} \int_0^{0^+} i_c(\tau) d\tau = 0 + \frac{1}{C} \int_0^{0^+} \frac{\delta(\tau)}{R} d\tau = \frac{1}{RC}$$
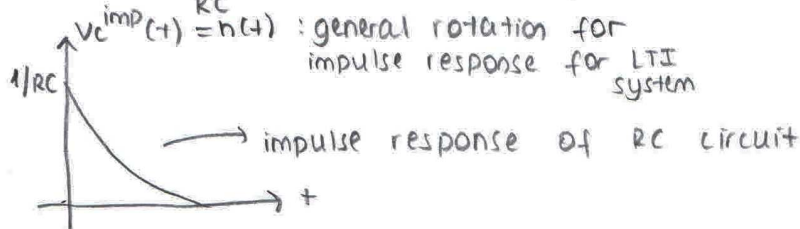
$$v_c^{imp}(t) = \frac{1}{RC} e^{-t/RC} u(t) \quad t \gg 0$$



Responses are calculated when the system does not contain any initial energy and the response is the reaction of the system to an input.



Linearity of zero-state Responses.

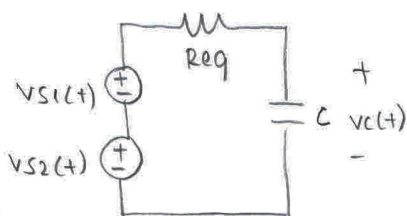

$$v_c(0^-) = 0V$$

$$\left(D + \frac{1}{RC}\right) v_c^{A+B}(t) = \frac{v_{s1}(t) + v_{s2}(t)}{RC}$$
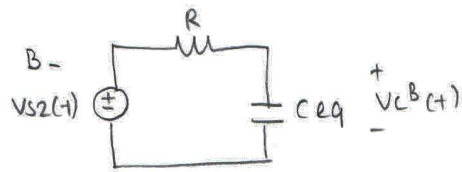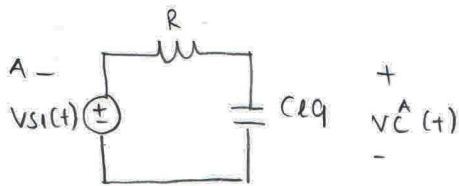
$$v_c^{A+B}(0^-) = 0V \rightarrow v_c^A + v_c^B = v_c^{A+B} \text{ satisfied}$$




$v_c^A(t)$  is the response to  $v_{s1}$

$v_c^B(t)$  is the response to  $v_{s2}$

So linearity of zero state responses follows from the discussion

EX:  $v_s(t) = 3u(t) + \delta(t)$

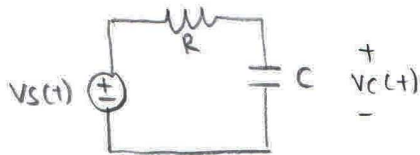


$v_c(0^-) = 0$

Find  $v_c(t)$ ?



$$v_c(t) = 3v_c^{\text{step}}(t) + h(t) \rightarrow (1 - e^{-t/RC})$$

$$= 3 + \left[ \frac{1}{RC} - 3 \right] e^{-t/RC} \quad t \gg 0$$


Time Invariancy

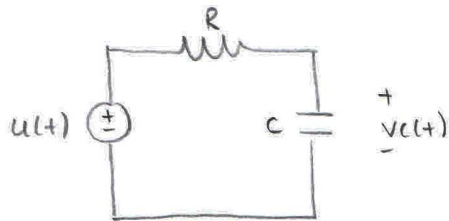

$v_c(0^-) = 0V$

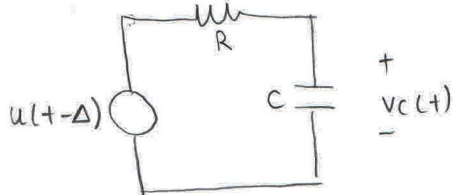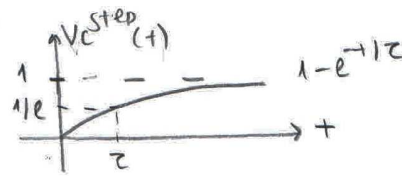

$v_c(\Delta^-) = 0V$

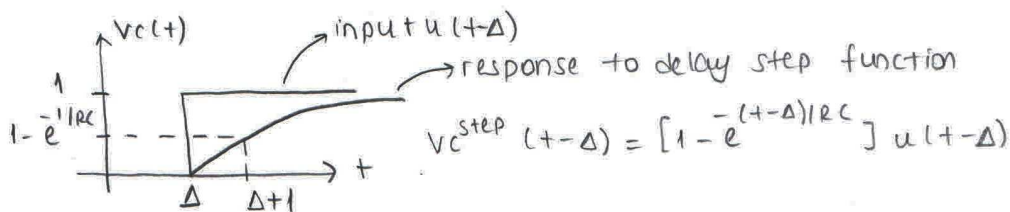

$v_c^{\text{step}}(t) = (1 - e^{-t/RC}) u(t)$

For time invariant systems



for RC circuit  $(D + \frac{1}{RC}) v_c(t) = \frac{v_s(t)}{RC}$   $v_c(0^-) = 0V$   $\Delta = 0$



$(D + \frac{1}{RC}) v_c(t) = \frac{v_s(t - \Delta)}{RC}$

$v_c^\Delta(\Delta) = 0V$   $v_c^\Delta(t) = v_c^{\Delta=0}(t - \Delta)$

$v_c^\Delta(\Delta) = 0$  Initial condition is satisfied

Diff. eqn is also time invariant

Ex:

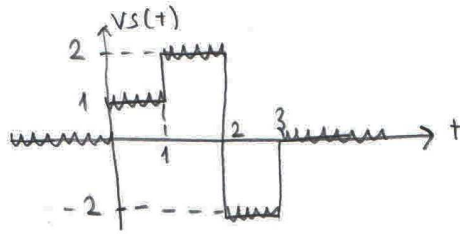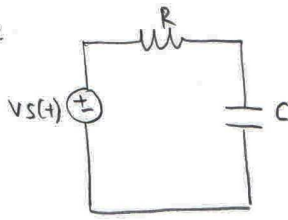


$$v_c(0^-) = 0V$$

Find  $v_c(t)$  in terms of step responses of the system

$$v_s(t) = \underbrace{u(t)}_{v_{s1}} + \underbrace{u(t-1)}_{v_{s2}} - \underbrace{4u(t-2)}_{v_{s3}} + \underbrace{2u(t-3)}_{v_{s4}}$$

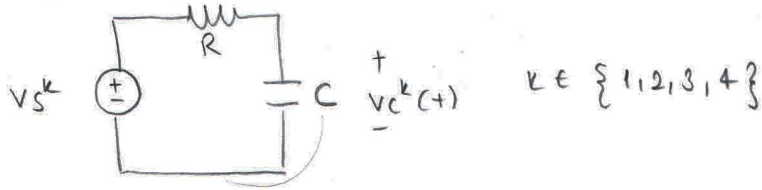By linearity of zero-state responses  $v_c(t) = v_{c1}(t) + v_{c2}(t) + v_{c3}(t) + v_{c4}(t)$





$$v_c(t) = \overset{\text{step}}{v_c(t)} + \overset{\text{step}}{v_c(t-1)} - 4 \overset{\text{step}}{v_c(t-2)} + 2 \overset{\text{step}}{v_c(t-3)}$$

↳ response to delayed step input (time invariance)

$$v_c^{\text{step}}(t) = (1 - e^{-t/RC})u(t)$$

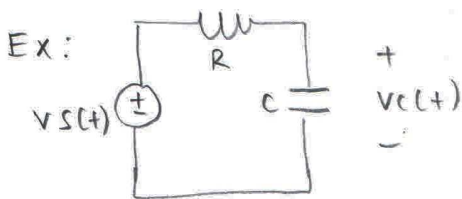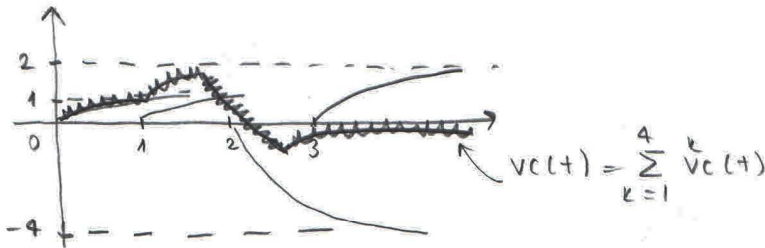
$$v_c(t) = (1 - e^{-t/RC})u(t) + (1 - e^{-(t-1)/RC})u(t-1) - 4(1 - e^{-(t-2)/RC})u(t-2) + 2(1 - e^{-(t-3)/RC})u(t-3)$$



$$v_s(t) = \delta(t) \rightarrow v_c(t) = \frac{1}{RC} e^{-t/RC} u(t) \text{ impulse resp.}$$

$$v_s(t) = u(t) \rightarrow v_c(t) = (1 - e^{-t/RC})u(t) \text{ step response}$$
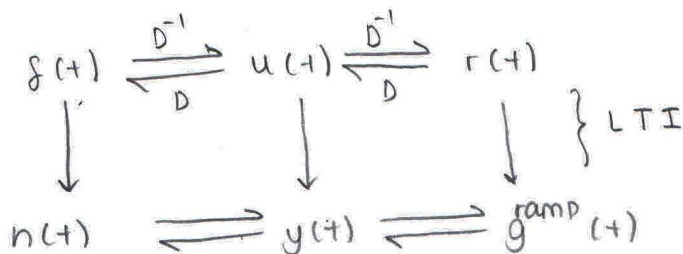
$$v_s(t) = t \rightarrow v_c(t) = (t - RC + RC e^{-t/RC})u(t) \text{ ramp resp.}$$



$$\begin{aligned} (d/dt) \overset{\text{step}}{y(t)} &= (d/dt) (1 - e^{-t/RC})u(t) + (1 - e^{-t/RC}) \frac{d}{dt} u(t) \\ &= \frac{1}{RC} e^{-t/RC} u(t) + \frac{1 - e^{-t/RC}}{1 - e^{-t/RC}} \delta(t) \\ &= \frac{1}{RC} e^{-t/RC} u(t) + \delta(t) \end{aligned}$$


$$h(t) = \frac{1}{RC} e^{-t/RC} u(t)$$



So impulse response can be calculated by

1. calculating step response
2.  $h(t) = \frac{d}{dt}$  (unit-step) response


EX:

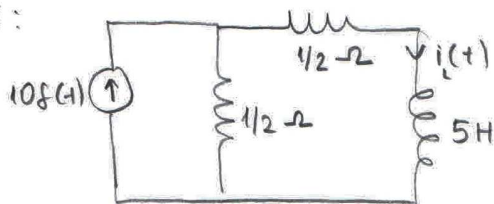

Find  $i_L(t) \quad t > 0$

$$i_L(0^-) = -2A$$


zero input

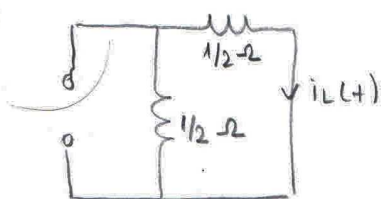

$$\tau = L/R = 5 \text{ sec's}$$

$$i_L^{zi}(t) = -2e^{-t/5} \text{ A}$$


zero state

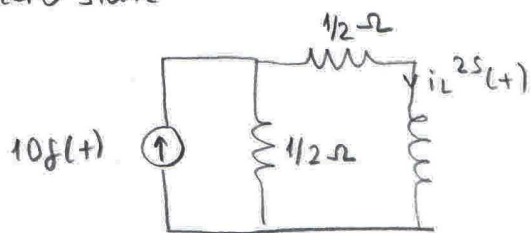

$$i_L^{zs}(t) = i_L(0^-) = 0A$$

$$i_L^{zs}(0^+) = \frac{1}{L} \int_0^{0^+} v_L(\tau) d\tau = 1A$$


for  $t > 0^+ \quad i_L(0^+) = 1A$

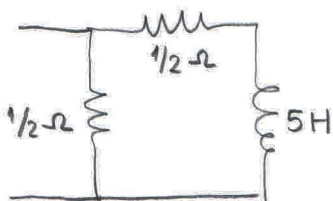

$$i_L^{zs}(t) = e^{-t/5} \text{ A}$$


$$\text{complete soln} = e^{-t/5} \text{ A}$$

Ex:

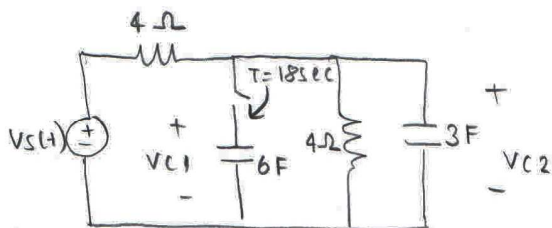


$$v_{c1}(0^-) = -2V \quad v_{c2}(0^-) = 7V$$

Input:

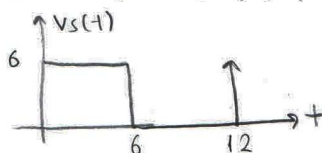

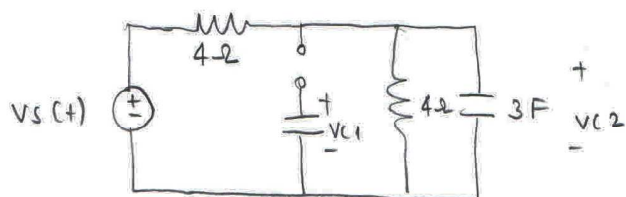Before switch closes  $t < 18 \text{ sec}$




$$v_{c1}(t) = v_{c1}(0^-) = -2 \quad 0^+ < t < 18^-$$

$$v_{c2}(0^-) = 7V$$

$$v_{c2}(t) = \frac{2e^{-t/\tau}}{7e^{-t/\tau} u(t)} + v_{c2}(t)$$

$$\tau = 2 \Omega \cdot 3F = 6 \text{ sec}$$

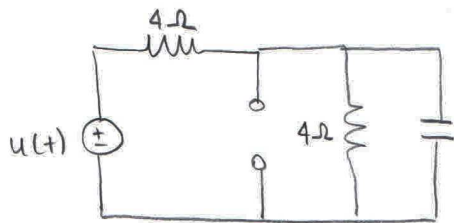Idea: Find the unit step response for  $v_{c2}(t)$ , and find the solution for the given input in terms of  $v_{c2}^{\text{unit step}}(t)$



$$v_{C2}^{\text{unit step}}(t) = \left[ \frac{1}{2} - \frac{1}{2} e^{-t/6} \right] u(t) \quad \text{zero state response}$$

$$v_{C2}(0^+) = 0 \text{ V} \quad v_{C2}(\infty) = 1/2 \text{ V}$$

$$h(t) = \frac{1}{12} e^{-t/6} u(t) \rightarrow \text{impulse response}$$


$$v_{C2}^{\text{zs}}(t) = v_{C2}^{\text{step}}(t) \times 6 - 6 v_{C2}^{\text{step}}(t-6) + h(t-12) \times 6 = 3(1 - e^{-t/6}) u(t) - 3(1 - e^{-(t-6)/6}) u(t-6) + \frac{1}{2} e^{-(t-12)/6} u(t-12) \quad 0^+ < t < 18^-$$

$$v_{C2}(t) = v_{C2}^{\text{zi}}(t) + v_{C2}^{\text{zs}}(t) \quad \text{complete solutions for } 0^+ < t < 18^-$$

$$v_{C2}(18^-) = 2.14 \text{ V}$$

$$v_{C1}(18^-) = -2 \text{ V}$$


After switch closes  $t > 18$

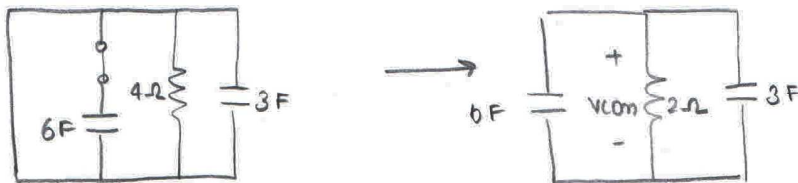

$$v_{\text{com}}(18^+) = \frac{2.14 \times 3 + (-2) \cdot 6}{9} = -0.62 \text{ V}$$

$$v_{C2}(t) = (-0.62) e^{-(t-18)/6} u(t-18) \quad \text{for } t > 18^+$$

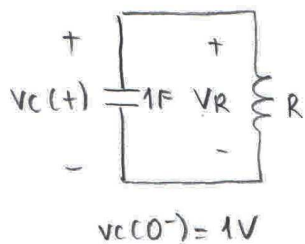Time varying and/or Nonlinear First Order Circuits



a-) R;  $R = 1 \Omega$  linear time invariant

b-) R;  $R(t) = \frac{1}{1+0.5 \cos t}$  linear time varying

c-) R; Nonlinear resistor with  $i_R = v_R^2$  nonlinear time inv

$$a-) C v_C' = -i_R \quad v_C' = -\frac{v_C}{1} \quad v_C(0^-) = 1 \text{ V} \quad v_C(t) = e^{-t/1} \text{ V}$$

$$b-) C v_C' = -\frac{v_C(t)}{R(t)} = -(1+0.5 \cos t) v_C(t)$$

$$\frac{d}{dt} v_C(t) = -(1+0.5 \cos t) v_C(t)$$

$$\frac{dv_C(t)}{v_C(t)} = -(1+0.5 \cos t) dt \quad \ln(v_C(t)) = -(t+0.5 \sin t) + K$$

$$v_C(t) = A e^{-(t+0.5 \sin t)}$$


$$V_c(0) = 1 \quad V_c(t) = e^{-(t+0.5 \sin t)} \quad V$$

$$C-) \quad C \dot{V}_c(t) = -iR = -V_c^2(t)$$

$$\frac{dV_c(t)}{dt} = -V_c^2(t) \quad ; \quad \frac{dV_c(t)}{V_c^2(t)} = -dt \quad ; \quad -[V_c(t)]^{-1} = -t + K$$


$$V_c(t) = \frac{1}{t-K} \quad V_c(0) = 1 \Rightarrow K = -1 \quad \text{then} \quad V_c(t) = \frac{1}{t+1}$$

EX:

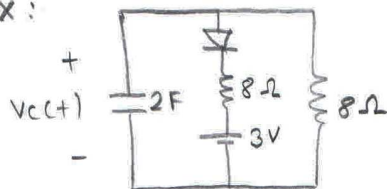

$$V_c(0^-) = 10V \quad V_c(t) = ?$$


If  $V_c(t) > 3V$  D: ON

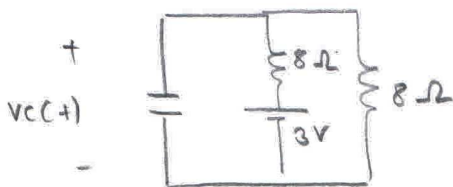


$$V(\infty) = 1.5V$$

$$V_c(t) = 1.5 + 8.5 e^{-t/8} \rightarrow V_c(t=3V) = 3V$$

$$t=3V = 8 \ln \frac{17}{3}$$

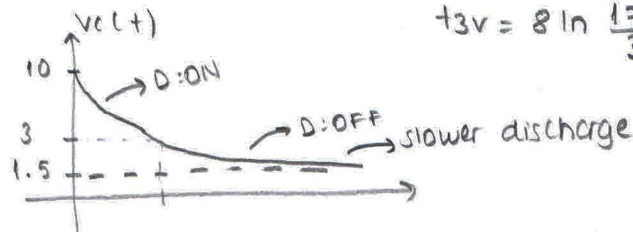


If  $V_c(t) < 3$  D: OFF

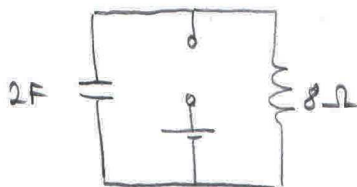


$$V_c(t=3V^+) = 3V$$

$$V_c(t) = 3 e^{-(t-3V)/16} \quad V$$

EX:

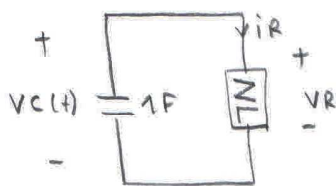

$$V_c(0^-) = 4V$$

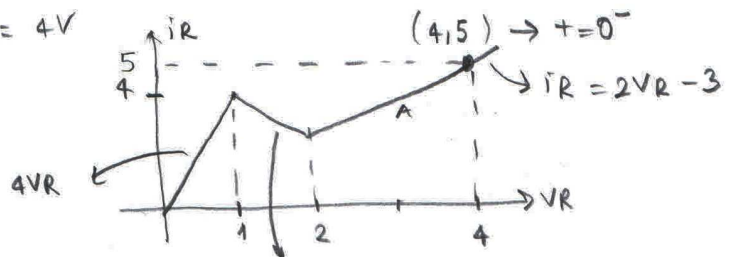

$$-3VR + 7$$

$$C \dot{V}_c(t) = -iR = -f(V_c)$$

$$V_c(0^-) = 4V$$


$$V_c(0^+) = -f(V_c(0^+))$$

a)  $2 < V_c < 4$  in (A) segment

$$V_c'(t) = -iR = 3 - 2V_c$$

$$V_c(t) (D+2) = 3 \quad V_c(0^-) = 4V \text{ then}$$

$$V_c(t) = 2.5 e^{-2t} + 1.5$$

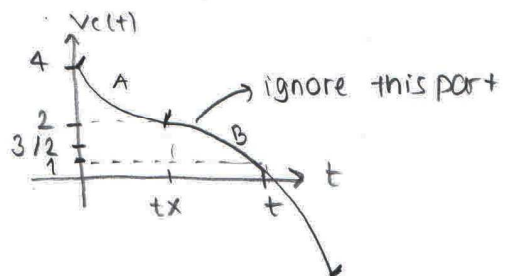



$b_1 < V_c < 2 \quad V_c'(t) = -iR = 3V_R - 7$

$(D-3)V_c(t) = -7$

$V_c(t+x) = 2V$

$V_c(t) = \left[ \frac{7}{3} - \frac{1}{3} e^{3(t-t_x)} \right] u(t-t_x)$

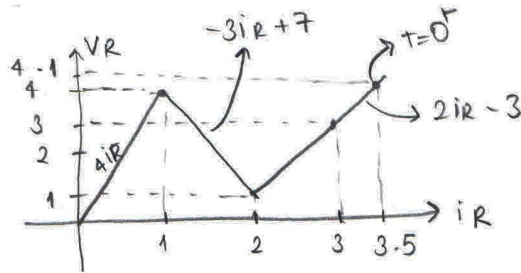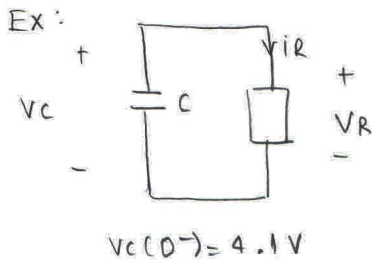$V_c'(t) = -iR = -4V_c \quad V_c'(t) = -iR = -4V_c \quad V_c(t_y) = 1V \quad V_c(t) = e^{-4(t-t_y)} u(t-t_y)$



current controlled

$C V_c'(t) = -iR(t) \quad C = 1F$

at  $t = 0^+ \quad V_c'(0^+) = -3.55$

for  $4 < V_c < 4.1$

$V_c'(t) = -iR(t) = -\frac{V_c(t)+3}{2} \quad (D + \frac{1}{2})V_c(t) = -\frac{3}{2}$

$V_c(t) = -3 + 7.1 e^{-t/2}$  for  $4 < V_c(t) < 4.1$


when  $1 < V_c(t) < 4$  there are 3 possibilities for  $iR(t)$  that is there are 3 operating points. The solution prefers to be on the same mode that it has travelled upon, so  $1 < V_c(t) < 4$  the previous diff. eqn is still valid.

$(D + 1/2)V_c(t) = -3/2$  is still valid since this is the preferred path

$V_c(t) = -3 + 7.1 e^{-t/2} \quad 1 < V_c(t) < 4.1$

for  $V_c(t) < 1$

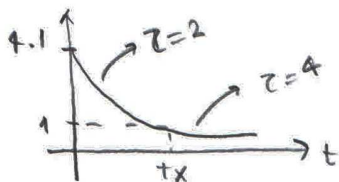$V_c'(t) = -iR(t) = -\frac{V_c(t)}{4} \quad V_c(t) = e^{-(t-t_x)/4} u(t-t_x)$  when  $t > t_x$




Second Order Systems

parallel RLC;

$i_L(0^-) = I_0$

$V_c(0^-) = V_0$

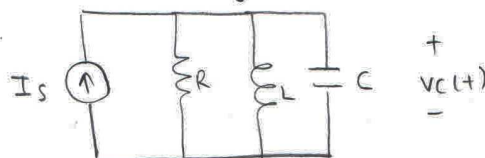

$\frac{V_c(t)}{R} + i_L(t) + C V_c'(t) = i_s(t)$   
 $i_L(0^-) + \frac{1}{L} \int_0^t V_c(\tau) d\tau$


$$\frac{v_c(t)}{R} + i_L(0^-) + \frac{1}{L} \int_0^+ v_c(z) dz + c \dot{v}_c(t) = i_s(t) \quad t \gg 0$$

↑  
integro differential equation

take  $\frac{d}{dt}$  ;  $\frac{1}{L} v_c(t) + \frac{1}{R} \dot{v}_c(t) + c \ddot{v}_c(t) = \frac{d}{dt} i_s(t)$

$$\left( D^2 + \frac{1}{RC} D + \frac{1}{LC} \right) v_c(t) = \frac{1}{c} \frac{d}{dt} i_s(t) \quad v_c(0^-) = V_0$$

At  $t=0^-$

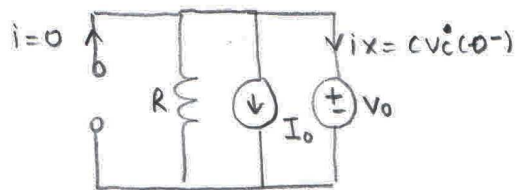

$$i_x = -\frac{V_0}{R} - I_0 \quad v_c(0^+) = \frac{-(V_0 + R I_0)}{RC}$$

State equation: 1<sup>st</sup> Order Matrix differential equations

State equation are first order diff. eqn. set such that right hand side is a linear combination of state variables and input. State variables =  $\{ v_c(t), I_L(t) \}$

$$\left. \begin{array}{l} \text{KCL: } \frac{v_c(t)}{R} + I_L(t) + C \dot{v}_c(t) = i_s(t) \\ \text{KVL: } L \dot{I}_L(t) = v_c(t) \end{array} \right\} \begin{bmatrix} \dot{v}_c(t) \\ \dot{I}_L(t) \end{bmatrix} = \begin{bmatrix} -1/RC & -1/C \\ 1/L & 0 \end{bmatrix} \begin{bmatrix} v_c(t) \\ I_L(t) \end{bmatrix} + i_s \begin{bmatrix} 1/C \\ 0 \end{bmatrix}$$

Zero Input Response

Parallel RLC ;  $(D^2 + \frac{1}{RC} D + \frac{1}{LC}) v_c(t) = \frac{1}{c} D i_s(t)$  ↗ 0 for zero input

$$(D^2 + 2\alpha D + \omega_0^2) v_c(t) = 0$$

For parallel RLC

$$2\alpha = 1/RC \quad \omega_0^2 = 1/LC$$

α : damping factor  
ω<sub>0</sub> : resonance frequency

$$(D^2 + 2\alpha D + \omega_0^2) v_c(t) = 0$$

$$v_c(0^-) = V_0$$

$$\dot{v}_c(0^-) = \dot{V}_0$$

Constant Coefficient Differential Equation

Guess  $v_c(t) = \beta e^{\lambda t}$  by substituting into diff eqn;

$$(\lambda^2 + 2\alpha \lambda + \omega_0^2) \beta e^{\lambda t} = 0$$

β=0 trivial solution

$$\lambda^2 + 2\alpha \lambda + \omega_0^2 = 0$$

$$\lambda_{1,2} = \frac{-2\alpha \pm \sqrt{4\alpha^2 - 4\omega_0^2}}{2}$$

$v_c(t) = 0$  initial condition

not satisfy

$$= -\alpha \pm \sqrt{\alpha^2 - \omega_0^2}$$

3 possible solutions for  $\lambda_1$  and  $\lambda_2$

1. Roots are real and distinct ( $\Delta > 0$ ),  $\alpha > \omega_0$  and  $\lambda_1 \neq \lambda_2$

$$v_c(t) = c_1 e^{-2t} + c_2 e^{-3t} \quad \lambda_1 = -2 \quad \lambda_2 = -3$$

2. Roots are real and same  $\lambda_1 = \lambda_2$  ( $\Delta = 0$   $\alpha = \omega_0$ )


$$v_c(t) = c_1 e^{-t} + c_2 t e^{-t} \quad \lambda_1 = \lambda_2 = -1$$

3. Roots are complex, discriminant is negative  $\Delta < 0$


$$v_c(t) = e^{-t} (c_1 \cos 3t + c_2 \sin 3t) \quad \lambda_1 = -1 + j3 \quad \lambda_2 = -1 - j3$$

$\lambda_1 = \lambda_2^*$  [polynomial has real coefficients]

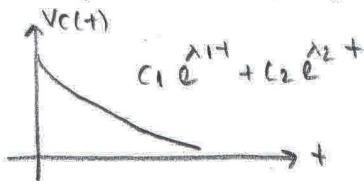
1. Overdamped ( $\lambda_1 \neq \lambda_2$ )



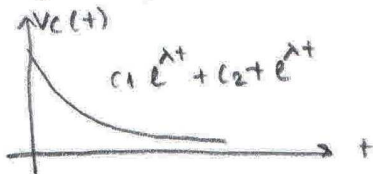
2. Critically damped ( $\lambda_1 = \lambda_2$ )



3. Underdamped

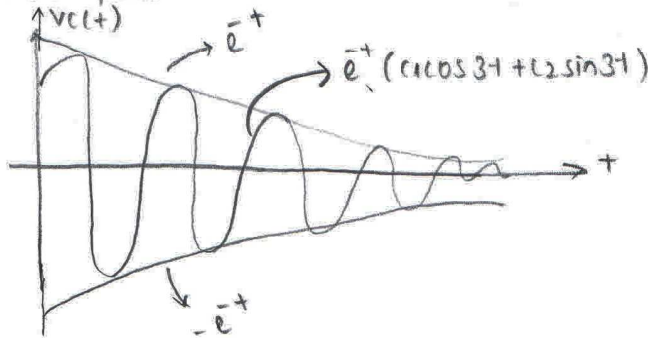

EX:

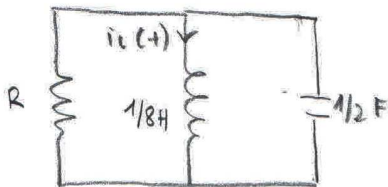

$v_c(t)$

$$i_L(0^-) = -4A$$


$$v_c(0^-) = 5V$$

a.)  $R = 1/5$

$$(D^2 + 2\alpha D + \omega_0^2)v_c(t) = 0$$

$$v_c(0^-) = ?$$
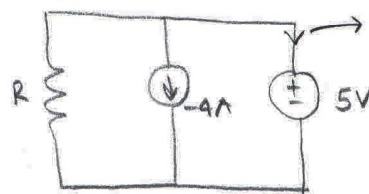
$$\alpha = \frac{1}{2RC} = 5 \quad \omega_0^2 = \frac{1}{LC} = 16$$



$$\frac{1}{2} v_c'(0^+) = 4 - \frac{5}{R}$$

$$v_c(0^+) = 8 - \frac{10}{R}$$

$$v_c'(0^+) = 42 \text{ V/sec}$$

a) wo overdamped case

$$V_c(t) = c_1 e^{\lambda_1 t} + c_2 e^{\lambda_2 t}$$

$$(D^2 + 10D + 16)V_c(t) = 0 \implies \lambda^2 + 10\lambda + 16 = 0 \quad \lambda_{1,2} = \{-2, -8\}$$

$$\left. \begin{aligned} V_c(t) &= c_1 e^{-2t} + c_2 e^{-8t} \\ V_c'(t) &= -2c_1 e^{-2t} - 8c_2 e^{-8t} \\ V_c(0^+) &= 5 \quad V_c'(0^+) = -42 \end{aligned} \right\} \begin{aligned} \begin{bmatrix} 1 & 1 \\ -2 & -8 \end{bmatrix} \begin{bmatrix} c_1 \\ c_2 \end{bmatrix} &= \begin{bmatrix} 5 \\ -42 \end{bmatrix} \\ c_1 &= -\frac{1}{3} \quad c_2 = \frac{16}{3} \end{aligned}$$

$$V_c(t) = -\frac{1}{3} e^{-2t} - \frac{16}{3} e^{-8t}$$

b-  $R = 1/4 \Omega$ ;

$$d = \frac{1}{2RC} = 4 \quad \omega_0 = 4 \quad d = \omega_0 \text{ critically damped}$$

$$(D^2 + 8D + 16)V_c(t) = 0$$

$$(D+4)^2 = 0 \quad V_c(t) = (5 - 12t) e^{-4t} \quad t > 0$$

c-  $R = 1/3 \Omega$

$$d = \frac{1}{2RC} = 3$$

$d < \omega_0$  underdamped

$$\omega_0 = 4$$

$$(D^2 + 6D + 16)V_c(t) = 0 \quad V_c(0^-) = 5$$

$$V_c'(0^-) = -\frac{1}{C} \left[ \frac{V_0}{R} + I_0 \right] = -22$$

$$\lambda^2 + 6\lambda + 16 = 0$$

$$\lambda_{1,2} = -3 \mp j\sqrt{7} \quad V_c(t) = \beta_1 e^{(-3+j\sqrt{7})t} + \beta_2 e^{(-3-j\sqrt{7})t}$$

$$V_c'(t) = \beta_1 \lambda_1 e^{\lambda_1 t} + \beta_2 \lambda_2 e^{\lambda_2 t}$$

$$\begin{bmatrix} 1 & 1 \\ \lambda_1 & \lambda_2 \end{bmatrix} \begin{bmatrix} \beta_1 \\ \beta_2 \end{bmatrix} = \begin{bmatrix} 5 \\ -22 \end{bmatrix}$$

therefore;  $\beta_1 = \frac{5}{2} + j\frac{\sqrt{7}}{2} \quad \beta_2 = \frac{5}{2} - j\frac{\sqrt{7}}{2}$


$$V_c(t) = \beta_1 e^{\lambda_1 t} + \beta_2 e^{\lambda_2 t}$$

$$= 2 \operatorname{Re} \left\{ \beta_1 e^{\lambda_1 t} \right\} = 2 \operatorname{Re} \left\{ \|\beta_1\| e^{j\Delta\beta_1} e^{\lambda_1 t} \right\} = 2 \operatorname{Re} \left\{ \|\beta_1\| e^{j\Delta\beta_1} (\lambda_1^r + j\lambda_1^i) e^{\lambda_1 t} \right\}$$

$$= 2 \|\beta_1\| e^{\lambda_1^r t} \operatorname{Re} \left\{ e^{j(\lambda_1^i t + \Delta\beta_1)} \right\} \quad \lambda_1 = \lambda_1^r + j\lambda_1^i$$


$$= 2 \|\beta_1\| e^{\lambda_1^r t} \cos(\lambda_1^i t + \Delta\beta_1) \quad V$$
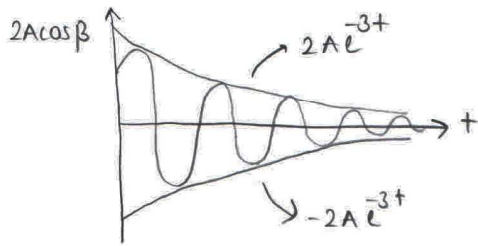
$$V_c(t) = 2A e^{-3t} \cos(\sqrt{7}t + \beta) \quad \text{select A and B to match initial condition}$$



$$v_c(t) = \gamma_1 e^{-3t} \cos(\sqrt{7}t) + \gamma_2 e^{-3t} \sin(\sqrt{7}t)$$

### 2<sup>nd</sup> Order Systems

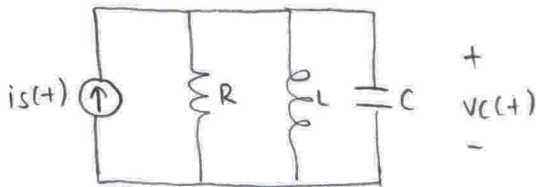

$$v_c(0^-) = V_0 \quad I_L(0^-) = I_0$$

$$\left(D^2 + \frac{1}{RC}D + \frac{1}{LC}\right)v_c(t) = \frac{1}{C} \frac{d}{dt} i_s(t)$$

$$v_c(t) = L \frac{d}{dt} i_L(t) = L D i_L(t)$$


$$\left(D^2 + \frac{1}{RC}D + \frac{1}{LC}\right)I_L(t) = \frac{1}{LC} i_s(t) \longleftarrow \left(D^2 + \frac{1}{RC}D + \frac{1}{LC}\right) D I_L(t) = \frac{1}{CL} D i_s(t)$$

a.) Overdamped ( $R=1/5, L=1/8, C=1/2 F$ )  $v_c^i(t) = \alpha e^{-2t} + \beta e^{-8t}$


b.) Critically damped ( $R=1/4, L=1/8, C=1/2 F$ )  $v_c^i(t) = \gamma_1 e^{-4t} + \gamma_2 t e^{-4t}$

c.) Underdamped system ( $R=1/3, L=1/8, C=1/2 F$ )  $v_c^i(t) = A e^{-3t} \cos \sqrt{7}t + B e^{-3t} \sin \sqrt{7}t$   
 $= \sqrt{A^2+B^2} e^{-3t} \cos(\sqrt{7}t - \tan^{-1}(B/A))$

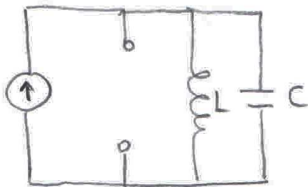d.) Lossless system ( $R=\infty, L=1/8, C=1/2 F$ )



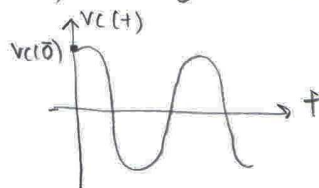
$$(D^2 + 16)v_c^i(t) = 0 \quad v_c^i(t) = A \cos 4t + B \sin 4t$$


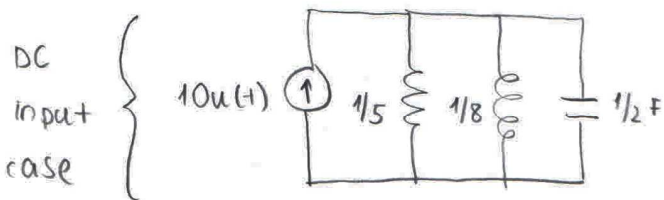
### Zero State Responses

Ramp, unitstep, impulse response: Remember for the zero state response, initial condition all zero. Hence the same zero state.




→ Overdamped case

$$v_c(0^-) = V_0 \quad I_L(0^-) = I_0$$

$$v_c(t) = \underbrace{A e^{-2t} + B e^{-8t}}_{\text{zero input}} + \underbrace{\quad}_{\text{response}}$$

as  $t \rightarrow \infty$

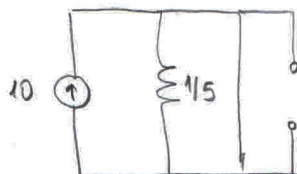

$$v_c(\infty) = 0V$$


$$I_L(\infty) = 10A$$

$$I_L(t) = C e^{-2t} + D e^{-8t} + 10$$

[A, B, C, D are found from] initial conditions



Ramp Response:

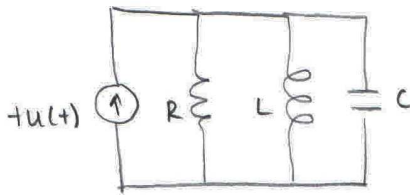

$$(D^2 + 2\alpha D + \omega_0^2) v_C^{2s}(t) = \frac{1}{C} \frac{d}{dt} (+u(t))$$

$$v_C^{2s}(0^-) = i_L^{2s}(0^-) = 0$$


$$(D^2 + 2\alpha D + \omega_0^2) v_C^{2s}(t) = \frac{1}{C} u(t) \quad t > 0$$

$$(D^2 + 2\alpha D + \omega_0^2) v_C^{2s}(t) = \frac{1}{C} \quad t > 0$$

$$v_C^{2s}(t) = A + B e^{\lambda_1 t} + C e^{\lambda_2 t} \quad t > 0$$


$A = \frac{1}{C\omega_0}$  Select B and C such that  $v_C(0^+)$  and  $v_C'(0^+)$  values are satisfied.

At  $t=0^+$

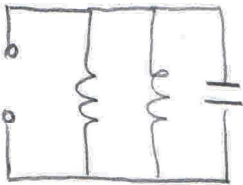

$$\left. \begin{aligned} v_C(0^+) &= v_C(0^-) = 0 \\ i_L(0^+) &= i_L(0^-) = 0 \end{aligned} \right\} \begin{aligned} v_C'(0^+) &= 0 \\ i_L'(0^+) &= 0 \end{aligned}$$

Unit Step Response:

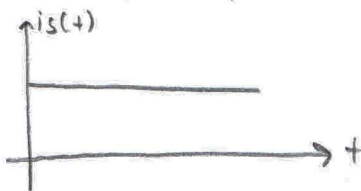

$$(D^2 + 2\alpha D + \omega_0^2) v_C^{2s}(t) = \frac{1}{C} f(t)$$


1. Circuit Theory based Approach:

$$(D^2 + 2\alpha D + \omega_0^2) v_C^{2s}(t) = 0 \quad t > 0$$

$$v_C^{2s}(t) = A e^{\lambda_1 t} + B e^{\lambda_2 t} \quad t > 0$$

At  $t=0^+$

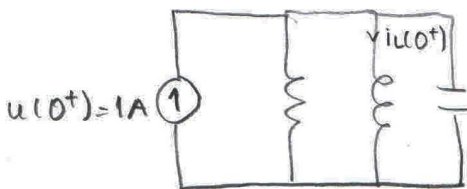using  $v_C(0^+) = 0$  and  $v_C'(0^+) = 1/C$  find A, B and finalize the step response




$$i_C(0^+) = C v_C'(0^+) = 1 \quad v_C'(0) = 1/C$$

$\begin{matrix} + \\ v_C(0^+) \\ - \end{matrix}$

$$v_C(0^-) = v_C(0^+) = 0$$

$$i_L(0^-) = i_L(0^+) = 0$$

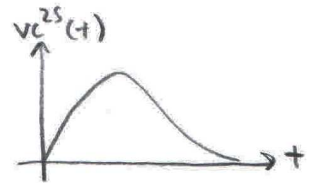

2. Mathematical Approach  $\rightarrow g_e(t)$

$$(D^2 + 2\alpha D + \omega_0^2) v_C(t) = \frac{1}{C} f(t)$$

$v_C(t)$  contains  $g_e(t)$

$v_C'(t)$  should contain  $g_e(t)$

Define  $\lim_{\epsilon \rightarrow 0} g_{\epsilon}(t) = \delta(t)$

But right hand side diff equation does not contain any  $g_{\epsilon}(t)$

So  $v_c(t)$  does not contain  $g_{\epsilon}(t)$

$v_c'(t)$  contain  $g_{\epsilon}(t)$

$v_c''(t)$  should contain  $g_{\epsilon}(t)$ . So this is not also possible

RHS has only  $g_{\epsilon}(t)$ ,  $v_c''(t)$  is impulsive

$v_c'(t)$  does not contain an impulse (step discontinuity)

$v_c(t) \rightarrow$  does not contain an impulse

Then integrate both sides of diff eqn between  $0^-$  and  $0^+$

$$\int_0^+ v_c''(t') dt' + 2d \int_0^+ v_c'(t') dt' + \omega_0^2 \int_0^+ v_c(t') dt' = \frac{1}{c} \int_0^+ \delta(t') dt' = \frac{1}{c}$$

↓  
does not  
contain an impulse

$$v_c'(0^+) - v_c'(0^-) + 2d \cdot 0 + \omega_0^2 \cdot 0 = 1/c$$


since  $v_c'(0^-) = I_c(0^-) = v_c(0^-) = I_c(0^-) = 0$

$$v_c'(0^+) = 1/c$$

$$v_c(0^+) = \int_0^+ v_c'(t') dt' + v_c(0^-) = 0$$

Same initial conditions found by circuit + theoretical inspection:

Impulse Response:

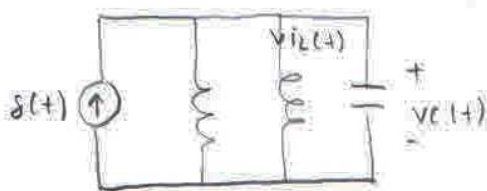


$$(D^2 + 2dD + \omega_0^2)v_C(t) = \frac{1}{c} \frac{d}{dt} \delta(t)$$

1- Solution by Circuit Theoretical Inspection

$$(D^2 + 2dD + \omega_0^2)v_C(t) = 0 \quad t > 0$$

$$v_C(t) = A e^{\lambda_1 t} + B e^{\lambda_2 t}$$

$$A + \quad 0^- < t < 0^+$$

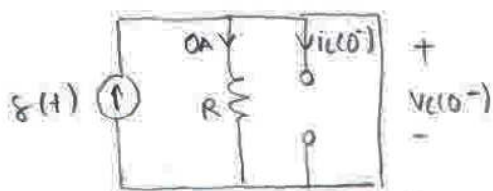


$$v_C(0^-) = 0V \quad I_L(0^-) = 0A$$

$$i_C(t) = \delta(t) \quad 0^- < t < 0^+$$

$$v_C(0^+) = v_C(0^-) + \frac{1}{c} \int_0^+ i_C(\tau) d\tau = v_C(0^-) + \frac{1}{c} = \frac{1}{c}$$

$$I_L(0^+) = I_L(0^-) + \frac{1}{L} \int_0^+ v_L(\tau) d\tau = 0$$

At  $t=0^+$

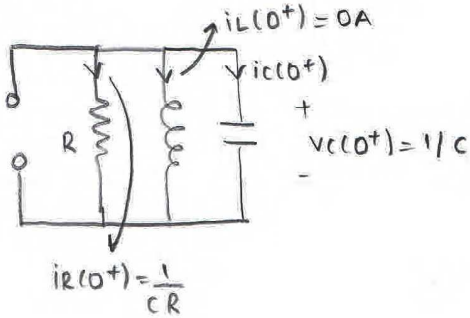

$$i_C(0^+) = -1/RC$$

$$C v_C'(0^+) = -1/RC$$

$$v_C'(0^+) = -1/RC^2$$

From I.C.'s I and II, the impulse response is found.

2. Mathematical Approach for the solution

$$(D^2 + 2dD + \omega_0^2) v_C(t) = \frac{1}{C} f'(t)$$

$v_C''(t)$  contains  $f'(t)$ ,  $v_C'(t)$  contains  $f(t)$ ,  $v_C(t)$  does not contain  $f(t)$

$$f'(t) \text{ doublet} \quad \int_0^+ f(t') f'(t') dt' = f'(0)$$

$$\int_0^+ v_C''(t') dt' + 2d \int_0^+ v_C'(t') dt' + \omega_0^2 \int_0^+ v_C(t') dt' = \frac{1}{C} \int_0^+ 1 \cdot f'(t') dt' = 0$$

$$v_C'(0^+) - v_C'(0^-) + 2d [v_C(0^+) - v_C(0^-)] + \omega_0^2 \cdot 0 = \frac{1}{C} \int_0^+ f'(t') dt' = 0$$

$$v_C'(0^+) + 2d v_C(0^+) = 0$$

To find another equation to find  $v_C(0^+)$  &  $v_C'(0^+)$


$$\begin{aligned} \bar{D}' \left\{ \begin{aligned} (D^2 + 2dD + \omega_0^2) v_C(t) &= \frac{1}{C} D f(t) \\ (D + 2d + \omega_0^2 D^{-1}) v_C(t) &= \frac{1}{C} f(t) \end{aligned} \right. \\ \bar{D}' \left\{ \begin{aligned} \int_0^+ v_C'(t') dt' + 2d \int_0^+ v_C(t') dt' + \omega_0^2 \int_0^+ \left[ \int_0^+ v_C(t'') dt'' \right] dt' &= \frac{1}{C} \end{aligned} \right. \end{aligned}$$

$$v_C(0^+) - v_C(0^-) + 2d \cdot 0 + \omega_0^2 \cdot 0 = \frac{1}{C}$$

$$v_C(0^+) = \frac{1}{C} \text{ and using the other equation}$$

$$v_C'(0^+) + 2d \frac{v_C(0^+)}{1/RC} = 0 \quad v_C'(0^+) = -1/RC^2$$

EX:

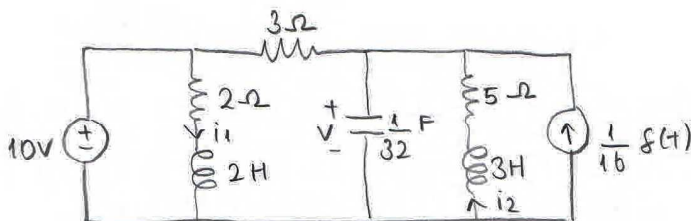


$$v(0^-) = 1V \quad i_1(0^-) = 0A$$

$$i_2(0^-) = 5A$$

Find  $t=0^+$  and  $t \rightarrow \infty$  solution of the circuit


at  $0^- < t < 0^+$

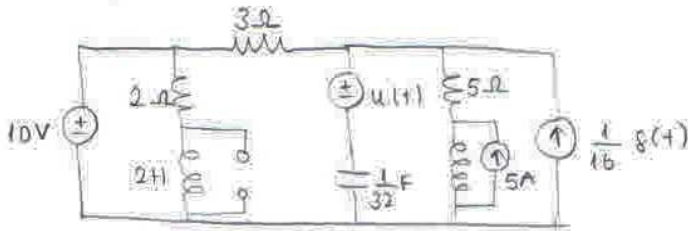

Initial condition models are implemented  
 cap, 2H and 3H shown have zero energy  
 $v_C(0^+)$ ,  $i_1(0^+)$  and  $i_2(0^+) = ?$

$$v_C(0^+) = v_C(0^-) + \frac{1}{C} \int_0^{0^+} i_C(\tau) d\tau$$

$i_C(t) = ?$   $0^- < t < 0^+$

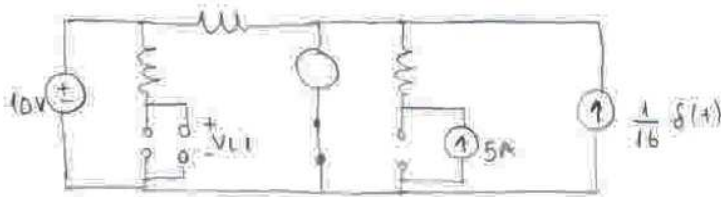

$$i_C(t) = \frac{1}{16} \delta(t) + 5 + \left(\frac{10-1}{3}\right) \quad v_C(0^+) = v_C(0^-) + \frac{1}{C} \int_0^{0^+} \left[\frac{1}{16} \delta(t') + k\right] dt'$$



$$v_C(0^+) = 3 \text{ V}$$

$$i_1(0^+) = i_1(0^-) + \frac{1}{L} \int_0^{0^+} v_{L1}(t') dt'$$

$$v_{L1} = 10 \text{ V} \quad v_{L2} = 26 \text{ V}$$

$$i_1(0^+) = i_1(0^-) = 0 \text{ A} \quad i_2(0^+) = i_2(0^-) = 5 \text{ A}$$
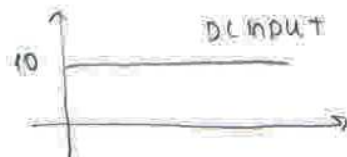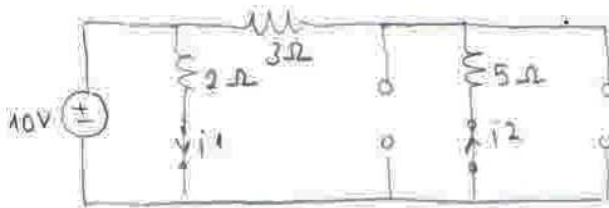
$$t \rightarrow \infty \quad i_1(t) \rightarrow A \quad i_2(t) \rightarrow B \quad v_C(t) \rightarrow C$$




$$i_1(\infty) = 5 \text{ A}$$

$$i_2(\infty) = -\frac{10}{8} \text{ A}$$

$$v_C(\infty) = \frac{25}{4} \text{ V}$$

### Series RLC Circuits

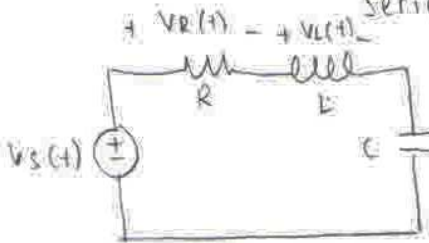

$v_C(0^-) = V_0 \quad I_L(0^-) = I_0$

= Dual of parallel RLC

$$\left(D^2 + \frac{1}{RC}D + \frac{1}{LC}\right)v_C(t) = \frac{1}{C} \frac{d}{dt} i_S(t)$$

Dual

$$v_C \leftrightarrow I_L \quad R \leftrightarrow G \quad L \leftrightarrow C \quad i_S \leftrightarrow v_S$$

$$\left(D^2 + \frac{R}{L}D + \frac{1}{LC}\right)I_L(t) = \frac{1}{L} D v_S(t)$$


by KVL;  $-v_s(t) + R i_L(t) + L \frac{di_L(t)}{dt} + v_C(t) = 0$

apply D  
divide by L  $(R + LD) i_L(t) + v_C(t) + \frac{1}{C} \int_0^t i_C(\tau) d\tau = v_s(t)$   
 $(D^2 + \frac{R}{L} D + \frac{1}{LC}) i_L(t) = \frac{1}{L} D v_s(t)$  series RLC


$(D^2 + 2\alpha D + \omega_0^2) D = \frac{1}{L} D v_s(t)$   $\alpha = R/2L$   $\omega_0 = \sqrt{1/LC}$  series RLC  
 $\alpha = 1/2RC$   $\omega_0 = \sqrt{1/LC}$  parallel RLC

So for both RLC configurations;

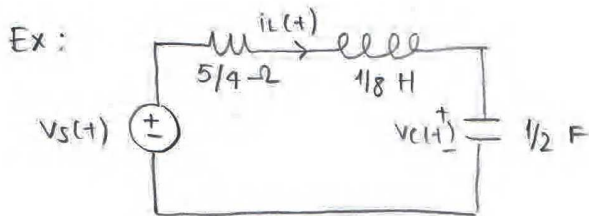- $\alpha > \omega_0 \rightarrow$  overdamped  $\gamma_1 e^{-\gamma_1 t} + \gamma_2 e^{-\gamma_2 t}$
- $\alpha = \omega_0 \rightarrow$  critically damped  $\gamma_1 e^{-\gamma_1 t} + \gamma_2 t e^{-\gamma_1 t}$
- $\alpha < \omega_0 \rightarrow$  underdamped  $\gamma_1 e^{-\alpha t} \cos \beta t + \gamma_2 e^{-\alpha t} \sin \beta t$



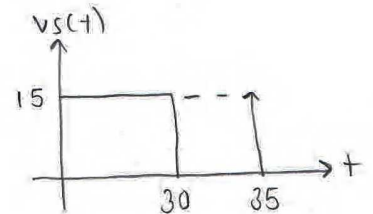$v_C(0^-) = -3V$   
 $i_L(0^-) = 0A$   
 Find  $v_C(t)$



$\alpha = 5$   $\omega_0 = 4$

short and preferred method

zi      zs

$(D^2 + 2\alpha D + \omega_0^2) i_C^z(t) = 0$   
 $\lambda^2 + 10\lambda + 16 = 0$   $\lambda = \{-2, -8\}$  overdamped

$v_C(t) = c_1 e^{-2t} + c_2 e^{-8t}$

$v_C(0^-) = -3V = c_1 + c_2$

$C \dot{v}_C(0^-) = I_L(0^-) = 0A$  ;

$c_1 + c_2 = -3$

$-2c_1 - 8c_2 = 0$

$c_1 = -4$   $c_2 = 1$


$v_C(t) = -4 e^{-2t} + e^{-8t}$

$v_C^{zs}(t) = ?$   
 $v_s(t) = 15(u(t) - u(t-30)) + 3\delta(t-35)$   
 $v_C^{zs} = 15(v_C^{step}(t) - v_C^{step}(t-30)) + 3v_C^{imp}(t-35)$   
 $v_C^{step}(t) = 1 + A e^{-2t} + B e^{-8t}$   
 $v_C(0^+) = 0V \rightarrow$  Equal to 0 values  
 $v_C^{step}(0^+) = 0V$   
 $A + B = -1$   
 $-2A - 8B = 0$   $A = -4/3$   $B = 1/3$   
 $v_C^{step}(t) = (1 - \frac{4}{3} e^{-2t} + \frac{1}{3} e^{-8t}) u(t)$

$h(t) = \frac{d}{dt} v_C^{step}(t) = \frac{v_C^{step}(t) \delta(t)}{v_C(0) \delta(t)} + (\frac{8}{3} e^{-2t} - \frac{8}{3} e^{-8t}) u(t)$


$h(t) = \frac{8}{3} (e^{-2t} - e^{-8t}) u(t)$

EX:

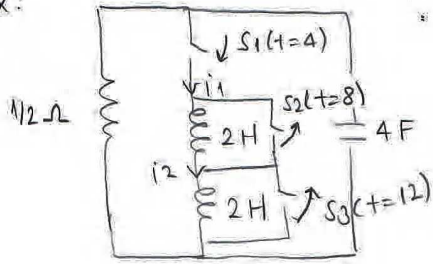

$S_1$  closes at  $t=4$  sec  
 $S_2$  opens at  $t=8$  sec  
 $S_3$  opens at  $t=12$  sec


$0 < t < 4$

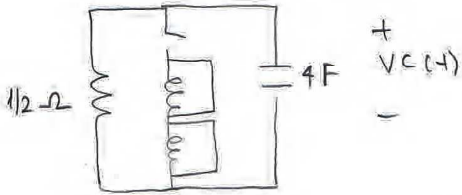

$$i_1(t) = i_1(0^-) + \frac{1}{L} \int_0^t V_{L1}(\tau) d\tau$$


$i_1(t) = 1A$   $i_2(t) = -2A$   $V_c(t) = 5e^{-t/2}$   $\tau = RC = 2sec$   
 $V_c(4^-) = 5e^{-2} V$

$4 < t < 8$

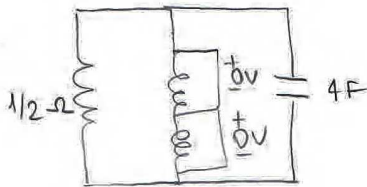


$V_c(4^+) \neq V_c(4^-)$   
 $V_c(4^+) = 0V$   
 $V_c(t) = 0$ ;  $4 < t < 8$

$8 < t < 12$

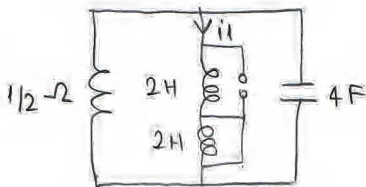

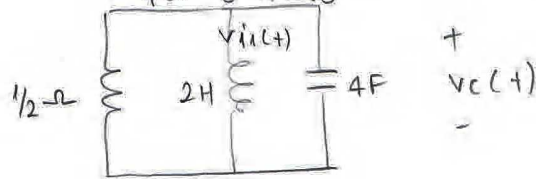$i_1(8^-) = 1A$   $V_c(8^-) = 0V$   $i_2(8^-) = -2A$   
 $i_1(8^+) = 1A$   $V_c(8^+) = 0V$   $i_2(8^+) = -2A$   
 since for  $8^- < t < 8^+$



$$\left( D^2 + \frac{1}{RC} D + \frac{1}{LC} \right) V_c(t) = 0$$

$V_c(8^+) = 0$   $V_c'(8^+) = -1$   $V_c''(8^+) = -1/4$

$\alpha = 1/4$   $\omega_0 = 1/2\sqrt{2}$   $\alpha < \omega_0$  Underdamped response

$8 < t < 12$


$\lambda_{1,2} = \left\{ \frac{1}{4} \mp j \frac{1}{4} \right\}$  Natural frequencies

$V_c(t) = e^{-(t-8)/4}$

$V_c(t) = e^{-(t-8)/4} \left( A \cos\left(\frac{t-8}{4}\right) + B \sin\left(\frac{t-8}{4}\right) \right) u(t-8)$  A, B to be found from I.C.

$$v_c(8^+) = 0 = A \quad \left. \begin{array}{l} \\ v_c'(8^+) = -\frac{1}{4} \end{array} \right\} \text{ solution } v_c(t) = \left[ -e^{-(t-8)/4} \sin\left(\frac{t-8}{4}\right) \right] u(t-8) \quad 8 < t < 12$$


$12 < t < \infty$

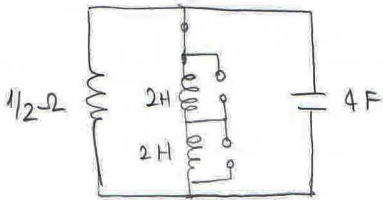

$i_1(12) \neq i_2(12)$  we apply conservation of flux  
 Total flux  $\rightarrow L_1 I_1(12^-) + L_2 I_2(12^-) = (L_1 + L_2) I_{\text{common}}(12^+)$   
 $-\frac{2}{e} - 4 = 4 I_{\text{common}}(12^+)$

$$I_{\text{common}}(12^+) = -1 - \frac{1}{2e}$$

$12 < t < \infty$

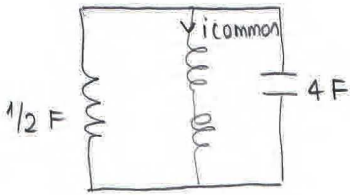


$$\alpha = 1/2RC = 1/4 \quad \left. \begin{array}{l} \\ \omega_0 = 1/\sqrt{LC} = 1/4 \end{array} \right\} \text{ critically damped}$$

$$(D^2 + 2\alpha D + \omega_0^2) v_c(t) = 0 \quad \lambda_{1,2} = \left\{ -1/4, -1/4 \right\}$$

$$v_c(t) = \left[ A e^{-(t-12)/4} + B (t-12) e^{-(t-12)/4} \right] u(t-12)$$

$$v_c(12) = -0.31 \text{ V}$$



at  $t = 12^+$

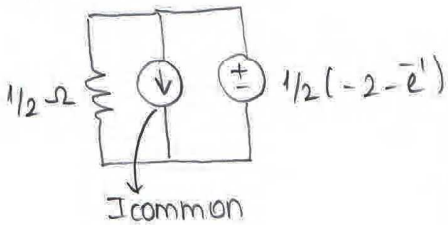

$$v_c'(12^+) = \frac{0.31}{1/2} + 1/2(2 + e^{-1})$$

Then A and B are found
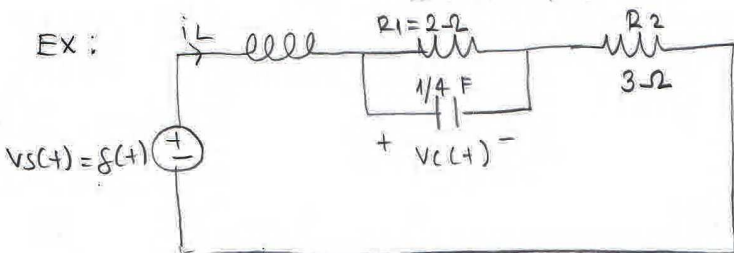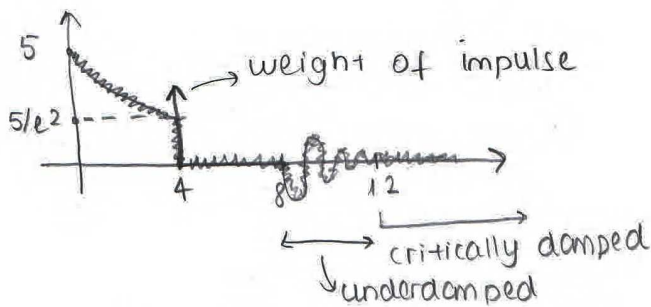
$$v_c(t) = e^{-(t-12)/4} \left[ -0.31 + 0.37(t-12) \right] u(t-12)$$



$i_L(0^-) = 0 \quad v_c(0^-) = 0$   
 Find  $v_c(t) \quad t > 0$

by KVL:  $-v_s(t) + L \frac{di_L(t)}{dt} + v_C(t) + R_2 i_L(t) = 0$

$i_L(t) = \frac{v_C(t)}{R_1} + C \frac{dv_C}{dt}$

$\frac{L}{R_1} v_C'' + C L v_C'' + v_C + \frac{R_2}{R_1} v_C + R_2 C v_C' = v_s(t)$

$v_C [ D^2 C L + D (\frac{L}{R_1} + R_2 C) + (\frac{R_2}{R_1} + 1) ] = v_s(t)$

$[ D^2 + (\frac{1}{R_1 C} + \frac{R_2}{L}) D + (\frac{R_2}{R_1} \frac{1}{L C} + \frac{1}{L C}) ] v_C(t) = v_s(t)$

$(D^2 + 5D + 10)v_C(t) = 4v_s(t)$


$D^2 + 2\alpha D + \omega_0^2 = 0 \quad \alpha = 2.5 \quad \omega_0 = \sqrt{10}$  Underdamped solution

$\lambda^2 + 2\alpha\lambda + \omega_0^2 = 0$

$-\alpha \pm \sqrt{\omega_0^2 - \alpha^2} = \lambda_{1,2} ; \quad \lambda_{1,2} = -\frac{5}{2} \pm j \sqrt{10 - \frac{25}{4}} = \frac{-5 \pm j\sqrt{15}}{2}$

$(D^2 + 2\alpha D + \omega_0^2)v_C(t) = 4\delta(t)$

$0^- < t < 0^+$

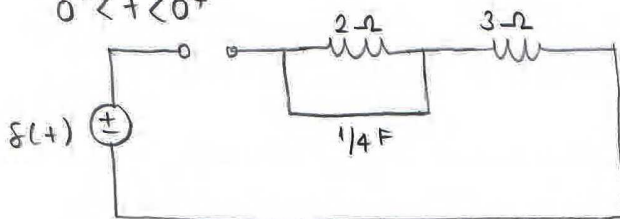


$i_L(t) = 0 \quad i_C(t) = 0$   
 $v_C(0^+) = v_C(0^-) + \frac{1}{C} \int_0^{0^+} 0 dt = 0$

$i_L(0^+) = i_L(0^-) + \frac{1}{L} \int_0^{0^+} \delta(t) dt = 1A$

$v_C(0^+) = 0V \quad \& \quad v_C'(0^+) = \frac{i_C(0^+)}{C}$

At  $t = 0^+$

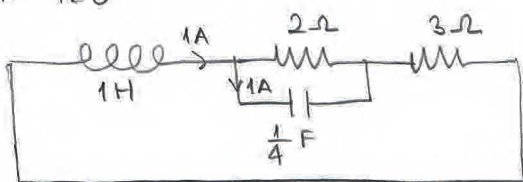

$2(1 - i_C(0^+)) = 0 ; \quad i_C(0^+) = 1A$

$v_C'(0^+) = \frac{1}{1/4} = 4 \text{ V/sec}$

$(D^2 + 5D + 10)v_C(t) = 0 \quad v_C(0^+) = 0 \quad v_C'(0^+) = 4$


$v_C(t) = e^{5/2 t} (c_1 \cos(\frac{\sqrt{15}}{2} t) + c_2 \sin(\frac{\sqrt{15}}{2} t))$

$v_C(0^+) = 0 = c_1$

$v_C'(0^+) = 4 ; \quad v_C(t) = e^{(5/2)t} \frac{8}{\sqrt{15}} \sin(\frac{\sqrt{15}}{2} t)$

$c_2 = \frac{8}{\sqrt{15}}$

ZPS VII, 12:

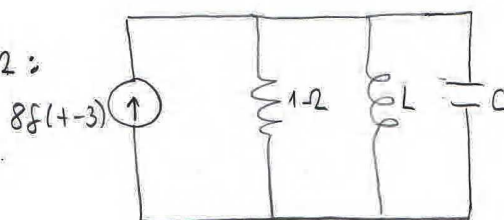

$v_C(3^+) = 1V$

The response is critically damped ( $\alpha = \omega_0$ )

$i_L(0^-) = 0 \quad v_C(0^-) = 0$


$\alpha = 1/2RC \quad \omega_0 = \sqrt{1/LC}$

$(\frac{1}{2C})^2 = \frac{1}{LC} \quad L = 4C$



$$\left(D^2 + \frac{1}{RC}D + \frac{1}{LC}\right)V_C(t) = \frac{1}{C} \frac{d}{dt} i_S(t)$$

$$3^- < t < 3^+$$

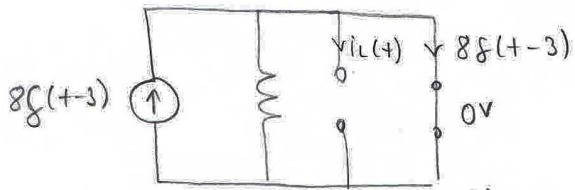

$$i_L(3^-) = 0 \quad V_L(3^-) = 0V$$

$$V_C(3^+) = V_C(3^-) + \frac{1}{C} \int_{3^-}^{3^+} 8\delta(t-3) dt = \frac{8}{C} = 1V$$

$$C = 8F \quad L = 32H$$

$$V_C(t) = c_1 e^{\lambda(t-3)} + c_2 e^{\lambda(t-3)}$$

$$V_C(3^+) = c_1 + 0 = 1 \quad c_1 = 1$$

$$V_C'(t) = c_1 \lambda e^{\lambda(t-3)} + c_2 (t-3) \lambda e^{\lambda(t-3)}$$

$$\left(D^2 + \frac{1}{8}D + \frac{1}{256}\right) = \left(D + \frac{1}{16}\right)^2 \quad \lambda = -1/16$$

$$-\frac{1}{16} + 0 + c_2 = -\frac{1}{8} \quad c_2 = -\frac{1}{16} \quad c_1 = 1$$

$$V_C(t) = e^{-\frac{1}{16}(t-3)} - \frac{1}{16} e^{-\frac{1}{16}(t-3)} \quad \text{for } t > 3$$