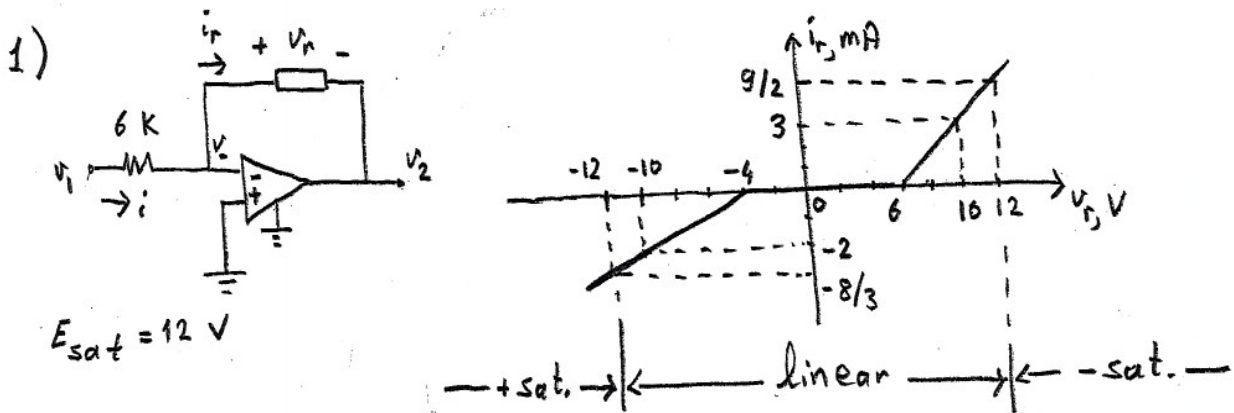


# On the Third Midterm Examination (Fall 2012)



The voltages are in volts; the currents are in milliamperes.

$$v_+ = 0, \quad i = i_r, \quad i_r = f(v_r); \quad v_1 = 6i + v_r, \quad v_r = v_- - v_2$$

$$f(v_r): \quad i_r = \begin{cases} \frac{1}{3}(v_r + 4), & v_r < -4 \\ 0, & -4 \leq v_r \leq 6 \\ \frac{3}{4}(v_r - 6), & v_r > 6 \end{cases}$$

linear region:  $v_- = 0, |v_2| \leq 12\text{ V}$

$$v_1 = 6i, \quad v_r = -v_2 \Rightarrow \boxed{i = v_1/6}, \quad |v_r| \leq 12\text{ V}; \quad \boxed{\frac{v_1}{6} = f(-v_2)}$$

$$v_r = 12\text{ V} \Rightarrow i_r = 9/2\text{ mA}, \quad v_1 = 27\text{ V}; \quad v_r = -12\text{ V} \Rightarrow i_r = -8/3\text{ mA}, \quad v_1 = -16\text{ V}$$

$$-\frac{8}{3} \leq i \leq \frac{9}{2}, \quad \boxed{-16 \leq v_1 \leq 27}$$

+ saturation region:  $v_- < 0, v_2 = 12\text{ V}$

$$v_1 < 6i, \quad v_r < -12\text{ V} \Rightarrow i_r < -8/3\text{ mA}, \quad \boxed{v_1 < -16\text{ V}}$$

$$\boxed{\begin{aligned} v_1 &= 6i + v_r + 12 \\ i &= f(v_r) \end{aligned}}$$

- saturation region:  $v_- > 0, v_2 = -12\text{ V}$

$$v_1 > 6i, \quad v_r > 12\text{ V} \Rightarrow i_r > 9/2\text{ mA}, \quad \boxed{v_1 > 27\text{ V}}$$

$$\boxed{\begin{aligned} v_1 &= 6i + v_r - 12 \\ i &= f(v_r) \end{aligned}}$$


Transfer characteristic:

linear region:

$$-12 \leq v_r < -4 \quad (4 < v_2 \leq 12) : \frac{v_1}{6} = \frac{1}{3}(-v_2 + 4) \Rightarrow v_2 = -\frac{1}{2}v_1 + 4 \quad (-16 \leq v_1 < 0)$$

$$-4 \leq v_r \leq 6 \quad (-6 \leq v_2 \leq 4) : \frac{v_1}{6} = 0 \Rightarrow v_1 = 0$$
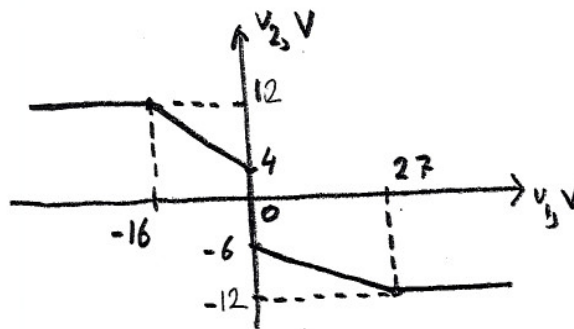
$$6 < v_r \leq 12 \quad (-12 \leq v_2 < -6) : \frac{v_1}{6} = \frac{3}{4}(-v_2 - 6) \Rightarrow v_2 = -\frac{2}{3}v_1 - 6 \quad (0 < v_1 \leq 27)$$




Input characteristic:

+ saturation region:


$$v_1 = 6i + (3i - 4) + 12 = 9i + 8 \Rightarrow i = \frac{1}{9}v_1 - \frac{8}{9}$$

- saturation region:
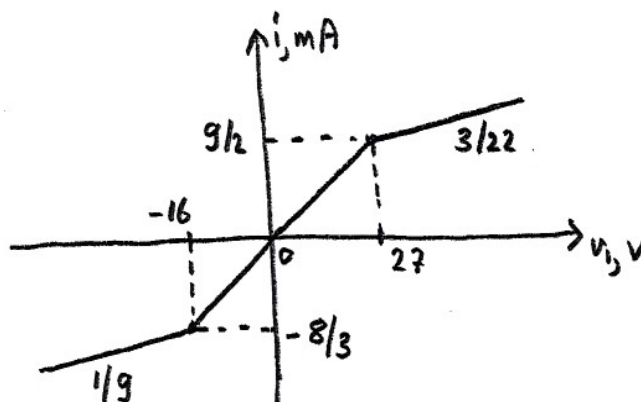
$$v_1 = 6i + \left(\frac{4}{3}i + 6\right) - 12 = \frac{22}{3}i - 6 \Rightarrow i = \frac{3}{22}v_1 + \frac{9}{11}$$



2)

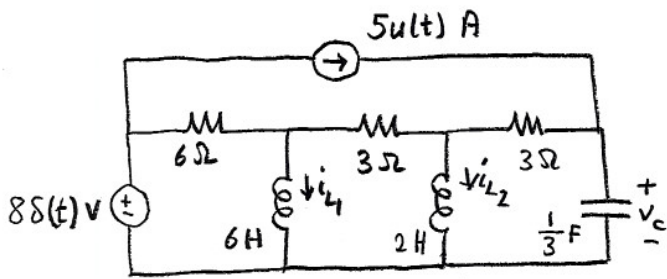

$$\begin{aligned} v_C(0^-) &= -4 \text{ V} \\ i_{L1}(0^-) &= 1 \text{ A} \\ i_{L2}(0^-) &= 3 \text{ A} \end{aligned}$$

For a LTI capacitor:  $v_C(t_1^+) = v_C(t_1^-) + \frac{1}{C} \int_{t_1^-}^{t_1^+} i(t) dt$


If  $i(t)$  is bounded at  $t=t_1$ , i.e., either  $i(t)$  is continuous at  $t_1$  or has a jump discontinuity at  $t_1$ , then  $\int_{t_1^-}^{t_1^+} i(t) dt = 0$  and  $v_C(t_1^+) = v_C(t_1^-)$ , i.e.,  $v_C(t)$  is continuous at  $t_1$ .

If  $i(t)$  is impulsive at  $t=t_1$ :  $i(t) = K\delta(t-t_1) + i'(t)$ , where  $i'(t)$  is bounded at  $t_1$

$\int_{t_1^-}^{t_1^+} (K\delta(t-t_1) + i'(t)) dt = K \Rightarrow v_C(t_1^+) = v_C(t_1^-) + \frac{K}{C}$ , i.e.,  $v_C(t)$  has a jump discontinuity at  $t_1$ , the jump amount is  $K/C$ .

If the capacitor is full, then  $q_C$  is constant and  $i = \frac{dq_C}{dt} = 0$ , i.e., the capacitor behaves like an open circuit.

For a LTI inductor: The dual case.

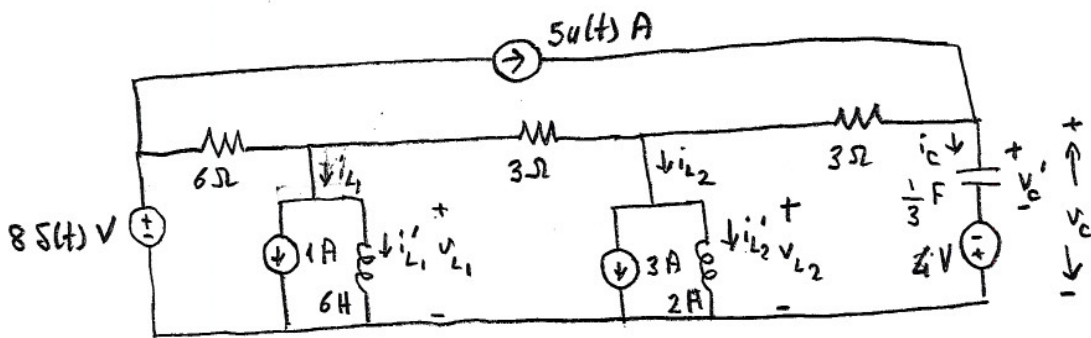

$$\begin{aligned} v_C'(0^-) &= 0 \\ i_{L1}'(0^-) &= 0 \\ i_{L2}'(0^-) &= 0 \end{aligned}$$


Let  $x(t)$  denote any current or voltage. Write

$$x(t) = x_1(t) + x_2(t) + x_3(t)$$

$\left. \begin{array}{l} \uparrow \text{due to the impulse source} \\ \uparrow \text{due to the step source} \end{array} \right\}$  the zero-state solution  
 $\left. \begin{array}{l} \uparrow \text{due to the constant sources} \\ \text{(initial conditions)} \end{array} \right\}$  the zero-input solution

$x_1(t)$  and  $x_2(t)$  are bounded.

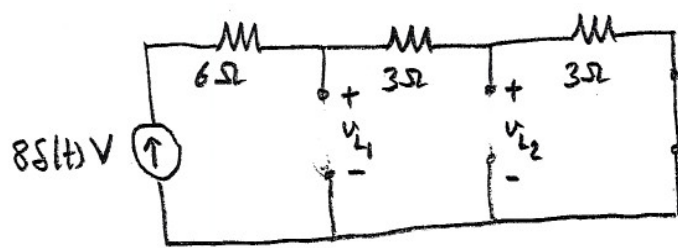For  $x_3(t)$ , set the initial conditions to zero (kill the constant sources) and kill the step source. Replace the inductors with open circuits (zero initial currents) and the capacitor with a short circuit (zero initial voltage).



$$i_c = \frac{8S(t)}{6+3+3} = \frac{2}{3} S(t) \text{ A}$$


$$v_{L2} = 3i_c = 2S(t) \text{ V}$$

$$v_{L1} = (3+3)i_c = 4S(t) \text{ V}$$

Hence  $v_{c3}(0^+) = \frac{2/3}{1/3} = 2 \text{ V}$ ,  $i_{L1}(0^+) = \frac{4}{6} = \frac{2}{3} \text{ A}$ ,  $i_{L2}(0^+) = \frac{2}{2} = 1 \text{ A}$ .


Then  $v_c(0^+) = -4 + 2 = -2 \text{ V}$ ,  $i_{L1}(0^+) = 1 + \frac{2}{3} = \frac{5}{3} \text{ A}$ ,  $i_{L2}(0^+) = 3 + 1 = 4 \text{ A}$

For  $t > 0$ :

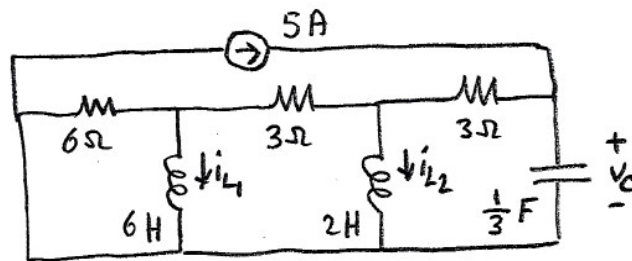


The circuit is passive. The input is constant.

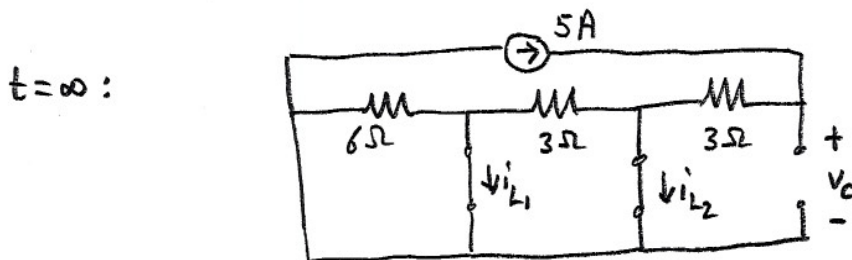At  $t = \infty$ , the capacitor and the inductors are full. Then




$$i_{L2} = 5 \text{ A}, i_{L1} = 0, v_c = 3 \times i_{L2} = 15 \text{ V}$$

3)

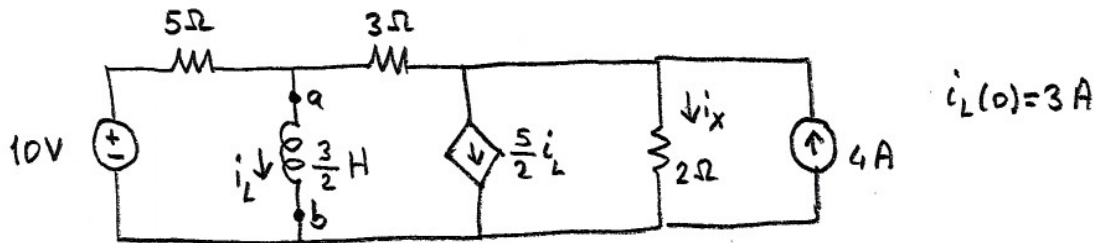

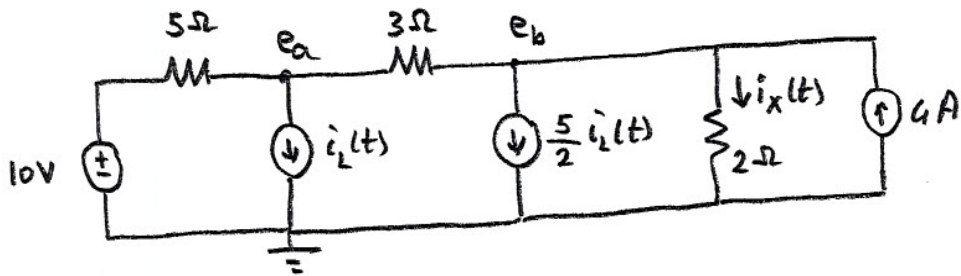Suppose that  $i_L(t)$  is known. Replacing the inductor with an independent current source of current  $i_L(t)$ ,



Solving this circuit,  $i_x(t)$  is determined.

Method 1: Node analysis

$$\left. \begin{aligned} \frac{e_a - 10}{5} + i_L + \frac{e_a - e_b}{3} &= 0 \\ \frac{e_b - e_a}{3} + \frac{5}{2} i_L + \frac{e_b}{2} - 4 &= 0 \end{aligned} \right\} \begin{bmatrix} 8/15 & -1/3 \\ -1/3 & 5/6 \end{bmatrix} \begin{bmatrix} e_a \\ e_b \end{bmatrix} = \begin{bmatrix} 2 - i_L \\ 4 - \frac{5}{2} i_L \end{bmatrix}$$

$$\begin{bmatrix} e_a \\ e_b \end{bmatrix} = \frac{1}{1/3} \begin{bmatrix} 5/6 & 1/3 \\ 1/3 & 8/15 \end{bmatrix} \begin{bmatrix} 2 - i_L \\ 4 - \frac{5}{2} i_L \end{bmatrix} \Rightarrow e_b = 2 - i_L + \frac{8}{5} \left( 4 - \frac{5}{2} i_L \right) = \frac{42}{5} - 5i_L$$

$$i_x = e_b / 2 = \frac{21}{5} - \frac{5}{2} i_L$$


Method 2: Superposition

$$i_x = \frac{10}{5+3+2} - \frac{5}{5+3+2} i_L + \frac{5+3}{5+3+2} \left( 4 - \frac{5}{2} i_L \right)$$


$$= 1 - \frac{1}{2} i_L + \frac{4}{5} \left( 4 - \frac{5}{2} i_L \right) = \frac{21}{5} - \frac{5}{2} i_L$$

Determination of  $i_L(t)$ :

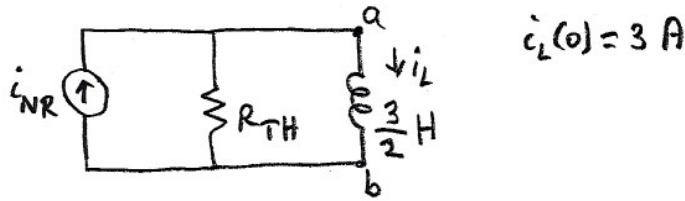Obtain the Norton (or the Thevenin) equivalent of the one-port as seen by the inductor.




$v_{TH}$  (or  $v_{oc}$ ):

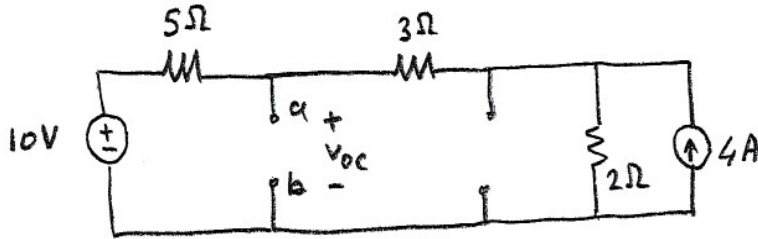

$$v_{oc} = (3+2) \frac{10}{5+3+2} + 5 \cdot \frac{2}{5+3+2} \cdot 4 = 5 + 4 = 9 \text{ V}$$

$i_{NR}$  (or  $i_{sc}$ ):

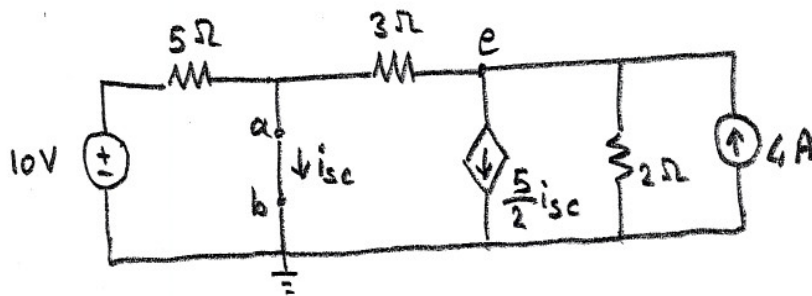

$$i_{sc} = \frac{10}{5} + \frac{e}{3} = \frac{1}{3}e + 2$$


$$\frac{e}{3} + \frac{5}{2}i_{sc} + \frac{e}{2} - 4 = 0 \Rightarrow \left(\frac{1}{3} + \frac{1}{2} + \frac{5}{2} \cdot \frac{1}{3}\right)e = 4 - \frac{5}{2} \cdot 2$$

$$\frac{5}{3}e = -1 \Rightarrow e = -\frac{3}{5} \text{ V}$$

$$i_{sc} = -\frac{1}{5} + 2 = \frac{9}{5} \text{ A}$$

$$R_{TH} = \frac{v_{oc}}{i_{sc}} = \frac{9}{9/5} = 5 \Omega$$

Note

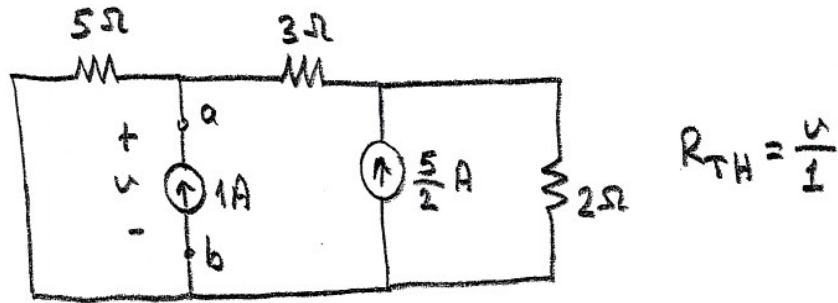


$$V = 5 \frac{3+2}{3+2+5} \cdot 1 + 5 \frac{2}{2+3+5} \frac{5}{2} = \frac{5}{2} + \frac{5}{2} = 5 \text{ V} \Rightarrow R_{TH} = 5 \Omega.$$


$$i_L(+\infty) = \frac{9}{5} \text{ A}, \quad \tau = \frac{3/2}{R_{TH}} = \frac{3}{10} \text{ sec}$$

$$i_L(t) = \frac{9}{5} + \underbrace{\left(3 - \frac{9}{5}\right)}_{6/5} e^{-10t/3} \text{ A}, \quad t \geq 0$$
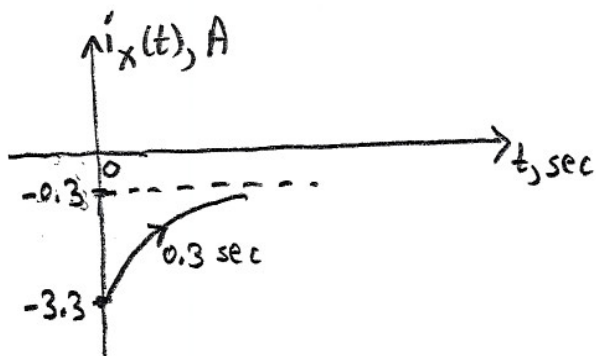
$$i_x(t) = \frac{21}{5} - \frac{5}{2} \left( \frac{9}{5} + \frac{6}{5} e^{-10t/3} \right) = \frac{21}{5} - \frac{9}{2} - 3 e^{-10t/3}$$
$$= -\frac{3}{10} - 3 e^{-10t/3} \text{ A}, \quad t \geq 0$$



4)

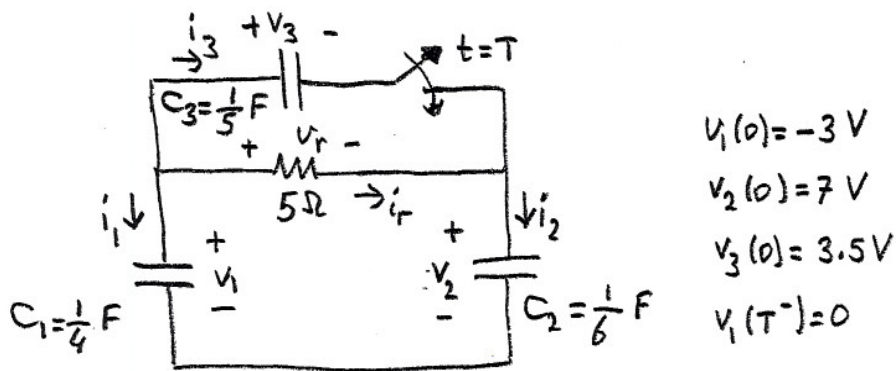

$$\begin{aligned} V_1(0) &= -3 \text{ V} \\ V_2(0) &= 7 \text{ V} \\ V_3(0) &= 3.5 \text{ V} \\ V_1(T^-) &= 0 \end{aligned}$$


Study the circuit in three parts:  $0 \leq t < T$ ,  $t: T^- \rightarrow T^+$ ,  $t > T$ .

$0 \leq t < T$

$i_3 = 0$  (the switch is open),  $v_3 = 3.5 \text{ V}$

$C_1$  and  $C_2$  are in series; the equivalent capacitance  $C'$  is
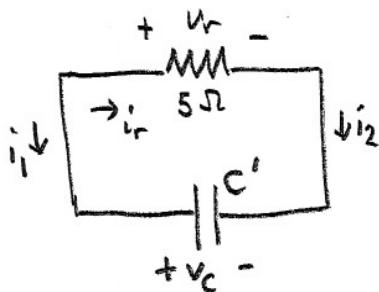
$$\frac{1}{C'} = \frac{1}{1/4} + \frac{1}{1/6} = 4 + 6 = 10 \Rightarrow C' = \frac{1}{10} \text{ F}$$



$$V_c = V_1 - V_2$$

$$V_c(0) = -3 - 7 = -10 \text{ V}$$

$$\tau_1 = 5 \times C' = \frac{1}{2} \text{ sec}$$

$$V_c(t) = -10 e^{-2t} \text{ V}$$


Method 1:  $i_r = V_c/5 = -2 e^{-2t} \text{ A}$ ,  $i_1 = -i_r$ ,  $i_2 = i_r$

$$V_1(t) = -3 + \frac{1}{1/4} \int_0^t (2 e^{-2t'}) dt' = -3 + 4(-e^{-2t'}) \Big|_0^t = -3 + 4(1 - e^{-2t}) = 1 - 4e^{-2t} \text{ V}$$

$$V_2(t) = 7 + \frac{1}{1/6} \int_0^t (-2 e^{-2t'}) dt' = 7 + 6(e^{-2t'}) \Big|_0^t = 7 + 6(e^{-2t} - 1) = 1 + 6e^{-2t} \text{ V}$$



Method 2:

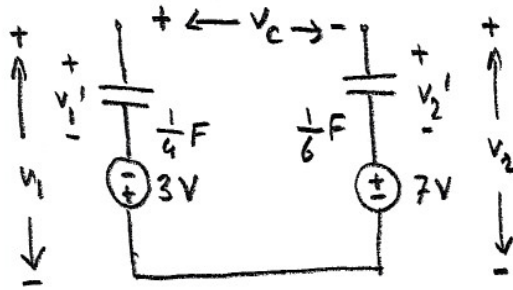

$$v_1'(0) = 0, v_2'(0) = 0$$

$$v_1' = \frac{\frac{1}{6}}{\frac{1}{6} + \frac{1}{4}} (v_c + (3+7)) = \frac{2}{5} (v_c + 10) = \frac{2}{5} v_c + 4$$

$$v_2' = -\frac{\frac{1}{4}}{\frac{1}{4} + \frac{1}{6}} (v_c + (3+7)) = -\frac{3}{5} (v_c + 10) = -\frac{3}{5} v_c - 6$$

$$v_1(t) = v_1'(t) - 3 = \frac{2}{5} v_c(t) + 1 = 1 - 4e^{-2t} \text{ V}$$


$$v_2(t) = v_2'(t) + 7 = -\frac{3}{5} v_c + 1 = 1 + 6e^{-2t} \text{ V}$$

$$\text{Note: } v_2 = v_1 - v_c = (1 - 4e^{-2t}) - (-10e^{-2t}) \text{ V}$$

$$v_1(T^-) = 0 : 1 - 4e^{-2T} = 0 \Rightarrow e^{-2T} = \frac{1}{4} \Rightarrow e^{2T} = 4 \Rightarrow T = \frac{1}{2} \ln 4 = \ln 2 \text{ sec}$$

$$v_2(T^-) = 1 + 6e^{-2T} = 1 + \frac{6}{4} = 2.5 \text{ V}$$

t: T^- \to T^+

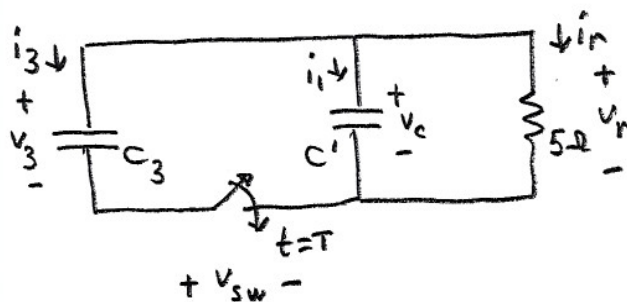

$$v_3(T^-) = 3.5 \text{ V}, v_c(T^-) = 0 - 2.5 = -2.5 \text{ V}$$

$$v_3(T^+) = v_c(T^+) = V_0$$

$$v_3(T^-) \neq v_c(T^-) \Rightarrow i_3 = -i_1 \text{ is impulsive at } t=T$$

$$i_3(t) = K \delta(t-T) + i_3'(t)$$

↑ bounded at t=T

$$V_0 = \frac{C_3 v_3(T^-) + C' v_c(T^-)}{C_3 + C'} = \frac{\frac{1}{5} 3.5 + \frac{1}{10} (-2.5)}{\frac{1}{5} + \frac{1}{10}} = 1.5 \text{ V}$$

$$v_3(T^+) = 3.5 + \frac{1}{1/5} \int_{T^-}^{T^+} i_3(t) dt = 3.5 + 5K = V_0 = 1.5 \Rightarrow K = -\frac{2}{5}$$

Note:  $v_c(T^+) = -2.5 + \frac{1}{1/10} \int_{T^-}^{T^+} (-i_3(t)) dt = -2.5 - 10K$

$$v_3(T^+) = v_c(T^+) \Rightarrow 3.5 + 5K = -2.5 - 10K \Rightarrow 15K = -6 \Rightarrow K = -\frac{2}{5}$$

$$v_3(T^+) = v_c(T^+) = 3.5 + 5(-\frac{2}{5}) = 1.5 \text{ V}$$

$$v_1(T^+) = 0 + \frac{1}{1/4} \int_{T^-}^{T^+} (-i_3(t)) dt = -4K = 8/5 \text{ V}$$

$$v_2(T^+) = 2.5 + \frac{1}{1/6} \int_{T^-}^{T^+} i_3(t) dt = 2.5 + 6K = 1/10 \text{ V}$$

$$\left\{ v_2(T^+) = v_1(T^+) - V_0 = 1.6 - 1.5 = 0.1 \text{ V} \right\}$$

$t > T$

$C_3$  and  $C'$  are in parallel; the equivalent capacitance  $C''$  is




$$C'' = C_3 + C' = \frac{1}{5} + \frac{1}{10} = \frac{3}{10} \text{ F}$$

$$\tau_2 = 5 \cdot C'' = 3/2 \text{ sec}$$

$$v_c(t) = v_3(t) = 1.5 e^{-\frac{2}{3}(t-T)} \text{ V}$$

$$v_1(t) = \frac{\frac{1}{6}}{\frac{1}{6} + \frac{1}{4}} (v_c - 1.5) + 1.6 = \frac{2}{5} (v_c - 1.5) + 1.6 = \frac{2}{5} v_c + 1 = 1 + 0.6 e^{-\frac{2}{3}(t-T)} \text{ V}$$
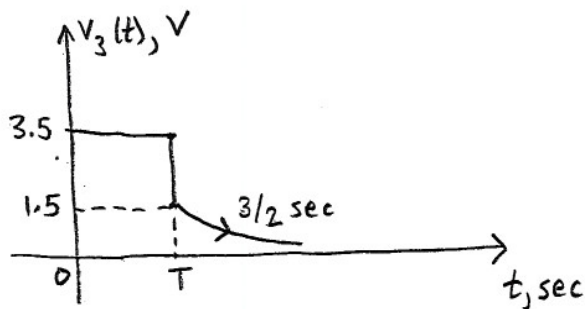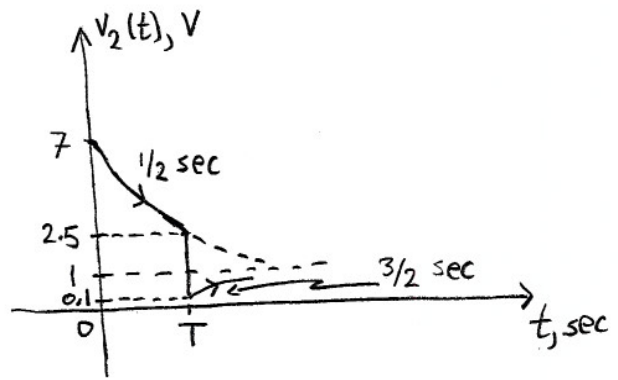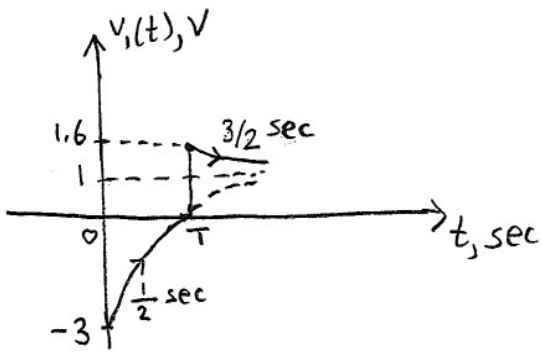
$$v_2(t) = -\frac{\frac{1}{4}}{\frac{1}{4} + \frac{1}{6}} (v_c - 1.5) + 0.1 = -\frac{3}{5} (v_c - 1.5) + 0.1 = -\frac{3}{5} v_c + 1 = 1 - 0.9 e^{-\frac{2}{3}(t-T)} \text{ V}$$



### Energy Considerations:

The energy delivered to the resistor on  $[0, T)$ :

$$W_r [0, T) = \int_0^T 5 i_r^2 dt = 20 \int_0^T e^{-4t} dt = -5 e^{-4t} \Big|_0^T = 5 (1 - \frac{e^{-4T}}{\sqrt{\frac{1}{4}}}) = \frac{75}{16} \text{ J}$$

The energy delivered to the resistor on  $(T, +\infty)$ :

$$W_r (T, +\infty) = \int_T^{+\infty} \frac{1}{5} v_c^2 dt = \frac{9}{20} \int_T^{+\infty} e^{-\frac{4}{3}(t-T)} dt = \frac{9}{20} \int_0^{+\infty} e^{-\frac{4}{3}t'} dt'$$

$$= -\frac{27}{80} e^{-\frac{4}{3}t'} \Big|_0^{+\infty} = \frac{27}{80} \text{ J}$$

The sum of the stored energies in  $C_1$  and  $C_2$

$$\text{at } t=0: e_a(0) = \frac{1}{2} \frac{1}{4} (-3)^2 + \frac{1}{2} \frac{1}{6} (7^2) = \frac{9}{8} + \frac{49}{12} = \frac{125}{24} \text{ J}$$

$$\text{at } t=T^-: e_a(T^-) = \frac{1}{2} \frac{1}{4} (0)^2 + \frac{1}{2} \frac{1}{6} (2.5)^2 = \frac{25}{48} \text{ J}$$

The sum of the stored energies in  $C_1, C_2$  and  $C_3$

$$\text{at } t=T^-: e_b(T^-) = \frac{25}{48} + \frac{1}{2} \frac{1}{5} (3.5)^2 = \frac{419}{240} \text{ J}$$

$$\text{at } t=T^+: e_b(T^+) = \frac{1}{2} \frac{1}{4} (1.6)^2 + \frac{1}{2} \frac{1}{6} (0.1)^2 + \frac{1}{2} \frac{1}{5} (1.5)^2 = \frac{131}{240} \text{ J}$$

$$\text{at } t=\infty: e_b(\infty) = \frac{1}{2} \frac{1}{4} (1)^2 + \frac{1}{2} \frac{1}{6} (1)^2 + \frac{1}{2} \frac{1}{5} (0)^2 = \frac{5}{24} \text{ J}$$

$$e_a(0) - e_a(T^-) = \frac{125}{24} - \frac{25}{48} = \frac{75}{16} \text{ J} \leftarrow W_r(0, T)$$

$$e_b(T^+) - e_b(\infty) = \frac{131}{240} - \frac{5}{24} = \frac{27}{80} \text{ J} \leftarrow W_r(T, \infty)$$



The energy given to the switch:

$$v_{sw}(T^-) = v_c(T^-) - v_3(T^-) = (0 - 2.5) - 3.5 = -6 \text{ V}, \quad v_{sw}(T^+) = 0$$

$$W_{sw} = \int_{T^-}^{T^+} \frac{(-6)+0}{2} i_3(t) dt = -3 \text{ K} = 1.2 \text{ J}$$


$$e_b(T^-) - e_b(T^+) = \frac{419}{240} - \frac{131}{240} = 1.2 \text{ J} \leftarrow W_{sw}$$

5)

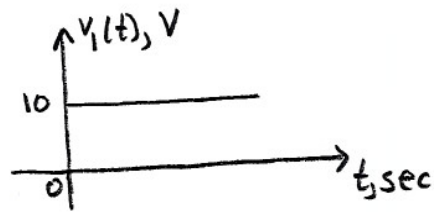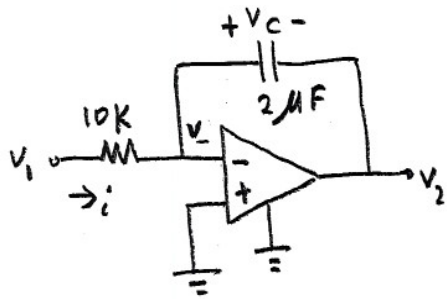

$E_{sat} = 15V, v_c(0^-) = -20V$

$t > 0$ :

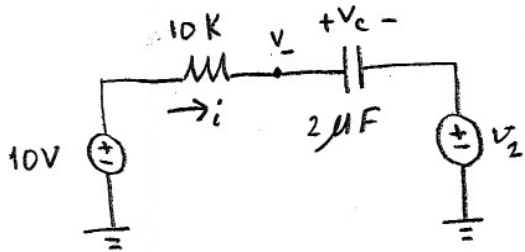

Preliminaries:

linear region:  $v_- = 0, |v_2| \leq 15V$

$$i = \frac{10}{10^4} = 10^{-3} A, \quad v_c(t) = v_c(t_0) + \frac{1}{2 \times 10^{-6}} \int_{t_0}^t 10^{-3} dt' = v_c(t_0) + 500(t - t_0)$$

+ saturation region:  $v_- < 0, v_2 = 15V$

$$\tau = 10^4 \times 2 \times 10^{-6} = 0.02 \text{ sec} \approx 20 \text{ msec}$$

$$v_c(t) = +5 + (v_c(t_1) + 5)e^{-(t-t_1)/\tau}, \quad v_-(t) = 10 + (v_c(t_1) + 5)e^{-(t-t_1)/\tau}$$

- saturation region:  $v_- > 0, v_2 = -15V$

$$v_c(t) = 25 + (v_c(t_2) - 25)e^{-(t-t_2)/\tau}, \quad v_-(t) = 10 + (v_c(t_2) - 25)e^{-(t-t_2)/\tau}$$

$$v_c(0^+) = -20V \Rightarrow v_-(0^+) = -20 + v_2$$

linear?  $v_-(0^+) = -20 + v_2 = 0 \quad \times$

+ sat?  $v_-(0^+) = -20 + 15 = -5 < 0 \quad \checkmark$

- sat?  $v_-(0^+) = -20 - 15 = -35 > 0 \quad \times$

At  $t=0^+$ , the op-amp is in the + saturation region.

$0 \leq t \leq T_1$  (+ sat)

$$v_c(t) = -5 + (-20+5)e^{-t/\tau} = -5 - 15e^{-50t} \text{ V}$$

$$v_-(t) = 10 - 15e^{-50t} \text{ V}; \quad v_-(T_1) = 0 \Rightarrow 10 - 15e^{-50T_1} \Rightarrow e^{50T_1} = 1.5 \Rightarrow T_1 = \frac{1}{50} \ln(1.5) \text{ sec}$$

$$v_c(T_1) = -15 \text{ V}$$

$T_1 \leq t \leq T_2$  (linear)

$$v_c(t) = -15 + 500(t - T_1) \text{ V}$$

$$v_2(t) = -v_c(t), \quad v_c(T_2) = -15 = 15 - 500(T_2 - T_1) \Rightarrow T_2 = T_1 + \frac{3}{50} \text{ sec}$$

$$v_c(T_2) = 15 \text{ V}$$

$t > T_2$  (- sat)

$$v_c(t) = 25 + (15 - 25)e^{-(t-T_2)/\tau} = 25 - 10e^{-50(t-T_2)} \text{ V}$$

$$v_-(t) = 10 - 10e^{-50(t-T_2)} \text{ V}$$

