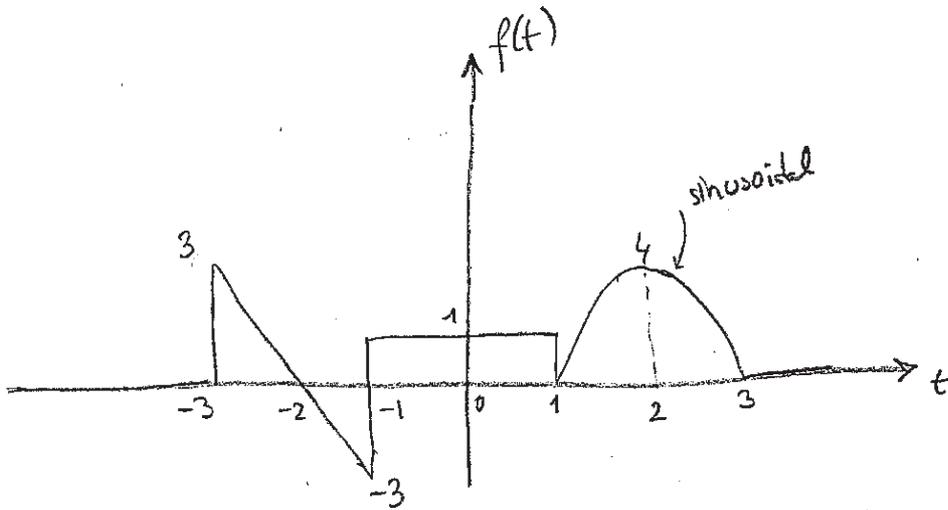


Example:




Write  $f(t)$  and determine  $f'(t)$ , both graphically & analytically.

Soln: Define  $p(t; a, b) = u(t-a) - u(t-b)$ , which is 1 for  $a < t < b$  and zero elsewhere.

$$f(t) = (-3t-6) p(t; -3, -1) + p(t; -1, 1) + 4 \sin\left(\frac{\pi}{2}(t-1)\right) p(t; 1, 3)$$

$$= (-3t-6) [u(t+3) - u(t-1)] + [u(t+1) - u(t-1)]$$
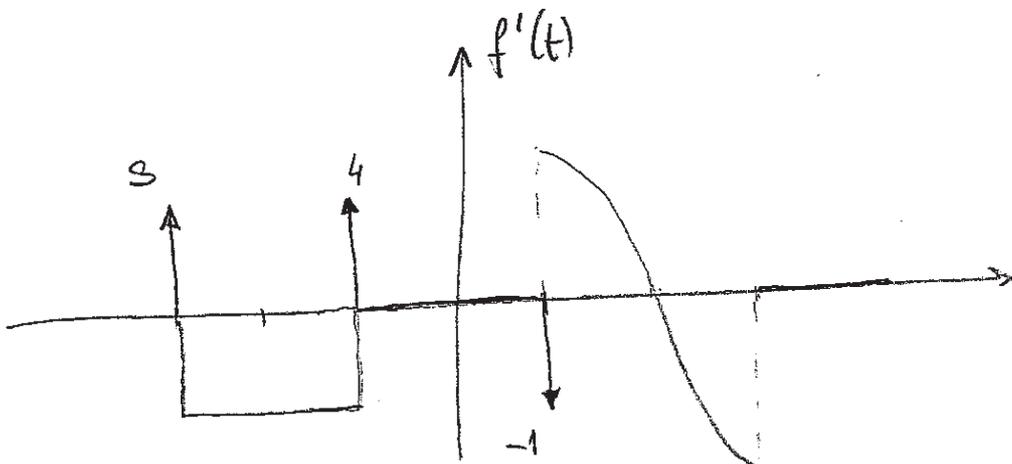
$$+ 4 \sin\left(\frac{\pi}{2}(t-1)\right) [u(t-1) - u(t-3)]$$



Analytically, we have

(2)

$$f'(t) = (-3) p(t; -3, -1) + (-3t-6) p'(t; -3, -1) + p'(t; -1, 1) \\ + \frac{4\pi}{2} \cos\left(\frac{\pi}{2}(t-1)\right) p(t; 1, 3) + 4 \sin\left(\frac{\pi}{2}(t-1)\right) p'(t; 1, 3)$$

Note that

$$p'(t; a, b) = [u(t-a) - u(t-b)]' = \delta(t-a) - \delta(t-b)$$

Then:

$$f'(t) = -3 [u(t+3) - u(t-1)] + \overbrace{(-3t-6) \delta(t+3)}^{3\delta(t+3)} - \overbrace{(-3t-6) \delta(t+1)}^{3\delta(t+3)} \\ + \delta(t+1) - \delta(t-1) + \frac{4\pi}{2} \cos\left(\frac{\pi}{2}(t-1)\right) [u(t-1) - u(t-3)] \\ + \underbrace{4 \sin\left(\frac{\pi}{2}(t-1)\right) \delta(t-1)}_0 + \underbrace{4 \sin\left(\frac{\pi}{2}(t-1)\right) \delta(t-3)}_0$$

Remembering that


$$f(t) \delta(t-a) = f(a) \delta(t-a)$$

we can write:

$$f'(t) = -3 [u(t+3) - u(t-1)] + 2\pi \cos\left(\frac{\pi}{2}(t-1)\right) [u(t-1) - u(t-3)] \\ + 3\delta(t+3) + 4\delta(t+1) - \delta(t-1)$$

Example: (2PS V, 6c)


(3)

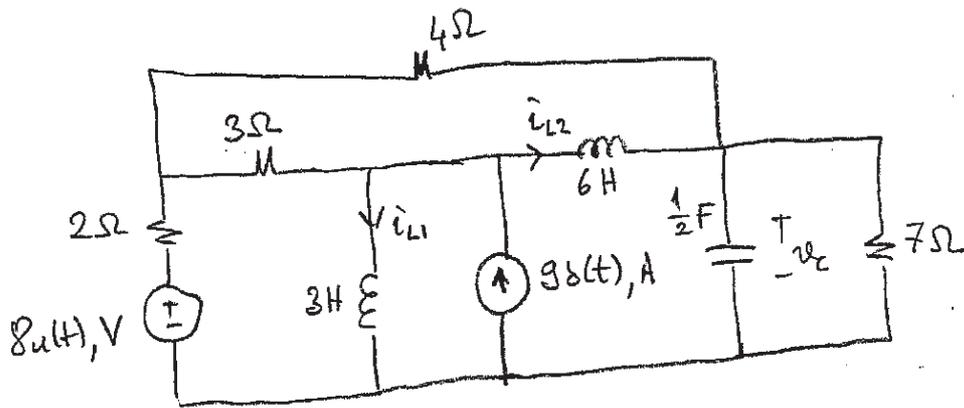

$$v_c(0^-) = 6V, \quad i_{L1}(0^-) = 3A, \quad i_{L2}(0^-) = 6A$$

Find  $v_c(0^+)$ ,  $i_{L1}(0^+)$ ,  $i_{L2}(0^+)$ ,  $v_c(\infty)$ ,  $i_{L1}(\infty)$ ,  $i_{L2}(\infty)$ .

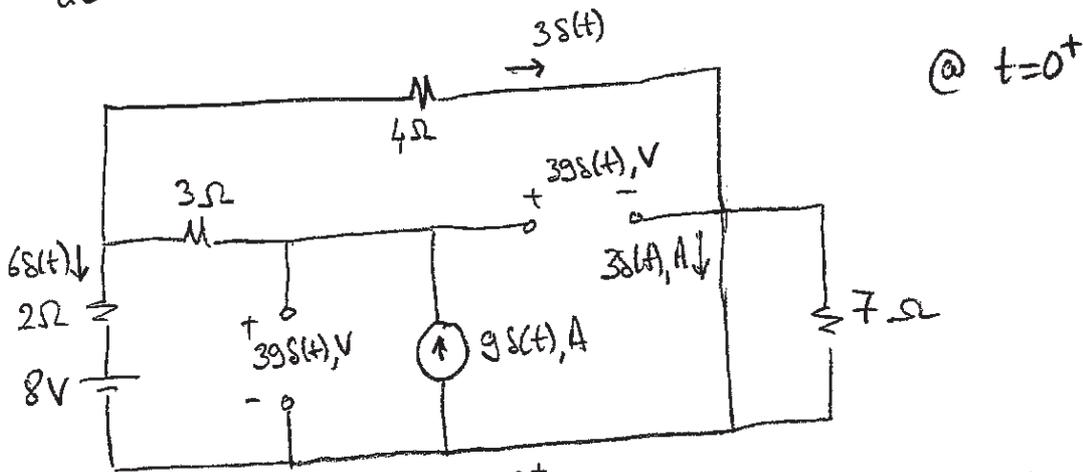Soln: Assume all initial values are zero. The step voltage input does not cause a jump in state variables. However, for the impulse we can draw the following equivalent at  $t=0^+$




$$v_c(0^+) = v_c(0^-) + \frac{1}{C} \int_{0^-}^{0^+} 3\delta(t) dt = 6 + 2 \cdot 3 = 12V$$

$$i_{L1}(0^+) = i_{L1}(0^-) + \frac{1}{L_1} \int_{0^-}^{0^+} 39\delta(t) dt = 3 + \frac{39}{3} = 16A$$

$$i_{L2}(0^+) = i_{L2}(0^-) + \frac{1}{L_2} \int_{0^-}^{0^+} 3\delta(t) dt = 6 + \frac{39}{6} = 12.5A$$

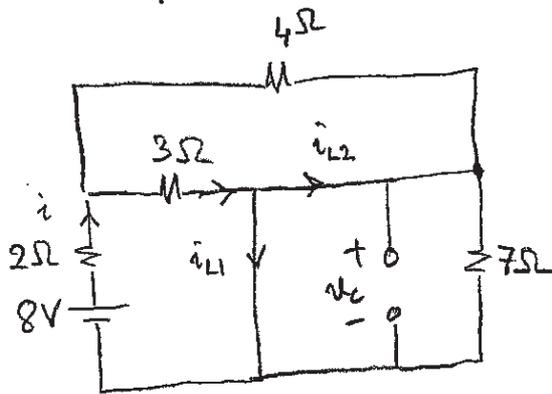The equivalent circuit at  $t \rightarrow \infty$  is:



$$v_c(\infty) = 0$$

$$i_{L1}(\infty) = \frac{56}{26} \text{ A} = 2.154 \text{ A}$$


$$i_{L2}(\infty) = -\frac{24}{26} \text{ A} = -0.923 \text{ A}$$

$$R_{eq} = 2 + 3 \parallel 4 = \frac{26}{7} \Omega$$

$$i = \frac{8}{R_{eq}} = \frac{56}{26} \text{ A} = i_{L1}$$

$$i_{L2} = -i_{4\Omega} = -\frac{3}{7} i = -\frac{24}{26} \text{ A}$$


Example:

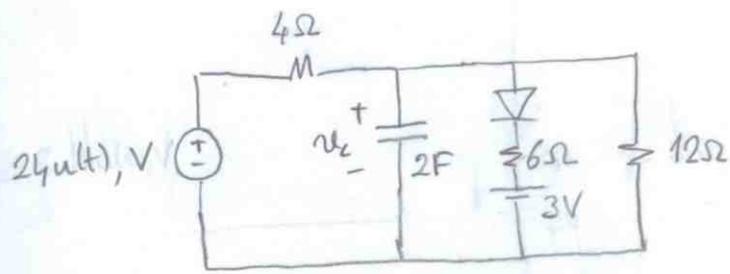

$u_c(0^-) = 0$

Find  $u_c(t)$  for  $t \geq 0$ .

$u_c(0^+) = 0 \Rightarrow D$  is OFF

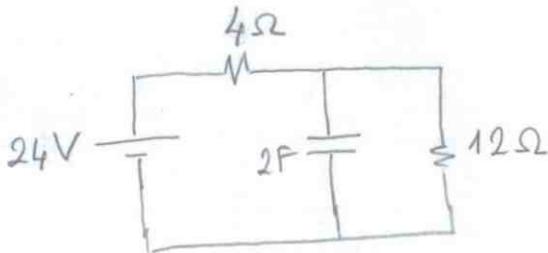

$R_1 = 4 \parallel 12 = 3\Omega$

$\tau_1 = 6 \text{ sec}$


$u_c(\infty) = \frac{12}{16} \cdot 24 = 18 \text{ V}$

$u_c(t) = 18 - 18 e^{-t/\tau_1}, \text{ V}$

D will turn on when  $u_c(t_1) = 3$ .

$18 - 18 e^{-t_1/\tau_1} = 3 \Rightarrow t_1 = \tau_1 \ln \frac{5}{6} \approx 0.182 \tau_1 = 1.09 \text{ sec}$

For  $t > t_1$ , the circuit becomes:

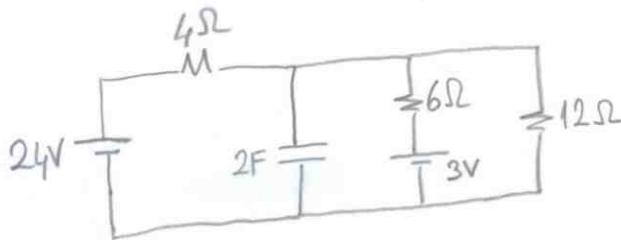

$R_2 = 2\Omega$


$\tau_2 = 4 \text{ sec}$

$u_c(\infty) = \frac{4}{8} \cdot 24 + \frac{3}{9} \cdot 3 = 13 \text{ V}$

$u_c(t_1) = 3 \text{ V}$


$u_c(t) = 13 - 10 e^{-(t-t_1)/\tau_2}, \text{ V}$
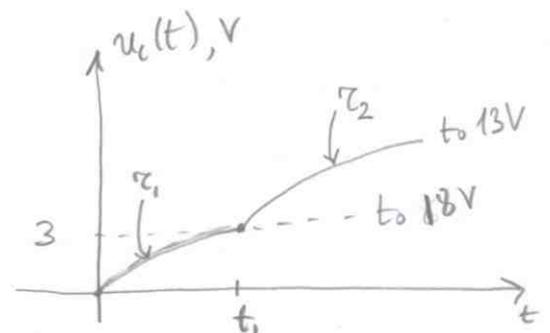
$$u_c(t) = \begin{cases} 6 - 6 e^{-t/\tau_1}, & 0 \leq t \leq t_1 \\ 13 - 10 e^{-(t-t_1)/\tau_2}, & t \geq t_1 \end{cases}$$




$\tau_1 = 6 \text{ sec}; \tau_2 = 4 \text{ sec}; t_1 = \tau_1 \ln \frac{5}{6}$

Example:

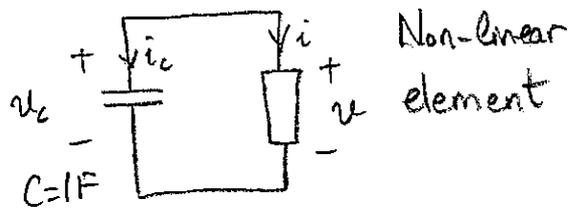

$$v_c(0) = 4V.$$

Find  $v_c(t)$ .

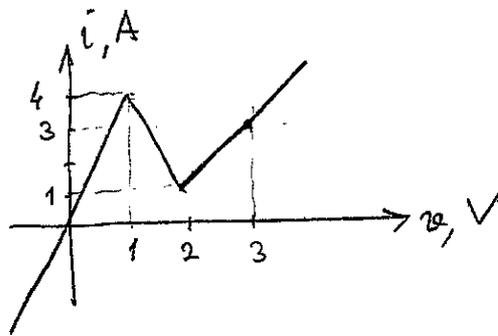

Sln: At  $t=0$   $V=4V \Rightarrow i=5A$

i) For  $2 \leq v \leq 4$  the device characteristics is  $i = 2\left(v - \frac{3}{2}\right)$

$$C \frac{dv_c}{dt} = -i \Rightarrow \frac{dv_c}{dt} + 2v_c = 3$$

$$v_c(0) = 4.$$

$$v_c(t) = \left(4 - \frac{3}{2}\right) e^{-2t} + \frac{3}{2} = \frac{5}{2} e^{-2t} + \frac{3}{2}, V \quad 0 < t < t_1$$

$$v_c(t_1) = 2 \Rightarrow t_1 = -\frac{1}{2} \ln \frac{1}{5} \approx 0.8 \text{ sec.}$$

ii) For  $1 \leq v \leq 2$  the device characteristics is  $i = -3\left(v - \frac{7}{3}\right)$

$$C \frac{dv_c}{dt} = -i \Rightarrow \frac{dv_c}{dt} - 3v_c = -7$$

$$v_c(t_1) = 2v$$

$$v_c(t) = \left(2 - \frac{7}{3}\right) e^{3(t-t_1)} + \frac{7}{3} = -\frac{1}{3} e^{3(t-t_1)} + \frac{7}{3}, V \quad t_1 \leq t \leq t_2$$

$$v_c(t_2) = 1 \Rightarrow t_2 = t_1 + \frac{1}{3} \ln 4 \approx 1.27 \text{ sec.}$$

iii) For  $v < 1$  the device characteristics is  $i = 4v$

$$\left. \begin{aligned} \frac{dv_c}{dt} &= -4v_c \\ v_c(t_2) &= 1 \end{aligned} \right\} \Rightarrow v_c(t) = e^{-4(t-t_2)}, V \quad \text{for } t \geq t_2$$

$v(t) \rightarrow 0$  as  $t \rightarrow \infty$



We can write:

$$v_c(t) = \begin{cases} \frac{5}{2}e^{-2t} + \frac{3}{2}, & 0 \leq t \leq t_1 \\ -\frac{1}{3}e^{3(t-t_1)} + \frac{7}{3}, & t_1 \leq t \leq t_2 \\ e^{-4(t-t_2)}, & t \geq t_2 \end{cases}$$

or


$$v_c(t) = \left( \frac{5}{2}e^{-2t} + \frac{3}{2} \right) [u(t) - u(t-t_1)] + \left( -\frac{1}{3}e^{3(t-t_1)} + \frac{7}{3} \right) [u(t-t_1) - u(t-t_2)] + e^{-4(t-t_2)} u(t-t_2)$$
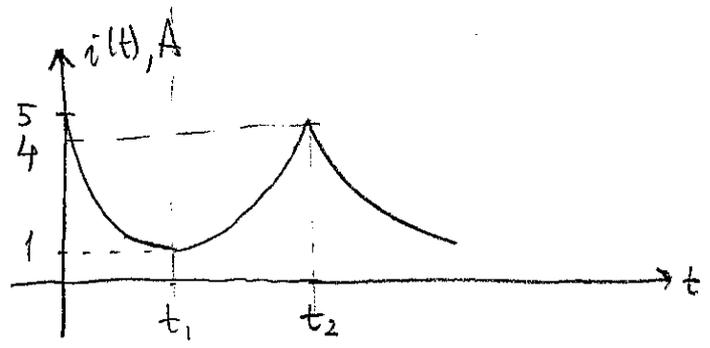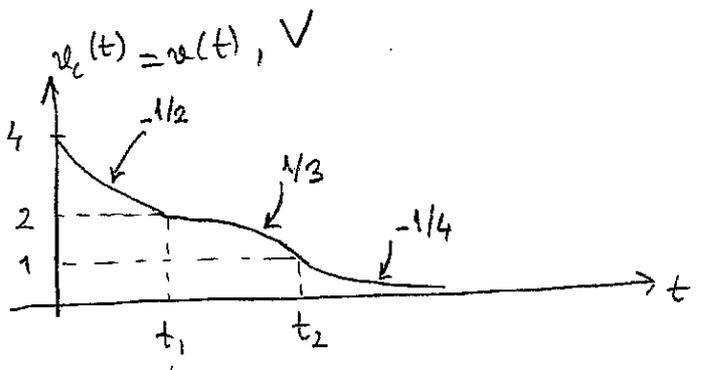
$$i(t) = -C \frac{dv_c}{dt} = -\frac{dv_c}{dt}$$



Example:

8

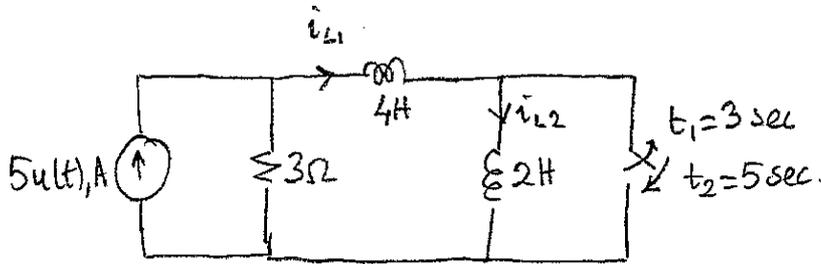


$$i_{L1}(0^-) = 2A$$

$$i_{L2}(0^-) = 1A$$

Find  $i_{L1}(t)$  for  $t > 0$

Switch is closed for  $0 < t < 3$   
 open for  $3 < t < 5$   
 closed for  $t > 5$ .

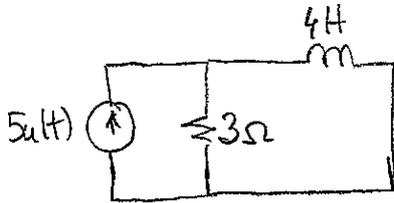Sln:  $i_{L1}(0^+) = 2A$ ;  $i_{L2}(0^+)$  is irrelevant since switch is closed.



$$\tau_1 = \frac{L_1}{R} = \frac{4}{3} \text{ sec.} \quad i_{L1}(\infty) = 5$$

$$i_{L1}(t) = -3e^{-t/\tau_1} + 5, \text{ A.}$$


While the switch is closed, the current through  $L_2$  will not change.

$$L \frac{di_L}{dt} = \mathcal{E}_L = 0 \Rightarrow i_L \text{ is constant} \Rightarrow i_{L2}(3^-) = 1A$$

When the switch is opened at  $t_1$ , we have the pathological case and we will use conservation of flux.

$$\begin{aligned} \frac{\phi}{L_T} &= \frac{\phi_1 + \phi_2}{L_T} = \frac{i_{L1}(t_1^-) L_1 + i_{L2}(t_1^-) L_2}{L_1 + L_2} = i_{L1}(t_1^+) = i_{L2}(t_1^+) \\ &= \frac{(-3e^{-t_1/\tau_1} + 5) 4 + 1 \cdot 2}{6} = 3.45A \end{aligned}$$

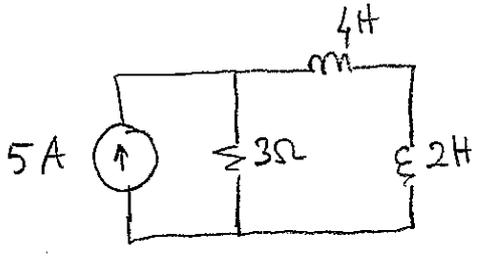For  $3 < t < 5$ , switch is open and we have:




$$\tau_2 = \frac{L_T}{R} = \frac{6}{3} = 2 \text{ sec.}$$

$$i_{L_1}(\infty) = 5A ; i_{L_1}(t_1^+) = 3.45A$$

$$i_{L_1}(t) = -1.55 e^{-(t-t_1)/2} + 5, A \quad 3 < t < 5$$

$$i_{L_1}(t_2) = -1.55 e^{-2/2} + 5 = 4.43A.$$

For  $t > 5$

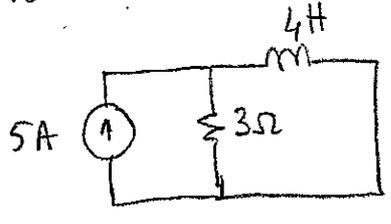


$$\tau_1 = \frac{L_1}{3} = \frac{4}{3} \text{ sec}$$


$$i_{L_1}(\infty) = 5A , i_{L_1}(t_2^+) = 4.43A.$$

$$i_{L_1}(t) = -0.57 e^{-(t-t_2)/\tau_1} + 5, A \quad t > 5.$$
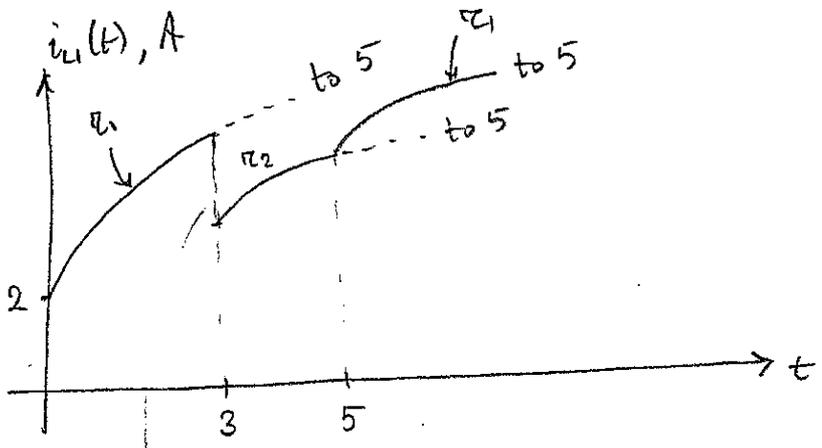
$$i_{L_1}(t) = \begin{cases} -3e^{-t/\tau_1} + 5, & 0 < t < t_1 \\ -1.55 e^{-(t-t_1)/\tau_2} + 5, & t_1 < t < t_2 \\ -0.57 e^{-(t-t_2)/\tau_1} + 5, & t > t_2 \end{cases}$$



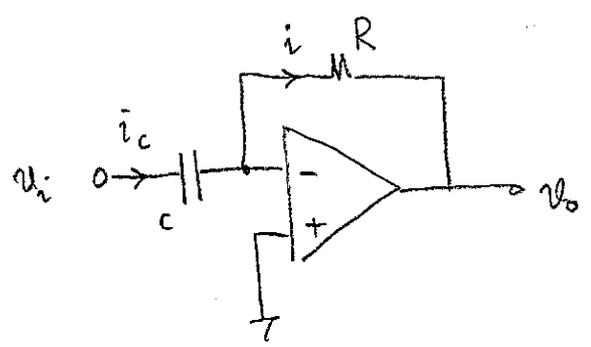
pathological case where energy is not conserved!



$$i_c = C \frac{dv_i}{dt} = i$$

$$v_o = -iR = -RC \frac{di_c}{dt}$$

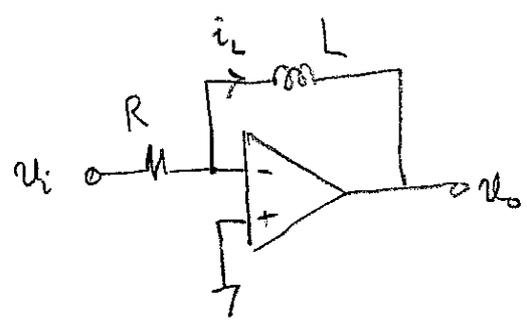Therefore, provided that the OP-AMP does not saturate, the output is the derivative of the input. This circuit is called a differentiator.




$$v_o = -v_L = -L \frac{di_L}{dt}$$

$$i_L = \frac{v_i}{R}$$

$$\therefore v_o = -\frac{L}{R} \frac{dv_i}{dt}$$

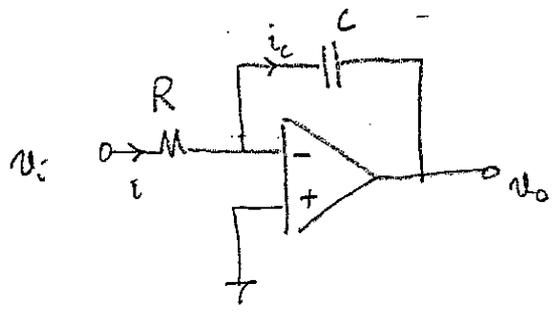Again we have a differentiator, provided that the OP-AMP does not saturate.




$$i = i_c = \frac{v_i}{R}$$

$$i_c = C \frac{dv_c}{dt}$$

$$v_o = -v_c$$

$$v_c(t) = v_c(0) + \frac{1}{C} \int_0^t i_c(\tau) d\tau = v_c(0) + \frac{1}{RC} \int_0^t v_i(\tau) d\tau = -v_o(t)$$

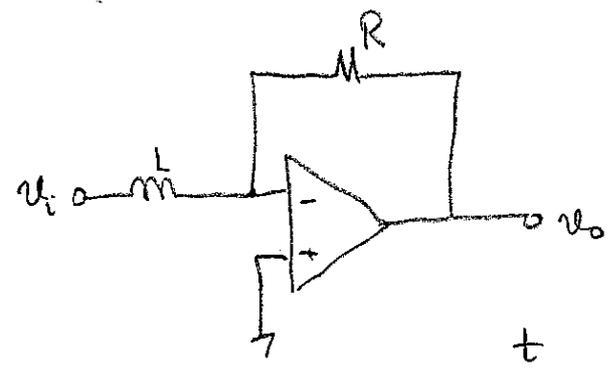Hence, we have an integrator, provided that the OP-AMP does not saturate.





$$v_L = v_i = L \frac{di_L}{dt}$$

$$v_o = -R i_L$$

$$v_o(t) = -R i_L(0) - \frac{R}{L} \int_0^t v_i(\tau) d\tau$$

Again, an integrator.

Example:

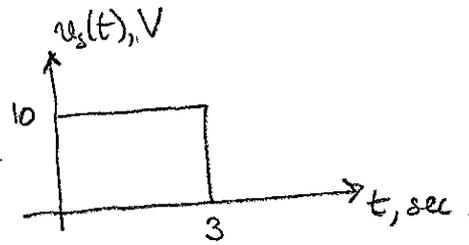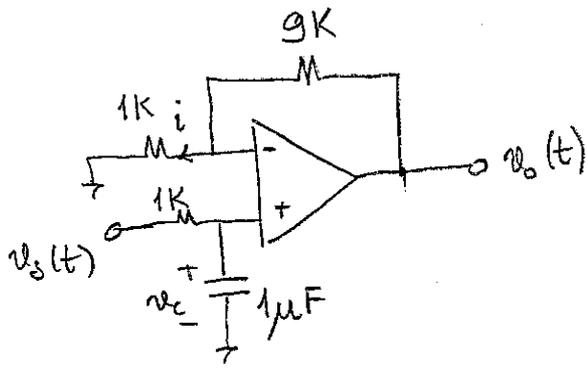

$v_c(0^-) = 0$ .

$E_s = 20V$

Determine  $v_o(t)$ .

$v_+ = v_c = 10 - 10e^{-t/\tau}$ , V       $\tau = 1K \times 1\mu F = 1msec$ .

$i = \frac{v_c}{1K} = 10(1 - e^{-t/\tau})$ , mA

$v_o = v_c + 9i = 100(1 - e^{-t/\tau})$ , V

$100(1 - e^{-t/\tau}) = 20 \Rightarrow t_1 = -\tau \ln \frac{4}{5} \approx 0.223\tau = 223\mu sec$ .

$v_c(3) = 10(1 - e^{-3000}) = 10V$ .

For  $t > 3$ , capacitor discharges through 1K resistor.

$v_c(t) = 10e^{-(t-3)/\tau}$ ,  $t > 3$ .

$v_o(t) = 10v_c(t)$ , hence will be sat initially.

$100v_c(t_2) = 20 \Rightarrow t_2 = 3 + \tau \ln 5 = 3 + 1.61 msec$ .

