

MIDDLE EAST TECHNICAL UNIVERSITY
ELECTRICAL AND ELECTRONICS ENGINEERING DEPARTMENT

EE 201 Circuit Theory I

Midterm Examination 3



December 26, 2012

Duration: 120 minutes


| | | |
|--------------|---------|--|
| Q1 | 20 pts | |
| Q2 | 15 pts | |
| Q3 | 20 pts | |
| Q4 | 25 pts | |
| Q5 | 20 pts | |
| Total | 100 pts | |

| |
|------------|
| Name: |
| Surname: |
| ID No: |
| Section: |
| Signature: |

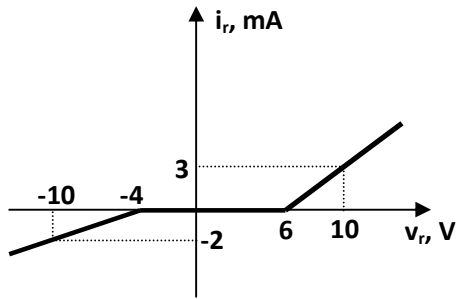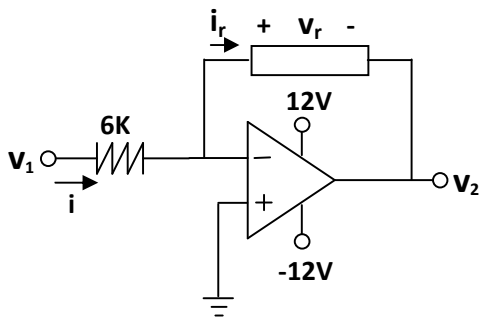Question 1 (20 pts) Obtain and sketch the *input* ($i-v_1$) and *transfer* (v_2-v_1) characteristics.



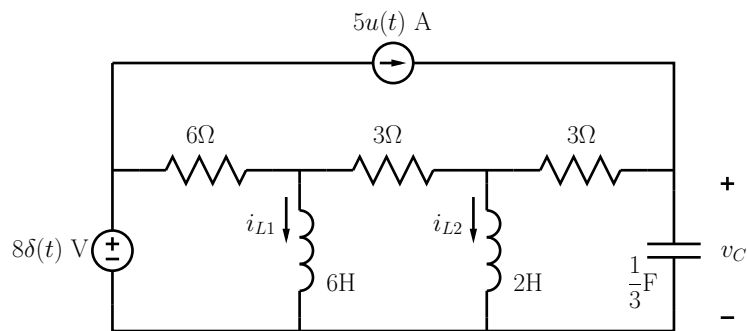Question 2 (15 pts) Consider the circuit below.




$$i_{L1}(0^-) = 1\text{A}$$

$$i_{L2}(0^-) = 3\text{A}$$


$$v_C(0^-) = -4\text{V}$$

Find the inductor currents and the capacitor voltage at $t = 0^+$ and $t = \infty$.

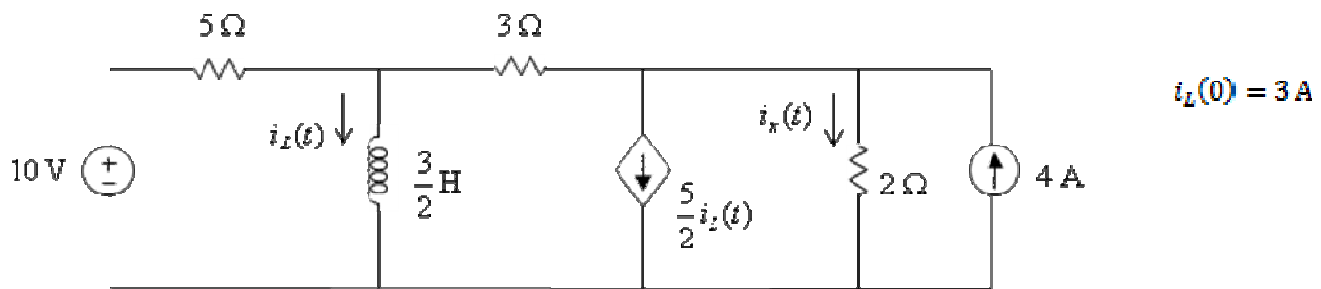Question 3 (20 pts) Find and sketch $i_x(t)$ for $t \geq 0$.




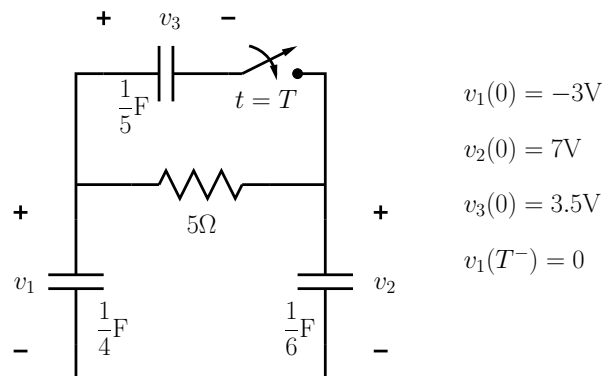Question 4 (25 pts) Consider the circuit below.



- Find and sketch $v_1(t)$ for $t \geq 0$.
- Find the energy delivered to the resistor on the interval $0 \leq t < T$.

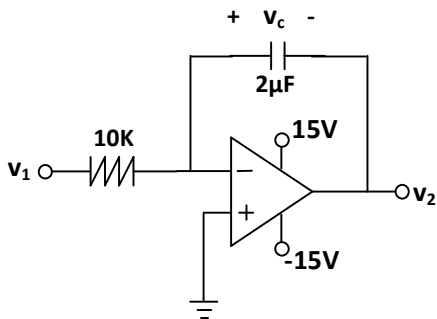Question 5 (20 pts) Obtain and sketch $v_c(t)$ for $t \geq 0$.



$$v_c(0^-) = -20\text{ V}$$

