
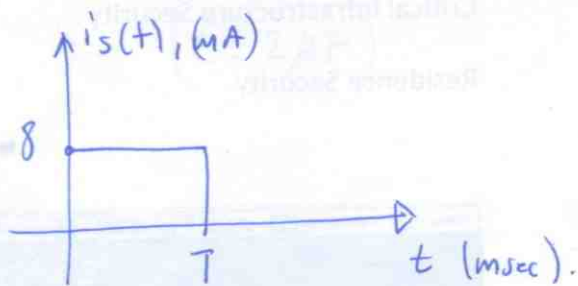


37

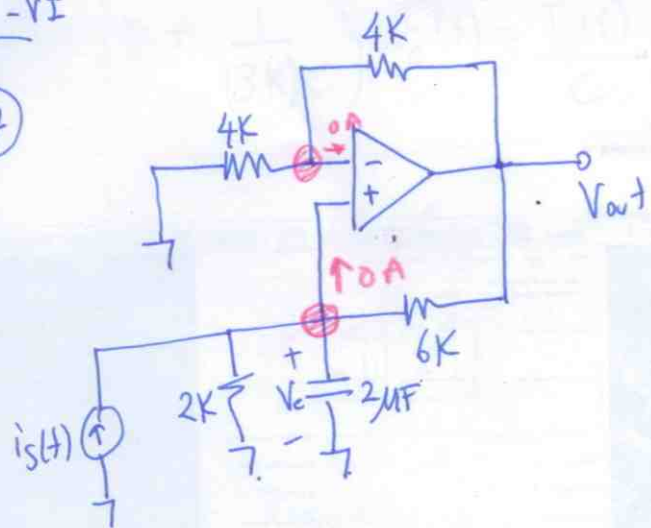

$E_{sat} = 16V$, Op-amp Ideal.
 $V_c(0) = 0$
 $V_c(T) = 12V$

Since Op-amp is ideal, ($R_{in} = \infty$); the following equations are valid in all operational regions of op-amp.

KCL at V_+ : $\frac{V_+}{2K} + \frac{V_+ - V_{out}}{6K} + C \dot{V}_c(t) = I_s(t)$; (I)
 $V_c(t) = V_+(t)$

KCL at V_- : $\frac{V_-}{4K} + \frac{V_- - V_{out}}{4K} = 0 \rightarrow 2V_- = V_{out}$; (II)

The next step is the investigation of operational regions of op-amp

Case (A): Linear Region

① $|V_{out}| < 16 \xrightarrow{(II)} |V_-| < 8V \xrightarrow{(II)} |V_+| < 8V \xrightarrow{(I)} |V_c(t)| < 8V$
 ② $V_+ = V_-$

Condition for Linear Region

$\rightarrow (II) \rightarrow V_{out} = 2V_- = 2V_+$ substitute in (I)

$V_c \rightarrow \frac{V_+}{2K} + \frac{V_+ - V_{out}}{6K} + C \dot{V}_c = I_s(t) \rightarrow \frac{V_c}{3K} + C \dot{V}_c = I_s(t)$

$$\rightarrow \left(D + \frac{1}{(3K)C} \right) V_c(t) = \frac{I_s(t)}{C} \quad (C=2\mu F)$$

Dynamic of Cap. in linear Region

Case (B): +Sat Region

- 1) $V_{out} = 16 \xrightarrow{(II)} V_- = 8V \xrightarrow{(2)} V_+ > V_-$
 - 2) $V_+ > V_-$
- $V_c > 8V$
Condi for +SAT.

(I) $\rightarrow \frac{V_+}{2K} + \frac{V_+ - V_{out}}{6K} + C \dot{V}_c(t) = I_s(t)$

$$\left(D + \frac{1}{\left(\frac{3}{2}K\right)C} \right) V_c(t) = \frac{I_s(t)}{C} + \frac{8}{(3K)C}$$

Dynamics of Cap. in +SAT Region.

Case (C): -SAT Region

- 1) $V_{out} = -16V \rightarrow V_- = -8V \xrightarrow{(2)} V_+ < V_-$
 - 2) $V_+ < V_-$
- $V_c < -8$
Condi for -SAT

(I) $\rightarrow \frac{V_+}{2K} + \frac{V_+ - V_{out}}{6K} + C \dot{V}_c = I_s(t)$

$$\left(D + \frac{1}{\left(\frac{3}{2}K\right)C} \right) V_c(t) = \frac{I_s(t)}{C} - \frac{8}{(3K)C}$$

Dynamics of Cap. in -SAT Region.

Now, we are ready to start integrating all pieces of analysis together. 3

Step 1 $V_c(0^-) = 0V \rightarrow V_c(0^+) = 0V$

↓ from Case A

Op-Amp in linear Region at $t=0^+$

↓

$$\left(D + \frac{1}{(3k)C} \right) V_c(t) = \frac{I_s(t)}{C}$$

} Dynamics of Op-amp in linear Region.

↓

$$\dot{V}_c(0^+) = \frac{I_s(0^+)}{C} - \frac{1}{(3k)C} V_c(0^+)$$

positive.

Cap. Voltage increases at $t=0^+$

Solving

Capacitor voltage keeps on increasing until T'th sec; or provided that

Solving for $V_c(t)$


$$\left(D + \frac{1}{(3k)C} \right) V_c(t) = \frac{I_s(t)}{C} = 4000$$

8mA
2μF
τ₁ = 6msec.

$$V_c(t) = 24 - 24 e^{-t/\tau_1}, t > 0$$

op-amp does not change its state from linear to smth. else.


(provided that op-amp is in linear)

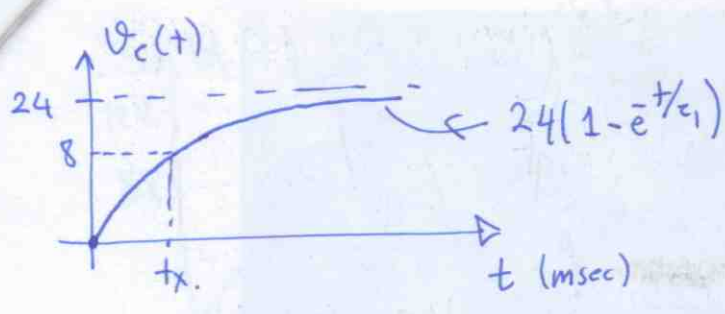

$V_c(t)$ approaches 24V asymptotically as ~~time~~ t increases.

But, note that linear region ~~condition~~ condition is violated, when $V_c(t) \geq 8$; so the graph given above is valid until

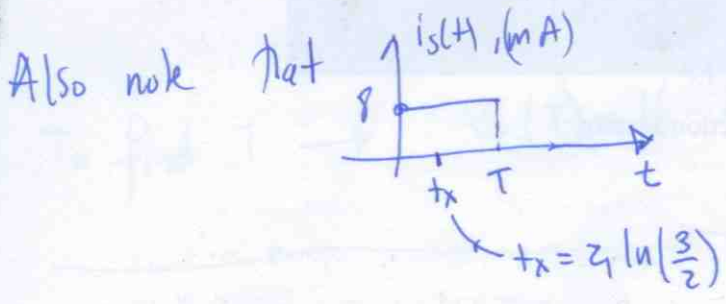$V_c(t_x) = 8 \rightarrow t_x = \tau_1 \ln\left(\frac{3}{2}\right)$. ($\tau_1 = 6\text{msec}$).



where $V_c(T) = 12\text{V}$ So input of 8mA is provided until eq. voltage is 12V.

For $8 \leq V_c(t) \leq 12$ (or $t_x \leq t \leq T$) \rightarrow Op-amp in SAT \rightarrow


$\rightarrow V_c(t_x^+) = 8\text{V}$ and

$\left(D + \frac{1}{\frac{3KC}{2}}\right) V_c(t) = \frac{I_s(t)}{C} + \frac{8}{(3K)e}$ } Op-amp Dynamics in SAT
 $\tau_2 = 3\text{msec}$. \leftarrow 2uF \leftarrow 8mA.

$\left(D + \frac{1}{\tau_2}\right) V_c(t) = \frac{4}{3} \cdot 4000$

$V_c(t) = \frac{16V}{3} - 8e^{-\frac{(t-t_x)}{\tau_2}}, t \geq t_x$
 $= 16 - 8e^{-\frac{(t-t_x)}{\tau_2}}, t \geq t_x$

Note: $V_c(t_x^+) = 8$ is satisfied!

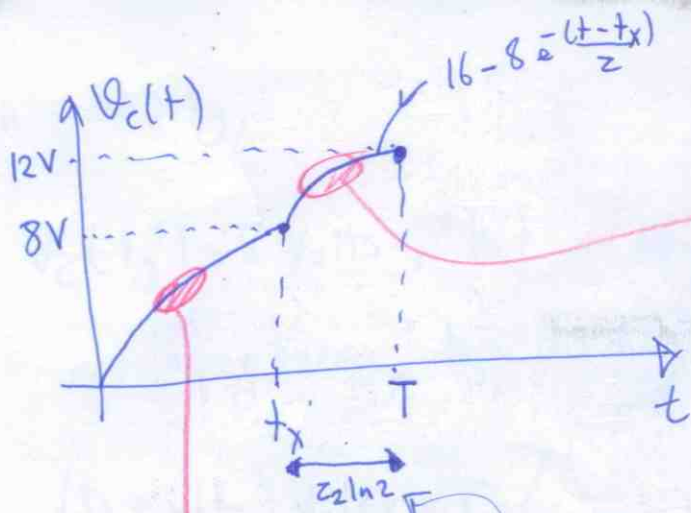

Cap. Charges in +SAT Region ($\tau_2 = 3\text{msec}$)


Cap. Charges in Linear Region (Op-amp) (Time-constant, $\tau_1 = 6\text{msec}$)

To find $T \rightarrow V_c(T) = 16 - 8e^{-\frac{(T-t_x)}{\tau_2}} \rightarrow T = t_x + \tau_2 \ln 2$

When $t > T$, the input is OFF! ($i_s(t) = 0$), but $V_c(T^+) = 12\text{V}$

$(D + \frac{1}{\tau_2}) V_c(t) = \frac{8}{(3\text{K})C}$ ← Op-amp is in +SAT
 ($\tau_2 = 3\text{msec}$)
 $V_c(T^+) = 12\text{V}$

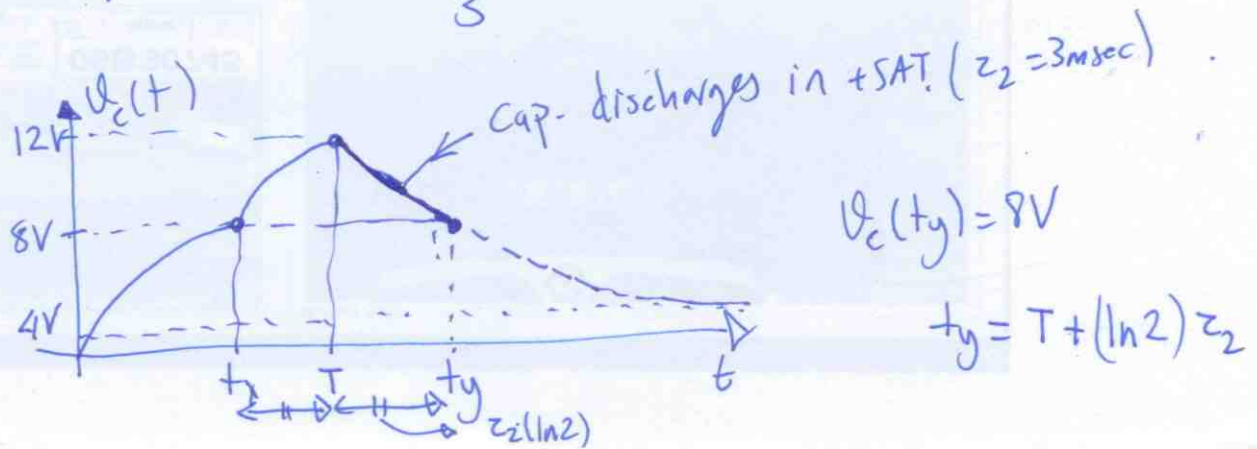$V_c(t) = \frac{4\text{V}}{3} + 8e^{-\frac{(t-T)}{\tau_2}}, t > T$



Cap. discharges in +SAT. ($\tau_2 = 3\text{msec}$)

$V_c(t_y) = 8\text{V}$

$t_y = T + (\ln 2) \tau_2$

When $t > t_y$,

$V_c(t_y^+) = 8$ Volts, but op-amp enters into linear region and C_{AP} continues to discharge in linear region. \rightarrow

$$\rightarrow \left. \begin{aligned} \left(D + \frac{1}{z_1}\right) V_c(t) &= 0 \\ V_c(t_y^+) &= 8V \end{aligned} \right\} \quad V_c(t) = 8e^{-\frac{(t-t_y)}{\tau_1}}, \quad t > t_y.$$

