

Ch. 1

BASIC CONCEPTS

Charge: A fundamental conserved property of subatomic particles. Measured in Coulombs (C). For instance, the electron has $-1e$ charge, the proton $+1e$. (e : elementary charge unit. $1e \approx 1.602 \times 10^{-19} C$) We can talk about the net charge of arbitrary matter.


Ex Block $\begin{bmatrix} n^0 & p^+ e^- \\ n^0 & p^+ \end{bmatrix}$ has net charge of $1e$.

charge is denoted by q or Q .

current: Rate of flow of (net) charge through a given area. Measured in Amperes (A). ($1A = 1C/s$) Denoted by i or I .

$$\boxed{i(t) = \frac{dq(t)}{dt}} \Rightarrow q(t) = q(0) + \int_0^t i(z) dz$$

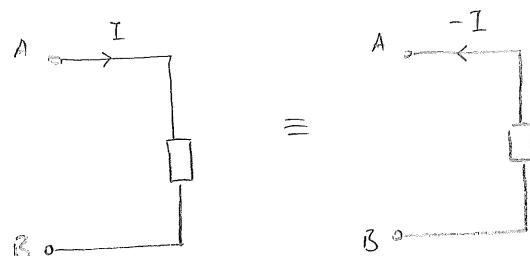To be able to talk about current we need a specified direction.



Voltage: Consider two points x & y . The work done against the electrical field to move a unit charge (1C) from y to x is the voltage V_{xy} . This work is independent of the path through which the charge travels and depends only on the endpoints x & y . Therefore $V_{xy} = -V_{yx}$.


Voltage is measured in volts (V). ($1V = 1J/C$)

$$V = \frac{dW}{dq}$$

(W: work, energy)

To be able to talk about voltage we need a specified polarity.

Ex Let $V_{AB} = -12V$

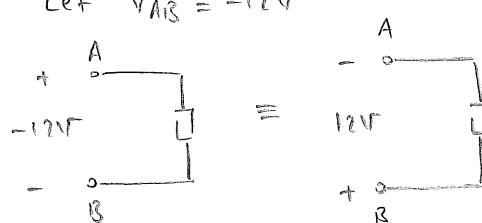


Ground: common reference point for voltage measurements in a circuit. Given some point x in a circuit, by v_x we mean the voltage between point x and ground, i.e. v_{xg} . Symbol for ground: —

Power rate of change of energy. Denoted by P or p . Measured in watts (W). ($1\text{W} = 1\text{J/s}$)

$$P = \frac{dW}{dt} = \underbrace{\frac{\partial W}{\partial q}}_{v(t)} \cdot \underbrace{\frac{dq}{dt}}_{i(t)} \Rightarrow P(t) = v(t) i(t)$$

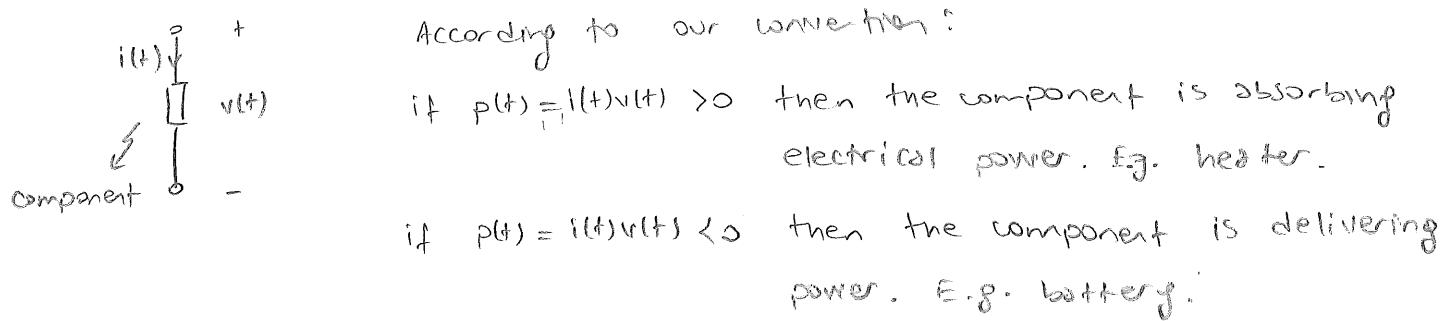Passive sign convention we adopt the convention that, given an electrical component, the polarity of voltage and the direction of current are chosen such that the current enters (the component) from the "+" labeled terminal and leaves from the "-" labeled terminal.




Assumptions In this course we make the following assumptions

(A1) Electrical effects happen instantaneously throughout the circuit.

(A2) The net charge inside any closed surface is always zero.

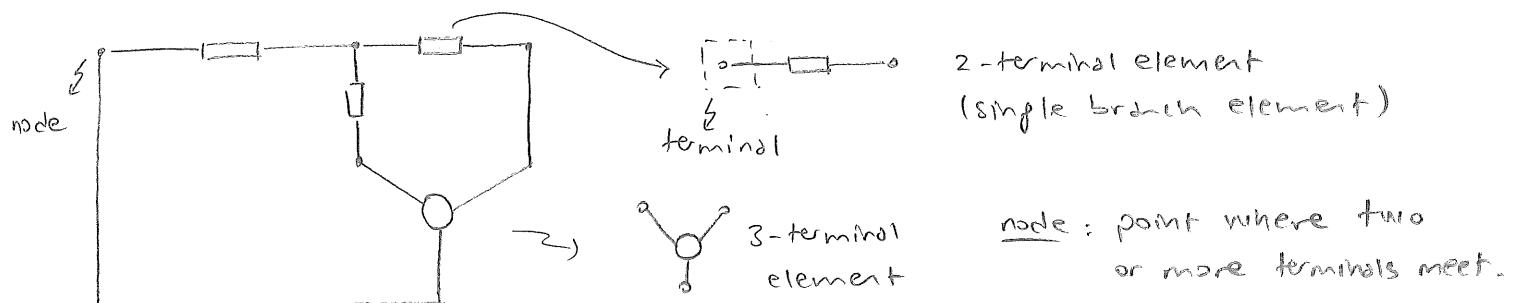
Electric circuit interconnection of (basic) electrical components. Circuits that let us make (A1) are called lumped circuits. Lumped circuit generally means a small circuit.



KIRCHHOFF'S LAWS


Kirchhoff's Current Law (KCL) (A direct implication of our assumption (A2))

"The net charge inside any closed surface is always zero." For any closed surface the sum of incoming currents equals the sum of outgoing currents.

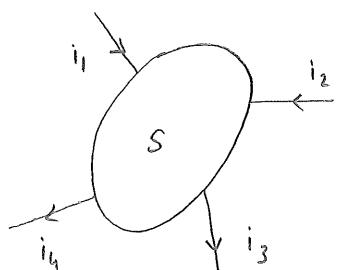Exincoming : i₁, i₂outgoing : i₃, i₄


$$\text{KCL} : \sum \text{incoming} = \sum \text{outgoing}$$

$$\Rightarrow i_1 + i_2 = i_3 + i_4$$

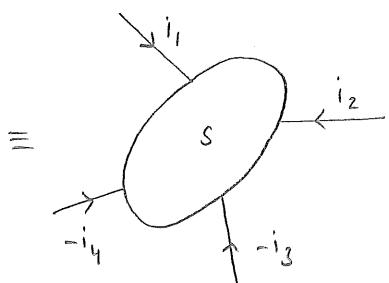incoming : i₁, i₂, -i₃, -i₄


outgoing : none

$$\text{KCL} \Rightarrow i_1 + i_2 + (-i_3) + (-i_4) = 0$$

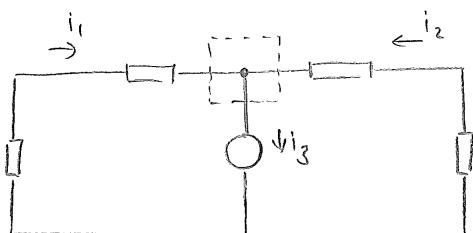Ex:

$$\text{KCL} \Rightarrow i_1 + i_2 = i_3$$

Kirchhoff's Voltage Law (KVL) (A direct implication of path independence for the potential energy difference between two points.) Sum of voltages along any loop (closed path) is zero.

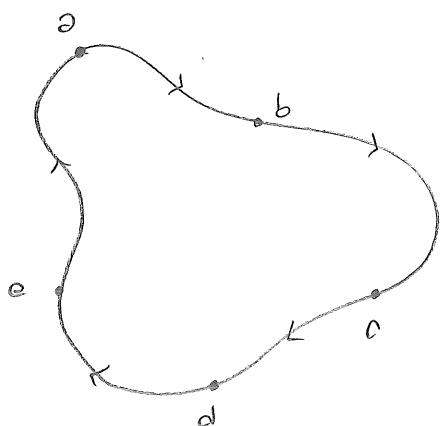
Ex:

$$V_{ab} + V_{bc} + V_{cd} + V_{de} + V_{ea} = V_{aa} = 0$$

$$\text{Likewise, } V_{ae} + V_{ed} + V_{dc} + V_{cb} + V_{ba} = 0$$

$$\text{Also, } V_{ab} + V_{bc} = V_{ae} + V_{ed} + V_{dc}$$

2nd so on.

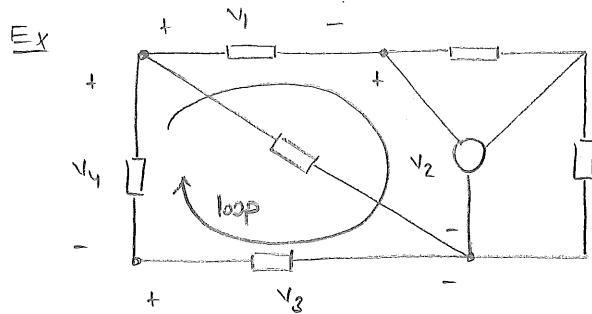

$$\text{KVL} \Rightarrow v_1 + v_2 - v_3 - v_4 = 0$$

let $v_1(t) = 2 \cos(10t + \frac{\pi}{6}) \text{ V}$

$v_2(t) = 12 \text{ V}$

$v_3(t) = 5 \sin(5t) \text{ V}$

$\left. \begin{array}{l} \\ \\ \end{array} \right\} v_4(t) = ?$




$$\text{KVL} \Rightarrow v_4(t) = v_1(t) + v_2(t) - v_3(t)$$

$$\Rightarrow v_4(t) = 12 + 2 \cos(10t + \frac{\pi}{6}) - 5 \sin(5t) \text{ V}$$

TERMINAL EQUATIONS

A circuit element is characterized by well-defined relations satisfied by the current(s) through the element and voltage(s) across its terminals. Such relations are called terminal equations. Terminal equations depend only on the element and not on the rest of the circuit that the element is part of.

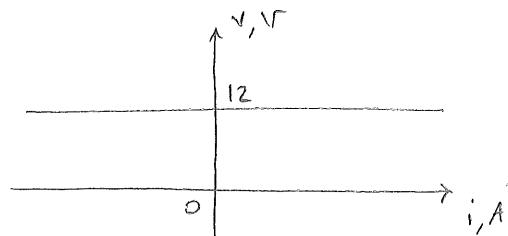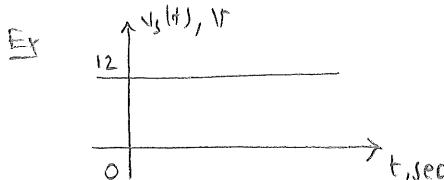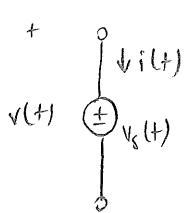Independent voltage source (IVS) A two-terminal (single branch) element with branch relation $v(t) = v_s(t)$, i.e., the voltage of IVS is independent of the current $i(t)$ passing through it.




schematic representation


A constant voltage source (sometimes called battery)

A battery is sometimes depicted by

$$\begin{array}{c} + \\ \text{v}(t) \\ | \\ \text{---} \\ - \end{array} \quad \begin{array}{c} \text{---} \\ | \\ \text{---} \\ \downarrow \\ \text{E} \end{array} \quad \text{v}(t) = \text{E}, \text{ (constant)}$$

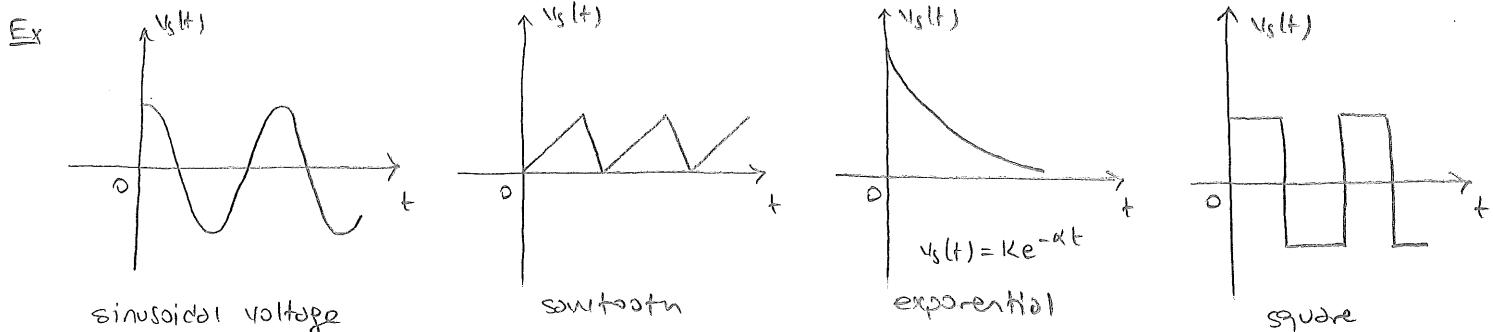

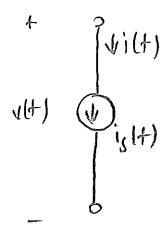Independent current source (ICS) A single branch element with branch relation $i(t) = i_s(t)$, i.e., the current of ICS is independent of the voltage across its terminals.




Ex $i_s(t) = I_m \cos(\omega t + \phi)$ sinusoidal current source (AC source)

$i_s(t) = I_0$ constant current source (DC source)


Remark IVS & ICS are called active elements because they are capable of delivering arbitrary amount of power to the circuit they are connected to throughout intervals of arbitrary length.

—o—

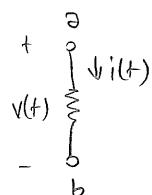
Resistor General name for a 2-terminal element whose branch current & branch voltage satisfy a relation described by a curve on the $i-v$ plane.




Examples

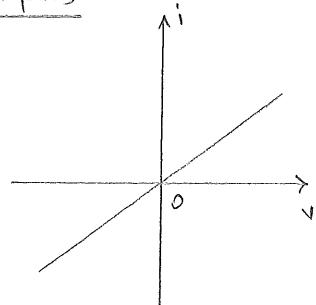


(a)

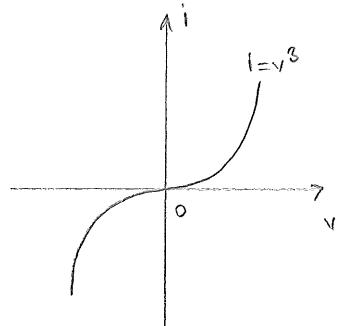


(b)

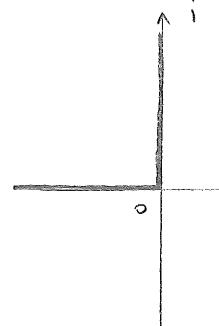


(c)

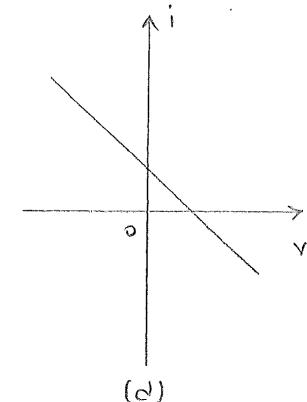


(d)

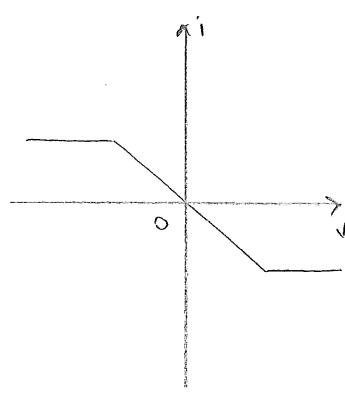


(e)

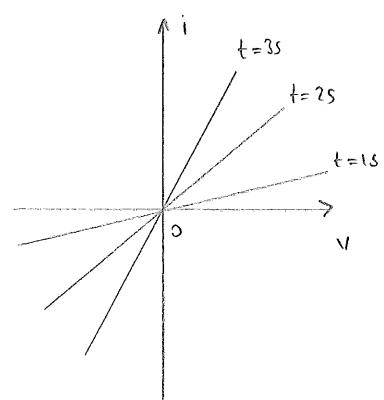

(f)

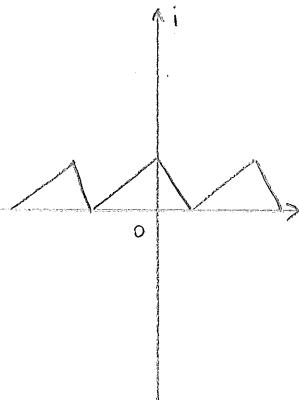

(g)

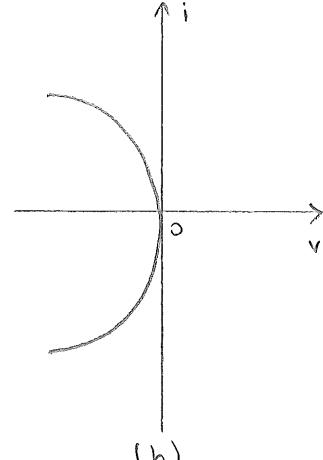

(h)


Linear: Variables x, y are said to satisfy a linear relation if there exist constants a, b (not both a and b are zero) such that $ax+by=0$.

Bilateral Bilateral elements have i-v curves that are symmetric w.r.t. the origin. When we are to connect a bilateral element between two nodes it is immaterial which terminal is connected to which node. For nonbilateral elements this is not so.

Active A resistor is said to be active if its i-v curve contains a point $(V_{o,i}, i_o)$ satisfying $V_{o,i} < 0$. In other words, active \Leftrightarrow i-v curve visits 2nd or 4th quadrant.


	linear / nonlinear	voltage-controlled / current-controlled	time-varying / time-invariant	bilateral / nonbilateral	active / passive
a	L	VC & CC	TI	B	P
b	N	VC & CC	TI	B	P
c	N	neither	TI	N	P
d	N	VC & CC	TI	N	A
e	N	VC	TI	B	A
f	L	VC & CC	TV	B	P
g	N	VC	TI	N	A
h	N	CC	TI	N	A

LTI (linear time-invariant) resistor

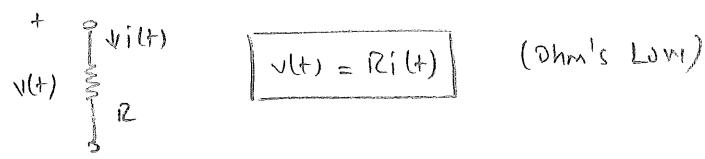

$$v(t) = R i(t) \quad (\text{Ohm's Law})$$

(R can be positive or negative.)


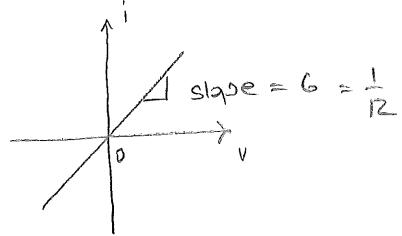


R : resistance, measured in Ohms (Ω)

G : conductance, measured in Siemens (S) or Mhos (M^{-1})



An LTI resistor is both voltage & current controlled for all IC except

$$R=0 \text{ & } R=\infty \quad (G=0)$$

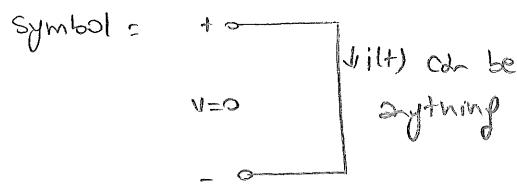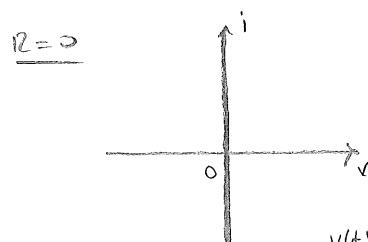

$$v(t) = 0$$

this case is called "short circuit"

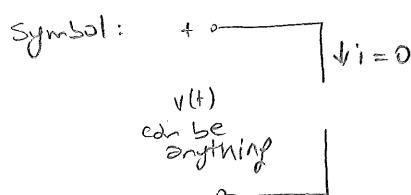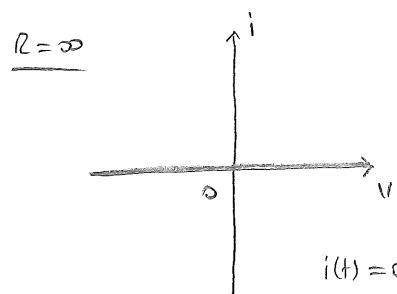


$$i(t) = 0$$




this case is called "open circuit"

power:
$$\begin{aligned} p &= vi = v \cdot \frac{v}{R} = \frac{1}{R} v^2 \\ &= Ri \cdot i = R i^2 \end{aligned} \quad \left. \right\} \quad \boxed{p = \frac{1}{R} v^2 = R i^2} \quad \text{for LTI resistor}$$

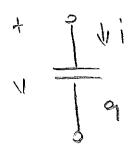Capacitor A 2-terminal element that can store charge. The charge q it stores and the voltage v across its terminals satisfy a relation described by a curve on the $q-v$ plane.



Ex

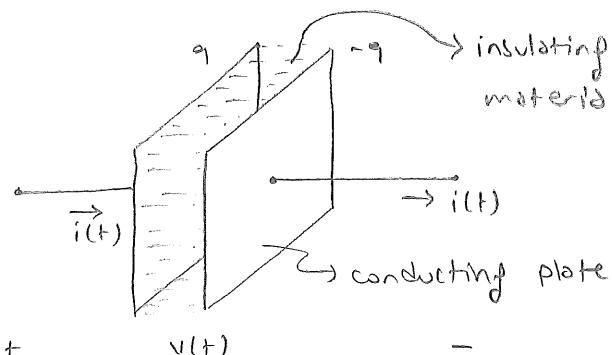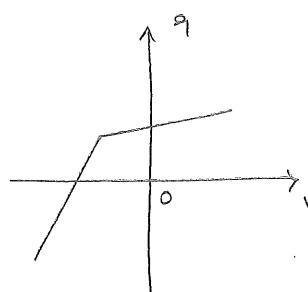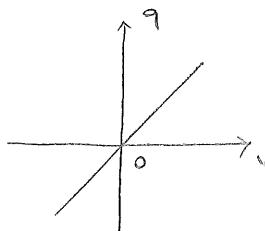

$$i(t) = \frac{d}{dt} q(t) \quad (\text{def. of current})$$

$$\Rightarrow q(t) = q(t_0) + \int_{t_0}^t i(\tau) d\tau$$

LTI Capacitor

$$q(t) = Cv(t)$$

C: constant named capacitance, measured in Farads (F)


i-v relation?

$$i(t) = \frac{d}{dt} q(t) = \frac{d}{dt} \{ Cv(t) \} = C \frac{dv(t)}{dt} \Rightarrow i(t) = C \frac{dv(t)}{dt}$$
 for LTI capacitor

Equivalently, $v(t) = \frac{1}{C} q(t) = \frac{1}{C} \left\{ q(t_0) + \int_{t_0}^t i(z) dz \right\} \Rightarrow v(t) = v(t_0) + \frac{1}{C} \int_{t_0}^t i(z) dz$

($v(t_0)$: initial voltage of the capacitor.)


Ex

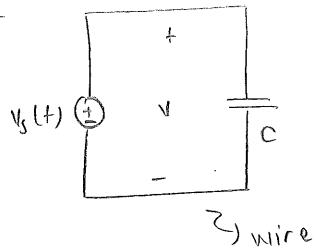

$$v_s(t_0) = 10V$$

$$C = 1\mu F$$

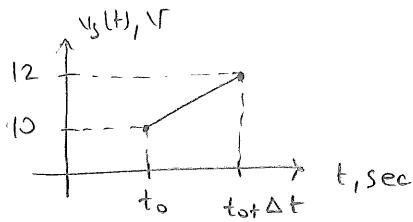Suppose the max. current the wire can carry is $40mA$. We want to raise the voltage from $10V$ to $12V$ without breaking the wire. What is the minimum time required for voltage raise?




$$v(t_0 + \Delta t) = \underbrace{v(t_0)}_{10V} + \frac{1}{C} \int_{t_0}^{t_0 + \Delta t} i_{\max} dt$$

$$\frac{1}{10^{-6}F} \quad \frac{40 \times 10^{-3}A}{\Delta t}$$

$$\Rightarrow 12 = 10 + \frac{40 \times 10^{-3} \Delta t}{10^{-6}} \Rightarrow \Delta t = 5 \times 10^{-5} = 50\mu s$$

Ex

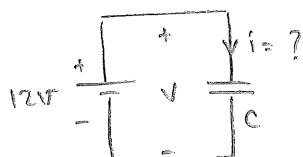

$$i = C \frac{dv}{dt} = 0$$

Therefore, the capacitor behaves as open circuit under DC voltage.

power

$$\left. \begin{aligned} p(t) &= i(t)v(t) \\ &= C \frac{dv(t)}{dt} v(t) \end{aligned} \right\} \boxed{p(t) = C v(t) \frac{dv(t)}{dt}} \quad \text{for LTI capacitor.}$$

stored energy ($C > 0$)

$$w(t) = \int_{-\infty}^t p(z) dz = \int_{v(-\infty)}^{v(t)} C v dv = \frac{1}{2} C v(t)^2$$


$\Rightarrow = 0$

Hence, energy stored in an LTI capacitor :

$$\boxed{w = \frac{1}{2} C v^2 = \frac{1}{2} \frac{1}{C} q^2}$$

$\left\{ \begin{array}{l} \text{Energy transfer during the interval } [t_0, t] : \Delta w = w(t) - w(t_0) = \frac{1}{2} C (v(t)^2 - v(t_0)^2) \\ \dots \end{array} \right\}$

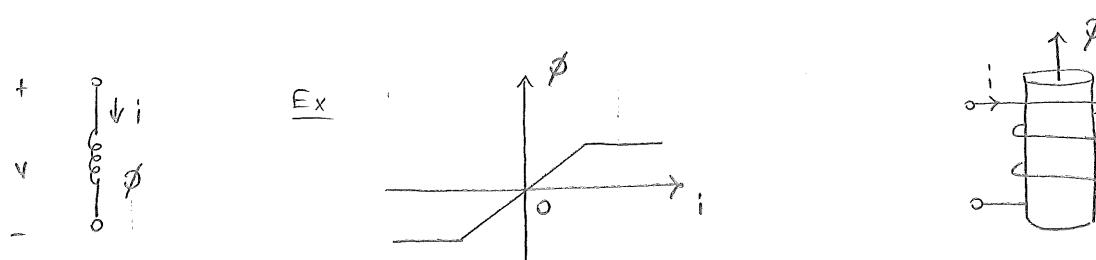
Inductor 2-terminal element whose magnetic flux ϕ and current i satisfy
 \Rightarrow relation described by a curve on the ϕ - i plane.



Faraday's Law :

$$\boxed{v(t) = \frac{d}{dt} \phi(t)}$$

LTI inductor

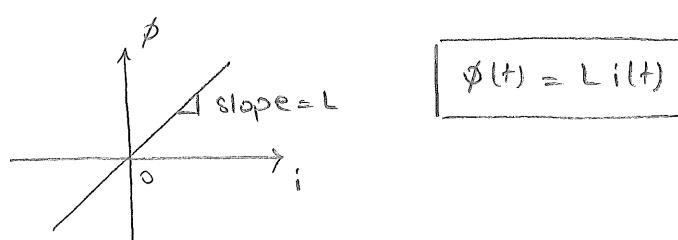

L : inductance, measured in Henries (H)

\Rightarrow relation ?

$$v(t) = \frac{d}{dt} \phi(t) = \frac{d}{dt} \{ L i(t) \} = L \frac{di(t)}{dt} \Rightarrow \boxed{v(t) = L \frac{di(t)}{dt}} \quad (\text{LTI in.})$$

Equivalently,

$$\boxed{i(t) = i(t_0) + \frac{1}{L} \int_{t_0}^t v(z) dz}$$

power

$$p(t) = v(t) i(t) \quad \left. \begin{array}{l} \\ = L \frac{di(t)}{dt} i(t) \end{array} \right\} \boxed{p(t) = L i(t) \frac{di(t)}{dt}}$$

stored energy ($L > 0$)


$$w(t) = \int_{-\infty}^t p(z) dz = \int_{i(-\infty)}^{i(t)} L i i = \frac{1}{2} L i(t)^2$$

≈ 0

$$\Rightarrow w = \frac{1}{2} L i^2$$

Summary of LTI R,L,C elements' properties

	Resistor (R)	Capacitor (C)	Inductor (L)
Algebraic equation	$v(t) = R i(t)$	$q(t) = C v(t)$	$\phi(t) = L i(t)$
inv char.	$v(t) = R i(t)$ $i(t) = \frac{1}{R} v(t)$	$i(t) = C \frac{dv(t)}{dt}$ $v(t) = v(t_0) + \frac{1}{C} \int_{t_0}^t i(z) dz$	$v(t) = L \frac{di(t)}{dt}$ $i(t) = i(t_0) + \frac{1}{L} \int_{t_0}^t v(z) dz$
energy stored at time t	—	$w(t) = \frac{1}{2} C v(t)^2$	$w(t) = \frac{1}{2} L i(t)^2$

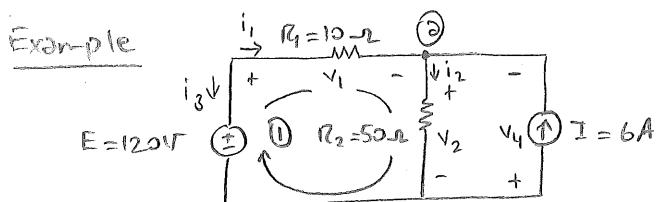

a) Find i_1, i_2, v_1, v_2

b) Verify total generated power equals total dissipated power.

Sol'n a) Ohm's law: $v_1 = R_1 i_1 = 10 i_1$ & $v_2 = R_2 i_2 = 50 i_2$

KCL at node ②: $i_1 - i_2 + I = 0 \Rightarrow i_1 - i_2 = -6 \quad (1)$

KVL at loop ①: $v_1 + v_2 - E = 0 \Rightarrow 10i_1 + 50i_2 = 120 \quad (2)$

(1) & (2) $\Rightarrow \boxed{i_1 = -3A, i_2 = 3A} \Rightarrow \boxed{v_1 = -30V, v_2 = 150V}$

Hence,

$$\text{power generated} = 120 \cdot 6 = \underline{\underline{720W}} \quad (\text{by KCL})$$

b) voltage source: $i_3 = -i_1 = 3A \Rightarrow P_E = 3 \cdot 120 = 360W$ (absorbing)

current source: $v_4 = -v_2 = -150V \Rightarrow P_I = 6 \cdot (-150) = -900W$ (delivering)

$R_1: P_{R_1} = i_1 v_1 = 90W$ (absorbing)

$R_2: P_{R_2} = R_2 i_2^2 = 450W$ (absorbing)

$= 360 + 90 + 450 = \underline{\underline{900W}}$

power dissipated:

Dependent Source: A linear dependent source has terminal characteristics controlled by a current or a voltage of some other branch in the circuit.


1) voltage controlled voltage source (VCCVS)



v_1 : control variable

μ : voltage gain

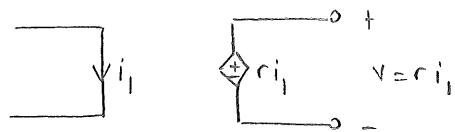
2) Current controlled voltage source (CCVS)



i_1 : control var.

r : transresistance

3) VCCS

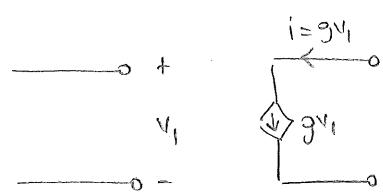

v_1 : control var.

g : transconductance


4) CCCS



i_1 : control var.


β : current gain

Ex

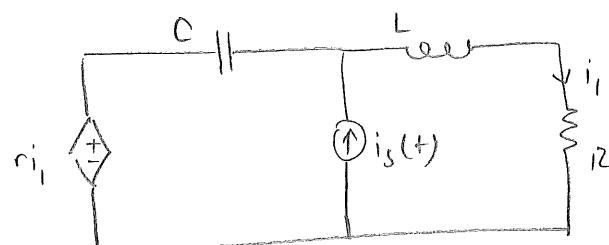

Ideal transformer

A k -branch IT is depicted by

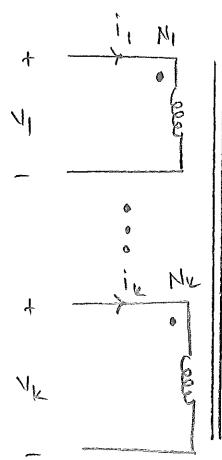

The branch relations:

$$\frac{v_1}{N_1} = \frac{v_2}{N_2} = \dots = \frac{v_k}{N_k}$$


$N_j > 0$ is the number of turns for the j th branch
 $j = 1, 2, \dots, k$

$$N_{i1} + N_{i2} + \dots + N_{ik} = 0$$

The total power of IT is $\sum_{j=1}^k i_j v_j \Rightarrow$ (Exercise: prove this.)


FROM CIRCUIT TO GRAPH

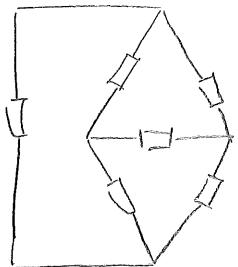To systematically analyze circuits we study their graphs




circuit N

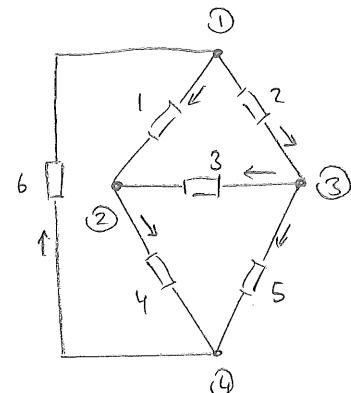- 1) label each branch
- 2) assign a (arbitrary) direction to each branch
- 3) label each node
- 4) obtain the graph



\Rightarrow the graph of circuit N is

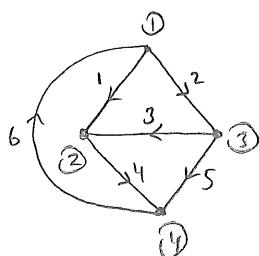


$$\text{nodes} = \{1, 2, 3, 4\}$$

$$\text{branches} = \{1, 2, 3, 4, 5\}$$



$$\# \text{ of nodes } n = 4$$

$$\# \text{ of branches } b = 6$$


How about the below circuit?

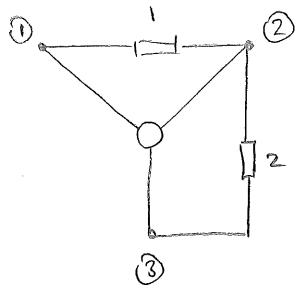

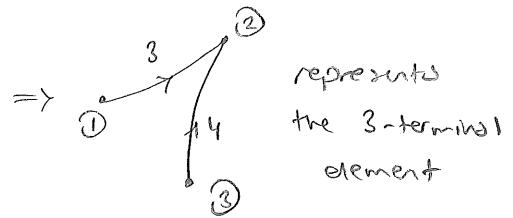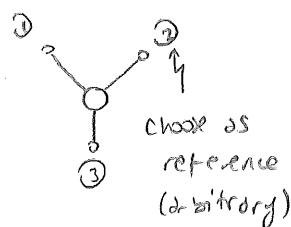
When we have a k-terminal ($k \geq 3$) element we assign one of its terminal nodes as reference and treat it as $k-1$ single branch elements as shown:



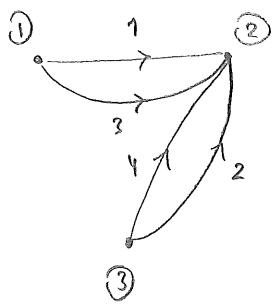
Then the graph of the original circuit becomes



for k-terminal

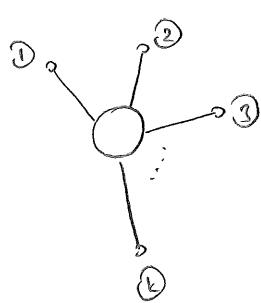


\Rightarrow

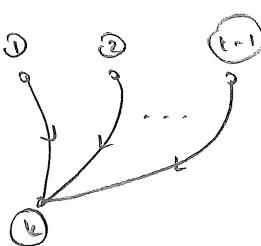

Matrix formulation of KCL

for

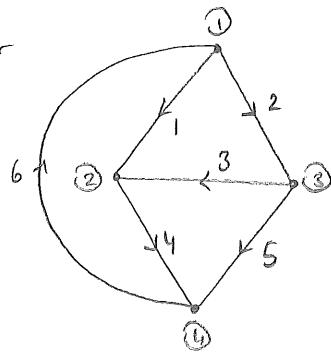

write KCL at each node :

$$\begin{aligned} \textcircled{1} : i_1 + i_2 - i_6 &= 0 \\ \textcircled{2} : -i_1 - i_3 + i_4 &= 0 \\ \textcircled{3} : -i_2 + i_3 + i_5 &= 0 \\ \textcircled{4} : -i_4 - i_5 + i_6 &= 0 \end{aligned} \quad \left. \begin{array}{l} \\ \\ \\ \end{array} \right\} (*)$$

Eqns (*) can be written as

$$\begin{matrix} & 1 & 2 & 3 & 4 & 5 & 6 \\ \textcircled{1} & 1 & 1 & 0 & 0 & 0 & -1 \\ \textcircled{2} & -1 & 0 & -1 & 1 & 0 & 0 \\ \textcircled{3} & 0 & -1 & 1 & 0 & 1 & 0 \\ \textcircled{4} & 0 & 0 & 0 & -1 & -1 & 1 \end{matrix} \left[\begin{matrix} i_1 \\ i_2 \\ i_3 \\ i_4 \\ i_5 \\ i_6 \end{matrix} \right] = \left[\begin{matrix} 0 \\ 0 \\ 0 \\ 0 \\ 0 \\ 0 \end{matrix} \right]$$

$\underbrace{\hspace{10em}}_{A_2}$ $\underbrace{\hspace{10em}}_i$

 A_2 : incidence matrix ($n \times b$ matrix) obtained as

$$a_{ij} = \begin{cases} +1 & \text{if } j^{\text{th}} \text{ branch leaves } i^{\text{th}} \text{ node} \\ -1 & \text{if } j^{\text{th}} \text{ branch enters } i^{\text{th}} \text{ node} \\ 0 & \text{otherwise} \end{cases}$$

 i : branch current vector $i = [i_1, i_2, \dots, i_b]^T$

— o —

linear dependence Let v_1, v_2, \dots, v_k be k vectors (all same size). If we can find real numbers $\alpha_1, \alpha_2, \dots, \alpha_k$ (not all zero) such that $\sum \alpha_i v_i = 0$ then the vectors v_1, v_2, \dots, v_k are lin. dependent. Otherwise, they are linearly independent.

Ex $\begin{bmatrix} 1 \\ 0 \end{bmatrix}, \begin{bmatrix} 0 \\ -1 \end{bmatrix}$ are lin. ind.whereas $\begin{bmatrix} 1 \\ 2 \\ 3 \end{bmatrix}, \begin{bmatrix} 4 \\ 5 \\ 6 \end{bmatrix}, \begin{bmatrix} 7 \\ 8 \\ 9 \end{bmatrix}$ are lin. dep. (because $3v_1 - 6v_2 + 3v_3 = 0$)

— o —



rows (row vectors) of A_2 sum up to zero. Therefore they're linearly dependent. Choose one node as reference node and remove the corresponding row from A_2 . The new matrix of size $(n-1) \times b$ is called the reduced incidence matrix and denoted by A .

$$A_d = \begin{bmatrix} 1 & 1 & 0 & 0 & 0 & -1 \\ -1 & 0 & -1 & 1 & 0 & 0 \\ 0 & -1 & 1 & 0 & 1 & 0 \\ 0 & 0 & 0 & -1 & -1 & 1 \end{bmatrix} \xrightarrow{\substack{\text{let } \textcircled{1} \text{ be the} \\ \text{reference node} \\ (\text{ground})}} A = \begin{bmatrix} 1 & 1 & 0 & 0 & 0 & -1 \\ -1 & 0 & -1 & 1 & 0 & 0 \\ 0 & -1 & 1 & 0 & 1 & 0 \end{bmatrix}$$

Rows of A are linearly independent if our graph is connected. Such A is called full row rank.

Definition A graph is connected if there is a path (disregarding the direction of branches) connecting any two nodes.

Ex:

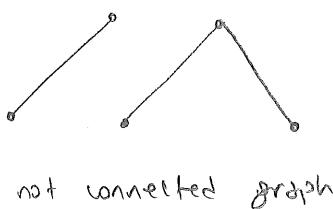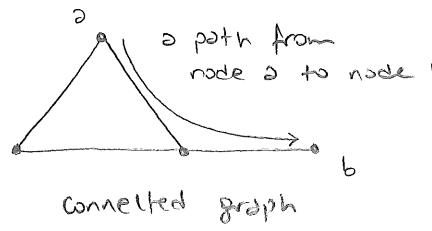

Hence, we obtained

$$A_i = 0 \quad (\text{KCL})$$


$$A \in \mathbb{R}^{(n-1) \times b}$$

: reduced incidence matrix

$$i \in \mathbb{R}^b \quad : \text{branch current vector}$$

Remark $A_i = 0 \Rightarrow A_{di} = 0$, (why?)

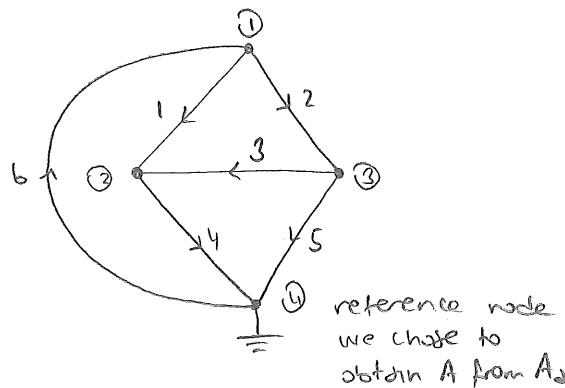Relation of incidence matrix to branch voltages



branch voltages : v_1, v_2, \dots, v_6

$v_1 = v_{12}$ (voltage between node 1 (+) and node 2 (-))

$$v_2 = v_{13}$$

:

$$v_6 = v_{45}$$

node voltages : e_1, e_2, e_3

$$e_1 = v_{12}, e_2 = v_{13}, e_3 = v_{34}$$

Thanks to KVL, each branch voltage can be written in terms of node vol.

$$\text{ex } v_1 = v_{12} = v_{10} - v_{02} = v_{10} - v_{10} = e_1 - e_2$$

$$\left. \begin{array}{l}
 v_1 = e_1 - e_2 \\
 v_2 = e_2 - e_3 \\
 v_3 = e_3 - e_4 \\
 v_4 = e_4 \\
 v_5 = e_5 \\
 v_6 = -e_1
 \end{array} \right\} \text{put in matrix form} \Rightarrow \begin{bmatrix} v_1 \\ v_2 \\ v_3 \\ v_4 \\ v_5 \\ v_6 \end{bmatrix} = \begin{bmatrix} 1 & -1 & 0 \\ 0 & 1 & -1 \\ 0 & 0 & 1 \\ 0 & 1 & 0 \\ 0 & 0 & 1 \\ -1 & 0 & 0 \end{bmatrix} \begin{bmatrix} e_1 \\ e_2 \\ e_3 \\ e_4 \\ e_5 \\ e_6 \end{bmatrix} \xrightarrow{\text{e} \in \mathbb{R}^{n+1} \text{ (node voltage vector)}} \begin{matrix} v \in \mathbb{R}^b \\ (\text{branch voltage vector}) \end{matrix} \quad A^T$$

Item 1, we obtained $\boxed{v = A^T e}$

Remark Once we know the node voltages we can determine all the branch voltages. Also, KVL puts no constraints on node voltages.

Tellegen's Theorem Consider two circuits that share the same graph. Let $i = [i_1, i_2, \dots, i_b]^T$ be the current vector from circuit 1 and $v = [v_1, v_2, \dots, v_b]^T$ be the voltage vector from circuit 2. Then $i^T v = 0$.

Proof : $i^T v = i^T (A^T e) = (i^T A^T) e = \underbrace{(A^T)^T}_0 e = 0 \quad \square$


Remark If $i = i(t)$ & $v = v(t)$ belong to the same circuit - then

$$0 = i(t)^T v(t) = \sum_{k=1}^b i_k(t) v_k(t) = \text{total power. (conservation of power)}$$

— — —


Planar graph can be drawn on plane in such a way that no two branches intersect at a point that is not a node.

Ex :

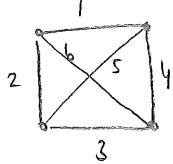


planar since

=

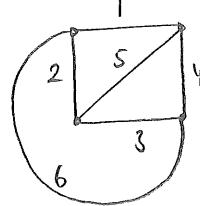

whereas

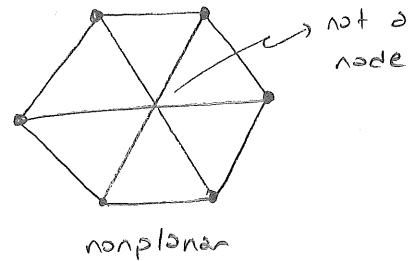


nonplanar

Nonseparable graph If a connected graph stays connected after removing any one node (and all the branches attached to that node) then it is nonseparable.

Matrix formulation of KVL

Let G be a planar, nonseparable graph. The mesh matrix M is an $\ell \times b$ matrix (where ℓ is the number of inner meshes and b is the number of branches) defined as follows:

$$M_{ij} = \begin{cases} +1 & \text{if } j^{\text{th}} \text{ branch belongs to } i^{\text{th}} \text{ mesh and their directions coincide} \\ -1 & \text{if } j^{\text{th}} \text{ branch belongs to } i^{\text{th}} \text{ mesh and their directions are opposite} \\ 0 & \text{otherwise} \end{cases}$$

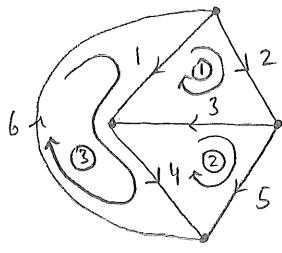Ex

Inner meshes = $\{①, ②, ③\}$ (directions are chosen cw by convention)

$$M = \begin{bmatrix} 1 & 2 & 3 & 4 & 5 & 6 \end{bmatrix} \leftarrow \text{branches}$$


$$\begin{bmatrix} -1 & 1 & 1 & 0 & 0 & 0 \\ 0 & 0 & -1 & -1 & 1 & 0 \\ 1 & 0 & 0 & 1 & 0 & 1 \end{bmatrix} \begin{array}{c} ① \\ ② \\ ③ \end{array}$$

↑ inner meshes

let $v = [v_1 \ v_2 \ \dots \ v_b]^T$ be the branch voltage vector. Then $Mv = 0$ by KVL.

— — —

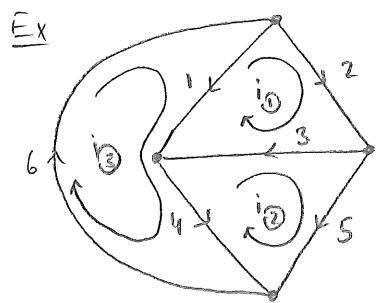To each (inner) mesh there corresponds a mesh current which is related to the branch currents as follows:



$$\left. \begin{aligned} i_1 &= i_3 - i_0 \\ i_2 &= i_0 \\ i_3 &= i_0 - i_2 \\ i_4 &= i_3 - i_2 \\ i_5 &= i_2 \\ i_6 &= i_3 \end{aligned} \right\} \Rightarrow \begin{bmatrix} i_1 \\ i_2 \\ i_3 \\ i_4 \\ i_5 \\ i_6 \end{bmatrix} = \begin{bmatrix} -1 & 0 & 1 & 0 & 0 & 0 \\ 1 & 0 & 0 & 1 & -1 & 0 \\ 0 & -1 & 0 & 0 & 1 & -1 \\ 0 & 1 & 0 & 0 & 0 & 1 \end{bmatrix} \begin{bmatrix} i_0 \\ i_1 \\ i_2 \\ i_3 \\ i_4 \\ i_M \end{bmatrix}$$

i = branch current vector

i_M = mesh current vector

$$\Rightarrow i = M^T i_M$$

Remark once we know the mesh currents we can determine all the branch currents. Also, KCL puts no constraints on mesh currents. Therefore:

$$0 = Ai = AM^T i_M \Rightarrow AM^T = 0. \text{ That is, rows of } A \text{ are orthogonal to rows of } M,$$





Summary go to #18
y
 i_M can be anything

Formulations for nonlinear circuits

Tree Given a connected graph G , its subgraph T is called a tree if

- 1) T has all the nodes of G ,
- 2) T is connected, and
- 3) T contains no loops.

Ex

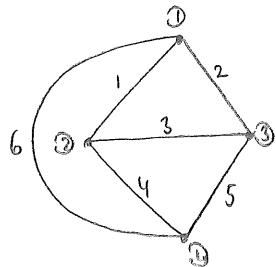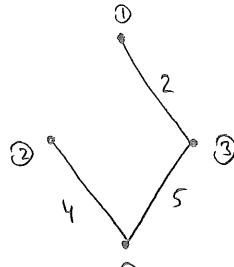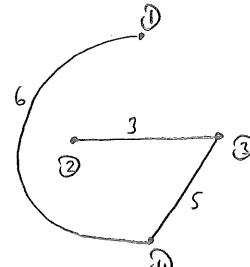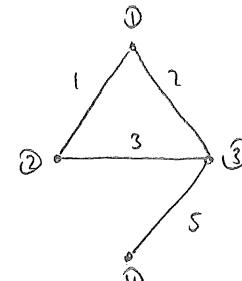graph G tree T_1 tree T_2 

not a tree! (contains loop)


Exercise Show that a tree always has $n-1$ branches. ($n = \#$ of nodes)

—o—

cutset let G be a connected graph. A set of branches C is called a cutset if

- 1) the removal of all the branches of C from G makes an unconnected graph and
- 2) if we remove all the branches of C except an arbitrary one, the graph G stays connected.

Ex

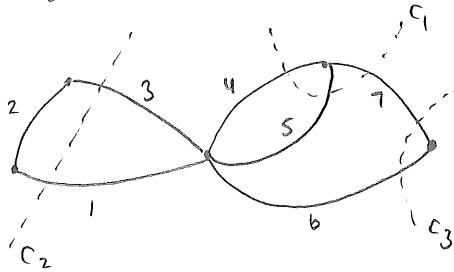

$$C_1 = \{4, 5, 7\}$$

$$C_2 = \{1, 3\}$$


$$C_3 = \{6, 7\}$$

cutsets

Set $\{1, 3, 4, 5, 6\}$ is not a cutset!

Fact Given a connected graph G and a tree T (of G), let β be a branch of T . Then there exists a cutset of G that contains β and no other branches from T . That cutset is unique and is called a fundamental cutset.

Ex

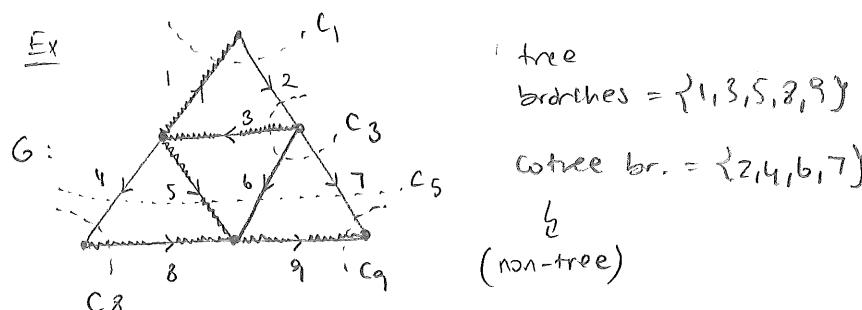

tree

$$\text{branches} = \{1, 3, 5, 8, 9\}$$

$$\text{cotree br.} = \{2, 4, 6, 7\}$$

(non-tree)

At each cutset we can obtain current equations by KCL:


$$C_1: i_1 - i_2 = 0$$

$$C_3: i_3 - i_2 + i_6 + i_7 = 0$$

$$C_5: i_5 + i_4 + i_6 + i_7 = 0$$

$$C_8: i_8 - i_4 = 0$$


$$C_9: i_9 + i_7 = 0$$

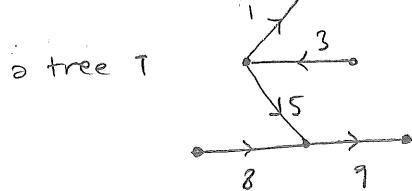

Remark Note that once all the cotree branch currents are known, the remaining (tree) branch currents can be computed.

— → —

Fundamental loop Remember that each tree branch defines a unique cutset (called a fundamental cutset). Likewise each cotree (non-tree) branch defines a unique loop (called a fundamental loop) such that it contains only one cotree branch.

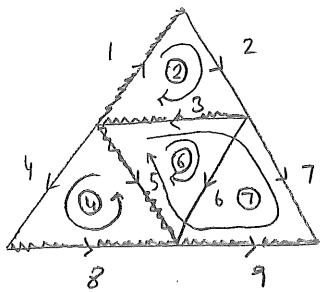Ex

$$\text{cotree} = \{2, 4, 6, 7\}$$

branch 2 defines loop (2), i.e., {2, 3, 1}

branch 4 defines loop (4), i.e., {4, 8, 5}

and so on

At each fund. loop we can

$$(2) : v_2 + v_3 + v_1 = 0$$

obtain voltage equations by KVL:

$$(4) : v_4 + v_8 - v_5 = 0$$

$$(6) : v_6 - v_5 - v_3 = 0$$

$$(7) : v_7 - v_9 - v_5 - v_3 = 0$$

Remark Note that once all the tree branch voltages are known, the remaining (cotree) branch voltages can be computed.

— → —

Summary Given a circuit with planar, nonseparable graph with n nodes & b branches

$A_i = 0$	$Mv = 0$
$v = A^T e$	$i = M^{-1} i_M$

A : reduced incidence matrix, $(n-1) \times b$

M : mesh matrix, $[b - (n-1)] \times b$

i : branch current vector

v : branch voltage vector



i_M : mesh current vector

e : node voltage vector

Duality


Dual graph Given a planar, nonseparable graph G , we construct its dual \hat{G} as follows:

- 1) Assign clockwise direction to each mesh and ccw to outermesh.
- 2) Let branch b_j be touching meshes m_x & m_y . If the direction of b_j is same as m_x and opposite to m_y , then \hat{b}_j leaves node \hat{n}_x and enters \hat{n}_y .

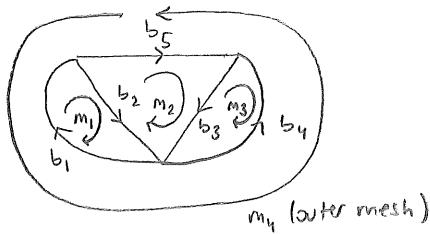
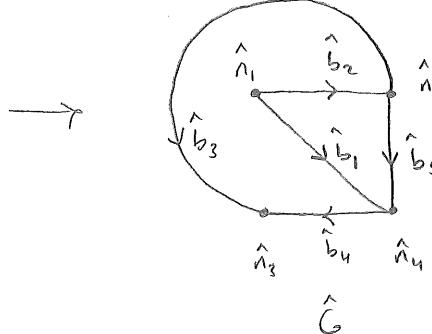
Ex G 

direction of	same as	opposite to
b_1	m_1	m_4
b_2	m_1	m_2
b_3	m_2	m_3
b_4	m_4	m_3
b_5	m_2	m_4

branch	leaves	enters
\hat{b}_1	\hat{n}_1	\hat{n}_4
\hat{b}_2	\hat{n}_1	\hat{n}_2
\hat{b}_3	\hat{n}_2	\hat{n}_3
\hat{b}_4	\hat{n}_4	\hat{n}_3
\hat{b}_5	\hat{n}_2	\hat{n}_4

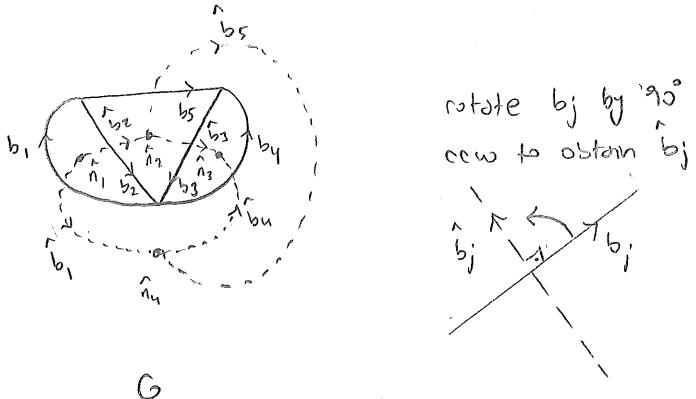shortwt

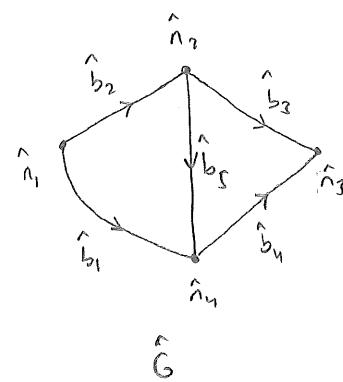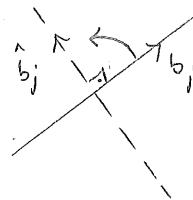rotate b_j by 90°
ccw to obtain \hat{b}_j




Dual circuit Let N be a circuit with only two-terminal elements and planar, nonseparable graph G . Circuit \hat{N} is the dual of circuit N if

- 1) Graph of \hat{N} is \hat{G} (dual of G)
- 2) The branch equation of branch \hat{b} of \hat{N} is obtained from its corresponding equation associated to branch b of N by performing the following substitutions:



variables of N	variables of \hat{N}
v_k	\hat{v}_k
i_k	\hat{i}_k
π_k	$\hat{\pi}_k$
ϕ_k	$\hat{\phi}_k$

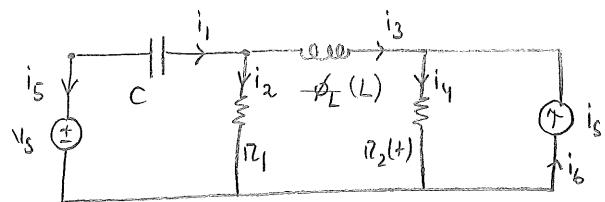Example Let us obtain the dual of the below circuit.




$$\begin{aligned}v_s(t) &= 2 \cos t \text{ V} & C &= 10 \mu\text{F} \\i_5(t) &= 2 \text{ A} & R_4 &= 10 \Omega \\i_L(t) &= \tanh(i_3) \text{ Vs} & R_2(t) &= 2 + \cos t \Omega \\(L = 3 \text{ H})\end{aligned}$$

circuit N

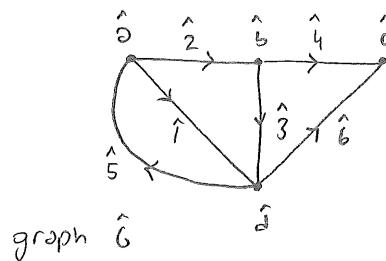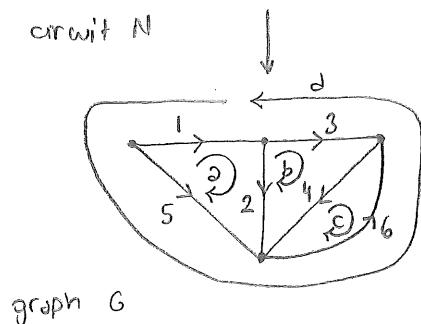
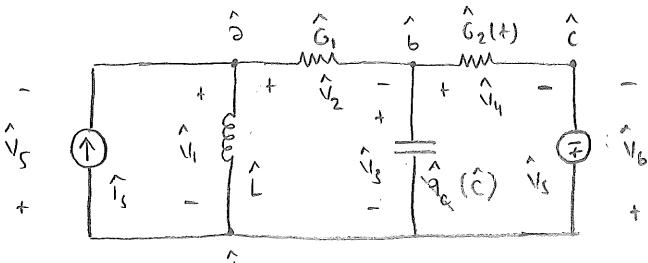
$$\begin{aligned}\hat{i}_s(t) &= 2 \cos t \text{ A} & \hat{L} &= 10 \text{ mH} \\ \hat{i}_5(t) &= 2 \text{ V} & \hat{G}_1 &= 10 \text{ } \Omega \\ \hat{q}_c &= \tanh(\hat{i}_3) C & \hat{G}_2(t) &= 2 + \cos t \text{ } \Omega \\ (\hat{C} = 3 \text{ F})\end{aligned}$$



circuit \hat{N}

At any given time we would have $\hat{v}_k = i_k$ & $\hat{i}_k = v_k$ for $k = 1, 2, \dots, 6$.

— o —

Principle of duality Let N and \hat{N} be dual circuits. Let S be a true statement about N . Obtain statement \hat{S} by replacing each graph-theoretic and electrical word / quantity by its dual. Then \hat{S} is a correct statement about \hat{N} .

Some dual pairs:

node - mesh

fund. cutset - fund. loops

ref. node - outer mesh

tree - cotree

voltage - current

KCL - KVL

charge - flux

resistance (Ω) - conductance (V)

inductor - capacitor

current source - volt. source

short circuit - open circuit

Exercise Think about the physical interpretation of mesh current. (Hint: use mesh current - node voltage duality.).

Ch. II Linear Time-Invariant Resistive Circuits

Q: What is an LTI resistive circuit?

Def. A nonlinear circuit contains a nonlinear R or L or C or dependent source (DS).

A circuit is linear if it is NOT nonlinear.

Def. A time-varying circuit contains a TV R or L or C or DS.


A circuit is time-invariant if it is NOT time-varying.

Def. A dynamic circuit contains an L or C .



A circuit is resistive if it is NOT dynamic.

— o —

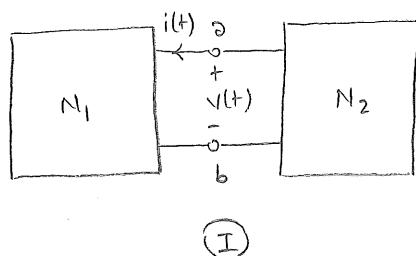Substitution Thm. Consider the two circuits N_1, N_2 below:




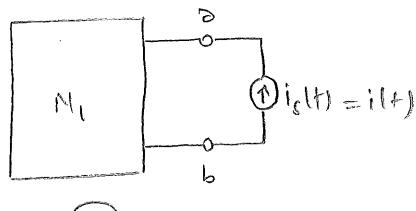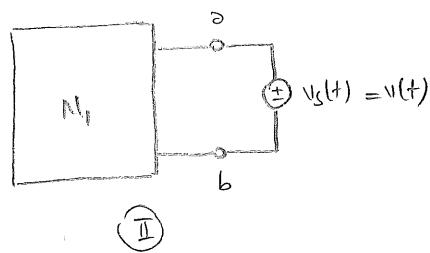We can replace N_2 by either an independent voltage source with $v_s(t) = v(t)$ or by an independent current source with $i_s(t) = i(t)$ without affecting any branch voltage/current inside N_1 .





In other words, an observer inside N_1 cannot tell the difference between the configurations I, II, III.

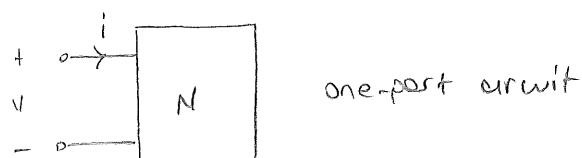Definition A pair of associated terminals is called a port. One-port is a circuit or circuit element that has one pair of terminals accessible from outside:




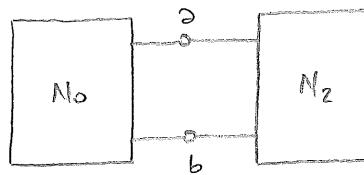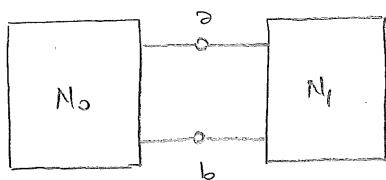Two one-ports are said to be equivalent if they have identical i-v characteristics at the port terminals. Let N_0, N_1, N_2 be one-ports and N_1 be equivalent to N_2 ($N_1 \equiv N_2$). Then for both of the following configurations the set of branch currents and voltages within N_0 will be the same.





$$(N_1 \equiv N_2)$$


Some equivalent one-ports

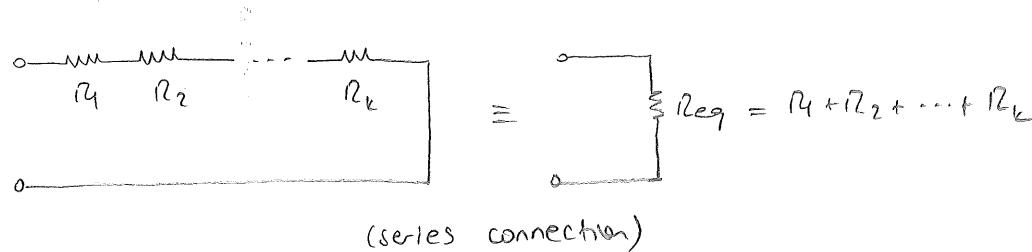


(series connection)

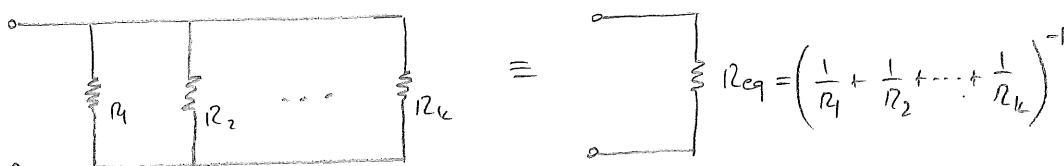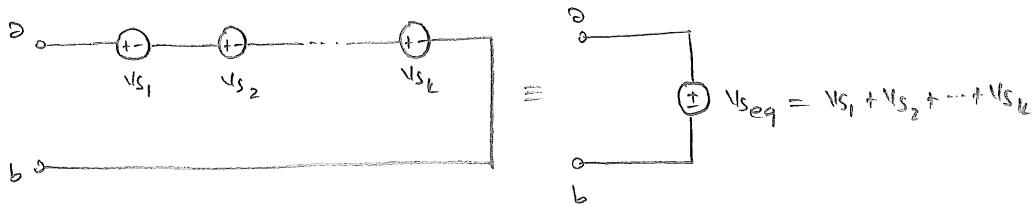


(parallel connection)

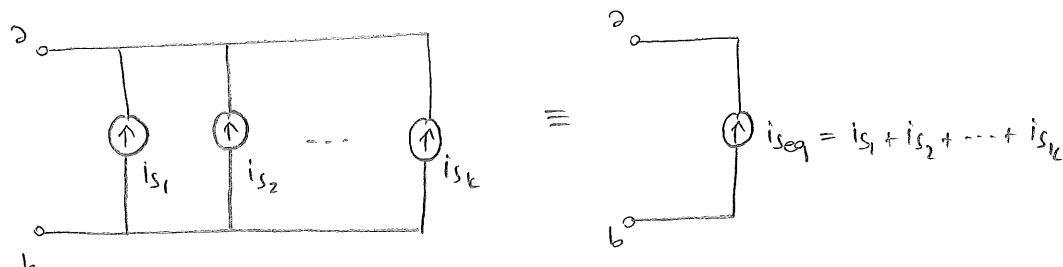

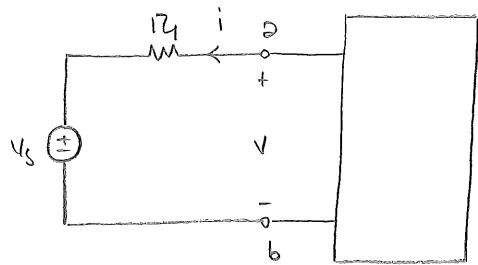


$$v = R_1 i + v_s \quad (1)$$

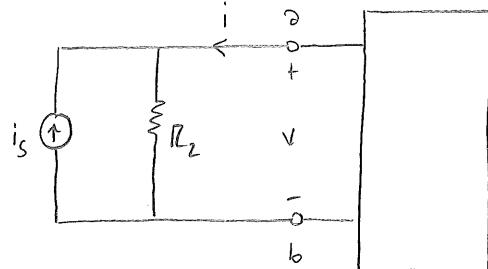

$$v = R_2 (i + i_s)$$


$$\Rightarrow v = R_2 i + R_2 i_s \quad (2)$$

→ The one-port

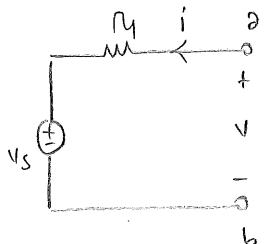

has the I-V char. given in Eq.(1)

→ The one-port


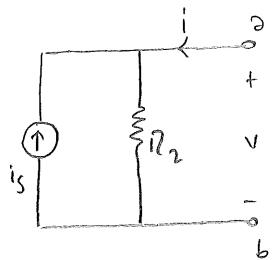


has the I-V char. given in Eq.(2)

Now, take $R_1 = R_2$ and $v_s = R_1 i_s$. Then (1) and (2) become identical.

Hence, one-parts become equivalent.

Ex

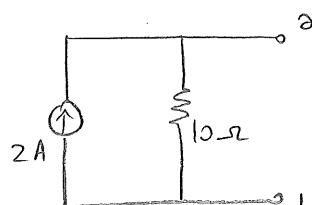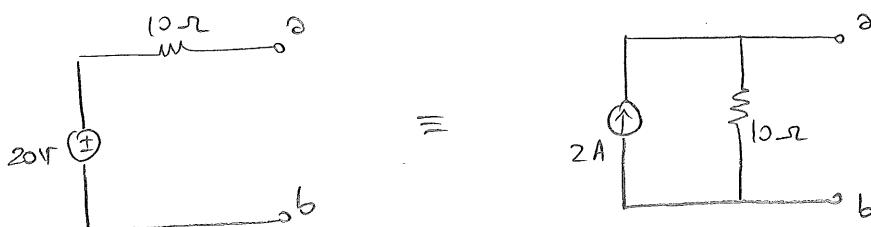


Solving LTI resistive circuits

There are two methods :

- 1) Node voltage analysis
- 2) Mesh current analysis

Node Voltage Analysis

The idea is to solve for node voltages by writing KCL at each node (except the reference node). Note that once the node voltages (e) are known, the branch voltages (v) can be computed easily, $v = A^T e$. And once the branch voltages are known, the branch currents can be computed via terminal equations.

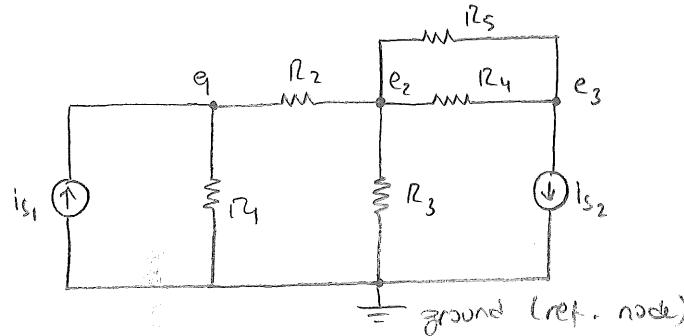Example

procedure:

- choose reference node
- label node voltages
- write KCL

$$\text{KCL at node } \textcircled{1} : -is_1 + i_{R_2} + i_{R_1} = 0 \quad \Rightarrow \quad -is_1 + \frac{e_1}{R_1} + \frac{e_1 - e_2}{R_2} = 0 \quad (1)$$

$$\frac{e_1}{R_1} \leftarrow \frac{V_R}{R_1} \quad \text{by} \quad \frac{V_R}{R_2} \rightarrow \frac{e_1 - e_2}{R_2}$$

$$\text{KCL at node } \textcircled{2} : \frac{e_2 - e_1}{R_2} + \frac{e_2}{R_3} + \frac{e_2 - e_3}{R_4} + \frac{e_2 - e_3}{R_5} = 0 \quad (2)$$

$$\text{KCL at node } \textcircled{3} : \frac{e_3 - e_2}{R_4} + \frac{e_3 - e_2}{R_5} + is_2 = 0 \quad (3)$$

In terms of conductances $G_k = 1/R_k$:

$$(1) \Rightarrow (G_1 + G_2)e_1 - G_2e_2 = is_1$$

$$(2) \Rightarrow -G_2e_1 + (G_2 + G_3 + G_4 + G_5)e_2 - (G_4 + G_5)e_3 = 0$$


$$(3) \Rightarrow -(G_4 + G_5)e_2 + (G_4 + G_5)e_3 = -is_2$$

(*)

$$(*) \Rightarrow \begin{bmatrix} G_1 + G_2 & -G_2 & 0 \\ -G_2 & G_2 + G_3 + G_4 + G_5 & -(G_4 + G_5) \\ 0 & -(G_4 + G_5) & G_4 + G_5 \end{bmatrix} \begin{bmatrix} e_1 \\ e_2 \\ e_3 \end{bmatrix} = \begin{bmatrix} is_1 \\ 0 \\ -is_2 \end{bmatrix}$$

$\underbrace{\quad}_{Y_n: \text{node admittance matrix}} \quad \underbrace{\quad}_e \quad \underbrace{\quad}_{i_s}$

↔ node eqn.'s in
matrix form

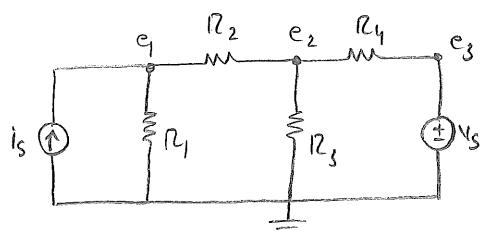Node analysis with voltage sourcesExampleFormulation variables : e_1, e_2, e_3


of eqn. needed = 3

$$\text{Node ①} : -i_s + \frac{e_1}{R_1} + \frac{e_1 - e_2}{R_2} = 0$$

$$\text{Node ②} : \frac{e_2 - e_1}{R_2} + \frac{e_2}{R_3} + \frac{e_2 - e_3}{R_4} = 0$$

Node ③ : KCL does not give us a useful equation (in terms of e_1, e_2, e_3) here!
However, note that $e_3 = v_s$ (this is the third equation)

Remark When there is an ind. voltage source v_s between the ground and some node k , we do not consider the node voltage e_k as a formulation variable (since it is NOT an unknown, $e_k = v_s$)

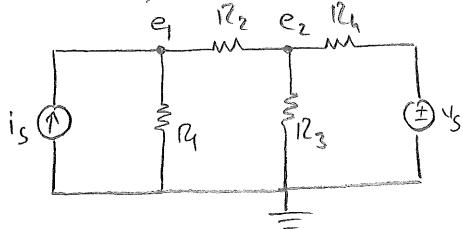Example (revisited)Formulation var. : e_1, e_2

of eqn. needed = 2

$$\text{Node ①} : -i_s + \frac{e_1}{R_1} + \frac{e_1 - e_2}{R_2} = 0$$

$$\text{Node ②} : \frac{e_2 - e_1}{R_2} + \frac{e_2}{R_3} + \frac{e_2 - v_s}{R_4} = 0$$


$$\left. \begin{array}{l} \\ \end{array} \right\} \begin{bmatrix} \frac{1}{R_1} + \frac{1}{R_2} & -\frac{1}{R_2} \\ -\frac{1}{R_2} & \frac{1}{R_2} + \frac{1}{R_3} + \frac{1}{R_4} \end{bmatrix} \begin{bmatrix} e_1 \\ e_2 \end{bmatrix} = \begin{bmatrix} i_s \\ \frac{v_s}{R_4} \end{bmatrix}$$

Modified node analysis

When there is a voltage source (dependent or independent) between two (non-ground) nodes a and b , we cannot express the current through it in terms of e_a and e_b . In such cases we do either of the following :

Method 1 Let the (unknown) current i through the voltage source be one of your formulation variables.

Example

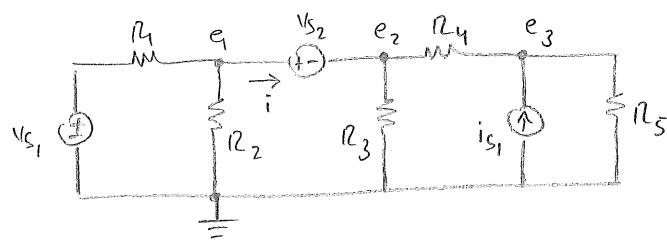

formulation var.: e_1, e_2, e_3, i

$$\text{Node ① : } \frac{e_1 - v_{s_1}}{R_1} + \frac{e_1}{R_2} + i = 0$$

$$\text{Node ② : } -i + \frac{e_2}{R_3} + \frac{e_2 - e_3}{R_4} = 0$$


$$\text{Node ③ : } \frac{e_3 - e_2}{R_5} - i_{s_1} + \frac{e_3}{R_4} = 0$$

$$\text{constraint eqn: } e_1 - e_2 = v_{s_2}$$

$$\left\{ \begin{array}{l} \left[\begin{array}{cccc} G_1+G_2 & 0 & 0 & 1 \\ 0 & G_3+G_4 & -G_4 & -1 \\ 0 & -G_4 & G_4+G_5 & 0 \\ 1 & -1 & 0 & 0 \end{array} \right] \begin{bmatrix} e_1 \\ e_2 \\ e_3 \\ i \end{bmatrix} = \begin{bmatrix} G_1 v_{s_1} \\ 0 \\ i_{s_1} \\ v_{s_2} \end{bmatrix} \\ G_K = 1/R_K \end{array} \right.$$

Method 2 Write KCL pretending that the two nodes (between which there is the voltage source) are a single node. Such node is called a supernode.

Example (revisited)

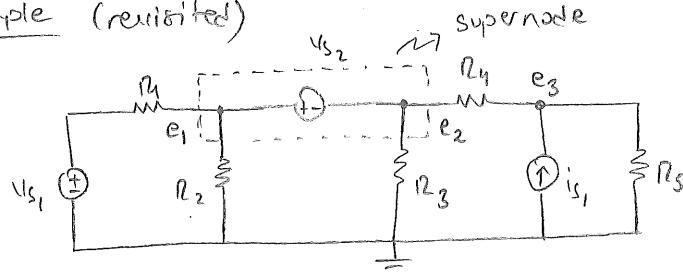

formulation var.: e_1, e_2, e_3

$$\text{Supernode ① : } \frac{e_1 - v_{s_1}}{R_1} + \frac{e_1}{R_2} + \frac{e_2}{R_3} + \frac{e_2 - e_3}{R_4} = 0$$


$$\text{Node ③ : } \frac{e_3 - e_2}{R_5} - i_{s_1} + \frac{e_3}{R_4} = 0$$

$$\text{constraint : } e_1 - e_2 = v_{s_2}$$

$$\left\{ \begin{array}{l} \left[\begin{array}{ccc} G_1+G_2 & G_3+G_4 & -G_4 \\ 0 & -G_4 & G_4+G_5 \\ 1 & -1 & 0 \end{array} \right] \begin{bmatrix} e_1 \\ e_2 \\ e_3 \end{bmatrix} = \begin{bmatrix} G_1 v_{s_1} \\ i_{s_1} \\ v_{s_2} \end{bmatrix} \end{array} \right.$$

Node equations in matrix form

Node equations

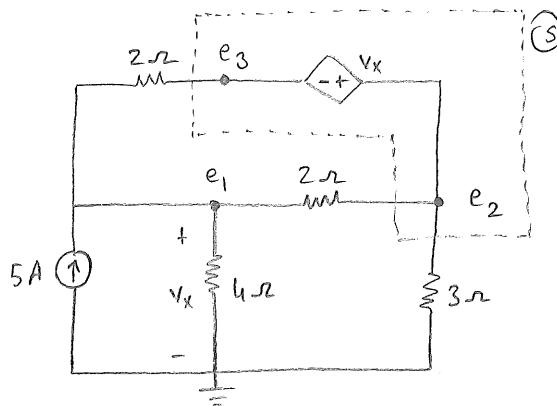Example

Find the power absorbed by the 3 ohm resistor.

$$KCL \text{ at node } 1 : -5 + \frac{e_1 - e_3}{2} + \frac{e_1}{4} + \frac{e_2 - e_3}{2} = 0 \quad (1)$$

$$KCL \text{ at node } 3 : \frac{e_3 - e_1}{2} + \frac{e_2 - e_1}{2} + \frac{e_2}{3} = 0 \quad (2)$$

$$\text{constraint eqn. : } e_2 - e_3 = v_x \quad \left. \begin{array}{l} e_2 - e_3 = e_1 \\ v_x = e_1 \end{array} \right\} \quad (3)$$

$$(1) \Rightarrow \left(\frac{1}{2} + \frac{1}{4} + \frac{1}{2} \right) e_1 - \frac{1}{2} e_2 - \frac{1}{2} e_3 = 5 \quad \stackrel{(3)}{\Rightarrow} \quad \frac{5}{4} (e_2 - e_3) - \frac{1}{2} e_2 - \frac{1}{2} e_3 = 5$$

$$\Rightarrow \frac{3}{4} e_2 - \frac{7}{4} e_3 = 5 \quad (4)$$

$$(2) \Rightarrow -\left(\frac{1}{2} + \frac{1}{2}\right) e_1 + \left(\frac{1}{2} + \frac{1}{3}\right) e_2 + \frac{1}{2} e_3 = 0 \quad \stackrel{(3)}{\Rightarrow} \quad -(e_2 - e_3) + \frac{5}{6} e_2 + \frac{1}{2} e_3 = 0$$

$$\Rightarrow -\frac{1}{6} e_2 + \frac{3}{2} e_3 = 0 \quad \Rightarrow \quad e_3 = \frac{1}{9} e_2 \quad (5)$$

$$(4) \& (5) \Rightarrow \frac{3}{4} e_2 - \frac{7}{4} \cdot \frac{1}{9} e_2 = 5 \quad \Rightarrow \quad \frac{26}{36} e_2 = 5 \quad \Rightarrow \quad e_2 = 9V \quad (e_3 = 1V, e_1 = 8V)$$

$$P_{3\text{-ohm}} = \frac{e_2^2}{3} = \frac{9^2}{3} = \boxed{27\text{W}}$$


Remark When there is a dependent source between node k and ground, do NOT write KCL at node k (because you cannot). Figure out the constraint eqn. introduced by the dep. source.

Exercise Redo the previous example by choosing node 3 as ground.

Mesh Current Analysis [Dual of Node Voltage Analysis]

The idea is to solve for mesh currents by writing KVL at inner meshes.

Example

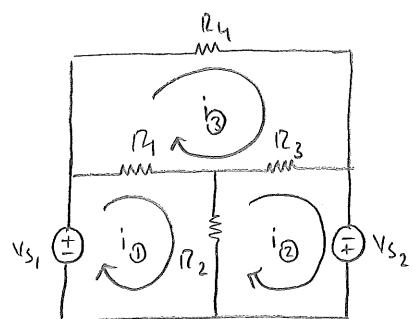

Formulation variables i_1, i_2, i_3

(mesh currents. by convention their directions are chosen cw.)

$$\text{KVL at mesh } ①: -VS_1 + VR_1 + VR_2 = 0$$

$$R_1(i_1 - i_3) \leftarrow R_1 i_1, \quad R_2 i_2 \rightarrow R_2(i_1 - i_2)$$

$$\Rightarrow -VS_1 + R_1(i_1 - i_3) + R_2(i_1 - i_2) = 0 \quad (1)$$

$$\text{KVL at mesh } ②: -VS_2 + R_2(i_2 - i_1) + R_3(i_2 - i_3) = 0 \quad (2)$$


$$\text{KVL at mesh } ③: R_4 i_3 + R_3(i_3 - i_2) + R_1(i_3 - i_1) = 0 \quad (3)$$

$$(1), (2), (3) \Rightarrow \begin{bmatrix} R_1 + R_2 & -R_2 & -R_1 \\ -R_2 & R_2 + R_3 & -R_3 \\ -R_1 & -R_3 & R_1 + R_3 + R_4 \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \\ i_3 \end{bmatrix} = \begin{bmatrix} VS_1 \\ VS_2 \\ 0 \end{bmatrix}$$

$\underbrace{\quad}_{Z_m: \text{ mesh-impedance}} \quad \underbrace{i_m}_{\text{matrix}} \quad \underbrace{VS}_{\text{matrix}}$

Mesh Analysis with current sources

Example

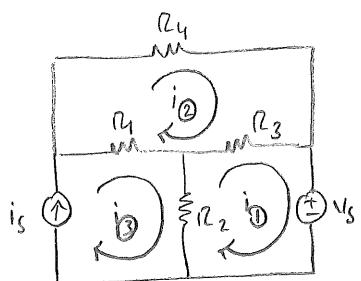

Note that $i_3 = i_s$, therefore known.

Formulation var.: i_1, i_2

$$\text{KVL at } \textcircled{1} : R_2(i_1 - i_s) + R_3(i_1 - i_2) + v_s = 0 \quad \left. \begin{array}{l} \\ \end{array} \right\} \Rightarrow \begin{bmatrix} R_2 + R_3 & -R_3 \\ -R_3 & R_2 + R_3 + R_4 \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \end{bmatrix} = \begin{bmatrix} R_2 i_s - v_s \\ R_4 i_s \end{bmatrix}$$


$$\text{KVL at } \textcircled{2} : R_4(i_2 - i_s) + R_2 i_2 + R_3(i_2 - i_1) = 0$$

Modified Mesh Analysis

When there is a current source between two inner meshes we cannot express its voltage in terms of mesh currents. In such a case we do either of the following:

Method 1 Let the (unknown) voltage v across the current source be one of our formulation variables.

Example

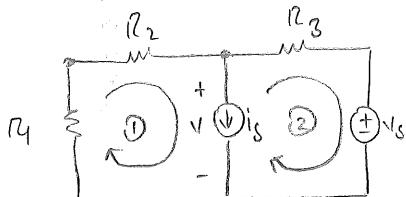


formulation var. : i_1, i_2, v

$$\left. \begin{array}{l} \text{mesh } \textcircled{1} : (R_1 + R_2)i_1 + v = 0 \\ \text{mesh } \textcircled{2} : R_3 i_2 + v_s - v = 0 \\ \text{constraint: } i_1 - i_2 = i_s \end{array} \right\} \begin{bmatrix} R_1 + R_2 & 0 & 1 \\ 0 & R_3 & -1 \\ 1 & -1 & 0 \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \\ v \end{bmatrix} = \begin{bmatrix} 0 \\ -v_s \\ i_s \end{bmatrix}$$

Method 2 Write KVL pretending that the two meshes (between which there is the current source) are a single mesh. Such mesh is called a supermesh.

Example

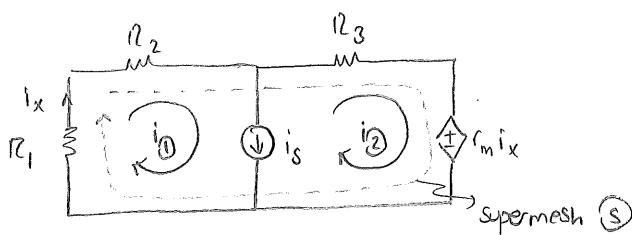


formulation var. : i_1, i_2

$$\left. \begin{array}{l} \text{KVL at supermesh } \textcircled{S} : (R_1 + R_2)i_1 + R_3 i_2 + r_{mix} = 0 \\ i_x = i_1 \end{array} \right\} (R_1 + R_2 + r_m)i_1 + R_3 i_2 = 0 \quad (1)$$

$$\text{constraint eqn. : } i_1 - i_2 = i_s \quad (2)$$

$$(1) \& (2) \Rightarrow \begin{bmatrix} R_1 + R_2 + r_m & R_3 \\ 1 & -1 \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \end{bmatrix} = \begin{bmatrix} 0 \\ i_s \end{bmatrix}$$

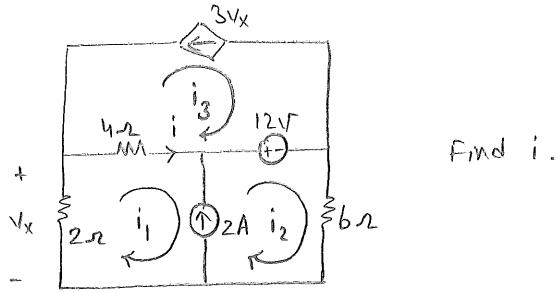ExampleFind i .Mesh Current Formulation

$$\text{supermesh (1) \& (2)} : 2i_1 + 4(i_1 - i_3) + 12 + 6i_2 = 0$$


$$\Rightarrow 6i_1 + 6i_2 - 4i_3 = -12 \quad (1)$$

$$\begin{aligned} \text{constraint 1: } i_3 &= -3Vx \\ Vx &= -2i_1 \end{aligned} \quad \left. \begin{array}{l} i_3 = 6i_1 \\ \hline \end{array} \right\} \quad (2)$$

$$\text{constraint 2: } i_2 - i_1 = 2 \Rightarrow i_2 = i_1 + 2 \quad (3)$$

$$(1), (2), (3) \Rightarrow 6i_1 + 6(i_1 + 2) - 4(6i_1) = -12 \Rightarrow -12i_1 = -24 \Rightarrow i_1 = 2A \quad (4)$$

$$(2) \& (4) \Rightarrow i = i_1 - i_3 = i_1 - 6i_1 = -5i_1 = \boxed{-10A}$$

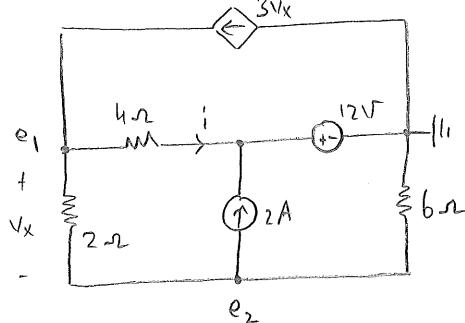Node Voltage Formulation

$$\begin{aligned} \text{Node (1)} : \frac{e_1 - e_2}{2} + \frac{e_1 - 12}{4} - 3Vx &= 0 \quad \& \quad Vx = e_1 - e_2 \\ \Rightarrow \left(\frac{1}{2} + \frac{1}{4} - 3\right)e_1 + \left(-\frac{1}{2} + 3\right)e_2 &= 3 \\ \Rightarrow -\frac{9}{4}e_1 + \frac{5}{2}e_2 &= 3 \quad (1) \end{aligned}$$


$$\begin{aligned} \text{Node (2)} : 2 + \frac{e_2 - e_1}{2} + \frac{e_2}{6} &= 0 \\ \Rightarrow -\frac{1}{2}e_1 + \frac{2}{3}e_2 &= -2 \quad (2) \end{aligned}$$

$$(1) \& (2) \Rightarrow \underbrace{\begin{bmatrix} -9/4 & 5/2 \\ -1/2 & 2/3 \end{bmatrix}}_{Y} \begin{bmatrix} e_1 \\ e_2 \end{bmatrix} = \begin{bmatrix} 3 \\ -2 \end{bmatrix} \Rightarrow \begin{bmatrix} e_1 \\ e_2 \end{bmatrix} = \underbrace{\frac{1}{-9/4 + 5/2} \begin{bmatrix} 2/3 & -5/2 \\ 1/2 & -9/4 \end{bmatrix}}_{Y^{-1}} \begin{bmatrix} 3 \\ -2 \end{bmatrix} = \begin{bmatrix} -28 \\ -24 \end{bmatrix}$$


$$\text{Hence, } i = \frac{e_1 - 12}{4} = \frac{-28 - 12}{4} = \boxed{-10A}$$


Input Resistances of LTI Resistive One-Ports


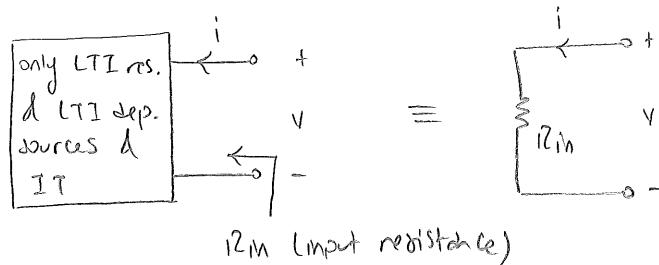
A one-port consisting only of ideal transformers, LTI resistors, and LTI dependent sources (whose control variables are within the one-port) is equivalent to a single LTI resistor.



Example

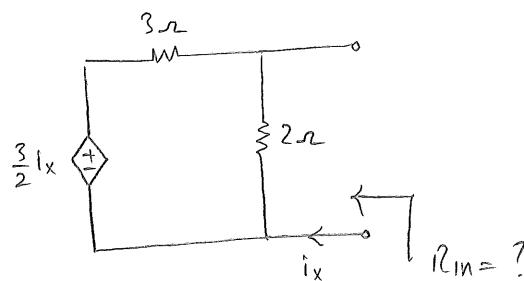

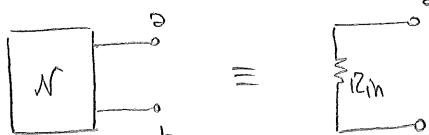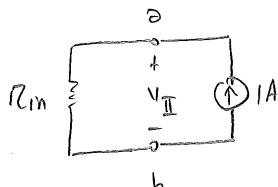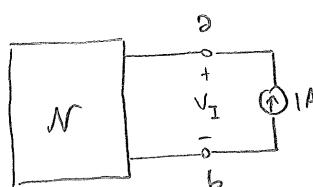Idea If  then we must have $v_I = v_{II}$ for the following configurations



$$R_{in} = \frac{v_{II}}{1} = v_I \xrightarrow{\text{can be computed by solving the circuit in config. I.}}$$

↓
unknown

Sol'n


$$\frac{e_1 - \frac{3}{2} i_x}{3} + \frac{e_1}{2} - 1 = 0 \quad \& \quad i_x = -1A$$

$$\Rightarrow \frac{e_1 + 3/2}{3} + \frac{e_1}{2} - 1 = 0 \Rightarrow \frac{5}{6} e_1 = \frac{1}{2}$$

$$\Rightarrow e_1 = \frac{3}{5} V \Rightarrow v_I = \frac{3}{5} V \Rightarrow R_{in} = \frac{3}{5} \Omega$$

Δ-Y Transform

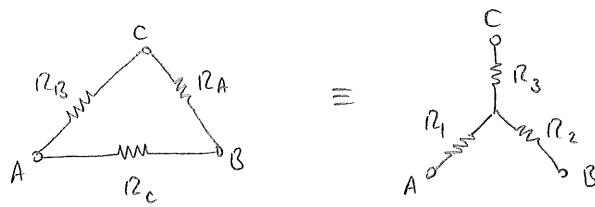Suppose the below 3-T components are equivalent.



Find the transformation relations between the triples (R_A, R_B, R_C) & (R_1, R_2, R_3) .

Ideas Equate the equiv. resistances seen between the terminals A-B, B-C, & C-A.

$$R_{AB} = R_C / \parallel (R_A + R_B) = \frac{R_C (R_A + R_B)}{R_A + R_B + R_C} = R_1 + R_2 \quad (1)$$

$$R_{BC} = \frac{R_A (R_B + R_C)}{R_A + R_B + R_C} = R_2 + R_3 \quad (2) \quad \& \quad R_{CA} = \frac{R_B (R_C + R_A)}{R_A + R_B + R_C} = R_1 + R_3 \quad (3)$$

$$(1) + (2) + (3) \Rightarrow \cancel{\frac{R_A R_B + R_B R_C + R_C R_A}{R_A + R_B + R_C}} = \cancel{(R_1 + R_2 + R_3)} \quad (4)$$


$$(4) - (2) \Rightarrow R_1 = \boxed{\frac{R_B R_C}{R_A + R_B + R_C}} \quad (4) - (3) \Rightarrow R_2 = \boxed{\frac{R_C R_A}{R_A + R_B + R_C}} \quad (4) - (1) \Rightarrow R_3 = \boxed{\frac{R_A R_B}{R_A + R_B + R_C}}$$

Now, write

$$R_1 R_2 + R_2 R_3 + R_3 R_1 = \frac{R_A R_B R_C (R_A + R_B + R_C)}{(R_A + R_B + R_C)^2} = \frac{R_A R_B R_C}{R_A + R_B + R_C} = R_A R_1 = R_B R_2 = R_C R_3$$

$$\Rightarrow R_A = \boxed{\frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_1}}, \quad R_B = \boxed{\frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_2}}, \quad \& \quad R_C = \boxed{\frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_3}}$$


Remark :

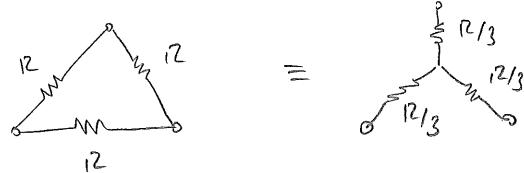

Exercise Find the transformation relations between the triples (G_A, G_B, G_C) & (G_1, G_2, G_3)


$$[G_\square = 1/R_\square]$$

Example

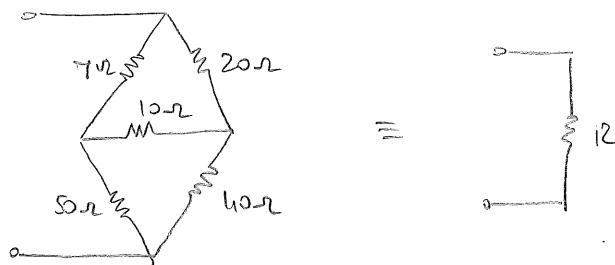

Find R .

Sol:

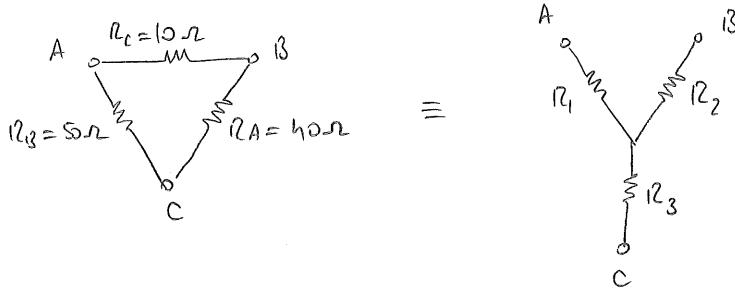


$$R_1 = \frac{R_B R_C}{R_A + R_B + R_C} = \frac{500}{100} = 5\Omega$$

$$R_2 = \frac{R_C R_A}{R_A + R_B + R_C} = \frac{400}{100} = 4\Omega$$

$$R_3 = \frac{R_A R_B}{R_A + R_B + R_C} = \frac{200}{100} = 20\Omega$$


Then

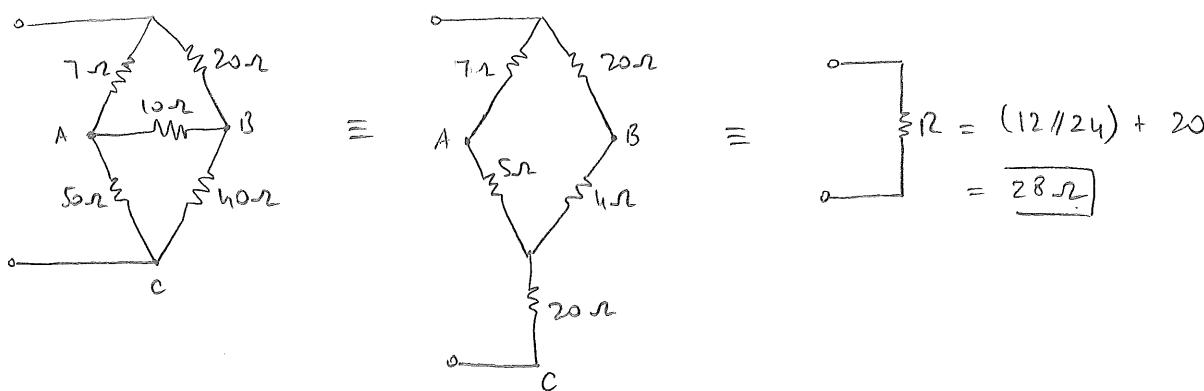

Linearity

Consider an LTI resistive circuit. Let output y be any branch voltage/current. Let the vector $u = [v_1 \ v_2 \ \dots \ v_m]^T$ be the input vector whose entries are the voltages of the IRS's and the currents of the ICS's in the circuit.

Ex

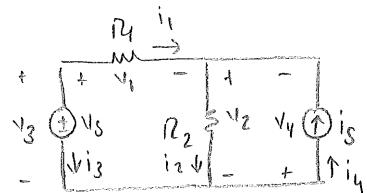


output y can be any one of these:

$$i_1, v_1, i_2, v_2, i_3, v_3, i_4, v_4$$

input vector: $u = \begin{bmatrix} v_s \\ i_s \end{bmatrix}$

Linearity: For each output y , there exists $k \in \mathbb{R}^{1 \times m}$, $k = [k_1 \ k_2 \ \dots \ k_m]$

such that $\boxed{y = ku}$ That is, $y(t) = k_1 u_1(t) + k_2 u_2(t) + \dots + k_m u_m(t)$.

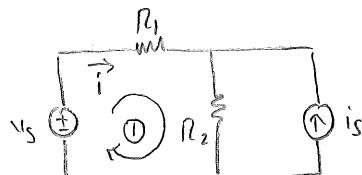
Example

For the output $y = i$ find k_1 & k_2 such that

$$i = k_1 v_s + k_2 i_s.$$

LNL at ①: $-v_s + R_1 i + R_2(i + i_s) = 0$

$$\Rightarrow i = \frac{1}{R_1 + R_2} v_s - \frac{R_2}{R_1 + R_2} i_s \Rightarrow k_1 = \frac{1}{R_1 + R_2}, \ k_2 = -\frac{R_2}{R_1 + R_2}$$

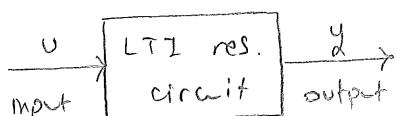Block diagram representation

Note that y is a function of u .

That is, $y = y(u)$.

A direct implication of linearity is


$$\boxed{y(\alpha u + \beta v) = \alpha y(u) + \beta y(v)}$$

where u, v : mat vectors ; α, β : real numbers.

Example

$$V_s = 20V$$

$$i_s = 4A$$

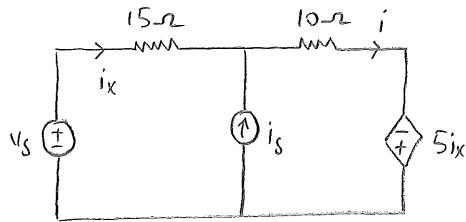

Find i by superposition (i.e. consider one ind. source at a time)

input vector $v = \begin{bmatrix} V_s \\ i_s \end{bmatrix}_{2 \times 1}$. Linearity implies: $\exists k = [k_1 \ k_2]_{1 \times 2}$ exists such that $i = kv$.


$$\text{We can write } i = k \begin{bmatrix} V_s \\ i_s \end{bmatrix} = k \left(\begin{bmatrix} V_s \\ 0 \end{bmatrix} + \begin{bmatrix} 0 \\ i_s \end{bmatrix} \right)$$

$$= k \underbrace{\begin{bmatrix} V_s \\ 0 \end{bmatrix}}_{i_1} + k \underbrace{\begin{bmatrix} 0 \\ i_s \end{bmatrix}}_{i_2}$$

i_1 : the current passing through 10Ω resistor when $i_s = 0$ (when ind. current source is killed)

i_2 : the current passing through 10Ω resistor when $V_s = 0$ (when ind. voltage source is killed)


To compute i_1 , kill the current source

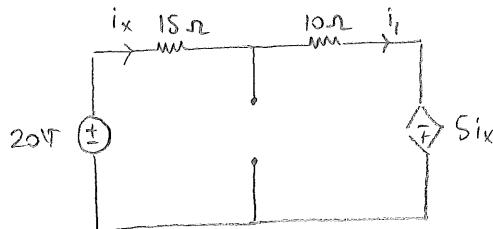

$$\text{KVL: } -20 + 15i_x + 10i_1 - 5i_x = 0 \quad (i_x = i_1)$$

$$\Rightarrow 20i_1 = 20 \Rightarrow \boxed{i_1 = 1A}$$

To compute i_2 , kill the voltage source

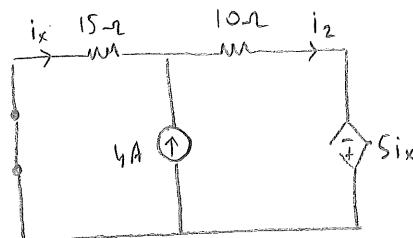

$$\text{KVL: } 15i_x + 10i_2 - 5i_x = 0 \quad (i_x = i_2 - 4)$$

$$\Rightarrow 20i_2 = 40 \Rightarrow \boxed{i_2 = 2A}$$


Finally, to find i we superpose i_1, i_2 : $i = i_1 + i_2 = \boxed{3A}$

Remark killing an IVS means replacing it with short circuit.

killing an ICS means replacing it with open circuit.

Warning: Do NOT kill dependent sources. (Because they are not inputs.)

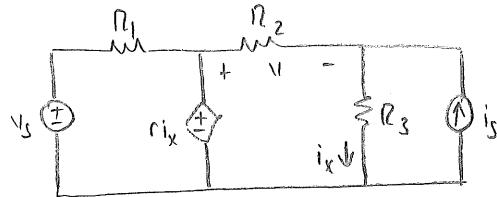Example Three experiments are performed on the below circuit.



	v_s	i_s	v
Exp #1	12V	0	v_1
Exp #2	-6V	6A	v_2
Exp #3	4V	4A	v_3

Express v_3 in terms of v_1 & v_2 .

Sol'n By linearity there exists $\mathbf{K} \in \mathbb{R}^{1 \times 2}$ such that $v = \mathbf{K} \begin{bmatrix} v_s \\ i_s \end{bmatrix}$

$$\text{exp\#1} \Rightarrow v_1 = \mathbf{K} \begin{bmatrix} 12 \\ 0 \end{bmatrix} \quad \left. \begin{array}{l} \\ \end{array} \right\} \quad \left. \begin{array}{l} [v_1 \ v_2] = \mathbf{K} \begin{bmatrix} 12 & -6 \\ 0 & 6 \end{bmatrix} \\ \Rightarrow \mathbf{K} = [v_1 \ v_2] \begin{bmatrix} 12 & -6 \\ 0 & 6 \end{bmatrix}^{-1} \end{array} \right.$$

$$\text{exp\#2} \Rightarrow v_2 = \mathbf{K} \begin{bmatrix} -6 \\ 6 \end{bmatrix}$$

$$\text{exp\#3} \Rightarrow v_3 = \mathbf{K} \begin{bmatrix} 4 \\ 4 \end{bmatrix} = \underbrace{[v_1 \ v_2] \begin{bmatrix} \frac{1}{12} & \frac{1}{6} \\ 0 & \frac{1}{6} \end{bmatrix}}_{\mathbf{K}} \begin{bmatrix} 4 \\ 4 \end{bmatrix} = \underbrace{\frac{2}{3}v_1 + \frac{2}{3}v_2}_{\begin{bmatrix} 2/3 \\ 2/3 \end{bmatrix}}$$


$$\text{or}, \quad v_3 = v \begin{pmatrix} 4 \\ 4 \end{pmatrix} = v \left(\alpha \begin{bmatrix} 12 \\ 0 \end{bmatrix} + \beta \begin{bmatrix} -6 \\ 6 \end{bmatrix} \right) = \alpha \cdot v \begin{pmatrix} 12 \\ 0 \end{pmatrix} + \beta \cdot v \begin{pmatrix} -6 \\ 6 \end{pmatrix} = \alpha v_1 + \beta v_2$$

$$\Rightarrow \alpha \begin{bmatrix} 12 \\ 0 \end{bmatrix} + \beta \begin{bmatrix} -6 \\ 6 \end{bmatrix} = \begin{bmatrix} 4 \\ 4 \end{bmatrix} \Rightarrow \begin{cases} 12\alpha - 6\beta = 4 \\ 6\beta = 4 \end{cases} \quad \left. \begin{array}{l} \alpha = \frac{2}{3}, \beta = \frac{2}{3} \\ \end{array} \right\} \text{as expected.}$$

Thevenin & Norton Equivalent Circuits

Recall: two one-parts are equivalent if they have identical i-v char.

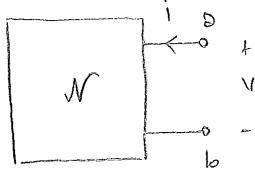
Thevenin's Theorem Consider the below one-part, where N is an LTI resistive circuit satisfying:



(A1) Any dep. source in N has its control var. also in N .


(A2) One-part is both voltage- and current-controlled.

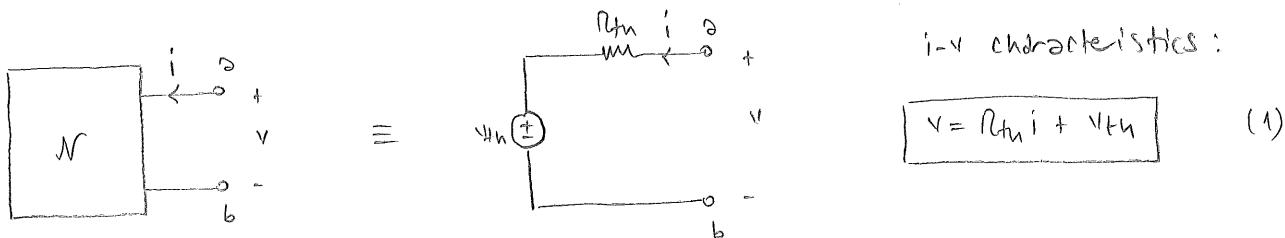Then we can find v_{th} , i_N and establish the below equivalence



Norton's Theorem Under the same conditions (A1) & (A2) we can find i_N , R_N


and the below equivalence holds

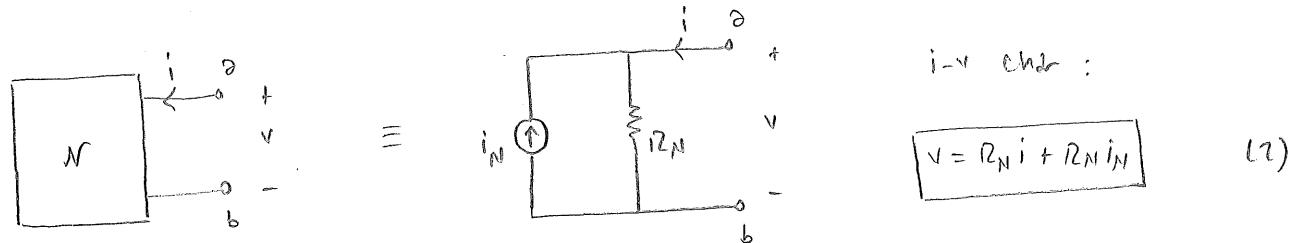


Remark Since (1) \equiv (2) we have to have $R_{th} = R_N$ and $v_{th} = R_{th}i_N$.

Computing v_{th} , R_{th} , i_N (pr a given one-port N)


1) Open circuit voltage equals v_{th} :

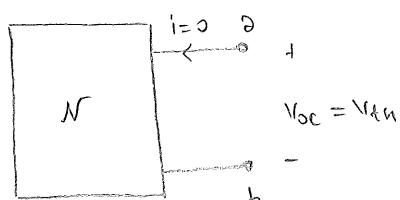


2) Short circuit current equals i_N :

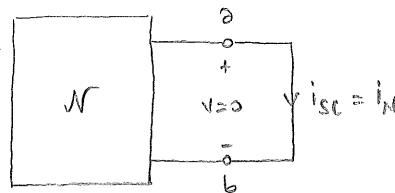

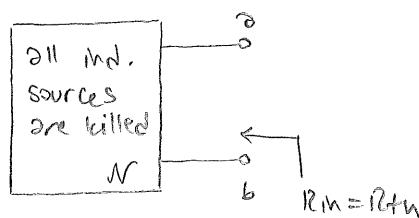3) Once v_{th} and i_N are known we have $R_{th} = v_{th}/i_N$. Another way to obtain R_{th} is to kill all independent sources within N and compute the input resistance:



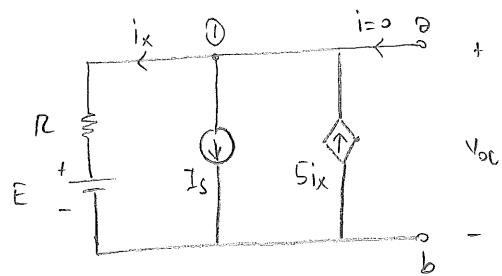Example Find the Thevenin and Norton equivalents of the below one-port.




Step 1 Find the open-circuit voltage v_{oc} .

$$\text{KCL at } \textcircled{1}: i_x + I_s - S_{ix} = 0 \Rightarrow i_x = \frac{1}{4} I_s$$

$$v_{oc} = R i_x + E = \frac{R}{4} I_s + E$$

$$\Rightarrow v_{th} = \frac{R}{4} I_s + E$$

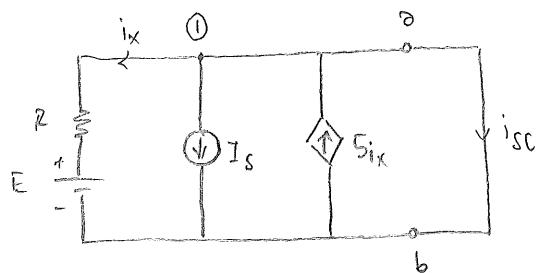Step 2 Find the short-circuit current i_{sc} .



$$R i_x + E = 0 \Rightarrow i_x = -\frac{E}{R}$$


$$\text{KCL at } \textcircled{1}: i_x + I_s - S_{ix} + i_{sc} = 0$$

$$\Rightarrow i_{sc} = -I_s + i_x = -I_s - \frac{4}{R} E$$

$$\Rightarrow i_N = -I_s - \frac{4}{R} E$$

Step 3 Find R_{th} . $R_{th} = \frac{V_{th}}{I_N} = \frac{\frac{R}{4} I_S + E}{-(I_S + \frac{E}{R})} \Rightarrow R_{th} = -\frac{R}{4}$

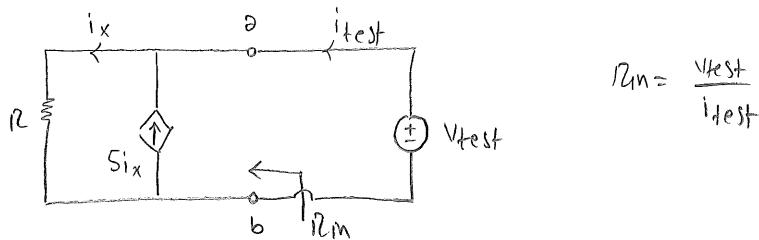Alternative way to compute R_{th} : kill all ind. sources.




Choose $V_{test} = 1V$. Then $i_x = \frac{V_{test}}{R} = \frac{1}{R}$

I_{CL} $\Rightarrow i_x - S_{i_x} - i_{test} = 0 \Rightarrow i_{test} = -i_x = -\frac{1}{R}$

$R_{th} = \frac{V_{test}}{i_{test}} = \frac{1}{-\frac{1}{R}} = -R$ as expected.

Therefore

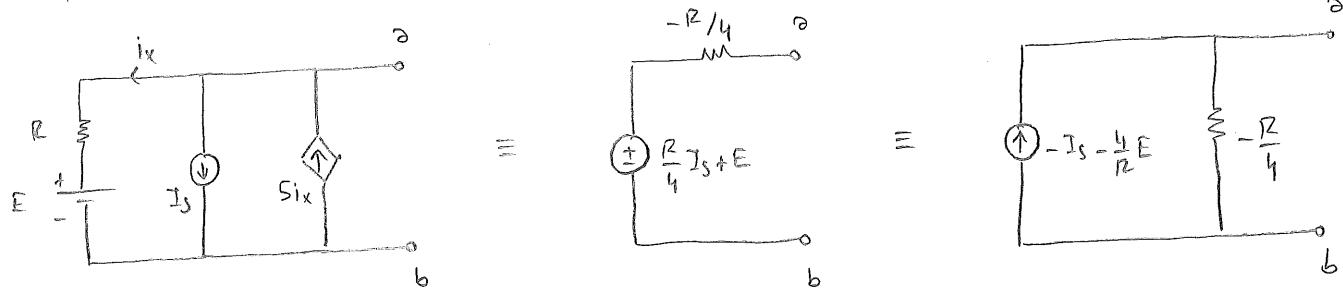


thévenin equiv.


norton equiv.

Example Find the thévenin equiv. circuit as viewed by the resistor R .

What should R be so that $V_{12} = -7V$.

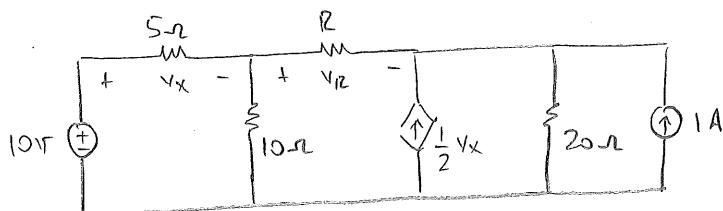

Sol'n First. Remove 12 and find V_{OC} .

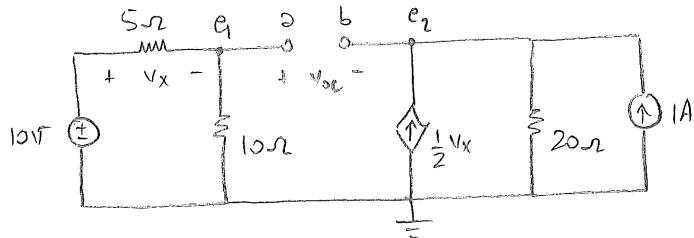


$$\text{Node } ① : \frac{e_1 - 10}{5} + \frac{e_1}{10} = 0 \Rightarrow e_1 = \frac{20}{3} \text{ V}$$

$$\begin{aligned} \text{Node } ② : -\frac{1}{2}v_x + \frac{e_2}{20} - 1 &= 0 \\ v_x = 10 - e_1 = \frac{10}{3} \text{ V} &\quad \left. \begin{aligned} -\frac{5}{3} + \frac{e_2}{20} - 1 &= 0 \Rightarrow e_2 = \frac{160}{3} \text{ V} \end{aligned} \right\} \end{aligned}$$

$$V_{OC} = e_1 - e_2 = \frac{20}{3} - \frac{160}{3} = -\frac{140}{3} \text{ V} \Rightarrow V_{TH} = -\frac{140}{3} \text{ V}$$

Then. Find i_{SC} .

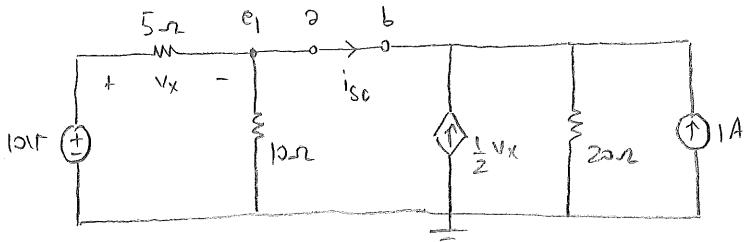


$$\begin{aligned} \text{kCL at node } ① : \frac{e_1 - 10}{5} + \frac{e_1}{10} - \frac{1}{2}v_x + \frac{e_1}{20} - 1 &= 0 \\ v_x = 10 - e_1 &\quad \left. \begin{aligned} \left(\frac{1}{5} + \frac{1}{10} + \frac{1}{2} + \frac{1}{20} \right) e_1 &= 1 + 2 + 5 \Rightarrow e_1 = \frac{160}{17} \text{ V} \end{aligned} \right\} \end{aligned}$$

$$\text{Once again kCL at node } ① : \frac{e_1 - 10}{5} + \frac{e_1}{10} + i_{SC} = 0 \Rightarrow i_{SC} = 2 - \frac{3}{10} e_1 = -\frac{14}{17} \text{ A} \Rightarrow I_N = -\frac{14}{17} \text{ A}$$

$$\text{Hence } R_{TH} = \frac{V_{TH}}{I_N} = \frac{-\frac{140}{3}}{-\frac{14}{17}} = \frac{170}{3} \Omega$$

Finally,

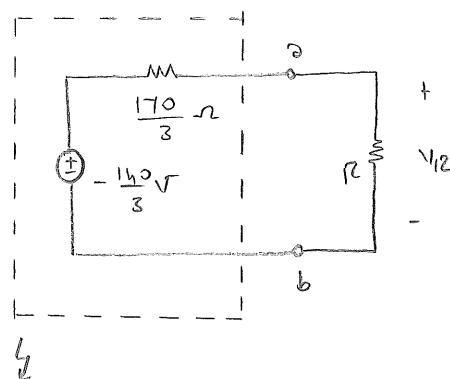

Want: $v_{12} = -7V$


design parameter: R

$$v_R = \frac{12}{12 + \frac{170}{3}} \cdot \left(-\frac{140}{3} \right) = -7$$


thenenin equiv.

seen by 12

$$\Rightarrow \frac{140R}{3R+170} = 7 \Rightarrow R = 10\Omega$$

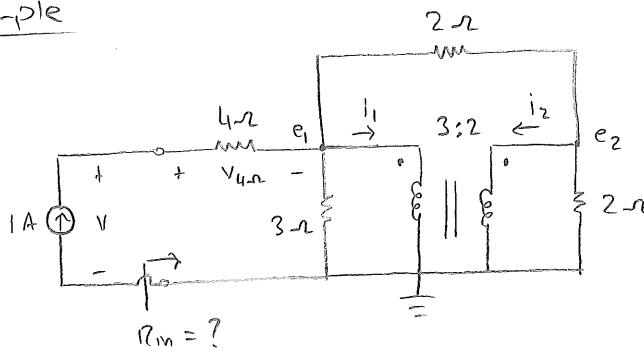Example

Recall IT equations

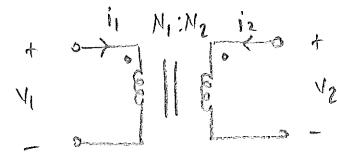

$$\frac{v_1}{N_1} = \frac{v_2}{N_2} \quad \& \quad N_1 i_1 + N_2 i_2 = 0$$

$$\text{Node ①: } -1 + \frac{e_1}{3} + i_1 + \frac{e_1 - e_2}{2} = 0$$

$$\text{Node ②: } i_2 + \frac{e_2}{2} + \frac{e_2 - e_1}{2} = 0$$

$$\text{IT eqn.'s: } \frac{e_1}{3} = \frac{e_2}{2}, \quad 3i_1 + 2i_2 = 0$$

Four equations four unknowns


$$\Rightarrow e_1 = \frac{18}{11} V$$

$$\text{Then, } V = v_{12} + e_1 = 4 \cdot 1 + \frac{18}{11} = \frac{62}{11} V$$

$$\Rightarrow R_{12} = \frac{62}{11} \Omega$$

Maximum Power Transfer

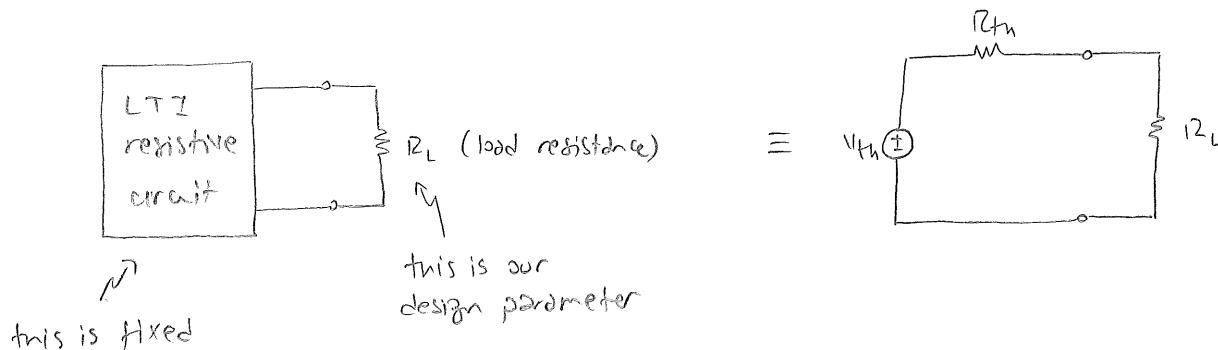There are many applications in circuit theory where it is desirable to extract the maximum possible power from a given circuit.



$$\text{Now, the power delivered to the load is : } P_L = R_L \left[\frac{V_{th}}{R_{th} + R_L} \right]^2$$


P_L : function of R_L (since V_{th} & R_{th} are fixed)

Question: $P_{L,\max} = ?$


Answer: Differentiate w.r.t. R_L .

$$\frac{dP_L}{dR_L} = \frac{V_{th}^2}{(R_L + R_{th})^2} - 2R_L \frac{V_{th}^2}{(R_L + R_{th})^3} = V_{th}^2 \left\{ \frac{(R_L + R_{th}) - 2R_L}{(R_L + R_{th})^3} \right\} = V_{th}^2 \frac{R_{th} - R_L}{(R_L + R_{th})^3}$$
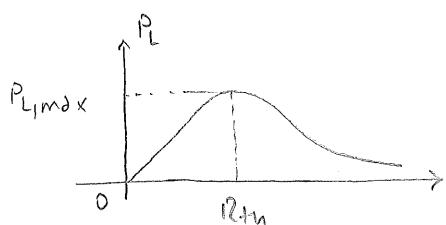
$$\frac{dP_L}{dR_L} = 0 \Rightarrow R_L = R_{th}$$



Conclusion For max power transfer to the load, R_L must equal R_{th} !

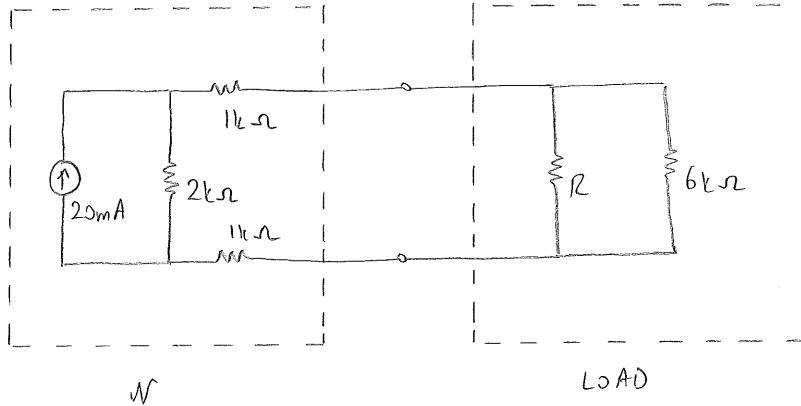Example

- a) Find R so that max power is delivered to the load.
 b) Find this max power.

Step 1 Find the Thevenin equiv. of the circuit N .

$$V_{th} = (20 \text{ mA}) \times (2 \text{ k}\Omega) = 40 \text{ V}$$

$$\Rightarrow \boxed{V_{th} = 40 \text{ V}}$$

$$R_{th} = 1 + 2 + 1 = 4 \text{ k}\Omega$$

$$\Rightarrow \boxed{R_{th} = 4 \text{ k}\Omega}$$

Step 2 Study the equiv. circuit

$$R_L = R // 6k$$


$$\Rightarrow \frac{1}{R} + \frac{1}{6} = \frac{1}{4} \Rightarrow \boxed{R = 12 \text{ k}\Omega}$$

$$P_{L,\max} = R_L \left(\frac{40}{4k + R_L} \right)^2 \Big|_{R_L=4k} = 4k \left(\frac{40}{8k} \right)^2 = (4 \text{ k}\Omega) \times (5 \text{ mA})^2 = 4000 \times (5 \times 10^{-3})^2 = 0.1 \text{ W}$$

$$\Rightarrow \boxed{P_{L,\max} = 0.1 \text{ W}}$$

Two Ports

Consider an LTI resistor

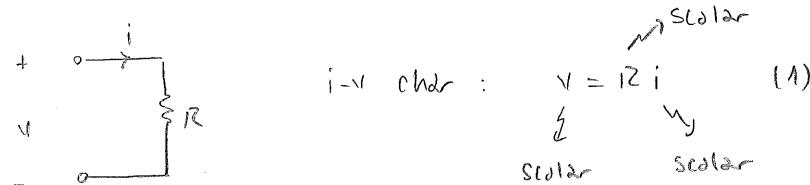

Eq. (1) has a natural generalization:

$$v = Ri \quad \begin{matrix} \text{vector in } \mathbb{R}^n \\ \text{vector in } \mathbb{R}^n \end{matrix} \rightarrow \text{vector in } \mathbb{R}^n$$

$\xrightarrow{\text{matrix}}$
 $n \times 1$ matrix


We will be interested in the case $n=2$ (two ports).

$$\left. \begin{array}{l} v_1 = r_{11}i_1 + r_{12}i_2 \\ v_2 = r_{21}i_1 + r_{22}i_2 \end{array} \right\} \begin{bmatrix} v_1 \\ v_2 \end{bmatrix} = \underbrace{\begin{bmatrix} r_{11} & r_{12} \\ r_{21} & r_{22} \end{bmatrix}}_{R} \begin{bmatrix} i_1 \\ i_2 \end{bmatrix}$$

R : resistance matrix

Example (trivial case)

$$\left. \begin{array}{l} v_1 = R_1 i_1 + 0 \cdot i_2 \\ v_2 = 0 \cdot i_1 + R_2 i_2 \end{array} \right\} \begin{bmatrix} v_1 \\ v_2 \end{bmatrix} = \underbrace{\begin{bmatrix} R_1 & 0 \\ 0 & R_2 \end{bmatrix}}_R \begin{bmatrix} i_1 \\ i_2 \end{bmatrix}$$

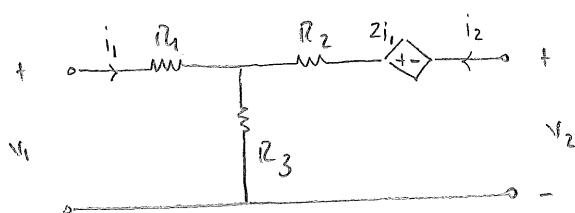Example Find the resistance matrix R 

Solut'n by KVL:

$$\left. \begin{array}{l} v_1 = R_1 i_1 + R_3(i_1 + i_2) \\ v_2 = -2i_1 + R_2 i_2 + R_3(i_1 + i_2) \end{array} \right\} (*)$$

$$(*) \Rightarrow \begin{bmatrix} v_1 \\ v_2 \end{bmatrix} = \underbrace{\begin{bmatrix} R_1 + R_3 & R_3 \\ R_3 - 2 & R_2 + R_3 \end{bmatrix}}_R \begin{bmatrix} i_1 \\ i_2 \end{bmatrix}$$

Another approach

$v_1 = r_{11}i_1 + r_{12}i_2 \Rightarrow r_{11} = \left. \frac{v_1}{i_1} \right|_{i_2=0}$ that is, r_{11} equals the ratio v_1/i_1 when the 2nd port is open-circuited ($i_2=0$)

$$\& r_{12} = \left. \frac{v_1}{i_2} \right|_{i_1=0}$$

likewise, $v_2 = r_{21}i_1 + r_{22}i_2 \Rightarrow r_{21} = \left. \frac{v_2}{i_1} \right|_{i_2=0}$ & $r_{22} = \left. \frac{v_2}{i_2} \right|_{i_1=0}$.

Let's apply this approach to the previous example:

when $i_2=0$

$$v_1 = R_1 i_1 + R_3 i_1 = (R_1 + R_3) i_1 \Rightarrow r_{11} = R_1 + R_3$$

$$v_2 = -2i_1 + R_3 i_1 = (R_3 - 2) i_1 \Rightarrow r_{21} = R_3 - 2$$

when $i_1=0$


$$v_1 = R_3 i_2 \Rightarrow r_{12} = R_3$$

$$v_2 = R_2 i_2 + R_3 i_2 \Rightarrow r_{22} = R_2 + R_3$$

$$R = \begin{bmatrix} R_1 + R_3 & R_3 \\ R_3 - 2 & R_2 + R_3 \end{bmatrix}$$

as expected


other representations are also possible & used:

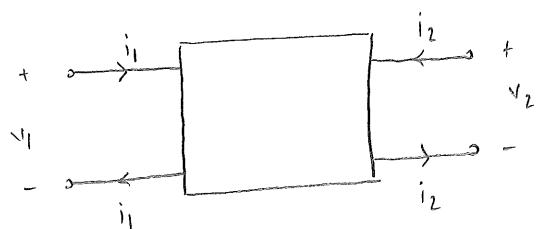Conductance matrix

$$\begin{bmatrix} i_1 \\ i_2 \end{bmatrix} = \begin{bmatrix} g_{11} & g_{12} \\ g_{21} & g_{22} \end{bmatrix} \begin{bmatrix} v_1 \\ v_2 \end{bmatrix}$$

conductance
matrix, G


Example Find \mathcal{B} .

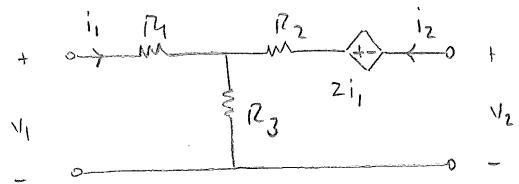

Note that $\mathfrak{g}_{11} = \frac{i_1}{v_1} \Big|_{v_2=0}$ (ratio $\frac{i_1}{v_1}$ when 2nd port is short-circuited ($v_2=0$))

$$\& \quad \mathfrak{g}_{21} = \frac{i_2}{v_1} \Big|_{v_2=0}, \quad \mathfrak{g}_{12} = \frac{i_1}{v_2} \Big|_{v_1=0}, \quad \mathfrak{g}_{22} = \frac{i_2}{v_2} \Big|_{v_1=0}$$

When $v_2=0$

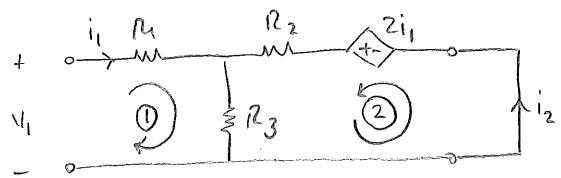

$$\textcircled{1}: -v_1 + R_1 i_1 + R_3(i_1 + i_2) = 0 \quad (1)$$

$$\textcircled{2}: -2i_1 + R_2 i_2 + R_3(i_1 + i_2) = 0 \quad (2)$$

$$(1) \& (2) \Rightarrow \begin{bmatrix} R_1+R_3 & R_3 \\ R_3 & R_2+R_3 \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \end{bmatrix} = \begin{bmatrix} 1 \\ 0 \end{bmatrix} v_1 \quad (3)$$

$$(3) \Rightarrow \begin{bmatrix} \mathfrak{g}_{11} \\ \mathfrak{g}_{21} \end{bmatrix} = \begin{bmatrix} i_1/v_1 \\ i_2/v_1 \end{bmatrix}_{v_2=0} = \begin{bmatrix} R_1+R_3 & R_3 \\ R_3 & R_2+R_3 \end{bmatrix}^{-1} \begin{bmatrix} 1 \\ 0 \end{bmatrix} = \frac{1}{\Delta} \begin{bmatrix} R_2+R_3 & -R_3 \\ 2-R_3 & R_2+R_3 \end{bmatrix} \begin{bmatrix} 1 \\ 0 \end{bmatrix} \quad (4)$$


$$\Delta := (R_1+R_3)(R_2+R_3) - R_3(R_3-2) = R_1R_2 + R_2R_3 + R_1R_3 + 2R_3.$$

$$(4) \Rightarrow \mathfrak{g}_{11} = \frac{R_2+R_3}{\Delta} \quad \& \quad \mathfrak{g}_{21} = \frac{2-R_3}{\Delta}.$$

Exercise : Compute \mathfrak{g}_{12} & \mathfrak{g}_{22} . ($\mathfrak{g}_{12} = -\frac{R_3}{\Delta}$ & $\mathfrak{g}_{22} = \frac{R_1+R_3}{\Delta}$)

Hence, $\begin{bmatrix} i_1 \\ i_2 \end{bmatrix} = \underbrace{\begin{bmatrix} \frac{R_2+R_3}{\Delta} & -\frac{R_3}{\Delta} \\ \frac{2-R_3}{\Delta} & \frac{R_1+R_3}{\Delta} \end{bmatrix}}_G \begin{bmatrix} v_1 \\ v_2 \end{bmatrix}$ (observe that $G = \mathcal{I}^{-1}$, the inverse of the resistance matrix)

Remark In general the resistance (conductance) matrix \mathcal{I}^{-1} (4) need not be invertible. When the inverse exists we have $G = \mathcal{I}^{-1}$ ($\mathcal{I} = G^{-1}$).

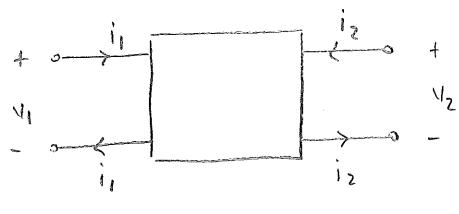Hybrid matrices

$$\begin{bmatrix} v_1 \\ i_2 \end{bmatrix} = \underbrace{\begin{bmatrix} h_{11} & h_{12} \\ h_{21} & h_{22} \end{bmatrix}}_H \begin{bmatrix} i_1 \\ v_2 \end{bmatrix} \quad \text{and} \quad \begin{bmatrix} i_1 \\ v_2 \end{bmatrix} = \underbrace{\begin{bmatrix} h'_{11} & h'_{12} \\ h'_{21} & h'_{22} \end{bmatrix}}_{H'} \begin{bmatrix} v_1 \\ i_2 \end{bmatrix}$$

$$H' = H^{-1} \quad (\text{If the inverse exists})$$


Transmission matrix (chained parameters)

$$\begin{bmatrix} v_1 \\ i_1 \end{bmatrix} = \underbrace{\begin{bmatrix} A & B \\ C & D \end{bmatrix}}_T \begin{bmatrix} v_2 \\ -i_2 \end{bmatrix}$$

Example Find the matrix T for the ideal transformer.


$$\begin{array}{c} + \xrightarrow{i_1} \boxed{\begin{array}{c} N_1 : N_2 \\ || \\ \circ \end{array}} \xleftarrow{i_2} + \\ \begin{array}{c} v_1 \\ - \end{array} \quad \begin{array}{c} v_2 \\ - \end{array} \end{array} \quad \left. \begin{array}{l} \frac{v_1}{N_1} = \frac{v_2}{N_2} \Rightarrow v_1 = \frac{N_1}{N_2} v_2 \\ N_1 i_1 + N_2 i_2 = 0 \Rightarrow i_1 = -\frac{N_2}{N_1} i_2 \end{array} \right\} \quad \begin{bmatrix} v_1 \\ i_1 \end{bmatrix} = \underbrace{\begin{bmatrix} \frac{N_1}{N_2} & 0 \\ 0 & \frac{N_2}{N_1} \end{bmatrix}}_T \begin{bmatrix} v_2 \\ -i_2 \end{bmatrix}$$

Example Find the input resistance

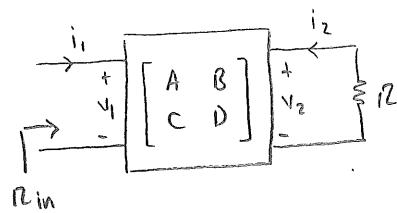

$$\text{where } \begin{bmatrix} v_1 \\ i_1 \end{bmatrix} = \begin{bmatrix} A & B \\ C & D \end{bmatrix} \begin{bmatrix} v_2 \\ -i_2 \end{bmatrix}$$

$$R_{in} = \frac{v_1}{i_1} \quad \left| \begin{array}{l} v_1 = Av_2 - Bi_2 \\ i_1 = Cv_2 - Di_2 \\ v_2 = -Ri_2 \end{array} \right. \quad \left| \begin{array}{l} v_1 = -A(Ri_2) - Bi_2 = -(AR+B)i_2 \\ i_1 = -C(Ri_2) - Di_2 = -(CR+D)i_2 \end{array} \right. \quad \left| \frac{v_1}{i_1} = \frac{AR+B}{CR+D} \right.$$

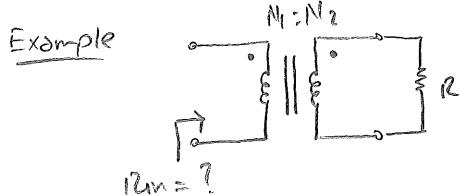


Combining the previous two examples:


$$R_{in} = \frac{AR+B}{CR+D} = \frac{\frac{N_1}{N_2} \cdot R + 0}{0 + \frac{N_2}{N_1}}$$

$$= \left(\frac{N_1}{N_2} \right)^2 R$$

Exercise:

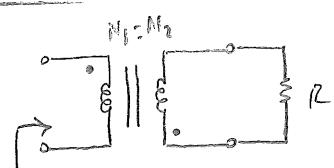


$$R_{in} = ?$$

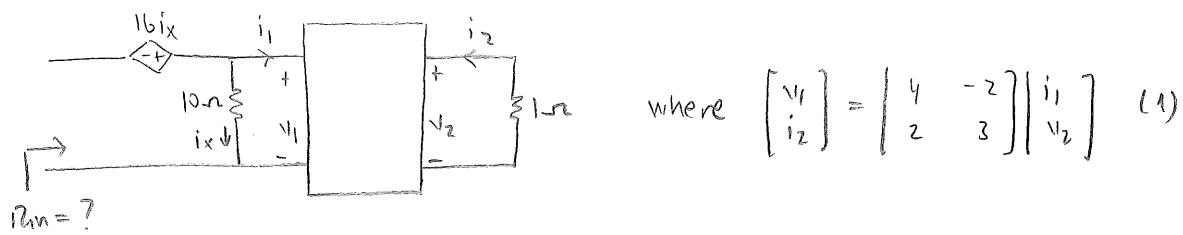Example

$$\text{where } \begin{bmatrix} v_1 \\ i_2 \end{bmatrix} = \begin{bmatrix} 4 & -2 \\ 2 & 3 \end{bmatrix} \begin{bmatrix} i_1 \\ v_2 \end{bmatrix} \quad (1)$$

Step 1 Find R_i

$$v_2 = -R_i i_2 \quad (2)$$

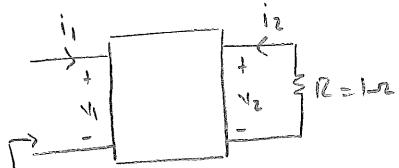

$$(1) \& (2) = \begin{bmatrix} v_1 \\ i_2 \end{bmatrix} = \begin{bmatrix} 4 & -2 \\ 2 & 3 \end{bmatrix} \begin{bmatrix} i_1 \\ -R_i i_2 \end{bmatrix}$$

$$R_i = v_1 / i_1$$

$$\Rightarrow v_1 = 4i_1 + 2R_i i_2$$

$$\& i_2 = 2i_1 - 3R_i i_2 \Rightarrow i_2 = \frac{2}{3R_i + 1} i_1$$


Then,

$$v_1 = 4i_1 + 2R_i \left(\frac{2}{3R_i + 1} i_1 \right) = \left[4 + \frac{4R_i^2}{3R_i + 1} \right] i_1$$

$$\Rightarrow R_i = \frac{v_1}{i_1} \Big|_{i_2=1} = \left[4 + \frac{4R_i^2}{3R_i + 1} \right]_{i_1=1} = \boxed{5\Omega}$$

Step 2 Compute R_m using

$$10i_x = 5i_1 \Rightarrow i_1 = 2i_x$$

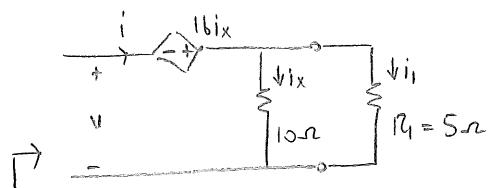

$$R_m = \frac{v}{i}$$


$$i = i_x + i_1 = 3i_x$$

$$v = -16i_x + 10i_x = -6i_x$$

$$\left. \begin{array}{l} R_m = \frac{v}{i} = \frac{-6i_x}{3i_x} = -2\Omega \\ \end{array} \right\}$$

Power of two-port

Let P_N be the sum of powers of all individual components inside N .

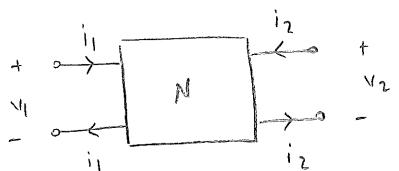
Theorem $P_N = i_1 v_1 + i_2 v_2$ Proof Exercise. (You may assume N contains only 2-terminal components)

Hint: use Tellegen's Thm.

Definition A two-port is passive if $P_N \geq 0$ for all possiblesets of port variables (i_1, v_1, i_2, v_2) . Active if not passive.

Interconnections of two-parts

parallel

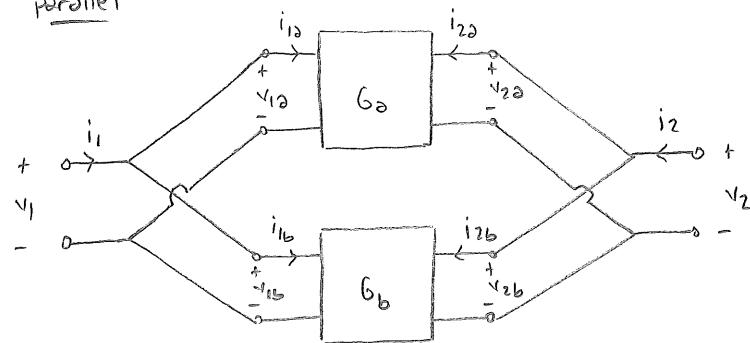


$$v_1 = v_{1a} = v_{1b} \quad \& \quad v_2 = v_{2a} + v_{2b}$$

$$\begin{bmatrix} i_1 \\ i_2 \end{bmatrix} = \begin{bmatrix} i_{1a} \\ i_{2a} \end{bmatrix} + \begin{bmatrix} i_{1b} \\ i_{2b} \end{bmatrix}$$

$$= G_a \begin{bmatrix} v_{1a} \\ v_{2a} \end{bmatrix} + G_b \begin{bmatrix} v_{1b} \\ v_{2b} \end{bmatrix}$$


$$= [G_a + G_b] \begin{bmatrix} v_1 \\ v_2 \end{bmatrix}$$

Series

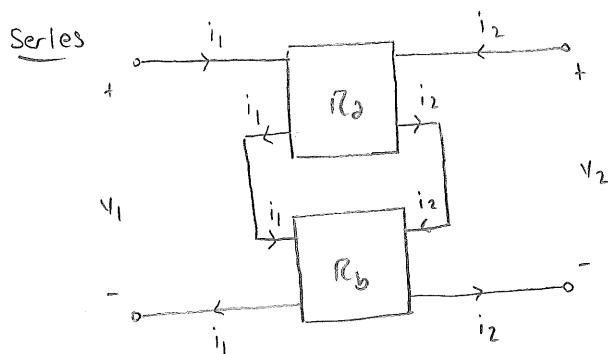


$$\begin{bmatrix} v_1 \\ v_2 \end{bmatrix} = [R_a + R_b] \begin{bmatrix} i_1 \\ i_2 \end{bmatrix}$$

Cascade

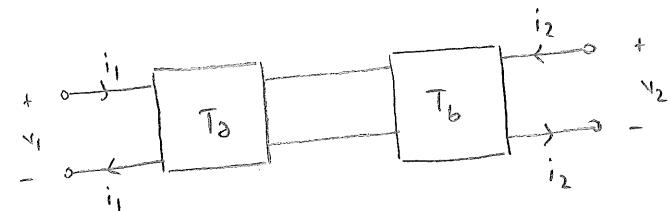

$$\begin{bmatrix} v_1 \\ i_1 \end{bmatrix} = T_a T_b \begin{bmatrix} v_2 \\ -i_2 \end{bmatrix}$$

Example

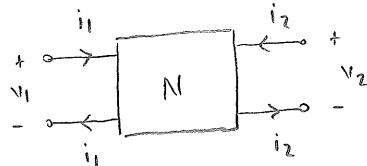

Given the following measurements on N, find \mathbf{T} .

	v_1	v_2	i_1	i_2
Exp#1	1	2	3	4
Exp#2	5	6	7	8

$$\text{Soll: } \text{Exp}\#1 \Rightarrow \begin{bmatrix} 1 \\ 2 \end{bmatrix} = \mathbf{T} \begin{bmatrix} 3 \\ 4 \end{bmatrix}$$

$$\left\{ \begin{bmatrix} 1 & 5 \\ 2 & 6 \end{bmatrix} = \mathbf{T} \begin{bmatrix} 3 & 7 \\ 4 & 8 \end{bmatrix} \Rightarrow \mathbf{T} = \begin{bmatrix} 1 & 5 \\ 2 & 6 \end{bmatrix} \begin{bmatrix} 3 & 7 \\ 4 & 8 \end{bmatrix}^{-1} \right.$$

$$\text{Exp}\#2 \Rightarrow \begin{bmatrix} 5 \\ 6 \end{bmatrix} = \mathbf{T} \begin{bmatrix} 7 \\ 8 \end{bmatrix}$$


Exercise Given $H = \begin{bmatrix} h_{11} & h_{12} \\ h_{21} & h_{22} \end{bmatrix}$, find \mathbf{T} .

$$\left| \begin{array}{l} \text{Hint:} \\ H \Rightarrow \end{array} \right.$$


	v_1	v_2	i_1	i_2
Exp#1	h_{11}	0	1	h_{21}
Exp#2	h_{12}	1	0	h_{22}

$$\mathbf{T}_{\text{table}} \Rightarrow \begin{bmatrix} h_{11} \\ 1 \end{bmatrix} = \mathbf{T} \begin{bmatrix} 0 \\ -h_{21} \end{bmatrix} \quad \& \quad \begin{bmatrix} h_{12} \\ 0 \end{bmatrix} = \mathbf{T} \begin{bmatrix} 1 \\ -h_{22} \end{bmatrix} \Rightarrow \begin{bmatrix} h_{11} & h_{12} \\ 1 & 0 \end{bmatrix} = \mathbf{T} \begin{bmatrix} 0 & 1 \\ -h_{21} & -h_{22} \end{bmatrix} \Rightarrow \boxed{\mathbf{T} = X^{-1}Y}$$


Reciprocity

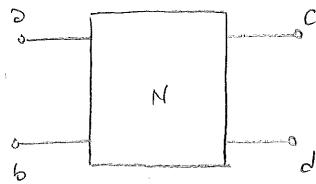

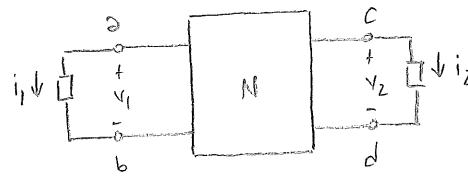Let the two-port N contain only LTI resistors and ideal transformers. Such N is called reciprocal and satisfies:



case C

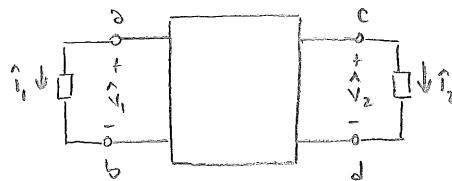case \hat{C}

: arbitrary one-ports (including open circuit & short circuit.)

$$\hat{i}_1 v_1 + \hat{i}_2 v_2 = \hat{i}_1 \hat{v}_1 + \hat{i}_2 \hat{v}_2 \quad (1)$$

Also, for reciprocal N we have

$$\begin{aligned} r_{12} &= r_{21} & h_{12} &= -h_{21} \\ g_{12} &= g_{21} & h'_{12} &= -h'_{21} \end{aligned}$$

Proof of eq. (1) [For simplicity assume N does not contain any IT's.]

Since both cases have the same graph, by Tellegen's Thm we can write

$$0 = \sum_{k=1}^b \hat{i}_k \hat{v}_k = \sum_{k=1}^b i_k \hat{v}_k \quad (2) \quad i_k (\hat{v}_k) : k^{\text{th}} \text{ branch current (voltage)} \text{ at } C (\hat{C})$$

Note that for $k \geq 3$ we have $v_k = R_k i_k$ ($\hat{v}_k = R_k \hat{i}_k$) since N is reciprocal. Rewrite

$$(2) \text{ as } \hat{i}_1 v_1 + \hat{i}_2 v_2 + \sum_{k=3}^b \hat{i}_k \hat{v}_k = \hat{i}_1 \hat{v}_1 + \hat{i}_2 \hat{v}_2 + \sum_{k=3}^b i_k \hat{v}_k. \text{ Then}$$

$$\hat{i}_1 v_1 + \hat{i}_2 v_2 = \hat{i}_1 \hat{v}_1 + \hat{i}_2 \hat{v}_2 + \sum_{k=3}^b i_k \hat{v}_k - \sum_{k=3}^b \hat{i}_k \hat{v}_k$$

$$= \hat{i}_1 \hat{v}_1 + \hat{i}_2 \hat{v}_2 + \sum_{k=3}^b \left\{ i_k \hat{v}_k - \hat{i}_k \hat{v}_k \right\}$$

$$= \hat{i}_1 \hat{v}_1 + \hat{i}_2 \hat{v}_2 + \sum_{k=3}^b \underbrace{\left(i_k R_k \hat{i}_k - \hat{i}_k R_k i_k \right)}_0$$


$$= \hat{i}_1 \hat{v}_1 + \hat{i}_2 \hat{v}_2.$$

□

Exercise Prove the general case, where we also have IT's.

Implications of Reciprocity


①

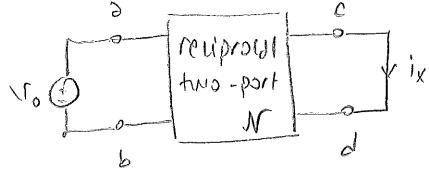

why?

$$i_1 = ? \quad v_1 = V_o$$

$$i_2 = i_x \quad v_2 = 0$$

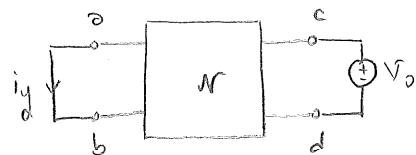



$$\hat{i}_1 = \hat{i}_y \quad \hat{v}_1 = 0$$

$$\hat{i}_2 = ? \quad \hat{v}_2 = V_o$$

$$i_x = i_y$$



$$\hat{i}_1 v_1 + \hat{i}_2 v_2 = \hat{i}_1 v_1 + \hat{i}_2 \cdot 0 \Rightarrow i_1 \cdot 0 + i_x \cdot V_o = i_y V_o + \hat{i}_2 \cdot 0 \Rightarrow i_x = i_y$$

②

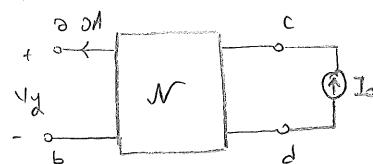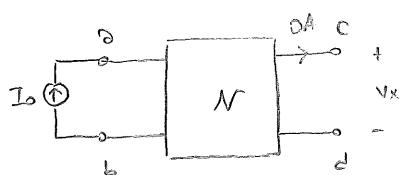


$$V_x = V_y \quad (\text{why?})$$

③

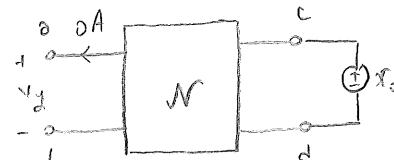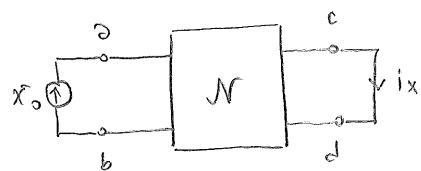

$$i_x = V_o \quad (\text{why?})$$

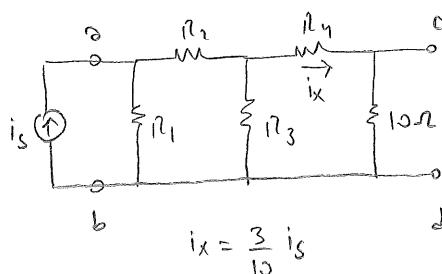Example following measurements are made. Determine i_x ,




$$i_x = \frac{3}{10} i_s$$

$$i_1 = -i_s$$

$$i_2 = 0$$

$$v_1 = ?$$

$$v_2 = 10 i_x$$

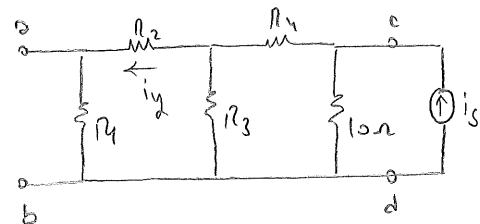

$$i_y = \frac{2}{10} i_s$$

$$\hat{i}_1 = 0$$

$$\hat{v}_1 = R_1 i_y$$

$$\hat{i}_2 = -i_s$$

$$\hat{v}_2 = ?$$



By reciprocity we can write

$$\hat{i}_1 v_1 + \hat{i}_2 v_2 = \hat{i}_1 v_1 + \hat{i}_2 \cdot 0 \Rightarrow -i_s R_1 i_y + 0 \cdot \hat{v}_2 = 0 \cdot v_1 - i_s \cdot 10 i_x$$


$$\Rightarrow R_1 i_y = 10 i_x \Rightarrow R_1 \left(\frac{2}{10} i_s \right) = 10 \left(\frac{3}{10} i_s \right) \Rightarrow \underline{\underline{R_1 = 15 \Omega}}$$

Symmetric Circuits

Ex

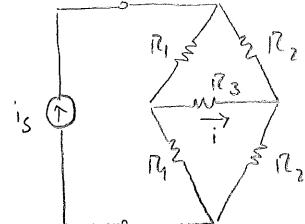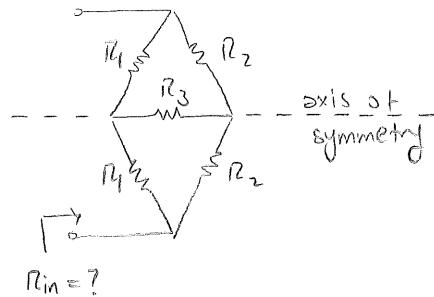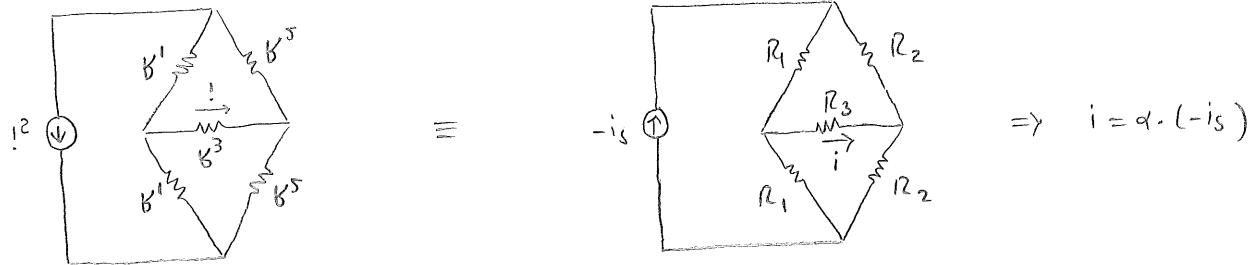Question : $i = ?$ Answer : $i = 0$. (Why?)


Because By linearity $i = \alpha \cdot i_s$ (for some α). Rotate the circuit about the axis of sym.






$$\alpha i_s = -\alpha i_s \Rightarrow \alpha = 0 \Rightarrow i = 0.$$

Remark Since $i = 0$, we can replace R_3 with open circuit. Also, the voltage across R_3 equals $v = R_3 \cdot i = 0$. Hence we can replace R_3 with short circuit, too.

[Substitution theorem] Therefore

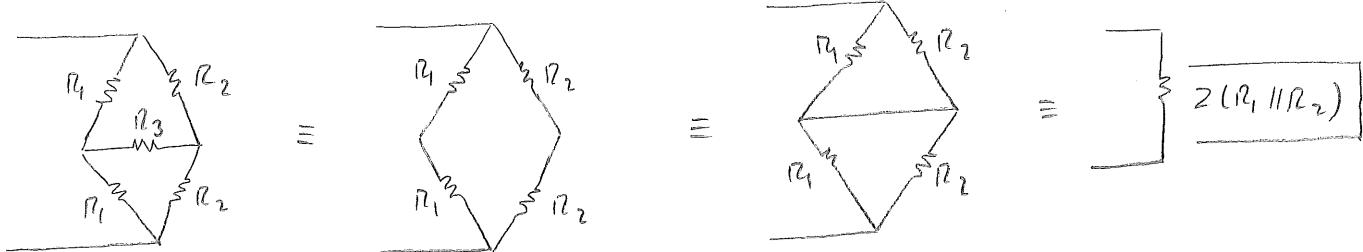


Ex

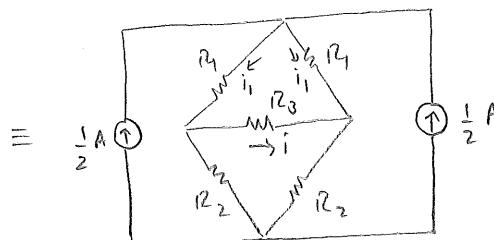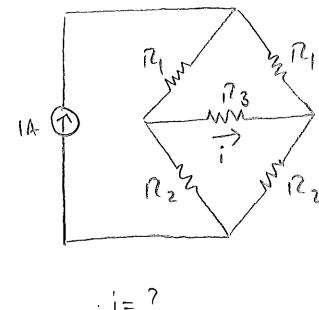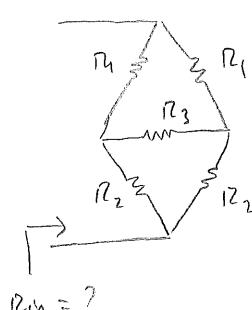


$$WL: R_1 i_1 + R_3 i - R_1 i_1 = 0 \Rightarrow i = 0$$

$$\Rightarrow R_{in} = \frac{R_1 + R_2}{2}$$

Example (All resistors are 1Ω)

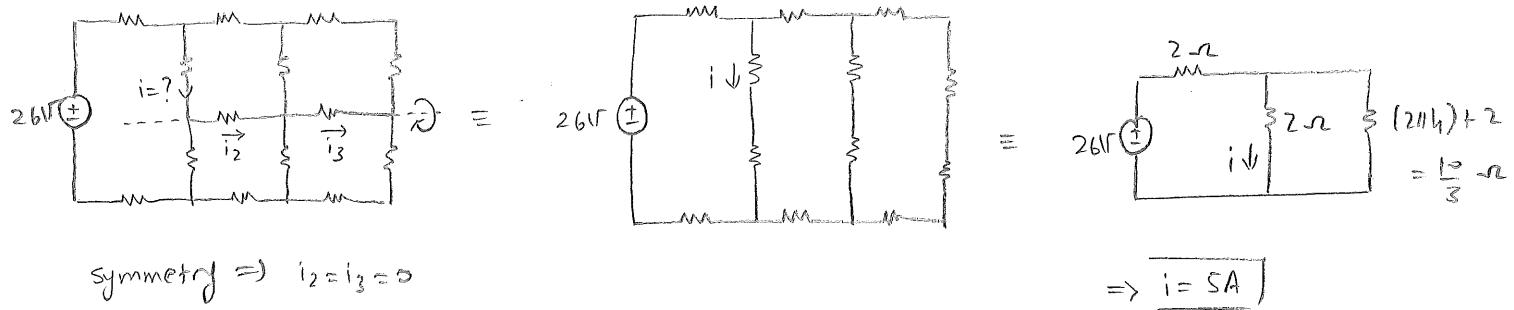


Exercise (All resistors are 1Ω) Find i .

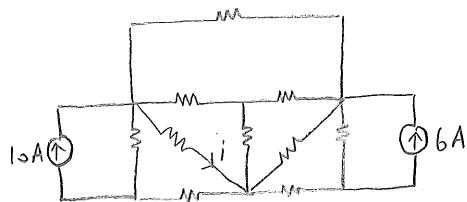


Hint The input vector $\begin{bmatrix} 10 \\ 6 \end{bmatrix}$ can be written as

$$\begin{bmatrix} 10 \\ 6 \end{bmatrix} = \begin{bmatrix} 8 \\ 8 \end{bmatrix} + \begin{bmatrix} 2 \\ -2 \end{bmatrix}.$$

Step 1 Find i_1 in the following circuit

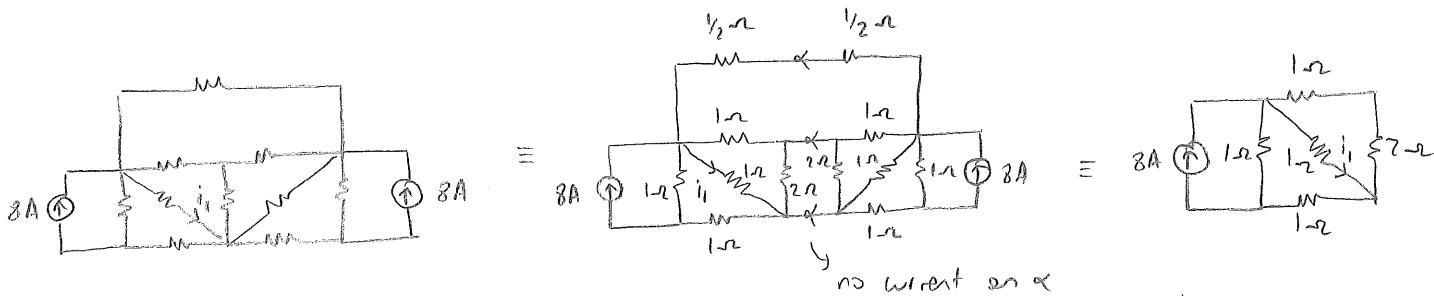


Step 2 Find i_2 in the following circuit

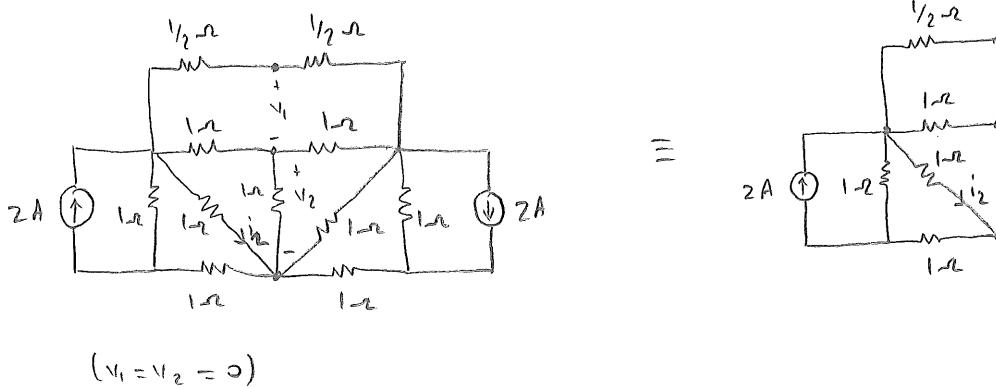

Step 3 $i = i_1 + i_2$ (linearity)


Ch. III

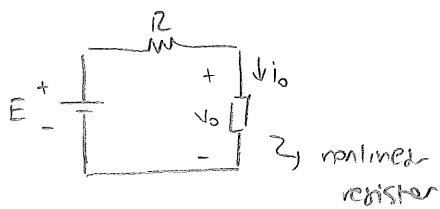
Circuits with a single nonlinear resistor

i-v char. of the nonlinear element :


$$\begin{array}{c} + \\ \text{v} \\ - \end{array} \quad \downarrow i \quad i = g(v) \quad (\text{or } v = f(i))$$

$$\begin{aligned} \text{VIL} \Rightarrow E &= Ri_o + v_o \\ &= Rg(v_o) + v_o \quad (\text{or } E = Ri_o + f(i_o)) \end{aligned}$$

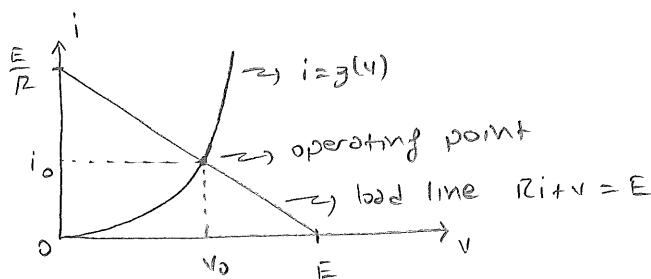Problem Find (i_o, v_o) Solution 1 (Algebraic Solution) Solve $E = Rg(v_o) + v_o$ for v_o Then $(i_o, v_o) = (g(v_o), v_o)$ is the solutionRemark Sometimes the i-v char. of the nonlinear element is available only as a measured curve. Then:Solution 2 (Graphical Solution) We have two constraints on the set of possible (i_o, v_o) pairs:→ constraint 1: $Ri + v - E = 0$ (due to circuit)→ constraint 2: $i - g(v) = 0$ (due to nonlinear resistor)Any solution (i_o, v_o) must simultaneously satisfy both constraintsRemark sometimes solution does not exist. Sometimes multiple operating points can exist.

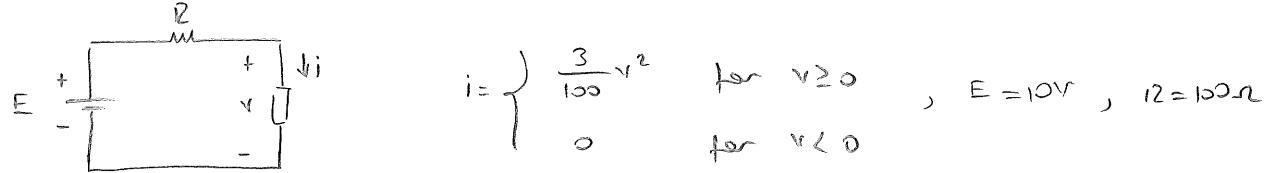Example

Find the operating point.

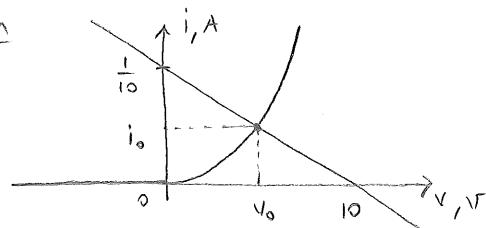Soln

By KVL we have

$$0 = Ri + v - E$$

$$= 100i + v - 10 \quad (1)$$

case $v < 0$ ($i = 0$)(1) $\Rightarrow v = 10V$ but $v < 0$. Hence no solution exists with $v < 0$.case $v \ge 0$ ($i = \frac{3}{100}v^2$)

$$(1) \Rightarrow 0 = 100\left(\frac{3}{100}v^2\right) + v - 10 = 3v^2 + v - 10 = (3v - 5)(v + 2)$$



$$\Rightarrow v = \frac{5}{3} \text{ or } -2 \quad \text{2) because } v \ge 0$$

$$\text{Hence } v_0 = \frac{5}{3}V \Rightarrow i_0 = \frac{3}{100}v_0^2 = \frac{1}{12}A$$

$$\Rightarrow \text{operating point } (i_0, v_0) = \left(\frac{1}{12}, \frac{5}{3}\right)$$


Remark Let us have a circuit as

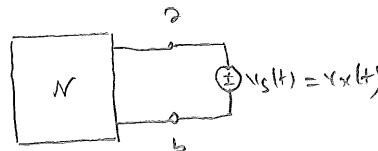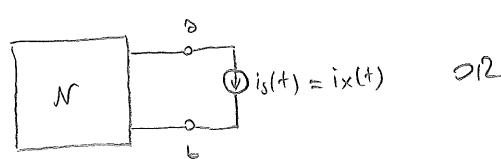Then (by Substitution Thm) we can make the following substitutions




without affecting any branch current or voltage within N.

Example Find v

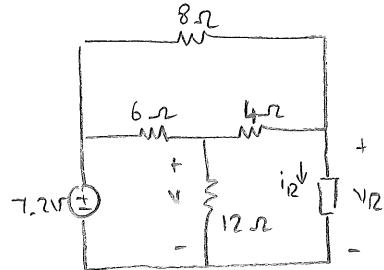

$$i_{12} = \begin{cases} \frac{1}{4}v_2^2 & \text{for } v_2 \geq 0 \\ 0 & \text{for } v_2 < 0 \end{cases}$$

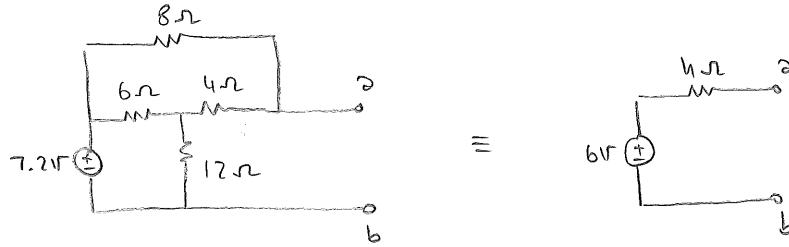Step 1 obtain the Thvenin equiv. seen by the nonlinear resistor.



Step 2 obtain the operating point using the Thvenin equiv. circuit

$$0 = 4i_{12} + v_{12} - 6 = 4 \frac{v_2^2}{4} + v_2 - 6 = v_2^2 + v_2 - 6 = (v_2 + 3)(v_2 - 2)$$

$$\Rightarrow v_2 = 2V \quad (\text{because } v_2 \geq 0) \quad \& \quad i_{12} = 1A$$

Step 3 substitute the nonlinear resistor with a voltage source $v_s = 2V$ or a current source $i_s = 1A$ and solve for v .


$$\frac{e-7.2}{6} + \frac{e}{12} + \frac{e-2}{4} = 0$$

$$\Rightarrow e = 3.4V$$

$$\Rightarrow v = 3.4V$$

Small Signal Analysis

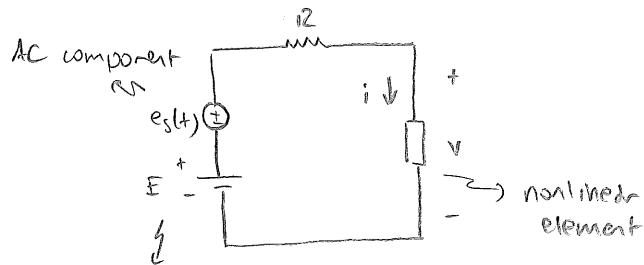A circuit with a nonlinear resistive element and a time-varying input can be analyzed using small signal analysis's method if the magnitude of the AC component of the input is sufficiently smaller than that of the DC component.




known : $i = g(v)$ & $|es(t)| \ll E$

asked : $v(t), i(t) = ?$ (approximately)

DC component

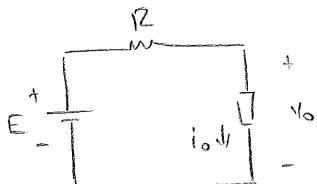Step 1 Ignore $es(t)$ and obtain the "DC operating point"





$$\text{Solve } E = Rg(v_0) + v_0 \text{ for } v_0$$

Then the DC oper. point is $(i_0, v_0) = (g(v_0), v_0)$

DC circuit

Step 2 Since $|es(t)|$ is small $v(t) \approx v_0(t)$ for all t .

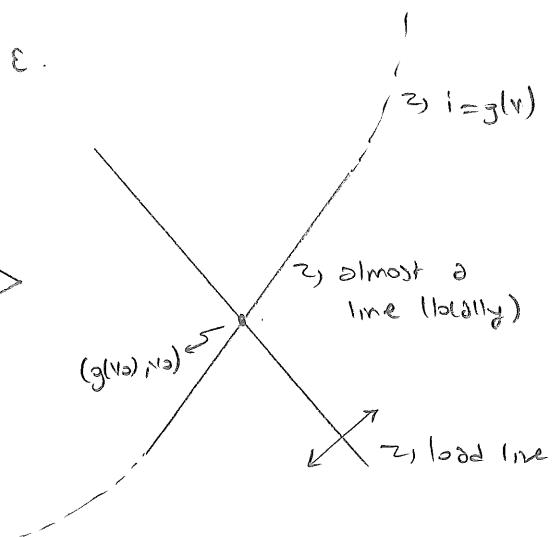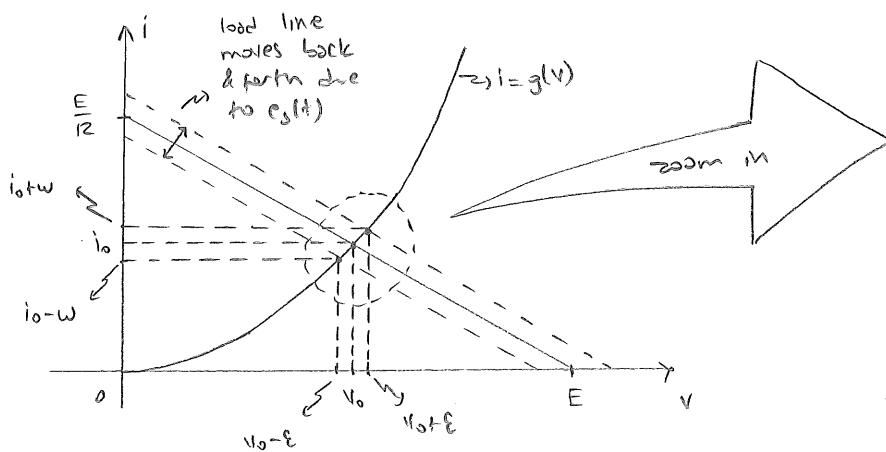That is, $v(t) \in [v_0 - \epsilon, v_0 + \epsilon]$ for some small ϵ .



First order approximation of $g(v)$ around $v=v_0$ is :

$$g(v) \approx g(v_0) + \left. \frac{dg}{dv} \right|_{v=v_0} \times (v-v_0) \quad \text{let us define } g_m := \left. \frac{dg}{dv} \right|_{v=v_0}$$

(g_m = slope of the line tangent to $g(v)$ at $v=v_0$)

$$\Rightarrow g(v) \approx g(v_0) + g_m(v-v_0) \quad \text{for } v \in [v_0-\epsilon, v_0+\epsilon], \epsilon \text{ small}$$

Now, we can write

$$E + e_s(t) = Rg(v) + v \quad \text{replace } g(v) \text{ with its approximation}$$


$$\Rightarrow E + e_s(t) \approx R[g(v_0) + g_m(v-v_0)] + v \quad \Rightarrow E = Rg(v_0) + v_0$$

$$\Rightarrow \cancel{Rg(v_0) + v_0} + e_s(t) \approx \cancel{Rg(v_0)} + Rg_m(v-v_0) + v$$

$$\Rightarrow e_s(t) \approx Rg_m(v-v_0) + (v-v_0) \quad \text{let us define } \delta v := v-v_0 \quad (\text{i.e. the deviation of } v(t) \text{ around } v_0)$$

$$\Rightarrow \boxed{e_s(t) \approx Rg_m \delta v + \delta v} \quad (1)$$

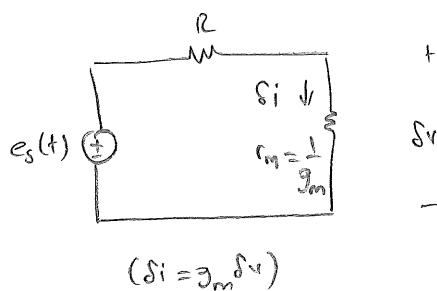Eq. (1) suggests the following linear circuit (if resistance, g_m conductance)



because :


$$\delta v = \frac{1/g_m}{R + 1/g_m} \cdot e_s(t) \quad (\text{voltage division})$$

$$\Rightarrow e_s(t) = Rg_m \delta v + \delta v \quad (\text{same as (1)})$$

AC circuit (small signal circuit)


Step 3 $v(t) = v_0 + \delta v(t)$ is the approximate solution for $v(t)$

$$i(t) = i_0 + \delta i(t) \quad " " " " " " " i(t).$$

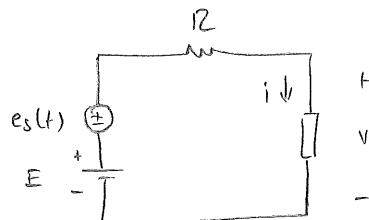Example

$$\begin{aligned} R &= 100\Omega \\ E &= 10V \\ es(t) &= 5v \end{aligned}$$

$$i = \begin{cases} 0.03v^2 & \text{for } v \geq 0 \\ 0 & \text{for } v < 0 \end{cases}$$

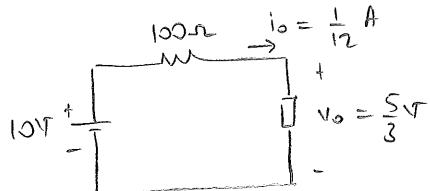
Find $i(t), v(t)$.Step1 Solve the DC circuit.

How about AC circuit?

First find gm :

$$g(v) = 0.03v^2 \quad \& \quad v_0 = \frac{5}{3}V$$

$$\Rightarrow \text{gm} = \left. \frac{dg}{dv} \right|_{v=v_0} = 0.06 \left(\frac{5}{3} \right) = 0.1V^{-1}$$

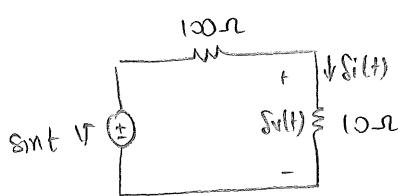Step2 Solve the AC circuit.


$$\delta v(t) = \frac{1}{11} \sin t V$$

$$\delta i(t) = \frac{1}{110} \sin t A$$

Step3 Write the approximate solution

$$v(t) \approx v_0 + \delta v(t) = \frac{5}{3} + \frac{1}{11} \sin t V$$


$$i(t) \approx i_0 + \delta i(t) = \frac{1}{12} + \frac{1}{110} \sin t A$$

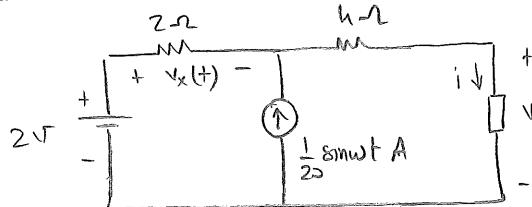Example


$$i = \begin{cases} v^2 & \text{for } v \geq 0 \\ 0 & \text{for } v < 0 \end{cases}$$

Find $v_x(t)$.

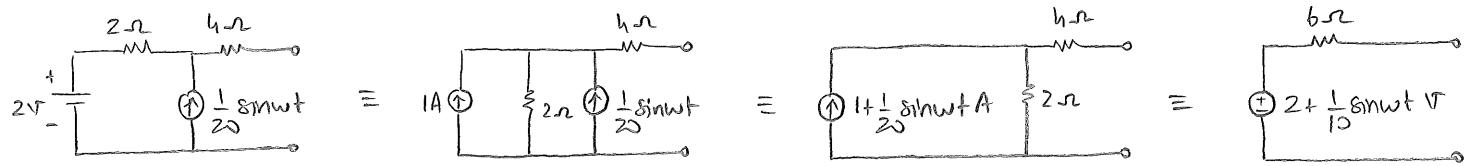Step 0 Find the trevenin equiv. seen by the nonlinear resistor.




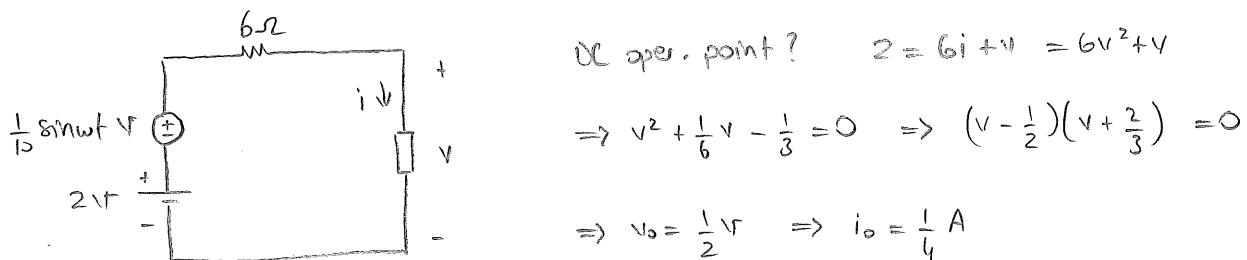Step 1 Find $v(t)$ & $i(t)$ by small signal analysis




$$\text{Compute } g_m : g_m = \left. \frac{d}{dV} v^2 \right|_{V=v_0} = 2v \Big|_{v=\frac{1}{2}} = 1 \text{ S}$$

Small signal circuit :

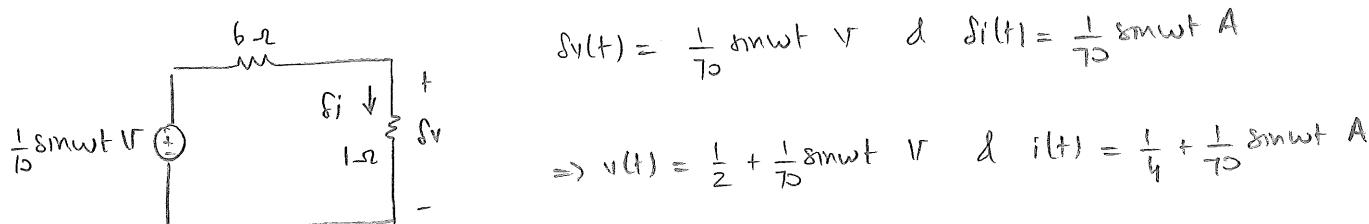

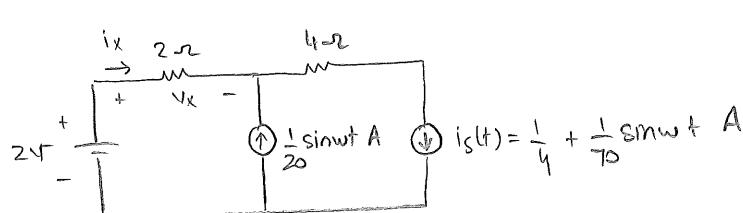Step 2 Go back to the original circuit & apply substitution thm. to



$$\Rightarrow i_x + \frac{1}{20} \sin \omega t = \frac{1}{4} + \frac{1}{70} \sin \omega t \Rightarrow i_x(t) = \frac{1}{4} - \frac{1}{28} \sin \omega t \text{ A} \quad \& \quad v_x(t) = 2i_x(t)$$


$$\Rightarrow v_x(t) \approx \frac{1}{2} - \frac{1}{14} \sin \omega t \text{ V}$$

Remark Exact sol'n is


$$v_x(t) = \frac{25}{36} - \frac{1}{15} \sin \omega t - \frac{1}{3} \sqrt{\frac{49}{144} + \frac{1}{60}} \sin \omega t \text{ V} \Rightarrow \text{error} \leq 60 \mu \text{V} \quad (\leq 0.01\%)$$

Piecewise linear Resistive Circuits


Ideal Diode

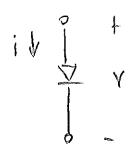



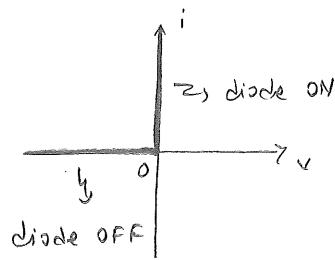
$$i-v \text{ char: } \begin{cases} v=0 \text{ (short circuit) when } i \geq 0 \\ i=0 \text{ (open circuit) when } v < 0 \end{cases}$$













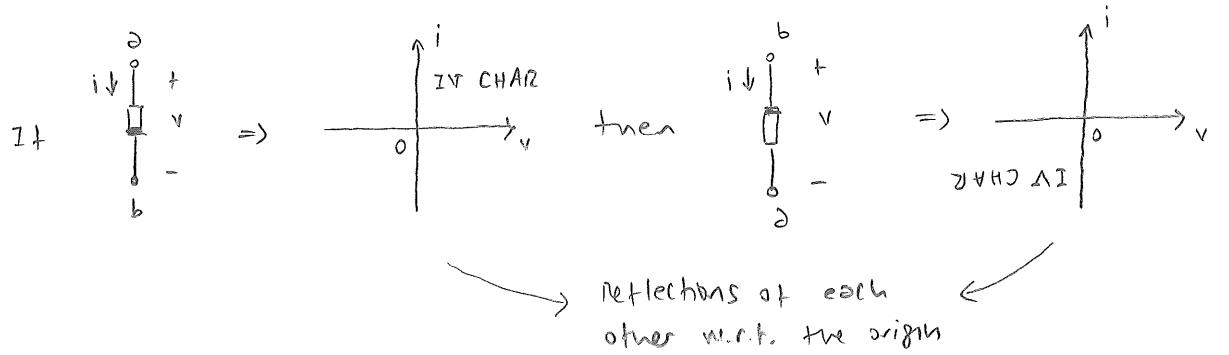Remark Let $\overset{a}{\circ} \square \overset{b}{\circ}$ be an arbitrary resistive component.



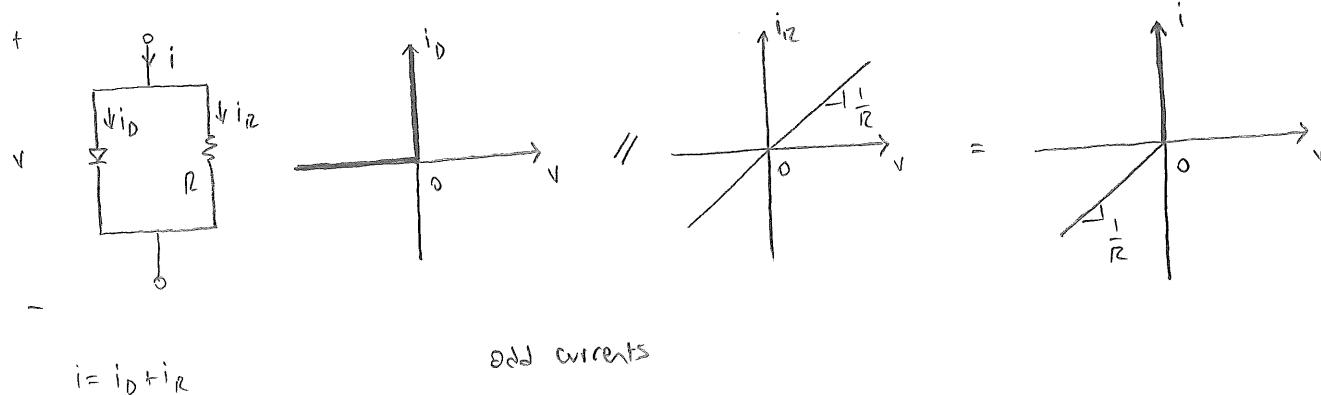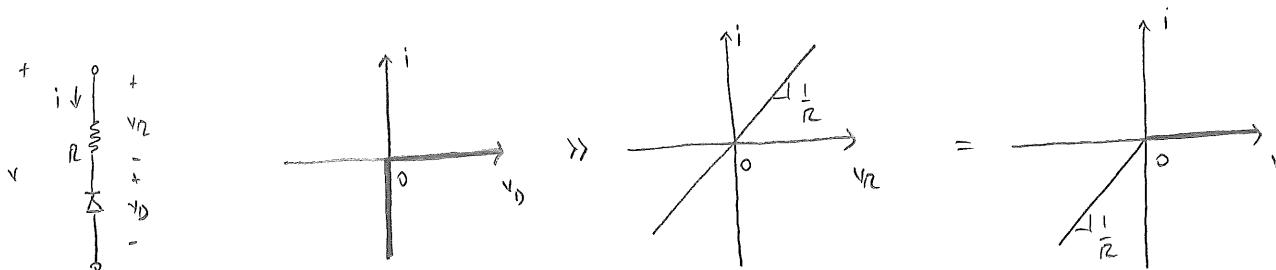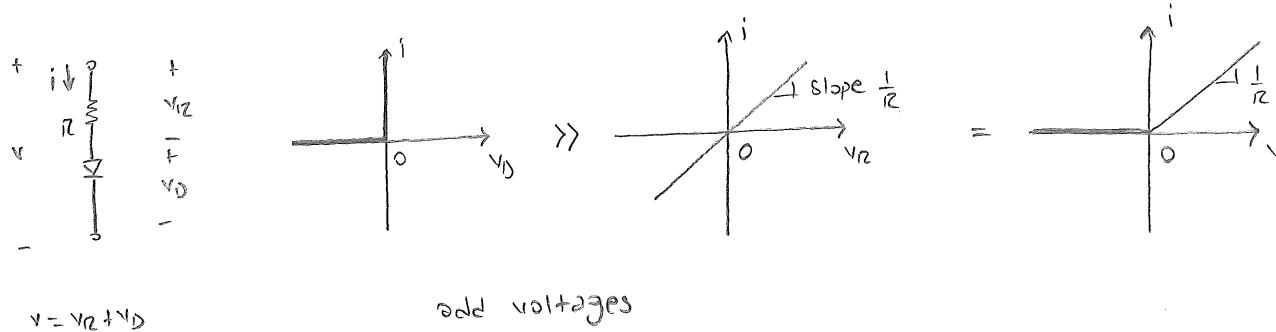Series & parallel connections of diodes, LTI resistors, & constant sources



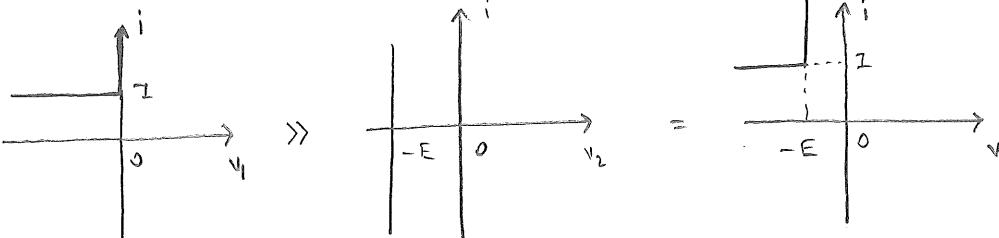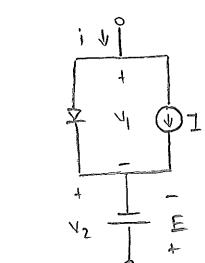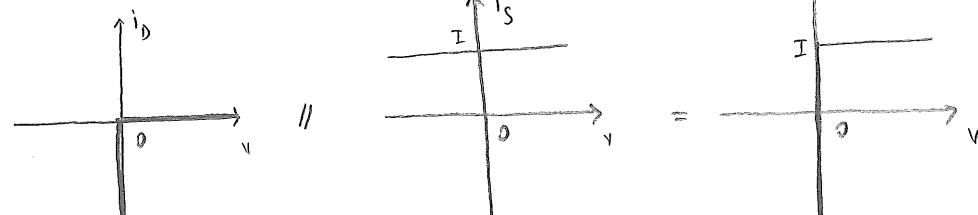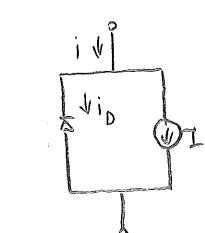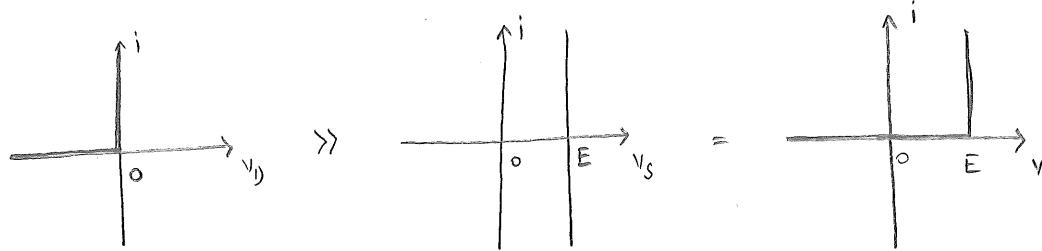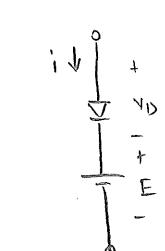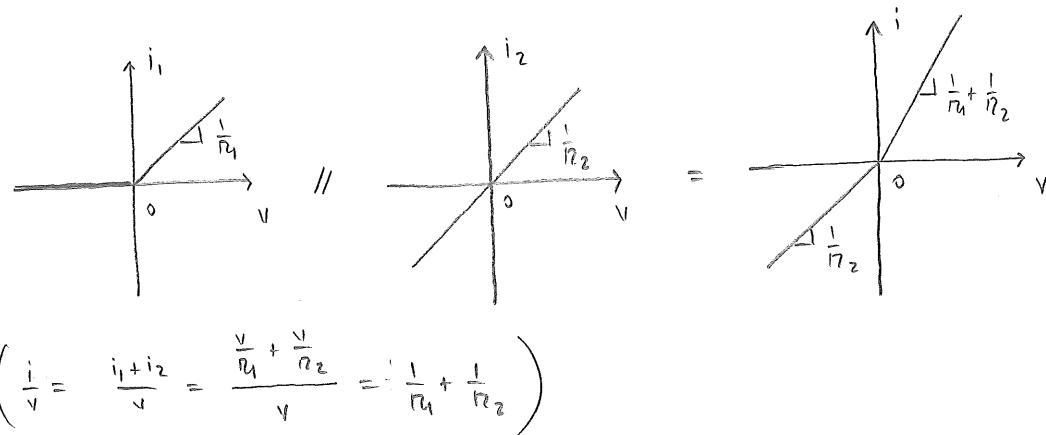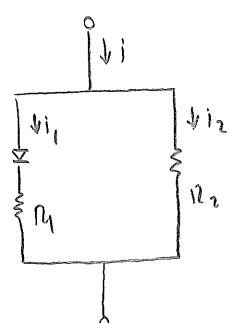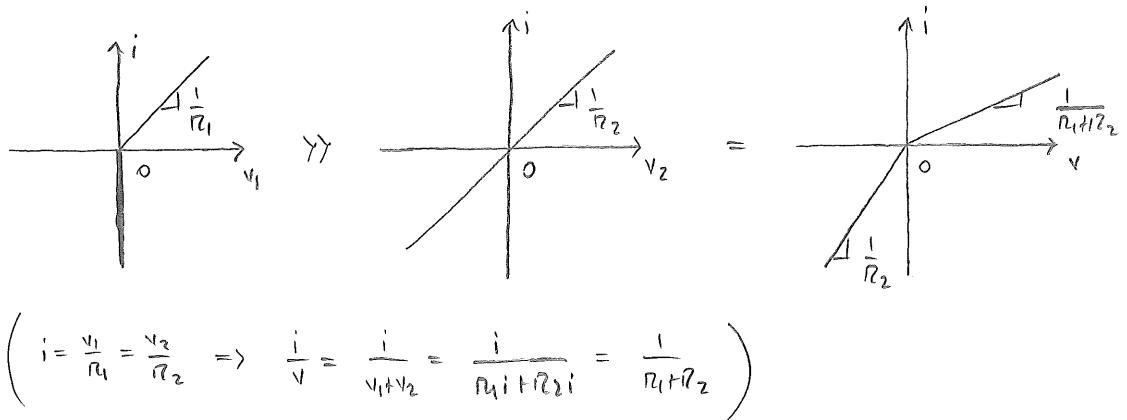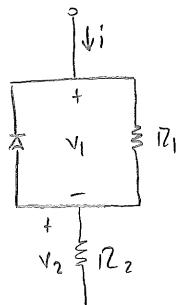


Exercise


$$= \begin{array}{c} \textcircled{2} \\ \textcircled{1} \end{array}$$

Find R_1, R_2 .

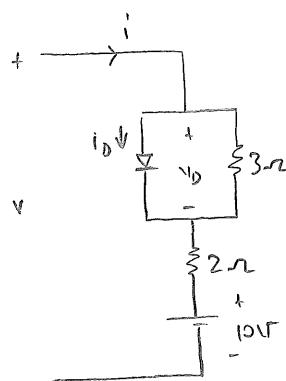Example [Nongraphical method] Plot I-V char. of



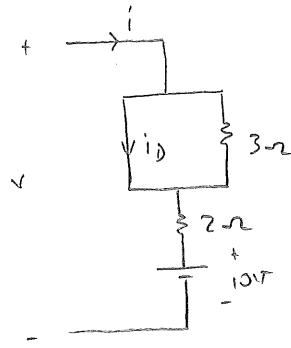Assume diode ON (condition: $i_D \geq 0$)




$$v = 2i + 10 \quad \text{when diode ON}$$

check condition:

$$i_D = i \Rightarrow v = 2i_D + 10 \Rightarrow i_D = \frac{v - 10}{2}$$

$$i_D \geq 0 \Rightarrow v \geq 10 \quad \text{for diode to be ON}$$

Assume diode OFF (condition: $v_D < 0$)

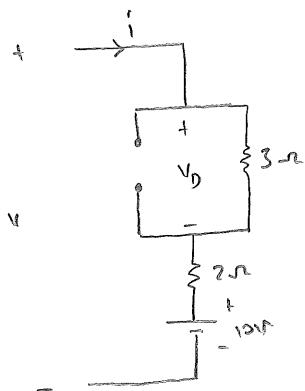


$$v = 5i + 10 \quad \text{when diode OFF}$$

check condition:







$$v_D = 3i = 3 \left(\frac{v - 10}{5} \right)$$

$$v_D < 0 \Rightarrow v < 10 \quad \text{for diode to be OFF}$$




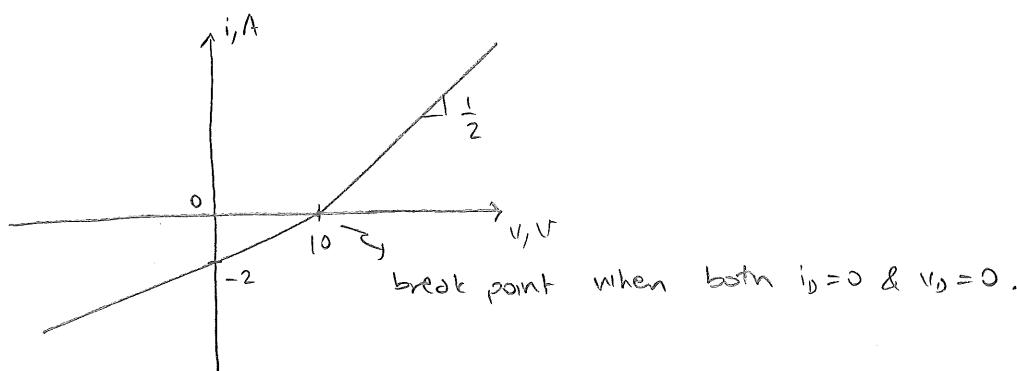
Hence, $i = \begin{cases} \frac{v - 10}{2} & \text{for } v \geq 10 \\ \frac{v - 10}{5} & \text{for } v < 10 \end{cases}$



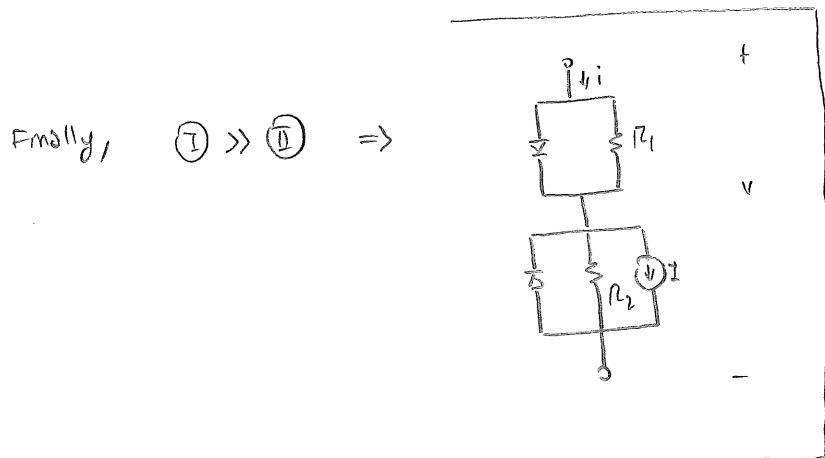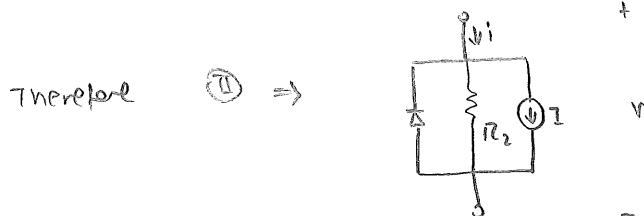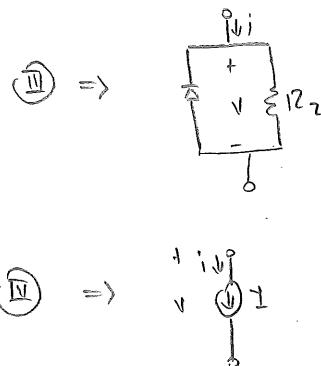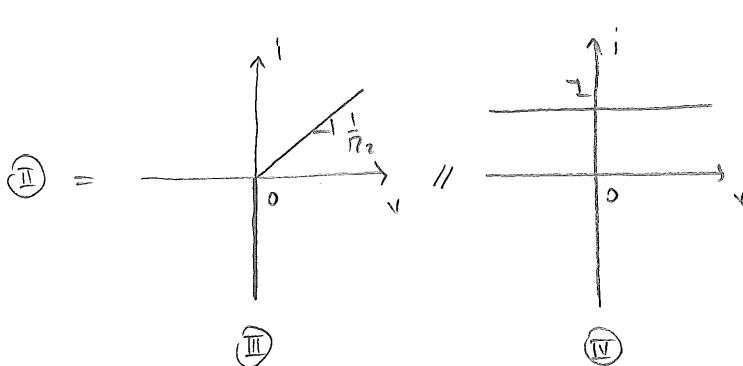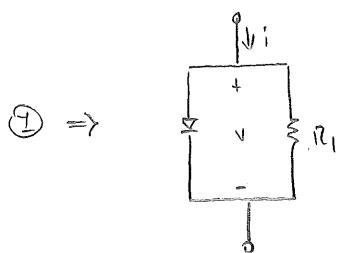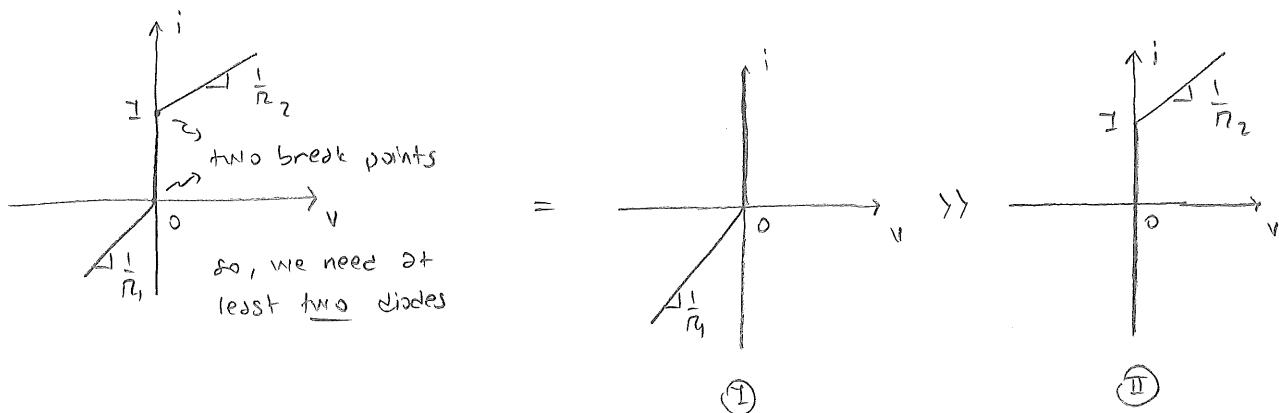Example [Synthesis, i.e., obtaining the circuit from i-v char.]




Remark Two different circuits may have the same i-v char. (nonuniqueness)

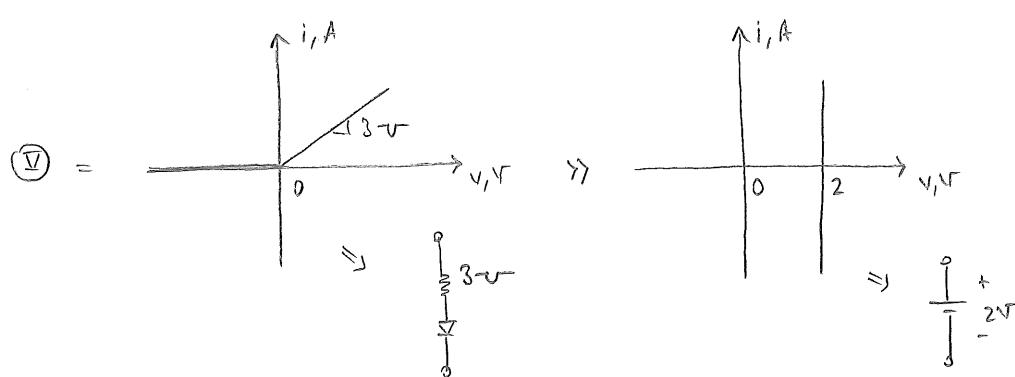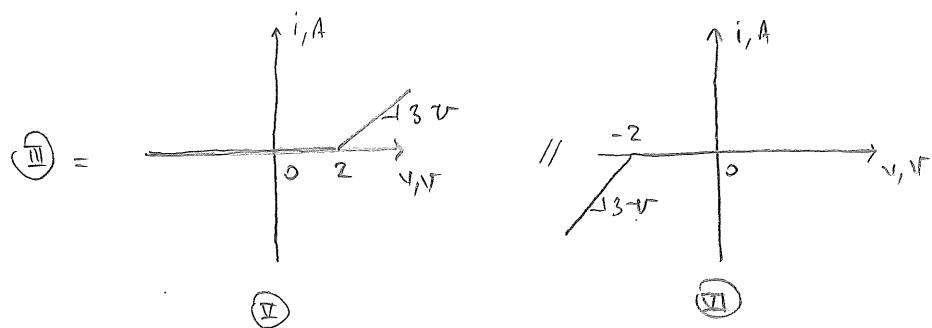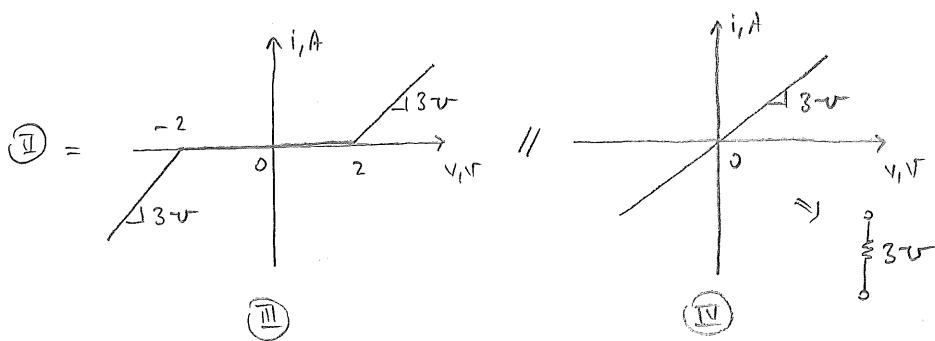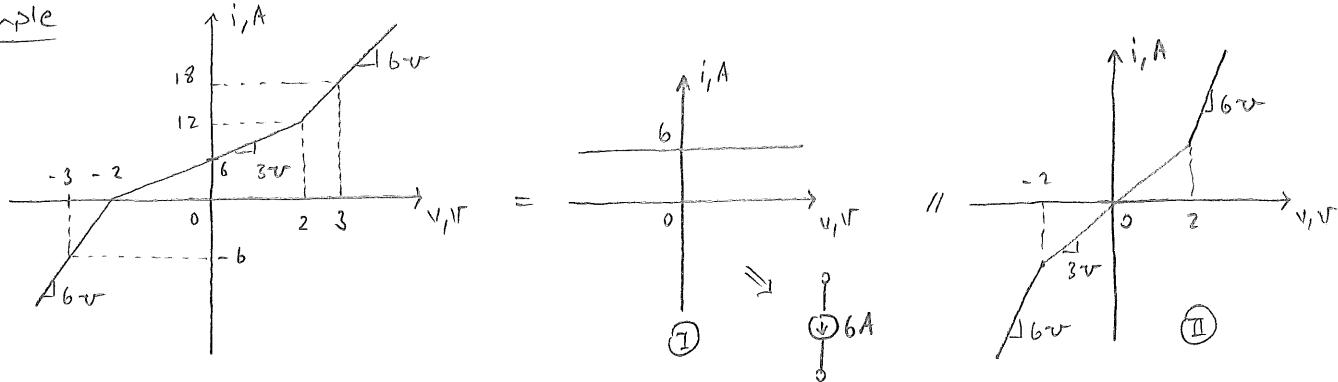Example


\textcircled{VI} is the reflection of \textcircled{V} w.r.t. the origin. Hence

$$\begin{array}{c} \textcircled{VI} \Rightarrow \\ \frac{1}{2} \\ \frac{3v}{-2v} \\ \frac{1}{2} \end{array}$$

NOW, we glue the pieces together :

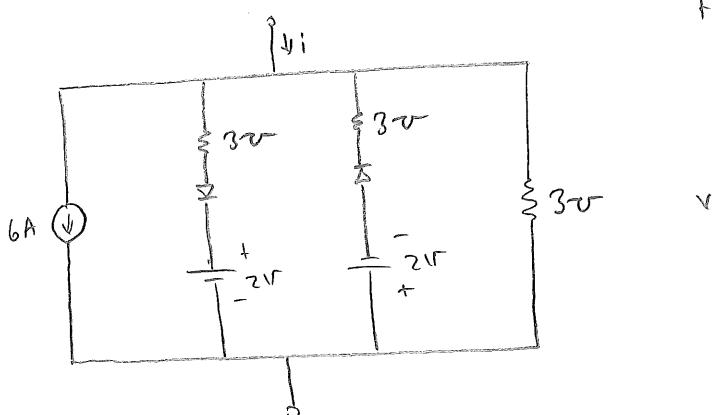

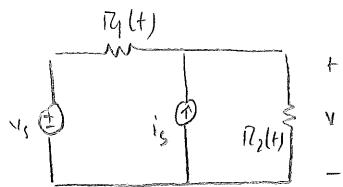Example [Linear Time-varying Resistive Circuit]



$$VCL : \frac{v - v_s}{R_1} - i_s + \frac{v}{R_2} = 0$$

$$\Rightarrow v = \frac{R_2(t)}{R_1(t) + R_2(t)} v_s + \frac{R_1(t)R_2(t)}{R_1(t) + R_2(t)} i_s$$


$$\Rightarrow v = \underbrace{\begin{bmatrix} k_1(t) & k_2(t) \end{bmatrix}}_{k(t)} \underbrace{\begin{bmatrix} v_s \\ i_s \end{bmatrix}}_u \quad (1)$$

Remark Note that (1) implies


$$v(\alpha u_a + \beta u_b) = \alpha v(u_a) + \beta v(u_b) \quad \alpha, \beta: \text{scalars}; \quad u_a, u_b: \text{input vectors}$$

Hence, superposition is still applicable for LTV resistive circuits.


Ideal Zener Diode

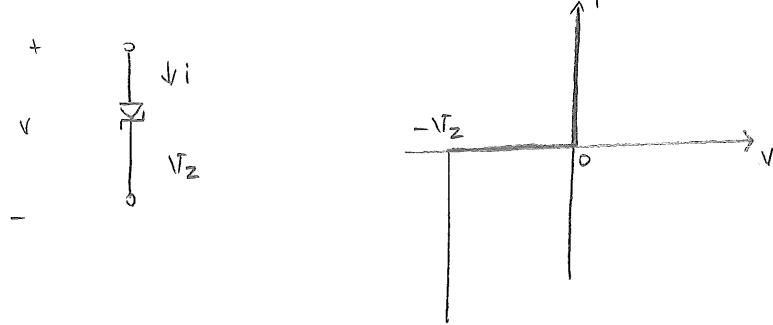

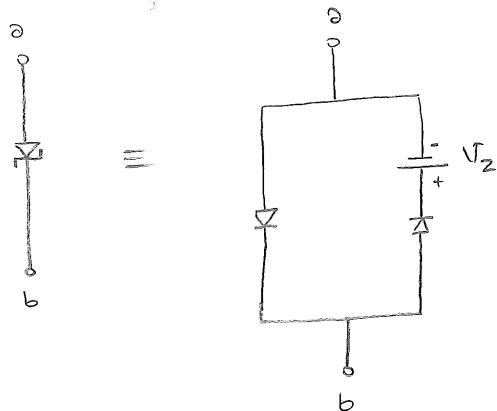
Note that we can represent the Zener diode with two diodes and a battery



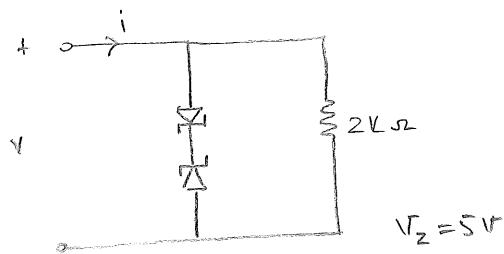Exercise [ZPS III-9(c)] Sketch the part (i-v) characteristics for :




Answer :

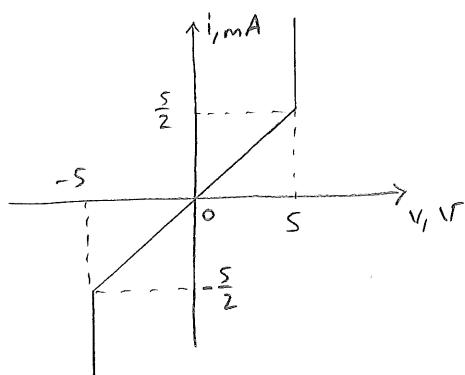

Ch. IV


operational Amplifiers

Six (or more) terminal device

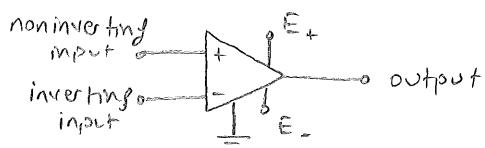

E_+ & E_- terminals are connected to DC voltage supplies. The values $E_+ > E_-$ determine the upper & lower limits of the output voltage v_o .

That is, $E_- \leq v_o \leq E_+$

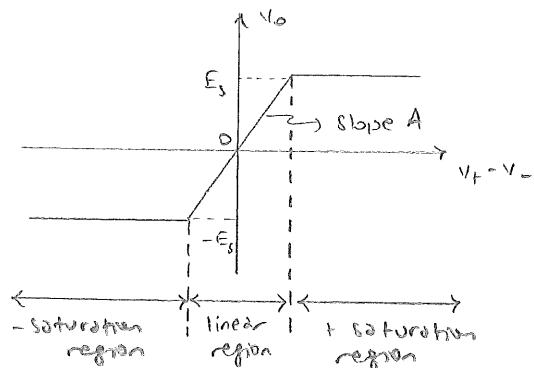Transfer Characteristics (let $E_+ = E_s$ & $E_- = -E_s$)

A : open-loop voltage gain

Typically $A \approx 200,000$


v_o : voltage of the output terminal
 v_+ : voltage of the \oplus terminal
 v_- : voltage of the \ominus terminal

} Work zone
Werner
grund

OP-AMP has three operating modes:

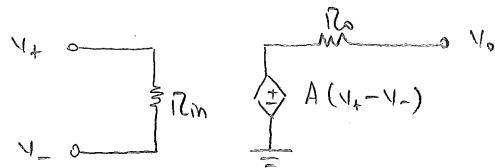- 1) linear mode, $v_o = A(v_+ - v_-)$ and $-E_s < v_o < E_s$
- 2) + Sat mode, $v_o = E_s$ and $A(v_+ - v_-) > E_s$
- 3) - Sat mode, $v_o = -E_s$ and $A(v_+ - v_-) < -E_s$

Dependent source model of an OPAMP operating in linear region:



R_{in} : input resistance, $\sim 10^6 - 10^{12} \Omega$


R_o : output resistance, $\sim 10 - 100 \Omega$

A : voltage gain, $\sim 10^5 - 10^8 \text{ V/V}$


Remark For many applications it is reasonable to work with the ideal OP-AMP model. There are two idealizations:

- 1) Finite-gain ideal OP-AMP model: $R_{in} = \infty$, $R_o = 0$, $A < \infty$
- 2) Infinite-gain ideal OP-AMP model: $R_{in} = \infty$, $R_o = 0$, $A = \infty$

Infinite-gain ideal OP-AMP

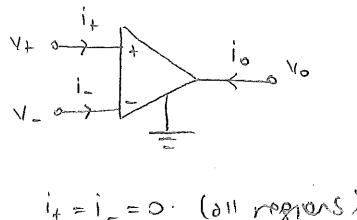


Linear region	+sat region	-sat region
$V_+ = V_-$	$V_+ > V_-$	$V_+ < V_-$
$-E_S \leq V_o \leq E_S$	$V_o = E_S$	$V_o = -E_S$

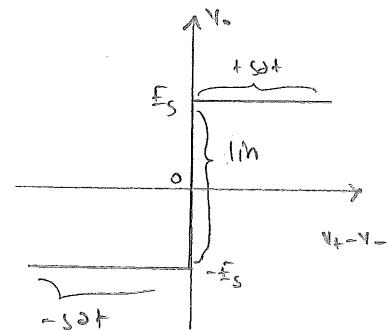

Remark : $i_o \neq 0$!

Some useful OPAMP circuits :

Voltage follower (buffer)

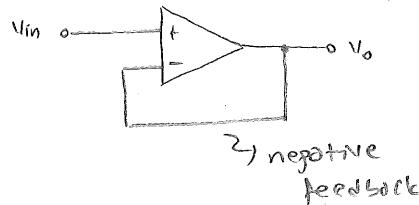

$$V_+ = V_{IN}, V_- = V_o$$

Linear $V_+ = V_- \& -E_S \leq V_o \leq E_S$


$$\Rightarrow V_o = V_{IN} \& -E_S \leq V_{IN} \leq E_S$$

+sat $V_+ > V_- \& V_o = E_S$


$$\Rightarrow V_{IN} > E_S$$

-sat $V_+ < V_- \& V_o = -E_S$

$$\Rightarrow V_{IN} < -E_S$$

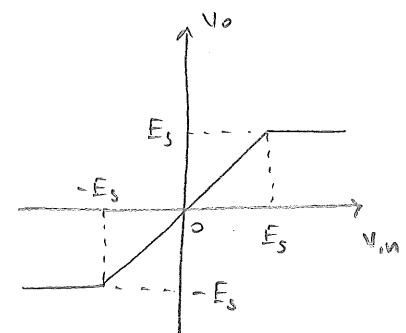


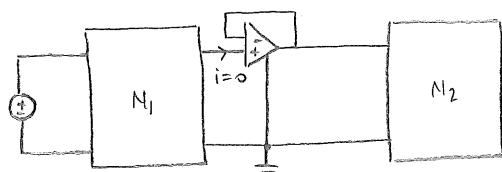Remark Buffers are widely used to isolate 2 two-parts





Here, the buffer prevents N_2 from "loading down" N_1 .

Ex:

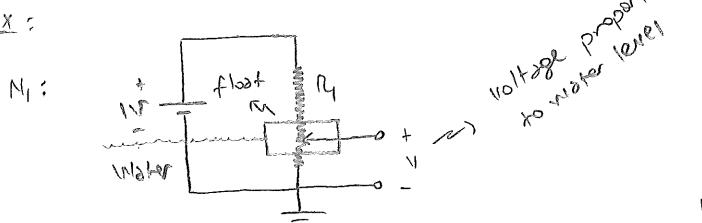


~) circuitry that controls the water pump to regulate the water level where $R_2 \ll R_1$

How about?

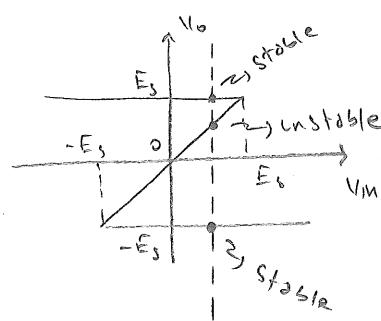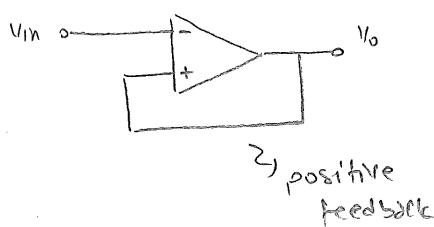

(i.e. in practice the OP-AMP will quickly jump to either to +sat or to -sat region under any disturbance.)

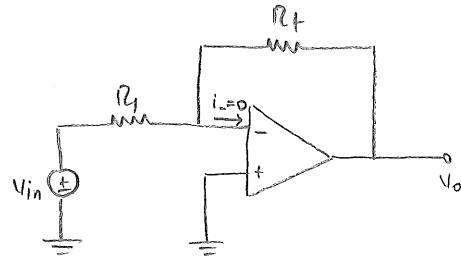Inverting amplifier

$$KCL : \frac{V_- - V_{in}}{R_1} + \frac{V_- - V_0}{R_f} = 0$$

$$\Rightarrow \left(\frac{1}{R_1} + \frac{1}{R_f} \right) V_- = \frac{1}{R_1} V_{in} + \frac{1}{R_f} V_0$$

$$\Rightarrow V_- = \left(\frac{1}{R_1} + \frac{1}{R_f} \right)^{-1} \left\{ \frac{1}{R_1} V_{in} + \frac{1}{R_f} V_0 \right\} \quad (1)$$

$V_f = 0$ (2). Note that (1) & (2) are valid at all regions.

linear $V_- = V_+$ & $-E_s \leq V_0 \leq E_s$

$$\left(\frac{1}{R_1} + \frac{1}{R_f} \right)^{-1} \left\{ \frac{1}{R_1} V_{in} + \frac{1}{R_f} V_0 \right\} = 0 \Rightarrow V_0 = - \frac{R_f}{R_1} V_{in}$$


$$\& -E_s \leq - \frac{R_f}{R_1} V_{in} \leq E_s \Rightarrow - \frac{R_1}{R_f} E_s \leq V_{in} \leq \frac{R_1}{R_f} E_s$$


+Sat $V_- < V_+$ & $V_0 = E_s$

$$\left(\frac{1}{R_1} + \frac{1}{R_f} \right)^{-1} \left\{ \frac{1}{R_1} V_{in} + \frac{1}{R_f} E_s \right\} < 0 \Rightarrow V_{in} < - \frac{R_1}{R_f} E_s$$

-Sat $V_- > V_+$ & $V_0 = -E_s$ $\Rightarrow V_{in} > \frac{R_1}{R_f} E_s$

Hence,

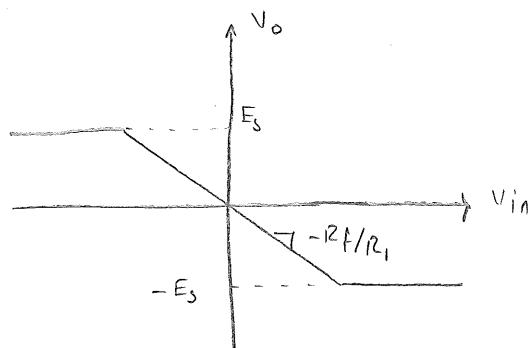

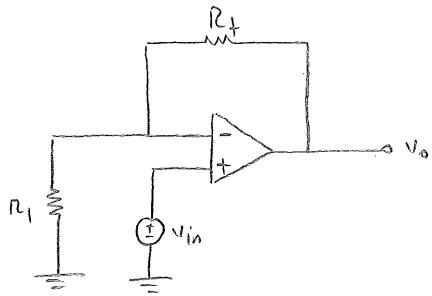Noninverting amplifier

$$V_{CL} : \frac{V_-}{R_1} + \frac{V_- - V_o}{R_f} = 0 \Rightarrow V_- = \left(1 + \frac{R_f}{R_1}\right)^{-1} V_o \quad (1)$$

$$\& V_f = V_o \quad (2)$$

linear $V_- = V_f \& -E_s \leq V_o \leq E_s$

$$\Rightarrow \left(1 + \frac{R_f}{R_1}\right)^{-1} V_o = V_m \Rightarrow \boxed{V_o = \left(1 + \frac{R_f}{R_1}\right) V_m}$$

$$\& -E_s \leq \left(1 + \frac{R_f}{R_1}\right) V_m \leq E_s \Rightarrow \boxed{-\left(1 + \frac{R_f}{R_1}\right)^{-1} E_s \leq V_m \leq \left(1 + \frac{R_f}{R_1}\right)^{-1} E_s}$$


+Sat $V_- < V_f \& \boxed{V_o = E_s}$

-Sat $V_- > V_f \& \boxed{V_o = -E_s}$


$$\boxed{\left(1 + \frac{R_f}{R_1}\right)^{-1} E_s < V_m}$$

$$\boxed{-\left(1 + \frac{R_f}{R_1}\right)^{-1} E_s > V_m}$$

Hence,

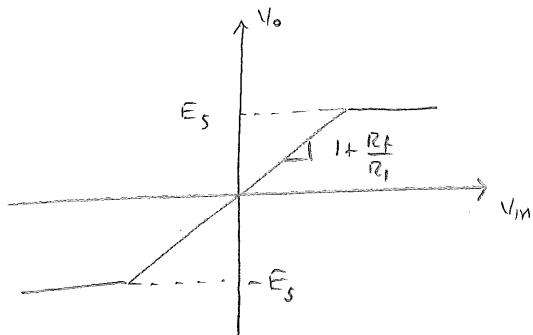

Remark Note that the voltage follower is a special case of the noninverting amplifier with $R_f = 0$ & $R_1 = \infty$.

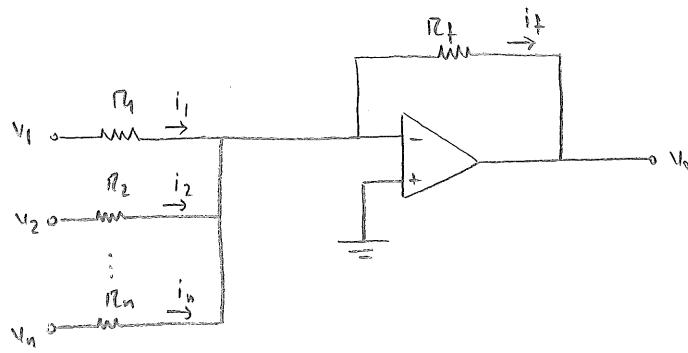Summing amplifierIn linear region $v_- = v_+ = 0$

$$\Rightarrow i_k = \frac{v_k - v_-}{R_k} = \frac{v_k}{R_k} \quad \text{and} \quad i_f = \frac{v_- - v_o}{R_f} = -\frac{v_o}{R_f}$$


$$\text{KCL} \Rightarrow i_1 + i_2 + \dots + i_n = i_f$$

$$\Rightarrow \frac{v_1}{R_1} + \frac{v_2}{R_2} + \dots + \frac{v_n}{R_n} = -\frac{v_o}{R_f}$$

$$\Rightarrow v_o = - \left(\frac{R_f}{R_1} v_1 + \frac{R_f}{R_2} v_2 + \dots + \frac{R_f}{R_n} v_n \right) \quad \boxed{\text{(in linear region)}}$$

Difference amplifier
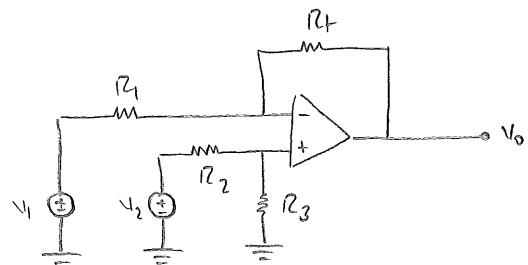
$$v_f = \frac{R_3}{R_2 + R_3} v_2 = \left[1 + \frac{R_2}{R_3} \right]^{-1} v_2 \quad (1)$$



$$\frac{v_- - v_1}{R_1} + \frac{v_- - v_o}{R_f} = 0 \Rightarrow \left(\frac{1}{R_1} + \frac{1}{R_f} \right) v_- = \frac{v_1}{R_1} + \frac{v_o}{R_f}$$


$$\Rightarrow v_o = \frac{R_f}{R_1} \left\{ \left[1 + \frac{R_2}{R_3} \right] v_- - v_1 \right\} \quad (2)$$

in linear region $v_f = v_-$

$$(1) \text{ and } (2) \Rightarrow v_o = \frac{R_f}{R_1} \left\{ \left[1 + \frac{R_2}{R_f} \right] \left[1 + \frac{R_2}{R_3} \right]^{-1} v_2 - v_1 \right\}$$

Then choosing $\frac{R_2}{R_f} = \frac{R_2}{R_3}$ yields


$$\boxed{v_o = \frac{R_f}{R_1} (v_2 - v_1)} \quad \text{(in lin. region)}$$

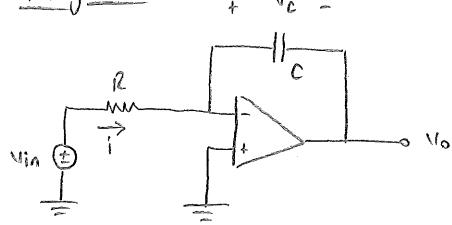IntegratorIn linear region $v_- = v_+ = 0$

$$\Rightarrow i = \frac{v_{in}}{R} \quad (1) \quad \& \quad v_c = -v_o \quad (2)$$

$$\text{Also, } v_c(t) = v_c(0) + \frac{1}{C} \int_0^t i(\tau) d\tau \quad (3)$$

$$(1), (2), (3) \Rightarrow v_o(t) = v_o(0) - \frac{1}{RC} \int_0^t v_{in}(\tau) d\tau \quad (\text{in lin. region})$$

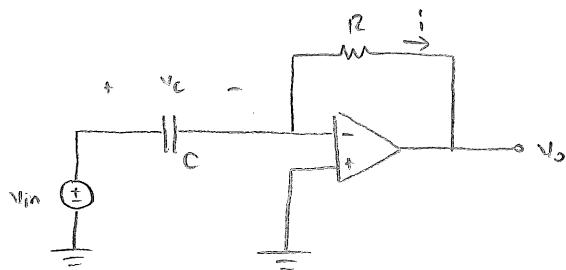DifferentiatorIn linear region $v_- = v_+ = 0$


$$v_{in} = v_c$$

$$i = C \frac{dv_c}{dt} = C \frac{dv_{in}}{dt}$$

$$v_o = -RI$$

$$v_o(t) = -RC \frac{dv_{in}}{dt} \quad (\text{in lin. region})$$

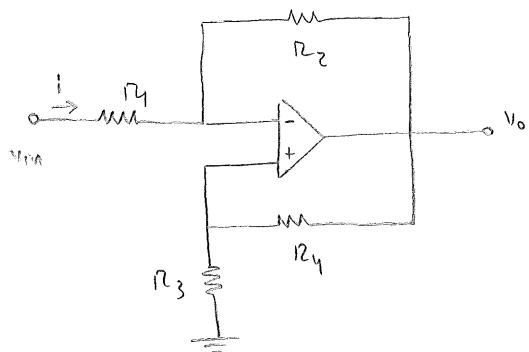Example obtain the input ($v_{in} - i$) & transfer ($v_o - v_o$) char.



$$v_+ = \frac{R_2}{R_3 + R_2} v_o \quad (1)$$

$$\frac{v_- - v_{in}}{R_1} + \frac{v_- - v_o}{R_2} = 0$$

$$\Rightarrow v_- = \frac{R_2}{R_1 + R_2} v_{in} + \frac{R_1}{R_1 + R_2} v_o \quad (2)$$

$$\text{and } i = \frac{1}{R_1 + R_2} (v_{in} - v_o) \quad (3)$$

Define $\beta := \frac{R_2}{R_3 + R_2}$, $\gamma := \frac{R_1}{R_1 + R_2}$ (Note that $0 < \beta < 1$ & $0 < \gamma < 1$.)

Linear region $v_+ = v_-$ & $-E_S \leq v_o \leq E_S$

$$(1) \& (2) \Rightarrow \beta v_o = (1-\gamma) v_{in} + \gamma v_o \Rightarrow v_o = \frac{1-\gamma}{\beta-\gamma} v_{in}$$

$$\text{Define } \bar{v}_i := \left| \frac{\beta-\gamma}{1-\gamma} \right| E_S \Rightarrow \text{In linear region } -\bar{v}_i \leq v_{in} \leq \bar{v}_i$$

$$(3) \Rightarrow i = \frac{1}{R_1 + R_2} \left(1 - \frac{v_o}{v_{in}} \right) v_{in}$$

$$= \frac{1}{R_1 + R_2} \left(1 - \frac{1-\gamma}{\beta-\gamma} \right) v_{in}$$

$$\Rightarrow i = \frac{1}{R_1 + R_2} \cdot \frac{\beta-1}{\beta-\gamma} v_{in}$$

$$\text{Define } G := \left| \frac{1}{R_1 + R_2} \cdot \frac{\beta-1}{\beta-\gamma} \right|$$

+ Sat region $v_+ > v_- \quad \& \quad v_o = E_s$

$$(1) \& (2) \Rightarrow \beta v_o > (1-\gamma) v_{in} + \gamma v_o$$

$$\Rightarrow \beta E_s > (1-\gamma) v_{in} + \gamma E_s \Rightarrow v_{in} < \frac{\beta - \gamma}{1-\gamma} E_s$$







$$(3) \Rightarrow i = \frac{1}{R_1 + R_2} (v_{in} - E_s)$$

- Sat region $v_+ < v_- \quad \& \quad v_o = -E_s$


$$v_{in} > -\frac{\beta - \gamma}{1-\gamma} E_s$$

$$i = \frac{1}{R_1 + R_2} (v_{in} + E_s)$$

Cases : $\beta > \gamma$

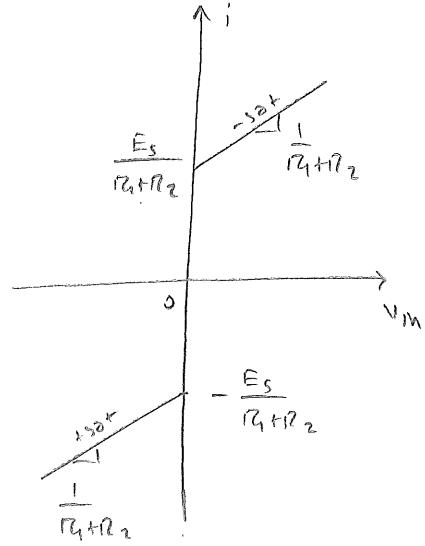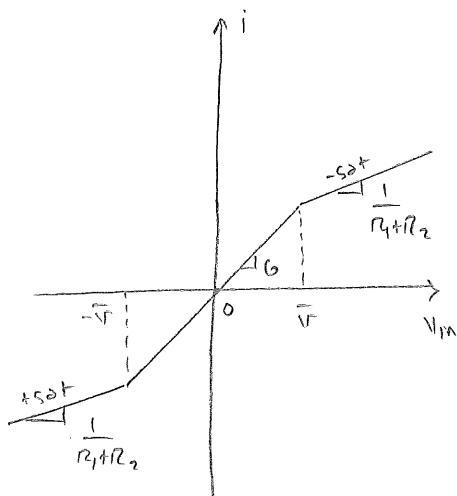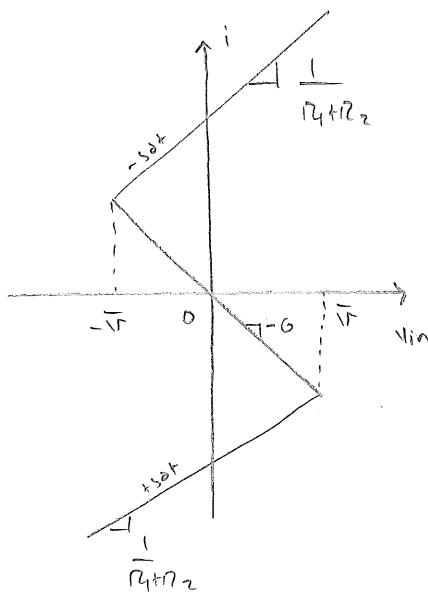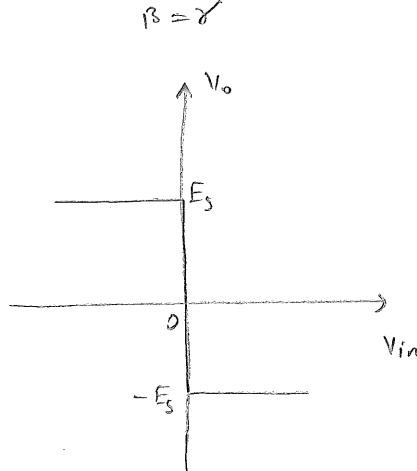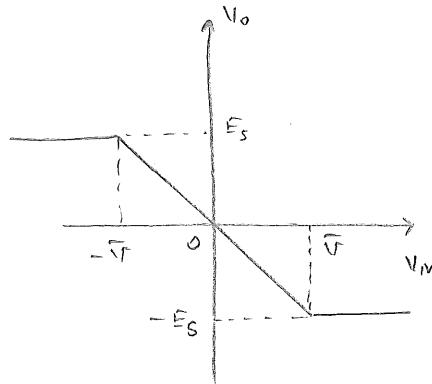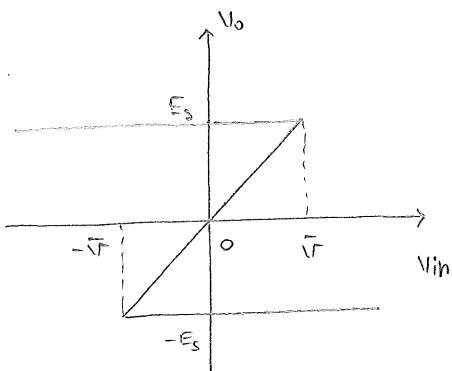

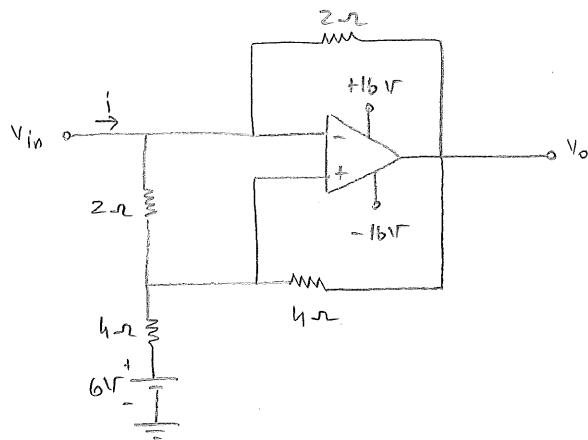Example Obtain the input (v_{in}) & transfer ($v_{in} \sim v_o$) char.



$$v_- = v_{in} \quad (1)$$

$$v_+ = ?$$

$$\frac{v_+ - v_{in}}{2} + \frac{v_+ - 6}{4} + \frac{v_+ - v_o}{4} = 0$$

$$\Rightarrow \left\{ \frac{1}{2} + \frac{1}{4} + \frac{1}{4} \right\} v_+ = \frac{1}{2} v_{in} + \frac{1}{4} v_o + \frac{3}{2}$$

$$\Rightarrow v_+ = \frac{1}{2} v_{in} + \frac{1}{4} v_o + \frac{3}{2} \quad (2)$$

$$i = ?$$

$$i = \frac{v_{in} - v_+}{2} + \frac{v_{in} - v_o}{2}$$

$$= v_{in} - \frac{1}{2} v_o - \frac{1}{2} \left\{ \frac{1}{2} v_{in} + \frac{1}{4} v_o + \frac{3}{2} \right\}$$

$$\Rightarrow i = \frac{3}{4} v_{in} - \frac{5}{8} v_o - \frac{3}{4} \quad (3)$$

Eq. (1), (2), (3) are valid in all regions!

Linear region $v_- = v_+$ & $-16 \leq v_o \leq 16$

$$v_- = v_+ \Rightarrow v_{in} = \frac{1}{2} v_{in} + \frac{1}{4} v_o + \frac{3}{2} \Rightarrow v_o = 2v_{in} - 6$$

$$-16 \leq v_o \leq 16 \Rightarrow -16 \leq 2v_{in} - 6 \leq 16 \Rightarrow -5 \leq v_{in} \leq 11$$

$$(3) \Rightarrow i = \frac{3}{4} v_{in} - \frac{5}{8} (2v_{in} - 6) - \frac{3}{4} \Rightarrow i = -\frac{1}{2} v_{in} + 3$$

Sat $v_- < v_+$ & $v_o = 16V$

$$v_- < v_+ \Rightarrow v_{in} < \frac{1}{2} v_{in} + \frac{1}{4}(16) + \frac{3}{2} \Rightarrow v_{in} < 11$$



$$(3) \Rightarrow i = \frac{3}{4} v_{in} - \frac{5}{8}(16) - \frac{3}{4} \Rightarrow i = \frac{3}{4} v_{in} - \frac{43}{4}$$




Sat $v_- > v_+$ & $v_o = -16V$

$$v_- > v_+ \Rightarrow v_{in} > \frac{1}{2} v_{in} + \frac{1}{4}(-16) + \frac{3}{2} \Rightarrow v_{in} > -5$$

$$(3) \Rightarrow i = \frac{3}{4} v_{in} - \frac{5}{8}(-16) - \frac{3}{4} \Rightarrow i = \frac{3}{4} v_{in} + \frac{37}{4}$$


Hence,

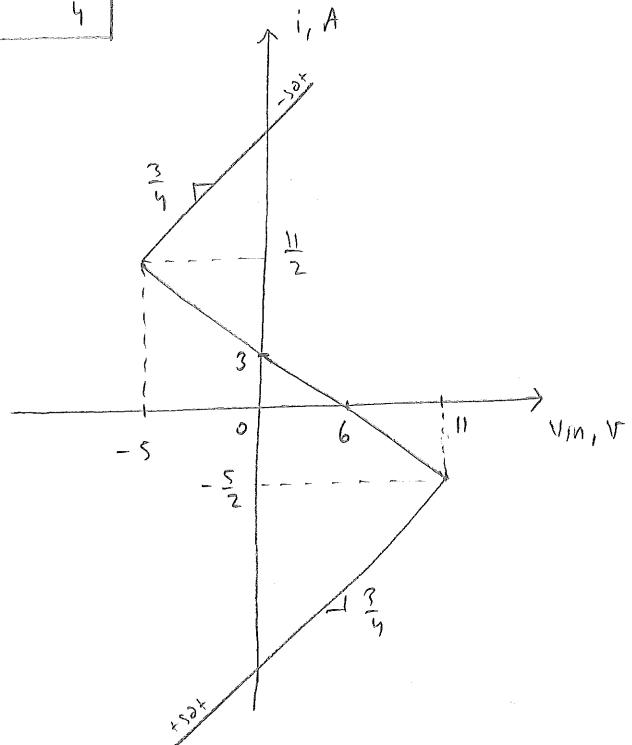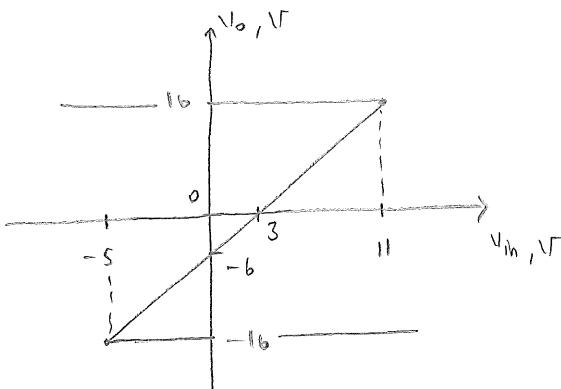

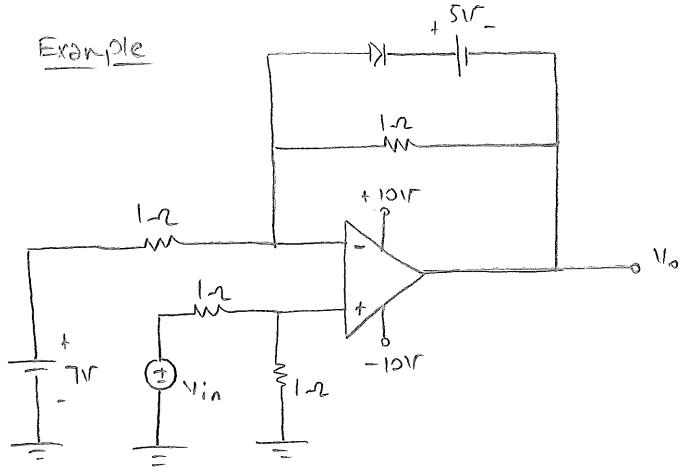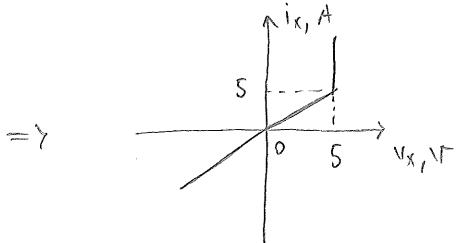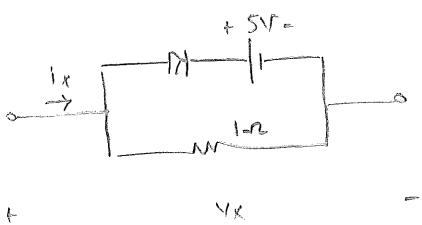Exampleobtain the transfer char. ($V_{in} - V_o$ curve)Soln

$$\Rightarrow V_x = \begin{cases} i_x & \text{for } i_x \leq 5 \quad (\text{diode OFF}) \\ 5 & \text{for } i_x > 5 \quad (\text{diode ON}) \end{cases} \quad (1)$$

Hence

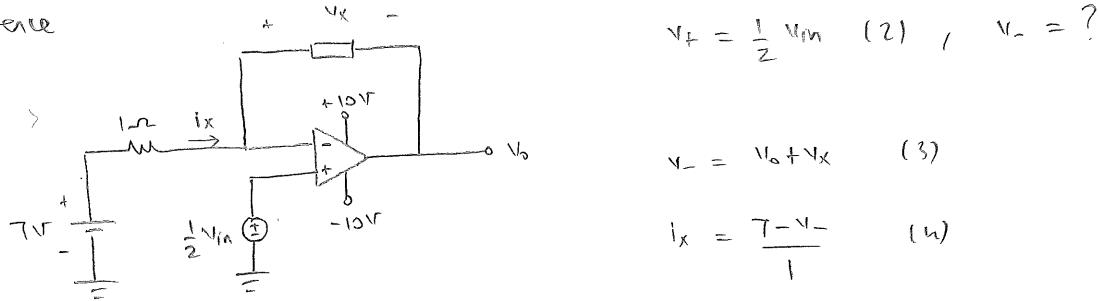

Using (1), (3), (4) :

$$V_- = \begin{cases} V_o + (7 - V_-) & \text{for } 7 - V_- \leq 5 \\ V_o + 5 & \text{for } 7 - V_- > 5 \end{cases}$$

$$\Rightarrow V_- = V_o + 7 - V_- \Rightarrow V_- = \frac{1}{2}(V_o + 7) \quad \text{under } 7 - V_- \leq 5 \Rightarrow 7 - \frac{1}{2}(V_o + 7) \leq 5 \Rightarrow V_o \geq -3$$

$$\text{and } V_- = V_o + 5 \quad \text{under } 7 - V_- > 5 \Rightarrow 7 - (V_o + 5) > 5 \Rightarrow V_o < -3$$

$$\text{Therefore } V_- = \begin{cases} \frac{1}{2}(V_o + 7) & \text{for } V_o \geq -3 \quad (\text{OFF}) \\ V_o + 5 & \text{for } V_o < -3 \quad (\text{ON}) \end{cases} \quad (5)$$

Note that (2) & (5) are valid in all regions!

linear $v_+ = v_-$, $-10 \leq v_o \leq 10$

$$(2) \& (5) \Rightarrow \frac{1}{2}v_{in} = \begin{cases} \frac{1}{2}(v_o + 7) & \text{for } -3 \leq v_o \leq 10 \\ v_o + 5 & \text{for } -10 \leq v_o < -3 \end{cases}$$

$$\Rightarrow \frac{1}{2}v_{in} = \frac{1}{2}(v_o + 7) \Rightarrow \boxed{v_o = v_{in} - 7} \quad \text{when } -3 \leq v_{in} - 7 \leq 10 \Rightarrow \boxed{4 \leq v_{in} \leq 17}$$

$$\& \frac{1}{2}v_{in} = v_o + 5 \Rightarrow \boxed{v_o = \frac{1}{2}v_{in} - 5} \quad \text{when } -10 \leq \frac{1}{2}v_{in} - 5 < -3 \Rightarrow \boxed{-10 \leq v_{in} < 4}$$

sat $v_+ > v_-$, $\boxed{v_o = 10V}$

since $v_o = 10V$, (5) $\Rightarrow v_- = \frac{1}{2}(10 + 7) = \frac{17}{2}V$


Then (2) $\Rightarrow \frac{1}{2}v_{in} > \frac{17}{2} \Rightarrow \boxed{v_{in} > 17}$

-sat $v_+ < v_-$, $\boxed{v_o = -10V}$

(5) $\Rightarrow v_- = -10 + 5 = -5V$



(2) $\Rightarrow \frac{1}{2}v_{in} < -5 \Rightarrow \boxed{v_{in} < -10}$

Hence,

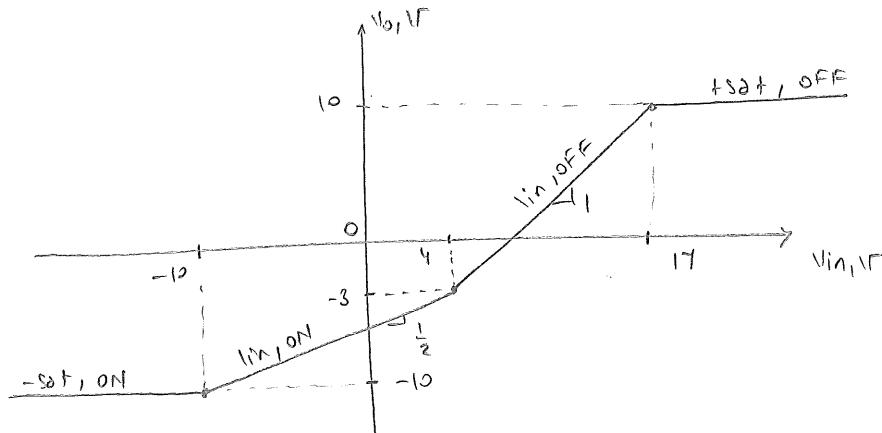

More realistic model of opAmp

Finite gain model in linear region

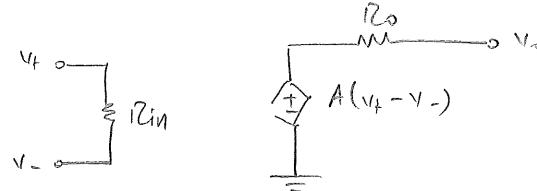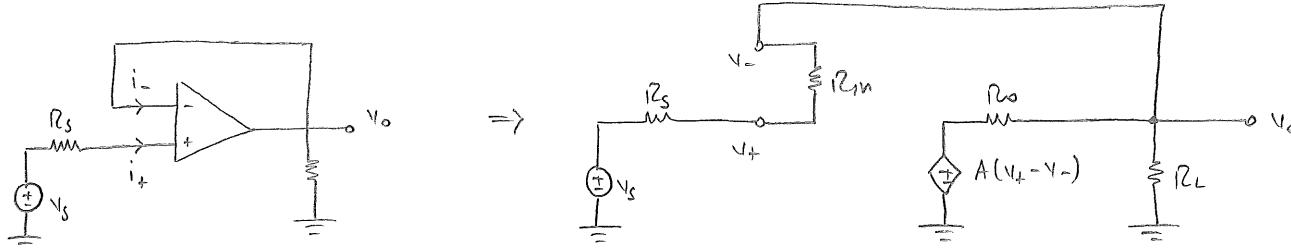Example Analyze the voltage follower circuit using the finite-gain model

$$\text{Let } A = 10^5, R_s = 1k\Omega, R_m = 100k\Omega$$

$$R_o = 100\Omega, R_L = 10k\Omega$$

Remark Recall that using the ideal model we've obtained $\frac{v_o}{v_s} = 1$ under the assumption that $i_+ = i_- = 0$.

Sol'n Write KCL at the output node

$$\left. \begin{aligned} \frac{v_o - A(v_+ - v_-)}{R_o} + \frac{v_o}{R_L} + \frac{v_o - v_s}{R_s + R_m} &= 0 \\ \frac{1}{R_o} \left(v_o - \frac{A R_m (v_s - v_o)}{R_m + R_s} \right) + \frac{v_o}{R_L} + \frac{v_o - v_s}{R_s + R_m} &= 0 \end{aligned} \right\}$$


$$\& v_+ - v_- = \frac{R_m}{R_m + R_s} (v_s - v_o)$$

$$\Rightarrow \frac{v_o}{v_s} = \frac{\left[\frac{A R_m}{R_o (R_m + R_s)} + \frac{1}{R_s + R_m} \right] \approx 990.1}{\left[\frac{A R_m}{R_o (R_m + R_s)} + \frac{1}{R_s + R_m} \right] + \left[\frac{1}{R_o} + \frac{1}{R_L} \right] \approx 0.0101} = 0.999898 \approx 1$$

$$\& i_+ = \frac{v_s - v_o}{R_s + R_m} = \frac{\left(1 - \frac{v_o}{v_s} \right)}{R_s + R_m} \cdot v_s, \text{ for } v_s = 10V \text{ we have } i_+ = 1.01 \times 10^{-9} A \approx 0$$

Conclusion The (infinite-gain) ideal opAmp model works well!

Common Mode Rejection Ratio (CMRR)

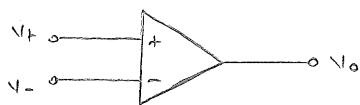

The output voltage for actual opamps satisfy

$$V_0 = A_+ V_+ - A_- V_- \quad (1)$$

[Up to now we've taken $A_+ = A_- = A$ but $A_+ \neq A_-$ in reality.]

$$(1) \Rightarrow v_o = A_d (v_+ - v_-) + A_c \left(\frac{v_+ + v_-}{2} \right)$$



 differential voltage common mode voltage

where $A_d := \frac{A_+ + A_-}{2}$ differential gain


$$A_C := A_+ - A_- \quad \text{common mode gain}$$

[Up to now we've taken $A_c = 0$]


$$\text{Definition} \quad CMR12 := \left| \frac{A_d}{A_c} \right| \quad \text{or} \quad CMR12_{dB} := 20 \log \left| \frac{A_d}{A_c} \right|$$

Remark The higher the CMR_{DC} the better it is. Generally CMR_{DC} > 70 dB works fine for most applications. Widely used op-amp chip 741 has a CMR_{DC} of 90 dB.


Ch. II

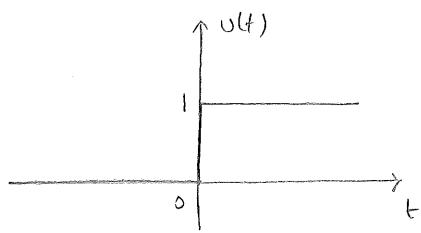Dynamic ElementsElementary functions:


unit step function

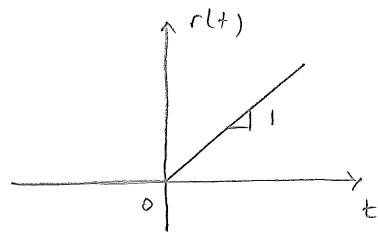

unit ramp function

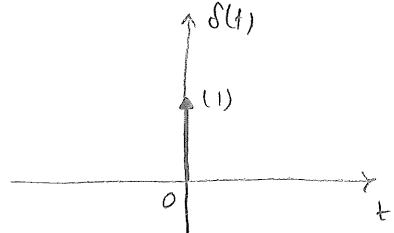unit impulse function
(delta function)

$$\delta(t) = ?$$

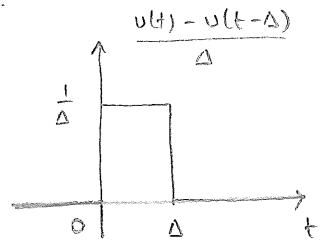delta function $\delta(t) := \lim_{\Delta \rightarrow 0} \frac{u(t) - u(t - \Delta)}{\Delta}$

$$\Rightarrow \delta(t) := \begin{cases} 0 & \text{for } t \neq 0 \\ \underbrace{\text{singular}}_? & \text{for } t=0 \end{cases}$$

\rightarrow singularity is such that $\int_{-\infty}^{\infty} \delta(t) dt = 1$ for all $\alpha, \beta > 0$.

$$\text{observe: } \int_{-\infty}^t \delta(\tau) d\tau = u(t) \quad \text{and} \quad \int_{-\infty}^t u(\tau) d\tau = r(t).$$

$$\text{By convention: } \delta(t) = \frac{d}{dt} u(t) \quad \text{and} \quad u(t) = \frac{d}{dt} r(t).$$


Example Sketch $f(t) = 2u(-t-1)$


$$\text{let } s = -t-1 \Rightarrow 2u(s) = \begin{cases} 2 & \text{for } s > 0 \\ 0 & \text{for } s < 0 \end{cases}$$

$$s > 0 \Rightarrow -t-1 > 0 \Rightarrow t < -1$$


$$s < 0 \Rightarrow -t-1 < 0 \Rightarrow t > -1$$
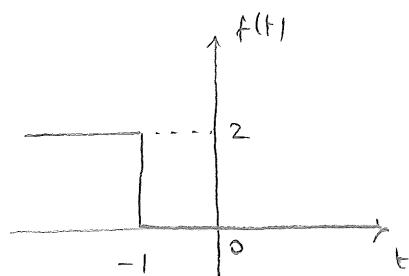
$$\text{Hence } f(t) = \begin{cases} 2 & \text{for } t < -1 \\ 0 & \text{for } t > -1 \end{cases}$$




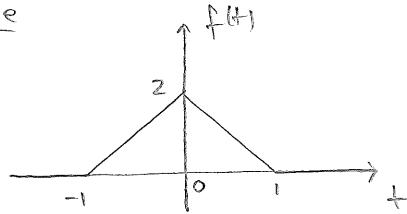Example

Express $f(t)$ in terms of elementary functions $\delta(t)$, $u(t)$, $r(t)$.

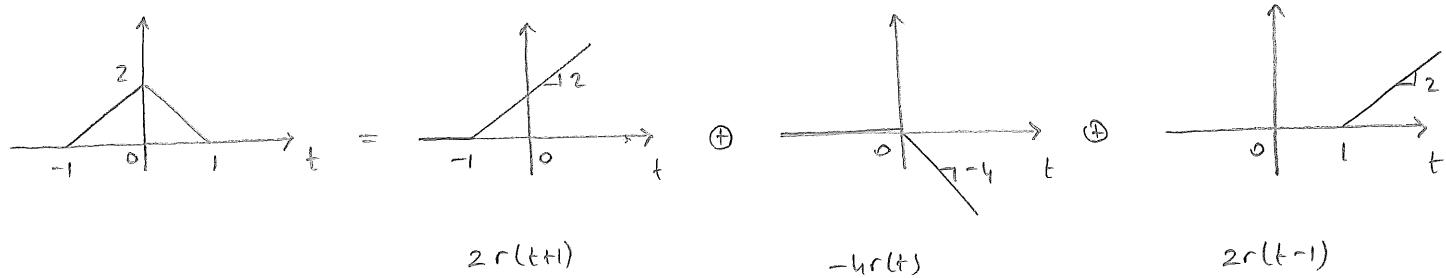Sol'n


$$\Rightarrow f(t) = 2r(t+1) - 4r(t) + 2r(t-1).$$

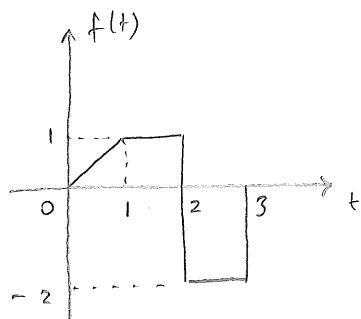Example

$$f(t) = r(t) - r(t-1) - 3u(t-2) + 2u(t-3)$$

$$\dot{f}(t) := \frac{d}{dt} f(t) = ?$$

$$\dot{f}(t) = u(t) - u(t-1) - 3\delta(t-2) + 2\delta(t-3)$$

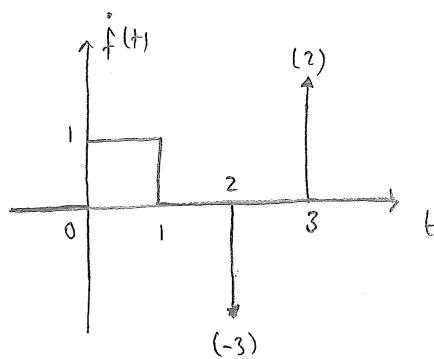Exercise [Sifting property of the impulse function]

Show that $\int_{-\infty}^{\infty} f(t)\delta(t)dt = f(0)$ for continuous f ($T > 0$)

Hence, in general

$$f(t)\delta(t-t_0) = f(t_0)\delta(t-t_0) \quad (\text{for continuous } f.)$$

LTI capacitor

$$\begin{array}{l} + \\ \text{v} \\ - \end{array} \quad \frac{\text{d}q(t)}{\text{d}t} = C \text{v}(t) \quad \left. \begin{array}{l} q(t) = Cv(t) \\ i(t) = \frac{\text{d}}{\text{d}t} q(t) \end{array} \right\}$$

$i(t) = C \frac{\text{d}v(t)}{\text{d}t}$
 $v(t) = v(t_0) + \frac{1}{C} \int_{t_0}^t i(z) \text{d}z$

C: capacitance measured in Farads (F)




instantaneous power: $p(t) = v(t)i(t)$

energy accumulated during interval $[t_0, t]$:

$$\begin{aligned} w(t_0, t) &= \int_{t_0}^t v(z)i(z) \text{d}z \\ &= \int_{t_0}^t v(z) \left\{ C \frac{\text{d}v(z)}{\text{d}z} \right\} \text{d}z \\ &= \int_{v(t_0)}^{v(t)} Cv \text{d}v = \frac{1}{2} Cv^2 \Big|_{v(t_0)}^{v(t)} = \frac{1}{2} Cv(t)^2 - \frac{1}{2} Cv(t_0)^2 \end{aligned}$$

energy stored at time t :

$$w(t) := w(-\infty, t) = \underbrace{\frac{1}{2} Cv(t)^2}_{=0 \text{ by assumption}} - \underbrace{\frac{1}{2} Cv(-\infty)^2}_{=0} = \boxed{\frac{1}{2} Cv(t)^2}$$

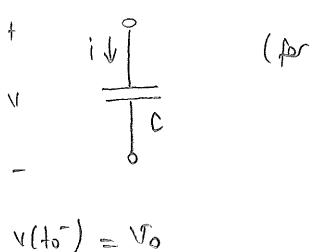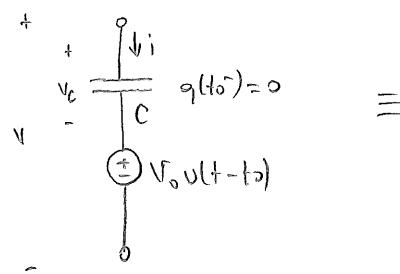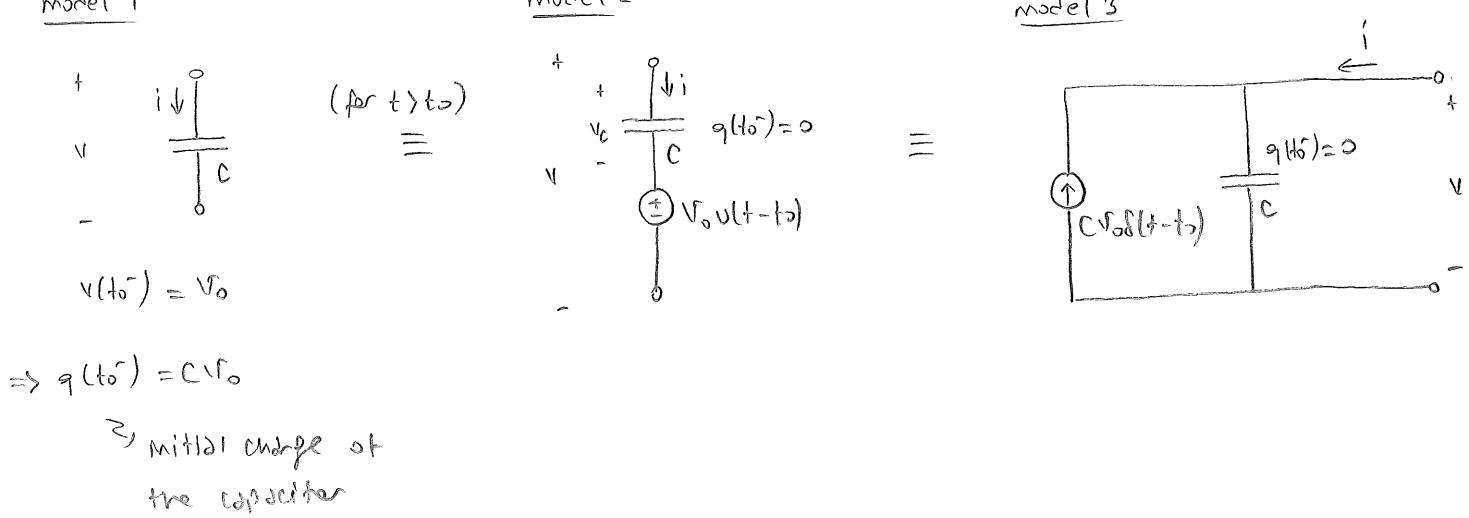Initial condition modelsmodel 1model 2model 3

By equivalence " \equiv " we mean the following: all three models will have the same $v(t)$, $i(t)$ readings for $t > t_0$. [Note that in models 2 & 3 the capacitors are initially uncharged.]

Proof model 1: $v(t) = v(t_0^-) + \frac{1}{C} \int_{t_0^-}^t i(z) dz = V_0 + \frac{1}{C} \int_{t_0^-}^t i(z) dz$

model 2: $v(t) = \underbrace{v_c(t_0^-)}_{=0} + \frac{1}{C} \int_{t_0^-}^t i(z) dz + \underbrace{V_0 v(t-t_0)}_{=V_0 \text{ for } t > t_0}$


$$= V_0 + \frac{1}{C} \int_{t_0^-}^t i(z) dz \quad (\text{for } t > t_0)$$

model 3: $v(t) = \underbrace{v(t_0^-)}_{=0} + \frac{1}{C} \int_{t_0^-}^t [i(z) + C V_0 \delta(z - t_0)] dz$


$$= V_0 \underbrace{\int_{t_0^-}^t \delta(z - t_0) dz}_{=1 \text{ for } t > t_0} + \frac{1}{C} \int_{t_0^-}^t i(z) dz$$

$$= V_0 + \frac{1}{C} \int_{t_0^-}^t i(z) dz \quad (\text{for } t > t_0)$$

Capacitors in parallel connection

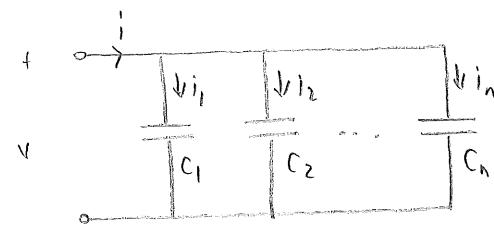

$$v(t_0) = V_0$$

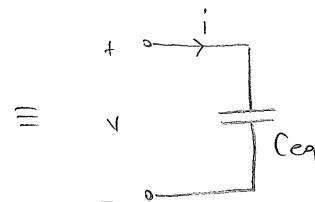


$$v(t_0) = V_0$$

$$C_{eq} = ?$$

$$i(t) = i_1(t) + i_2(t) + \dots + i_n(t) = C_1 \frac{dv_1}{dt} + C_2 \frac{dv_2}{dt} + \dots + C_n \frac{dv_n}{dt}$$

$$= \underbrace{(C_1 + C_2 + \dots + C_n)}_{C_{eq}} \frac{dv}{dt} \Rightarrow \boxed{C_{eq} = C_1 + C_2 + \dots + C_n}$$

Capacitors in series connection

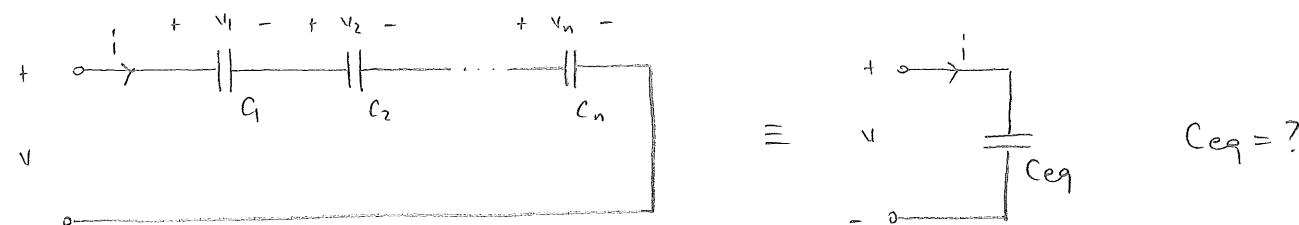

$$v_1(t_0) = V_{10}, v_2(t_0) = V_{20}, \dots, v_n(t_0) = V_{n0}$$

$$v(t_0) = v_1(t_0) + v_2(t_0) + \dots + v_n(t_0)$$

$$v(t) = v_1(t) + v_2(t) + \dots + v_n(t)$$

$$= \left\{ v_1(t_0) + \frac{1}{C_1} \int_{t_0}^t i(z) dz \right\} + \dots + \left\{ v_n(t_0) + \frac{1}{C_n} \int_{t_0}^t i(z) dz \right\}$$

$$= \underbrace{\{V_{10} + V_{20} + \dots + V_{n0}\}}_{v(t_0)} + \underbrace{\left\{ \frac{1}{C_1} + \frac{1}{C_2} + \dots + \frac{1}{C_n} \right\}}_{\frac{1}{C_{eq}}} \int_{t_0}^t i(z) dz$$


$v(t_0)$

$\frac{1}{C_{eq}}$

$$\Rightarrow \frac{1}{C_{eq}} = \frac{1}{C_1} + \frac{1}{C_2} + \dots + \frac{1}{C_n}$$

Current division

$$i_1(t), i_2(t) = ?$$

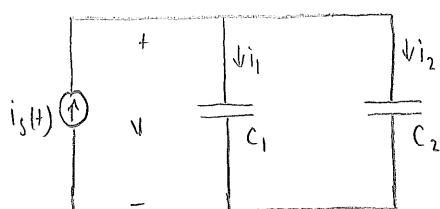


$$\left. \begin{aligned} i_1(t) &= C_1 \frac{dv}{dt} \Rightarrow \frac{dv}{dt} = \frac{1}{C_1} i_1(t) \\ i_2(t) &= C_2 \frac{dv}{dt} \Rightarrow \frac{dv}{dt} = \frac{1}{C_2} i_2(t) \end{aligned} \right\}$$

$$\frac{i_1(t)}{C_1} = \frac{i_2(t)}{C_2} \quad (1)$$

$$(CCl) : i_1(t) + i_2(t) = i_s(t) \quad (2)$$

$$(1) \& (2) \Rightarrow i_1(t) = \frac{C_1}{C_1 + C_2} i_s(t) \quad \& \quad i_2(t) = \frac{C_2}{C_1 + C_2} i_s(t)$$

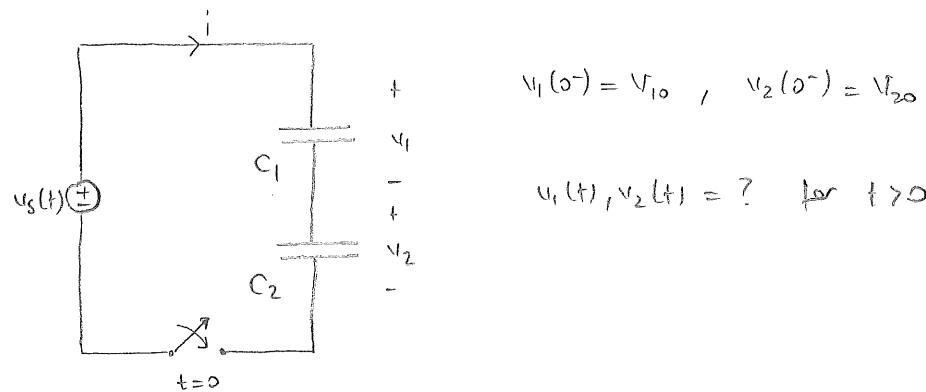Voltage Division

Since the same current visits both capacitors

$$v_1(t) = v_1(0^-) + \frac{1}{C_1} \int_{0^-}^t i(\tau) d\tau \Rightarrow \int_{0^-}^t i(\tau) d\tau = C_1 (v_1(t) - v_{10})$$

$$v_2(t) = v_2(0^-) + \frac{1}{C_2} \int_{0^-}^t i(\tau) d\tau \Rightarrow \int_{0^-}^t i(\tau) d\tau = C_2 (v_2(t) - v_{20})$$


$$\Rightarrow C_1 (v_1(t) - v_{10}) = C_2 (v_2(t) - v_{20}) \quad (1)$$

$$i(v_L) = v_1(t) + v_2(t) = v_s(t) \quad (2)$$

$$(1) \& (2) \Rightarrow v_1(t) = \frac{C_2}{C_1 + C_2} v_s(t) + \frac{C_1 v_{10} - C_2 v_{20}}{C_1 + C_2}$$

$$\& v_2(t) = \frac{C_1}{C_1 + C_2} v_s(t) + \frac{C_2 v_{20} - C_1 v_{10}}{C_1 + C_2}$$

for $t > 0$

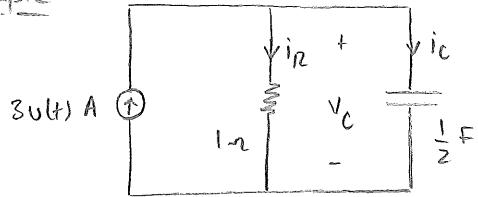
Example

Find $v_c(t)$, $i_R(t)$, $i_C(t)$ for
 a) $v_c(0^-) = 0$
 b) $v_c(0^-) = 4V$

Assumption Henceforth we will assume that the energy stored at a capacitor (or an inductor) is always finite.

Remark Finite energy assumption is not really necessary, we make it because it simplifies analysis.

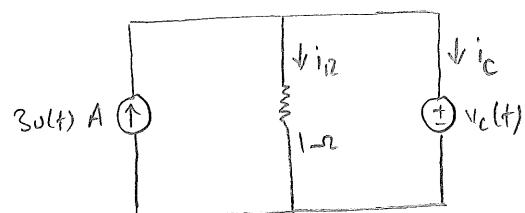Sol'n $v_c(0^-) = 0$ for $0^- < t < 0^+$ let's replace the capacitor with IVS.
 (substitution thm.)



What do we know about $v_c(t)$?

Recall stored energy = $\frac{1}{2}CV_c(t)^2$

Hence finite energy \Rightarrow bounded (finite) $v_c(t)$


Now, bounded $v_c(t) \Rightarrow$ bounded $i_R(t)$

Then LCL \Rightarrow $3A(t) = i_R(t) + i_C(t) \Rightarrow$ bounded $i_C(t)$.

\downarrow
bounded \downarrow
bounded

$$\Rightarrow v_c(0^+) = v_c(0^-) + \underbrace{\frac{1}{12} \int_{0^-}^{0^+} i_C(z) dz}_{\text{=0 since } i_C \text{ bounded}} \Rightarrow v_c(0^+) = v_c(0^-) = 0$$


At $t = 0^+$

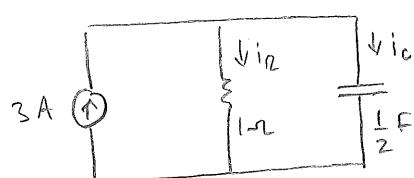

$$v_c(0^+) = 0 \Rightarrow i_R(0^+) = 0$$

$$\Rightarrow i_C(0^+) = 3A$$

b) $v_c(0^-) = 4V$. Exercise. Answer: $v_c(0^+) = 4V$, $i_R(0^+) = 4A$, $i_C(0^+) = -1A$.

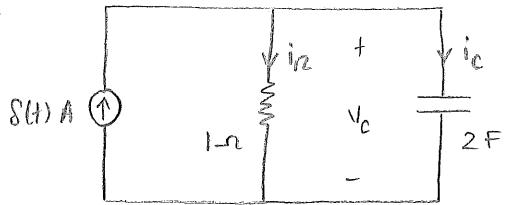
Example

$$v_c(0^-) = V_0$$

Find $v_c(0^+)$, $i_R(0^+)$, $i_C(0^+)$

$0^- < t < 0^+$

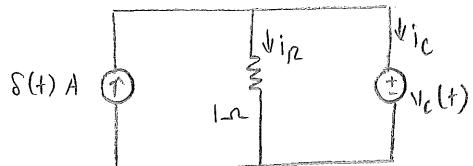finite stored energy \Rightarrow bounded $v_c(t) \Rightarrow$ bounded $i_R(t)$




$$v_c(0^+) = v_c(0^-) + \frac{1}{C} \int_{0^-}^{0^+} i_C(\tau) d\tau$$

$$= V_0 + \frac{1}{2} \int_{0^-}^{0^+} \{ \delta(\tau) - i_R(\tau) \} d\tau$$

$$= V_0 + \frac{1}{2} \underbrace{\int_{0^-}^{0^+} \delta(\tau) d\tau}_{= \frac{1}{2}} - \frac{1}{2} \underbrace{\int_{0^-}^{0^+} i_R(\tau) d\tau}_{=0 \text{ since } i_R \text{ bounded}}$$

$$\text{Hence } v_c(0^+) = V_0 + \frac{1}{2} \text{ Volts.}$$

$t = 0^+$

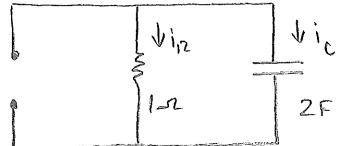

$$i_R(0^+) = \frac{v_c(0^+)}{1} = V_0 + \frac{1}{2} \text{ Amps}$$

$$i_C(0^+) = -i_R(0^+) = -V_0 - \frac{1}{2} \text{ Amps}$$

Remark Note that for $0^- < t < 0^+$ we obtained $i_C(t) = \delta(t) + \{-i_R(t)\}$

Note also that the bounded term has no effect on the value of $v_c(0^+)$. Since any bounded voltage source instead of $\oplus v_c(t)$


$$= \underbrace{\delta(t) + \{-v_c(t)/R\}}_{\substack{\text{impulsive} \\ \text{term}}} + \underbrace{\frac{v_c(t)}{R}}_{\substack{\text{bounded} \\ \text{term}}}$$

would yield the same impulsive term, we can replace $\oplus v_c(t)$ with the


simplest bounded voltage source, i.e., the short circuit to compute the impulsive term of $i_C(t)$ on $0^- < t < 0^+$.

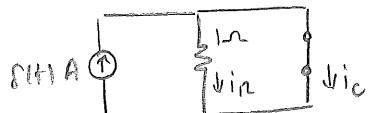Example (revisited) For $0^- < t < 0^+$

$$i_C(t) = \delta(t) \Rightarrow v_c(0^+) = V_0 + \frac{1}{2} \int_{0^-}^{0^+} \delta(\tau) d\tau$$



$$= V_0 + \frac{1}{2} \text{ Volts as expected.}$$

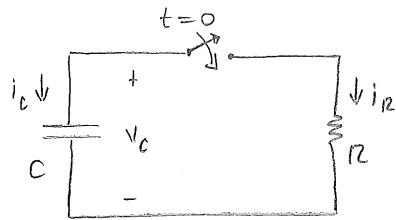Example



$$V_C(0^+) = V_0$$

Note that $V_C(0^+) = V_0$ (1) (why?)

For $t > 0$

$$\left. \begin{aligned} V_C &= RI_R \\ i_C &= C \frac{dV_C}{dt} \\ i_R + i_C &= 0 \end{aligned} \right\} \quad \frac{d}{dt} V_C(t) = -\frac{1}{RC} V_C(t) \quad (2)$$
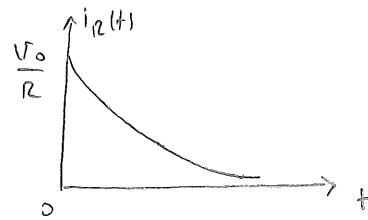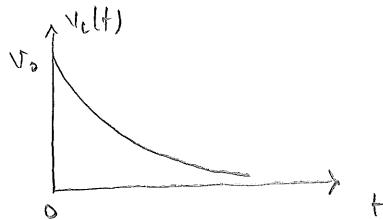
$$(1) \text{ and } (2) \Rightarrow V_C(t) = V_0 e^{-t/RC} \quad \text{and} \quad i_R(t) = \frac{V_0}{R} e^{-t/RC}$$



Energy dissipated at capacitor during $[0, t]$:


$$W_C(0, t) = \frac{1}{2} C V_C^2(t) - \frac{1}{2} C V_0^2 = \frac{1}{2} C V_0^2 [e^{-2t/RC} - 1]$$

Note that $W_C(t) < 0$. Therefore energy is drawn from the capacitor by the circuit.

Energy dissipated at resistor during $[0, t]$:

$$\begin{aligned} W_R(0, t) &= \int_0^t \underbrace{i_R(\tau) V_R(\tau)}_{P_R(\tau)} d\tau = \frac{V_0^2}{R} \int_0^t e^{-2\tau/RC} d\tau = \frac{V_0^2}{R} \left\{ -\frac{RC}{2} e^{-2\tau/RC} \right\}_0^t \\ &= \frac{1}{2} C V_0^2 [1 - e^{-2t/RC}] \end{aligned}$$

Observe $W_C(0, t) + W_R(0, t) = 0$. Hence the energy drawn from the capacitor is dissipated at the resistor.

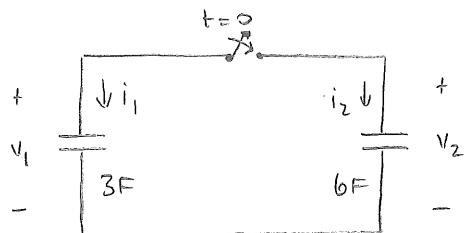Example

$v_1(0^-) = 0, v_2(0^-) = 3V$

Find $v_1(0^+)$ and the total stored energy at $t=0^-$ & $t=0^+$.

Sol'n

$v_1(t) = v_1(0^-) + \frac{1}{3} \int_{0^-}^t i_1(z) dz \Rightarrow \int_{0^-}^t i_1(z) dz = 3v_1 \quad (1)$

$v_2(t) = v_2(0^-) + \frac{1}{6} \int_{0^-}^t i_2(z) dz \Rightarrow \int_{0^-}^t i_2(z) dz = 6(v_2 - 3) \quad (2)$

$kCL \Rightarrow i_1 + i_2 = 0 \quad (3)$

$(1), (2), (3) \Rightarrow 3v_1 + 6(v_2 - 3) = 0 \quad (4)$

$t>0 \quad kCL \Rightarrow v_1 = v_2 \quad (5)$


$(4) \& (5) \Rightarrow 3v_1 + 6(v_1 - 3) = 0 \Rightarrow \boxed{v_1(t) = 2V} \quad \text{for all } t>0.$

$E(0^-) = \frac{1}{2} C_1 v_1(0^-)^2 + \frac{1}{2} C_2 v_2(0^-)^2 = 0 + 27 = \boxed{27 J}$

$E(0^+) = \frac{1}{2} C_1 v_1(0^+)^2 + \frac{1}{2} C_2 v_2(0^+)^2 = \frac{1}{2} (C_1 + C_2) v_1(0^+)^2 = \boxed{18 J}$

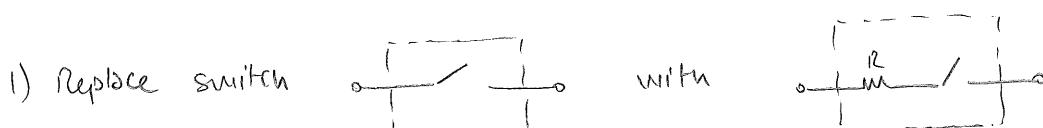Question What happened to $E(0^-) - E(0^+) = 9J$?

Answer Dissipated at the switch. To see this:



2) Compute the energy $W_R(0, T)$ dissipated at R during the interval $[0, T]$

3) Show that $\lim_{T \rightarrow \infty} W_R(0, T) = 9J$ for any $T > 0$.

LTI Inductors

$$\begin{aligned} \phi(t) &= L i(t) \\ v(t) &= \frac{d}{dt} \phi(t) \end{aligned}$$

$$v(t) = L \frac{di(t)}{dt}$$


$$i(t) = i(t_0) + \frac{1}{L} \int_{t_0}^t v(z) dz$$

L : inductance, measured in Henries (H)

instantaneous power: $p(t) = v(t)i(t)$


energy accumulated during interval $[t_0, t]$: $w(t_0, t) = \frac{1}{2} L i(t)^2 - \frac{1}{2} L i(t_0)^2$

energy stored at time t : $w(t) = \frac{1}{2} L i(t)^2$

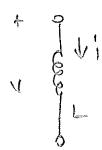Initial Condition Models


$$i(t) = I_0 + \frac{1}{L} \int_{t_0}^t v(z) dz$$

$$i(t_0) = I_0$$


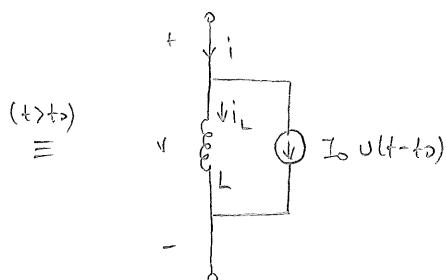


$$\begin{aligned} i(t) &= I_0 v(t-t_0) + i_L(t) \\ &= I_0 + \frac{1}{L} \int_{t_0}^t v(z) dz \quad \text{for } t > t_0 \end{aligned}$$

$$i_L(t_0) = 0$$

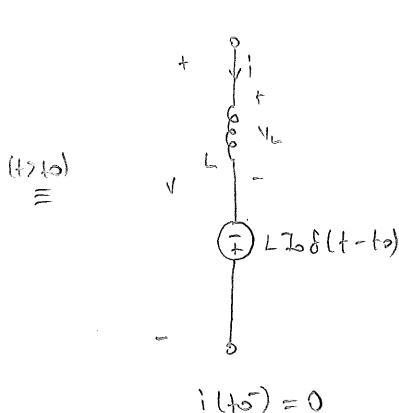

$$\begin{aligned} i(t) &= \frac{1}{L} \int_{t_0}^t u_L(z) dz \\ &= \frac{1}{L} \int_{t_0}^t \{ L I_0 \delta(z-t_0) + v(z) \} dz \\ &= I_0 \int_{t_0}^t \delta(z-t_0) dz + \frac{1}{L} \int_{t_0}^t v(z) dz \\ &= I_0 + \frac{1}{L} \int_{t_0}^t v(z) dz \quad \text{for } t > t_0 \end{aligned}$$

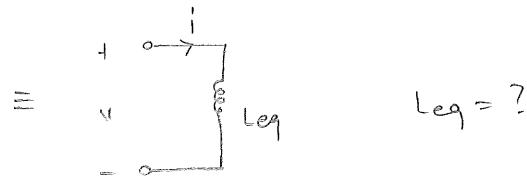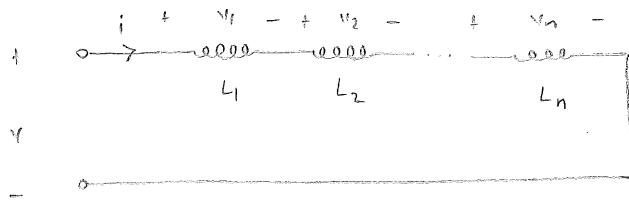Inductors in series connection

$$i(t_0) = I_0$$

$$i(t_0) = I_0$$



$$V = V_1 + V_2 + \dots + V_n$$

$$V = L_{eq} \frac{di}{dt}$$

$$= L_1 \frac{di}{dt} + L_2 \frac{di}{dt} + \dots + L_n \frac{di}{dt}$$

$$\Rightarrow L_{eq} = L_1 + L_2 + \dots + L_n$$

$$= \underbrace{\{L_1 + L_2 + \dots + L_n\}}_{L_{eq}} \frac{di}{dt}$$

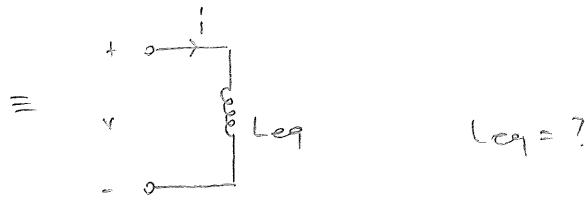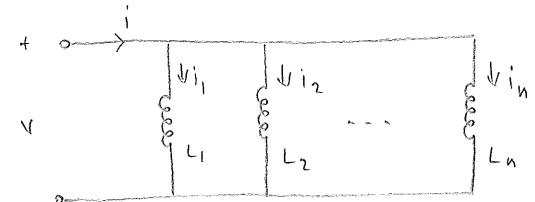Inductors in parallel connection

$$i_1(t_0) = I_{10}, i_2(t_0) = I_{20}, \dots, i_n(t_0) = I_{n0}$$

$$i(t_0) = I_{10} + I_{20} + \dots + I_{n0}$$

$$i(t) = i_1(t) + i_2(t) + \dots + i_n(t)$$


$$i(t) = i(t_0) + \left[\frac{1}{L_{eq}} \int_{t_0}^t V(z) dz \right]$$

$$= \left\{ I_{10} + \frac{1}{L_1} \int_{t_0}^t V(z) dz \right\} + \dots + \left\{ I_{n0} + \frac{1}{L_n} \int_{t_0}^t V(z) dz \right\}$$

$$= (I_{10} + \dots + I_{n0}) + \underbrace{\left(\frac{1}{L_1} + \frac{1}{L_2} + \dots + \frac{1}{L_n} \right)}_{\frac{1}{L_{eq}}} \int_{t_0}^t V(z) dz$$

$$\frac{1}{L_{eq}}$$

$$\Rightarrow L_{eq} = \left(\frac{1}{L_1} + \frac{1}{L_2} + \dots + \frac{1}{L_n} \right)^{-1}$$

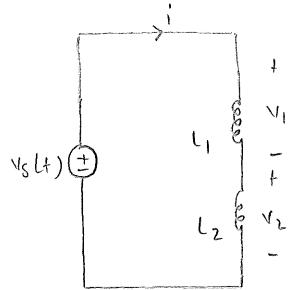
Voltage Division

$$\left. \begin{array}{l} v_1 = L_1 \frac{di}{dt} \\ v_2 = L_2 \frac{di}{dt} \end{array} \right\} \quad \left. \begin{array}{l} \frac{v_1}{L_1} = \frac{v_2}{L_2} \quad (1) \\ v_1 + v_2 = v_s \quad (2) \end{array} \right\}$$

(1) & (2) :

$$v_1(t) = \frac{L_1}{L_1 + L_2} v_s(t)$$

$$v_2(t) = \frac{L_2}{L_1 + L_2} v_s(t)$$

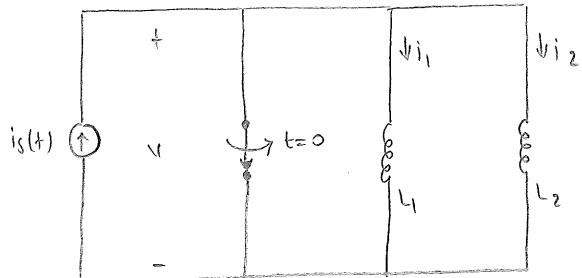Current division

$$i_1(0^-) = I_{10}, \quad i_2(0^-) = I_{20}$$

$$i_1(t), i_2(t) = ? \quad \text{for } t > 0$$

Since both inductors have the same voltage

$$i_1(t) = i_1(0^-) + \frac{1}{L_1} \int_{0^-}^t v(z) dz \Rightarrow \int_{0^-}^t v(z) dz = L_1 (i_1(t) - I_{10})$$

$$i_2(t) = i_2(0^-) + \frac{1}{L_2} \int_{0^-}^t v(z) dz \Rightarrow \int_{0^-}^t v(z) dz = L_2 (i_2(t) - I_{20})$$


$$\Rightarrow L_1 (i_1(t) - I_{10}) = L_2 (i_2(t) - I_{20}) \quad (1)$$

$$\text{ICCL: } i_1(t) + i_2(t) = i_s(t) \quad (2)$$

$$(1) \& (2) \Rightarrow i_1(t) = \frac{L_2}{L_1 + L_2} i_s(t) + \frac{L_1 I_{10} - L_2 I_{20}}{L_1 + L_2}$$


for $t > 0$

$$\& i_2(t) = \frac{L_1}{L_1 + L_2} i_s(t) + \frac{L_2 I_{20} - L_1 I_{10}}{L_1 + L_2}$$

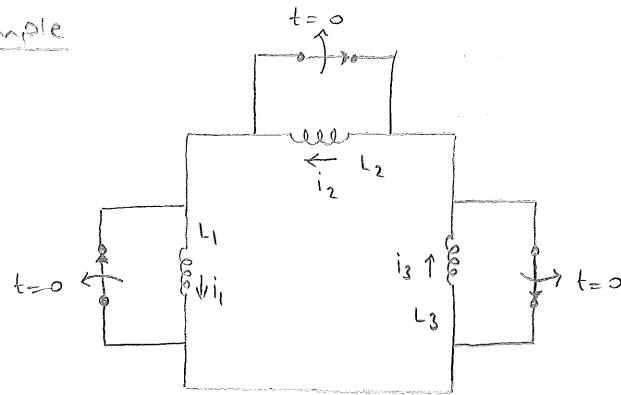Example

$$i_1(0^-) = I_1, \quad i_2(0^-) = I_2, \quad i_3(0^-) = I_3$$

$$i_1(0^+) = ?$$

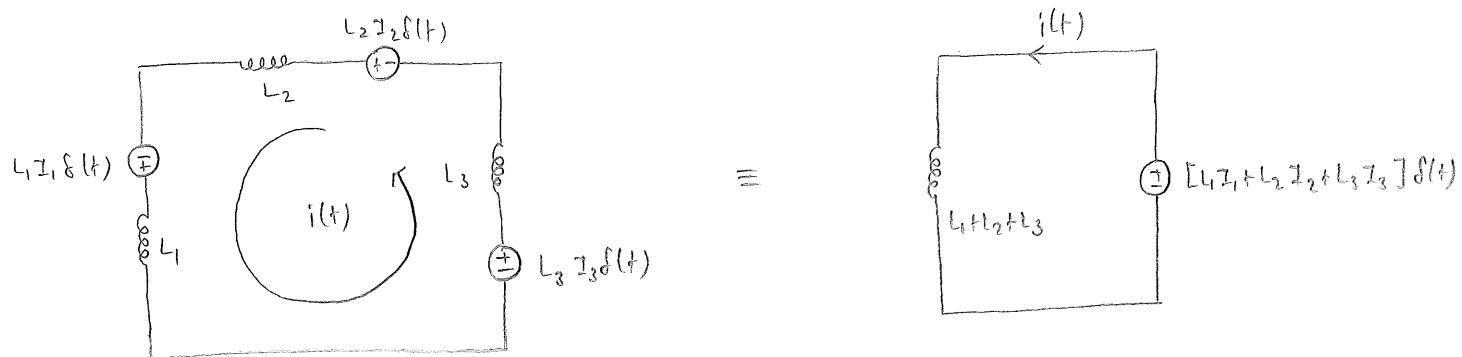Sol'n 1 Use initial condition model

[No initial current on inductors]

$$i(0^+) = \frac{1}{L_1 + L_2 + L_3} \int_{0^-}^{0^+} [L_1 I_1 + L_2 I_2 + L_3 I_3] \delta(t) dt = \frac{L_1 I_1 + L_2 I_2 + L_3 I_3}{L_1 + L_2 + L_3}$$

Sol'n 2



$$i(t) = i_k(0^-) + \frac{1}{L_k} \int_{0^-}^t v_k(\tau) d\tau \quad k=1,2,3$$

$$\Rightarrow \int_{0^-}^t v_k(\tau) d\tau = L_k i(t) - L_k I_k \quad k=1,2,3$$

$$\Rightarrow \int_{0^-}^{t^3} [v_1(\tau) + v_2(\tau) + v_3(\tau)] d\tau = \sum_{k=1}^3 (L_k i(t) - L_k I_k)$$


$\approx \log 10^3 L$

$$\Rightarrow (\sum L_k) i(t) \approx \sum L_k I_k \Rightarrow i(t) = \frac{\sum L_k I_k}{\sum L_k}$$

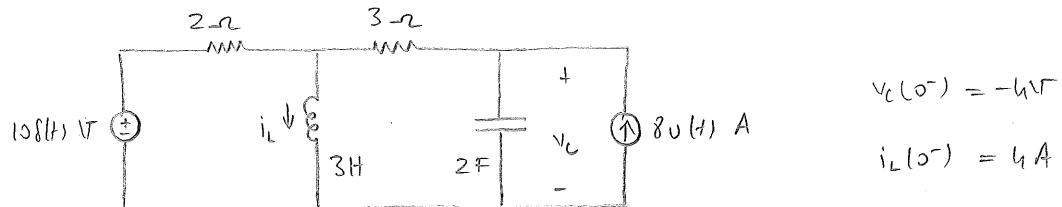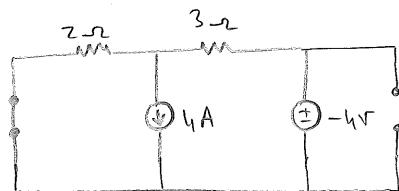ExampleFind all branch voltages & currents at $t=0^-$, $t=0^+$, $t=\infty$.Sol'n $t=0^-$ solve the following circuit

$t \leq t < 0^+$ To determine whether there will be a jump (discontinuity) at the capacitor voltage or inductor current at $t=0$ we need to figure out the impulsive component of the capacitor current and the inductor voltage during $t \leq t < 0^+$.

How to compute impulsive components? Assuming the capacitor voltage and inductor current cannot be unbounded, replace the capacitor with any bounded voltage source (e.g. short circuit) and the inductor with any bounded current source (e.g. open circuit) provided that KCL and KVL are not violated.

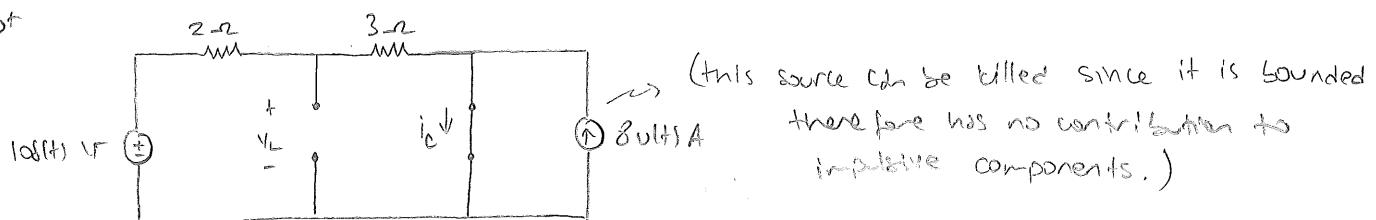 $0^- \leq t < 0^+$ 

$$i_C(t) = \frac{10\delta(t)}{5} + 2v(t) = 2\delta(t) + 8v(t) A$$

$$v_L(t) = v_{3\Omega}(t) = \frac{3}{3+2} \cdot 10\delta(t) V = 6\delta(t) V$$


Now we can compute $v_C(0^+)$ and $i_L(0^+)$

$$v_C(0^+) = v_C(0^-) + \frac{1}{C} \int_{0^-}^{0^+} i_C(t) dt = -4 + \frac{1}{2} \int_{0^-}^{0^+} (2\delta(t) + 8v(t)) dt = \boxed{-3V}$$

this term has no effect since bounded

$$i_L(0^+) = i_L(0^-) + \frac{1}{L} \int_{0^-}^{0^+} v_L(t) dt = 4 + \frac{1}{3} \int_{0^-}^{0^+} 6\delta(t) dt = \boxed{6A}$$

$t=0^+$ Solve the following circuit

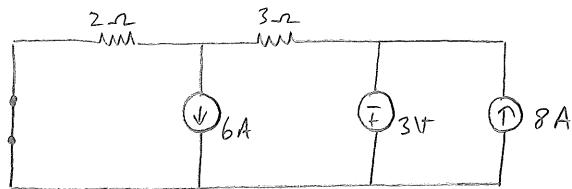

$t=\infty$ The only remaining source in the circuit for $t \rightarrow \infty$ is $\uparrow 8A$ DC current source. "Assuming" the circuit reaches the DC steady state as $t \rightarrow \infty$ we can proceed as follows.


$\uparrow 8A$ DC current

every voltage and current becomes constant


$$i_c(\infty) = C \frac{d v_c(t)}{dt} \Big|_{t=\infty} = 0 \quad \text{Hence the capacitor behaves as open circuit at DC steady state.}$$

$$v_L(\infty) = L \frac{d i_L(t)}{dt} \Big|_{t=\infty} = 0 \quad \text{Hence the inductor behaves as short circuit at DC steady state.}$$

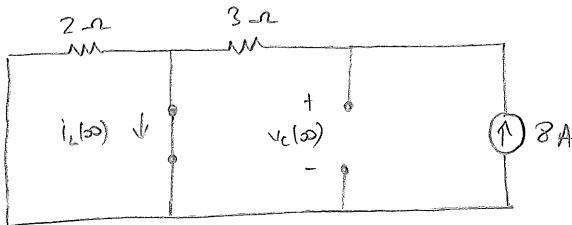Solve the following circuit for $t=\infty$ values.




Example Compute $i_c(t)$.

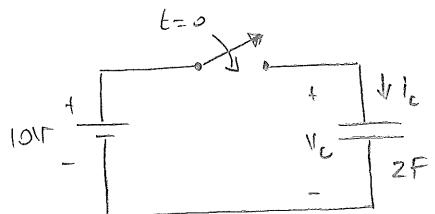

Sol'n

Note that

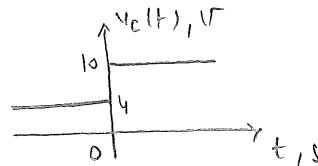


That is, $v_c(t) = 4 + 6v(t) \text{ V}$

$$v_c(0^+) = 6V$$

$$\text{Hence } i_c(t) = C \frac{d}{dt} v_c(t)$$

$$= 2 \frac{d}{dt} [4 + 6v(t)] = \boxed{12\delta(t) \text{ A}}$$

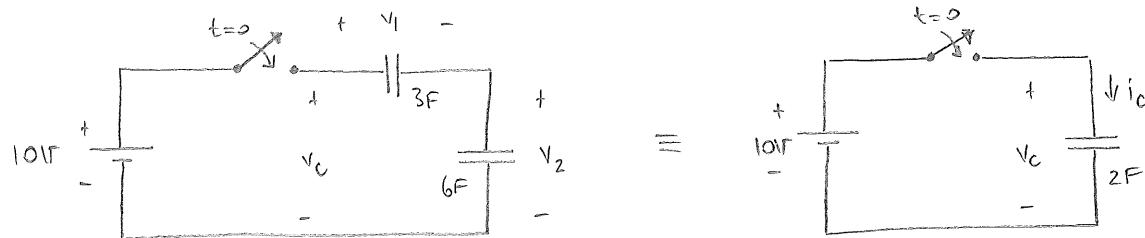Example

$$v_1(0^-) = 3V, \quad v_2(0^-) = 1V$$


$$v_2(t) = ? \quad \text{for } t > 0$$

$$v_c(0^-) = 3 + 1 = 4V$$

$$\Rightarrow i_c(t) = 12\delta(t) A$$

Hence, $v_2(t) = v_2(0^-) + \frac{1}{6} \int_{0^-}^t i_c(\tau) d\tau$

$$= 1 + \frac{1}{6} \int_{0^-}^t 12\delta(\tau) d\tau = \boxed{3V} \quad (\text{for } t > 0)$$

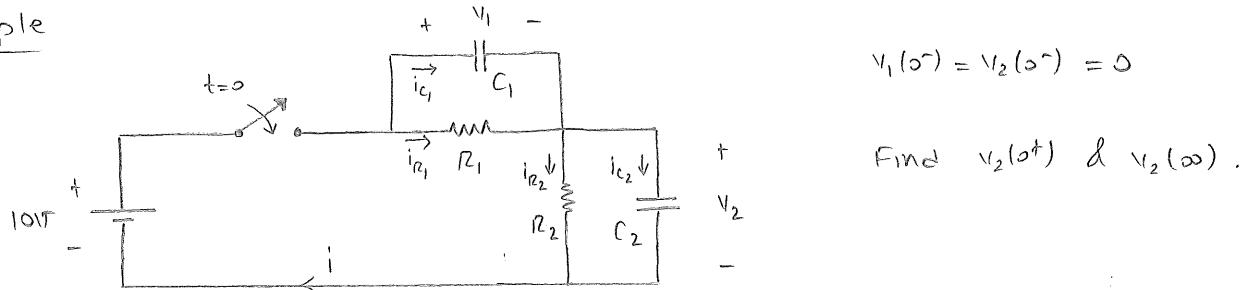Example

$$v_1(0^-) = v_2(0^-) = 0$$

Find $v_2(0^+)$ & $v_2(\infty)$.

$t=0^+$

$$v_1(0^+) = \frac{1}{C_1} \int_{0^-}^{0^+} i_{C1} dt = \frac{1}{C_1} \int_{0^-}^{0^+} (i - i_{R1}) dt = \frac{1}{C_1} \int_{0^-}^{0^+} idt - \frac{1}{C_1} \int_{0^-}^{0^+} \frac{V_1}{R_1} dt$$

○ (why?)

likewise, $v_2(0^+) = \frac{1}{C_2} \int_{0^-}^{0^+} idt$

Hence $C_1 v_1(0^+) = C_2 v_2(0^+)$


Also, $v_1(0^+) + v_2(0^+) = 10$

$\left. \begin{array}{l} \\ \\ \end{array} \right\} v_2(0^+) = \boxed{\frac{C_1}{C_1 + C_2} 10V}$

$t=\infty$ (DC steady state, capacitors become open circuit)

$$v_2(\infty) = \boxed{\frac{R_2}{R_1 + R_2} 10V}$$

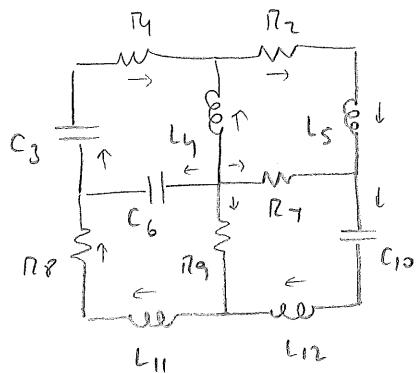Example Show that all branch currents / voltages remain bounded for $t \geq 0$.



$$v_3(0) = 3V, v_6(0) = 6V, v_{10}(0) = 10V$$

$$i_4(0) = 4A, i_5(0) = 5A, i_6(0) = 11A, i_{11}(0) = 12A$$

$$R_2 = l \Omega, C_1 = l F, L_1 = l H, l = 1, 2, \dots, 12$$

Question: How to solve this circuit?

Answer: Trick is not to.

Sol'n Total stored energy at time t , $E(t) = ?$

$$E(t) = E_C(t) + E_L(t) = \sum_{k \in \text{Cap.}} \frac{1}{2} C_k v_k(t)^2 + \sum_{k \in \text{Ind.}} \frac{1}{2} L_k i_k(t)^2 \quad (1)$$

$$\dot{E}(t) = ?$$


$$\dot{E} = \sum_{k \in \text{Cap.}} \frac{C_k v_k \dot{v}_k}{i_k} + \sum_{k \in \text{Ind.}} \frac{L_k i_k \dot{i}_k}{v_k} = \sum_{k \in \text{Cap., Ind.}} i_k v_k \quad (2)$$

$$\text{Tellegen's Thm} \Rightarrow 0 = \sum_{k \in \text{Cap.}} i_k v_k = \sum_{k \in \text{Cap., Ind.}} i_k v_k + \sum_{k \in \text{Res.}} i_k v_k \quad (3)$$

$$(2) \& (3) \Rightarrow \dot{E} = - \sum_{k \in \text{Res.}} i_k v_k = - \sum_{k \in \text{Res.}} R_k i_k^2 \leq 0 \quad (4)$$

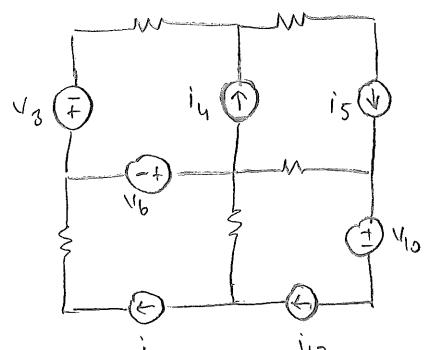(1) & (4) $\Rightarrow E(t)$ bounded for all $t \Rightarrow$ All cap. volt. & ind. curr. bounded for all t .

Substitution form. \Rightarrow Replace cap. & ind. with ZVS & ICS respectively



In circuit N all currents and voltages are bounded because


banded input \Rightarrow banded output (linearity)

LTZ res.
circuit

Ch. VII

First Order Circuits

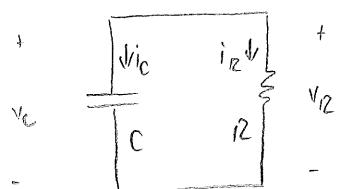zero input response Response of a circuit to initial conditions only - (No input.)



$$v_c(t) = ? \quad \text{for } t \geq 0$$

$$i_c = C \frac{dv_c}{dt}$$

(Notation: $Df := \frac{df}{dt}$)

$$v_c(0) = V_0$$

$$\begin{aligned} &= \frac{1}{C} v_c = \frac{1}{C} i_R \\ &= -\frac{1}{C} i_R \quad \left. \begin{array}{l} \text{KCL} \\ \text{terminal eqn.} \end{array} \right. \\ &= -\frac{1}{C} \frac{V_R}{R} \\ &= -\frac{1}{RC} v_c \quad \left. \begin{array}{l} \text{KVL} \end{array} \right. \end{aligned}$$

$$\Rightarrow DV_c + \frac{1}{RC} v_c = 0 \quad (1)$$

Eqn. (1) is a first-order homogeneous [i.e. right-hand side zero] differential equation. (The right-hand side is zero because we have no input.) Solution to (1) is of the form $v_c(t) = Ke^{st}$ where K & s are to be determined.


$$\frac{d}{dt} (Ke^{st}) + \frac{1}{RC} (Ke^{st}) = 0 \Rightarrow sKe^{st} + \frac{1}{RC} Ke^{st} = 0$$

$$\Rightarrow \left[s + \frac{1}{RC} \right] Ke^{st} = 0 \Rightarrow s = -\frac{1}{RC} : \text{"natural frequency"}$$

Then $v_c(t) = Ke^{-t/RC}$ for $t \geq 0$. How about K ?

$$\text{Initial cond. constraint: } V_0 = v_c(0) = Ke^{-t/RC} \Big|_{t=0} = K \Rightarrow K = V_0$$

Hence $v_c(t) = V_0 e^{-t/RC}$

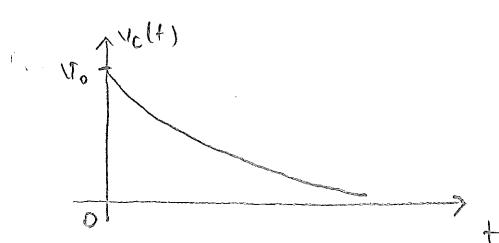


Remark $\tau = RC$ is sometimes called the "time constant". Note that the smaller the time constant the faster the response.

How about $i_C(t)$, $i_R(t)$?

$$\left. \begin{aligned} i_C(t) &= C \frac{d}{dt} v_C(t) = C \frac{d}{dt} \left\{ V_0 e^{-t/RC} \right\} = -\frac{V_0}{RC} e^{-t/RC} \\ i_R(t) &= \frac{v_R(t)}{R} = \frac{v_C(t)}{R} = \frac{V_0}{R} e^{-t/RC} \end{aligned} \right\} \text{Note that } i_C(t) + i_R(t) = 0 \quad (\text{KCL})$$

as expected.

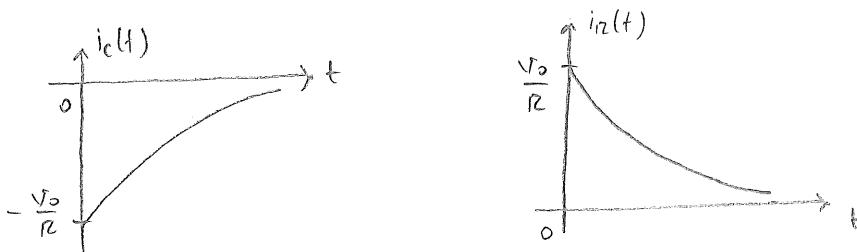

Example $i_L(t) = ?$ for $t \geq 0$

$$\begin{array}{c} + \\ \text{v}_L \\ - \end{array} \quad \begin{array}{c} \downarrow i_L \\ \text{v}_L \\ \uparrow i_R \\ \text{v}_R \\ \text{R} \end{array} \quad \begin{array}{c} + \\ \text{v}_R \\ - \end{array}$$

$$Di_L = \frac{1}{L} v_L = \frac{1}{L} v_R = \frac{1}{L} R i_R = -\frac{R}{L} i_L$$

$$\Rightarrow Di_L + \frac{R}{L} i_L = 0$$

$$i_L(0) = I_0 \quad \text{Natural freq. } s = -\frac{R}{L} \Rightarrow i_L(t) = I_0 e^{-\frac{R}{L} t}, \quad I_0 = ?$$


Init. cond. constraint : $i_L(0) = I_0 \Rightarrow I_0 = ?$

$$\Rightarrow i_L(t) = I_0 e^{-\frac{R}{L} t} \quad [\text{Sometimes we write } i_L(t) = I_0 e^{-t/\tau} \text{ where } \tau = \frac{L}{R} \text{ is the time constant.}]$$

— o —

zero-state response Response of a circuit with zero init. cond. to an input.

Example [constant input]

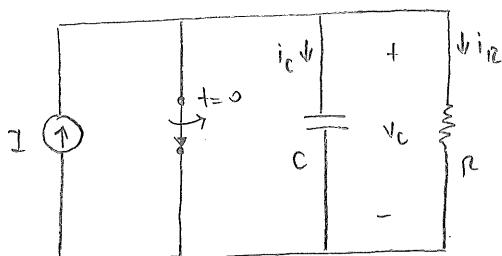

Note that $v_C(0-) = 0$

"zero initial condition"

For $t > 0$ we can write

$$\left. \begin{aligned} Di_C &= \frac{1}{C} i_C \\ &= \frac{1}{C} (I - i_R) \\ &= \frac{1}{C} \left(I - \frac{v_C}{R} \right) \end{aligned} \right\} Di_C + \frac{1}{RC} v_C = \frac{I}{C} \quad \begin{matrix} \nearrow \text{input term} \\ \searrow \text{homogeneous soln} \end{matrix}$$

solution is of the form: $v_C(t) = v_{nh}(t) + v_{sp}(t)$

$\begin{cases} \text{homogeneous soln} \\ \text{particular soln} \end{cases}$

to find $v_h(t)$ ignore the righthand side (i.e. consider the homogeneous diff. eqn.)

$$Dv_c + \frac{1}{RC} v_c = 0 \Rightarrow v_h(t) = Ke^{-t/RC}$$

hom. solution (K to be determined later)

$$\text{Natural freq.} = -\frac{1}{RC} \quad (\text{time constant} = RC)$$

to find $v_p(t)$: v_p has the same "form" as input [Ex input constant $\Rightarrow v_p$ constant]

Hence let $v_p(t) = A$ (constant)

Substitute $v_p(t)$ in the diff. eqn.

$$\frac{d}{dt} v_p(t) + \frac{1}{RC} v_p(t) = \frac{I}{C} \quad \left| \begin{array}{l} \\ v_p(t) = A \end{array} \right. \Rightarrow \frac{A}{RC} = \frac{I}{C} \Rightarrow A = IR$$


$$\Rightarrow v_p(t) = IR$$

Hence the overall solution : $v_c(t) = v_h(t) + v_p(t) = Ke^{-t/RC} + IR$ (K yet unknown)

To find K , use the initial cond. constraint :

$$Ke^{-t=0/RC} + IR \quad \left|_{t=0} \right. = 0 \Rightarrow K = -IR$$

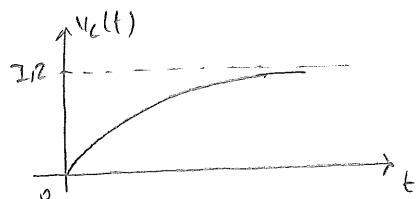Finally, $v_c(t) = \boxed{IR(1 - e^{-t/RC})}$



Remark Note that in our example $\lim_{t \rightarrow \infty} v_h(t) = 0$. This is due to that the natural freq. is negative. Such circuits (i.e. circuits whose natural frequencies have negative real parts) are called stable. Otherwise, they are called unstable.

Step response


The step response of a circuit is its zero-state response to a unit step excitation. That is, we set

i) initial conditions to zero


ii) input = $v(t)$

y

[$i_s(t)$ or $v_s(t)$]

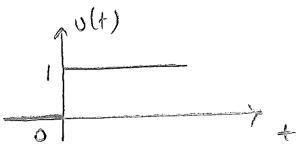

Example Find the step response $v_R(t)$

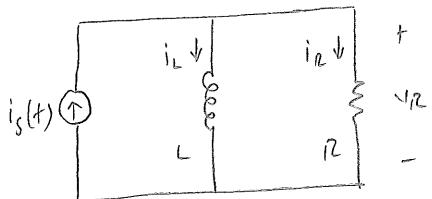

Sol'n

Diff eqn.?

$$Di_L = \frac{1}{L} v_L$$

$$= \frac{1}{L} R i_R$$

$$= \frac{R}{L} (i_s - i_L)$$


$$\left. \begin{aligned} Di_L + \frac{R}{L} i_L &= \frac{R}{L} i_s \\ (i_s(t) = v(t)) \end{aligned} \right\}$$

$$\left. \begin{aligned} \text{Hence for } t > 0 : Di_L + \frac{R}{L} i_L &= \frac{R}{L} i_s \\ i_L(0) &= 0 \end{aligned} \right\} \quad \begin{aligned} \text{Homogeneous sol'n} \quad i_h(t) &= Ke^{-\frac{R}{L}t} \\ \text{part. sol'n} \quad i_p(t) &= A \Rightarrow \frac{R}{L} A = \frac{R}{L} \Rightarrow A = 1 \end{aligned}$$

$$\Rightarrow i_L(t) = i_h(t) + i_p(t) = 1 + Ke^{-\frac{R}{L}t}$$

$$\text{init. cond. constraint: } 1 + Ke^{-\frac{R}{L}t} \Big|_{t=0} = 0 \Rightarrow K = -1$$

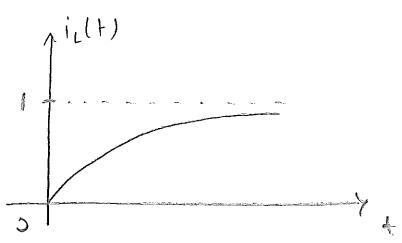
$$\Rightarrow i_L(t) = 1 - e^{-\frac{R}{L}t} \quad (t > 0)$$



$$v_R(t) = ? \quad v_R(t) = R i_R(t) = R (i_s(t) - i_L(t))$$


$$= R [1 - (1 - e^{-\frac{R}{L}t})]$$

$$= Re^{-\frac{R}{L}t} \quad (t > 0)$$

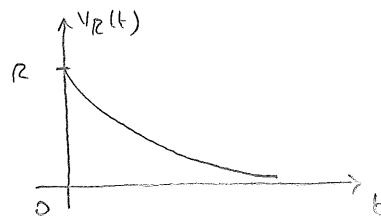

$$\text{or, } v_R(t) = v_L(t) = L Di_L(t)$$

Example [Sinusoidal input]

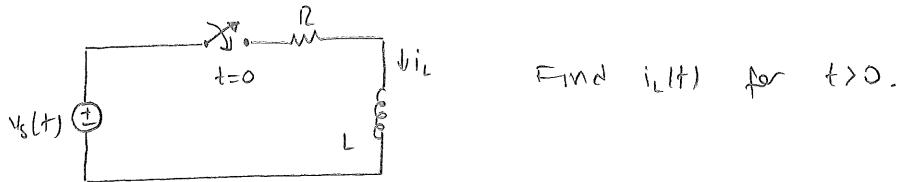

Find $i_L(t)$ for $t > 0$.

$$\text{Sol'n} \quad L \frac{di_L}{dt} = v_L = v_s - Ri_L \Rightarrow \frac{di_L}{dt} + \frac{R}{L} i_L = \frac{1}{L} v_s$$

$$\text{Hence} \quad \frac{di_L}{dt} + \frac{R}{L} i_L = \frac{V_0}{L} \cos(\omega t + \phi) \quad [\text{Diff. Eqn.}] \quad \left(\text{Note: natural freq. } s = -\frac{R}{L} \right)$$

$i_L(0) = 0 \quad [\text{Init. cond.}]$

$$\text{Then hmp. sol'n : } i_h(t) = k e^{-\frac{R}{L}t}$$

part. sol'n : $i_p(t) = A \cos \omega t + B \sin \omega t$ (i.e. a sinusoidal function whose freq. ω same as that of the input.)

To be determined: A, B, k (use the diff. eqn. to find A, B ; use the initial cond. constraint to find k)

$$D i_p + \frac{R}{L} i_p = \frac{V_0}{L} \cos(\omega t + \phi) \quad (\cos(\alpha + \beta) = \cos \alpha \cos \beta - \sin \alpha \sin \beta)$$

$$\Rightarrow \frac{d}{dt} \{ A \cos \omega t + B \sin \omega t \} + \frac{R}{L} \{ A \cos \omega t + B \sin \omega t \} = \frac{V_0}{L} \{ \cos \phi \cos \omega t - \sin \phi \sin \omega t \}$$

$$\Rightarrow -A \omega \sin \omega t + B \omega \cos \omega t + \frac{A R}{L} \cos \omega t + \frac{B R}{L} \sin \omega t = \frac{V_0 \cos \phi}{L} \cos \omega t - \frac{V_0 \sin \phi}{L} \sin \omega t$$

$$\Rightarrow \left\{ B \omega + \frac{A R}{L} - \frac{V_0 \cos \phi}{L} \right\} \cos \omega t + \left\{ -A \omega + \frac{B R}{L} + \frac{V_0 \sin \phi}{L} \right\} \sin \omega t = 0$$

$$\underbrace{\qquad}_{=0}$$

$$\underbrace{\qquad}_{=0}$$

$$\Rightarrow \begin{bmatrix} \frac{R}{L} & \omega \\ -\omega & \frac{R}{L} \end{bmatrix} \begin{bmatrix} A \\ B \end{bmatrix} = \begin{bmatrix} \frac{V_0 \cos \phi}{L} \\ -\frac{V_0 \sin \phi}{L} \end{bmatrix} \Rightarrow \begin{bmatrix} A \\ B \end{bmatrix} = \frac{V_0/L}{\frac{R^2}{L^2} + \omega^2} \begin{bmatrix} \frac{R}{L} & -\omega \\ \omega & \frac{R}{L} \end{bmatrix} \begin{bmatrix} \cos \phi \\ -\sin \phi \end{bmatrix}$$

$$\Rightarrow i_L(t) = i_{hL}(t) + i_{pL}(t) = k e^{-\frac{R}{L}t} + A \cos \omega t + B \sin \omega t$$

$$i_C(0) = 0 \Rightarrow k = -A$$


Hence $i_L(t) = -A e^{-\frac{R}{L}t} + A \cos \omega t + B \sin \omega t \quad (t > 0)$

Let $R = 3\Omega$, $L = 2H$, $\omega = 2\text{rad/sec}$, $\phi = 0^\circ$, $V_0 = 10V$

$$\Rightarrow A = \frac{6}{5} \text{ and } B = \frac{8}{5} \Rightarrow i_L(t) = -\frac{6}{5} e^{-\frac{3}{2}t} + \frac{6}{5} \cos 2t + \frac{8}{5} \sin 2t \text{ Amps}$$

transient part (sinusoidal) steady state part

Superposition in linear dynamic circuits

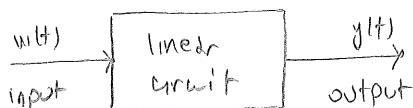

Note that

$$y(t) = y(t, x, w(\cdot))$$

y

initial condition
(vector)
input signal
(vector)

Init. cond. $x = [v_{C_1}(0^-) \dots v_{C_m}(0^-), i_{L_1}(0^-) \dots i_{L_n}(0^-)]^T$

input $w(t) = [v_{S_1}(t) \dots v_{S_p}(t), i_{S_1}(t) \dots i_{S_q}(t)]^T$


We have =

$$1) y(t, \alpha_1 x_1 + \alpha_2 x_2, \omega) = \alpha_1 y(t, x_1, \omega) + \alpha_2 y(t, x_2, \omega) \quad \text{superposition w.r.t. init. cond.}$$

$$2) y(t, 0, \beta_1 w_1 + \beta_2 w_2) = \beta_1 y(t, 0, w_1) + \beta_2 y(t, 0, w_2) \quad \text{superposition w.r.t. inputs}$$

$$3) y(t, \alpha x, \beta w) = \alpha y(t, x, \omega) + \beta y(t, 0, w) \quad \text{superposition w.r.t. init. cond. \& input}$$


Exercise Find the zero-state response

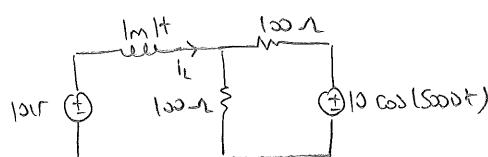

Step 1 Use AC input to find i_{L_1}



Step 2 Use DC mat to find i_{L_2}

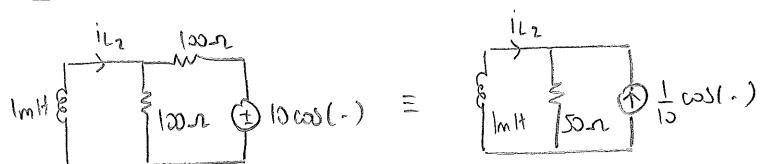


$$i_{L_2}(0) = 0$$

Step 3 Superpose


$$i_L(t) = i_{L_1}(t) + i_{L_2}(t)$$

Complete response [nonzero input + nonzero init. cond.]

Example

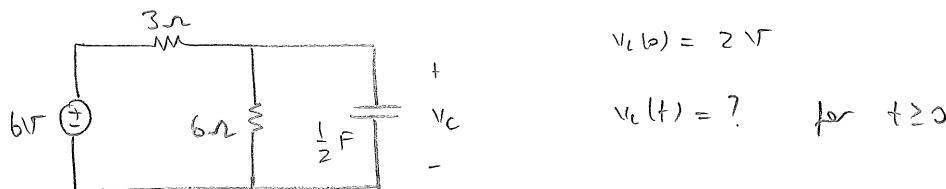

Sol'n

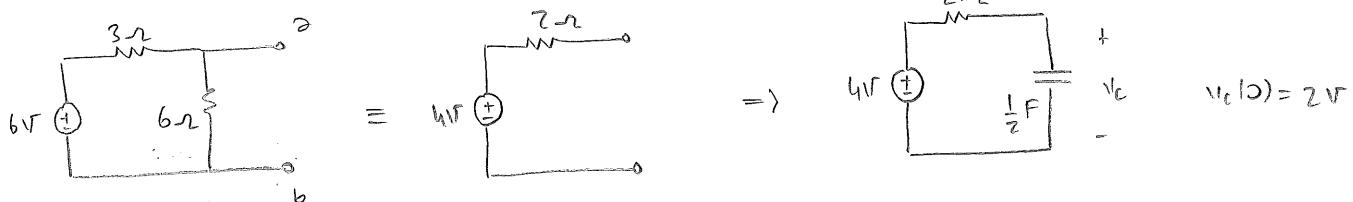

$$\text{KVL: } 0 = -4 + 2i_c + v_c = -4 + 2\left[\frac{1}{2}v_c\right] + v_c \Rightarrow 0v_c + v_c = 4 \quad (\text{diff. eqn.})$$

$$\begin{aligned} \text{Imp. sol'n: } v_c(t) &= 4e^{-t} \\ \text{prt. sol'n: } v_p(t) &= 4 \end{aligned} \quad \left. \begin{aligned} v_c(t) &= 4 + 4e^{-t} \\ v_c(0) &= 2 \text{ V} \end{aligned} \right\} \quad v_c(t) = 4 - 2e^{-t} \text{ V}$$

Another approach (superposition)

Step 1 Find zero-state resp. $v_{2S}(t)$

$$0v_c + v_c = 4 \quad \text{with } v_c(0) = 0 \Rightarrow v_{2S}(t) = 4 - 4e^{-t} \text{ V}$$

Step 2 Find zero-input resp. $v_{2i}(t)$

$$0v_c + v_c = 0 \quad \text{with } v_c(0) = 2 \text{ V} \Rightarrow v_{2i}(t) = 2e^{-t} \text{ V}$$

Step 3 Superpose

$$v_c(t) = v_{2S}(t) + v_{2i}(t)$$

$$= 4 - 2e^{-t} \text{ V}$$

(as expected)

Yet another approach

What do we know?


→ form of diff. eqn. $0v_c + \frac{1}{C}v_c = \text{constant}$

→ form of sol'n $v_c(t) = A + Be^{-t/C}$ (1)

How to find A, B, C ?

$$\begin{aligned} (1) \Rightarrow v_c(\infty) &= A \\ (2) \Rightarrow v_c(\infty) &= V_{oc} \end{aligned} \quad \left. \begin{aligned} A &= V_{oc} \\ (2) \Rightarrow C &= R \ln C \end{aligned} \right.$$


$$(2) \Rightarrow C = R \ln C$$


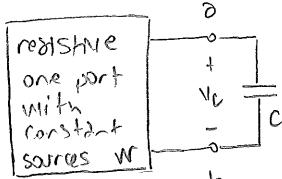


$$v_c(0) = V_{oc}$$

$$\text{Let } N \equiv \begin{array}{c} \text{resistive} \\ \text{one port} \\ \text{with} \\ \text{constant} \\ \text{sources } N \end{array} \quad (2)$$

Exercise Work out the dual case

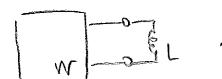


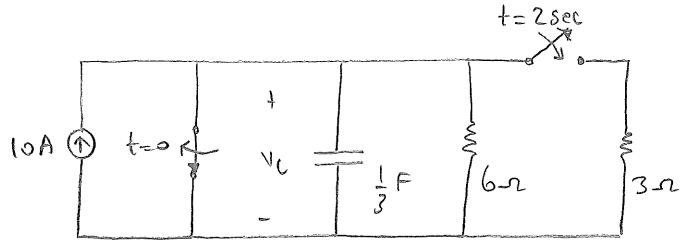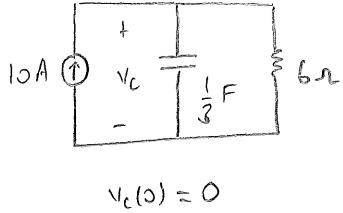ExampleFind $V_c(t)$ for $t \geq 0$.Sol'n $0 \leq t < 2$ 

$$V_{LL} \Rightarrow \frac{1}{3} 10 V_C + \frac{V_C}{6} = 10 \Rightarrow 10 V_C + \frac{1}{2} V_C = 30$$

$$\left. \begin{aligned} V_{in}(t) &= 10e^{-t/2} \\ V_p(t) &= 60 \end{aligned} \right\} \left. \begin{aligned} V_C(t) &= 60 + V_C e^{-t/2} \\ &= 60 - 60e^{-t/2} \end{aligned} \right\} V_C(0) = 0$$

$$\text{at } t = 2^- \quad V_C(2) = 60 \left(1 - \frac{1}{e}\right) =: V_2 \approx 38 \text{ V}$$

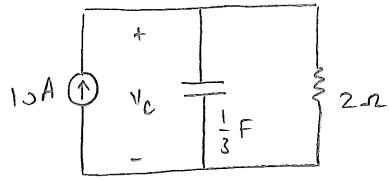 $t \geq 2$ 

$$10 V_C + \frac{3}{2} V_C = 30$$


$$\left. \begin{aligned} V_{in}(t) &= K e^{-\frac{3}{2}(t-2)} \\ V_p(t) &= 20 \text{ V} \end{aligned} \right\} \left. \begin{aligned} V_C(t) &= 20 + V_C e^{-\frac{3}{2}(t-2)} \\ &= 20 + [V_2 - 20] e^{-\frac{3}{2}(t-2)} \end{aligned} \right\} V_C(2) = V_2$$

$$V_C(2) = V_2$$

$$\text{or, } \left. \begin{aligned} V_{in}(t) &= K e^{-\frac{3}{2}t} \\ V_p(t) &= 20 \text{ V} \end{aligned} \right\} \left. \begin{aligned} V_C(t) &= 20 + V_C e^{-\frac{3}{2}t} \\ &= 20 + t(V_2 - 20)e^{\frac{3}{2}t} \end{aligned} \right\} V_C(2) = V_2$$



Hence
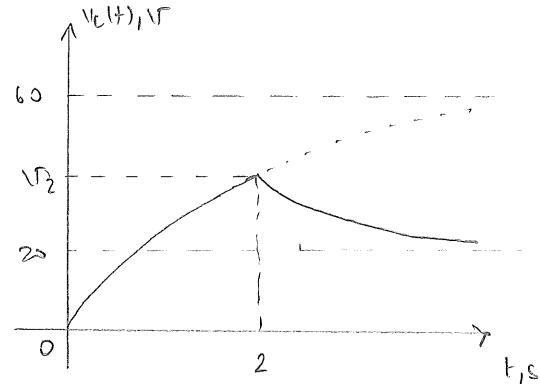
$$V_C(t) = \left\{ \begin{array}{ll} 60[1 - e^{-t/2}] \text{ V} & \text{for } 0 \leq t < 2 \\ 20 + [V_2 - 20] e^{-\frac{3}{2}(t-2)} & \text{for } t \geq 2 \end{array} \right.$$




Example [Ramp excitation]

Find $i_L(t)$.

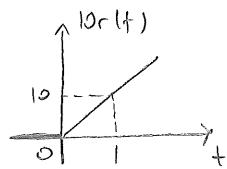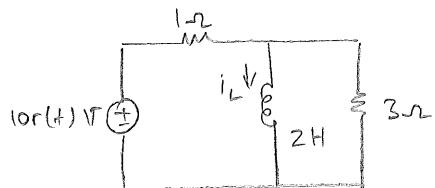

$$i_L(0) = 0$$

Sol'n Equivalent circuit:

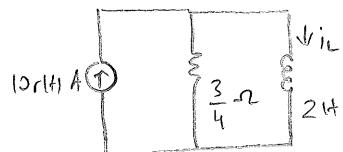

$$\text{KCL: } i_L + \frac{20i_L}{3/4} = 10r(t) \quad \stackrel{(t>0)}{\Rightarrow} \quad Di_L + \frac{3}{8}i_L = \frac{15}{4}t \quad (1)$$

$$\Rightarrow i_h(t) = V e^{-\frac{3}{8}t} \quad \& \quad i_p(t) = A + \beta t$$


$$i_p(t) = ? \quad i_p \text{ should solve (1). Hence}$$

$$\frac{d}{dt} \{ (A + \beta t) \} + \frac{3}{8} \{ A + \beta t \} = \frac{15}{4}t \quad \Rightarrow \quad \underbrace{[3 + \frac{3}{8}A]}_0 + \frac{3\beta}{8}t = \frac{15}{4}t$$

$$\Rightarrow \beta = 10 \quad \& \quad A = -\frac{80}{3} \quad \Rightarrow \quad i_p(t) = -\frac{80}{3}t + 10t \text{ Amps}$$


$$\Rightarrow i_L(t) = -\frac{80}{3}t + 10t + V e^{-\frac{3}{8}t} \quad \left. \begin{array}{l} \\ \\ \end{array} \right\} \quad i_L(t) = -\frac{80}{3}t + 10t + \frac{80}{3} e^{-\frac{3}{8}t} \text{ Amps}$$
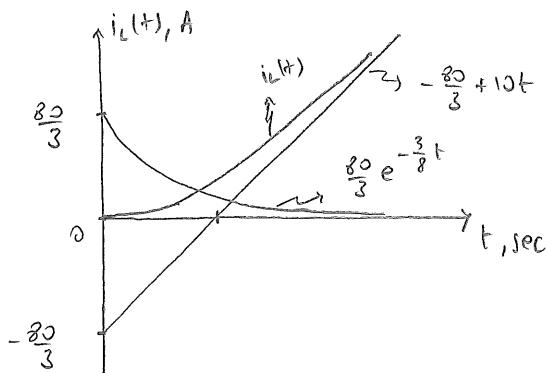
$$i_L(0) = 0 \Rightarrow V = \frac{80}{3}$$



$i_L(t)$ remains positive because $i_L(0) \Rightarrow d$



$$Di_L = 10 - 10e^{-\frac{3}{8}t} > 0 \quad \text{for } t > 0$$

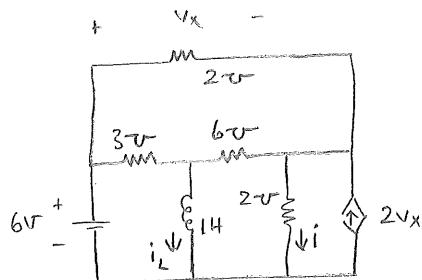Example

$$i_L(0) = 6A, \quad i(t) = ? \text{ for } t > 0$$

Step 1 Find the norton / thenevin equiv.

current seen by the inductor

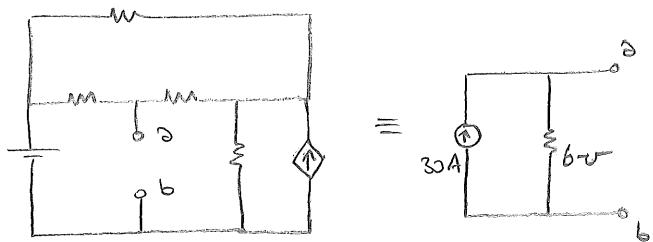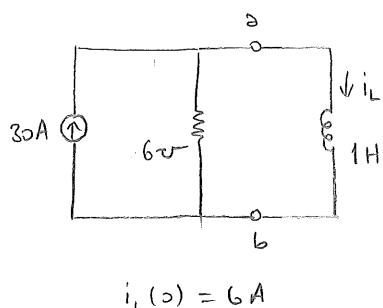
Step 2 Using the equiv. circuit find $i_L(t)$ 

$$VCL : -30 + i_L + 6LDi_L = 0$$




$$\Rightarrow Di_L + \frac{1}{6}i_L = 5 \Rightarrow i_L(t) = 30 + ke^{-t/6}$$

$$i_L(0) = 6 \Rightarrow k = -24 \Rightarrow i_L(t) = 30 - 24e^{-t/6} A$$


$$\Rightarrow v_L(t) = 4e^{-t/6} V$$

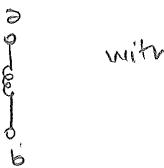Step 3 Substitute


with

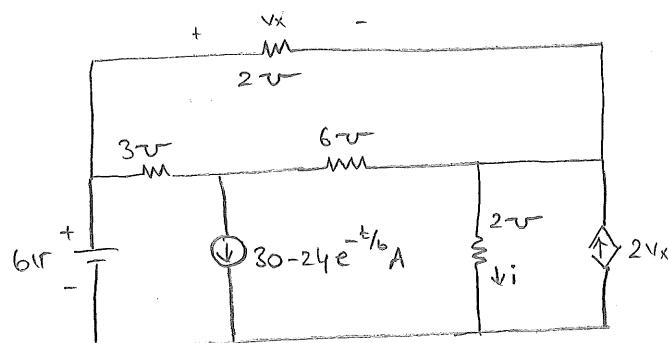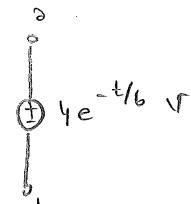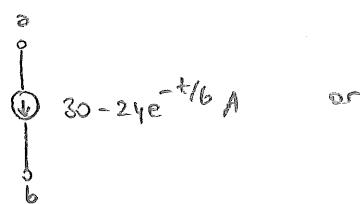Solve for i

$$\text{Answer: } i(t) = 4 + 4e^{-t/6} A \text{ for } t > 0$$

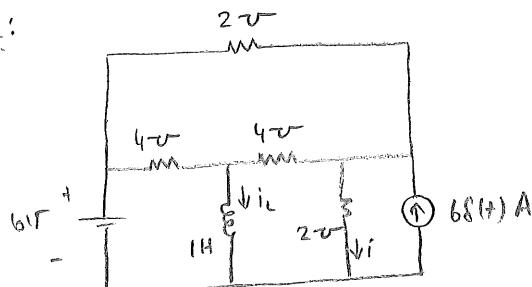Exercise:

$$i_L(0) = 6A, \quad i(t) = ? \text{ for } t > 0$$

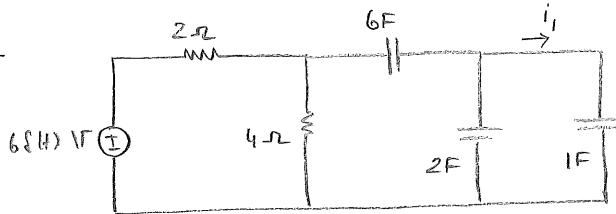Example

Capacitors initially uncharged.

Find $i_c(t)$ for $t > 0$.Sol'n

$$\begin{array}{c} + \xrightarrow{i_c} \\ \text{---} \\ v_c \\ - \end{array} \parallel \begin{array}{c} 6F \\ | \\ 2F \quad 1F \end{array} \equiv \begin{array}{c} + \xrightarrow{i_c} \\ \text{---} \\ v_c \\ - \end{array} \frac{1}{2F} = (2//1) \gg 6$$

$v_c(0^-) = 0$

 $0^- < t < 0^+$

$$\begin{array}{c} 2\Omega \\ | \\ 6\delta(t) \\ | \\ 4\Omega \end{array} \quad i_c(t) = \frac{6\delta(t)}{2} = 3\delta(t) \text{ A}$$


$$\Rightarrow v_c(0^+) = v_c(0^-) + \frac{1}{2} \int_{0^-}^{0^+} i_c(t) dt = \frac{1}{2} \int_{0^-}^{0^+} 3\delta(t) dt = \frac{3}{2} \text{ V}$$

 $t > 0$

$$2\delta(t) = \frac{4}{8} \Omega \parallel \begin{array}{c} + \\ v_c \\ - \end{array} \quad \begin{aligned} \text{---} \\ \downarrow i_c \\ \frac{3}{8} v_c = 0 \\ \Rightarrow v_c(t) = \frac{3}{2} e^{-\frac{3t}{8}} \text{ V} \\ \Rightarrow i_c(t) = 2\delta(t) = -\frac{9}{8} e^{-\frac{3t}{8}} \text{ A} \end{aligned}$$

$$v_c(0^+) = \frac{3}{2} \text{ V}$$



Return to the original configuration:

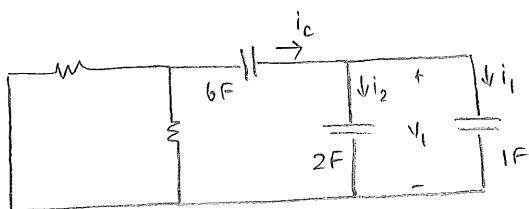

$$\left. \begin{array}{l} i_1 = 6i_1 \\ i_2 = 2i_1 \end{array} \right\} \Rightarrow i_2 = 2i_1$$

$$i_c = i_1 + i_2 = 3i_1 \Rightarrow i_1 = \frac{1}{3} i_c$$

$$\Rightarrow i_1(t) = -\frac{3}{8} e^{-\frac{3t}{8}} \text{ A} \quad \text{for } t > 0$$

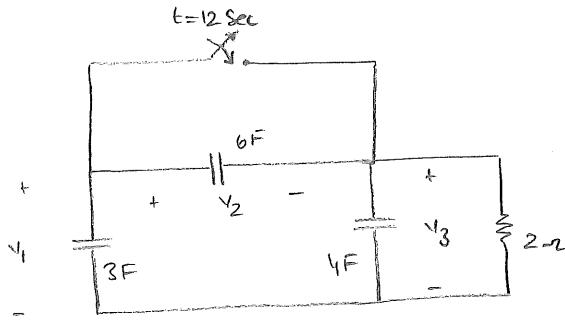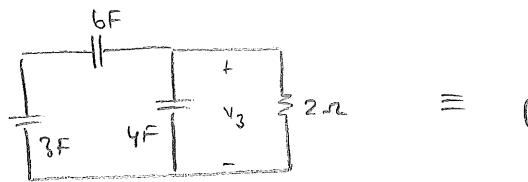Example $0 \leq t < 12$ 

$$\equiv (6 \gg 3) // 4 = 6F \quad \boxed{\begin{array}{c} + \\ v_3 \\ - \end{array}} \quad 2\Omega$$


$$v_3(0) = v_1(0) - v_2(0)$$

$$= 4V$$

$$\Rightarrow v_3(t) = v_3(0) e^{-t/2C}, \quad \boxed{v_3(t) = 4 e^{-t/12} V}$$

how about $v_1(t), v_2(t)$?

$$\left. \begin{aligned} v_1 - v_2 &= v_3 \\ v_1(t) &= v_1(0) + \frac{1}{3} \int_0^t i_1(\tau) d\tau \\ v_2(t) &= v_2(0) + \frac{1}{6} \int_0^t -i_1(\tau) d\tau \end{aligned} \right\} \quad \left. \begin{aligned} 3(v_1(t) - v_1(0)) &= 6(v_2(0) - v_2(t)) \\ &= 6(v_2(0) - v_1(t) + v_3(t)) \end{aligned} \right\} \quad \left. \begin{aligned} v_1(t) &= \frac{7}{3} + \frac{2}{3} v_3(t) \\ v_2(t) &= \frac{7}{3} - \frac{1}{3} v_3(t) \end{aligned} \right.$$

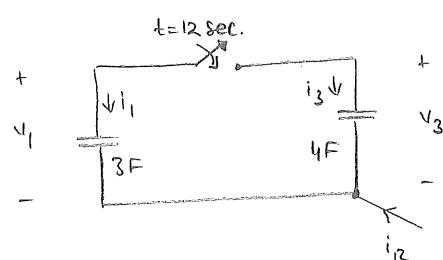 $12^- < t < 12^+$ 

$$v_1(12^-) = \frac{7}{3} + \frac{8}{3e} V$$

$$v_3(12^-) = \frac{4}{e} V$$


$v_1(12^-) \neq v_3(12^-)$ but $v_1(12^+) = v_3(12^+)$ \Rightarrow impulsive current

$$v_1(12^+) = v_1(12^-) + \frac{1}{3} \int_{12^-}^{12^+} i_1(t) dt$$

$$v_3(12^+) = v_3(12^-) + \frac{1}{4} \int_{12^-}^{12^+} (-i_1(t) - i_2(t)) dt = v_3(12^-) - \frac{1}{4} \int_{12^-}^{12^+} i_1(t) dt$$


$$\Rightarrow \int i_1 = 3(v_3(12^+) - v_1(12^-)) = 4(v_3(12^-) - v_3(12^+))$$



$$\Rightarrow v_3(12^+) = \frac{9v_1(12^-) + 4v_3(12^-)}{9+4} = \frac{1}{7} \left\{ 7 + \frac{8}{e} + \frac{16}{e} \right\} \approx 2.26V$$

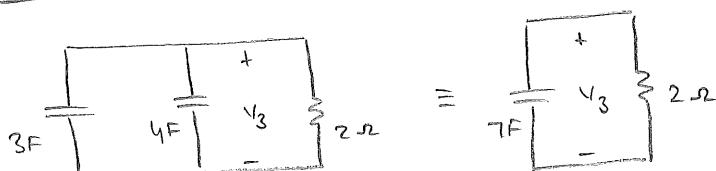 $t > 12$ 

$$v_3(12^+) = 2.26V$$


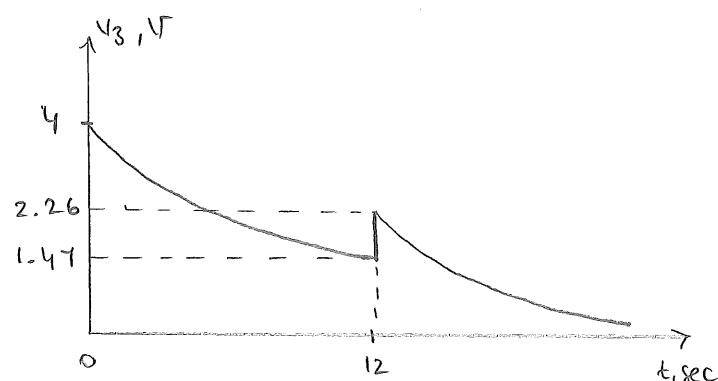
$$\Rightarrow v_3(t) = 2.26 e^{-t/12} V$$



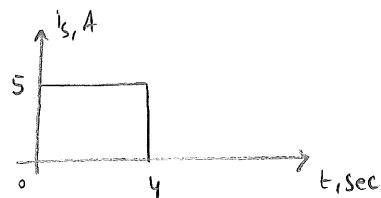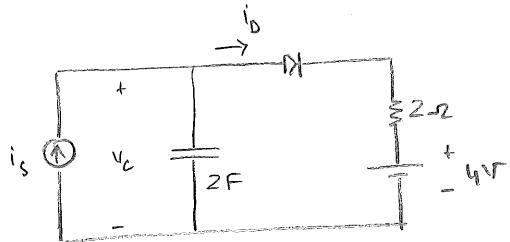Example

$$v_c(0) = -1V$$

$$v_c(t) = ?$$

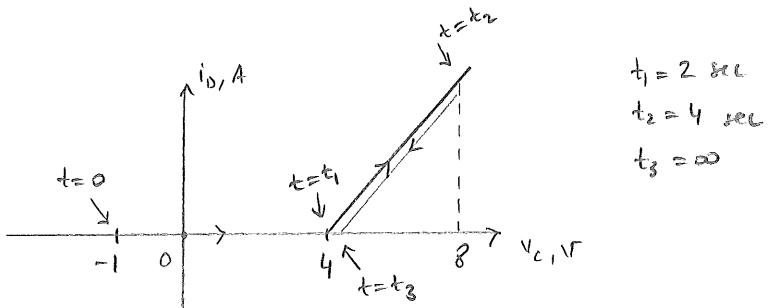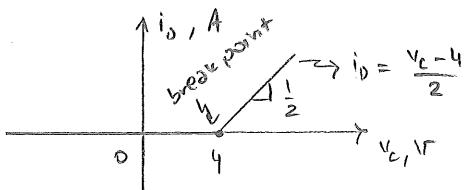Sol'n obtain i_D -v_c char.

$$0 \leq t < t_1 \quad i_D = 0 \Rightarrow i_c = i_s \Rightarrow 20v_c = 5 \Rightarrow v_c(t) = -1 + \frac{5}{2}t \text{ V}$$

$$t_1 = ? \quad t_1 = \min\{t_2, t_b\} \quad \text{where } t_2 = 4 \text{ sec} \quad \text{when } i_s(t) \text{ becomes zero}$$

$v_c(t_b) = 4 \text{ V}$
the break point
of the i_D -v_c curve

$$\Rightarrow -1 + \frac{5}{2}t_b = 4 \Rightarrow t_b = 2 \text{ sec} \Rightarrow t_1 = 2 \text{ sec} \Rightarrow v_c(t_1) = 4 \text{ V}$$

$$t_1 \leq t < t_2 \quad i_s = i_c + i_D \Rightarrow 5 = 20v_c + \frac{v_c + 4}{2} \Rightarrow 10v_c + \frac{1}{4}v_c = \frac{7}{2}$$

$$\Rightarrow v_c(t) = 14 - 10e^{-\frac{(t-2)}{4}} \text{ V}$$

$$t_2 = ? \quad t_2 = 4 \text{ sec} \quad (\text{when } i_s(t) \text{ becomes zero}) \Rightarrow v_c(t_2) = 14 - 10e^{-\frac{1}{2}} \approx 8 \text{ V}$$


$$t_2 \leq t < t_3 \quad i_s = 0 \Rightarrow i_c + i_D = 0 \Rightarrow 20v_c + \frac{v_c + 4}{2} = 0 \Rightarrow 10v_c + \frac{1}{4}v_c = 1$$

$$\Rightarrow v_c(t) = 4 + (v_c(4) - 4)e^{-\frac{1}{4}(t-4)} \text{ V}$$

$t_3 = ?$ Note that $v_c(t) > 4$ for $t > t_2$

\Rightarrow we never exactly reach the break point

$\Rightarrow t_3 = \infty$






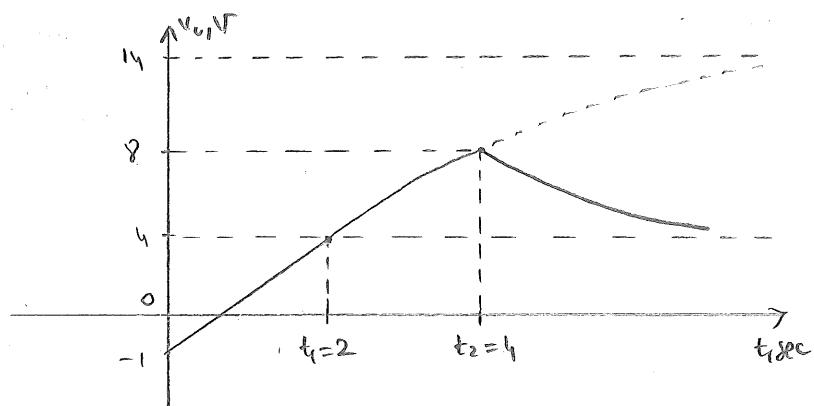


Time-invariance of the zero-state response


Let



Example [Time-invariance]

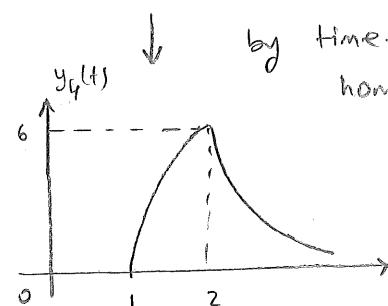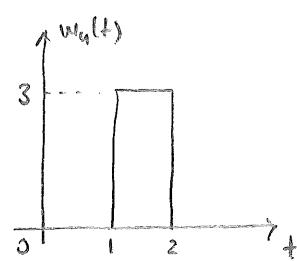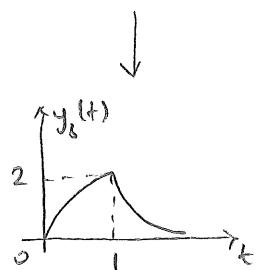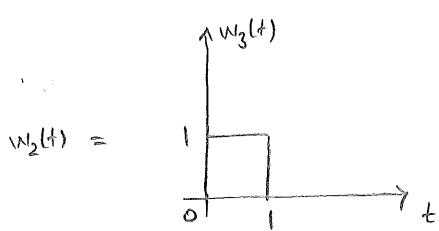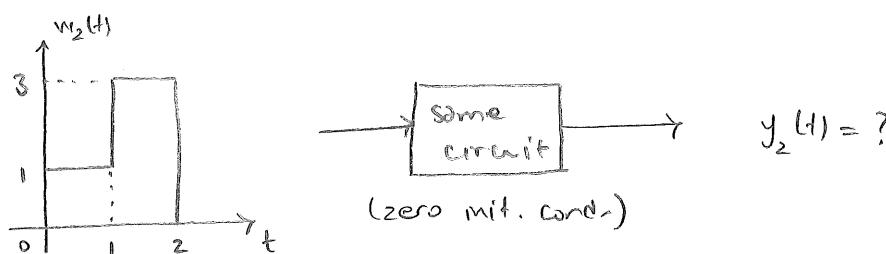
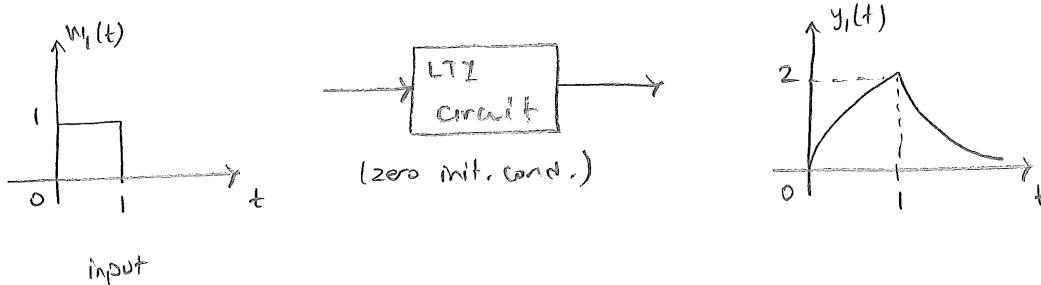

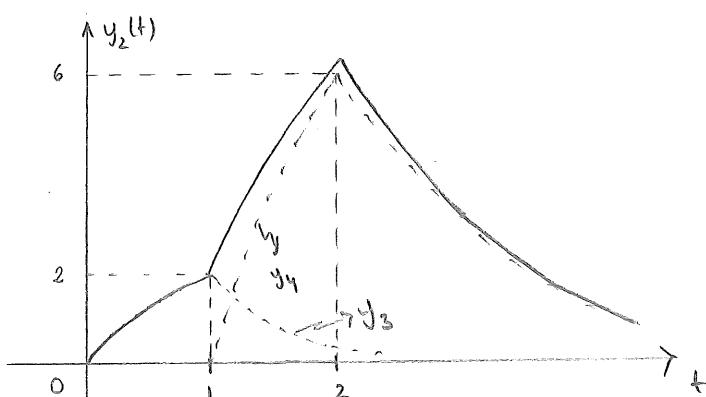
$$\text{By superposition : } y_2(t) = y_3(t) + y_4(t)$$



Pulse Response

Ex

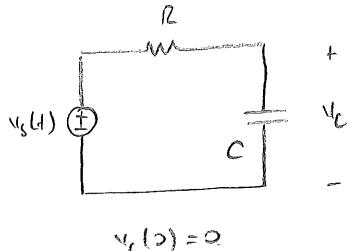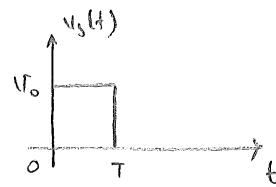Find $v_c(t)$ for


$$\text{Note that } v_s(t) = V_0 u(t) - V_0 u(t-T)$$

Since the initial condition is zero we can apply superposition:


$$\text{response due to } V_0 u(t) : v_1(t) = V_0 (1 - e^{-t/RC}) u(t)$$

$$\text{response due to } -V_0 u(t-T) : v_2(t) = -V_0 (1 - e^{-(t-T)/RC}) u(t-T)$$

$$v_c(t) = v_1(t) + v_2(t)$$

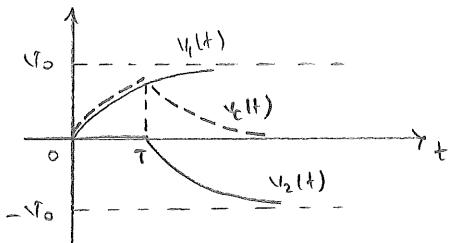

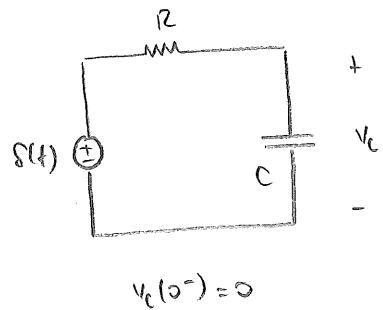Impulse response $\stackrel{\text{def}}{=} \text{zero state response for unit impulse } \delta(t) \text{ input.}$



Diff. eqn?

$$\delta(t) = R i_C + v_C = R C D v_C + v_C$$

$$\Rightarrow D v_C + \frac{1}{RC} v_C = \frac{1}{RC} \delta(t) \quad (1)$$

In this case [that is, init. cond. = 0 & input = $\delta(t)$] the solution $v_c(t)$ to diff. eqn. (1) is called the impulse response. Impulse response is usually denoted by $h(t)$.

Consider (1). Due to $\delta(t)$ function $v_c(0^+)$ may not equal $v_c(0^-) = 0$. Let $V_0 = v_c(0^+)$

Then, for $t > 0$, $v_c(t) = V_0 e^{-t/RC}$ } Hence we can write $v_c(t) = V_0 e^{-t/RC} u(t)$
 Also, for $t < 0$, $v_c(t) = 0$ }

Question : $V_0 = ?$

Answer : Place $v_c(t) = V_0 e^{-t/RC} u(t)$ into the diff. eqn. (1).

$$\Rightarrow \frac{d}{dt} \left\{ V_0 e^{-t/RC} u(t) \right\} + \frac{1}{RC} V_0 e^{-t/RC} u(t) = \frac{1}{RC} \delta(t)$$


$$\Rightarrow -\frac{V_0}{RC} e^{-t/RC} u(t) + \underbrace{V_0 e^{-t/RC} \delta(t)}_{= V_0 e^{-t/RC} |_{t=0} \cdot \delta(t)} + \frac{1}{RC} V_0 e^{-t/RC} u(t) = \frac{1}{RC} \delta(t)$$

$$= V_0 \delta(t) \quad (\text{sifting property})$$

$$\Rightarrow V_0 f(t) = \frac{1}{RC} \delta(t) \Rightarrow V_0 = \frac{1}{RC}$$


Therefore the impulse response is $h(t) = \frac{1}{RC} e^{-t/RC} u(t)$

Impulse Response by limit approach

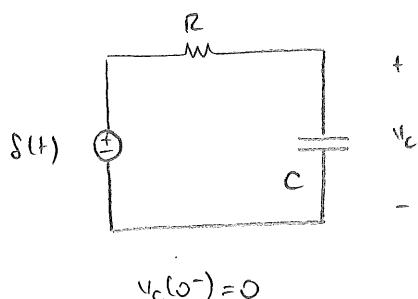

Approximate the unit impulse $\delta(t)$ by the pulse function:
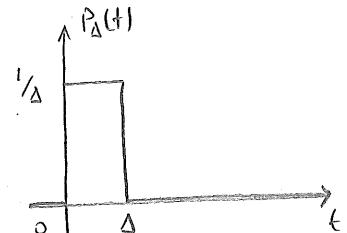
$$P_\Delta(t) = \frac{u(t) - u(t-\Delta)}{\Delta}$$



Let $h_\Delta(t)$ denote the response due to $P_\Delta(t)$



since $\delta(t) = \lim_{\Delta \rightarrow 0} P_\Delta(t)$, we should have $h(t) = \lim_{\Delta \rightarrow 0} h_\Delta(t)$

$h_\Delta(t) = ?$

$$h_\Delta(t) = \frac{1}{\Delta} (1 - e^{-t/RC}) u(t) - \frac{1}{\Delta} (1 - e^{-(t-\Delta)/RC}) u(t-\Delta)$$

clearly, $h_\Delta(t) = 0$ for $t < 0$. How about for $t > \Delta$?

$$\text{for } t > \Delta \quad h_\Delta(t) = \frac{1}{\Delta} (1 - e^{-t/\Delta}) - \frac{1}{\Delta} (1 - e^{\frac{\Delta}{RC}} e^{-t/RC})$$

$$= \frac{e^{\Delta/RC} - 1}{\Delta} \cdot e^{-t/RC}$$

$$\Rightarrow \lim_{\Delta \rightarrow 0} h_\Delta(t) = \underbrace{\left\{ \lim_{\Delta \rightarrow 0} \frac{e^{\Delta/RC} - 1}{\Delta} \right\}}_{?} e^{-t/RC} = \frac{1}{RC} e^{-t/RC}$$

$$e^{\Delta/RC} = 1 + \frac{\Delta}{RC} + \frac{1}{2} \left(\frac{\Delta}{RC} \right)^2 + \frac{1}{3!} \left(\frac{\Delta}{RC} \right)^3 + \dots$$


$$\frac{e^{\Delta/RC} - 1}{\Delta} = \frac{1}{RC} + \frac{1}{2} \frac{\Delta}{(RC)^2} + \frac{1}{3!} \frac{\Delta^2}{(RC)^3} + \dots$$

these vanish as $\Delta \rightarrow 0$

$$\text{Therefore } h(t) = \lim_{\Delta \rightarrow 0} h_\Delta(t) = \begin{cases} \frac{1}{RC} e^{-t/RC} & \text{for } t > 0 \\ 0 & \text{for } t < 0 \end{cases}$$

$$\Rightarrow h(t) = \frac{1}{RC} e^{-t/RC} v(t) \quad \text{as expected.}$$

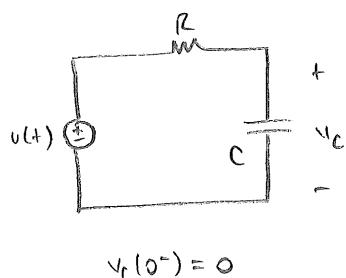Let's find the step response of the same circuit. [Let $s(t)$ denote the step response.]



$$\text{For } t > 0 \quad Dv_c + \frac{1}{RC} v_c = \frac{1}{RC} \Rightarrow v_c(t) = 1 - e^{-t/RC}$$

$$\text{For } t < 0 \quad v_c(t) = 0$$


$$\text{Hence } s(t) = (1 - e^{-t/RC}) v(t)$$

$$\text{Recall: } \delta(t) = Dv(t)$$

$$\text{Claim: } h(t) = Ds(t). \text{ Proof: } \frac{d}{dt} s(t) = \underbrace{\frac{1}{RC} e^{-t/RC} v(t)}_{h(t)} + \underbrace{(1 - e^{-t/RC}) \delta(t)}_{= (1 - e^{-t/RC}) \Big|_{t=0} \delta(t) = 0 \delta(t) = 0}.$$

□

This is true in general. Let

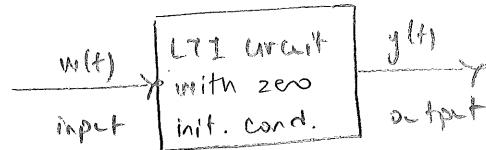

Then by time-invariance & homogeneity



Take the limit $\Delta \rightarrow 0$


$$\lim_{\Delta \rightarrow 0} \left\{ \frac{w(t) - w(t-\Delta)}{\Delta} \right\} \xrightarrow{N} \frac{y(t) - y(t-\Delta)}{\Delta} \right\} = \frac{dw(t)}{dt} \xrightarrow{N} \frac{dy(t)}{dt}$$

Exercise : For the previous circuit compute the ramp response and verify


$$\frac{d}{dt} \left\{ \begin{array}{l} \text{ramp} \\ \text{response} \end{array} \right\} = \left\{ \begin{array}{l} \text{Step} \\ \text{response} \end{array} \right\} .$$

[Ramp response $\stackrel{\text{def}}{=} \text{zero-state response to unit ramp } r(t) \text{ excitation.}]$

Example

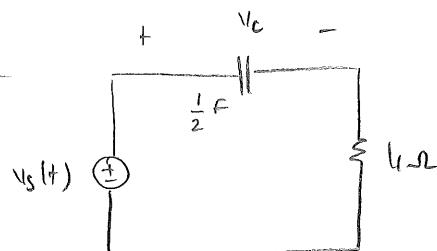

$$v_c(0) = 0$$

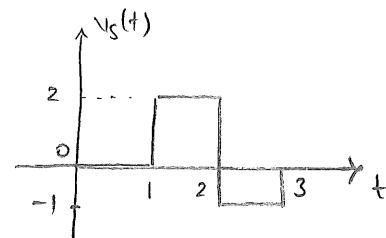


$$v_c(t) = ?$$


sol'n step response $s(t) = (1 - e^{-t/2}) v(t) \quad \forall$

input : $v_s(t) = 2v(t-1) - 3v(t-2) + v(t-3) \quad \forall$

Therefore : $v_c(t) = 2s(t-1) - 3s(t-2) + s(t-3) .$

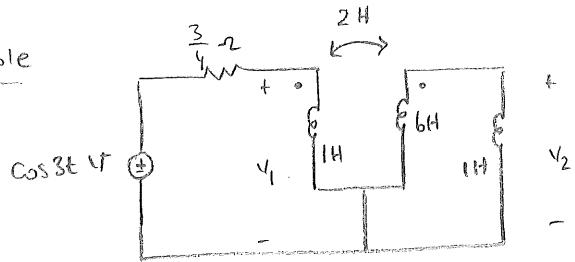Example

Assume zero init. conditions.

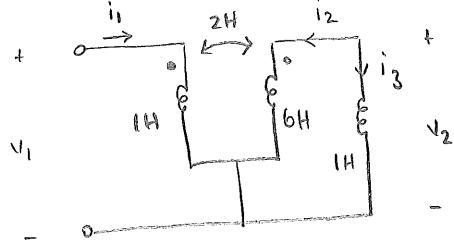
Find $v_1(t)$, $v_2(t)$.Step 1 Find equiv. inductance

$$v_1 = Di_1 + 2Di_2 \quad (1)$$

$$v_2 = 6Di_2 + 2Di_1 \quad \left. \right\} \Rightarrow -Di_2 = 6Di_2 + 2Di_1$$

$$v_2 = Di_3 = -Di_2 \quad \left. \right\} \Rightarrow Di_2 = -\frac{2}{7}Di_1 \quad (2)$$

$$(1) \text{d}(2) \Rightarrow v_1 = Di_1 - \frac{4}{7}Di_1 \Rightarrow v_1 = \frac{3}{7}Di_1 \Rightarrow L_{eq} = \frac{3}{7}H$$

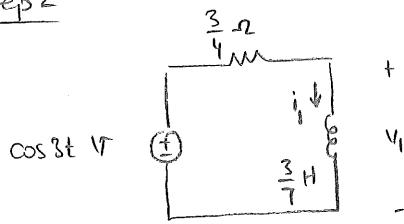Step 2

$$\cos 3t = \frac{3}{4}i_1 + \frac{3}{7}Di_1$$

$$\Rightarrow Di_1 + \frac{7}{4}i_1 = \frac{7}{3}\cos 3t$$

$$i_h(t) = Ke^{-\frac{7}{4}t} \quad (\text{nat. freq. } s = -\frac{7}{4})$$

$$i_p(t) = A\cos 3t + B\sin 3t$$

$$Di_p + \frac{7}{4}i_p = \frac{7}{3}\cos 3t \Rightarrow -3Asin 3t + 3B\cos 3t + \frac{7}{4}\{A\cos 3t + B\sin 3t\} = \frac{7}{3}\cos 3t$$


$$\Rightarrow \underbrace{\left\{ -3A + \frac{7B}{4} \right\}}_{=0} \sin 3t + \underbrace{\left\{ 3B + \frac{7A}{4} \right\}}_{=0} \cos 3t = \frac{7}{3} \cos 3t$$

$$\Rightarrow \begin{bmatrix} -3 & \frac{7}{4} \\ \frac{7}{4} & 3 \end{bmatrix} \begin{bmatrix} A \\ B \end{bmatrix} = \begin{bmatrix} 0 \\ \frac{7}{3} \end{bmatrix} \quad \text{compute } A \text{ & } B$$

$$\text{Then } i_1(t) = i_h(t) + i_p(t) \quad \left. \right\} K = -A \quad \Rightarrow i_1(t) = A\cos 3t + B\sin 3t - Ae^{-\frac{7}{4}t} \quad \text{Amps}$$

$$i_1(0) = 0 \quad \boxed{v_1(t) = \frac{3}{7}Di_1(t) \Rightarrow v_1(t) = \frac{3}{7}\left\{ -3A\sin 3t + 3B\cos 3t + \frac{7}{4}Ae^{-\frac{7}{4}t} \right\} V}$$

$$\left. \begin{array}{l} v_2 = -Di_2 \\ Di_2 = -\frac{2}{7}Di_1 \end{array} \right\} v_2 = \frac{2}{7}Di_1 \quad \& \quad v_1 = \frac{3}{7}Di_1 \quad \Rightarrow \boxed{v_2(t) = \frac{2}{7}v_1(t)}$$

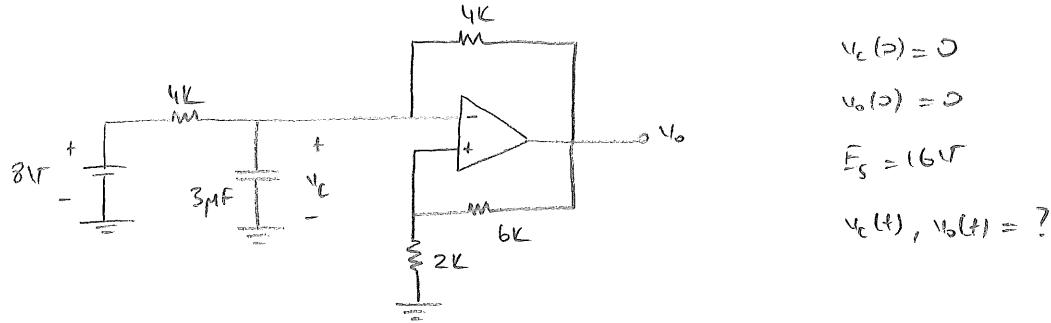Example

$$\text{Node eqn. } \frac{v_c - 8}{4K} + 3\mu F v_c + \frac{v_c - v_o}{4K} = 0 \Rightarrow DV_c + \frac{500}{3} v_c = \frac{250}{3} (v_o + 8) \quad (1)$$

$$\text{Also, } v_+ = \frac{v_o}{4} \quad \& \quad v_- = v_c$$

Initially, $|v_o(0)| < 16$. Hence OP-Amp is in linear region.

$$\text{linear : } v_+ = v_- , |v_o| < 16V$$

$$v_+ = v_- \Rightarrow v_o = 4v_c$$

$$(1) \Rightarrow DV_c + \frac{500}{3} v_c = \frac{250}{3} (4v_c + 8) \Rightarrow DV_c - \frac{500}{3} v_c = \frac{2000}{3} \quad \& \quad v_c(0) = 0$$

$$\Rightarrow v_c(t) = -4 + 4e^{\frac{500}{3}t} V \quad \& \quad v_o(t) = -16 + 16e^{\frac{500}{3}t} V \quad \text{for } 0 \leq t < t_s$$

$$t_s = ? \quad v_o(t_s) = -16 + 16e^{\frac{500}{3}t_s} = 16 \Rightarrow t_s = \frac{3}{500} \ln 2 \text{ sec} \quad \& \quad v_c(t_s) = 4V$$

At $t = t_s$ OPAMP leaves the linear region!

$$+\text{sat region? } v_+ > v_- , v_o = 16V \Rightarrow v_+ = 16V$$

$$(1) \Rightarrow DV_c + \frac{500}{3} v_c = 2000 , v_c(t_s) = 4V$$

$$\Rightarrow v_c(t) = 12 - 8 e^{-\frac{500}{3}(t-t_s)} V \quad (2)$$

However, (2) $\Rightarrow v_c(t) > 4$ for $t > t_s \Rightarrow v_- > 4 \Rightarrow v_- > v_+ \Rightarrow +\text{sat impossible.}$



-sat region $v_+ < v_-$, $v_0 = -16V \Rightarrow v_+ = -4V$

$$(1) \Rightarrow DV_C + \frac{500}{3}v_C = -\frac{2000}{3}$$

$v_C(t) = -4 + 8e^{-\frac{500}{3}(t-t_s)} V$ for $t > t_s$


$v_C(t_s) = 4V$

$v_o(t) = -16V$

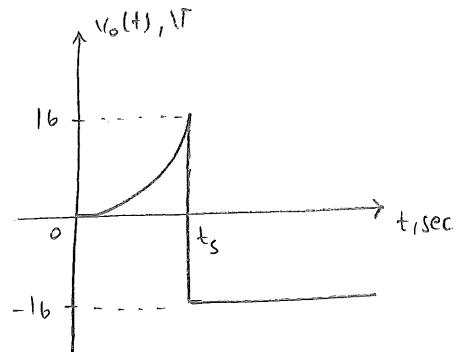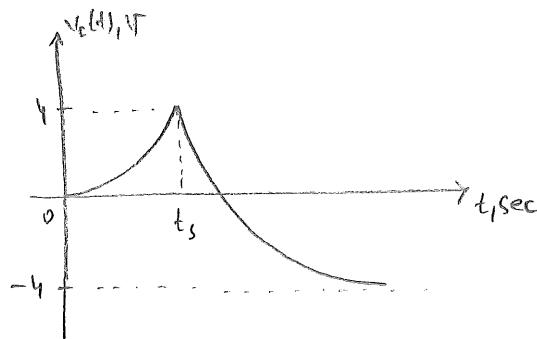

Note that $v_+ < v_-$ for $t > t_s$.

Example [Exponential Input]

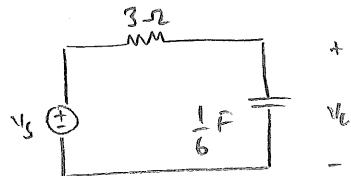

Find $v_c(t)$ for

a) $\alpha = -3$

b) $\alpha = -2$

$$v_c(0) = 6V, v_{in}(t) = e^{\alpha t} V$$

Soln Diff eqn. $DV_C + \frac{1}{RC}v_C = \frac{1}{RC}v_s \Rightarrow DV_C + 2v_C = 2e^{\alpha t}$

$$\text{Nat. freq. } s = -\frac{1}{RC} = -2$$

a) $\alpha = -3 \quad DV_C + 2v_C = 2e^{-3t}$

$$\left. \begin{array}{l} v_p(t) = Ae^{-3t} \\ v_h(t) = Ke^{-2t} \end{array} \right\} DV_p + 2v_p = 2e^{-3t} \Rightarrow -3Ae^{-3t} + 2Ke^{-2t} = 2e^{-3t} \Rightarrow A = -2$$

$$\Rightarrow v_c(t) = v_h(t) + v_p(t) = Ke^{-2t} - 2e^{-3t}, v_c(0) = 6 \Rightarrow K = 8$$

$$\Rightarrow v_c(t) = 8e^{-2t} - 2e^{-3t} V$$

b) $\alpha = -2$ $Dv_c + 2v_c = 2e^{-2t}$


Since α coincides with nat. freq. $s = -2$, $v_p(t) = Ate^{-2t}$

$$Dv_p + 2v_p = 2e^{-2t} \Rightarrow \cancel{\{Ae^{-2t} - 2Ate^{-2t}\}} + \cancel{2Ate^{-2t}} = 2e^{-2t} \Rightarrow A = 2$$

$$\Rightarrow v_c(t) = v_h(t) + v_p(t) = (e^{-2t} + 2te^{-2t}), v_c(0) = 6 \Rightarrow C = 6$$

$$\Rightarrow v_c(t) = 6e^{-2t} + 2te^{-2t} \quad \boxed{V}$$

Example [LTV resistor]

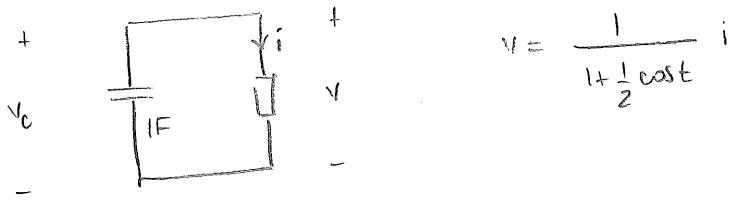

$$v_c(0) = 1V, v_c(t) = ?$$

Soll'n $Dv_c = i_c = -i = -(1 + \frac{1}{2} \cos t)v_c \Rightarrow \frac{dv_c}{v_c} = -(1 + \frac{1}{2} \cos t)dt$

$$\Rightarrow \int \frac{dv_c}{v_c} = - \int (1 + \frac{1}{2} \cos t) dt \Rightarrow \ln v_c = -(t + \frac{1}{2} \sin t) + \text{constant}$$

$$\Rightarrow v_c(t) = C e^{-(t + \frac{1}{2} \sin t)}, v_c(0) = 1 \Rightarrow C = 1 \Rightarrow v_c(t) = e^{-[t + \frac{1}{2} \sin t]} \quad \boxed{V}$$

How about?




$$\hat{v}_c(\pi) = 1V, \hat{v}_c(t) = ? \text{ for } t \geq \pi$$

Soln $\hat{v}_c(t) = \hat{L} e^{-(t + \frac{1}{2}\delta m t)} , \hat{v}_c(\pi) = 1 \Rightarrow \hat{L} = e^{\pi}$

$$\Rightarrow \hat{v}_c(t) = e^{\pi} e^{-[t + \frac{1}{2}\delta m t]} = e^{-[(t - \pi) + \frac{1}{2}\delta m t]} \boxed{V}$$

Remark Note that the time-invariance property is lost. That is, $\hat{v}_c(t) \neq v_c(t - \pi)$

Example [Nonlinear resistor]

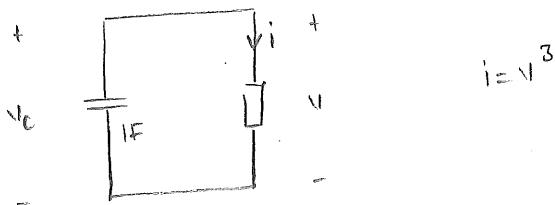

$$v_c(0) = V_0 > 0 , v_c(t) = ? \text{ for } t \geq 0$$

Soln $Dv_c = i = -v_c^3$



$$\Rightarrow -\frac{dv_c}{v_c^3} = dt \Rightarrow \frac{1}{2} v_c^{-2} = t + \text{constant} \Rightarrow v_c(t) = \frac{1}{\sqrt{2t + C}}$$

$$v_c(0) = V_0 \Rightarrow \frac{1}{\sqrt{C}} = V_0 \Rightarrow C = \frac{1}{V_0^2}$$

$$\Rightarrow v_c(t) = \frac{V_0}{\sqrt{1 + 2V_0^2 t}} \boxed{\text{for } t \geq 0}$$


Remark Note that the homogeneity property is lost. That is,

Let $v_c(0) = V_0$ & $\hat{v}_c(0) = \lambda V_0$. But $\hat{v}_c(t) \neq \lambda v_c(t)$.

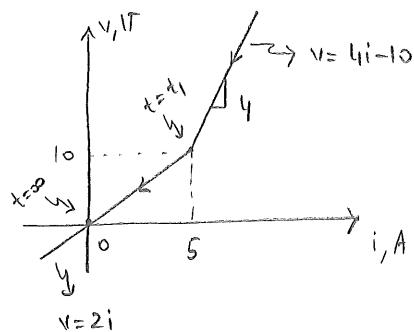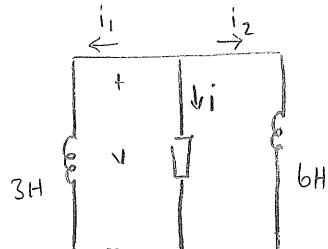Example

$i_1(0) = 3A, i_2(0) = -10A$

$i_1(t), i_2(t) = ?$

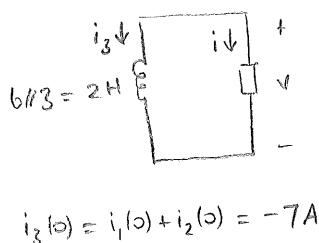

$0 \leq t < t_1$

$i(0) = 7A \Rightarrow v = 4i - 10$

$2Di_3 = v = 4(-i_3) - 10 \Rightarrow Di_3 + 2i_3 = -5$
 $\Rightarrow i_3(t) = -\frac{5}{2} - \frac{9}{2}e^{-2t} A$

$t_1 = ? \quad i(t_1) = 5 \Rightarrow i_3(t_1) = -5 \Rightarrow -5 = -\frac{5}{2} - \frac{9}{2}e^{-2t_1} \Rightarrow t_1 = \frac{1}{2} \ln \frac{9}{5} \text{ sec}$

$t \geq t_1 \quad v = 2i \Rightarrow 2Di_3 = v = -2i_3 \Rightarrow Di_3 + i_3 = 0 \Rightarrow i_3(t) = i_3(t_1)e^{-(t-t_1)}$

$\Rightarrow i_3(t) = -5e^{-(t-t_1)} A$

$\Rightarrow i_3(t) = \begin{cases} -\frac{5}{2} - \frac{9}{2}e^{-2t} A & \text{for } 0 \leq t < t_1 \\ -5e^{-(t-t_1)} A & \text{for } t \geq t_1 \end{cases}$

$i_1(t), i_2(t) = ?$

$i_1(t) = i_1(0) + \frac{1}{3} \int_0^t v(z) dz \quad \left. \right\} 3(i_1(t) - 3) = 6(i_2(t) + 10) \quad (1)$

$i_2(t) = i_2(0) + \frac{1}{6} \int_0^t v(z) dz \quad \left. \right\} \text{Also, } i_1 + i_2 = i_3 \quad (2)$


$(1) \& (2) \Rightarrow 3i_1 - 9 = 6i_3 - 6i_1 + 60 \Rightarrow 9i_1 = 6i_3 + 69 \Rightarrow i_1(t) = \frac{2}{3}i_3(t) + \frac{23}{3} A$

$\& i_2(t) = \frac{1}{3}i_3(t) - \frac{23}{3} A$

Second Order Circuits

zero-input response

series RLC circuit

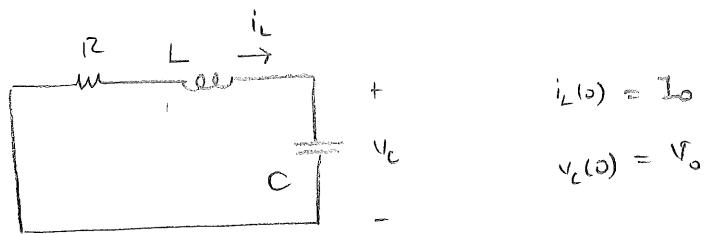formulation variable: v_C

$$KVL: v_R + v_L + v_C = 0$$

$$\Rightarrow Rv_C + Lv_C + v_C = 0 \quad \Rightarrow i_C = Cdv_C$$

$$\Rightarrow RCdv_C + LCD^2v_C + v_C = 0$$


$$\Rightarrow D^2v_C + \frac{R}{L}Dv_C + \frac{1}{LC}v_C = 0 \quad \boxed{\text{Diff. eqn.}}$$

init. cond. $v_C(0)$, $Dv_C(0) = ?$

$$\therefore \rightarrow v_C(0) = V_0 \quad (\text{given})$$

$$\rightarrow Dv_C(0) = \frac{1}{C}i_L(0) = \frac{I_0}{C}$$

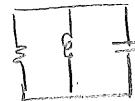Exercise: Work out the dual case
(parallel RLC circuit)



Characteristic polynomial: $d(s) = s^2 + \frac{R}{L}s + \frac{1}{LC}$ (char. eqn., $d(s) = 0$)

In general, characteristic eqn. can be written as

$$\boxed{s^2 + 2\alpha s + \omega_0^2 = 0}$$

Then the roots are $s_{1,2} = -\alpha \pm \sqrt{\alpha^2 - \omega_0^2}$

Def Roots of char. poly. = natural frequencies of the circuit

$\omega_0 = \frac{1}{\sqrt{LC}}$ is called the resonant frequency

formulation variable: i_L

$$v_R + v_L + v_C = 0$$

$$\Rightarrow Ri_L + LDi_L + v_C(0) + \frac{1}{C} \int_0^t i_L(\tau) d\tau = 0 \quad \Rightarrow$$

$$\Rightarrow RDi_L + LD^2i_L + \frac{1}{C}i_L = 0$$

$$\Rightarrow D^2i_L + \frac{R}{L}Di_L + \frac{1}{LC}i_L = 0 \quad \boxed{\text{Diff. eqn.}}$$


init. cond. $i_L(0)$, $Di_L(0) = ?$

$$\rightarrow i_L(0) = I_0$$

$$\rightarrow Di_L(0) = \frac{1}{L}v_L(0) = \frac{1}{L}(-Ri_L(0) - v_C(0))$$

$$= -\frac{R}{L}I_0 - \frac{1}{L}V_0$$

Solution of the circuit depends on the locations of the nat. frequencies on complex plane. Four cases are possible (for passive circuits)

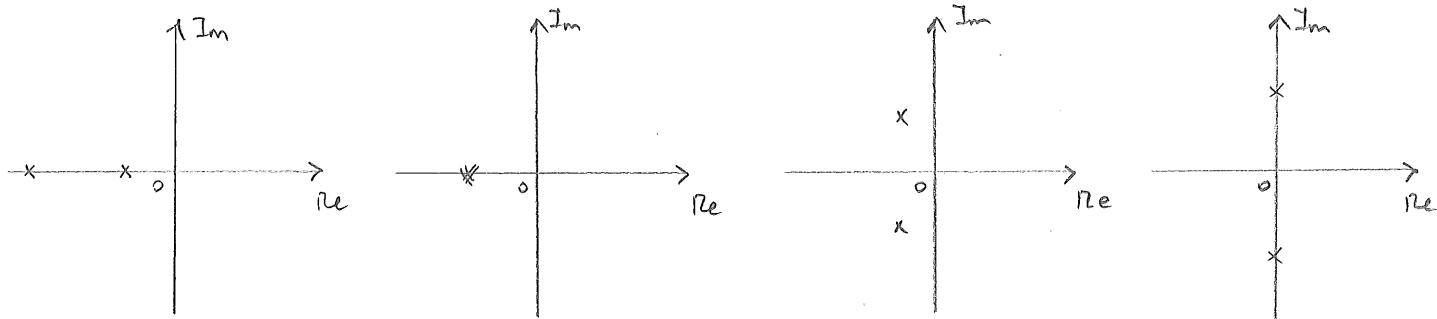


Case 1 : $\alpha > \omega_0 > 0$ (circuit is overdamped)

$$s_{1,2} = -\alpha \pm \sqrt{\alpha^2 - \omega_0^2} = -\alpha \pm \alpha_d \quad (\text{the natural frequencies are negative, real, distinct})$$

$$\Rightarrow v_c(t) = k_1 e^{s_1 t} + k_2 e^{s_2 t}$$

$$\text{Ex: } R = \frac{3}{2} \Omega, L = \frac{1}{2} H, C = 1 F$$

$$v_c(0^-) = 2V, i_L(0^-) = 10A$$

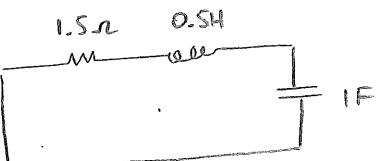

$$\Rightarrow 0^2 v_c + 30 v_c + 2 v_c = 0$$

$$v_c(0^-) = 2V, Dv_c(0^-) = \frac{i_L(0^-)}{C} = 10V/s$$

$$\Rightarrow \text{charac. poly. } d(s) = s^2 + 3s + 2 = (s+1)(s+2)$$

$$\text{natural frequencies: } s_{1,2} = -1, -2$$


$$\Rightarrow v_c(t) = k_1 e^{-t} + k_2 e^{-2t}$$

$$\left. \begin{aligned} v_c(0) &= k_1 + k_2 = 2 \\ Dv_c(0) &= -k_1 - 2k_2 = 10 \end{aligned} \right\} \left. \begin{aligned} k_1 &= 14 \\ k_2 &= -12 \end{aligned} \right\}$$

$$\boxed{v_c(t) = 14e^{-t} - 12e^{-2t} \text{ V}}$$

for $t \geq 0$

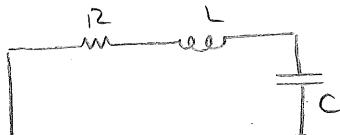Case 2: $\alpha = \omega_0 > 0$ (critically damped)



$$\frac{R}{2L} = \frac{1}{\sqrt{LC}}$$


$$\text{char. poly: } d(s) = s^2 + 2\alpha s + \omega_0^2 = (s + \alpha)^2$$

$$\text{natural freq: } s_{1,2} = -\alpha, -\alpha$$

$$\Rightarrow v_c(t) = k_1 e^{-\alpha t} + k_2 t e^{-\alpha t}$$

$$\text{Ex: } R = 1\Omega, L = 1H, C = 4F$$

$$v_c(0^-) = 2V, i_L(0^-) = 4A$$

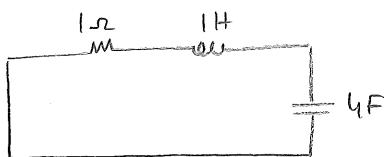

$$\Rightarrow D^2 v_c + DV_c + \frac{1}{4} v_c = 0$$

$$v_c(0^-) = 2V, DV_c(0^-) = 1V/s$$

$$\Rightarrow \text{char. poly. } d(s) = s^2 + 8 + \frac{1}{4} = \left(s + \frac{1}{2}\right)^2$$

$$\text{nat. freq: } s_{1,2} = -\frac{1}{2}, -\frac{1}{2}$$

$$\Rightarrow v_c(t) = k_1 e^{-\frac{t}{2}} + k_2 t e^{-\frac{t}{2}}$$

$$v_c(0) = k_1 = 2$$

$$DV_c(0) = -\frac{1}{2}k_1 + k_2 = 1 \Rightarrow k_2 = 2$$

$$\left. \begin{aligned} v_c(t) &= 2e^{-\frac{t}{2}} + 2te^{-\frac{t}{2}} \quad \text{for } t \geq 0 \\ \end{aligned} \right\}$$

Case 3: $\omega_0 > \alpha > 0$ (underdamped)


$$\text{char. poly. } d(s) = s^2 + 2\alpha s + \omega_0^2$$

$$\text{natural freq. } s_{1,2} = -\alpha \pm j\omega_d \quad \text{where } \omega_d = \sqrt{\omega_0^2 - \alpha^2}$$

$$\Rightarrow v_c(t) = k_1 e^{-\alpha t} \sin \omega_d t + k_2 e^{-\alpha t} \cos \omega_d t$$

$$Ex: R = \frac{3}{25} \Omega, L = 1mH, C = \frac{1}{10} F$$

$$v_c(0^-) = 3V, i_L(0^-) = 14A$$

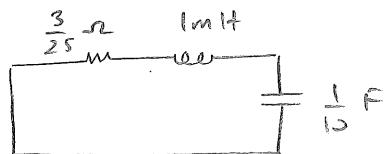

$$\Rightarrow 0^2 v_c + 120Dv_c + 10^4 v_c = 0$$

$$v_c(0^-) = 3V, Dv_c(0^-) = 140V/s$$

$$\Rightarrow d(s) = s^2 + 120s + 10^4 = (s+60)^2 + 80^2$$

$$\text{nat. freq. } s_{1,2} = -60 \pm j80$$

$$\Rightarrow v_c(t) = k_1 e^{-60t} \sin 80t + k_2 e^{-60t} \cos 80t$$

$$v_c(0) = k_2 = 3$$

$$Dv_c(0) = 80k_1 - 60k_2 = 140 \Rightarrow k_1 = 4$$


$$v_c(t) = 4e^{-60t} \sin 80t + 3e^{-60t} \cos 80t \quad \boxed{\text{for } t \geq 0}$$

Note that we can write


$$v_c(t) = e^{-60t} \left\{ 4 \sin 80t + 3 \cos 80t \right\}$$

$$= \sqrt{3^2 + 4^2} e^{-60t} \left\{ \underbrace{\frac{4}{\sqrt{3^2 + 4^2}} \sin 80t}_{\cos \phi} + \underbrace{\frac{3}{\sqrt{3^2 + 4^2}} \cos 80t}_{\sin \phi} \right\} \quad (\phi = \arctan \frac{3}{4})$$

$$= 5e^{-60t} \sin(80t + \phi)$$

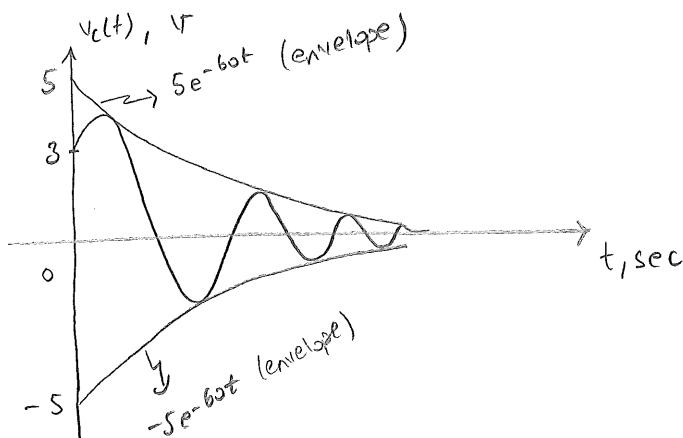

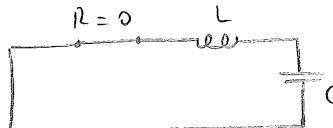Case 4: $\omega_0 > \alpha = 0$ (lossless)




$$\text{diff. eqn. } D^2V_C + \frac{1}{LC}V_C = 0$$

$$\text{char. poly. } D(s) = s^2 + \frac{1}{LC} = s^2 + \omega_0^2$$

$$\text{nat. freq. } s_{1,2} = \mp j\omega_0 = \mp j\frac{1}{\sqrt{LC}}$$

$$\Rightarrow V_C(t) = k_1 \sin \omega_0 t + k_2 \cos \omega_0 t \quad (\text{sustaining oscillations})$$
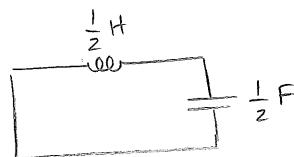
$$\text{Ex: } R=0, L=\frac{1}{2}H, C=\frac{1}{2}F$$



$$V_C(0^-) = 10V, i_L(0^-) = 10A$$

$$\Rightarrow D^2V_C + 4V_C = 0$$

$$V_C(0^-) = 10V, DV_C(0^-) = 20V/s$$


$$\Rightarrow D(s) = s^2 + 4, \text{ nat. freq. } s_{1,2} = \mp j2$$

$$\Rightarrow V_C(t) = k_1 \sin 2t + k_2 \cos 2t$$

$$V_C(0) = k_2 = 10$$

$$DV_C(0) = 2k_1 = 20 \Rightarrow k_1 = 10$$

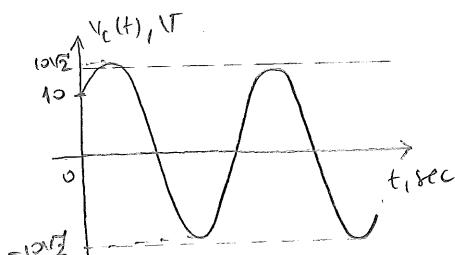
$$\begin{aligned} V_C(t) &= 10 \sin 2t + 10 \cos 2t \\ &= 10\sqrt{2} \left\{ \frac{1}{\sqrt{2}} \sin 2t + \frac{1}{\sqrt{2}} \cos 2t \right\} \\ &= 10\sqrt{2} \left\{ \cos \frac{\pi}{4} \sin 2t + \sin \frac{\pi}{4} \cos 2t \right\} \\ &= 10\sqrt{2} \sin \left(2t + \frac{\pi}{4} \right) V \quad \text{for } t \geq 0 \end{aligned}$$



Why "lossless"?

$$\text{Total stored energy } E(t) = \frac{1}{2}L i(t)^2 + \frac{1}{2}C V(t)^2$$

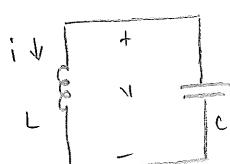
$$\frac{dE}{dt} = L i D i + C V D V = i \underbrace{(L D i)}_V + V \underbrace{(C D V)}_{-i} = iV - Vi = 0$$



$$\Rightarrow E(t) = E(0) \quad \text{for all } t \geq 0 \Rightarrow \text{Electrical energy is conserved.}$$

zero-state response

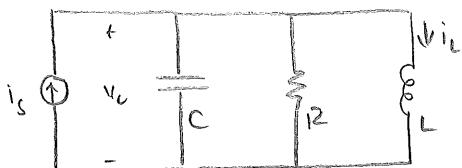For the following circuit find the step response $i_L(t)$



By definition:

$$\rightarrow i_s(t) = u(t) \quad (\text{unit step input})$$

$$\rightarrow i_L(0^-) = 0, v_c(0^-) = 0 \quad (\text{zero init. cond.})$$

$$\begin{aligned} i_s &= i_C + i_R + i_L \\ &= C\dot{v}_c + \frac{1}{R}v_c + i_L \end{aligned}$$

$$= C(D(L)i_L) + \frac{1}{R}(L\dot{i}_L) + i_L = LC\ddot{i}_L + \frac{1}{R}\dot{i}_L + i_L$$

$$D^2 i_L + \frac{1}{RC} D i_L + \frac{1}{LC} i_L = \frac{1}{LC} u(t) \quad \text{Diff. eqn.}$$

$$\left. \begin{array}{l} i_L(0^-) = 0 \\ \dot{i}_L(0^-) = \frac{v_c(0^-)}{L} = \frac{v_c(0^-)}{L} = 0 \end{array} \right\} \begin{array}{l} \text{init.} \\ \text{cond.} \end{array}$$

Example: Let $R = 1\Omega$, $C = 1F$, $L = 1H$.

$$\text{For } t > 0 \quad D^2 i_L + Di_L + i_L = 1$$

$$i_L(0^+) = 0, \dot{i}_L(0^+) = 0 \quad (\text{WHY?})$$

$$\left. \begin{array}{l} \text{char. poly. } d(s) = s^2 + s + 1 = \left(s + \frac{1}{2}\right)^2 + \frac{3}{4} \\ \text{nat. freq. } s_{1,2} = -\frac{1}{2} \pm j\frac{\sqrt{3}}{2} \quad (\text{underdamped}) \end{array} \right\}$$

$$\Rightarrow \text{hmp sol'n: } i_h(t) = k_1 e^{-t/2} \sin \frac{\sqrt{3}}{2} t + k_2 e^{-t/2} \cos \frac{\sqrt{3}}{2} t$$

$$\text{particular sol'n: } i_p(t) = A \quad (\text{constant}) \Rightarrow D^2 i_p + Di_p + i_p = 1 \quad \left|_{i_p = A} \right. \Rightarrow A = 1$$

$$\Rightarrow i_L(t) = i_h(t) + i_p(t) = k_1 e^{-t/2} \sin \frac{\sqrt{3}}{2} t + k_2 e^{-t/2} \cos \frac{\sqrt{3}}{2} t + 1$$


$$\text{init. cond: } i_L(0) = 0 \Rightarrow k_2 + 1 = 0 \Rightarrow k_2 = -1$$

$$Di_L(0) = 0 \Rightarrow \frac{\sqrt{3}}{2} k_1 - \frac{1}{2} k_2 = 0 \Rightarrow k_1 = -\frac{1}{\sqrt{3}}$$

$$\Rightarrow i_L(t) = -\frac{1}{\sqrt{3}} e^{-t/2} \sin \frac{\sqrt{3}}{2} t - e^{-t/2} \cos \frac{\sqrt{3}}{2} t + 1 \quad \text{Amps} \quad \text{for } t > 0$$

transient part


steady state part

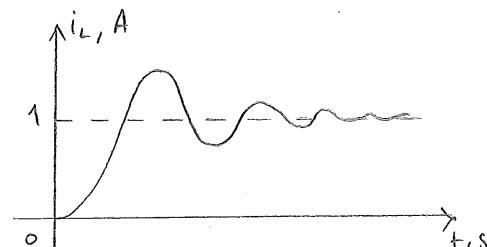

Hence, the step response is:

$$s(t) = \left[-\frac{1}{\sqrt{3}} e^{-t/2} \sin \frac{\sqrt{3}}{2} t - e^{-t/2} \cos \frac{\sqrt{3}}{2} t + 1 \right] u(t) \quad \text{Amps}$$

Impulse response?

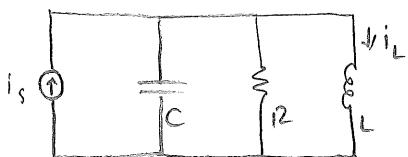

By definition:

$$\rightarrow i_s(t) = \delta(t) \quad (\text{unit impulse input})$$

$$\rightarrow i_L(0^-) = 0, v_c(0^-) = 0 \quad (\text{zero init. cond.})$$

$$\text{Diff. eqn. } D^2 i_L + \frac{1}{RC} Di_L + \frac{1}{LC} i_L = \frac{1}{LC} i_s \Rightarrow D^2 i_L + \frac{1}{RC} Di_L + \frac{1}{LC} i_L = \frac{1}{LC} \delta(t)$$


Example: Consider the same circuit ($R=1\Omega$, $C=1F$, $L=1H$)

$$\begin{aligned} \text{For } t > 0 \quad D^2 i_L + Di_L + i_L &= 0 \\ i_L(0^+) = ? \quad Di_L(0^+) &= ? \end{aligned} \quad \left. \right\} (*)$$

For $0^- < t < 0^+$

$$i_L(0^+) = i_L(0^-) + \underbrace{\frac{1}{L} \int_{0^-}^{0^+} v_c(t) dt}_{=0} \xrightarrow{\text{bounded}} = i_L(0^-) = 0$$

Also,

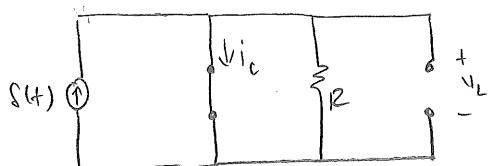

$$i_c(t) = \delta(t)$$

$$\Rightarrow v_c(0^+) = v_c(0^-) + \frac{1}{C} \int_{0^-}^{0^+} \delta(t) dt = v_c(0^-) + \frac{1}{C}$$

$$\Rightarrow v_c(0^+) = 1V$$

$$\Rightarrow Di_L(0^+) = \frac{v_c(0^+)}{L} = 1A/s$$

Return to (*)

$$s(s) = s^2 + s + 1 = (s + \frac{1}{2})^2 + \frac{3}{4} \Rightarrow s_{1,2} = -\frac{1}{2} \pm j \frac{\sqrt{3}}{2}$$


$$\Rightarrow i_L(t) = k_1 e^{-t/2} \sin \frac{\sqrt{3}}{2} t + k_2 e^{-t/2} \cos \frac{\sqrt{3}}{2} t \quad \left. \right\} i_L(t) = \frac{2}{\sqrt{3}} e^{-t/2} \sin \frac{\sqrt{3}}{2} t \text{ Amps for } t > 0$$

$$i_L(0) = 0 \Rightarrow k_2 = 0$$

$$Di_L(0) = 1 \Rightarrow \frac{\sqrt{3}}{2} k_1 = 1 \Rightarrow k_1 = \frac{2}{\sqrt{3}}$$


Hence, the impulse response is:
$$h(t) = \left(\frac{2}{\sqrt{3}} e^{-t/2} \sin \frac{\sqrt{3}}{2} t \right) u(t) \text{ Amps}$$

Exercise : Verify $h(t) = \frac{d}{dt} s(t)$.

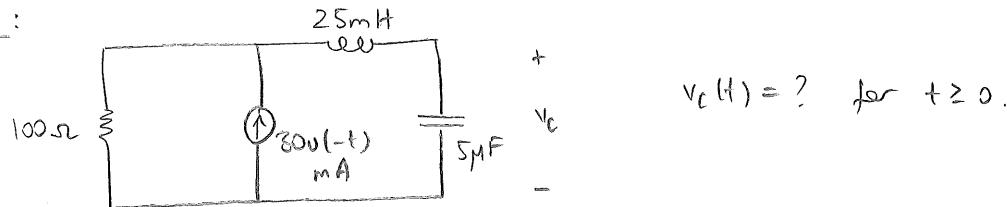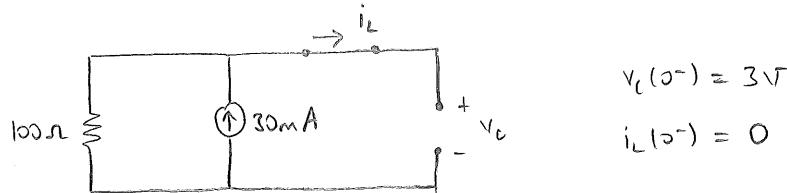Example:

$$v_c(t) = ? \quad \text{for } t \geq 0.$$


For $t < 0$ (assume that the circuit is at DC steady state)



$$v_c(0^-) = 3\sqrt{V}$$

$$i_L(0^-) = 0$$

for $t > 0$

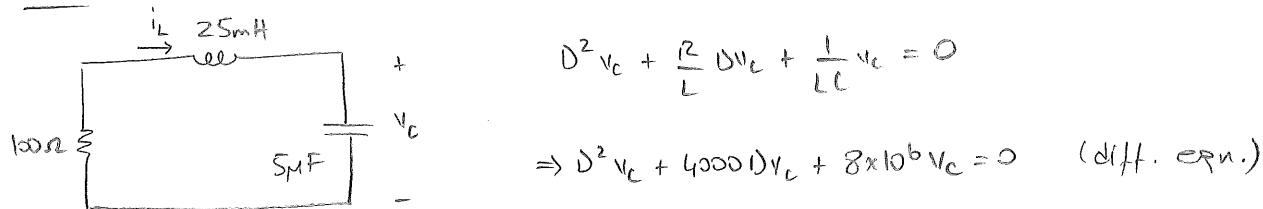

$$D^2 v_c + \frac{R}{L} Dv_c + \frac{1}{LC} v_c = 0$$

$$\Rightarrow D^2 v_c + 4000Dv_c + 8 \times 10^6 v_c = 0 \quad (\text{diff. eqn.})$$

$$\begin{array}{l|l} \text{init. cond.} & v_c(0^+) = v_c(0^-) = 3\sqrt{V} \\ & i_L(0^+) = i_L(0^-) = 0 \end{array} \quad \left| \quad Dv_c(0^+) = \frac{i_L(0^+)}{C} = \frac{i_L(0^-)}{C} = 0 \right.$$

$$\text{chr. poly. } d(s) = s^2 + 4000s + 8 \times 10^6 = (s+2000)^2 + 2000^2$$


$$\text{nrt. freq. } s_{1,2} = -2000 \pm j2000 \quad (\text{underdamped})$$


$$\Rightarrow v_c(t) = e^{-2000t} (k_1 \sin 2000t + k_2 \cos 2000t)$$

$$v_c(0) = 3 \Rightarrow k_2 = 3$$

$$Dv_c(0) = 0 \Rightarrow -2000k_2 + 2000k_1 = 0 \Rightarrow k_1 = 3$$
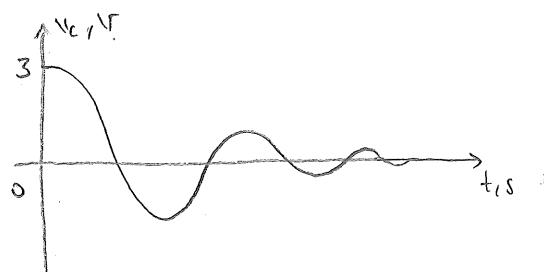
$$\Rightarrow v_c(t) = 3e^{-2000t} (3 \sin 2000t + \cos 2000t) \sqrt{V}$$



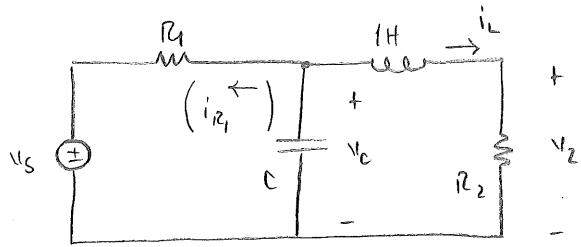Example

Design the circuit so that the step response for v_2 is (for $t > 0$)
 $v_2(t) = \frac{3}{4} + (A+Bt)e^{-4t}$ V. $A, B = ?$

Sol'n First obtain the diff. eqn. (in terms of i_L)

$$0 = i_L + i_C + i_R$$


$$= \frac{v_C - v_s}{R_1} + C D v_C + i_L$$

$$\therefore v_C = L D i_L + R_2 i_L$$

$$= \frac{1}{R_1} \left\{ L D i_L + R_2 i_L - v_s \right\} + C D \left\{ L D i_L + R_2 i_L \right\} + i_L$$

$$= L C D^2 i_L + \left\{ \frac{L}{R_1} + R_2 C \right\} D i_L + \left\{ 1 + \frac{R_2}{R_1} \right\} i_L - \frac{1}{R_1} v_s$$

$$\Rightarrow D^2 i_L + \left(\frac{1}{R_1 C} + \frac{R_2}{L} \right) D i_L + \left(1 + \frac{R_2}{R_1} \right) \frac{1}{L C} i_L = \frac{1}{R_1 L C} v_s$$

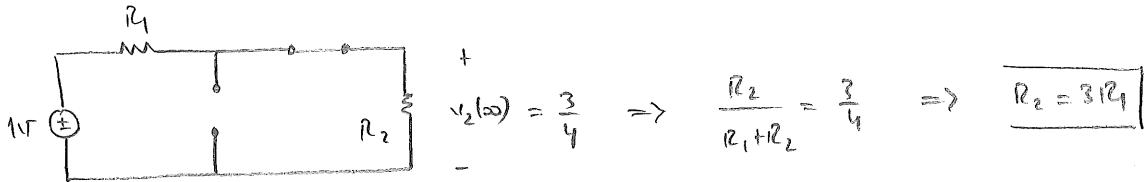 $t = \infty$ 

$$\Rightarrow \text{char. poly. } \mathcal{J}(s) = s^2 + \left(\frac{1}{R_1 C} + 3R_1 \right) s + \frac{4}{C} = (s+4)^2 = s^2 + 8s + 16$$

$$\Rightarrow C = \frac{1}{4} F \quad \& \quad \frac{4}{R_1} + 3R_1 = 8 \Rightarrow 3R_1^2 - 8R_1 + 4 = 0 \Rightarrow (3R_1 - 2)(R_1 - 2) = 0$$

$$\Rightarrow R_1 = \frac{2}{3} \Omega \quad \& \quad R_2 = 2 \Omega$$

or

$$R_1 = 2 \Omega \quad \& \quad R_2 = 6 \Omega$$

A, B = ? zero state $\Rightarrow i_L(0^-) = 0, v_c(0^-) = 0$ (by def.)

Then we have $i_L(0^+) = 0 \& v_c(0^+) = 0$ (WHY?)


$$v_L(0) = R_2 i_L(0) = 0$$

$$\text{D}v_L(0) = R_2 \text{D}i_L(0) = \frac{R_2}{L} v_L(0) = \frac{R_2}{L} (v_c(0) - R_2 i_L(0)) = 0$$

$$\text{Now, } v_L(0) = 0 \Rightarrow \frac{3}{4} + A = 0 \Rightarrow \boxed{A = -\frac{3}{4}}$$

$$\text{D}v_L(0) = 0 \Rightarrow -4A + B = 0 \Rightarrow \boxed{B = -3}$$

Example:

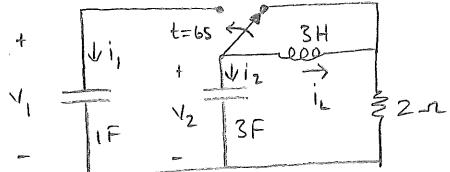

$$v_1(0) = 18V, v_2(0) = -10e^{-t/6}, i_L(0) = -2A$$


$$v_2(t) = ? \text{ for } t \geq 0$$

$$0 \leq t < 6$$

$$\text{D}v_1 = i_1 = 0 \Rightarrow v_1(t) = 18V$$

$$\text{D}i_L = \frac{1}{3} v_L = 0 \Rightarrow i_L(t) = -2A$$
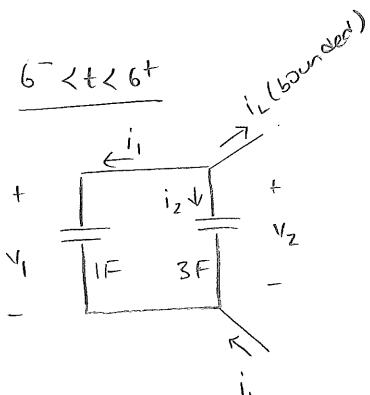
$$\text{D}v_2 = \frac{1}{3} i_2 = \frac{1}{3} \left\{ -\frac{v_2}{2} \right\} \Rightarrow \text{D}v_2 + \frac{1}{6} v_2 = 0 \Rightarrow v_2(t) = v_2(0) e^{-t/6} \Rightarrow v_2(t) = -10e^{-t/6} V$$




$$\begin{aligned} v_1(6^+) &= v_1(6^-) + \frac{1}{1} \int_{6^-}^{6^+} i_1(z) dz \\ v_2(6^+) &= v_2(6^-) + \frac{1}{3} \int_{6^-}^{6^+} i_2(z) dz \\ &= v_2(6^-) + \frac{1}{3} \int_{6^-}^{6^+} \left[-i_1(z) - \underbrace{(2i_1 - 2i_2)}_{\text{bounded}} \right] dz \\ &= v_2(6^-) - \frac{1}{3} \int_{6^-}^{6^+} i_1(z) dz \end{aligned}$$

$$v_1(6^+) = v_2(6^+) \Rightarrow \int_{6^-}^{6^+} i_1(z) dz = v_2(6^+) - v_1(6^-) \quad \left. \right\} \quad v_2(6^+) = \frac{v_1(6^-) + 3v_2(6^-)}{4}$$

$$= 3(v_2(6^-) - v_2(6^+)) \quad \left. \right\} \quad = \frac{18 + 3(-10e^{-6/6})}{4} = -3V$$

Also, $i_L(b^+) = i_L(b^-) = -2A$ (WHY?)

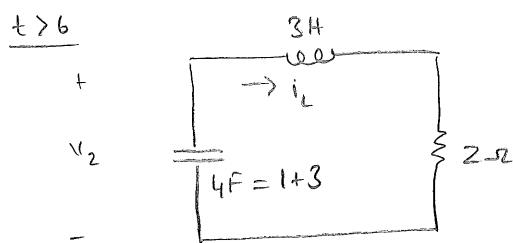

$$D^2 v_2 + \frac{R}{L} Dv_2 + \frac{1}{LC} v_2 = 0$$

$$\Rightarrow D^2 V_2 + \frac{2}{3} DV_2 + \frac{1}{12} V_2 = 0$$

$$\psi_2(6) = -3\sqrt{}$$

$$Dv_2(6) = \frac{i_c(6)}{4} = -\frac{i_L(6)}{4} = \frac{1}{2} \text{ V/s}$$

$$\text{Char. poly. } d(s) = s^2 + \frac{2}{3}s + \frac{1}{12} = \left(s + \frac{1}{2}\right)\left(s + \frac{1}{6}\right)$$


$$\text{nat. freq. } \omega_{1,2} = -\frac{1}{2}, -\frac{1}{6} \quad (\text{overdamped})$$


$$\Rightarrow v_2(t) = k_1 e^{-(t-6)/2} + k_2 e^{-(t-6)/6}$$

$$v_2(b) = -3 \Rightarrow k_1 + k_2 = -3$$

$$D_{Y_2}(6) = \frac{1}{2} \Rightarrow -\frac{1}{2}k_4 - \frac{1}{6}k_2 = \frac{1}{2}$$
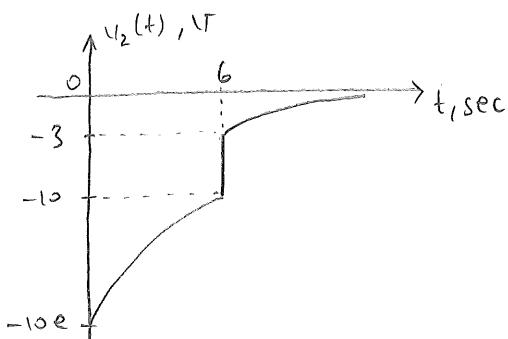
$$\Rightarrow v_2(t) = -3e^{-(t-6)/6} \quad \forall t$$



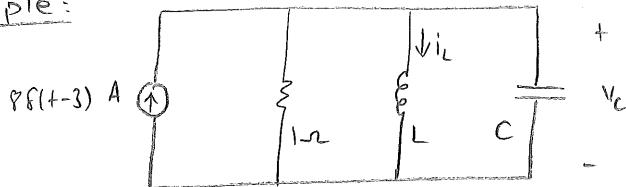Example:

$v_c(3^+) = 1V$ and the response is critically damped.


a) determine L & C.

$$i_L(0) = 0, \quad v_c(0) = 0$$

b) find $v_c(t)$ for $t \geq 0$.

 $0 \leq t < 3$


Everything is zero. $\Rightarrow \boxed{v_c(t) = 0}$

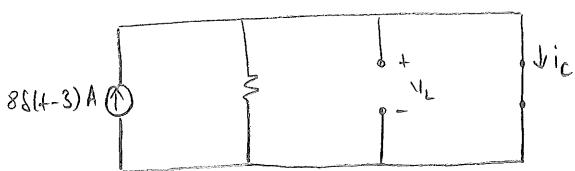 $3^- < t < 3^+$ 

$$i_L(t) = 8\delta(t-3)$$

$$\Rightarrow v_c(3^+) = v_c(3^-) + \frac{1}{C} \int_{3^-}^{3^+} 8\delta(t-3) dt = \frac{8}{C} = 1$$

$$\Rightarrow \boxed{C = 8F}$$

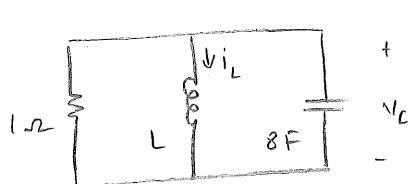 $t > 3$ 

$$D^2v_c + \frac{1}{R^2C} Dv_c + \frac{1}{LC} v_c = 0$$

$$\Rightarrow D^2v_c + \frac{1}{8} Dv_c + \frac{1}{8L} v_c = 0$$

$$v_c(3^+) = 1V, \quad i_L(3^+) = 0$$

$$\text{char. poly. } d(s) = s^2 + \frac{1}{8}s + \frac{1}{8L} = (s+\alpha)^2 = s^2 + 2\alpha s + \alpha^2$$

$$\Rightarrow 2\alpha = \frac{1}{8} \Rightarrow \alpha = \frac{1}{16}$$

$$\Rightarrow \frac{1}{8L} = \alpha^2 = \frac{1}{256} \Rightarrow \boxed{L = 32H}$$

$$\Rightarrow D^2v_c + \frac{1}{8} Dv_c + \frac{1}{256} v_c = 0$$

$$v_c(3) = 1V$$

$$Dv_c(3) = \frac{1}{8} i_L(3) = \frac{1}{8} (-i_L(3) - i_R(3)) = \frac{1}{8} \left(-i_L(3) - \frac{v_c(3)}{1} \right) = -\frac{1}{8} V/s$$

$$\text{char. poly. } d(s) = (s + \frac{1}{16})^2$$

$$\text{nat. freq. } s_{1,2} = -\frac{1}{16} \pm -\frac{1}{16}$$


$$v_c(t) = (k_1 + k_2(t-3)) e^{-\frac{1}{16}(t-3)}$$

$$v_c(3) = 1$$


$$Dv_c(3) = -\frac{1}{8}$$

$$k_1 = 1, \quad k_2 = -\frac{1}{16}$$

$$\Rightarrow v_c(t) = \left[1 - \frac{1}{16}(t-3) \right] e^{-\frac{1}{16}(t-3)} V \quad \boxed{\text{for } t > 3s}$$

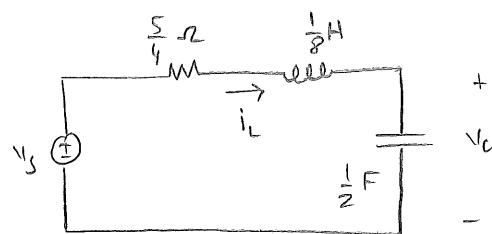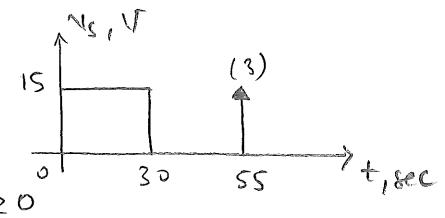Example:+
-

$$\begin{aligned}v_c(0^-) &= -3 \text{ V} \\i_L(0^-) &= 0 \\v_c(t) &=? \quad \text{for } t \geq 0\end{aligned}$$



$$\text{Diff. eqn. } D^2v_c + \frac{R}{L}Dv_c + \frac{1}{LC}v_c = \frac{1}{LC}v_s$$

$$\Rightarrow D^2v_c + 10Dv_c + 16v_c = 16v_s, \quad v_c(0^-) = -3 \text{ V}, \quad Dv_c(0^-) = \frac{i_L(0^-)}{C} = 0$$

zero-input response : $v_{zi}(t)$

$$\left. \begin{aligned}D^2v_c + 10Dv_c + 16v_c &= 0 \\v_c(0^-) &= -3 \text{ V}, \quad Dv_c(0^-) = 0\end{aligned} \right\} \text{ char. poly. } d(s) = s^2 + 10s + 16 = (s+2)(s+8)$$

$$\left. \begin{aligned}v_c(0) &= -3 \Rightarrow k_1 + k_2 = -3 \\Dv_c(0) &= 0 \Rightarrow -2k_1 - 8k_2 = 0\end{aligned} \right\} \left. \begin{aligned}k_1 &= -4 \\k_2 &= 1\end{aligned} \right\} \Rightarrow v_{zi}(t) = -4e^{-2t} + e^{-8t} \text{ V}$$

step response : $s(t)$

$$\left. \begin{aligned}D^2v_c + 10Dv_c + 16v_c &= 16u(t) \\v_c(0^-) &= 0, \quad Dv_c(0^-) = 0\end{aligned} \right\} \left. \begin{aligned}v_p(t) &= 1 \\v_h(t) &= k_3e^{-2t} + k_4e^{-8t}\end{aligned} \right\} \left. \begin{aligned}v_c(t) &= 1 + k_3e^{-2t} + k_4e^{-8t}\end{aligned} \right\}$$

$$\left. \begin{aligned}v_c(0^+) &= 0 \Rightarrow 1 + k_3 + k_4 = 0 \\Dv_c(0^+) &= 0 \Rightarrow -2k_3 - 8k_4 = 0\end{aligned} \right\} \left. \begin{aligned}k_3 &= -\frac{4}{3} \\k_4 &= \frac{1}{3}\end{aligned} \right\} \Rightarrow s(t) = \left[1 - \frac{4}{3}e^{-2t} + \frac{1}{3}e^{-8t} \right] u(t) \text{ V}$$


impulse response : $h(t) = \frac{d}{dt}s(t)$

$$\Rightarrow h(t) = \left[\frac{8}{3}e^{-2t} - \frac{8}{3}e^{-8t} \right] u(t) \text{ V}$$

zero state response : $v_{zs}(t)$

$$v_s(t) = 15u(t) - 15u(t-30) + 3\delta(t-55) \Rightarrow v_{zs}(t) = 15s(t) - 15s(t-3) + 3h(t-55)$$

Finally, overall response : $v_c(t) = v_{zi}(t) + v_{zs}(t)$

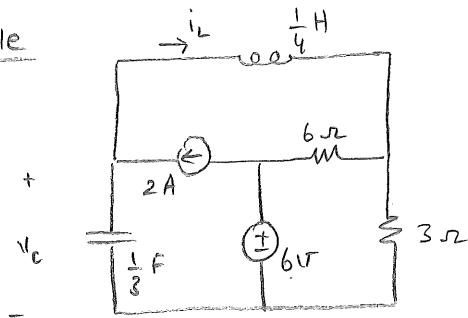Example $V_c(0) = 9V, i_L(0) = 0$. Find $v_c(t)$ for $t \geq 0$.Sol'n Classical way: 1) Derive the diff. eqn.2) Obtain init. cond. $V_c(0) = 9V$ (given)

$$Dv_c(0) = \frac{1}{C} i_c(0) = \frac{1}{C} (i_s(0) - i_L(0)) = 6V/s$$

3) Solve for $v_c(t)$.Another way: find the natural freq. first. Characteristic poly. does not depend on the inputs. Hence, kill the indep. sources:


$$\Rightarrow \text{series } RLC \Rightarrow D(s) = s^2 + \frac{R}{L}s + \frac{1}{LC} \quad \text{where } R = R_1 // R_2$$

$$\Rightarrow D(s) = s^2 + 8s + 12 = (s+2)(s+6)$$

$$\Rightarrow s_{1,2} = -2, -6$$

Then, Notice that the sources are DC. Hence the particular sol'n v_p will be constant.

$$\Rightarrow v_c(t) = \underbrace{k_1 e^{-2t} + k_2 e^{-6t}}_{v_h(t)} + \underbrace{A}_{v_p(t)}$$

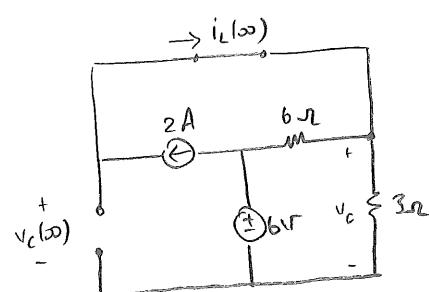Note that $A = v_c(\infty)$. Hence check the steady state circuit:

$$\Rightarrow \frac{V_c}{3} + \frac{V_c - 6}{6} - 2 = 0$$

$$\Rightarrow V_c(\infty) = 6V$$

$$\Rightarrow v_c(t) = k_1 e^{-2t} + k_2 e^{-6t} + 6$$

Finally, apply the init. cond constraints

$$\left. \begin{aligned} V_c(0) &= 9V \Rightarrow k_1 + k_2 + 6 = 9 \\ Dv_c(0) &= 6V/s \Rightarrow -2k_1 - 6k_2 = 6 \end{aligned} \right\} \quad \begin{aligned} k_1 &= 6, \\ k_2 &= -3 \end{aligned}$$

$$\Rightarrow \overline{v_c(t) = 6e^{-2t} - 3e^{-6t} + 6V}$$