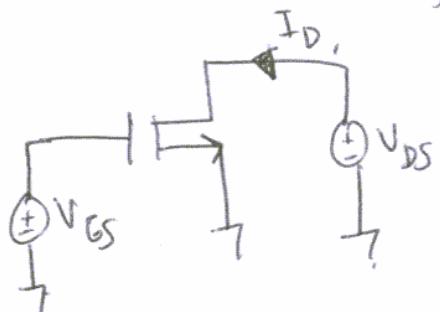


①



$$V_T = 2 \text{ V}$$

$$K = \frac{20 \mu \text{A}}{0.5} / \text{V}^2$$


- a) $V_{GS} = 6 \text{ V}$; $V_{DS} = 2 \text{ V}$; Find I_D
 b) $V_{GS} = 6 \text{ V}$; $V_{DS} = 6 \text{ V}$; Find I_D .
 c) $I_D = 4 \text{ mA}$ and Transistor is in SAT.
 Find V_{GS}
 d) $I_D = 6 \text{ mA}$ and Transistor is in SAT
 Find V_{GS} .

② NMOS device has $V_{GS} = V_{DS} = 9 \text{ V}$ and $I_D = 4 \text{ mA}$.

The same device has $V_{GS} = V_{DS} = 5 \text{ V}$ and $I_D = 1 \text{ mA}$

Find K and V_{T_0}

③

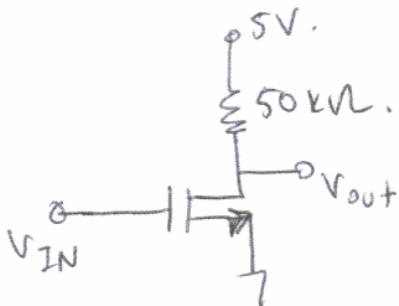


$$V_T = 1 \text{ V}$$

$$K = 40 \mu \text{A} / \text{V}^2$$

- a) Find V_{out} for $V_{IN} = 0 \text{ V}$
 b) Find V_{out} for $V_{IN} = 5 \text{ V}$
 c) Find V_{out} for $V_{IN} = 1 \text{ V}$
 d) Sketch VTC.

(4)

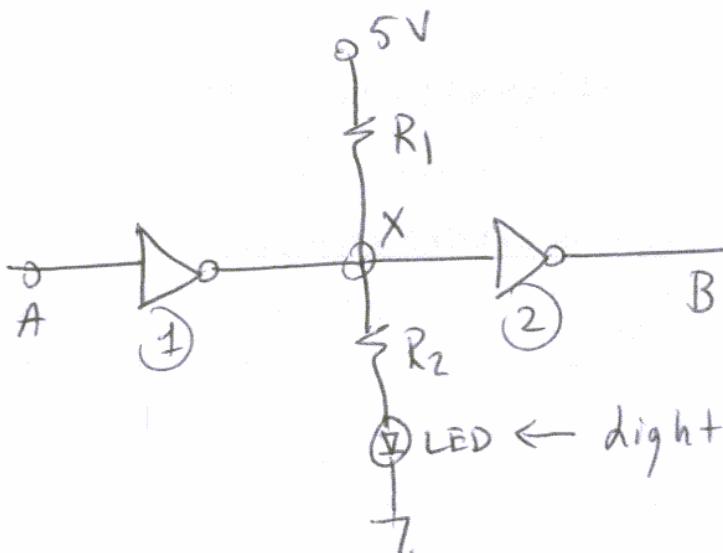LED \leftarrow light Emitting Diode.

LED is a diode which emits light when it is ON.
LED in the circuit requires 0.9V and $\geq 1\text{mA}$ to light.

a) Find minimum value of R_1 so that when the input is high ; led is OFF , B output is high.

b) Find maximum value of R_1 so that when the input is low, led is ON and B output is low.

Family 1 :

$$\text{I}_{OH}^{\max} = 250\text{ }\mu\text{A}$$

$$\text{I}_{OL}^{\max} = 20\text{ mA}$$

$$V_{OL}^{\max} = 0.4\text{ V}$$

$$V_{OH} = \text{Determined}$$

by
 R_1

Family 2 :

$$\text{I}_{IL}^{\max} = -2\text{ mA}$$

$$\text{I}_{IH}^{\max} = 250\text{ }\mu\text{A.}$$

$$V_{IH}^{\min} = 2.0\text{ V}$$

$$V_{IL}^{\max} = 0.8\text{ V}$$

Note: All $\text{I}_{IH}, \text{I}_{IL}, \text{I}_{OL}, \text{I}_{OH}$ are defined to be entering into the gate.