

## Homework 7

### Solution for Problem 4


Open Collector TTL

$V_{\text{supply}} = 5 \text{ V}$   
 $I_{\text{OH Max}} = 250 \mu\text{A}$   
 $I_{\text{OL Max}} = 20 \text{ mA}$   
 $V_{\text{OL Max}} = 0.4 \text{ V}$

Standart TTL

$V_{\text{supply}} = 5 \text{ V}$   
 $I_{\text{IL Max}} = -2 \text{ mA}$   
 $I_{\text{IH Max}} = 250 \mu\text{A}$   
 $V_{\text{IH Min}} = 2.0 \text{ V}$   
 $V_{\text{IL Max}} = 0.8 \text{ V}$

a)

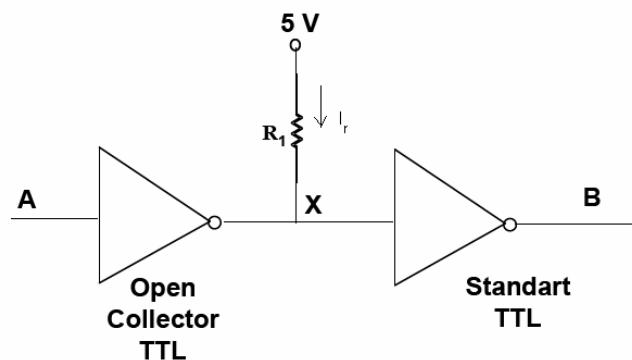


High input and high output ; and LED is off :

$$V_{x\max} = 0.4 \text{ V} ; I_{r\max} = 20 - 2 = 18 \text{ mA}$$

$$R_{1\min} = \frac{(5 - 0.4)V}{18mA} = 255.56 \Omega$$

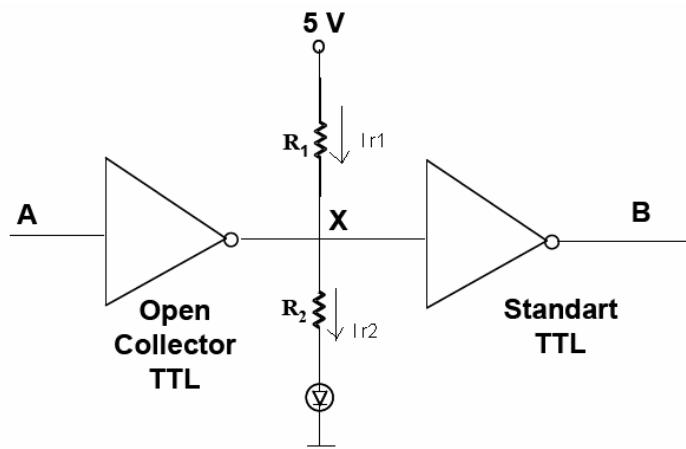b) Low input, output B is low and LED is on :




$$V_x = V_{IH\ min} ; I_{r2} = 1 \text{ mA}$$

For open collector TTL  $I_{OH\max} = 250 \mu\text{A}$  ; for standart TTL  $I_{IH\max} = 250 \mu\text{A}$

$$I_{r2\min} = 1 + 0,25 + 0,25 = 1.5 \text{ mA}$$

$$R_{1\max} = \frac{(5 - 2)V}{1.5 \mu\text{A}} = 2 \text{ k}\Omega$$

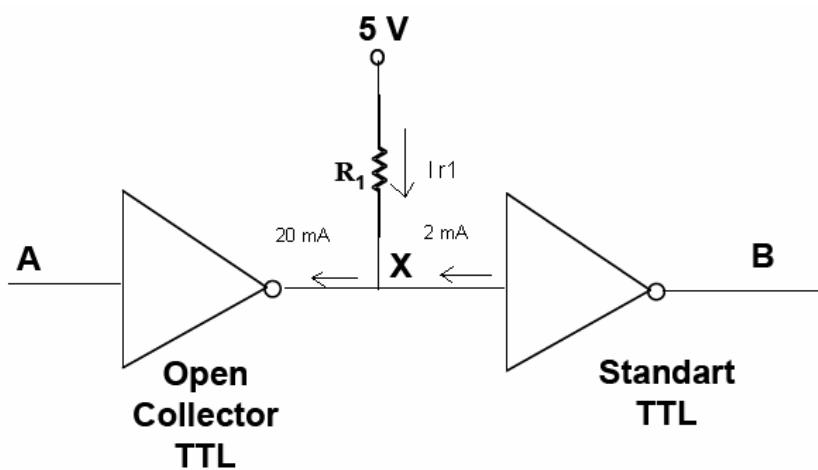c)  $R_1 = 1 \text{ k}\Omega$ ,  $R_2 = 500 \Omega$



**low X case :**

$$V_x = V_{OL\ max} = 0.4 \text{ V} ; I_{r2} = 0 ; I_{OL\max} = 20 \text{ mA} ; I_{IL\max} = -2 \text{ mA}$$


$$I_{r1} = \frac{5 - 0,4}{1000} = 4,6 \text{ mA}$$

$$I_{r1} + N I'_{IL\max} = I_{OL\max}$$

$$4,6 + 2 * N = 20$$

$$\underline{N=7}$$

**High X case :**

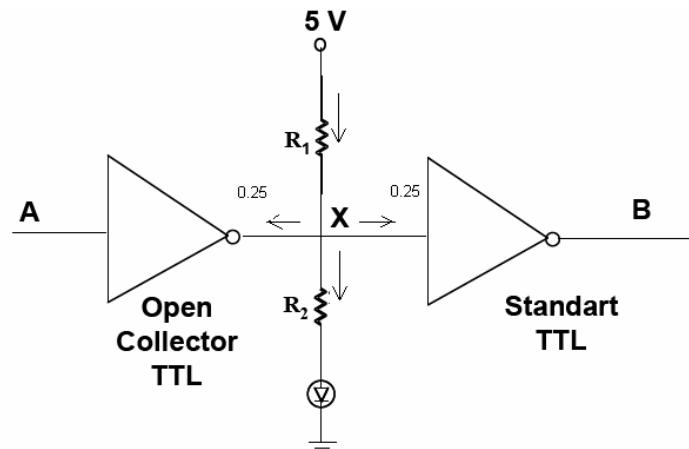


$$I_{r1} = \frac{5 - 2}{1000} = 3 \text{ mA} ; \quad I_{r2} = \frac{2 - 0,9}{500} = 2.2 \text{ mA}$$

$$I_{r1} = 0.25 + N \cdot 0.25 + I_{r2}$$

$$3 = 0.250 + 2.2 + N \cdot 0.25$$

$$\underline{N=2}$$

2)

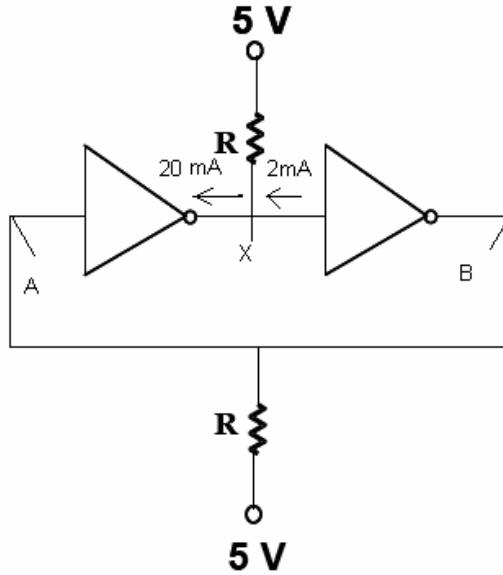

**Case 1 :**

A is high ; X low and B is high.


$$V_{OL\max} = 0.4 \text{ V}$$

$$I_R = I_{OL\max} - I_{IL\max} = 20 - 2 = 18 \text{ mA}$$

$$R \geq \frac{5 - 0.4}{18} = 255,56 \Omega$$

**Case 2 :**

A is low ; X high and B is low.

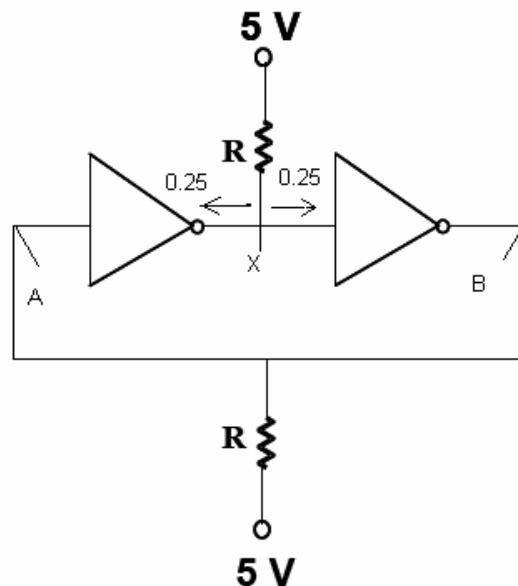

$$I_R = I_{OH\max} + I_{IH\max} = 0.25 + 0.25 = 0.5 \text{ mA}$$

$$V_X = V_{IH\min} = 2 \text{ V}$$

$$R \leq \frac{5 - 2}{0.5} = 6 \text{ k}\Omega$$

Therefore the interval of R should be ;

$$255.56 \Omega \leq R \leq 6000 \Omega$$