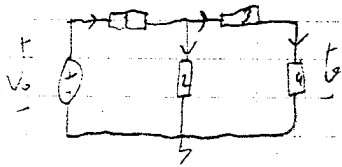


Nth ORDER DYNAMIC CIRCUITS

Review Graph Theoretical Node Analysis




$$A = \begin{bmatrix} 0 & 1 & 2 & 3 & 4 \\ 1 & 1 & 0 & 0 & 0 \\ 0 & -1 & 1 & 1 & 0 \\ 0 & 0 & 0 & -1 & 1 \end{bmatrix} \begin{bmatrix} J_0 \\ J_1 \\ J_2 \\ J_3 \\ J_4 \end{bmatrix} = \begin{bmatrix} 0 \\ 0 \\ 0 \\ 0 \\ 0 \end{bmatrix}$$

$$A \underline{J} = \underline{0}$$

↑
branch current vector


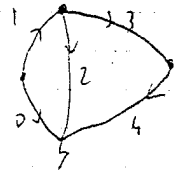
$$\begin{bmatrix} J_0 \\ J_1 \\ J_2 \\ J_3 \\ J_4 \end{bmatrix}$$





$$J_k = ?$$

$$J_k = \frac{V_k}{R_k} \quad \text{for resistors}$$

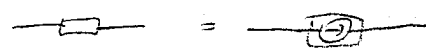
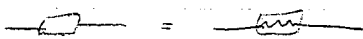
$$J_k = I_s \quad \text{for current sources}$$


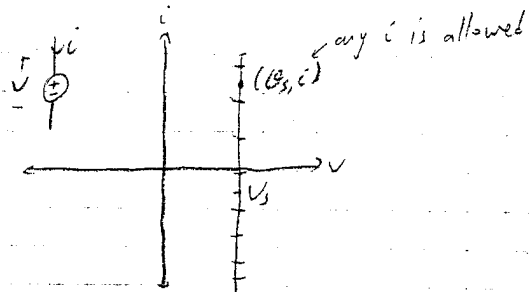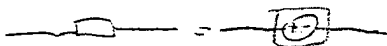
$$J_k = ? \quad \text{for voltage sources}$$



Generalized Branch

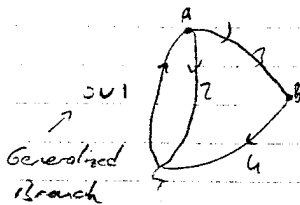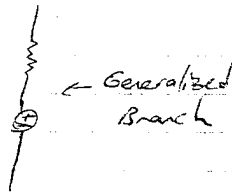

$$A = \begin{bmatrix} -1 & 1 & 1 & 0 \\ 0 & 0 & -1 & 1 \end{bmatrix}$$


$$A \underline{J} = \underline{0} \quad \text{KCL}$$

$$e = \begin{bmatrix} -1 & 0 \\ 1 & 0 \\ 1 & -1 \\ 0 & 1 \end{bmatrix} \begin{bmatrix} e_A \\ e_B \end{bmatrix} = \begin{bmatrix} e_A \\ e_B \\ e_A - e_B \\ e_B \end{bmatrix}$$

$$\underline{J} = \underline{G} \underline{v} \quad \text{Terminal eq}$$

$$\underline{v} = A^T \underline{e}$$


↑ ↑
Branch voltages Node voltages

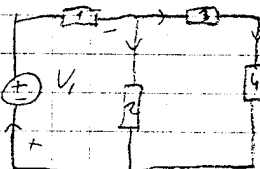


⇒ Insert $\underline{v} = \underline{A}^T \underline{e}$ in other equations.

$$\underline{J} = \underline{G} \underline{v} \Rightarrow \underline{J} = \underline{G} \underline{A}^T \underline{e}$$
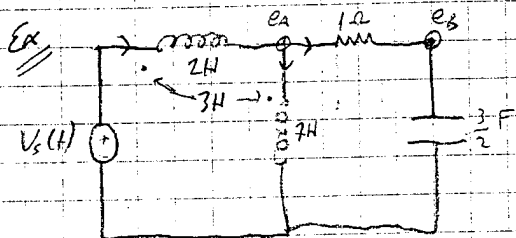
$$\Rightarrow \underline{A} \underline{J} = \underline{A} \underline{G} \underline{A}^T \underline{e} = \underline{0}$$



Graph theoretical node analysis

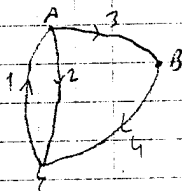

$$\underline{A} = \begin{bmatrix} -1 & 1 & 1 & 0 \\ 0 & 0 & -1 & 1 \end{bmatrix}$$

$$J_3 = \frac{V_3}{1\Omega} = i_3$$

$$J_4 = \frac{3}{2} \frac{dV_4(t)}{dt}$$

$$\begin{bmatrix} V_{2H}(t) \\ V_{7H}(t) \end{bmatrix} = \begin{bmatrix} 2 & 3 \\ 3 & 7 \end{bmatrix} \begin{bmatrix} \frac{d}{dt} i_{2H}(t) \\ \frac{d}{dt} i_{7H}(t) \end{bmatrix} \Rightarrow \begin{bmatrix} V_{2H}(t) \\ V_{7H}(t) \end{bmatrix} = \begin{bmatrix} 2 & 3 \\ 3 & 7 \end{bmatrix} \begin{bmatrix} D i_{2H}(t) \\ D i_{7H}(t) \end{bmatrix}$$

$$\Rightarrow \begin{bmatrix} D i_{2H}(t) \\ D i_{7H}(t) \end{bmatrix} = \frac{1}{5} \begin{bmatrix} 7 & -3 \\ -3 & 2 \end{bmatrix} \begin{bmatrix} V_{2H}(t) \\ V_{7H}(t) \end{bmatrix}$$

→ apply D^{-1} to both sides.

$$D^{-1}(D) i_{2H}(t) = \int_{t_0}^t \frac{1}{5} \begin{bmatrix} 7 & -3 \\ -3 & 2 \end{bmatrix} \begin{bmatrix} V_{2H}(z) \\ V_{7H}(z) \end{bmatrix} dz = i_{2H}(t) - i_{2H}(0)$$

$$L \Delta = 2 \times 7 - 3 \times 3 = 5$$

$$\Rightarrow \begin{bmatrix} i_{2H}(t) - i_{2H}(0) \\ i_{7H}(t) - i_{7H}(0) \end{bmatrix} = \frac{1}{5} \begin{bmatrix} 7 & -3 \\ -3 & 2 \end{bmatrix} \begin{bmatrix} \int_{t_0}^t V_{2H}(z) dz \\ \int_{t_0}^t V_{7H}(z) dz \end{bmatrix}$$

$$\Rightarrow J_1 = i_{2H}(0) + \frac{7}{5} D^{-1} V_{2H}(t) - \frac{3}{5} D^{-1} V_{7H}(t)$$

$$J_2 = i_{7H}(0) - \frac{3}{5} D^{-1} V_{2H}(t) + \frac{2}{5} D^{-1} V_{7H}(t)$$

$$\begin{bmatrix} J_1 \\ J_2 \\ J_3 \\ J_4 \end{bmatrix} = \begin{bmatrix} \frac{7}{5} D^{-1} & -\frac{3}{5} D^{-1} & 0 & 0 \\ -\frac{3}{5} D^{-1} & \frac{2}{5} D^{-1} & 0 & 0 \\ 0 & 0 & 1 & 0 \\ 0 & 0 & 0 & \frac{3}{2} D \end{bmatrix} \begin{bmatrix} v_1 \\ v_2 \\ v_3 \\ v_4 \end{bmatrix} + \begin{bmatrix} i_{2H}(0) \\ i_{7H}(0) \\ 0 \\ 0 \end{bmatrix} + \begin{bmatrix} \frac{7}{5} D^{-1} \\ -\frac{3}{5} D^{-1} \\ 0 \\ 0 \end{bmatrix} v_5(t)$$

$$\underline{J} = \underline{G} \underline{v} + \underline{i}(0) + \underline{v}_5$$

$$\underline{A} \underline{J} = \underline{0} \quad \underline{v} = \underline{A}^T \underline{e}$$

$$\underline{A} \underline{G} \underline{v} + \underline{A} \underline{i}(0) + \underline{A} \underline{v}_5 = \underline{0}$$

$$\underline{A} \underline{G} \underline{A}^T \underline{e} = -\underline{A} (\underline{i}(0) + \underline{v}_5)$$

$$\underline{A} \underline{G} \underline{A}^T \begin{bmatrix} e_a \\ e_b \end{bmatrix} = - \begin{bmatrix} i_{2H}(0) - i_{7H}(0) - 2D^{-1} V_5(t) \\ 0 \end{bmatrix}$$


$$\begin{bmatrix} 3D^{-1} + 1 & -1 \\ -1 & 1 + \frac{D}{2} \end{bmatrix} \begin{bmatrix} e_a \\ e_b \end{bmatrix} = \begin{bmatrix} i_{2H}(0) - i_{7H}(0) + 2D^{-1} V_5(t) \\ 0 \end{bmatrix}$$

← integro-differential equation

Initial Conditions for the solution of Dif. Eqn


$$I_{2H}(0^-) = I_{2H} ; I_{7H}(0^-) = I_{7H} ; V_{\frac{3}{2}F}(0^-) = V_{\frac{3}{2}F}$$

At $t=0^+$

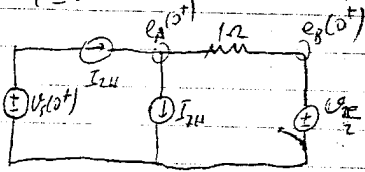

$$e_B(0^+) = V_{\frac{3}{2}F}(0^+)$$
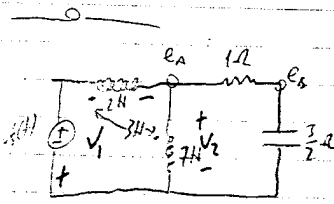
$$e_A(0^+) = e_B(0^+) + i_{2H}(0^-) - i_{7H}(0^-)$$



KCL at e_B :

$$\frac{e_B - e_A}{1} + \frac{3}{2} \frac{d}{dt} e_B(t) = 0 \quad \checkmark$$

KCL at e_A :


$$\frac{e_A - e_B}{1} + i_{7H}(t) - i_{2H}(t) = 0$$

$$\begin{bmatrix} i_{2H}(t) \\ i_{7H}(t) \end{bmatrix} = \begin{bmatrix} 7/5 D^{-1} & -3/5 D^{-1} \\ -3/5 D^{-1} & 2/5 D^{-1} \end{bmatrix} \begin{bmatrix} V_{2H}(t) \\ V_{7H}(t) \end{bmatrix} + \begin{bmatrix} i_{2H}(0^-) \\ i_{7H}(0^-) \end{bmatrix}$$

$$\Rightarrow i_{7H}(t) - i_{2H}(t) = -2D^{-1} V_{2H}(t) + D^{-1} V_{7H}(t) - i_{2H}(0^-) + i_{7H}(0^-)$$

$$= 3D^{-1} e_A - 2D^{-1} V_s(t) - i_{2H}(0^-) + i_{7H}(0^-)$$

Ex (Mesh Analysis)

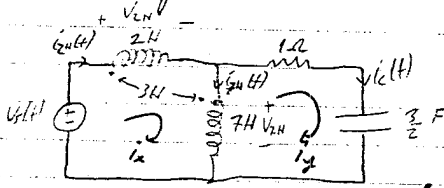

$$\begin{bmatrix} V_{2H}(t) \\ V_{7H}(t) \end{bmatrix} = \begin{bmatrix} 2 & 3 \\ 3 & 7 \end{bmatrix} \begin{bmatrix} \frac{d}{dt} i_x(t) \\ \frac{d}{dt} i_y(t) \end{bmatrix} + \begin{bmatrix} i_x(0^-) \\ i_y(0^-) \end{bmatrix}$$

KVL around i_x

$$-V_s(t) + V_{2H}(t) = V_{7H}(t) = 0$$

$$-V_s(t) + 5 \frac{d}{dt} i_x(t) - 3 \frac{d}{dt} i_y(t) + 10 \frac{d}{dt} i_x(t) - 7 \frac{d}{dt} i_y(t) = 0$$


$$\Rightarrow 15D i_x(t) - 10D i_y(t) = V_s(t)$$

KVL around i_y

$$-V_{7H}(t) + 1 i_y(t) + V_C(t) = 0$$

$$\Rightarrow -10D i_x(t) + 7D i_y(t) + i_y(t) + V_C(0^-) + \frac{2}{3} D^{-1} i_y(t) = 0$$
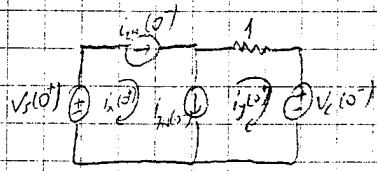
$$\begin{bmatrix} 150 & -100 \\ -100 & 70 + 1 + \frac{2}{3} D^{-1} \end{bmatrix} \begin{bmatrix} i_x(t) \\ i_y(t) \end{bmatrix} = \begin{bmatrix} V_s(t) \\ -V_c(t) \end{bmatrix}$$



$$i_x(0^+) = i_x(0^-)$$


$$i_y(0^+) = i_{2H}(0^-) - i_{2H}(0^-)$$

Modified Node Analysis (MNA):

In MNA, we write eqn.'s s.t. we end up with a differential eqn. instead of a integro-differential equation

To do that

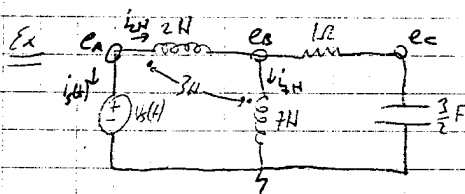
- ① Assign auxiliary variables (other than node voltage variables) for inductors, voltage sources
 - ② Write the KCL equations as in node analysis, use auxiliary variables where necessary
- Write additional equations for auxiliary variables



$$\begin{bmatrix} V_{2H} \\ V_{7H} \end{bmatrix} = \begin{bmatrix} 2 & 3 \\ 3 & 7 \end{bmatrix} \begin{bmatrix} D i_{2H}(t) \\ D i_{7H}(t) \end{bmatrix}$$

$$\begin{array}{l} \text{KCL at } e_A \\ \text{KCL at } e_B \\ \text{KCL at } e_C \end{array} \begin{bmatrix} 0 & 0 & 0 & 1 & 1 & 0 \\ 0 & 1 & -1 & 0 & -1 & 1 \\ 0 & -1 & 1 & 0 & 0 & 0 \\ 1 & 0 & 0 & 0 & 0 & 0 \\ 1 & -1 & 0 & 0 & -2 & -3 \\ 0 & 1 & 0 & 0 & -3 & -1 \end{bmatrix} \begin{bmatrix} e_A(t) \\ e_B(t) \\ e_C(t) \\ i_2(t) \\ i_3(t) \\ i_7(t) \end{bmatrix} = \begin{bmatrix} 0 \\ 0 \\ 0 \\ V_s(t) \\ 0 \\ 0 \end{bmatrix}$$

At $t = 0^+$

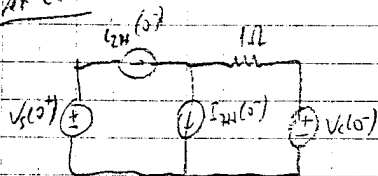

$$e_A(0^+) = V_s(0^+)$$

$$e_C(0^+) = V_c(0^-)$$

$$e_B(0^+) = V_c(0^-) + 1 \cdot (i_{2H}(0^+) - i_{2H}(0^-))$$

$$i_{2H}(0^+) = i_{2H}(0^-)$$

$$i_{2H}(0^+) = i_{2H}(0^-)$$

$$i_3(0^+) = -I_{2H}(0^-)$$

State Equations

$$\dot{x}(t) = \underline{A}x(t) + \underline{B}u(t)$$

Ex

$$\begin{bmatrix} \dot{x}_1(t) \\ \dot{x}_2(t) \end{bmatrix} = \begin{bmatrix} 1 & 2 \\ 5 & 6 \end{bmatrix} \begin{bmatrix} x_1(t) \\ x_2(t) \end{bmatrix} + \begin{bmatrix} 1 \\ 0 \end{bmatrix} u(t) + \begin{bmatrix} 0 \\ 2 \end{bmatrix} i_s(t)$$

$$\begin{bmatrix} 1 & 0 \\ 0 & 2 \end{bmatrix} \begin{bmatrix} v_s(t) \\ i_s(t) \end{bmatrix}$$

1st order matrix diff. eqn.

$$\begin{cases} x_1(0^+) = \dots \\ x_2(0^+) = \dots \end{cases} \text{ given}$$

Solution is by Laplace Transform or eigen-decomposition of \underline{A} through state-transition matrices series expansion.

State variables: { Cap. voltages, Inductor currents }

Steps: 1) Include all voltage sources in tree
all current sources in co-tree

2) Put max. number of possible capacitors in tree (if possible all)
min number of possible inductors in tree (if possible none)


3) If there is a transformer \rightarrow put only 1 (but 1) branch of transformer in tree.

Writing the equations

State variables: All cap. voltages in the tree and all inductor currents in the co-tree are state variables.


i) Write fun-loop for each inductor current in the co-tree (KVL)

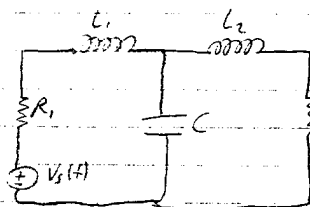ii) Write fun-cutset for each cap voltage in the tree (KCL)



$$\begin{cases} v_c(0^+) \\ i_{L_1}(0^+), i_{L_2}(0^+) \end{cases} \text{ given}$$
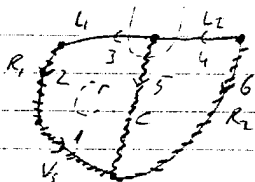
$$\text{State variables} = \{ v_c(t), i_{L_1}(t), i_{L_2}(t) \}$$



$$\text{Order of the circuit} = \# \text{ state-variables} = 3$$

For L_1

$$V_3 + V_2 + V_1 - V_5 = 0$$

$$L_1 \dot{i}_1 + R_1 i_1 + V_3 - V_5 = 0$$

state variable

↳ not a state variable

express i_1 in terms of state variables

write fun-cutset for i_1 branch

$$i_1 = \dot{q}_1 \checkmark$$

$$\dot{q}_1(t) = -\frac{R_1}{L_1} q_1(t) + \frac{1}{L_1} V_3(t) - \frac{V_5(t)}{L_1}$$

For L_2

$$V_2 + V_4 - V_{R_2} = 0$$

$$L_2 \dot{i}_2 + V_4 - R_2 i_2 = 0$$

$-i_2 =$ (fun-cutset)



$$\dot{q}_2(t) = -\frac{V_4(t)}{L_2} - \frac{R_2}{L_2} q_2(t)$$

For C

$$i_c - i_2 + i_1 = 0 \rightarrow \dot{V}_c(t) = -\frac{i_1(t)}{C} + \frac{i_2(t)}{C}$$

$$\begin{bmatrix} \dot{V}_c(t) \\ \dot{q}_1(t) \\ \dot{q}_2(t) \end{bmatrix} = \begin{bmatrix} 0 & -1/C & 1/C \\ 1/C & -R_1/L_1 & 0 \\ -1/L_2 & 0 & -R_2/L_2 \end{bmatrix} \begin{bmatrix} V_c(t) \\ q_1(t) \\ q_2(t) \end{bmatrix} + \begin{bmatrix} 0 \\ -V_3(t) \\ 0 \end{bmatrix}$$

25/02/2010
Persema

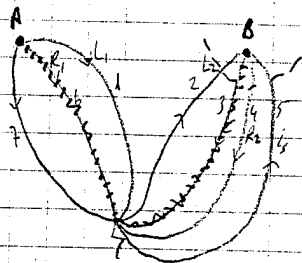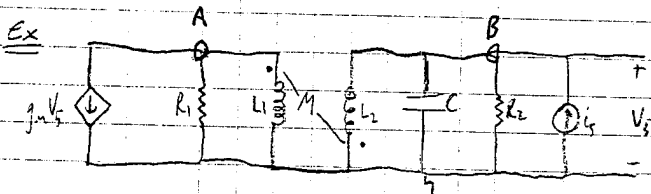

$$\begin{aligned} V_c(0) &= V_0 \\ I_4(0) &= I_0^4 \\ I_{L_2}(0) &= I_0^{L_2} \end{aligned}$$

State eqn:

Fun-cutset of Cap Branch

$$i_3 + i_4 - i_5 - i_2 = 0$$



$$C \dot{V}_c + \frac{V_0}{R_2} - i_5 - i_2 = 0 \rightarrow \dot{V}_c(t) = \frac{i_2(t)}{C} - \frac{V_c(t)}{R_2 C} + \frac{i_5(t)}{C}$$

Fun-loop $\rightarrow V_c = V_4$

$$\begin{bmatrix} \dot{V}_{L_1}(t) \\ \dot{V}_{L_2}(t) \end{bmatrix} = \begin{bmatrix} L_1 & M \\ M & L_2 \end{bmatrix} \begin{bmatrix} \frac{d}{dt} i_{L_1}(t) \\ \frac{d}{dt} i_{L_2}(t) \end{bmatrix}$$

$$\begin{bmatrix} \frac{d}{dt} i_{L_1}(t) \\ \frac{d}{dt} i_{L_2}(t) \end{bmatrix} = \frac{1}{L_1 L_2 - M^2} \begin{bmatrix} L_2 & -M \\ -M & L_1 \end{bmatrix} \begin{bmatrix} V_{L_1} \\ V_{L_2} \end{bmatrix}$$

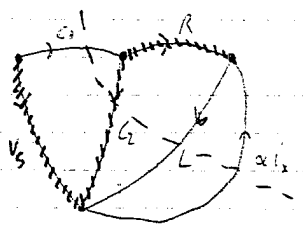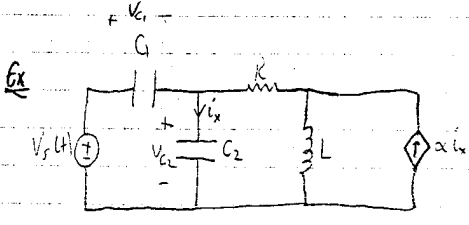$V_{L_1}^{FL} = V_{L_1}^{TE} = i_{L_1} R_1 = R_1 (-g_m V_2 - i_{L_1})$
 $V_{L_2}^{FL} = R_2 (-g_m V_2 - i_{L_2})$
 $V_{L_2}^{FL} = -V_2$



State variables: $\{ V_{C_2}, i_L \}$
 Cap's in tree Ind's in cotree

$$-i_{C_1} + i_{C_2} + i_L - \alpha i_L = 0$$

$$-C_1 \dot{V}_{C_2} + C_2 \dot{V}_{C_2} + i_L - \alpha C_2 \dot{V}_{C_2} = 0$$

$i_{C_1} = -V_2$

$$-C_1 (\dot{V}_s - \dot{V}_{C_2}) + C_2 \dot{V}_{C_2} + i_L - \alpha C_2 \dot{V}_{C_2} = 0$$

$$[C_1 + C_2(1-\alpha)] \dot{V}_{C_2} = -i_L + C_1 \dot{V}_s$$

$$\dot{V}_{C_2}(t) = \frac{-i_L}{C_1 + C_2(1-\alpha)} + \frac{C_1}{C_1 + C_2(1-\alpha)} \dot{V}_s(t)$$

Fun loop for L branch


$$V_L = -V_R + V_{C_2}$$

$$i_L R = (i_L - \alpha i_L) R = (i_L - \alpha C_2 \dot{V}_{C_2}) R$$

From 1st state eqn

$$L \dot{i}_L(t) = -R i_L(t) + R C_2 \alpha \left(\frac{-i_L(t)}{C_1 + C_2(1-\alpha)} + \frac{C_1}{C_1 + C_2(1-\alpha)} \dot{V}_s(t) \right) + V_{C_2}$$

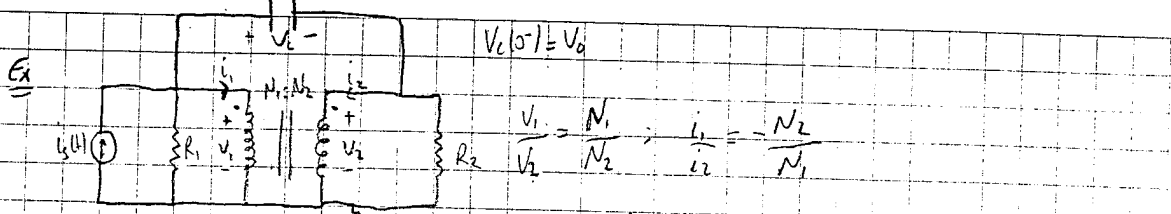
Note: 3 dynamic elements but 2-state variables!!!
 (Capacitive loop)
 (Inductive loop)



$$V_c(t) = V_0$$

$$\frac{v_1}{v_2} = \frac{N_1}{N_2} \quad ; \quad \frac{i_1}{i_2} = -\frac{N_2}{N_1}$$

state variable = $\{v_c\}$

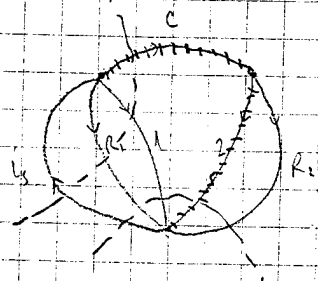

$$C \dot{v}_c = i_2 - i_{R1} - i_c$$

$$\frac{v_1}{v_c} = \frac{N_1}{N_2} \rightarrow \frac{v_c}{v_2} + 1 = \frac{N_1}{N_2}$$

$$i_2 = \left(\frac{N_1}{N_2} + 1 \right)^{-1} v_c = \frac{v_c N_2}{N_1 - N_2}$$

$$v_1 = \frac{v_c N_1}{N_1 - N_2}$$


Fun. Output for 2

$$i_2 = i_s - i_{R1} - i_c - i_{R2}$$

$$i_2 = i_s - \frac{v_1}{R_1} - i_c - \frac{v_2}{R_2} \rightarrow -\frac{N_1}{N_2} i_2 = i_s - \frac{v_c}{R_1} \frac{N_1}{N_1 - N_2} - i_c - \frac{v_c N_2}{R_2 (N_1 - N_2)}$$

$$i_1 = \frac{i_s - \frac{v_c}{N_1 - N_2} \left(\frac{N_1}{R_1} + \frac{N_2}{R_2} \right)}{1 - \frac{N_1}{N_2}}$$


Ex1

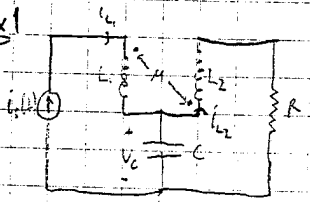

$$\begin{bmatrix} \dot{v}_c \\ \dot{i}_R \end{bmatrix} = \begin{bmatrix} 0 & 1/C \\ -1/C & -R/C \end{bmatrix} \begin{bmatrix} v_c \\ i_R \end{bmatrix} + \begin{bmatrix} 1/C \\ 0 \end{bmatrix} i_s + \begin{bmatrix} 0 \\ 1/C \end{bmatrix} i_s(t)$$

Verify the state equation


Ex2

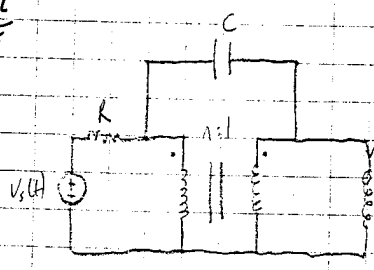

$$\begin{bmatrix} \dot{v}_c \\ \dot{i}_L \end{bmatrix} = \begin{bmatrix} -\frac{1}{RC} & -\frac{1}{C} \\ \frac{1}{L} & 0 \end{bmatrix} \begin{bmatrix} v_c \\ i_L \end{bmatrix} + \begin{bmatrix} \frac{1}{RC} + \frac{1}{RC} \\ 0 \end{bmatrix} v_s(t)$$

1st order matrix diff. eqn. with constant coef.

Ex1

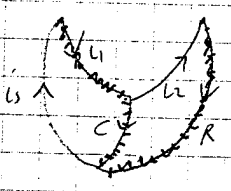

State variables: $\{v_c, i_L\}$

$$i_c = i_s - i_L$$

$$C \dot{v}_c = i_s - i_L$$

$$\dot{v}_c = \frac{i_s}{C} - \frac{i_L}{C}$$


$$v_L = v_c - v_R = M i_L + L \dot{i}_L$$

$$\Rightarrow L \dot{i}_L = v_c - v_R - M i_L$$

$$\dot{i}_L = \frac{v_c}{L} - \frac{R}{L} i_L - \frac{M}{L} i_s$$

$$\begin{bmatrix} \dot{V}_c \\ \dot{i}_L \end{bmatrix} = \begin{bmatrix} 0 & -\frac{1}{C} \\ \frac{1}{L} & -\frac{R}{L} \end{bmatrix} \begin{bmatrix} V_c \\ i_L \end{bmatrix} + \begin{bmatrix} \frac{1}{C} \\ 0 \end{bmatrix} V_s + \begin{bmatrix} 0 \\ -\frac{M}{L} \end{bmatrix} i_s$$

Ex 2

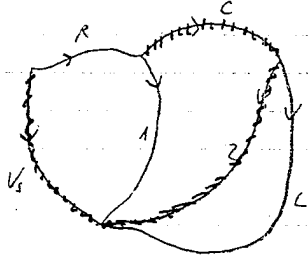

State variables: $\{V_c, i_L\}$

$$\frac{V_1}{V_2} = n \quad \frac{i_1}{i_2} = -\frac{1}{n}$$

$$V_2 = V_L = L \dot{i}_L = V_s - V_R - V_c = nL \dot{i}_L - V_c$$

$$V_1 = nL \dot{i}_L$$

$$V_R = V_s - nL \dot{i}_L$$

$$i_c = C \dot{V}_c - i_L \Rightarrow i_L = \frac{i_c - C \dot{V}_c}{n}$$

$$i_c = i_L - i_L$$

$$C \dot{V}_c = \frac{V_s - nL \dot{i}_L}{R} - \frac{i_c - C \dot{V}_c}{n}$$

$$V_c = V_2$$

$$C \dot{V}_c \left(\frac{n-1}{n} \right) = \frac{V_s}{R} - \frac{nL \dot{i}_L}{R} - \frac{i_c}{n}$$

$$L \dot{i}_L = nL \dot{i}_L - V_c$$

$$\dot{V}_c = \frac{n V_s}{(n-1)RC} - \frac{n^2 L \dot{i}_L}{RC(n-1)} - \frac{i_c}{C(n-1)}$$


$$i_L = \frac{V_c}{L(n-1)}$$

$$\dot{V}_c = \frac{1}{(n-1)RC} V_s - \frac{n^2 V_c}{RC(n-1)^2} - \frac{i_c}{C(n-1)}$$

$$\begin{bmatrix} \dot{V}_c \\ \dot{i}_L \end{bmatrix} = \begin{bmatrix} -\frac{n^2}{(n-1)^2 RC} & -\frac{1}{C(n-1)} \\ \frac{1}{(n-1)L} & 0 \end{bmatrix} \begin{bmatrix} V_c \\ i_L \end{bmatrix} + \begin{bmatrix} \frac{1}{(n-1)RC} \\ 0 \end{bmatrix} V_s$$

Linearity, Time-Invariance

A dynamic system is linear if

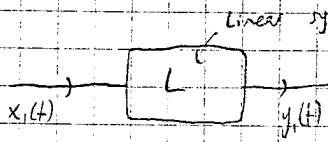

$$y_1(t) = \mathcal{L}\{x_1(t)\}, \quad y_2(t) = \mathcal{L}\{x_2(t)\}$$

Then;






$$\textcircled{1} \mathcal{L}\{\alpha x_1(t)\} = \alpha y_1(t)$$

$$\textcircled{2} \mathcal{L}\{x_1(t) + x_2(t)\} = \mathcal{L}\{x_1(t)\} + \mathcal{L}\{x_2(t)\} = y_1(t) + y_2(t)$$

} \mathcal{L} is a linear system

(superposition principle applies)


Time Invariance

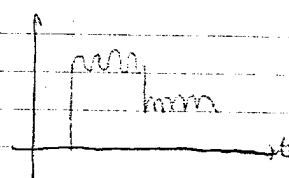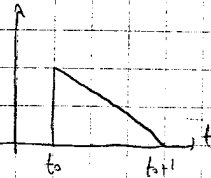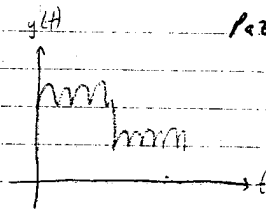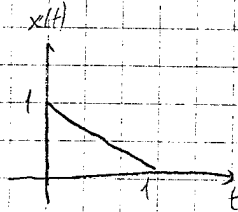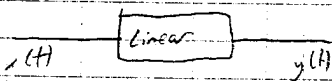

01/03/2010
Pezartesi

If output is also shifted \rightarrow system is time-invariant.

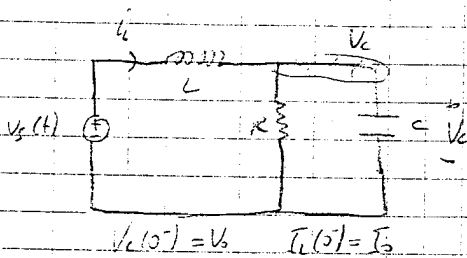Application: R, L, C \rightarrow LTI components



Node analysis

$$i_L(t) = \frac{1}{L} \int v_s(t) - v_c(t) dt$$


$$C \dot{v}_c + \frac{v_c}{R} - i_L = 0$$

$$C \dot{v}_c + \frac{v_c}{R} - \frac{v_s(t) - v_c(t)}{L} = 0$$

$$\left(D^2 + \frac{1}{RC} D + \frac{1}{LC} \right) v_c(t) = \frac{v_s(t)}{LC}$$

$$v_c(0^+) = v_s \quad v_c'(0^+) = ?$$

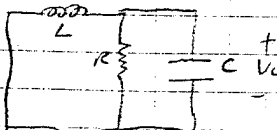Let's focus on $v_c(t) = 0$ (zero-input solution)




$$v_c(0^+) = v_s$$

$$i_L(0^+) = I_0$$

$$\left(D^2 + \frac{1}{RC} D + \frac{1}{LC} \right) v_c(t) = 0$$

$$v_c(0^+) = v_s$$



$$v_c'(0^+) = ?$$

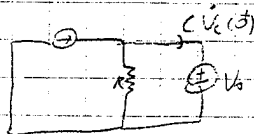

$$i_L(0^+) = I_0 - \frac{v_s}{R} = C \dot{v}_c(0^+)$$

$$\dot{v}_c(0^+) = \frac{I_0 - v_s/R}{C}$$

State eqn:

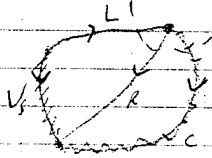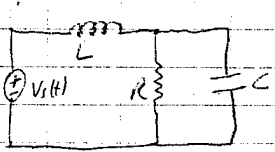

$$C \dot{V}_C = -\frac{V_C}{R} + I_L$$

$$L \dot{I}_L = V_s(t) - V_C(t)$$

$$\begin{bmatrix} \dot{V}_C(t) \\ \dot{I}_L(t) \end{bmatrix} = \begin{bmatrix} -\frac{1}{RC} & \frac{1}{C} \\ -\frac{1}{L} & 0 \end{bmatrix} \begin{bmatrix} V_C(t) \\ I_L(t) \end{bmatrix} + \begin{bmatrix} 0 \\ \frac{1}{L} \end{bmatrix} V_s(t)$$

1st order matrix diff eqn. is equivalent to 2nd order scalar diff. eqn?

Take another derivative of $V_C(t)$ equation:

Note: when using state equations

$$\ddot{V}_C(t) = -\frac{1}{RC} \dot{V}_C + \frac{1}{C} \left(\dot{I}_L \leftarrow \frac{V_s(t)}{L} - \frac{V_C(t)}{L} \right)$$

initial conditions are already given!

No need to calculate them from 0⁺ analysis.

$$D^2 V_C = -\frac{1}{RC} D V_C - \frac{1}{LC} V_C + \frac{1}{LC} V_s(t)$$

$$\left(D^2 + \frac{10}{RC} D + \frac{1}{LC} \right) V_C = \frac{1}{LC} V_s(t) \rightarrow \text{Same equation, we get from node analysis}$$

Solution of 2nd order scalar diff. eqn.

$$R = \frac{1}{3}, C = 1, L = \frac{1}{2}$$

$$\begin{aligned} (D^2 + 3D + 2) V_C(t) &= 0 && \text{(still no input)} \\ V_C(0) &= V_0 \\ \dot{V}_C(0) &= I_0 - 3V_0 \end{aligned}$$

$$V_C(t) = c e^{\lambda t} \quad \begin{array}{l} c: \text{constant} \leftarrow \text{I don't know them!} \\ \lambda: \text{constant} \end{array}$$

substitute the guess into diff eqn.

$$(D^2 + 3D + 2) c e^{\lambda t} = 0 \leftarrow \text{df terms}$$

$$(\lambda^2 + 3\lambda + 2) c e^{\lambda t} = 0$$

$$\begin{array}{l} c = 0 \\ \downarrow \\ \text{trivial solution} \end{array} \quad \begin{array}{l} c \neq 0 \\ \lambda^2 + 3\lambda + 2 = 0 \\ \lambda = \{-1, -2\} \end{array} \Rightarrow V_C(t) = \{e^{-t}, e^{-2t}\} = \alpha e^{-t} + \beta e^{-2t}$$

\uparrow a mode of the circuit.
 \uparrow zero input response
 \uparrow superposition of two modes.

$$V_C(t) = \underbrace{\alpha e^{-t}}_{\text{homogeneous}} + \underbrace{\beta e^{-2t} + \gamma e^{-2t}}_{\text{particular}} \quad \text{or is one mode excitation? nasil olurdu?}$$

(08/03/2010) *6

How do you excite only 1 mode?

$$V_c(0) = V_0$$

$$I_c(0) = I_0 - 3V_0$$

$$V_c(t) = \alpha e^{-t} + \beta e^{-2t} \Big|_{t=0} \rightarrow V_0 = \alpha + \beta$$

$$I_c(t) = -\alpha e^{-t} - 2\beta e^{-2t} \Big|_{t=0} \rightarrow I_0 - 3V_0 = -\alpha - 2\beta$$

Two single modes $\alpha \neq 0, \beta = 0 \rightarrow V_0 = \alpha$

$$V_0 = 1 \text{ V}$$

$$I_0 = 2 \text{ A}$$

$$V_c(t) = e^{-t} (\alpha=1, \beta=0)$$

$$I_0 - 3V_0 = -\alpha \Rightarrow I_0 = 2 \text{ A}$$

To excite the other mode $\alpha = 0, \beta \neq 0$

$$\left. \begin{array}{l} V_0 = \beta \\ I_0 = -2\beta \end{array} \right\} V_c(t) = \beta e^{-2t}$$

Natural frequencies Roots of characteristic eqn. are called natural freq (λ_1, λ_2)

Natural Response When we have zero-input response, \rightarrow natural response.

Mode: Individual components of natural response

$$\begin{bmatrix} V_c(t) \\ I_c(t) \end{bmatrix} = \begin{bmatrix} -3 & 1 \\ -2 & 0 \end{bmatrix} \begin{bmatrix} V_c(t) \\ I_c(t) \end{bmatrix} \quad V_c(0) = V_0; I_c(0) = I_0$$

$$\dot{x}(t) = \underline{A}x(t); x(0) = x_0$$

$$x(t) = \begin{bmatrix} c_1 \\ c_2 \end{bmatrix} e^{\lambda t} \Rightarrow \lambda \underline{I} \begin{bmatrix} c_1 \\ c_2 \end{bmatrix} e^{\lambda t} = \underline{A} \begin{bmatrix} c_1 \\ c_2 \end{bmatrix} e^{\lambda t}$$

$$(\lambda \underline{I} - \underline{A}) \begin{bmatrix} c_1 \\ c_2 \end{bmatrix} = \underline{0}$$

$$\begin{bmatrix} c_1 \\ c_2 \end{bmatrix} = \begin{bmatrix} 0 \\ 0 \end{bmatrix}$$

trivial

$$\begin{bmatrix} c_1 \\ c_2 \end{bmatrix} \neq \underline{0}$$

is not invertible

$$\Rightarrow \boxed{\det(\lambda \underline{I} - \underline{A}) = 0}$$

Remember $\det(\lambda \underline{I} - \underline{A})$ is called characteristic polynomial

Roots of $|\lambda \underline{I} - \underline{A}| = 0$ are the eigenvalues of \underline{A} matrix

$$|\lambda \underline{I} - \underline{A}| = \begin{vmatrix} \lambda + 3 & -1 \\ 2 & \lambda \end{vmatrix} = \lambda(\lambda + 3) + 2 = \lambda^2 + 3\lambda + 2$$

char eqn.

then natural freq. are the roots of

$$\lambda^2 + 3\lambda + 2 = 0 \Rightarrow \lambda = \{-1, -2\}$$

$$x(t) = \left\{ \begin{bmatrix} a \\ c_1 \end{bmatrix} e^{-t}, \begin{bmatrix} d_1 \\ d_2 \end{bmatrix} e^{-2t} \right\}$$

$$x(t) = c e^{\lambda_1 t} + d e^{\lambda_2 t}, \quad \lambda_1 = -1, \lambda_2 = -2$$

$$\dot{x}(t) = \underline{A} x(t)$$

$$\Rightarrow \dot{x}(t) = c \lambda_1 e^{\lambda_1 t} + d \lambda_2 e^{\lambda_2 t}$$

$$x(t) = \underline{A} x(t) \rightarrow c \lambda_1 e^{\lambda_1 t} + d \lambda_2 e^{\lambda_2 t} = \underline{A} (c e^{\lambda_1 t} + d e^{\lambda_2 t})$$

to excite $e^{\lambda_1 t}$ mode $d = 0$

$$c \lambda_1 e^{\lambda_1 t} + 0 = \underline{A} c e^{\lambda_1 t} + 0$$

$$\Rightarrow \underline{A} c = \lambda_1 c$$

To excite a single mode or mode with nat. freq. λ_1 , $V_c(0)$, $I_L(0)$ should be the eigenvector of \underline{A} corresponding to λ_1 .

A matrix of state eqs. is fundamental for analysis; since its eigenvalues are the natural frequencies the eigenvectors of A are the required initial conditions to excite a mode.


To excite $\lambda_1 = -1$ natural freq;

$$\begin{bmatrix} -3 & 1 \\ -2 & 0 \end{bmatrix} e_1 = \lambda_1 e_1$$

$$\Rightarrow (\lambda_1 \underline{I} - \underline{A}) e_1 = 0 \Rightarrow \begin{bmatrix} \lambda_1 + 3 & -1 \\ 2 & \lambda_1 \end{bmatrix} \begin{bmatrix} \alpha \\ \beta \end{bmatrix} = 0 \Rightarrow \lambda_1 = -1 \rightarrow \begin{bmatrix} 2 & -1 \\ 2 & -1 \end{bmatrix} \begin{bmatrix} \alpha \\ \beta \end{bmatrix} = 0$$

$$\begin{bmatrix} \alpha \\ \beta \end{bmatrix} = \begin{bmatrix} 1 \\ 2 \end{bmatrix} k \leftarrow \text{any number} \Rightarrow \begin{bmatrix} V_c(0) \\ I_L(0) \end{bmatrix} = \begin{bmatrix} 1 \\ 2 \end{bmatrix} k \rightarrow \text{excites } e^{-t} \text{ mode.}$$

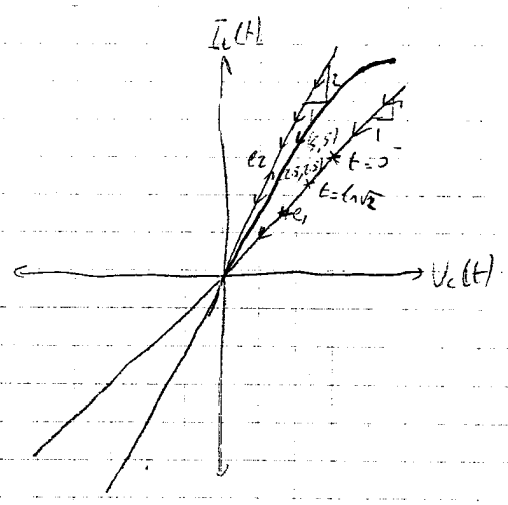
$$\lambda_1 = -2 \rightarrow \begin{bmatrix} 1 & -1 \\ 2 & -2 \end{bmatrix} \begin{bmatrix} \alpha \\ \beta \end{bmatrix} = \begin{bmatrix} 0 \\ 0 \end{bmatrix} \Rightarrow \text{eigen vector} = \begin{bmatrix} 1 \\ 1 \end{bmatrix} \Rightarrow \begin{bmatrix} V_c(0) \\ I_L(0) \end{bmatrix} = \begin{bmatrix} 1 \\ 1 \end{bmatrix} k \text{ excites } e^{-2t} \text{ mode}$$



$$x(t) = \begin{bmatrix} 5 \\ 5 \end{bmatrix} e^{-2t}$$

COMPLEX EXPONENTIAL FUNCTION

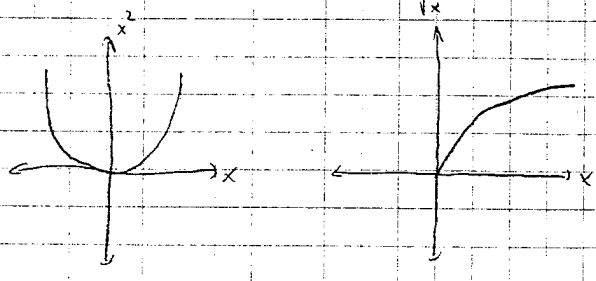
$f(x) : \text{Domain} \rightarrow \text{Range}$
 ↑
 an interval
 $(a, b), (-\infty, \infty)$
 ↓
 real numbers



$$f(x) = e^x = \sum_{k=0}^{\infty} \frac{x^k}{k!} \quad x \in \mathbb{R}$$

$z \Rightarrow z \in \mathbb{C} \leftarrow \text{complex field}$
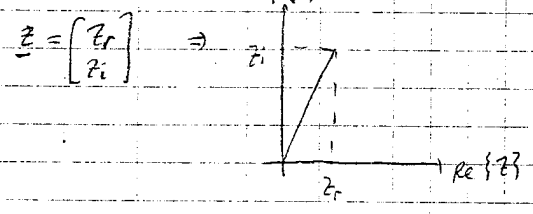
$$z = z_r + j z_i \quad \begin{matrix} z_r \in \mathbb{R} \\ z_i \in \mathbb{R} \end{matrix} \quad \begin{matrix} j^2 = -1 \\ j = \sqrt{-1} \end{matrix}$$




$$f(z) = e^z = \sum_{k=0}^{\infty} \frac{z^k}{k!} \quad , z \in \mathbb{C} \leftarrow \text{whole complex plane}$$


$f(z) : z \in \mathbb{C} \rightarrow \mathbb{C}$

- $\hookrightarrow z$: purely real and positive ($z = z$)
- $\hookrightarrow z$: purely real and negative ($z = -z$)
- $\hookrightarrow z$: purely imaginary ($z = jZ$)
- $\hookrightarrow z$: complex valued ($z = 1 + jZ$)

① Purely Real, positive valued.

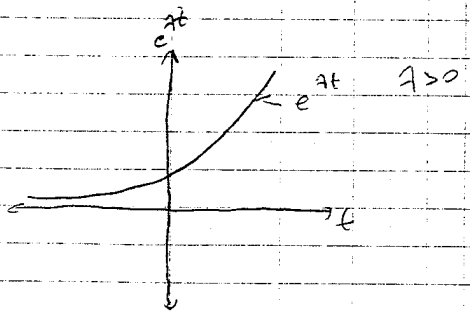

② Purely Real and negative valued.

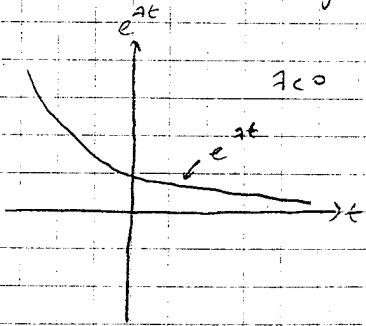

③ Purely Imaginary

$$f(t) = e^{j\omega t} \quad \begin{matrix} \leftarrow t \in \mathbb{R} \\ \leftarrow \omega \in \mathbb{R} \end{matrix}$$

$$e^{j\phi} = \sum_{k=0}^{\infty} \frac{(j\phi)^k}{k!} = \sum_{\substack{k \in \text{even} \\ \text{integers} \\ (k \geq 0)}} \frac{(j\phi)^k}{k!} + \sum_{\substack{k \in \text{odd} \\ \text{integers} \\ (k \geq 0)}} \frac{(j\phi)^k}{k!} = \sum_{l=0}^{\infty} \frac{(j\phi)^{2l}}{(2l)!} + \sum_{l=0}^{\infty} \frac{(j\phi)^{2l+1}}{(2l+1)!}$$

$$= \sum_{l=0}^{\infty} \frac{(j^2)^l \phi^{2l}}{(2l)!} + j \sum_{l=0}^{\infty} \frac{(j)^{2l+1} \phi^{2l+1}}{(2l+1)!} = \sum_{l=0}^{\infty} \frac{(-1)^l \phi^{2l}}{(2l)!} + j \sum_{l=0}^{\infty} \frac{(-1)^l \phi^{2l+1}}{(2l+1)!} = \cos \phi + j \sin \phi$$


$$\Rightarrow \boxed{e^{j\phi} = \cos \phi + j \sin \phi} \quad \text{Euler's Formula}$$

$$e^{jA} \cdot e^{jB} = e^{j(A+B)} = \cos(A+B) + j \sin(A+B)$$

$$(\cos A + j \sin A)(\cos B + j \sin B)$$

$$= (\cos A \cos B - \sin A \sin B) + j(\cos A \sin B + \sin A \cos B)$$
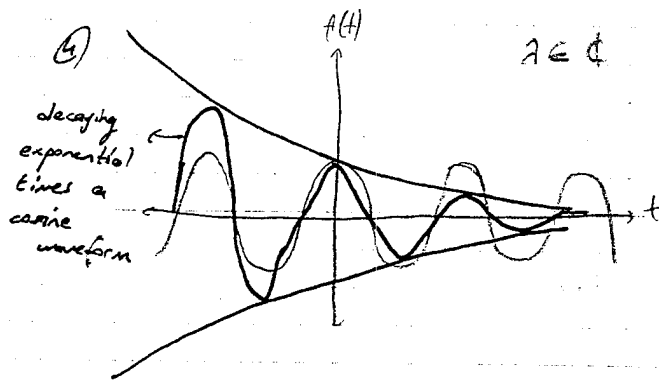
$$\underline{\text{Ex}} \quad \sum_{k=0}^{N-1} \cos(\omega k) = \cos(\omega N) \quad (\text{Hint: } \cos(\omega k) = \text{Re} \{ e^{j\omega k} \})$$



$$f(t) = e^{At} = e^{\text{Re}\{A\}t} \cdot e^{j\text{Im}\{A\}t}$$

$$\text{Re}\{A\} < 0 \\ \text{Re} \{ e^{At} \} = \text{Re} \{ e^{j\text{Im}\{A\}t} \} = \cos(\text{Im}\{A\}t)$$

STABILITY OF LTI SYSTEMS

Stability refers to keeping current, voltage of each branch bounded (not infinite, finite) through circuit components.

$$|V_L(t)| < M$$

$$\forall t$$

$$|I_L(t)| < N$$


① Zero-Input (No input)

② Stability concept with inputs (later)

① Stability for zero input case

$$(D^2 + 3D + 2)V_c(t) = 0 \quad V_c(0) = 5$$

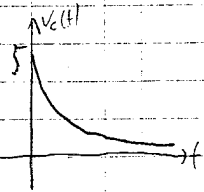Since natural freq. ($s^2 + 3s + 2 = 0$, $\lambda_{1,2} = \{-1, -2\}$) are negative valued term.



Then given any initial condition if each state goes to zero as $t \rightarrow \infty$;


then such a system is called asymptotically stable, (stable)

Note: There are more than one stability definitions such as exponentially stable, asymptotically stable, Lyapunov stability, etc.

For LTI systems all stability definitions converge to the same condition.

Then LTI stable systems \iff Natural freq. have negative valued real parts.

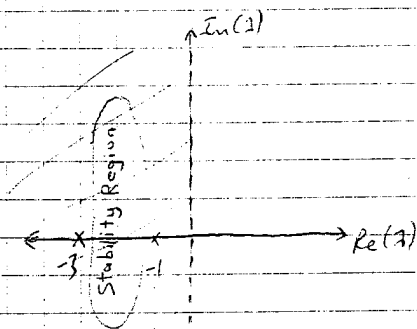Natural freq.: roots of char eq. (eigenvalues of A)



λ : natural freq of a system
(x: show a natural freq)

Solution of Dynamic System WITH INPUTS

Particular Solution of DE's:

$$(D^2 + 3D + 2)x(t) = f(t) \quad \leftarrow \begin{array}{l} \text{forcing term} \\ \text{(external input)} \end{array}$$

$f(t) = e^{st}$ (We limit our interest to exponential inputs. Later we will use more powerful

techniques covering more function types)

$$\text{Ex } (D^2 + 3D + 2)x(t) = e^{st}$$

Guessing method
 $x_p(t) = Ae^{st}$

$$A(s^2 + 3s + 2)e^{st} = e^{st} \implies A = \frac{1}{s^2 + 3s + 2} \quad \text{provided that } s^2 + 3s + 2 \neq 0 \quad (s \neq \text{natural freq.})$$

Ex $s = -3$

$$(D^2 + 3D + 2)x_p(t) = e^{-3t} \Rightarrow x_p(t) = Ae^{-3t} = \frac{1}{2}e^{-3t} \leftarrow \text{particular solution}$$

$$\Rightarrow x_{\text{complete}}(t) = x_p(t) + x_h(t)$$

$$= \frac{1}{2}e^{-3t} + C_1e^{s_1 t} + C_2e^{s_2 t} \quad \{s_1, s_2: \text{natural freq}\}$$

General \rightarrow for input e^{st}

\downarrow

$$x_{\text{complete}}(t) = \frac{1}{s^2 + 3s + 2} e^{st} + C_1e^{s_1 t} + C_2e^{s_2 t}$$

for DC input $f(t) = 1 \rightarrow s = 0$

for AC input $f(t) = \cos t \rightarrow s = j \rightarrow \text{Re}\{x_{\text{complete}}(t)\} \Big|_{s=j}$

Important Remark

For stable systems as $t \rightarrow \infty$; the zero-input solution goes to zero and in the complete response we are left with zero-state solution.

Then if input is in the form e^{st}

\downarrow

for LTI systems the particular solution is also an complex exponential with the same exponent

For N^{th} order systems, the changes are the following

$$(D^N + a_1 D^{N-1} + a_2 D^{N-2} + \dots + a_N) x(t) = f(t)$$

① Characteristic Polynomial = $A^N + a_1 A^{N-1} + \dots + a_N = 0$

(N natural freq. (can be complex valued))

② Particular solution for $f(t) = e^{st}$;

$$\text{The } x_p(t) = \frac{1}{s^N + a_1 s^{N-1} + \dots + a_N} e^{st} \quad s \notin \{\text{natural freq}\}$$


State Eqn's are favorite tool for analysis.

MNA, NA, Mesh Analysis: (Require more number of equation and initial conditions of LTI equation has to be found and integra-differential)

$$\dot{x}(t) = Ax(t) + u(t)$$

Particular Solution of N^{th} Diff. Eqn. (cont'd)

$$(D^2 + 3D + 2) V_c(t) = 2V_s(t)$$

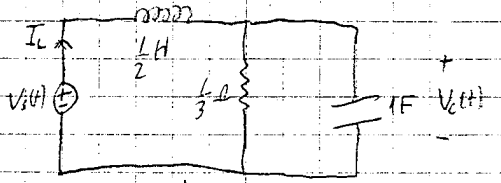

$$V_c(0^-) = V_s$$

$$I_L(0^-) = I_s$$

$$V^{\text{complete}}(t) = V^h(t) + V^p(t) \leftarrow \text{(input determined depends on } V_s(t))$$

↑
system determined (natural frequencies)

Homogeneous: $(D^2 + 3D + 2) V_c^h(t) = 0 \rightarrow \lambda^2 + 3\lambda + 2 = 0 \rightarrow V_c^h(t) = c_1 e^{\lambda_1 t} + c_2 e^{\lambda_2 t}$

$$\lambda_{1,2} = \{-1, -2\}$$

↑
natural

freq.

Particular: Assume exponential input, $V_s(t) = e^{st} \rightarrow s \in \mathbb{C}$

Guess: $V_c^p(t) = A e^{st}$

↑
unknown

Substitute the guess into diff. eqn. to find A.

$$(D^2 + 3D + 2) V_c^p(t) = 2e^{st}$$

$$(s^2 + 3s + 2) A e^{st} = 2e^{st} \rightarrow A = \frac{2}{s^2 + 3s + 2} \quad s \neq \{-1, -2\}$$

Case 1 $V_s(t) = e^{-5t}$, $V_c^p(t) = A e^{-5t}$

↑
A is unknown
real variable

Substitute the guess and proceed similarly.

$$(D^2 + 3D + 2) A e^{-5t} = 2e^{-5t}$$

$$A(D^2 e^{-5t} + 3D e^{-5t} + 2e^{-5t}) = 2e^{-5t}$$


$$A(25 + 15 + 2)e^{-5t} = 2e^{-5t} \rightarrow A = \frac{2}{12} = \frac{1}{6}$$

* 21.03.2010 Parabatesi

$$V^{\text{complete}}(t) = \underbrace{c_1 e^{-t} + c_2 e^{-2t}}_{\text{homogeneous (natural response)}} + \underbrace{\frac{1}{6} e^{-5t}}_{\text{particular}}$$

transient: the remaining part in the complete response apart from steady state.

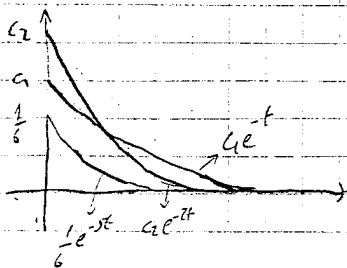Steady state: part of complete response as $t \rightarrow \infty$.




Case (2) $V_c(t) = V = e^{st} \Big|_{s=0}$

$V_c'(t) = Ae^{st} \Big|_{s=0} = A$

$(0^2 + 30 + 2)V_c'(t) = 2 \Rightarrow 2A = 2 \Rightarrow A = 1$


$V_c'(t) = 1$

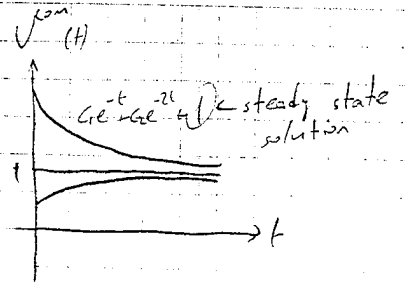

Method

For exponential inputs to find particular solution, we make the guess of Ae^{st} then find A.

A 2nd approach

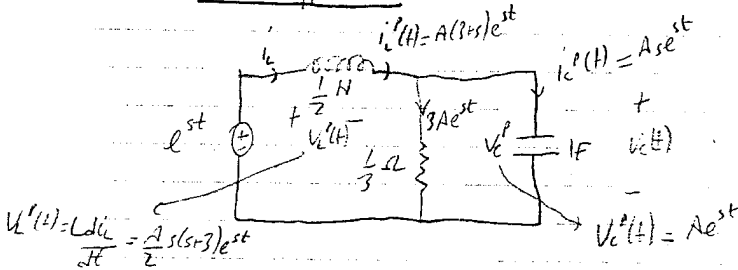

To find A from circuit write KVL

$e^{st} = V_L'(t) + V_C'(t)$

$e^{st} = \frac{A}{2}(s+3)e^{st} + Ae^{st}$

$e^{st} = \frac{A}{2}(s^2 + 3s + 2)e^{st} \Rightarrow A = \frac{2}{s^2 + 3s + 2}$

Case (3)

$V_c(t) = \cos(5t)$

$(0^2 + 30 + 2)V_c'(t) = 2 \cos(5t) \quad V_c'(t) = A \cos(5t) + B \sin(5t)$

$\cos(5t)[2A + 15B - 25A] + \sin(5t)[2B - 15A - 25B] = 2 \cos 5t$

$\begin{bmatrix} -23 & 15 \\ -15 & -23 \end{bmatrix} \begin{bmatrix} A \\ B \end{bmatrix} = \begin{bmatrix} 2 \\ 0 \end{bmatrix} \Rightarrow \begin{bmatrix} A \\ B \end{bmatrix} = \frac{1}{23^2 + 15^2} \begin{bmatrix} -23 & -15 \\ 15 & -23 \end{bmatrix} \begin{bmatrix} 2 \\ 0 \end{bmatrix} \Rightarrow \begin{bmatrix} A \\ B \end{bmatrix} = \begin{bmatrix} \frac{-46}{23^2 + 15^2} \\ \frac{30}{23^2 + 15^2} \end{bmatrix}$

$V_c'(t) = \frac{-46}{23^2 + 15^2} \cos(5t) + \frac{30}{23^2 + 15^2} \sin(5t)$

Case 3: A better Approach

$$V_c(t) = \cos 5t = \operatorname{Re} \{ e^{j5t} \}$$

$$(D^2 + 3D + 2)V_c'(t) = 2 \operatorname{Re} \{ e^{j5t} \}$$

$$V_c'(t) = \operatorname{Re} \{ A_c e^{j5t} \} \quad \text{Ac: complex-valued unknown}$$

↳

$$\frac{d}{dt} V_c'(t) = \frac{d}{dt} \operatorname{Re} \{ A_c e^{j5t} \} = \operatorname{Re} \left\{ \frac{d}{dt} A_c e^{j5t} \right\} = \operatorname{Re} \{ j5 A_c e^{j5t} \}$$

$$\int \frac{d^2}{dt^2} V_c'(t) = \operatorname{Re} \{ (j5)^2 A_c e^{j5t} \}$$

↳ the substitution;

$$D^2 V_c'(t) + 3D V_c'(t) + 2V_c'(t) = \operatorname{Re} \{ 2e^{j5t} \}$$

$$\operatorname{Re} \{ (j5)^2 A_c e^{j5t} \} + \operatorname{Re} \{ j15 A_c e^{j5t} \} + \operatorname{Re} \{ 2 A_c e^{j5t} \} = \operatorname{Re} \{ 2e^{j5t} \}$$


$$\operatorname{Re} \{ A_c ((j5)^2 + 3(j5) + 2) e^{j5t} \} = \operatorname{Re} \{ 2e^{j5t} \}$$

$$A_c = \frac{2}{(j5)^2 + 3(j5) + 2} = \frac{2}{-25 + j15 + 2} = \frac{2}{-23 + j15} = \frac{2(-23 - j15)}{23^2 + 15^2}$$

$$V_c'(t) = \operatorname{Re} \left\{ \frac{2(-23 - j15)}{23^2 + 15^2} e^{j5t} \right\} = \frac{-2}{23^2 + 15^2} \operatorname{Re} \{ (23 + j15)(\cos 5t + j \sin 5t) \}$$


$$= \frac{-2}{23^2 + 15^2} (23 \cos 5t - 15 \sin 5t)$$

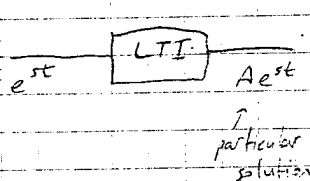Exponential functions are the "eigenfunction" of an LTI dynamic system



More on this at other courses

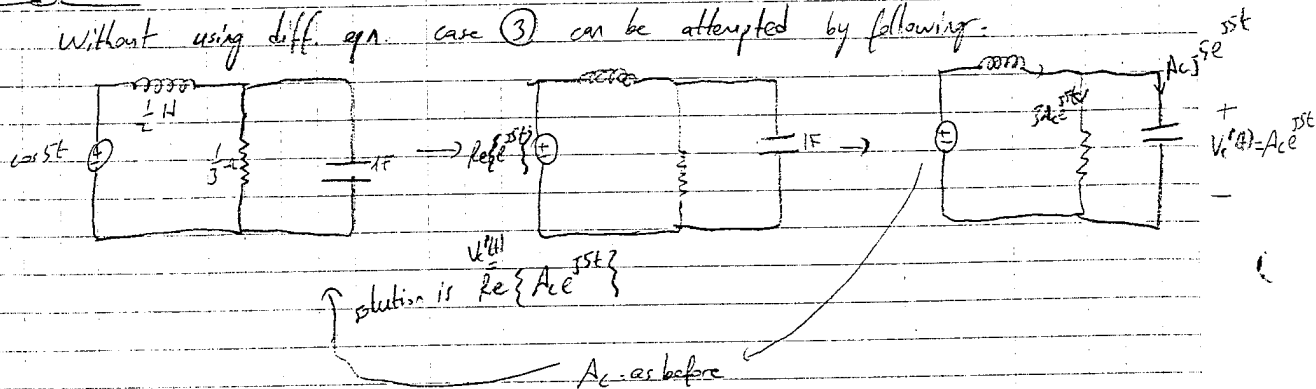
Without using diff. eqn. case ③ can be attempted by following.



Stability

$$(D^2 - (\lambda_1 + \lambda_2)D + \lambda_1 \lambda_2) V_c(t) = V_s(t) \quad \lambda_1, \lambda_2: \text{natural freq.}$$

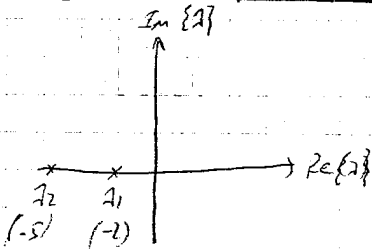① Asymptotically Stable ($\text{Re}\{\lambda_1\} < 0$ and $\text{Re}\{\lambda_2\} < 0$)



$$V_s(t) = e^{st}$$

$s=0$ (DC) \downarrow
 $V_c(t) = c_1 e^{-\lambda_1 t} + c_2 e^{-\lambda_2 t} + A$
 complete response \Rightarrow
 BIBO stability seems to be ok

$s=1$ \downarrow


 $V_c(t) = \text{natural response} + A e^t$

$s=j\omega$ (AC) \downarrow
 $V_c(t) = \text{natural response} + A e^{j\omega t}$

BIBO stability:
 All Bounded inputs \downarrow
 Bounded outputs
 Bounded functions:
 $|x(t)| < M \quad \forall t$

BIBO is ok for real part of the solution. (imaginary)

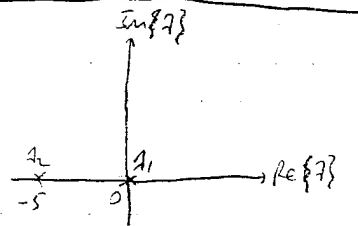② Stable ($\text{Re}\{\lambda_1\} \leq 0$ and $\text{Re}\{\lambda_2\} < 0$)




$$V_s(t) = e^{st}$$

$s=0$ (DC) \downarrow
 $V_{\text{complete}} = c_1 e^{0t} + c_2 e^{-\lambda_2 t} + \text{particular}$
 $\rightarrow A + Bt$
 Not BIBO stable

$s=-\sigma$ \downarrow
 $V_{\text{complete}} = c_1 + c_2 e^{-\sigma t} + A e^{-\lambda_1 t} + B t e^{-\lambda_1 t}$
 Seems ok for BIBO stability

$s=j\omega$ \downarrow
 $V_{\text{complete}} = c_1 + c_2 e^{-\lambda_2 t} + A e^{-\lambda_1 t}$

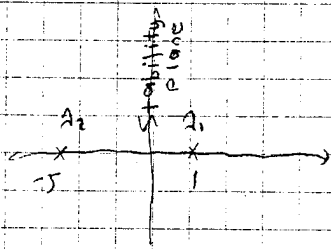Unstable ($\text{Re}\{A_i\} > 0$ or $\text{Re}\{A_n\} > 0$)



$$V_{\text{complete}} = V^h(t) + V^p(t)$$

$$= C_1 e^{A_1 t} + C_2 e^{A_2 t} + \text{particular}$$

11/03/2010

Perembe

About HW #1

A circuit is described by the following dif. eqn.

$$\begin{bmatrix} D+1 & 2 & 0 \\ -1 & D-1 & 1 \\ 0 & 0 & D+2 \end{bmatrix} \begin{bmatrix} x_1(t) \\ x_2(t) \\ x_3(t) \end{bmatrix} = \begin{bmatrix} 1 \\ 1 \\ 1 \end{bmatrix} u_s(t) ; \text{ initial cond's are also given.}$$

Find natural freq. of this circuit.

$$\begin{pmatrix} \begin{bmatrix} D & 0 & 0 \\ 0 & D & 0 \\ 0 & 0 & D \end{bmatrix} + \begin{bmatrix} 1 & 2 & 0 \\ -1 & -1 & 1 \\ 0 & 0 & 2 \end{bmatrix} \\ -A \end{pmatrix} \begin{bmatrix} x_1(t) \\ x_2(t) \\ x_3(t) \end{bmatrix} = \begin{bmatrix} 1 \\ 1 \\ 1 \end{bmatrix} u_s(t)$$

Bunu da asagıdaki gibi

yapamaz mıyız? Öyle yapmak işin

zero input mı olması gerekiyor?

$$\Rightarrow \begin{bmatrix} x_1(t) \\ x_2(t) \\ x_3(t) \end{bmatrix} = \underline{A} \begin{bmatrix} x_1 \\ x_2 \\ x_3 \end{bmatrix} + \begin{bmatrix} 1 \\ 1 \\ 1 \end{bmatrix} u_s(t)$$


Yoksa natural freq. sırdığı işin ne olması
olun btra inputu kendimiz mi sıfırlayacağız?

Natural freq: $u_s(t) = 0$ (zero-input) \rightarrow find the homogeneous of the system

$$\begin{bmatrix} D+1 & 2 & 0 \\ -1 & D-1 & 1 \\ 0 & 0 & D+2 \end{bmatrix} \begin{bmatrix} x_1(t) \\ x_2(t) \\ x_3(t) \end{bmatrix} = \begin{bmatrix} 0 \\ 0 \\ 0 \end{bmatrix} \hookrightarrow \begin{bmatrix} s+1 & 2 & 0 \\ -1 & s-1 & 1 \\ 0 & 0 & s+2 \end{bmatrix} e^{st} \begin{bmatrix} C_1 \\ C_2 \\ C_3 \end{bmatrix} = \begin{bmatrix} 0 \\ 0 \\ 0 \end{bmatrix}$$

$$\Rightarrow \begin{vmatrix} s+1 & 2 & 0 \\ -1 & s-1 & 1 \\ 0 & 0 & s+2 \end{vmatrix} = 0 \rightarrow \text{roots of this polynomial is natural frequencies.}$$

PHASORS

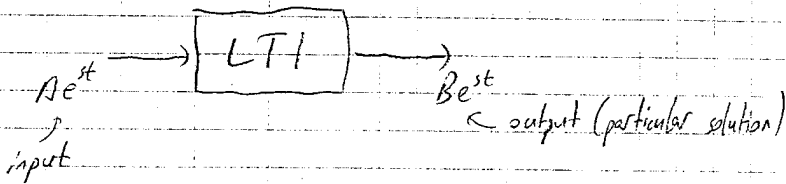

We know that exponential family of signals (Ae^{st}) at the input of a N^{th} order dynamic system produces an output (particular solution, solution due to forcing term, i.e. input) in the form Be^{st} . So exponential family, the output is determined by finding B .

Then the coefficient of the exponent is called the phasor. In general A, B are complex numbers.

Specific for AC inputs that is $f(t) = M \cos(\omega t + \phi)$, we have the following phasor definition

$$f(t) = M \cos(\omega t + \phi) = \text{Re} \{ M e^{j(\omega t + \phi)} \} = \text{Re} \left\{ \underbrace{M e^{j\phi}}_A e^{j\omega t} \right\} = \text{Re} \{ A e^{j\omega t} \}$$

\rightarrow complex valued
 $\rightarrow A$: phasor, the coefficient of $e^{j\omega t}$

Then

$$2 \cos(\omega t + 30^\circ) \xrightarrow[\text{phasor form}]{} 2 e^{j\pi/6}$$

$$\frac{1 \angle 45^\circ}{\omega=2} \xrightarrow{\text{time}} \text{Re} \left\{ \frac{1 \angle 45^\circ}{1 e^{j\frac{\pi}{4}}} e^{j2t} \right\} = \cos(2t + \frac{\pi}{4})$$

Ex $\cos(\underbrace{4t+30^\circ}_A) + \cos(\underbrace{4t+60^\circ}_B) = 2 \cos(\frac{A+B}{2}) \cos(\frac{A-B}{2}) = 2 \cos(4t+45^\circ) \cos(15^\circ)$

$$\text{Re} \{ e^{j30^\circ} e^{j4t} \} + \text{Re} \{ e^{j60^\circ} e^{j4t} \} = \text{Re} \{ e^{j4t} (e^{j30^\circ} + e^{j60^\circ}) \}$$

$$\begin{aligned} \text{Re} \{ e^{j4t} [(\cos 30^\circ + j \sin 30^\circ) + (\cos 60^\circ + j \sin 60^\circ)] \} &= \text{Re} \{ e^{j4t} [(\frac{\sqrt{3}}{2} + \frac{1}{2}) + j(\frac{1}{2} + \frac{\sqrt{3}}{2})] \} = \text{Re} \{ e^{j4t} \frac{(1+j\sqrt{3})}{2} (1+j) \} \\ &= \text{Re} \left\{ e^{j4t} \left(\frac{1+\sqrt{3}}{2} \right) \sqrt{2} e^{j\pi/4} \right\} = \frac{1+\sqrt{3}}{\sqrt{2}} \cos(4t + 45^\circ) \end{aligned}$$

In the previous example, we have repeatedly used $\text{Re} \{ e^{j\omega t} (\dots) \}$ at every step. We do not write $\text{Re} \{ e^{j\omega t} (\dots) \}$ at every step; but prefer to write the phasor instead.

That's

$$\cos(4t+30^\circ) + \cos(4t+60^\circ) \xrightarrow{\text{phasor}} 1\angle 30^\circ + 1\angle 60^\circ = \left(\frac{\sqrt{3}+j}{2}\right) + \left(\frac{1+j\sqrt{3}}{2}\right) \leftarrow \text{resulting phasor}$$

$$= \frac{1+\sqrt{3}}{\sqrt{2}} e^{j\pi/4} \xrightarrow[\omega=4]{\text{time domain}} \frac{1+\sqrt{3}}{\sqrt{2}} \cos(4t+45^\circ)$$

About ZPS-I

Problem 1) $\begin{bmatrix} D+1 & 0 \\ 1+D & D^2+2 \end{bmatrix} \begin{bmatrix} e_1(t) \\ e_2(t) \end{bmatrix} = \begin{bmatrix} 0 \\ 0 \end{bmatrix} \quad V_s(t) = 0$

$\begin{bmatrix} \lambda+1 & 0 \\ 1+\lambda & \lambda^2+2 \end{bmatrix} \rightarrow \text{characteristic eqn}$

MATLAB

`>> syms D;`

`>> A = [D+1 -0; 1 D] $\begin{bmatrix} D+1 & -0 \\ 1 & D \end{bmatrix}$`

`>> det(A)`

`= D^2 + 2D`

`>> roots(det(A))`

`[0 -2]`


NA \rightarrow Some of natural frequencies at zero can be missing due to D, D^2 cancellation

MNA \rightarrow used to find natural freq. (has only D's)

State eqn \rightarrow used for natural frequencies (has only D's)

Ex $\frac{d}{dt} A \cos(\omega t + \phi) = -A \omega \sin(\omega t + \phi)$
 $= A \omega \cos(\omega t + \phi + 90^\circ)$

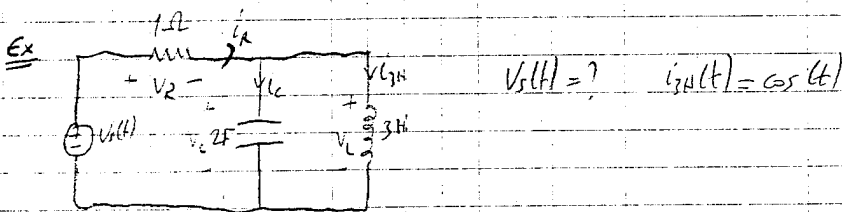
$\Rightarrow A \frac{d\phi}{dt} \rightarrow A [\phi + 90^\circ]$



$V_{3H}(t) = 3 i_L(t) = 3 \sin(t) \rightarrow V_C(t) = C \dot{V}_C(t) = -6 \cos(t)$

$V_R = V_C + V_{3H} = -5 \cos(t) \rightarrow V_R(t) = -5 \cos(t)$

$V_s(t) = -5 \cos(t) - 3 \sin(t)$

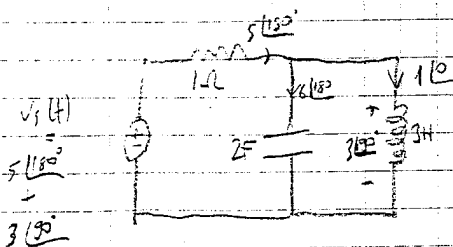

$V_s \rightarrow 5 \angle 160^\circ + 3 \angle 90^\circ = -5 + j3 = \sqrt{25+9} e^{j(\tan^{-1} 3/5)}$

$V_s(t) = \sqrt{25+9} \cos(t - \tan^{-1} \frac{3}{5})$

Phasors allow us


① Add cosines (with the same frequency)

② Differentiate cosines

so adding differentiated and scaled many cosine terms is possible with phasors.


15/03/2010
Pazartesi

Ex

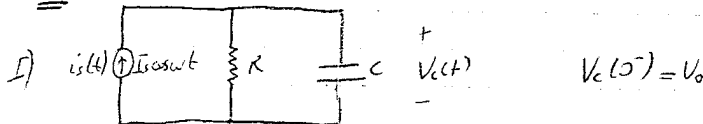

$$(D + \frac{1}{RC}) V_c(t) = \frac{i_s(t)}{C} = \frac{I_s \cos \omega t}{C}$$
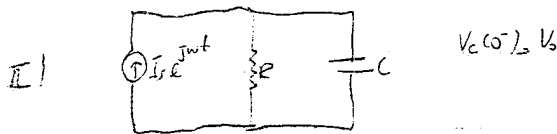
$$V_c^{\text{complete}}(t) = C_1 e^{-\frac{t}{RC}} + A \cos(\omega t) + B \sin(\omega t)$$



$$(D + \frac{1}{RC}) V_c(t) = \frac{I_s e^{j\omega t}}{C}$$

$$V_c^{\text{complete}} = d_1 e^{-\frac{t}{RC}} + D e^{j\omega t} \Rightarrow V_c^{\text{complete}}(t) = \text{Re} \{ V_{II}^{\text{complete}}(t) \}$$


can be complex

$$V_c^{\text{complete}}(t) = d_1 e^{-\frac{t}{RC}} + \frac{I_s R}{1 + \omega^2 R^2 C^2} \cos(\omega t) + \frac{I_s \omega R^2 C}{1 + \omega^2 R^2 C^2} \sin \omega t$$

$$V_c^{\text{complete}}(0) = d_1 + \frac{I_s R}{1 + \omega^2 R^2 C^2} = V_0 \Rightarrow d_1 = V_0 - \frac{I_s R}{1 + \omega^2 R^2 C^2}$$

If we're only interested in particular solution for A.C. excitations, we have some simplifications!

Phasor Circuit Analysis

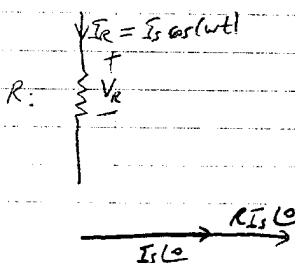

Time domain:


$$I_R(t) = I_s \cos(\omega t)$$

$$V_R(t) = R I_s \cos(\omega t)$$

Phasor

$$I_R = I_s \angle 0$$

$$V_R = R I_s \angle 0$$

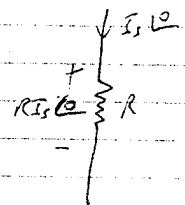


$$I_c = I_s \cos(\omega t + \phi)$$

$$V_c = I_s \sin(\omega t + \phi) = \frac{I_s}{\omega C} \cos(\omega t + \phi - \frac{\pi}{2})$$

$$I_c = I_s \angle \phi$$
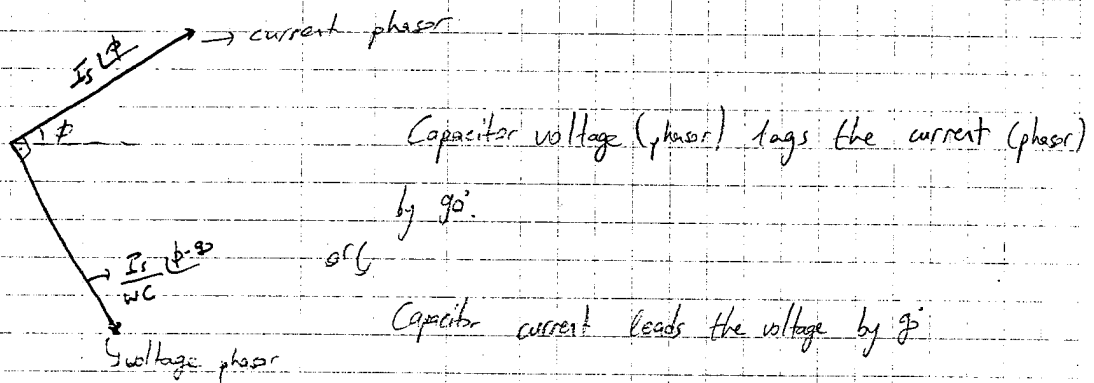
$$V_c = \frac{I_s}{\omega C} \angle (\phi - 90^\circ)$$




$$I_L(t) = I_s \cos(\omega t + \phi)$$

$$V_L(t) = -\omega L I_s \sin(\omega t + \phi) = \omega L I_s \cos(\omega t + \phi + \frac{\pi}{2})$$

$$I_L = I_s \angle \phi$$
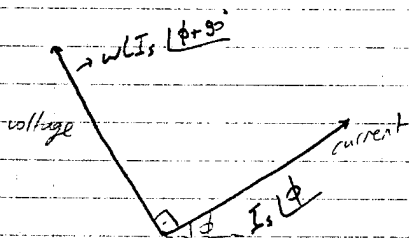
$$V_L = \omega L I_s \angle (\phi + 90^\circ)$$



Impedance and Admittance


$$\text{Impedance} \Rightarrow Z = \frac{\text{Voltage Phasor}}{\text{Current Phasor}} = \frac{V_x \angle \theta - \phi}{I_x} \quad (\Omega)$$

$$\text{Admittance} \Rightarrow Y = \frac{1}{Z} = \frac{\text{Current Phasor}}{\text{Voltage Phasor}} = \frac{I_x \angle \phi - \theta}{V_x} \quad (S)$$


$$Z = \underbrace{Re\{Z\}}_{\text{Resistance}} + j \underbrace{Im\{Z\}}_{\text{Reactance}}$$

$$Y = \underbrace{Re\{Y\}}_{\text{Conductance}} + j \underbrace{Im\{Y\}}_{\text{Susceptance}}$$

Ex

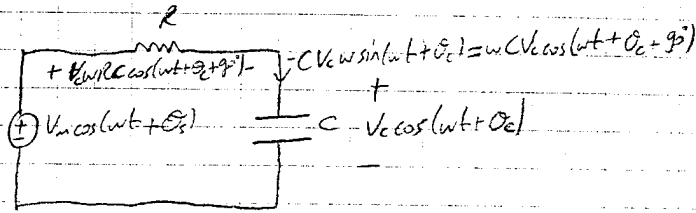
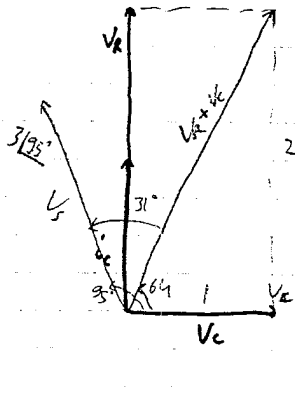
$$V_s \cos(\omega t + \theta_s) = V_R(t) + V_C(t)$$




$\omega C = 1$
 $R = 2$
 $V_s = 3 \cos(\omega t + 95^\circ)$

$V_C(t) = \frac{3\sqrt{5}}{5} \cos(\omega t + 31^\circ)$

Series and Parallel Combination:

Series

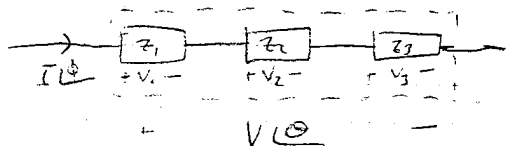


$$V_1 + V_2 + V_3 = (I \angle \phi) Z_1 + (I \angle \phi) Z_2 + (I \angle \phi) Z_3$$

$$V \angle \phi = I \angle \phi (Z_1 + Z_2 + Z_3)$$

Z_{comb}


Parallel

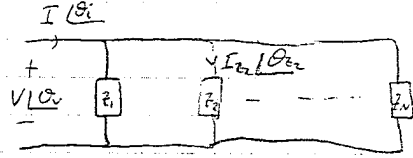

$$I \angle \phi = \sum_{k=1}^N I_k \angle \phi_k$$

$$= \sum_k \frac{V \angle \phi}{Z_k} = V \angle \phi \sum_k \frac{1}{Z_k} \Rightarrow \frac{V \angle \phi}{I \angle \phi} = \left(\sum_k \frac{1}{Z_k} \right)^{-1}$$

$\Delta - Y$

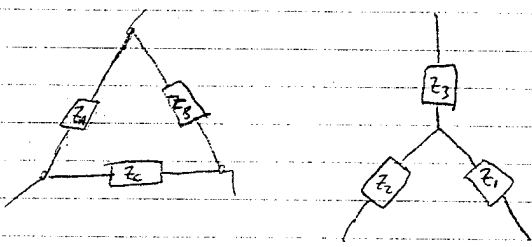

$$Z_1 = \frac{Z_2 Z_3}{Z_1 + Z_2 + Z_3}$$

$$Z_2 = \frac{Z_1 Z_3}{Z_1 + Z_2 + Z_3}$$



$$Z_3 = \frac{Z_1 Z_2}{Z_1 + Z_2 + Z_3}$$

GENERAL AC CIRCUIT ANALYSIS

AC steady-state analysis: (Particular solution due to AC excitation)

- ① Node
 - ② Mesh
 - ③ Thevenin-Norton
 - ④ Other simplification methods
- } AC Analysis

Ex Node Analysis:

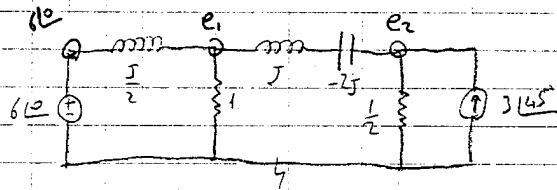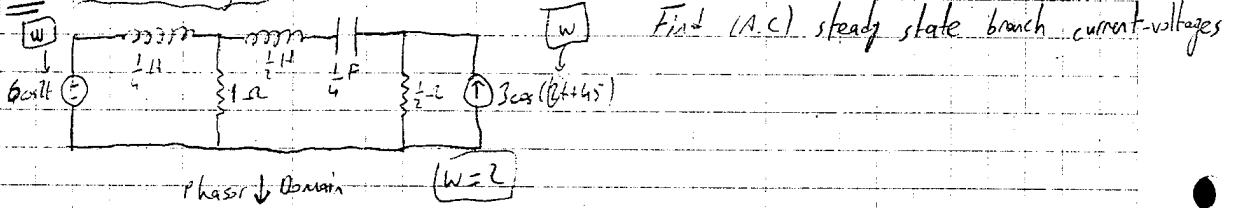

KCL at e_1 :

$$\frac{e_1}{1} + \frac{e_1 - 6\angle 0^\circ}{\frac{j}{2}} + \frac{e_1 - e_2}{-j} = 0 \Rightarrow e_1 - 2j(e_1 - 6\angle 0^\circ) + j(e_1 - e_2) = 0$$


KCL at e_2 :

$$\frac{e_2}{\frac{j}{2}} + \frac{e_2 - e_1}{-j} - 3\angle 45^\circ = 0$$

$$2e_2 + j(e_2 - e_1) - 3\angle 45^\circ = 0$$

$$\begin{bmatrix} 1-j & -j \\ -j & 2+j \end{bmatrix} \begin{bmatrix} e_1 \\ e_2 \end{bmatrix} = \begin{bmatrix} -12j \\ 3\angle 45^\circ \end{bmatrix}$$

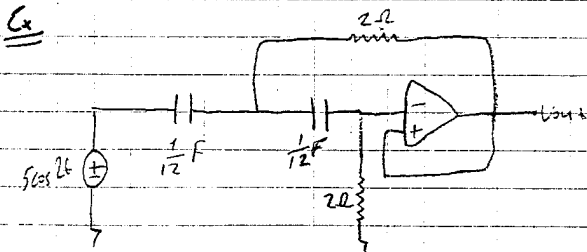
$$\Rightarrow \begin{bmatrix} e_1 \\ e_2 \end{bmatrix} = \begin{bmatrix} 7 \\ 3.63 \angle 14^\circ \end{bmatrix} \Rightarrow e_2(t) = 3.63 \cos(2t + 14^\circ) \text{ V}$$



Assume Op-Amp is in linear region

Find $V_{out}(t)$

Phasor domain

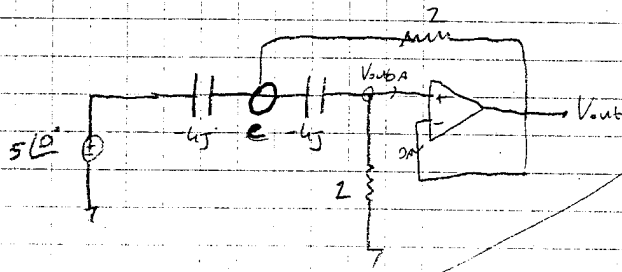

KCL at e:

$$\frac{e-5}{-4j} + \frac{e-V_{out}}{2} + \frac{e-V_{out}}{-4j} = 0$$

KCL at Vout:

$$\frac{e-V_{out}}{-4j} = \frac{V_{out}}{2}$$

$$e = (1-2j)V_{out}$$


$$e(j+2+j) + V_{out}(-2-j) = 5j$$

$$V_{out}(1-2j)$$

$$V_{out} [(1-2j)(2+j) - 2-j] = 5j$$


$$V_{out} = \frac{5j}{4-3j} = \frac{55}{5\sqrt{33}} = 1\angle 127^\circ \Rightarrow V_{out} = 1\cos(7t+127^\circ)$$

Ex Mesh Analysis

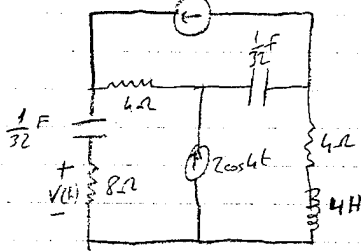

Find V(t)

Phasor Domain

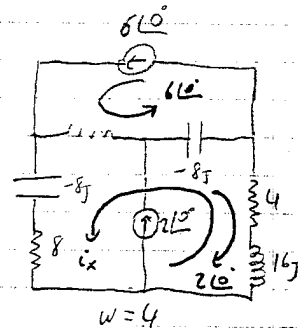


KCL around red loop:


$$4(i_x - 6) + (8-8j)i_x + (16j+4)(i_x-2) - 8j(i_x-2-6) = 0$$

$$i_x = \frac{24 + 8(4j+1) - 64j}{4 + 8-8j + 16j + 4-8j} = \frac{8(3-4j)}{16} = \frac{1}{2} \angle 53^\circ \rightarrow V^s(t) = 2\cos(4t-53^\circ)$$

Sources with different frequencies (ω):

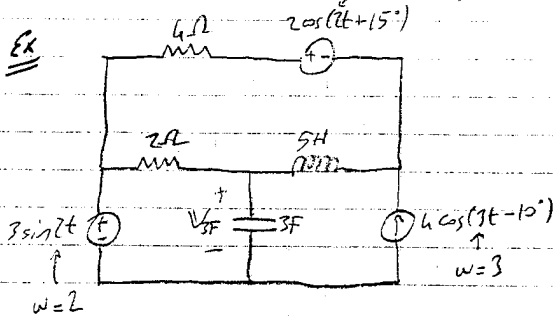


$$V_{3F}(t) = ?$$

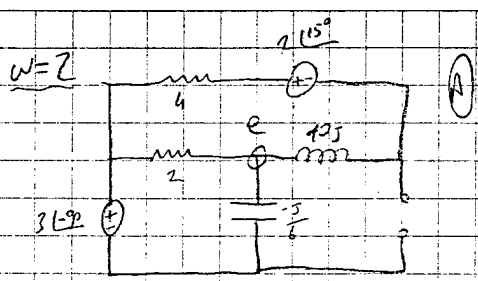

$$\Rightarrow \frac{e}{-j} + \frac{e - (3 \angle 90^\circ - 2 \angle 15^\circ)}{4 + j10} + \frac{e - 3 \angle 90^\circ}{2} = 0$$

$$e = V_{3F}^{(A)} \angle \theta_A$$
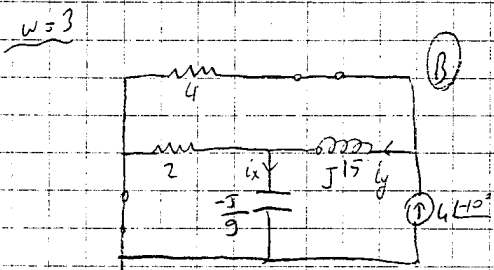
$$V_{3F}^{(A)}(t) = V_{3F}^{(A)} \cos(2t + \theta_A)$$



$$\rightarrow i_x = 4 \angle 120^\circ \frac{4}{4 + (j15 + (-j)11.2)} = \frac{2}{-j/3 + 2}$$


$$V_{3F} = -\frac{j}{3} i_x = V_{3F}^{(B)} \angle \theta_B$$

$$V_{3F}^{(B)}(t) = V_{3F}^{(B)} \cos(3t + \theta_B)$$

Superposition: $V_{3F}(t) = V_{3F}^{(A)}(t) + V_{3F}^{(B)}(t)$


$$V_{3F}(t) = V_{3F}^{(A)} \cos(2t + \theta_A) + V_{3F}^{(B)} \cos(3t + \theta_B) \quad V$$

i_x

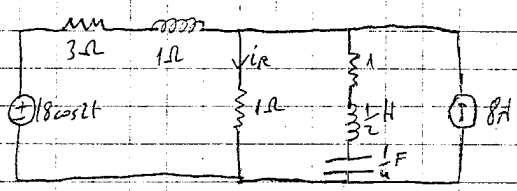

$i_x^{ss}(t) = ?$


$\omega = \{2, 0\}$

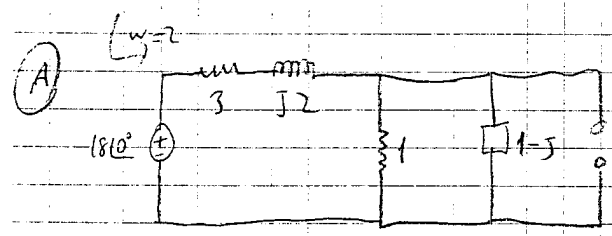

source transformation

$$\rightarrow i_x^{(A)} = \frac{18}{3 + j2} \cdot \frac{1}{\frac{1}{1} + \frac{1}{1-j} + \frac{1}{3 + j2}} = 2(1-j) = 2\sqrt{2} \angle -45^\circ$$
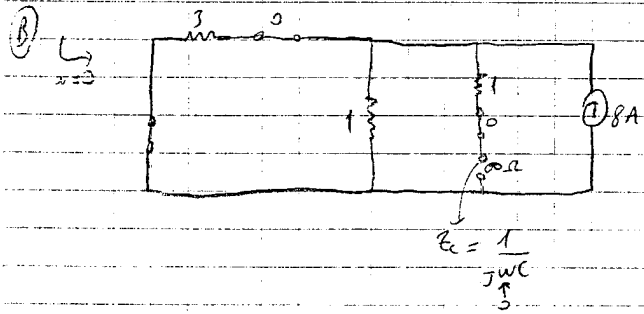
$$i_x^{(A)}(t) = 2\sqrt{2} \cos(2t - 45^\circ)$$



$$i_x^{(B)} = 8 \cdot \frac{3}{1+3} = 6 \text{ A}$$

Superposition

$$i_x(t) = 6 + 2\sqrt{2} \cos(2t - 45^\circ) \text{ A}$$

Ex $(D^2+4)V_c(t) = \cos(2t)$

$(D^2+4)V_c(t) = 0$
 $\lambda^2+4=0$
 $\lambda_{1,2} = \pm 2j$

$V_c^{hom}(t) = c_1 e^{2jt} + c_2 e^{-2jt} + A e^{j2t} + B t e^{j2t}$
 $- c_1 e^{j2t} + c_2 e^{-j2t} + A e^{j2t} + B t e^{j2t}$
 part. soln

$\cos(2t+\theta) + t \dots$
 $(E \cos(2t+\theta))$
 unbounded
 no steady state

~~AC POWER ANALYSIS~~

AC POWER ANALYSIS


RMS or Effective Values

$x(t)$ - periodic function $\Leftrightarrow x(t-T) = x(t) \quad \forall t$


Root Mean Square \Rightarrow RMS $\rightarrow \sqrt{\frac{1}{T} \int_0^T (x(t))^2 dt}$
 Integrate over a full period

Ex $x(t) = A \cos(\omega t + \phi)$

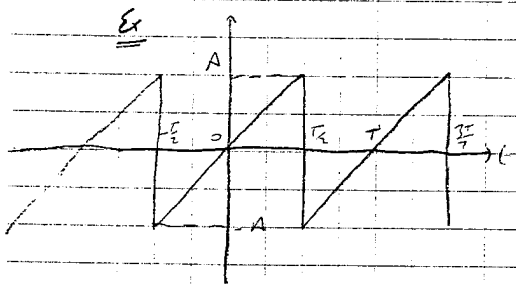RMS $\rightarrow \sqrt{\frac{1}{T} \int_0^T A^2 \cos^2(\omega t + \phi) dt} = \sqrt{\frac{A^2}{T} \int_0^T \frac{1 + \cos(2\omega t + 2\phi)}{2} dt} = \sqrt{\frac{A^2}{T} \left(\frac{T}{2} + \frac{\int_0^T \cos(2\omega t + 2\phi) dt}{2} \right)} = \frac{A}{\sqrt{2}}$




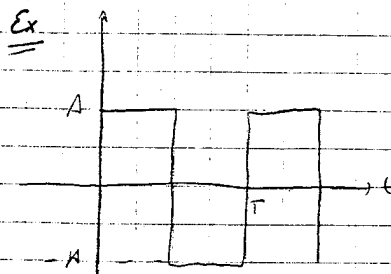RMS $\rightarrow \sqrt{\frac{1}{T} \int_{-T/2}^{T/2} \left(\frac{2A}{T}t\right)^2 dt} = \sqrt{\frac{1}{T} \cdot 2 \int_0^{T/2} \left(\frac{2A}{T}t\right)^2 dt}$
 $= \sqrt{\frac{2}{T} \frac{4A^2}{T^2} \int_0^{T/2} t^2 dt} = \sqrt{\frac{2}{T} \frac{4A^2}{T^2} \frac{(T/2)^3}{3}} = \frac{A}{\sqrt{3}}$



\Rightarrow RMS (effective) $\{x(t)\} = A$

WHY RMS?

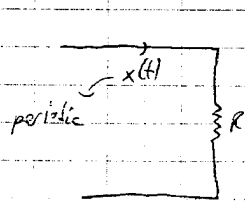


$$p(t) = R(x(t))^2$$

$$E_{\text{absorbed by } R} = \int_0^T p(t) dt = \int_0^T R x^2(t) dt = RT \left(\frac{1}{T} \int_0^T x^2(t) dt \right)^2 = RT (x_{\text{RMS}})^2$$

$$= (R x_{\text{RMS}})^2 T$$

energy calculation.

Average Power

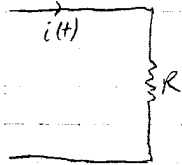


$$P_{\text{AV}} = \frac{1}{T} \int_0^T p(t) dt \quad \text{or} \quad P_{\text{AV}} = \lim_{T \rightarrow \infty} \frac{1}{T} \int_0^T p(t) dt$$

$$= \left(\frac{1}{T} \int_0^T i^2(t) dt \right) R \Rightarrow P_{\text{AV}} = (i_{\text{RMS}})^2 R$$

Energy consumed in 5 periods = $(P_{\text{AV}} \cdot \underbrace{5T}_{\text{duration}})$ Energy consumed.

Average and Instantaneous Power

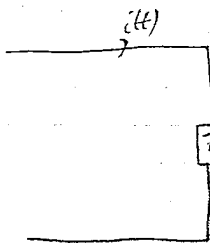

$$\left. \begin{aligned} V(t) &= V_m \cos(\omega t + \theta_v) \rightarrow V = V_m \angle \theta_v \\ i(t) &= I_m \cos(\omega t + \theta_i) \rightarrow i = I_m \angle \theta_i \end{aligned} \right\} \theta = \frac{V_m}{I_m} (\theta_v - \theta_i)$$

$$p(t) = V(t) i(t) = V_m I_m \cos(\omega t + \theta_v) \cos(\omega t + \theta_i)$$


$$= \frac{V_m I_m}{2} \left[\cos(\underbrace{\theta_v - \theta_i}_{\theta_z}) + \cos(2\omega t + \underbrace{\theta_v + \theta_i}_{2\theta_i + \theta_z}) \right]$$

$$= \frac{V_m I_m}{2} \left[\cos \theta_z + \cos(2\omega t + \theta_i) \cos \theta_z - \sin(2\omega t + \theta_i) \sin \theta_z \right]$$

$$= \frac{V_m I_m}{2} \cos \theta_z \left\{ 1 + \cos(2\omega t + \theta_i) \right\} - \frac{V_m I_m}{2} \sin \theta_z \sin(2\omega t + \theta_i)$$

$$P_{\text{AV}} = \frac{1}{T} \int_0^T p(t) dt = \frac{V_m I_m}{2} \cos \theta_z = V_{\text{rms}} I_{\text{rms}} \cos \theta_z = P_{\text{AV}}$$

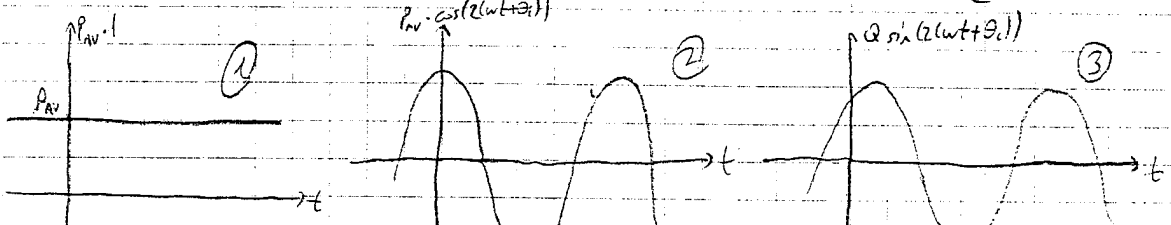
$$p(t) = P_{\text{AV}} \left\{ 1 + \cos(2\omega t + \theta_i) \right\} - Q \sin(2\omega t + \theta_i) \quad Q = \frac{V_m I_m}{2} \sin \theta_z$$



$$\textcircled{1} + \textcircled{2} + \textcircled{3} = p(t)$$

$$p(t) = P_{AV} + P_{AV} \cos(2(\omega t + \theta_i)) - Q \sin(2(\omega t + \theta_i))$$

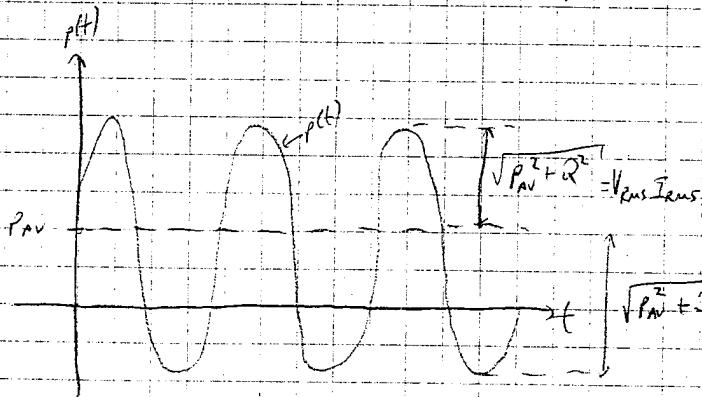
$$= P_{AV} + \sqrt{P_{AV}^2 + Q^2} \cos(2\omega t + 2\theta_i + \tan^{-1} \frac{Q}{P_{AV}})$$



$$\sqrt{P_{AV}^2 + Q^2} = \sqrt{\left(\frac{V_m I_m \cos \theta_z}{2}\right)^2 + \left(\frac{V_m I_m \sin \theta_z}{2}\right)^2}$$


$$= \frac{V_m I_m}{2} = V_{rms} I_{rms}$$

$V_{rms} I_{rms}$: Apparent power

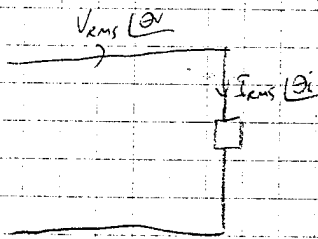

$$\text{Apparent Power} = V_{rms} I_{rms}$$

Special Cases

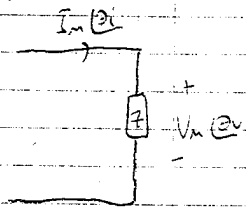


$$Z = \frac{V_m \angle \theta_v - \theta_i}{I_m}$$

① $Z=R \rightarrow \theta_z=0$


$$P_{AV} = \frac{V_m I_m}{2} = V_{rms} I_{rms} \quad Q=0$$
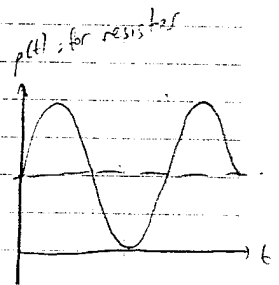
$$p(t) = P_{AV} \{1 + \cos(2(\omega t + \theta_i))\}$$



② $Z = \text{Inductor} \rightarrow \theta_z = 90^\circ$
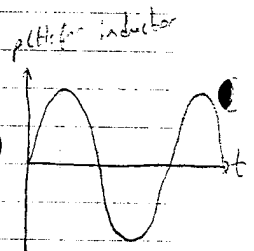
$$P_{AV} = 0 \quad Q = \frac{V_m I_m}{2} \quad p(t) = \frac{V_m I_m}{2} \sin(2(\omega t + \theta_i))$$



Q : Reactive Power (VAR)
Watt Reactive

$$Q = \frac{V_m I_m}{2} \sin(\theta_z)$$

25/03/2010
Perseus

$$p(t) = P_{AV} \{1 + \cos(2(\omega t + \theta_i))\} - Q \sin(2(\omega t + \theta_i))$$

$$P_{AV} = V_{rms} I_{rms} \cos(\theta_z)$$

$$Q = V_{rms} I_{rms} \sin(\theta_z)$$


$$\frac{1}{T} \int_0^T p(t) dt = P_{AV} \text{ in watts (time average of } p(t))$$

work done = $P_{AV} \cdot T_s \rightarrow$ Joule's

T_s sec's \times watts \rightarrow Assume $(T_s = kT)$
 k : integer


Let's check
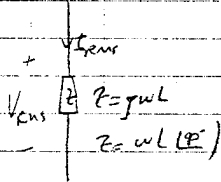
$$p(t) = -V_{rms} I_{rms} \sin(2(\omega t + \phi))$$



$$P_{av} = V_{rms} I_{rms} \cos(\phi) = 0$$

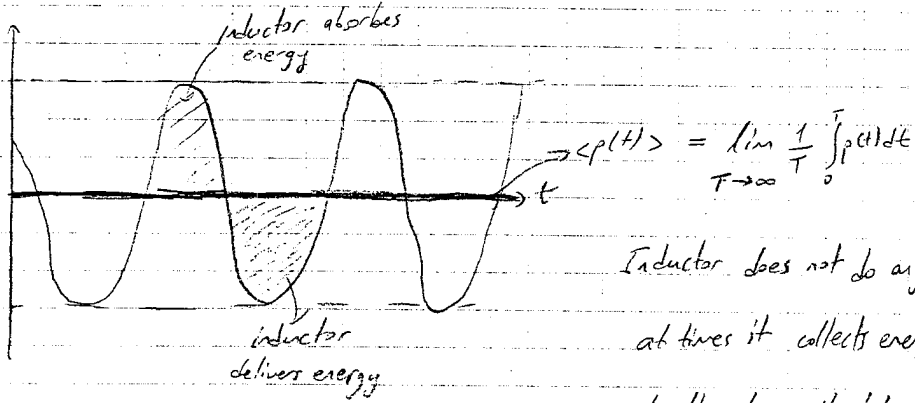
$$Q = V_{rms} I_{rms} \sin(\phi) = V_{rms} I_{rms}$$



Inductor does not do any work!


at times it collects energy

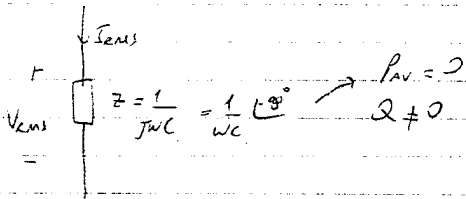at other times it delivers (energizes) other component.



$$P_{av} = 0$$

$$Q \neq 0$$

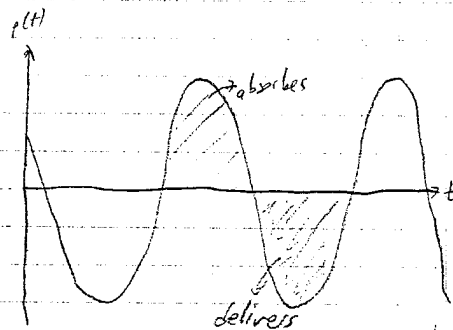

Average Stored Energy;

① Capacitor: $E_c(t) = \frac{1}{2} C V_c^2(t)$

$$E_c^{avg} = \frac{1}{T} \int_0^T (E_c(t)) dt \Rightarrow E_c^{avg} = \frac{1}{2} C (V_{c,rms})^2$$

② Inductor: $E_L^{avg} = \frac{1}{2} L (I_L^{rms})^2$

Then:

$$Z = \frac{V_{rms}}{I_{rms}} = \frac{1}{j\omega C} \quad Q = V_{rms} I_{rms} \sin(\phi) = -V_{rms} I_{rms}$$

$$P_{av} = 0$$


$$\frac{V_{rms}}{I_{rms}} = Z = \frac{1}{j\omega C}$$

$$\frac{V_{rms}}{I_{rms}} = |Z| = \frac{1}{\omega C}$$

$$Q = -V_{rms} \frac{V_{rms}}{\frac{1}{\omega C}}$$



$$Q = -\omega C V_{rms}^2$$

$$Q = -\omega E_c^{avg}$$

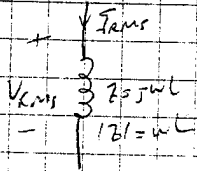

$$Q = V_{rms} I_{rms} \sin(\theta) = V_{rms} I_{rms} = \omega L I_{rms}^2 = 2\omega F_L P_{AVG}$$

Conservation of P_{avg} and Q :

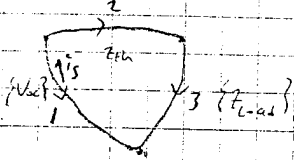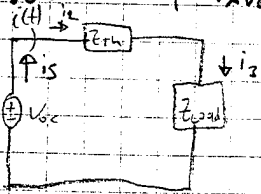

$$i_1(t) = I_{rms}^e \cos(\omega t + \theta_i^e)$$

$$v_1(t) = V_{rms}^e \cos(\omega t + \theta_v^e)$$

Pellegrini's theorem;

$$\sum_{k=1}^3 p_k(t) = 0 \Rightarrow p_1(t) + p_2(t) = -p_3(t) = p_3(t) \leftarrow \text{power supplied by } V_{oc} \quad \forall t$$


$$P_{AV}^{(1)} \{1 + \cos(2\omega t + \theta_i^{(1)})\} + P_{AV}^{(2)} \{1 + \cos(2\omega t + \theta_i^{(2)})\} = P_{AV}^{(3)} \{1 + \cos(2\omega t + \theta_i^{(3)})\} - Q^{(1)} \sin(2\omega t + \theta_i^{(1)}) - Q^{(2)} \sin(2\omega t + \theta_i^{(2)}) - Q^{(3)} \sin(2\omega t + \theta_i^{(3)}) \quad \forall t$$

due to \int for $\forall t$ valid

$$\sum P_{AV}^{absorbed} = P_{AV}^{supplied}$$

$$\sum Q^{absorbed} = Q^{supplied}$$

Complex Power

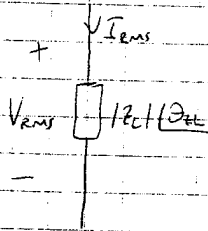


$$S = P + jQ = V_{rms} I_{rms} \cos(\theta_e) + j V_{rms} I_{rms} \sin(\theta_e)$$

complex power

Note: $p(t) = P_{AVG} + P_{AVG} \cos(2\omega t + \theta_i) - Q \sin(2\omega t + \theta_i)$

$$= P_{AVG} + \text{Re} \left\{ \underbrace{(P_{AVG} + jQ)}_S e^{j2(\omega t + \theta_i)} \right\}$$

Ex

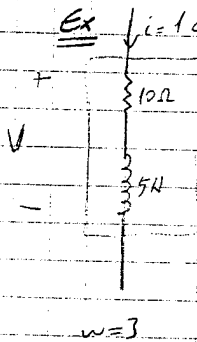

Find P_{AV} , Q , S for the component

Method (1)

$$i_{rms} = \frac{1}{\sqrt{2}}$$


$$V_{rms} = \frac{5\sqrt{13}}{\sqrt{2}}$$

$$V = (115) (10 + j15) = (115) \sqrt{13} \angle \tan^{-1} \frac{15}{10}$$

$$= 5\sqrt{13} \angle [15^\circ + \tan^{-1} \frac{15}{10}]$$

$$P_{AVG} = I_{rms} V_{rms} \cos(\theta_e)$$

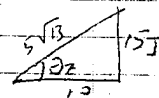
$$= \frac{5\sqrt{13}}{2} \frac{10}{5\sqrt{13}} = 5 \text{ watts}$$



$$Q = I_{rms} V_{rms} \sin(\theta_e) = \frac{5\sqrt{13}}{2} \frac{15}{5\sqrt{13}} = 7.5 \text{ VAR}$$

Method 2

Part of $(10 + j15)$ is only due to 10Ω

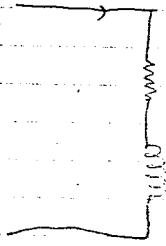

$$I_{rms} = \frac{1}{\sqrt{2}}$$

$$P_{avg}^{10\Omega} = V_{rms} I_{rms} \cos(\theta_R)$$

for a resistor $\theta = 0$

$$= (I_{rms} R) I_{rms}$$

$$= I_{rms}^2 R = \left(\frac{1}{\sqrt{2}}\right)^2 10 = 5 \text{ watts}$$


$$Q^{15} = V_{rms} I_{rms} \sin(\theta_2)$$

$$= (15 I_{rms}) (I_{rms})$$

$$= 15 (I_{rms})^2$$

$$= \frac{15}{2} = 7.5 \text{ VAR}$$


So in general;

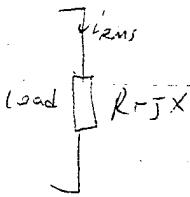

$$P_{load} = I_{rms}^2 R$$

$$Q_{load} = I_{rms}^2 X$$

Method 3

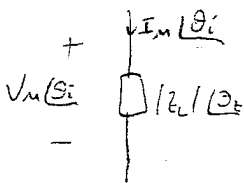


$$S = \frac{1}{2} V I^*$$


$$S = V_{rms} I_{rms} (\cos(\theta_z) + j \sin(\theta_z))$$

$$= \frac{|V|}{\sqrt{2}} \frac{|I|}{\sqrt{2}} e^{j(\theta_v - \theta_z)} = \frac{1}{2} (|V| e^{j\theta_v}) (|I| e^{-j\theta_z}) = \frac{1}{2} \underbrace{V I^*}_{\text{phasor}}$$
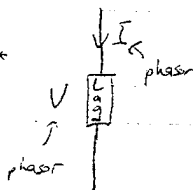
$$\Rightarrow S_{load} = \frac{1}{2} V I^*$$



Note: Inductive loads

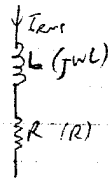


$$S_{load} = P + jQ_{ind} \quad (P > 0, Q > 0)$$

$$P = I_{rms}^2 R$$

$$Q_{ind} = I_{rms}^2 \omega L$$

Capacitive loads

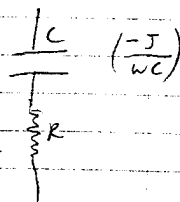


$$S_{load} = P + jQ_{cap} \quad (P > 0, Q < 0)$$


$$P = I_{rms}^2 R$$

$$Q_{cap} = -I_{rms}^2 \frac{1}{\omega C}$$

Ex $S = 1 + j10$

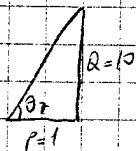

$S = 1 - j1$

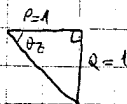

Power factor


Power factor = $\cos(\theta_z)$

For inductor \rightarrow lagging (Current lags)

For capacitor \rightarrow leading (Current leads)

29/03/2010
Pazartesi


Review AC Steady-State Power

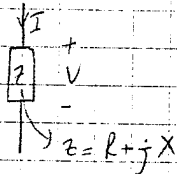

$S = \frac{1}{2} V I^* = \frac{1}{2} |I|^2 Z = I_{rms}^2 Z = I_{rms}^2 (R + jX)$

$\angle S = \angle Z$

$$\text{p.f.} = \cos(\angle Z) \begin{cases} \text{lagging} \\ \text{leading} \end{cases} \quad \left| \begin{array}{l} S = P + jQ \\ P = I_{rms}^2 R \\ Q = I_{rms}^2 X \end{array} \right.$$

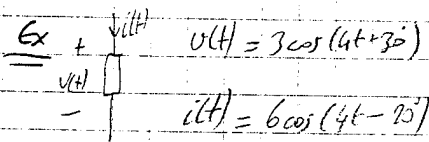

① Find real power (watts) and Reactive Power (VAR) of the component.

$S = \frac{1}{2} V I^* = \frac{1}{2} 3 \angle 30^\circ (6 \angle -75^\circ)^* = 9 \angle 50^\circ = 5.7 + j6.8$


$P = 5.7 \text{ watts} \quad Q = 6.8 \text{ VAR's}$


② Find p.f. of the component

$\text{p.f.} = \cos(\angle S) = \cos(50^\circ) = 0.64 \text{ (lagging) (inductive load)}$
 (current lags voltage)

③ Assuming that the component is constructed from R, L, C, find suitable R, L, C to realize the component

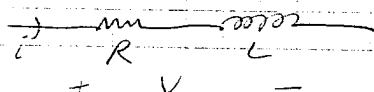$Z = \frac{V}{I} = \frac{3 \angle 30^\circ}{6 \angle -75^\circ} = \frac{1}{2} \angle 105^\circ = \frac{0.32}{R} + j \frac{0.38}{\omega L} \Rightarrow L = \frac{0.38}{4} = 0.095 \text{ H}$



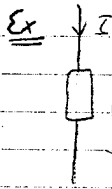


$$V = 100 \text{ V (RMS)} \leftarrow V(t) = 100\sqrt{2} \cos(\omega t + \theta)$$

$$P = 5 \text{ kW}$$

$$p.f. = 0.8 \text{ (lagging)}$$

a) Find VAR (Reactive Power)

$\theta = \text{lagging}$

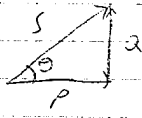

$$p.f. = \cos \theta = 0.8$$

$$S = P \angle \theta = 5 \text{ kW} \angle \theta$$

$$Q = P \cdot \tan(\theta) = 5000 \cdot \frac{3}{4} = 3750$$

$$S = 5000 + j 3750$$

b) Apparent Power = ?


$$\text{Apparent Power} = V_{\text{rms}} I_{\text{rms}}$$

$$S = 5000 + j 3750 = I_{\text{rms}}^2 (R + jX) = \frac{1}{2} |I|^2 Z = \frac{1}{2} \left| \frac{V}{Z} \right|^2 Z = \frac{1}{2} \frac{|V|^2}{|Z|^2} Z = \frac{1}{2} \frac{|V|^2}{Z^*} = \frac{V_{\text{rms}}^2}{Z^*}$$


$$S = 5000 + j 3750 = \frac{10000}{Z^*} \Rightarrow Z = \frac{1}{0.5 + j 0.375} = \frac{0.5 - j 0.375}{0.5^2 + 0.375^2}$$

$$\text{Apparent power} = V_{\text{rms}} I_{\text{rms}} = \frac{100 \cdot 100}{|Z|} = \frac{100 \cdot 100}{\frac{1}{\sqrt{0.5^2 + 0.375^2}}} = 10000 \sqrt{0.5^2 + 0.375^2} = 6250$$

$$\text{Apparent power} = |S| \quad \left\{ \begin{array}{l} S = V_{\text{rms}} I_{\text{rms}} (\cos \theta + j \sin \theta) \\ |S| = V_{\text{rms}} I_{\text{rms}} \end{array} \right.$$

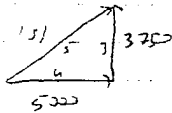

$$|S| = \frac{5000}{0.8} = 6250 \text{ VA}$$

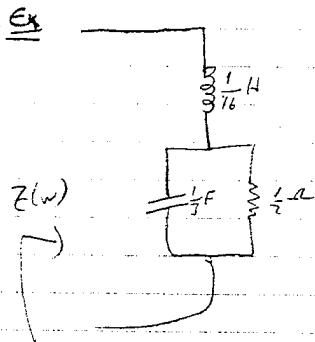

$$Z(w) = j\omega \frac{1}{16} + \frac{3}{\frac{1}{j\omega} + \frac{1}{2}}$$

$$Z(w) = \frac{j\omega}{16} + \frac{3}{6 + j\omega} = \frac{j\omega}{16} + \frac{3(6 - j\omega)}{36 + \omega^2}$$

$$Z(w) = \frac{j 36\omega + j\omega^3 + 288 - j48\omega}{16(36 + \omega^2)}$$


① $\omega = \sqrt{12} \rightarrow Z(w) \Big|_{\omega = \sqrt{12}} = \frac{288}{16(36 + 12)}$

$$Z(w) = \frac{288 + j\omega(\omega^2 - 12)}{16(36 + \omega^2)}$$

② $\omega > \sqrt{12} \rightarrow$ Inductive load

③ $\omega < \sqrt{12} \rightarrow$ Capacitive load

Superposition in AC Power

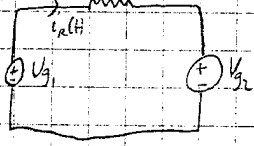

$$V_{11} = V_1 \cos(\omega_1 t + \theta_1) \quad \omega_1 \neq \omega_2$$

$$V_{22} = V_2 \cos(\omega_2 t + \theta_2)$$


$$i_R(t) = I_1 \cos(\omega_1 t + \phi_1) + I_2 \cos(\omega_2 t + \phi_2) \quad (\text{By superposition principle})$$

$$P_{av} = \frac{1}{T} \int_0^T (i_R(t))^2 R dt \rightarrow P_{av} = \lim_{T \rightarrow \infty} \frac{1}{T} \int_0^T (i_R(t))^2 R dt$$

$$i_R^2(t) = I_1^2 \cos^2(\omega_1 t + \phi_1) + I_2^2 \cos^2(\omega_2 t + \phi_2) + 2 I_1 I_2 \cos(\omega_1 t + \phi_1) \cos(\omega_2 t + \phi_2)$$

$$P_{av} = (I_1^{rms})^2 R + (I_2^{rms})^2 R + \frac{2}{T} \int_0^T \frac{1}{2} (\cos((\omega_1 + \omega_2)t + \phi_1 + \phi_2) + \cos((\omega_1 - \omega_2)t + \phi_1 - \phi_2)) dt$$


Ex

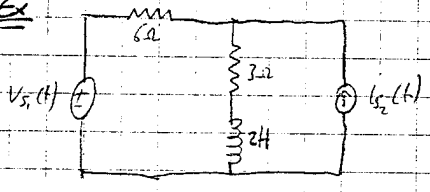

$$v_s(t) = 6 \cos(3t) \text{ V} \quad P_{3\Omega}^{avg} = ?$$


$$i_s(t) = 2 \cos(4t + 33^\circ) \text{ A}$$

$\omega = 3$

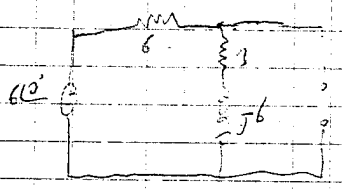

$$i_2 = \frac{6 \angle 0^\circ}{9 + j6} = \frac{2}{3 + j2} = \frac{2(3 - j2)}{13} = \frac{2\sqrt{13} \angle (-33.7^\circ)}{13} \rightarrow I_{2,rms} = \frac{2}{\sqrt{13}} \frac{1}{\sqrt{2}} = \frac{\sqrt{2}}{\sqrt{13}}$$

$\omega = 4$

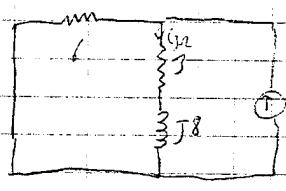


$$i_2 = \frac{2 \angle 0^\circ}{9 + j8} = \frac{12 \angle 3^\circ}{\sqrt{145} \angle 41.7^\circ} = \frac{12}{\sqrt{145}} \angle (-38.7^\circ), \quad I_{2,rms} = \frac{6\sqrt{2}}{\sqrt{145}}$$

$$i_2(t) = 0.555 \cos(3t - 33.69^\circ) + 0.997 \cos(4t - 11.634^\circ) \text{ A}$$

$$P_{av} = P_{av}^{\omega=3} + P_{av}^{\omega=4} = (I_{rms}^{\omega=3})^2 \cdot 3 + (I_{rms}^{\omega=4})^2 \cdot 1 = 0.462 + 1.491 = 1.953 \text{ Watt}$$

Maximum Power Transfer

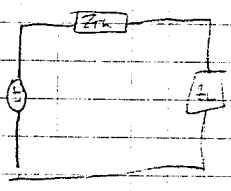

v_s, R_s fixed

What should be the value for R_L

such that P_{av} of the load (R_L) is maximized?

$R_L = R_s^*$ is the max. power transfer solution

Proof

$$P_{load} = I_{rms}^2 \cdot R_L = \frac{1}{2} \left| \frac{V_{oc}}{(R_{Th} + jX_{Th}) + (R_L + jX_L)} \right|^2 \cdot R_L$$

$$P_{load}(R_L, X_L) = \frac{1}{2} \frac{(V_{oc})^2}{(R_{Th} + R_L)^2 + (X_{Th} + X_L)^2} \cdot R_L \Rightarrow \frac{\partial P_{load}}{\partial R_L} = 0 \Rightarrow \frac{\partial P_{load}}{\partial X_L} = 0$$

solve together GIPTA

d) Active efficiency

$$\text{efficiency} = \frac{\text{Real Power supplied to load}}{\text{Real Power supplied by source}}$$


$$\rightarrow \text{p.f.} = 0.85 \quad \text{eff} = \frac{100}{100 + 28.6} = 77.1\%$$

$$\rightarrow \text{p.f.} = 0.95 \quad \text{eff} = \frac{100}{100 + 22} = 82.1\%$$


Ex Load requires 2 kW at 0.75 p.f. lagging at 220 V (RMS)

Calculate the reactive power supplied by the compensating capacitor to make p.f. 0.9 and find the impedance ^{of the capacitor} and assuming 50 Hz, 220 V (RMS) system find the capacitor value in terms of Farads.


Before

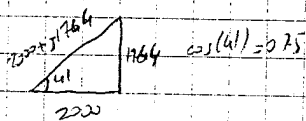

After

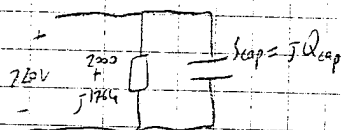

$$S_{\text{before}} = 2000 + j1764$$

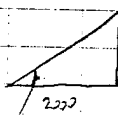

p.f. = 0.9

$$\cos(25) = 0.9$$

$$\Rightarrow Q_{\text{cap}} = 796$$

$$\Rightarrow S_{\text{cap}} = -j796$$

$$\frac{|S_{\text{cap}}|}{220} = \frac{796}{220} = 3.61 \text{ A} = I (\text{RMS})$$

$$\Rightarrow S_{\text{cap}} = I_{\text{RMS}}^2 Z_{\text{cap}} = -j796 \Rightarrow Z_{\text{cap}} = \frac{-j796}{(3.61)^2} = -j61.07$$


$$Z_{\text{cap}} = \frac{-j}{\omega C} \Rightarrow +j61.07 \Rightarrow C = \frac{1}{2\pi \times 50 \times 61.07} = 52 \mu\text{F}$$

Watt-Ampere Method:

We make use of conservation of complex power in the Watt-Ampere method

$$\sum_{k=1}^{\text{\# of generators}} S_k^{\text{supplied}} = \sum_{k=1}^{\text{\# of absorbing elements}} S_k^{\text{absorbed}}$$

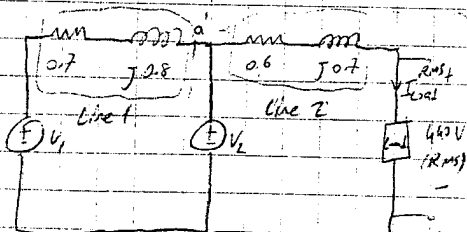Ex Two generators supply 10 kW load at 0.8 p.f. lagging. The generator-2 supplies 5 kW at 0.6 p.f. lagging. Find the voltages of V_1 and V_2 (RMS), the apparent power of generator-1 and p.f. of generator-1



$$S_{\text{sup}} = 53000 + j6666 \text{ VA}$$

$$S_L = 10000 + j7500 \text{ VA}$$

$$I_{Load}^{RMS} = \frac{|S_{Load}|}{V_{Load}^{RMS}} = \frac{10000/0.8}{440} = \frac{12500}{440} = 28.4 \text{ A RMS}$$

$$S_{Line2} = (I_{Load}^{RMS})^2 (0.6 + j0.7) = 484 + j565$$

$$S_{Load+Line2} = 10484 + j8065$$

$$|S_{Load+Line2}| = I_{Load}^{RMS} V_2^{RMS}$$

$$\sqrt{10484^2 + 8065^2} = (28.4) V_2^{RMS}$$

$$V_2^{RMS} = 466 \text{ V RMS}$$

$$S_{right\ of} = S_{Load+Line2} = S_{G2} = 5484 + j1339$$

$$\Rightarrow |S_{right\ of}| = I_{Line1}^{RMS} V_{a-a'}^{RMS}$$

$$\sqrt{5484^2 + 1339^2} = I_{Line1}^{RMS} 466$$


$$I_{Line1}^{RMS} = 12.14 \text{ A}$$

$$\Rightarrow S_{Line1} = (I_{Line1}^{RMS})^2 (0.7 + j0.8) = 103 + j118$$

$$S_{G1}^{supp} = S_{Line1} + S_{right\ of} = 5587 + j1316$$

$$|S_{G1}^{supp}| = V_1^{RMS} I_{Line1}^{RMS} \Rightarrow V_1^{RMS} = \frac{\sqrt{5587^2 + 1316^2}}{12.14} = V_1^{RMS} = 477 \text{ V}$$

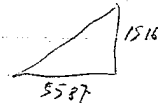
$$p.f. \text{ of generator 1} = \frac{5587}{\sqrt{5587^2 + 1316^2}} \text{ lagging} = 0.965$$



05/04/2010
Pazartesi

3-PHASE BALANCED CIRCUITS


Y connection

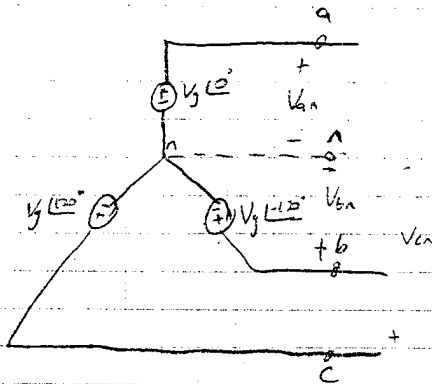


$$V_{an} = V_y \angle 0^\circ$$

$$V_{bn} = V_y \angle -120^\circ$$




$$V_{cn} = V_y \angle 120^\circ$$

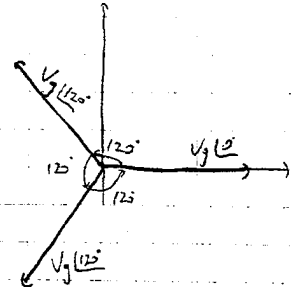

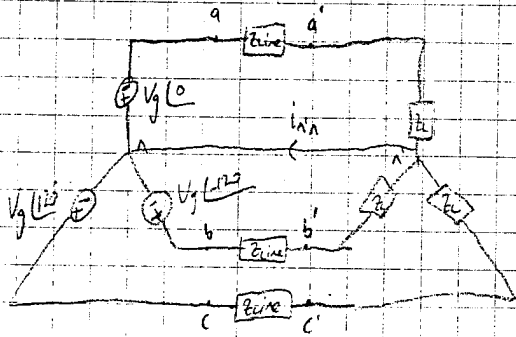


balanced 3- ϕ system

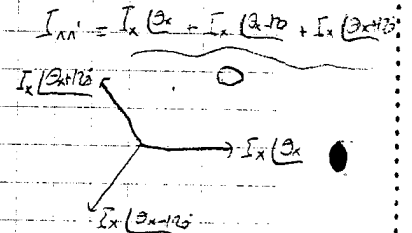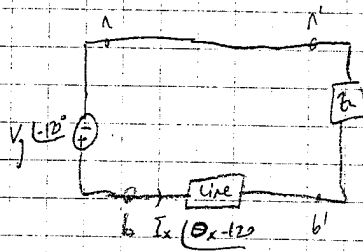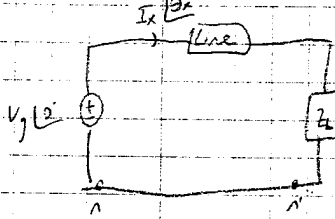Note Solving only phase a is equivalent to solving all phases



Phase-Line Currents/Voltages

Y Connection

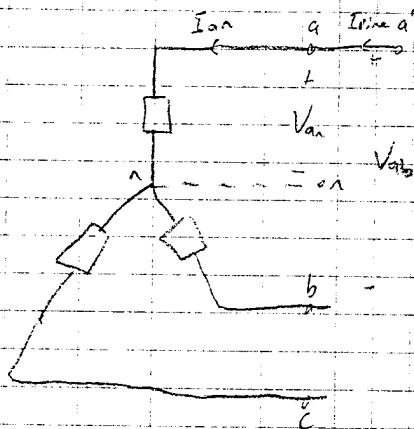

$V_{a_n}, V_{b_n}, V_{c_n}$: Phase voltages

V_{ab}, V_{bc}, V_{ca} : Line voltages (Line to Line)

$$V_{ab} = V_a - V_b = V_{a_n} - V_{b_n} = V_{a_n} + V_{b_n}$$

I_{a_n} : Phase current

$I_{a'}$: Line current


} Y connection $\Rightarrow I_{a'} = I_{a_n}$

Phase voltage \neq Line voltage

Phase current \neq Line current

} For Y connection

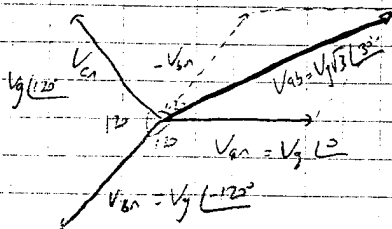Line-Voltage, Phase-Voltage Relation for Y-Connection



$$V_{ab} = \sqrt{3} V_g \angle 30^\circ$$


$$V_{bc} = \sqrt{3} V_g \angle -30^\circ$$

$$V_{ca} = \sqrt{3} V_g \angle 90^\circ$$

Line voltages

Review

08/04/2010
Perseus

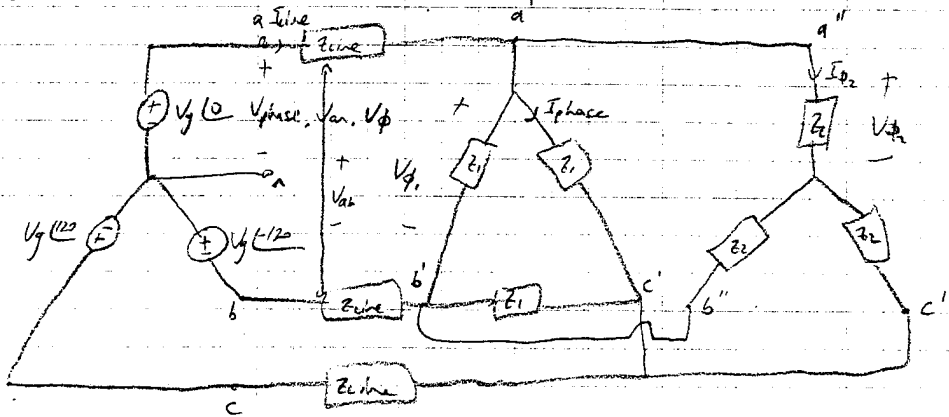

V_ϕ : phase voltage

V_{line} : Line voltage (V_{ab}, V_{bc}, V_{ca})

I_ϕ : Phase current

I_{line} : Current passing through the line (Z_{line})

(Current in a single phase of the component)

Power Relations for Y Connection

$$P_{tot} = 3 P_\phi \text{ per phase}$$

$$P_\phi = |I_\phi, rms|^2 R_\phi$$

$$S_{tot} = 3 S_\phi$$


$$S_\phi = |I_\phi, rms|^2 (R_\phi + jX_\phi)$$

$$P_{tot} = \text{Re}\{S_{tot}\} = 3 \text{Re}\{S_\phi\}$$


$$= 3 \text{Re}\{|I_\phi, rms|^2 |Z_\phi| e^{j\angle Z_\phi}\}$$

$$= 3 \text{Re}\{|I_\phi, rms| \cdot |V_\phi, rms| e^{j\angle Z_\phi}\}$$

$$= 3 |I_\phi, rms| |V_\phi, rms| \cos(\angle Z_\phi) = \sqrt{3} |V_{line, rms}| |I_{line, rms}| \cos(\angle Z_\phi)$$

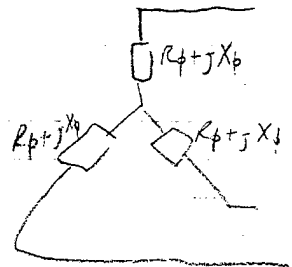

Δ - Connection

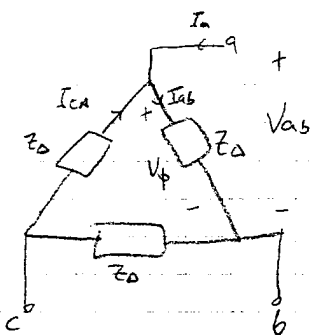

For Δ - load;

$$I_a = I_{ab} - I_{ca}$$

$$|V_{line, rms}| = |V_\phi, rms|$$

$$= \frac{V_{ab}}{Z_D} - \frac{V_{ca}}{Z_D}$$

$$|I_{line, rms}| = \sqrt{3} |I_\phi, rms|$$

$$= \frac{V_\phi \angle 0^\circ}{Z_D} - \frac{V_\phi \angle -120^\circ}{Z_D}$$

$$= I_\phi - I_\phi \angle -120^\circ$$

$$I_a = \sqrt{3} I_\phi \angle 30^\circ$$

Generators are Y connected


In general, not Δ connected

Power Calculation For Δ load:

$$P_{tot} = 3P\phi = 3 \operatorname{Re} \{ V_{\phi, rms} I_{\phi, rms} e^{j\angle\phi} \}$$

$$= 3 \operatorname{Re} \left\{ V_{line, rms} \frac{I_{line, rms}}{\sqrt{3}} e^{j\angle\phi} \right\}$$
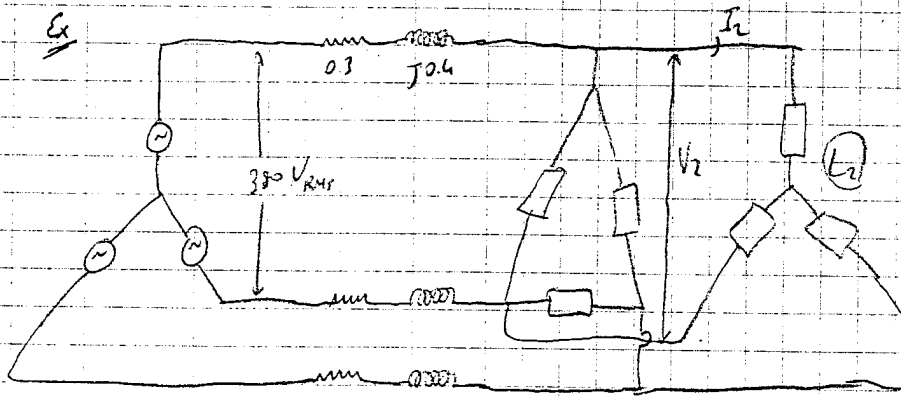
$$= \sqrt{3} V_{line, rms} I_{line, rms} \cos(\angle\phi) \leftarrow \text{same formula for both } \Delta \text{ and } Y \text{ loads.}$$




Generator { produces 380 V_{rms} line to line voltage
 { produces 9 kW and 9 kVAR

Load 1 6 kW at 0.6 p.f. lagging $\rightarrow (6000 + j8000)$

Find V_L , I_L and power absorbed by L_2 .

① Using single phase equivalent circuit.

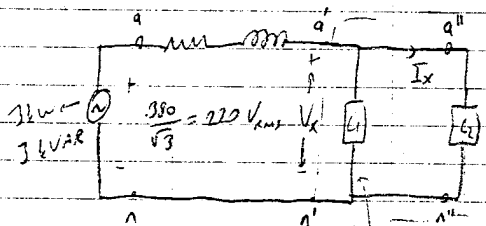

$$S_G = 3 + j3 \text{ kVA}$$

$$|S_G| = 3\sqrt{2} \text{ kVA} = 220 I_{rms} \rightarrow I_{rms} = 19.3 \text{ A}$$

$$S_{line} = I_{s, rms}^2 (0.3 + j0.4) = 112 + j149$$

$$S_{L1} + S_{L2} = 3000 + j3000 - (112 + j149) = 2888 + j2851$$

$$|S_{L1+L2}| = V_{L, rms} |I_{s, rms}|$$

$$6.058 \text{ kVA} = V_{L, rms} \cdot 19.3$$

$$V_{L, rms} = 210.3 \Rightarrow V_L = \sqrt{3} V_L = 364 \text{ V}_{rms}$$

$$S_{L2} = S_{L1+L2} - S_{L1}$$


$$S_{L2} = \frac{2888 + j2851 - (6000 + j8000)}{3} = 888 + j187$$

$$|S_{L2}| = |V_L| \cdot |I_{L, rms}| \Rightarrow I_{L, rms} = 4.31 \text{ A}_{rms} \Rightarrow I_L = I_{L, rms} = 4.31 \text{ A}_{rms}$$

power absorbed by load 2

$$S_{L2}^{tot} = 3S_{L2} = \boxed{2664 + j561}$$

② Single Line Diagram

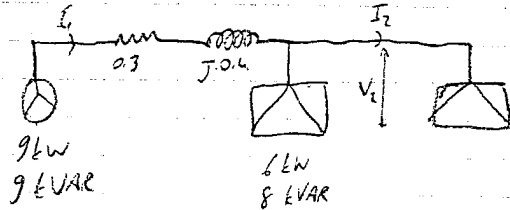

For both loads

3 ϕ Total power quantities

$$\left\{ \begin{aligned} P_{load} &= \sqrt{3} V_{line,rms} I_{line,rms} \cos(\phi) \quad (\text{4 } \phi_{load}) \\ Q_{load} &= \sqrt{3} V_{line,rms} I_{line,rms} \sin(\phi) \quad (\text{4 } \phi_{load}) \\ S_{load} &= P_{load} + jQ_{load} \end{aligned} \right.$$

① Find $I_1 \rightarrow \frac{S_{generator}^{total}}{3 \times 2000\sqrt{2}} = \sqrt{3} \frac{V_{line,rms}^{generator} I_{line}^{generator}}{380} \Rightarrow I_{line}^{generator} = 19.3 \text{ Arms}$


② Line losses $S_{line} = 3(19.3)^2(0.3 + j0.4) = 336 + j447$

③ Power left for L_1 and $L_2 \rightarrow S_{L1} + S_{L2} = 8664 + j8553$

④ $\frac{|S_{L1+L2}|}{12174.5} = \sqrt{3} \frac{|V_{L1+L2}^{line}| |I_{L1+L2}^{line}|}{19.3} \Rightarrow |V_{L1+L2}^{line}| = 364 \text{ V rms}$

⑤ $S_{L2} = 8664 - 6000 + j(8553 - 8000) = 2664 + j561$

12/04/2010
Pazartesi

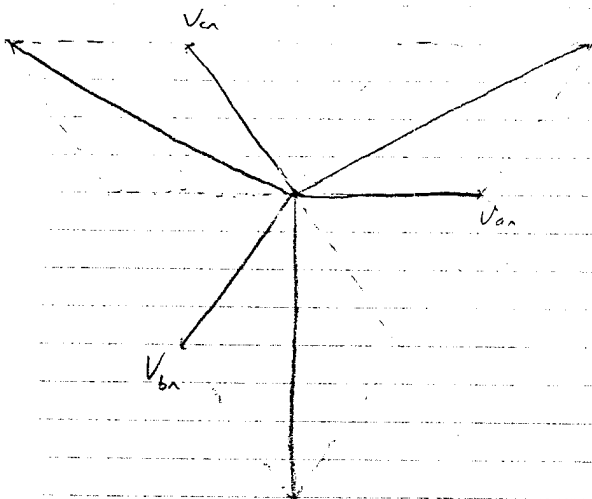


ω ← phasor diagram rotates ω rad/sec


$a \rightarrow b \rightarrow c$ (positive sequence) \Rightarrow (a at 0°, then b at 120°, c at 240°)

$a \rightarrow c \rightarrow b$ (negative sequence)

Δ-Y Transformation

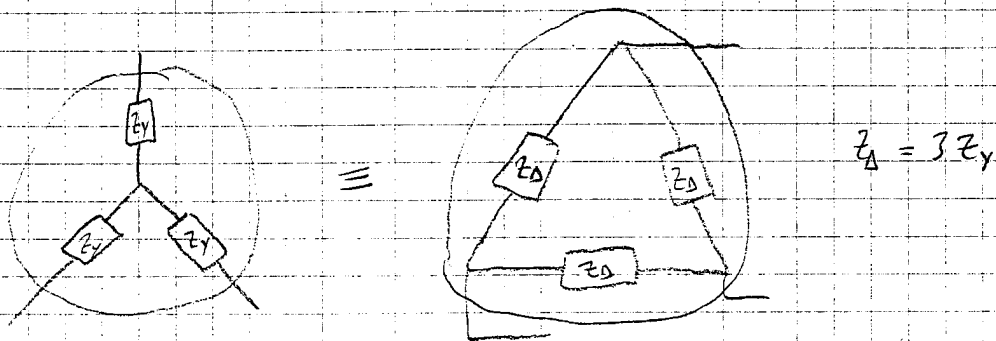

Ex. ZPS IV Problem 6

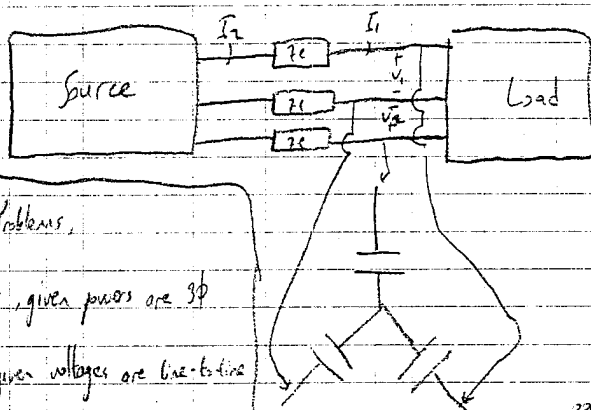

A balanced 3φ circuit

Load: 400 kW $pf = \frac{1}{\sqrt{2}}$ lagging

$V_L = 400 \angle 0^\circ$ $V_C = 400 \angle -30^\circ$ V_{rms}

$Z_C = 0.27 + j0.16$

In 3φ problems,

① by default, given powers are 3φ

② by default, given voltages are line-to-line


a) Switches are open. Find I_L , V_{eff} , the complex power supplied by the source and efficiency.

$$P_{tot} = 400 \text{ kW} = \sqrt{3} \frac{V_{line}}{\sqrt{3}} \frac{I_{line}}{\sqrt{3}} \cos(\theta_{\phi}) \Rightarrow I_L = 816.5 \text{ Arms}$$

$$S_{line}^{tot} = 3 I_{line}^2 Z_C = 140 + j320 \text{ kVA}$$

$$S_{supp}^{tot} = 540 + j(320 - 400) = 540 + j70 \text{ kVA}$$



$$Eff = \frac{400}{540} = 74\%$$

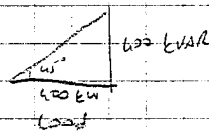

b) Switches are closed, and pf of the compensated load becomes 0.8 lagging. Find the susceptance of the capacitors in the bank, I_L , I_C , V_{eff} , complex power supplied by the load

b) Before Comp.

After Comp.

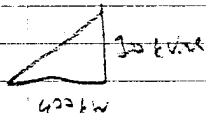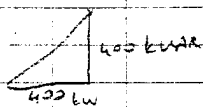

$$|S_{3\phi}^{load}| = \sqrt{3} V_{line} I_{line}$$

$$500 = \sqrt{3} 400 I_{line} \Rightarrow I_{line} = I_L = 721.6 \text{ A}$$

$$S_{line}^{tot} = 3 (I_{line,rms})^2 Z_C = 109 + j250 \text{ kVA}$$

$$S_{supp}^{tot} = 509 + j555 \text{ kVA}$$


$$Eff = \frac{400}{509} = 78\%$$

$$V_{line}^{supp} = \frac{|S_{supp}^{tot}|}{\sqrt{3} |I_{supp}|} = 600 \text{ Vrms}$$


$\leftarrow 721.6$

$$S_{cap-bank} = -j100 \text{ kVA}$$

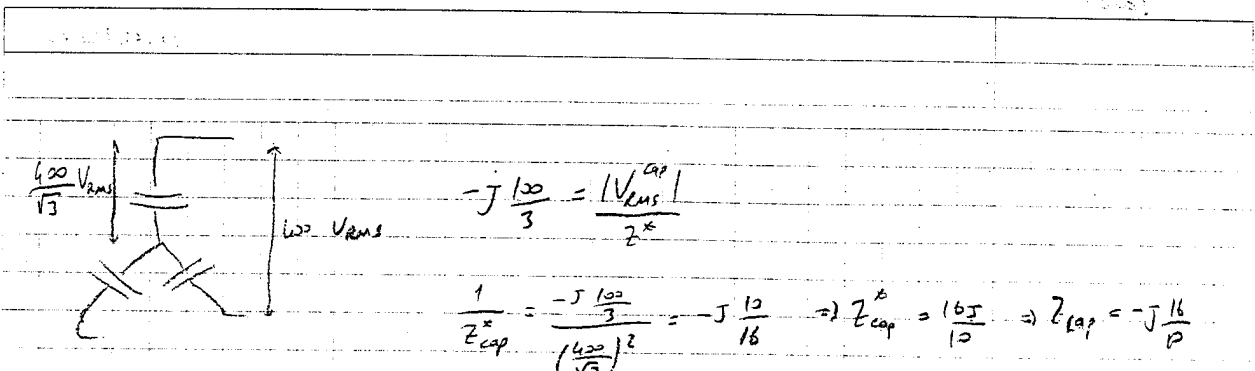
$$S_p^{supp} = -j\frac{100}{3} \text{ kVA}$$



3-φ Power Measurement

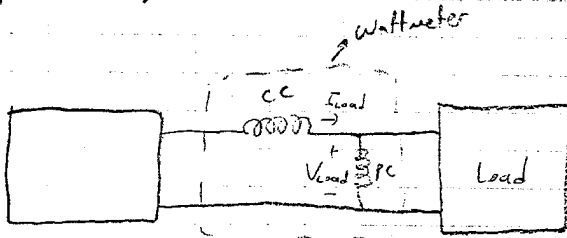

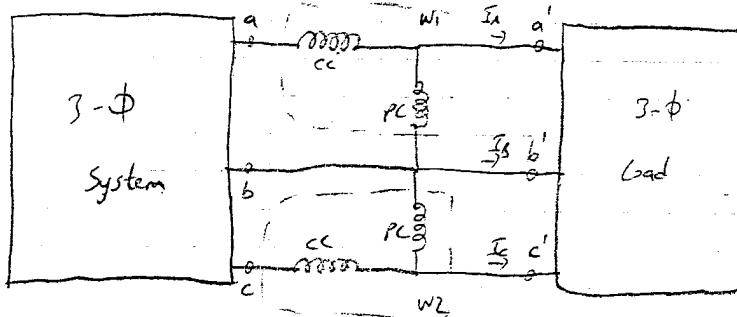CC: Current coil (low impedance)
 PC: Potential coil (high impedance)




Measurement of $W_1: \text{Re}\{V_{ab} I_A^*\}$

Measurement of $W_2: \text{Re}\{V_{cb} I_C^*\}$

$V_{a'b'} = V_{line} \angle 30^\circ$

$V_{b'c'} = V_{line} \angle -90^\circ$

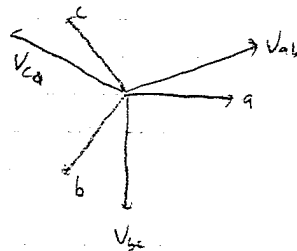


$I_A = I_{line} \angle -\theta$

$I_C = I_{line} \angle -\theta + 120^\circ$

$W_1 = \text{Re}\{V_{line} \angle 30^\circ I_{line} \angle -\theta\} = V_{line} I_{line} \cos(\theta + 30^\circ)$

$W_2 = \text{Re}\{-V_{line} \angle 90^\circ I_{line} \angle -\theta + 120^\circ\} = V_{line} I_{line} \cos(\theta - 30^\circ)$

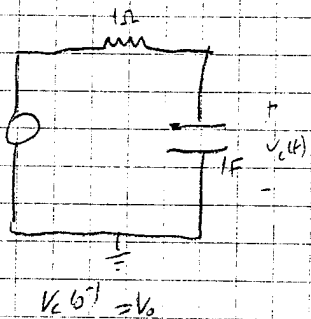$W_1 + W_2 = V_{line} I_{line} (\cos(\theta + 30^\circ) + \cos(\theta - 30^\circ)) = \sqrt{3} V_{line} I_{line} \cos \theta \rightarrow$ The total power absorbed by the load



$$V_C(t) = -V_C(t) + V_S(t)$$

$$V_C(0^+) = V_0$$

s-domain

$$\mathcal{L}\{V_C(t)\} = \mathcal{L}\{-V_C(t) + V_S(t)\}$$

$$sV_C(s) - \underbrace{V_C(0^+)}_{V_0} = -V_C(s) + V_S(s)$$

$$(s+1)V_C(s) + V_0 = -V_C(s) + V_S(s)$$

$$(s+1)V_C(s) = V_0 + V_S(s)$$

$$V_S(t) = \delta(t) \Rightarrow V_S(s) = 1 \Rightarrow V_{C_{25}}(s) \leftarrow H(s) = \frac{1}{s+1}$$

$$h(t) = e^{-t}u(t)$$

$$V_C(s) = \frac{1}{s+1} V_C(s) + \frac{V_0}{s+1}$$

$$\underbrace{V_C(s)}_{V_{C_{25}}(s)} \quad \underbrace{V_C(s)}_{V_{C_1}(s)}$$

$$V_C(t) = V_{C_{25}}(t) + V_0 e^{-t}$$

$$\underline{u(t)} = \frac{1}{s} \quad V_{C_{25}}(s) = \frac{1}{s+1} \frac{1}{s} = \frac{a}{s+1} + \frac{b}{s} \quad a = -1 \quad b = 1$$

$$\underline{t u(t)} \rightarrow \frac{1}{s^2}$$

$$= \frac{1}{s+1} + \frac{1}{s} \Rightarrow V_{C_{25}}(t) = -e^{-t} + 1, t > 0$$

$$V_{C_{25}}(s) = \frac{1}{s+1} \frac{1}{s^2} = \frac{a}{s+1} + \frac{b}{s} + \frac{c}{s^2} \quad a = 1, b = -1, c = 1$$

$$V_{C_{25}}(t) = 1e^{-t} - t + t^2$$

$$\underline{e^t u(t)} \rightarrow \frac{1}{s-1}$$

$$\underline{e^{-t} u(t)} \rightarrow \frac{1}{s+1}$$

$$V_{C_{25}}(s) = \frac{1}{(s+1)(s-1)} = \frac{a}{s+1} + \frac{b}{s-1}$$

$$V_{C_{25}}(s) = \frac{1}{(s+1)^2}$$

$$a = -\frac{1}{2} \quad b = \frac{1}{2}$$

$$V_{C_{25}}(t) = \frac{1}{2} e^{-t} - \frac{1}{2} t e^{-t}, t > 0$$

$$V_{C_{25}}(t) = -\frac{1}{2} e^{-t} + \frac{1}{2} t e^{-t}, t > 0$$

$$\underline{\cos(t) u(t)} \rightarrow \frac{s}{s^2+1}$$

$$V_{C_{25}}(s) = \frac{s}{(s+1)(s^2+1)} = \frac{a}{s+1} + \frac{bs+c}{s^2+1}$$

$$a = -\frac{1}{2} \quad b = \frac{1}{2} \quad c = \frac{1}{2}$$

$$V_{C_{25}}(t) = -\frac{1}{2} e^{-t} + \frac{1}{2} \cos(t) + \frac{1}{2} \sin(t)$$

$$i_1(t) + i_2(t) - i_3(t) = 0$$

$$v_R(t) = R i_R(t)$$

$$v_L(t) = L \dot{i}_L(t)$$

$$i_C(t) = C \dot{V}_C(t)$$

$$I_1(s) + I_2(s) - I_3(s) = 0$$


$$V_R(s) = R I_R(s)$$

$$V_L(s) = L \{s I_L(s) - I_{L0}\}$$

$$I_C(s) = s C V_C(s) - C V_{C0}$$

$$V_L(s) = s L I_C(s) - L I_{C0}$$
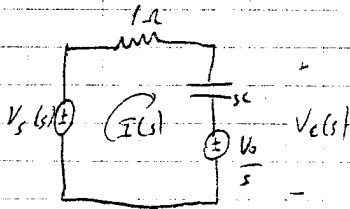
$$V_C(s) = \frac{1}{sC} I_C(s) + \frac{V_{C0}}{s}$$




$$V_C(s) = \frac{V_0}{s} + \frac{1}{\frac{1}{s} + 1} (V_s(s) - \frac{V_0}{s})$$



$$= \frac{1}{s+1} V_s(s) + \frac{V_0}{s} \left(\frac{1-s}{s+1} \right)$$

$$V_C(s) = \frac{1}{s+1} V_s(s) + \frac{V_0}{s+1}$$

Ex

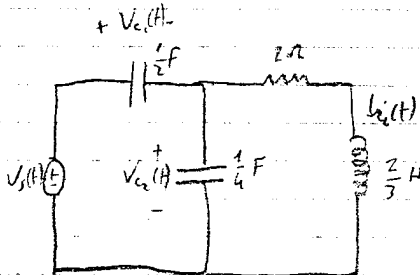

s-domain

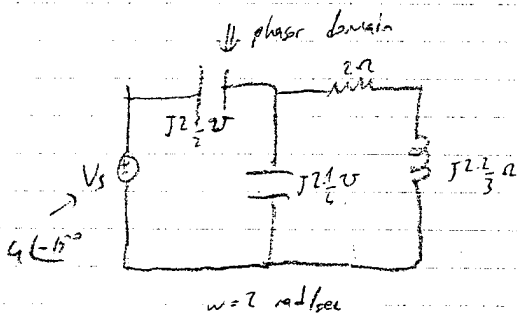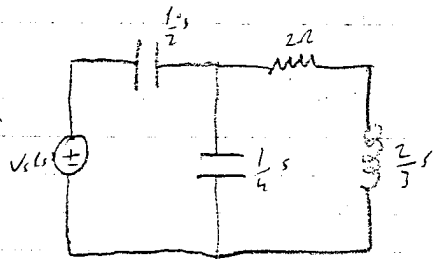

$$Z_0 = \frac{1}{\frac{1}{s}} \parallel \left(2 + \frac{2s}{3} \right) = \frac{\frac{4}{s} \left(2 + \frac{2s}{3} \right)}{\frac{4}{s} + 2 + \frac{2s}{3}} = \frac{8 \left(\frac{s}{3} + 1 \right)}{4 + 2s + \frac{2s^2}{3}} = \frac{4(s+3)}{s^2 + 3s + 6}$$

$$V_C(s) = \frac{Z_0}{2 + \frac{1}{\frac{1}{s}}} V_s(s)$$

$$\Rightarrow V_C(s) = \frac{4(s+3)}{s^2 + 3s + 6} V_s(s) = \frac{2}{3} \frac{s(s+3)}{(s+1)(s+2)} V_s(s)$$

$H(s)$

$$H(s) = \frac{2}{3} - \frac{4}{3} \frac{1}{(s+1)(s+2)} = \frac{2}{3} - \frac{4}{3} \left(\frac{1}{s+1} - \frac{1}{s+2} \right)$$

$$h(t) = \frac{2}{3} \delta(t) - \frac{4}{3} e^{-t} + \frac{4}{3} e^{-2t}$$

S-DOMAIN ANALYSIS

19/04/2019
Parvathi

$$(D^2 + 3D + 2)x(t) = f(t)$$

↓

$$\begin{bmatrix} \dot{x}_1(t) \\ \dot{x}_2(t) \end{bmatrix} = \begin{bmatrix} - & - \\ - & - \end{bmatrix} \begin{bmatrix} x_1(t) \\ x_2(t) \end{bmatrix} + \begin{bmatrix} 1 \\ 0 \end{bmatrix} f(t)$$

Char. eqn: $\rightarrow \lambda^2 + (-)\lambda + (-) = 0$

Laplace transform

$$F(s) = \int_{-\infty}^{\infty} f(t)e^{-st} dt \Rightarrow \mathcal{L}\{f(t)\} = F(s)$$

$s \in \mathbb{C}$
 $s \in$ Region of Convergence (R.O.C)
 (for which Laplace Transform integral converges)

Ex: $\mathcal{L}\{u(t)\} = \int_{-\infty}^{\infty} u(t)e^{-st} dt = \int_0^{\infty} e^{-st} dt = \frac{e^{-st}}{-s} \Big|_{t=0}^{t=\infty} = e^{-s\infty} - \left(-\frac{1}{s}\right) = \frac{1}{s}$

if real $s > 0$
 $\text{Re}\{s\} > 0$
 R.O.C

Types of Laplace Transforms:

1) Unilateral

$$F(s) = \int_0^{\infty} f(t)e^{-st} dt$$

2) Bilateral

$$F(s) = \int_{-\infty}^{\infty} f(t)e^{-st} dt$$

More interesting since we have initial value problems.

Ex: $\mathcal{L}\{f'(t)\} = \int_0^{\infty} f'(t)e^{-st} dt = e^{-st}f(t) \Big|_{t=0}^{t=\infty} - \int_0^{\infty} f(t)(-se^{-st}) dt$

$$= [e^{-\infty s} f(\infty) - e^{-0} f(0)] + s \int_0^{\infty} f(t)e^{-st} dt = sF(s) - f(0)$$

Ex: $\mathcal{L}\{f''(t)\} = \mathcal{L}\{g'(t)\} = sG(s) - g(0)$ $g(t) = f'(t) = s \mathcal{L}\{f(t)\} - f(0)$

$$= s(sF(s) - f(0)) - f'(0) = s^2 F(s) - sf(0) - f'(0)$$

Ex: $(D^2 + 3D + 2)v_c(t) = f(t) \leftarrow f(t) = u(t)$

$$v_c(0) = v_0 \quad v_c'(0) = v_0'$$

Let there be a solution;

$$2v_c(t) \Rightarrow 2V_c(s)$$

$$3v_c'(t) \Rightarrow 3sV_c(s) - 3v_0'$$

$$+ v_c''(t) \Rightarrow s^2 V_c(s) - sv_0 - v_0'$$

$$\rightarrow (D^2 + 3D + 2)v_c(t) \Rightarrow V_c(s)[s^2 + 3s + 2] - v_0(s+3) - v_0'$$

$$\frac{1}{s} \Leftrightarrow \frac{1}{s}$$

$$V_c(s)[s^2 + 3s + 2] - v_0(s+3) - v_0' = \frac{1}{s}$$

$$V_c(s) = \frac{\frac{1}{s} + v_0 + v_0'(s+3)}{s^2 + 3s + 2}$$

$$V_c(s) = \frac{1+sV_0+s(s+3)V_0}{s(s^2+3s+2)} = \frac{(1+sV_0+s(s+3))V_0}{s(s+1)(s+2)}$$

$$= \frac{A}{s} + \frac{B}{s+1} + \frac{C}{s+2}$$

$$A = \frac{1}{2} \quad B = 2V_0 + V_0 - 1 \quad C = \frac{1-2V_0-2V_0}{2}$$

$$V_c(s) = \frac{1}{2s} + \frac{2V_0 + V_0 - 1}{s+1} + \frac{1-2V_0-2V_0}{2(s+2)}$$


$$V_c(t) = \frac{1}{2} u(t) + (2V_0 + V_0 - 1) e^{-t} + \frac{(1-2V_0-2V_0)}{2} e^{-2t}$$

Ex) $F(s) = \frac{(s-2)}{s(s+1)^2}$

$$F(s) = \frac{A}{s} + \frac{B}{s+1} + \frac{C}{(s+1)^2} \Rightarrow A = -2 \quad C = 3 \quad B = 2$$

Circuit Response using S-domain Methods

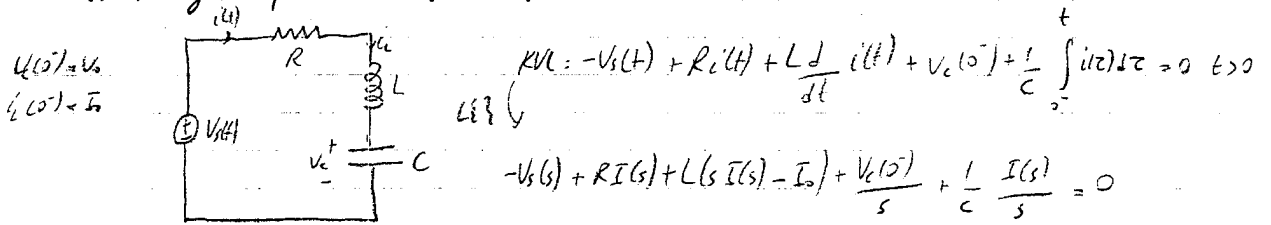1) Taking Laplace Transform of Time-Domain Relation



$$\Rightarrow I(s) \left[sL + R + \frac{1}{Cs} \right] = V_0(s) + L I_0 - \frac{V_0}{s} \Rightarrow I(s) = \frac{Cs V_0(s) + sL C I_0 - C V_0}{s^2(LC) + RCs + 1}$$

$$I(s) = \frac{s V_0(s)/L}{s^2 + \frac{R}{L}s + \frac{1}{LC}} + \frac{s I_0 - \frac{1}{L} V_0}{s^2 + \frac{R}{L}s + \frac{1}{LC}}$$

$\mathcal{L}^{-1}\{ \}$

$$i(t) : \text{complete solution} = i^{(h)}(t) + i^{(p)}(t)$$

22/04/2010

Perseme

a) Let $L = 1 \text{ H}$; $R = 6 \Omega$; $C = 0.04 \text{ F}$; $I_0 = 5 \text{ A}$; $V_0 = 1 \text{ V}$; $V_0(t) = 12 \sin 5t \quad t > 0$

$$\Rightarrow I(s) = \frac{s V_0(s)}{s^2 + 6s + 25} + \frac{s I_0 - 1}{s^2 + 6s + 25}$$

$$V_0(s) = \mathcal{L}\{12 \sin 5t\} = \frac{12 \cdot 5}{s^2 + 25}$$

$$\Rightarrow I_s = \frac{60s}{(s^2 + 6s + 25)(s^2 + 25)} + \frac{s I_0 - 1}{s^2 + 6s + 25}$$

$$(s^2)^2 + 16 = (s+3+j4)(s+3-j4)$$

$$\Rightarrow \bar{I}^{(s)}(s) = \frac{60s}{(s^2 + 6s + 25)(s^2 + 25)} = \frac{K_1}{(s+3+j4)} + \frac{K_1^*}{(s+3-j4)} + \frac{K_2}{(s+5j)} + \frac{K_2^*}{(s-5j)}$$

$$K_1 = -j1.25 \quad K_2 = j$$

$$I^{25}(s) = \frac{j1.25}{s+3-j4} + \frac{-j1.25}{s+3+j4} + \frac{-j}{s-j5} + \frac{j}{s+j5}$$

$$I^{25}(s) = \frac{-10}{(s+3)^2 + 4^2} + \frac{10}{s^2 + 25}$$

Σ{}

$$i^{25}(t) = \underbrace{-\frac{5}{2} e^{-3t} \sin(4t)}_{\text{transient part for 25 solution}} + \underbrace{2 \sin(5t)}_{\text{steady state part of zero state response}}$$

(AC phasor domain analysis gives us this solution)

→ 2nd method → Σ{ } ⇒ $i^{25}(t) = j1.25 e^{-(3-j4)t} - j1.25 e^{-(3+j4)t} - j e^{j5t} + j e^{-j5t}$

← conjugate of each other

$$= 2 \operatorname{Re} \left\{ j1.25 e^{-(3-j4)t} \right\} + 2 \operatorname{Re} \left\{ -j e^{j5t} \right\} = \sum \frac{e^{-3t} \operatorname{Re} \left\{ e^{j(4t+90^\circ)} \right\}}{\cos(4t+90^\circ)} - 2 \operatorname{Re} \left\{ e^{j(5t+90^\circ)} \right\} / \cos(5t+90^\circ)$$

$$= \frac{5}{2} e^{-3t} \sin(4t) + 2 \sin(5t)$$

$$I^{26}(s) = \frac{5s-1}{(s+3)^2 + 4^2} = \frac{K_1}{s+3+j4} + \frac{K_1^*}{s+3-j4} \Rightarrow K_1 = \frac{5}{2} - j2$$

Σ{}

$$i^{26}(t) = 2 \operatorname{Re} \left\{ K_1 e^{-(3+j4)t} \right\} = 2 e^{-3t} \operatorname{Re} \left\{ K_1 e^{-j4t} \right\} = 2 e^{-3t} \left(\frac{5}{2} \cos 4t - 2 \sin 4t \right)$$

$$i^{26}(t) = 2 e^{-3t} \sqrt{\left(\frac{5}{2}\right)^2 + 2^2} \cos(4t - \tan^{-1}\left(\frac{-2}{5/2}\right))$$

b) Step response (Zero-state response for $u(t)$ input)

Same values for R, L, C , etc. $I\{u(t)\} = \frac{1}{s}$

$$I^{25}(s) = \frac{sV_o(s)}{s^2 + 6s + 25}$$

$$\Rightarrow I^{25}(s) = \frac{1}{s^2 + 6s + 25} = \frac{K_1}{s+3-j4} + \frac{K_1^*}{s+3+j4} \Rightarrow K_1 = -\frac{j}{8}$$

$$i^{25}(t) = \frac{1}{4} e^{-3t} \cos(4t - 90^\circ)$$

c) Impulse response

$$\mathcal{L}\{s(t)\} = 1$$

$$I^{TS}(s) = \frac{s V_s(s)}{s^2 + 6s + 25}$$

$$I^{TS}(s) = \frac{s}{s^2 + 6s + 25} = \frac{s+3}{(s+3)^2 + 4^2} - \frac{3}{(s+3)^2 + 4^2}$$

$$i^{TS}(t) = h(t) = e^{-3t} \cos(4t) - \frac{3}{4} e^{-3t} \sin(4t)$$










Poles and Zeros in s-domain

$$I^{TS}(s) = K \frac{\prod_{k=1}^z (s - z_k)}{\prod_{k=1}^p (s - p_k)}$$

a ratio of two polynomials in $\{s\}$ "s-domain"

p_k : Poles of $I^{TS}(s)$ (singularities)

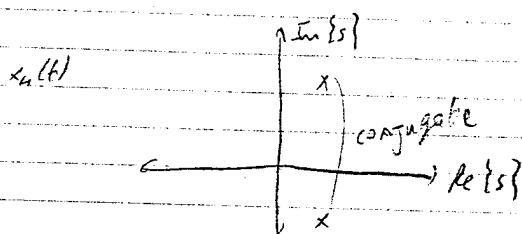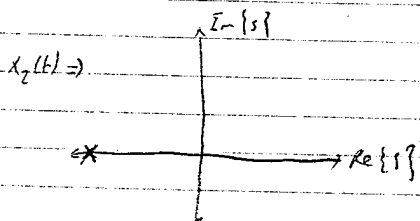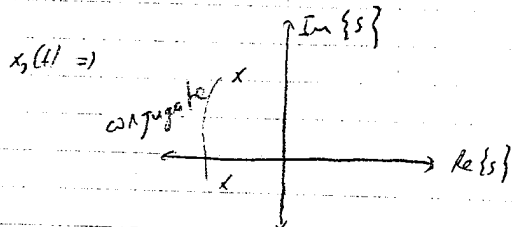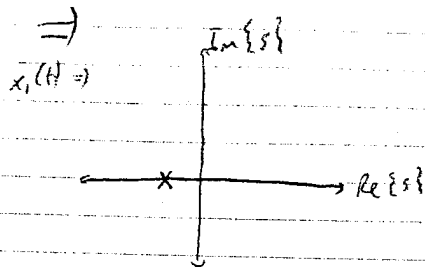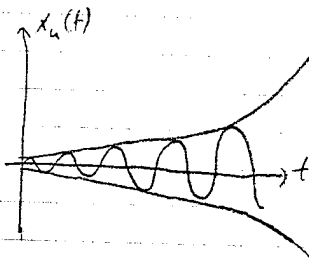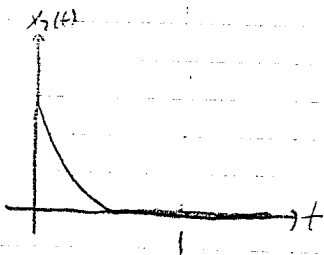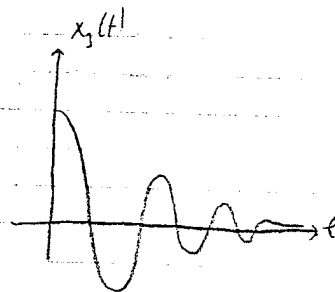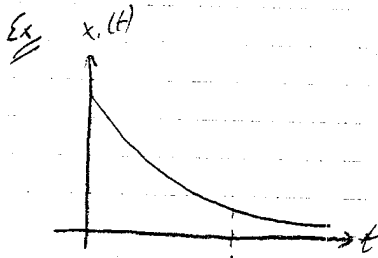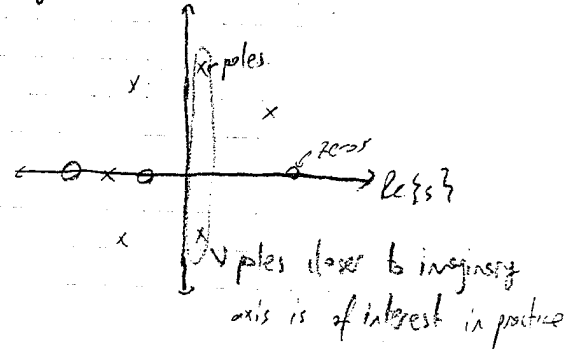z_k : Zeros of $I^{TS}(s)$ ($I^{TS}(s_k) = 0$)



Initial and Final Value Theorems

Initial Value $\Rightarrow \lim_{t \rightarrow 0^+} f(t) = \lim_{s \rightarrow \infty} sF(s)$


Final Value $\Rightarrow \lim_{t \rightarrow \infty} f(t) = \lim_{s \rightarrow 0} sF(s)$

Ex Step response

$i^{ES}(t) = \frac{1}{4} e^{-3t} \sin 4t \iff I^{ES}(s) = \frac{1}{s^2 + 6s + 25}$

$i^{ES}(0^+) = 0 \xrightarrow{\text{initial value theorem}} \lim_{s \rightarrow \infty} s I^{ES}(s) = 0$

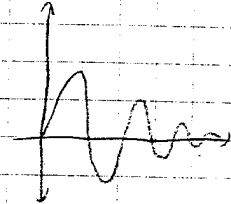$i^{ES}(\infty) = 0 \xrightarrow{\text{final value theorem}} \lim_{s \rightarrow 0} s I^{ES}(s) = 0$



Some Important Details

To use Initial Value Theorem $s = \infty$ should be in R.O.C


To use Final Value Theorem $s = 0$ should be in R.O.C.

Eg. $\mathcal{L}\{\cos(\beta t)\} = \frac{s}{s^2 + \beta^2} \rightarrow$ apply final value theorem $\lim_{s \rightarrow 0} s \cdot \frac{s}{s^2 + \beta^2} = 0$ but,

$\lim_{t \rightarrow \infty} \cos(\beta t)$ does not exist

do not forget R.O.C when $I(s)$ is discussed.

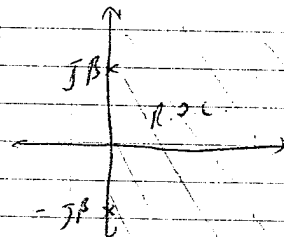$\mathcal{L}\{\cos(\beta t)\} = \frac{s}{s^2 + \beta^2}$ for R.O.C




$I(s) = \int_0^{\infty} \cos(\beta t) e^{-st} dt$

26/04/2010
Parvati

Circuit Components in s-Domain

Capacitor:

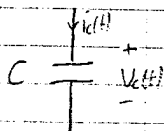


Time Domain

$i_c(t) = C \frac{dv_c(t)}{dt}$
 $v_c(0^-) = V_0$


s-Domain

$I_c(s) = C s V_c(s) - C V_c(0^-)$

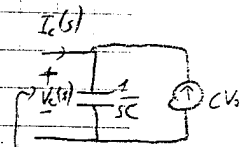
$V_c(s) = \frac{I_c(s)}{sC} + \frac{V_0}{s}$



source transformation

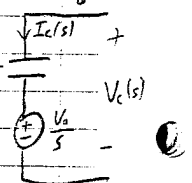

Inductor:

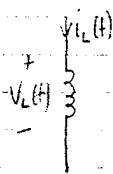

Time Domain



$$v_L(t) = L \frac{di_L(t)}{dt}$$

$$i_L(0^-) = I_0$$

s-Domain

$$V_L(s) = Ls I_L(s) - LI_0$$


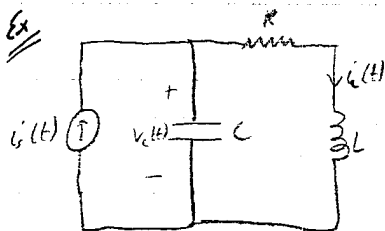
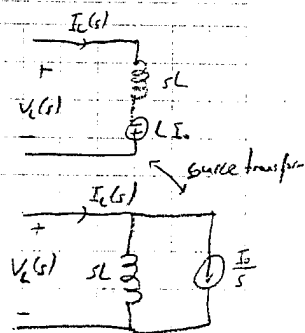
$$I_L(s) = \frac{V_L(s)}{sL} + \frac{I_0}{s}$$



$$v_L(0^-) = V_0$$

$$i_L(0^-) = I_0$$


↳ Substrate equivalent

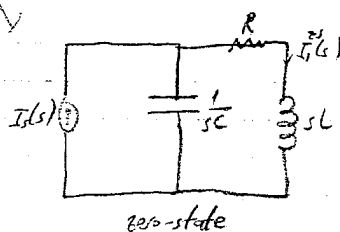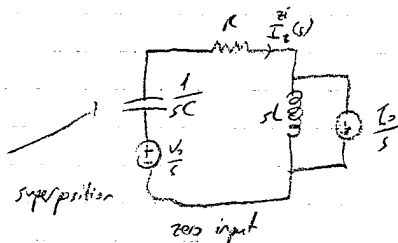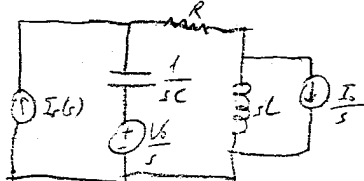

Zero state \Rightarrow

$$I_1^{zs}(s) = I_i(s) \frac{1/sC}{1/sC + R + sL} = \frac{1}{LCs^2 + sRC + 1} I_i(s) = \frac{1/LC}{s^2 + \frac{R}{L}s + \frac{1}{LC}} I_i(s)$$

Zero input \Rightarrow

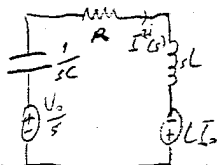

$$I_1^{zi}(s) = \frac{V_0/s + LI_0}{1/sC + R + sL} = \frac{V_0/s + sLI_0}{s^2 + \frac{R}{L}s + \frac{1}{LC}}$$

$$I_1^{zs}(s) = \frac{1}{LC} I_i(s) \Rightarrow \left(s^2 + \frac{R}{L}s + \frac{1}{LC} \right) I_1(s) = \frac{I_i(s)}{LC}$$

$\mathcal{L}^{-1}\{ \}$

$$\left(D^2 + \frac{R}{L}D + \frac{1}{LC} \right) i_L(t) = \frac{i_i(t)}{LC}$$


natural freq: (roots of char. poly)

poles of $I_x(s)$ solution $I_x(s) = \frac{1}{LC} I_s(s)$

$$s^2 + \frac{R}{L}s + \frac{1}{LC}$$

poles of this

Ex: Mesh analysis in s-Domain

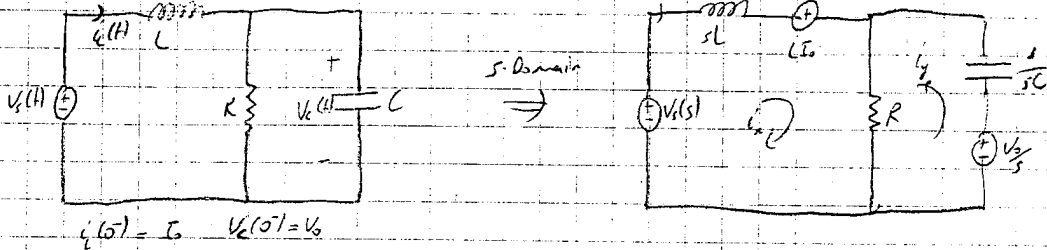

$i(t) = I_0$ $V_C(t) = V_0$

$$\begin{bmatrix} sL+R & R \\ sRC & 1+sRC \end{bmatrix} \begin{bmatrix} I_x(s) \\ I_y(s) \end{bmatrix} = \begin{bmatrix} V_s(s) + LI_0 \\ CV_0 \end{bmatrix}$$

multiply $\begin{bmatrix} 1 & 0 \\ 0 & RC \end{bmatrix}$ with $\begin{bmatrix} I_x(s) \\ I_y(s) \end{bmatrix}$

Cramer's Rule $\Rightarrow I_x(s) = \frac{\begin{vmatrix} V_s(s) + LI_0 & R \\ CV_0 & 1+sRC \end{vmatrix}}{\begin{vmatrix} sL+R & R \\ sRC & 1+sRC \end{vmatrix}}$

$$\Rightarrow I_x(s) = \frac{(V_s(s) + LI_0)(1+sRC) - V_0 CR}{(sL+R)(1+sRC) - sR^2C} = \frac{V_s(s)(1+sRC) + (LI_0 - RC V_0) + sRCL I_0}{s^2RLC + s(L+R^2/C - R^2C) + R}$$

$$\Rightarrow I_x(s) = \frac{\frac{1}{RCL} + \frac{s}{L}}{s^2 - \frac{s}{RC} + \frac{1}{LC}} V_s(s) + \frac{\frac{I_0}{RC} - \frac{V_0}{L} + s I_0}{s^2 + \frac{1}{RC}s + \frac{1}{LC}}$$

Let $R=8\Omega$, $L=6H$, $C=\frac{1}{48}F$

$$I_x(s) = \frac{(1+\frac{s}{6})}{s^2+6s+8} V_s(s) + \frac{6I_0 - \frac{V_0}{6} + sI_0}{s^2+6s+8}$$

zero state
zero input

zero input $\Rightarrow I_x(s) = \frac{1}{2} \frac{(2I_0 - \frac{V_0}{6})}{s+4} + \frac{1}{2} \frac{(4I_0 - \frac{V_0}{6})}{s+2}$ zero state $\Rightarrow I_x(s) = \frac{(1+\frac{s}{6})}{s^2+6s+8} V_s(s)$

Assume: We have zero-input case, problem is find initial cond. to excite mode with $\lambda = -2$

$$i_x(t) = \left[\left(\frac{V_0}{12} - I_0 \right) e^{-4t} + \left(2I_0 - \frac{V_0}{12} \right) e^{-2t} \right] u(t)$$


then $V_0 = 12I_0$ $\begin{bmatrix} V_0 \\ I_0 \end{bmatrix} = \alpha \begin{bmatrix} 12 \\ 1 \end{bmatrix} \rightarrow$ excites $\lambda = -2$ mode only

Assume: $V_1(t) = 16 \cos 2t \text{ u}(t)$ find $i_x^{2s}(t)$

$$I_x^{2s}(s) = \frac{1 + \frac{s}{6}}{s^2 + 6s + 8} \cdot \frac{16s}{s^2 + 4} = \frac{-\frac{4}{3}}{s+2} + \frac{\frac{8}{15}}{s+4} + \frac{\frac{4s + \frac{32}{15}}{s^2 + 4}}$$

$$i_x^{2s}(t) = -\frac{4}{3} e^{-2t} + \frac{8}{15} e^{-4t} + \frac{4}{5} \cos(2t) + \frac{16}{15} \sin(2t)$$

Coupled Inductor

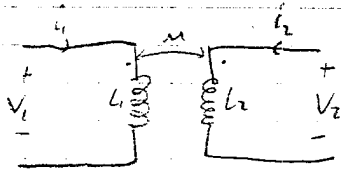


$$\begin{bmatrix} V_1(t) \\ V_2(t) \end{bmatrix} = \begin{bmatrix} L_1 & M \\ M & L_2 \end{bmatrix} \begin{bmatrix} D i_1(t) \\ D i_2(t) \end{bmatrix} \quad \begin{matrix} i_1(0^-) = I_1 \\ i_2(0^-) = I_2 \end{matrix}$$

Laplace

$$\begin{bmatrix} V_1(s) \\ V_2(s) \end{bmatrix} = \begin{bmatrix} L_1 & M \\ M & L_2 \end{bmatrix} \begin{bmatrix} s I_1(s) - I_1 \\ s I_2(s) - I_2 \end{bmatrix} = \begin{bmatrix} L_1 & M \\ M & L_2 \end{bmatrix} \begin{bmatrix} s I_1(s) \\ s I_2(s) \end{bmatrix} - \begin{bmatrix} L_1 & M \\ M & L_2 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix}$$

Transformer

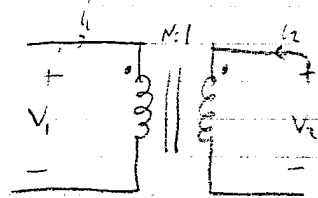


$$\frac{i_1(t)}{i_2(t)} = -\frac{1}{N} \quad \frac{V_1(t)}{V_2(t)} = \frac{N}{1}$$

Laplace

$$\frac{I_1(s)}{I_2(s)} = -\frac{1}{N} ; \quad \frac{V_1(s)}{V_2(s)} = N$$

29/04/2010
Persema

NETWORK FUNCTIONS

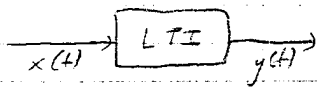

output at zero state


$$H(s) = \frac{\int \{ y^{2s}(t) \}}{\int \{ x(t) \}}$$

Network function

$$\frac{I_c^{2s}(s)}{V_s(s)} = \frac{s}{s+1} \rightarrow (s+1) I_c^{2s}(s) = V_s(s) s$$

$$(0+1) i_c^{2s}(t) = \frac{d}{dt} v_s(t)$$

output (unknown) input

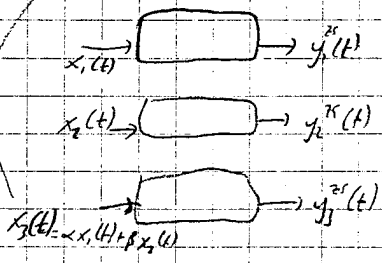

$$\mathcal{L}\{y_1^zs(t)\} = H(s) \mathcal{L}\{x_1(t)\}$$


$$\mathcal{L}\{y_2^zs(t)\} = H(s) \mathcal{L}\{x_2(t)\}$$

$$\mathcal{L}\{y_3^zs(t)\} = H(s) \mathcal{L}\{\alpha x_1(t) + \beta x_2(t)\}$$

$$y_3^zs(t) = \alpha y_1^zs(t) + \beta y_2^zs(t)$$

The ZS solutions obey the superposition principle so ZS solution can be found by superposition method.

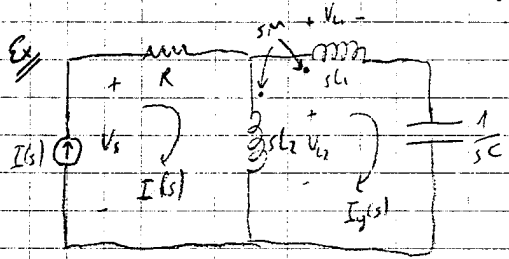If initial conditions are non-zero, they should be treated separately by ZI solution.



Note: no initial conditions since network func. are always expressed in ZS.

$$Z(s) = \frac{V(s)}{I(s)}$$

$$V(s) = I(s)R + sL_1(I(s) - I_y(s)) + \frac{1}{sC}I_y(s)$$


$$\text{KVL: } -V_L + V_C + I_y(s) \frac{1}{sC} = 0$$

$$-(sL_1(I(s) - I_y(s)) + \frac{1}{sC}I_y(s)) + (sL_1 I_y(s) + \frac{1}{sC}I_y(s)) = 0$$

Find I_y in terms of input $I(s)$


Replace $I_y(s)$ in the output relation and express output in terms of $I(s)$ (input)
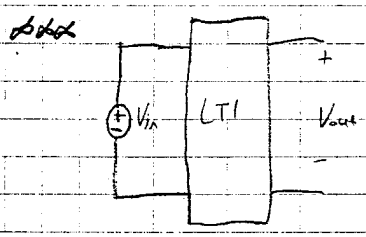
$$Z(s) = \frac{V(s)}{I(s)} = \frac{R + s^2 L_1 C (L_1 + L_2 - 2M) - s^3}{s^2 C (L_1 + L_2 - 2M) + 1}$$




$$H_v(s) = \frac{V_{out}(s)}{V_{in}(s)}$$

voltage transfer function

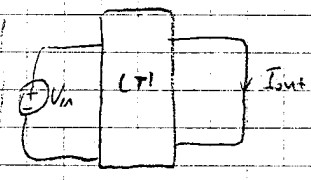


$$\frac{I_{out}(s)}{V_{in}(s)}$$


Transfer admittance

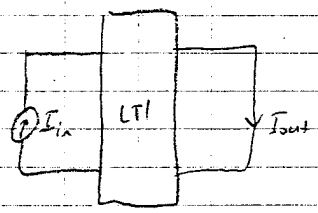

current transfer function

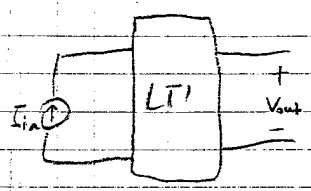

Transfer impedance

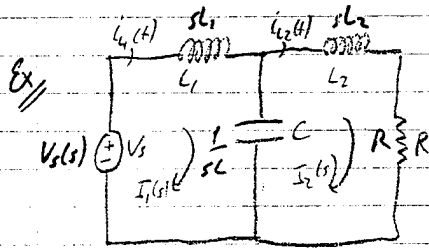

$$\text{KVL: } -V_s(s) + sL_1 I_1(s) + \frac{1}{sC} (I_1(s) - I_2(s)) = 0$$

$$\frac{1}{sC} (I_2(s) - I_1(s)) + sL_2 I_2(s) + R I_2(s) = 0$$


$$\begin{bmatrix} sL_1 + \frac{1}{sC} & -\frac{1}{sC} \\ -\frac{1}{sC} & \frac{1}{sC} + sL_2 + R \end{bmatrix} \begin{bmatrix} I_1(s) \\ I_2(s) \end{bmatrix} = \begin{bmatrix} V_s(s) \\ 0 \end{bmatrix}$$

$$\begin{bmatrix} I_1(s) \\ I_2(s) \end{bmatrix} = \frac{1}{\Delta(s)} \begin{bmatrix} \frac{1}{sC} + sL_2 + R & \frac{1}{sC} \\ \frac{1}{sC} & sL_1 + \frac{1}{sC} \end{bmatrix} \begin{bmatrix} V_s(s) \\ 0 \end{bmatrix}$$

$$\Delta(s) = (sL_1 + \frac{1}{sC})(sL_2 + \frac{1}{sC} + R) - \frac{1}{sC^2}$$

$$\begin{bmatrix} I_1(s) \\ I_2(s) \end{bmatrix} = \begin{bmatrix} \frac{\frac{1}{sC} + sL_2 + R}{\Delta(s)} \cdot V_s(s) \\ \frac{\frac{1}{sC}}{\Delta(s)} \cdot V_s(s) \end{bmatrix} \quad H(s) = \frac{I_2(s)}{V_s(s)} = \frac{\frac{1}{sC} + sL_1 + R}{\Delta(s)}$$

Network Functions and Impulse Response

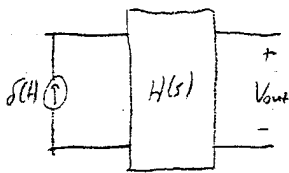

$$V_{out}(s) = H(s) \cdot \mathcal{L}\{\delta(t)\}$$

$$V_{out}(s) = H(s) \cdot 1$$

$$H(s) = \mathcal{L}\{V_{out}(t) \text{ for } \delta(t) \text{ input}\}$$

impulse response (defined for) $\frac{1}{s}$

impulse response in "s domain"

$$V_{out}(s) = H(s) I_{in}(s)$$


$$\mathcal{L}^{-1}\{ \} \downarrow$$

$$V_{out}(t) = \int_{-\infty}^{\infty} h(\tau) i_{in}(t-\tau) d\tau \quad \leftarrow \text{convolution}$$

$$V_{out}(t) = h(t) * i_{in}(t)$$

convolution

About the integral

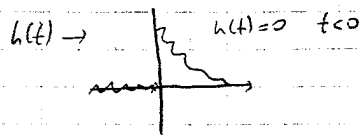


$i_{in}(t)$ given for $t > 0$
 $i_{in}(t) = 0$ for $t < 0$

$$\Rightarrow V_{out}(t) = \int_{-\infty}^{\infty} h(\tau) i_{in}(t-\tau) d\tau = \int_{-\infty}^0 + \int_0^t + \int_t^{\infty}$$

since $h(\tau) = 0$ in the integration range
 since $i_{in}(t-\tau) = 0$ for integration range

$$= \int_0^t h(\tau) i_{in}(t-\tau) d\tau$$

Step Response

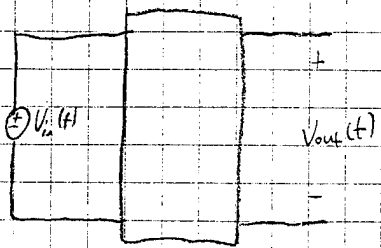

$$V_{out}(s) = H(s) V_{in}(s) \leftarrow \mathcal{L}\{u(t)\} = \frac{1}{s}$$


$$V_{out}^{step}(s) = H(s) \frac{1}{s}$$

$$V_{out}^{step}(t) = \mathcal{L}^{-1}\left\{ \frac{H(s)}{s} \right\} = \int_{-\infty}^{+\infty} h(\tau) d\tau$$

OR By Convolution:

$$V_{out}^{step}(t) = \int_{-\infty}^{\infty} h(\tau) V_{in}(t-\tau) d\tau = \int_{-\infty}^t h(\tau) \underbrace{V_{in}(t-\tau)}_1 d\tau = \int_{-\infty}^t h(\tau) d\tau$$

Ex 11

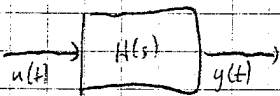

$$H(s) = \frac{1}{(s+2)(s+3)} = \frac{V_{out}(s)}{V_{in}(s)}$$

$$V_{out}^{step}(s) = H(s) \frac{1}{s}$$

$$= \frac{1}{(s+2)(s+3)} \frac{1}{s} = \frac{\frac{1}{-2}}{s+2} + \frac{\frac{1}{3}}{s+3} + \frac{\frac{1}{6}}{s}$$


response related frequencies natural frequencies response related to step

$$\Rightarrow V_{out}(t) = -\frac{1}{2} e^{-2t} + \frac{1}{3} e^{-3t} + \frac{1}{6}$$

03/05/2010

Parvathi

Sinusoidal Steady State Response

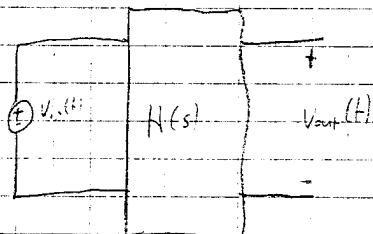

$$H(s) = \frac{V_{out}(s)}{V_{in}(s)}$$

$$\mathcal{L}\{V_{in}(t)\} = \mathcal{L}\{A \cos(\omega t + \phi)\} = A \cos \phi \mathcal{L}\{\cos \omega t\} - A \sin \phi \mathcal{L}\{\sin \omega t\}$$

$$= \frac{A \cos \phi s}{s^2 + \omega^2} - \frac{A \sin \phi \omega}{s^2 + \omega^2} = A \frac{(\cos \phi)s - (\sin \phi)\omega}{s^2 + \omega^2}$$

$$V_{in}(t) = A \cos(\omega t + \phi)$$

$$V_{out}(t) = ?$$

$$\mathcal{L}\{V_{in}(t)\} = A \frac{(\cos \phi)s - (\sin \phi)\omega}{s^2 + \omega^2}$$

$$V_{out}(s) = H(s) V_{in}(s) = H(s) \left[A \frac{(\cos \phi)s - (\sin \phi)\omega}{s^2 + \omega^2} \right] = \frac{K}{s - j\omega} + \frac{K^*}{s + j\omega} + \frac{A_1}{s - \alpha_1} + \frac{A_2}{s - \alpha_2} + \dots + \frac{A_n}{s - \alpha_n}$$

Let's focus on the response due to sinusoidal input;

$$K = ?$$

$$K = H(s) A \left(\frac{\cos \phi s - \sin \phi \omega}{(s+j\omega)(s-j\omega)} \right) \Big|_{s=j\omega}$$

$$K = H(j\omega) A \frac{\cos \phi j\omega - \sin \phi \omega}{2j\omega} = H(j\omega) \frac{A}{2} [\cos \phi + j \sin \phi] = \frac{H(j\omega) A}{2} e^{j\phi}$$

$$\mathcal{L}^{-1} \left\{ \frac{K}{s-j\omega} + \frac{K^*}{s+j\omega} \right\} = K e^{j\omega t} + K^* e^{-j\omega t} = 2 \operatorname{Re} \{ K e^{j\omega t} \}$$


$$= 2 \operatorname{Re} \{ |K| e^{j(\omega t + \angle K)} \} = 2|K| \cos(\omega t + \angle K)$$

$$K = \frac{A}{2} |H(j\omega)| e^{j(\angle H(j\omega) + \phi)}$$


$$V_{out}(t) = A |H(j\omega)| \cos(\omega t + \phi + \angle H(j\omega))$$

The output at steady state
(free of natural response terms)

Ex 1

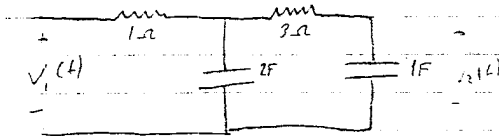

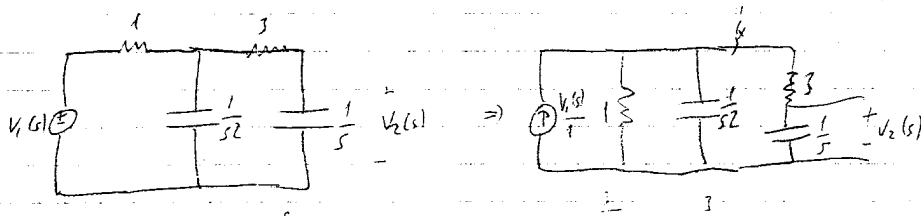a) $V_2^{ss}(t) = ?$ for $V_1(t) = 4 \cos\left(\frac{1}{2}t + 30^\circ\right)$



$$i_2(s) = \frac{\frac{1}{s^2} \cdot \frac{1}{1+s} \cdot V_1(s)}{1+s+\frac{1}{s} + \frac{1}{s^2} + \frac{3}{s}} \cdot V_1(s)$$

$$V_2(s) = i_2(s) \cdot \frac{1}{s} = \frac{s}{(1+s)(1+3s)+s} \cdot \frac{1}{s} V_1(s) = \frac{1}{6} \frac{1}{s^2+s+1} V_1(s)$$


$$H(s) = \frac{1}{6}$$

a) $V_2^{ss}(t) = 4 \left(|H(j\frac{1}{2})| \cos\left(\frac{1}{2}t + 30^\circ + \angle H(j\frac{1}{2})\right) \right)$

$$H(j\frac{1}{2}) = \frac{1}{6} = \frac{1}{-0.5 + j3} = \frac{1}{\sqrt{3+1}} e^{-j(\pi - \tan^{-1} 3/0.5)}$$

If $4 \cos\left(\frac{1}{2}t + 30^\circ\right) \rightarrow [H(s)] \rightarrow \frac{4}{3} \cos\left(\frac{1}{2}t + 30^\circ + (\tan^{-1} 3/0.5 - \pi)\right)$

FREQUENCY RESPONSE




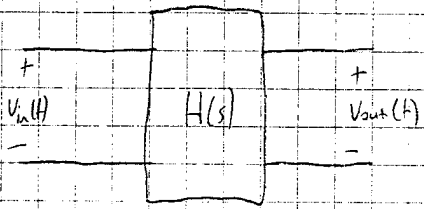


$$V_{in}(t) = A_{in} \cos(\omega t + \phi_{in})$$


$$V_{out}(t) = A_{in} |H(j\omega)| \cos(\omega t + \phi_{in} + \angle H(j\omega))$$

Gain function : $|H(j\omega)|$ (Magnitude Response)

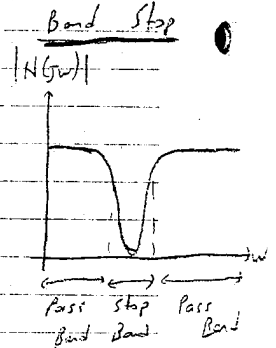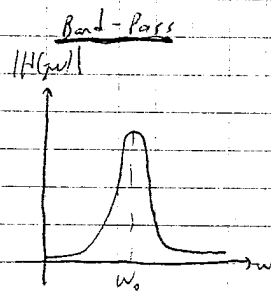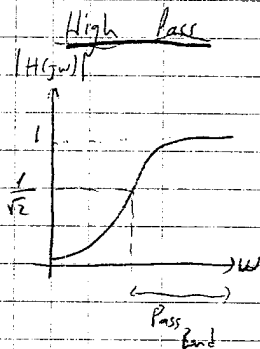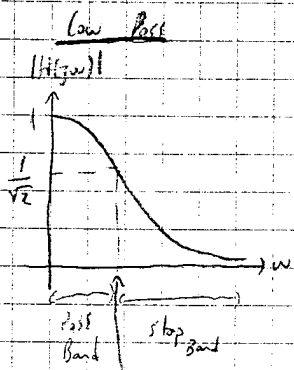Phase function : $\angle H(j\omega)$ (Phase Response)




Decibel

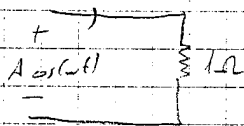


$$P_{avg} = \frac{A^2}{2} R \quad R=1\Omega = \frac{A^2}{2}$$

↑
square of RMS of $A \cos(\omega t)$

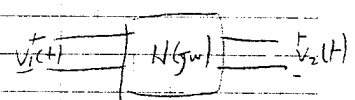

\Rightarrow The avg. power at the input is $\frac{A^2}{2}$ = AVG. power dissipated over 1Ω resistor.

Decibel $\Rightarrow 10 \log_{10} \left(\frac{\text{Power at the output}}{\text{Power at the input}} \right) = 10 \log_{10} \left(\frac{\frac{|AH(j\omega)|^2}{2} R}{\frac{A^2}{2} R} \right) = 10 \log_{10} (|H(j\omega)|^2) \text{ dB}$

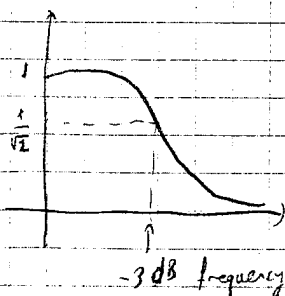

$ H(j\omega) ^2$	dB ($10 \log_{10} (H(j\omega) ^2)$)
1	0
2	3
3	4.77
4	6
5	7
6	7.78
7	8.45
8	9
9	9.54
10	10

$$20 \log |H(j\omega)|^2 = 20 \log |H(j\omega)|$$

~~Ex~~


Frequency Response of 1st Order Circuits

a) Low-pass

$$H(s) = \frac{K}{s + \alpha} \quad \xrightarrow{X(s)} \boxed{H(s)} \rightarrow Y(s)$$

$$\frac{Y(s)}{X(s)} = \frac{K}{s + \alpha} \Rightarrow Y(s)s + \alpha Y(s) = KX(s)$$
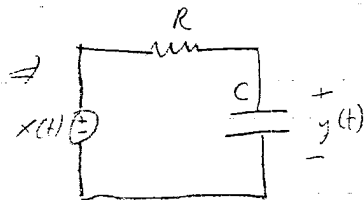
$$\boxed{\frac{d}{dt}y(t) + \alpha y(t) = Kx(t)}$$



$$-x(t) + (C \dot{y}(t))R + y(t) = 0$$


$$\dot{y}(t) + \frac{1}{RC}y(t) = \frac{1}{RC}x(t)$$

$$x(t) = A \cos(\omega t + \phi_{in}); \quad y(t) = A |H(j\omega)| \cos(\omega t + \phi_{in} + \angle H(j\omega))$$

$|H(j\omega)|$: Magnitude response





$$|H(j\omega)| = \left| \frac{K}{\alpha + j\omega} \right| = \frac{|K|}{\sqrt{\omega^2 + \alpha^2}}$$
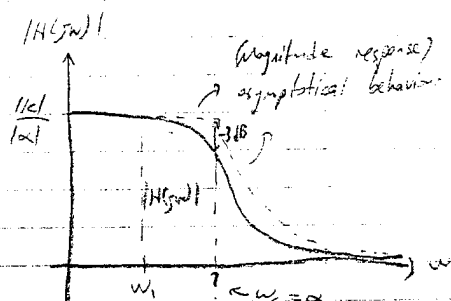
$$\angle H(j\omega) = \angle \left(\frac{K}{\alpha + j\omega} \right) = \angle K - \tan^{-1} \frac{\omega}{\alpha}$$




06/05/2010
Persema

$$|H(j\omega)| = \frac{|K|}{\omega \sqrt{1 + \left(\frac{\alpha}{\omega}\right)^2}} \Rightarrow |H(j\omega)| \approx \begin{cases} \frac{|K|}{\alpha} & \omega \ll \alpha \\ \frac{|K|}{\omega} & \omega \gg \alpha \end{cases}$$

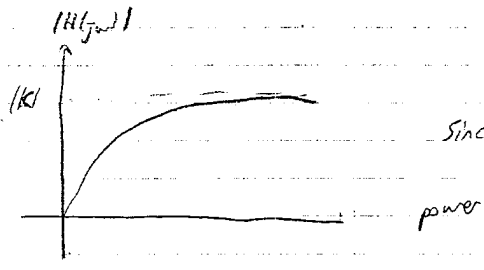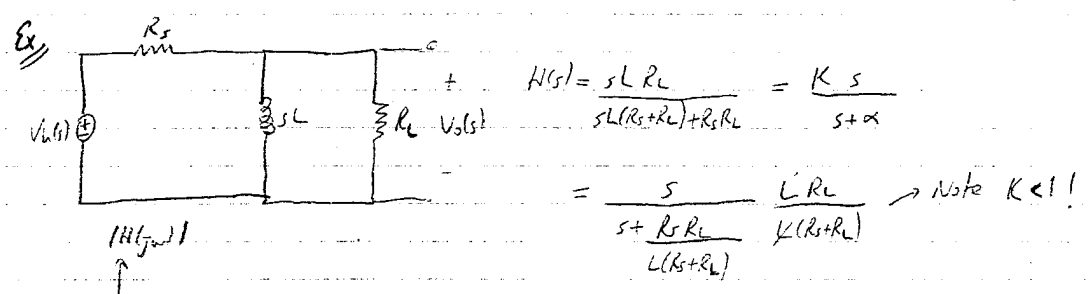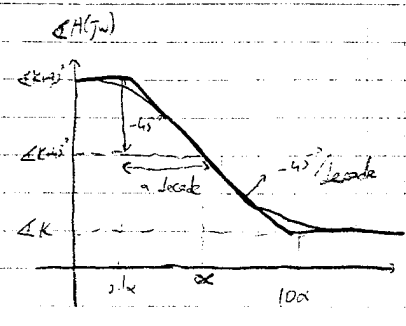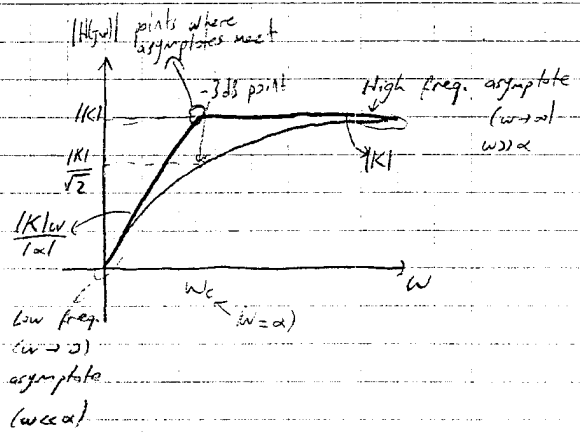


Since $|K| < 1$ I have less power at the output than input

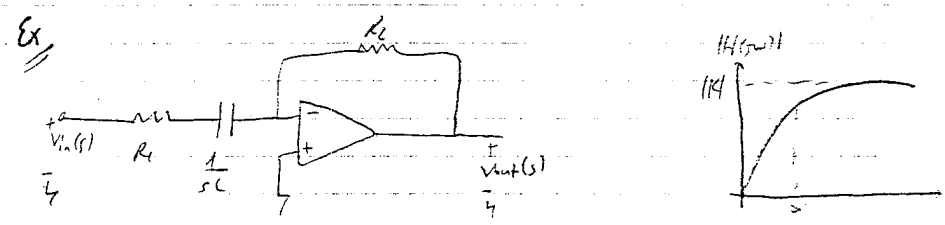


depending on R_2 , output power can be greater than input power at pass band freq.

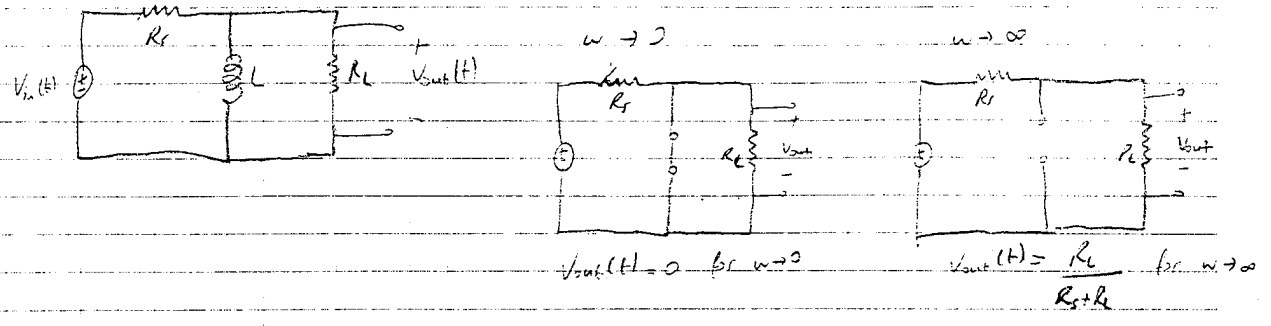Understanding the frequency behavior of simple circuit by inspection;



Bandpass - Bandstop Filters using 1st Order Circuits


13/05/2010
Persema

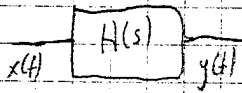



$$H_1(s) = K_1 \frac{s}{s + \alpha_1} \leftarrow \text{High-pass system}$$

$$H_2(s) = K_2 \frac{1}{s + \alpha_2} \leftarrow \text{Low pass system}$$




Band-Pass System

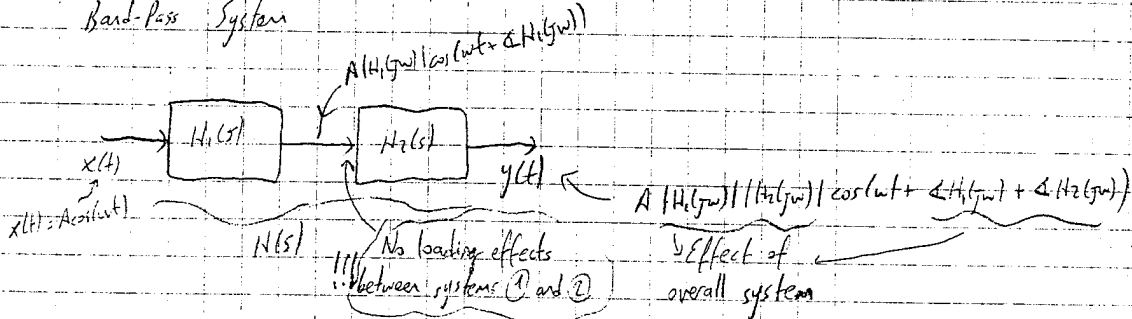

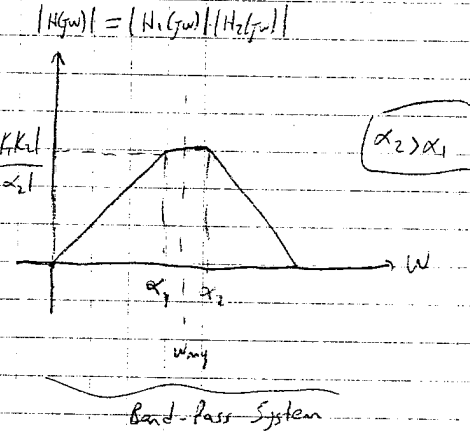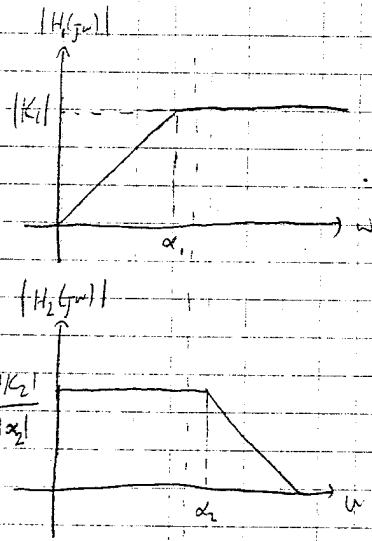
$$H(s) = H_1(s) H_2(s) \quad (\text{We have not shown this result in detail; it follows from "convolution" result})$$



Parallel Combination

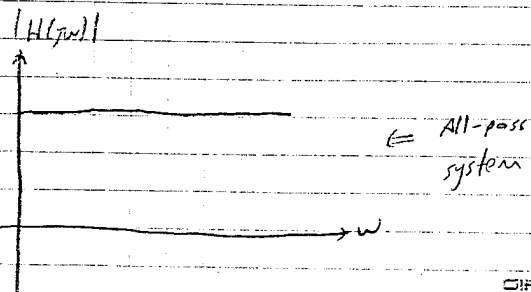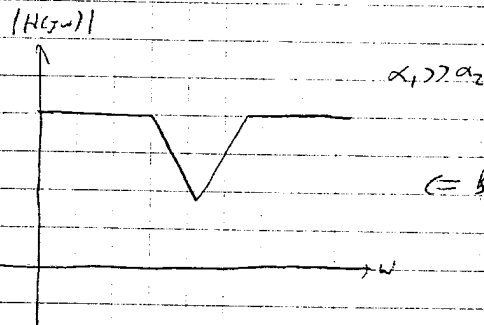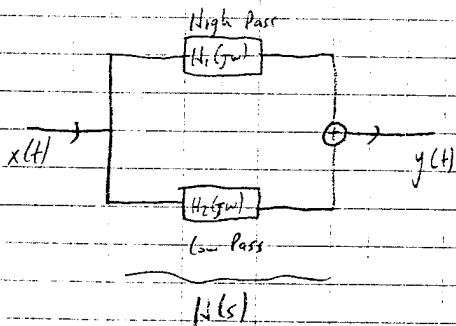

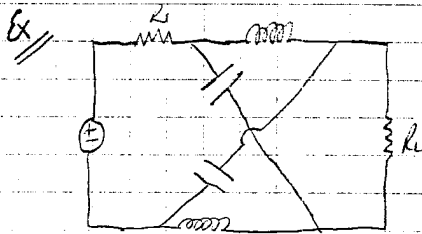

All pass system
 $\frac{L}{C} = R_s^2$

$$H(j\omega) = \frac{R_s}{R_L + R_s} \frac{1 - j\omega C R_s}{1 + j\omega C R_s}$$

$$|H(j\omega)| = \frac{R_s}{R_L + R_s} ; \angle H(j\omega) = 2 \tan^{-1}(-\omega C R_s)$$

SECOND ORDER CIRCUITS

(A) Band-Pass System

$$H(s) = K \frac{s}{s^2 + 2\delta\omega_0 s + \omega_0^2}$$

$s^2 + 2\delta\omega_0 s + \omega_0^2$: char. poly

$$H(s) = K \frac{s}{s - z_1} \frac{1}{s - z_2}$$

\rightarrow distinct roots $\Rightarrow z_1 \neq z_2$
 \rightarrow identical roots $\Rightarrow z_1 = z_2 \rightarrow |H(s)| = K \frac{s}{(s - z_1)^2}$
 \rightarrow complex conjugate roots $\Rightarrow z_1 = z_2^*$

$$H(s) \Big|_{s=j\omega} = K \frac{j\omega}{-\omega^2 + 2\delta\omega_0 j\omega + \omega_0^2}$$

$$= K \frac{1}{\frac{-\omega^2}{j\omega} + \frac{2\delta\omega_0 j\omega}{j\omega} + \frac{\omega_0^2}{j\omega}}$$

$$= K \frac{1}{2\delta\omega_0 + j\left[\omega - \frac{\omega_0^2}{\omega}\right]}$$

2nd order system with complex poles. Requires some special interest

$$= K \frac{1}{\omega_0 \left(2\delta + j \left[\frac{\omega}{\omega_0} - \frac{\omega_0}{\omega} \right] \right)}$$

$$\Rightarrow |H(j\omega)| = \frac{|K|}{\omega_0} \frac{1}{\sqrt{(2\delta)^2 + \left(\frac{\omega}{\omega_0} - \frac{\omega_0}{\omega} \right)^2}}$$

$$\angle H(j\omega) = \angle K - \tan^{-1} \left[\frac{\left(\frac{\omega}{\omega_0} - \frac{\omega_0}{\omega} \right) / 2\delta}{1} \right]$$

$$s^2 + 2\delta\omega_0 s + \omega_0^2 = 0$$

$$s_{1,2} = \left\{ -\delta\omega_0 \pm \omega_0 \sqrt{\delta^2 - 1} \right\}$$


① $\delta = 1 \rightarrow s_{1,2} = \left\{ -\omega_0 \right\}$ double roots (critically damped) $z_{1,2} = -\omega_0$

② $\delta > 1 \rightarrow$ distinct roots (over damped)

③ $\delta = 0 \rightarrow s_{1,2} = \left\{ -j\omega_0 \right\}$

④ $|\delta| < 1 \rightarrow$ complex roots.

Pole-zero plot for $H(s)$

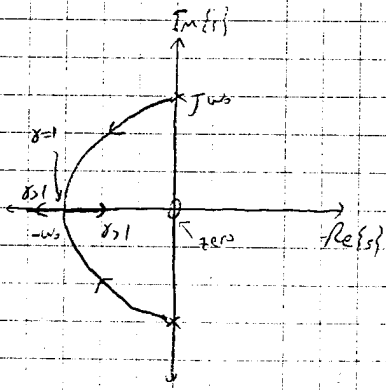


$$H(s) = K \frac{s}{s^2 + 2\delta\omega_0 s + \omega_0^2}$$

δ : damping coefficient

ω_0 : resonant frequency (rad/sec)

$$H(s) = K \frac{s}{(s-p_1)(s-p_2)}$$

$$|H(j\omega)| = |H(s)| \Big|_{s=j\omega}$$

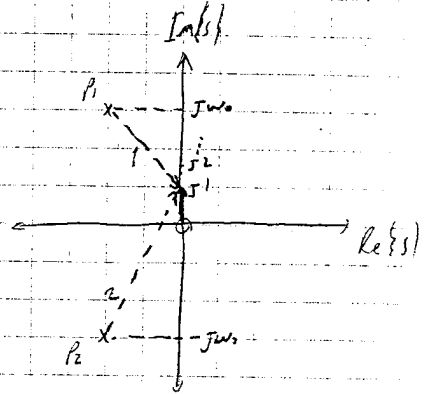

$$|H(j\omega)| = |K| \cdot \frac{|z_1|}{|p_1-p_1| \cdot |p_2-p_1|} = |K| \cdot \frac{\text{Length of blue solid vector}}{\text{length of blue shaded vector 1} \cdot \text{length of blue shaded vector 2}}$$

Returning to Algebraic Discussion


$$H(j\omega) = \frac{K}{2\delta + j\left(\frac{\omega}{\omega_0} - \frac{\omega_0}{\omega}\right)}$$

$$\arg \max_{\omega} (|H(j\omega)|) = \omega_0$$


$$|H(j\omega_0)| = \max_{\omega} |H(j\omega)| = \frac{|K|}{2\delta\omega_0}$$

$$\textcircled{1} \omega \ll \omega_0 \rightarrow H(j\omega) = \frac{K/\omega_0}{2\delta + j\left(\frac{\omega}{\omega_0} - \frac{\omega_0}{\omega}\right)} \approx \frac{K/\omega_0}{2\delta + j\left(-\frac{\omega_0}{\omega}\right)} \approx \frac{K/\omega_0}{j\frac{\omega_0}{\omega}} \approx j\frac{K\omega}{\omega_0^2}$$
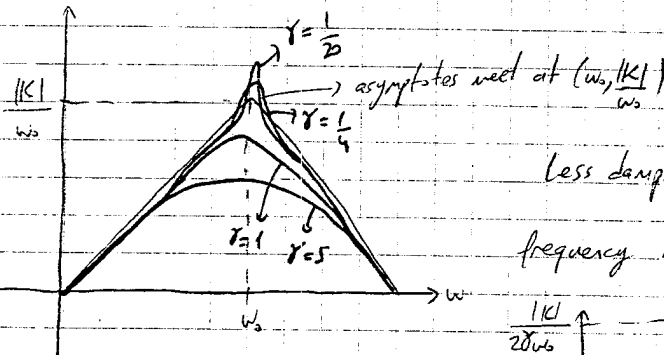
$$\textcircled{2} \omega \gg \omega_0 \rightarrow H(j\omega) \approx \frac{K/\omega_0}{2\delta + j\frac{\omega}{\omega_0}} \approx -j\frac{K}{\omega}$$



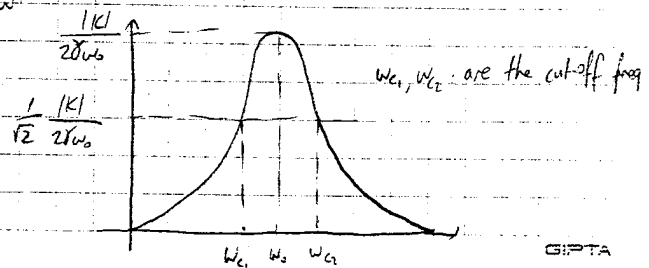Less damping (δ smaller) results in peaky frequency response



$$|H(j\omega)| = \frac{K/\omega_0}{\sqrt{2\delta + J\left(\frac{\omega_0}{\omega} - \frac{\omega}{\omega_0}\right)}} = \frac{|K|/\omega_0}{\sqrt{2\delta}}$$

$\omega = \omega_{c1}, \omega_{c2}$

The cut off frequencies satisfy the following quadratic.

$$\left(\frac{\omega}{\omega_0} - \frac{\omega_0}{\omega}\right) = 2\delta$$

$\omega^2 - 2\delta\omega_0\omega - \omega_0^2 = 0$ ← solution gives me the cut off frequencies

roots = $\left\{ \omega_0 (\delta \pm \sqrt{1 + \delta^2}) \right\}$ the meaningful root is the positive one

$$\omega_{c2} = \omega_0 (\delta + \sqrt{1 + \delta^2})$$

For ω_{c1} , we repeat same calculation for $\left(\frac{\omega}{\omega_0} - \frac{\omega_0}{\omega}\right) = -2\delta$ and get

$$\omega_{c1} = \omega_0 (-\delta + \sqrt{1 + \delta^2})$$


Then Bandwidth of the system = $\omega_{c2} - \omega_{c1} = 2\delta\omega_0$

$$\text{Then } Q: \text{Quality factor} = \frac{\omega_0}{BW} = \frac{1}{2\delta}$$

17/05/2010
Paartesi

- ① δ : small \Rightarrow peaky response $\rightarrow Q$: high \rightarrow High Q filters \rightarrow Narrow band filters
- ② δ : large \Rightarrow broad response $\rightarrow Q$: low \rightarrow low Q filter \rightarrow Wide band filter

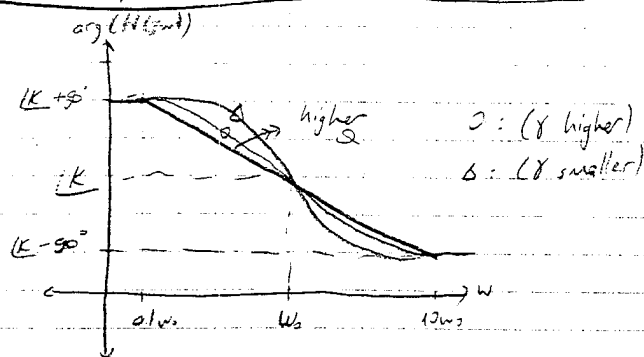Phase Response (2nd order Band Pass Systems)



Second Order Low-Pass System

$$H(s) = \frac{K}{s^2 + 2\delta\omega_s s + \omega_s^2}, \quad H(j\omega) = \frac{K}{\omega_s^2 - \omega^2 + j2\delta\omega_s\omega}$$


$$|H(j\omega)| = \frac{|K|}{\sqrt{(\omega_s - \omega)^2 + 4\delta^2\omega_s^2\omega^2}}$$

$$\angle H(j\omega) = \angle K - \tan^{-1}\left(\frac{2\delta\omega_s\omega}{\omega_s^2 - \omega^2}\right)$$

$$① \omega \ll \omega_s \rightarrow |H(j\omega)| = \frac{|K|}{\omega_s^2}$$

$$② \omega \gg \omega_s \rightarrow |H(j\omega)| = \frac{|K|}{\omega^2}$$

$$③ |H(j\omega)| = \frac{|K|}{2\delta\omega_s^2}$$

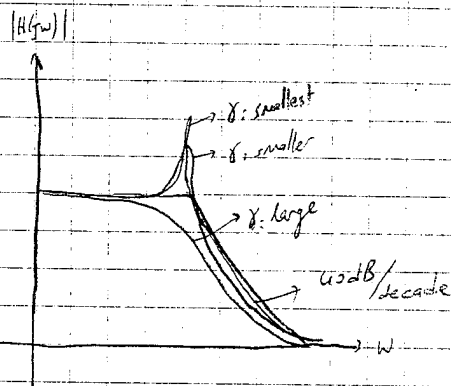


Second Order High-Pass System

$$H(s) = \frac{Ks^2}{s^2 + 2\delta\omega_s s + \omega_s^2}$$

$$H(j\omega) = \frac{K(-\omega^2)}{\omega_s^2 - \omega^2 + j2\delta\omega_s\omega} = \frac{-K\omega^2}{\omega_s^2 \left(1 - \left(\frac{\omega}{\omega_s}\right)^2 + j\frac{2\delta\omega}{\omega_s}\right)}$$

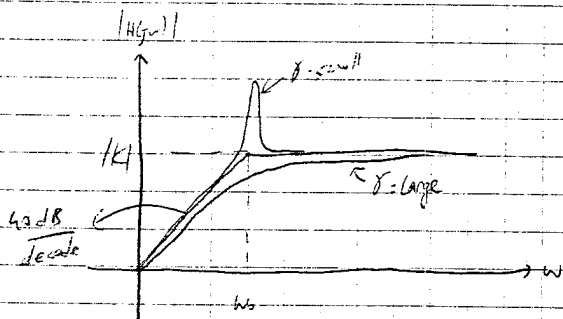
$$\arg(H(j\omega)) = 180^\circ + \angle \left(\frac{2\delta\omega/\omega_s}{1 - (\omega/\omega_s)^2} \right)$$




$$① \omega \ll \omega_s \rightarrow H(j\omega) = \frac{-K\omega^2}{\omega_s^2}, \quad |H(j\omega)| = \frac{|K|\omega^2}{\omega_s^2}$$

$$② \omega \gg \omega_s \rightarrow H(j\omega) = \frac{-K\omega^2}{-\omega^2} = K, \quad |H(j\omega)| = |K|$$

$$③ \omega = \omega_s \rightarrow |H(j\omega)| = \frac{|K|}{2\delta}$$

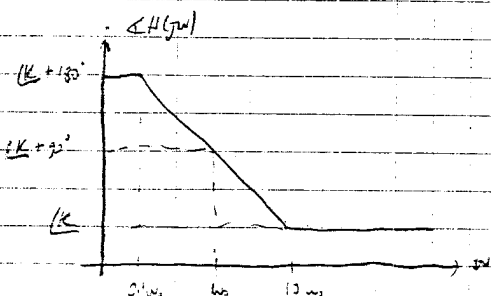

20/09/2010
Persema

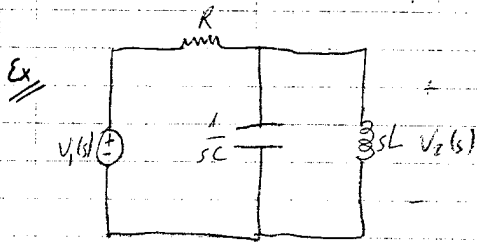

Find the type of filter and $H(s)$

L.P
 $\omega = 0$
 $V_2(s) = 0$
 \Downarrow
 not L.P

H.P
 $\omega = \infty$
 $V_2(s) = 0$
 \Downarrow
 not H.P

$$H(s) = \frac{V_2(s)}{V_1(s)} = \frac{\left(\frac{1}{sC} \parallel sL\right)}{R + \left(\frac{1}{sC} \parallel sL\right)} = \frac{s/RC}{s^2 + \frac{s}{RC} + \frac{1}{LC}}$$

← Compare this form with previously studied L.P, H.P, Band Pass 2nd Order Systems

$$\Rightarrow H(s) = K \frac{s}{s^2 + 2\zeta\omega_0 s + \omega_0^2}$$

$\frac{1}{RC}$ $\frac{1}{RC}$ $\frac{1}{LC}$


Band pass

Let $L = 0.25 \text{ H}$ $R = 1 \text{ k}\Omega$ $C = 1 \mu\text{F}$


$$\omega_0 = \frac{1}{\sqrt{LC}} = 2 \text{ krad/sec} \Rightarrow f_0 = \frac{\omega_0}{2\pi} = 318.3 \text{ Hz}$$

$$BW = 2\zeta\omega_0 = \frac{1}{RC} = 1 \text{ krad/sec} \Rightarrow (BW = 159.15 \text{ Hz})$$

$$Q = \frac{\omega_0}{BW} = 2$$

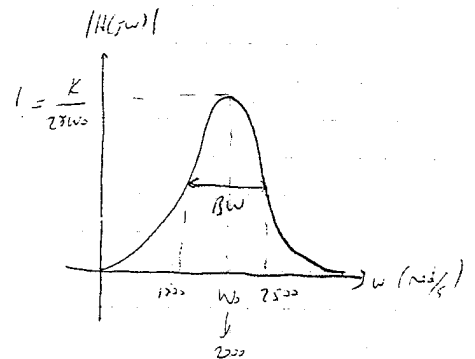

Ex //

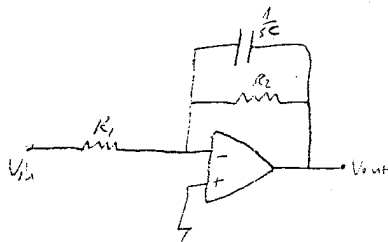


$$H(s) = \frac{-R_f}{R_i} \frac{1}{1 + sR_f C}$$

Scaling:

Used to modify a given filter to

- i) a realizable filter (with components on the shelf)
- ii) Changing (scaling) gain-phase response

1- Magnitude Scaling

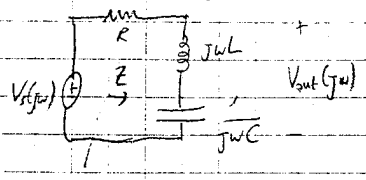

$$Z(j\omega) = R + j\omega L + \frac{1}{j\omega C}$$



$$I_s(j\omega) = \frac{V_s(j\omega)}{R + j\omega L + \frac{1}{j\omega C}} \Rightarrow \frac{V_{out}(j\omega)}{V_s(j\omega)} = \frac{j\omega L + \frac{1}{j\omega C}}{R + j\omega L + \frac{1}{j\omega C}} \quad (*)$$

Replace $R \rightarrow k_m R$
 $L \rightarrow k_m L$
 $C \rightarrow \frac{C}{k_m}$

After replacement (*)

$$\frac{V_{out}(j\omega)}{V_{in}(j\omega)} = \frac{(j\omega L + \frac{1}{j\omega C}) k_m}{(R + j\omega L + \frac{1}{j\omega C}) k_m} \quad \text{So no change in the transfer function after replacement.}$$

2- Frequency Scaling

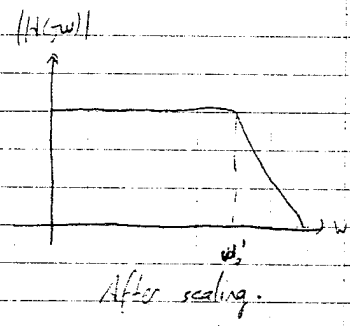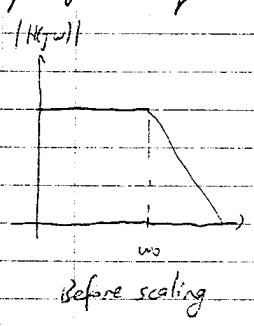


$$H(j\omega) = \frac{j\omega L + \frac{1}{j\omega C}}{R + j\omega L + \frac{1}{j\omega C}}$$

Replace $R \rightarrow R$
 $L \rightarrow L$
 $C \rightarrow \frac{C}{k_f}$

After scaling

$$H(j\omega) = \frac{j\omega L + \frac{1}{j\omega C}}{R + j\omega L + \frac{1}{j\omega C}}$$
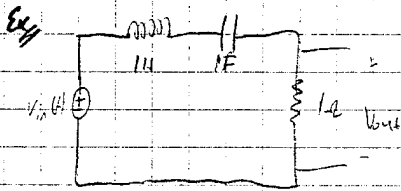
$$H(j\omega) = H(j\omega)_{before} \quad \text{select } k_f = \frac{\omega'_0}{\omega_0}$$



$$\omega_0 = \frac{1}{\sqrt{LC}} = 1 \text{ rad/sec}$$

$$BW = 2\delta\omega_0 = \frac{R}{L} = 1 \text{ rad/sec} \quad Q = \frac{\omega_0}{\delta\omega} = 1$$



Scale the circuit s.t. the resonant freq. is at 500 Hz, and use a 2kF cap.

$$\omega_0' = 2\pi f = 1000\pi \quad k_f = \frac{\omega_0'}{\omega_0} = 1000\pi$$

$$R \xrightarrow{k_f} R' \xrightarrow{k_m} R' k_m \rightarrow 160 \Omega$$

$$L \xrightarrow{k_f} \frac{L}{k_f} \xrightarrow{k_m} L' k_m \rightarrow 50 \text{ mH}$$
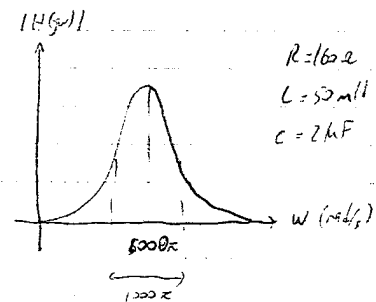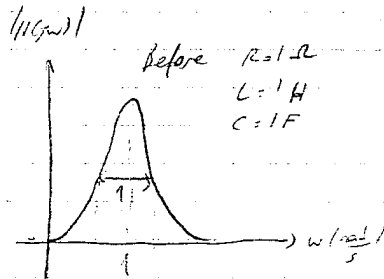
$$C \xrightarrow{k_f} \frac{C}{k_f} \xrightarrow{k_m} \frac{C}{k_f k_m} = 2 \mu\text{F} \Rightarrow \frac{1}{1000\pi k_m} = \frac{2}{10^6} \Rightarrow k_m = \frac{500}{\pi} \approx 160$$



Bode Plots

$$H(s) = 12500 \frac{(s+10)}{(s+50)(s+500)}$$

1) Bring $H(s)$ into standard form


$$H(s) = \frac{K (1 + s/\alpha_1)}{(1 + s/\alpha_2)(1 + s/\alpha_3)} \Rightarrow H(s) = \frac{12500 \cdot 10 (1 + \frac{s}{10})}{50 (1 + \frac{s}{50}) 500 (1 + \frac{s}{500})} = \frac{5 (1 + \frac{s}{10})}{(1 + \frac{s}{50})(1 + \frac{s}{500})}$$

2) Find critical freq.

$$\omega_{critical} = \{50, 500\}$$

$$3) |H(j\omega)| = \frac{5 |1 + j\omega/10|}{|1 + j\omega/50| |1 + j\omega/500|}$$



$$|H(j\omega)|_{dB} = 20 \log_{10} |H(j\omega)| = 20 \log_{10} (5) + 20 \log_{10} |1 + j\omega/10| - 20 \log_{10} |1 + j\omega/50| - 20 \log_{10} |1 + j\omega/500|$$

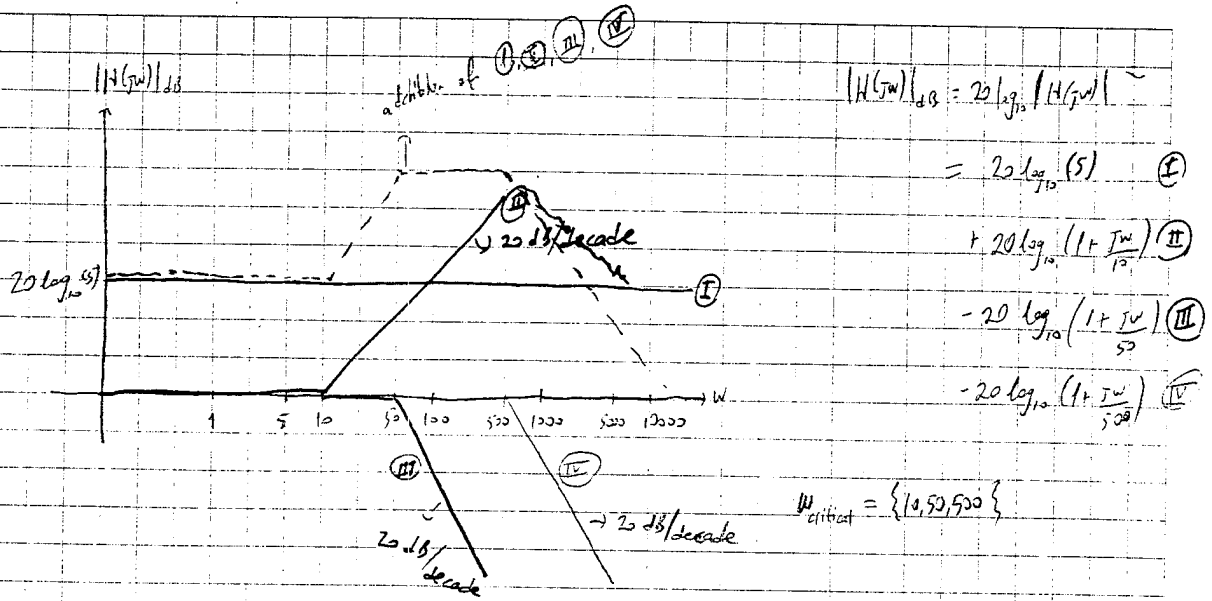

$$\begin{aligned}
 |H(jw)|_{dB} &= 20 \log_{10} |H(jw)| \\
 &= 20 \log_{10} (5) \quad \text{I} \\
 &+ 20 \log_{10} (1 + \frac{jw}{10}) \quad \text{II} \\
 &- 20 \log_{10} (1 + \frac{jw}{50}) \quad \text{III} \\
 &- 20 \log_{10} (1 + \frac{jw}{500}) \quad \text{IV}
 \end{aligned}$$

Phase Plot

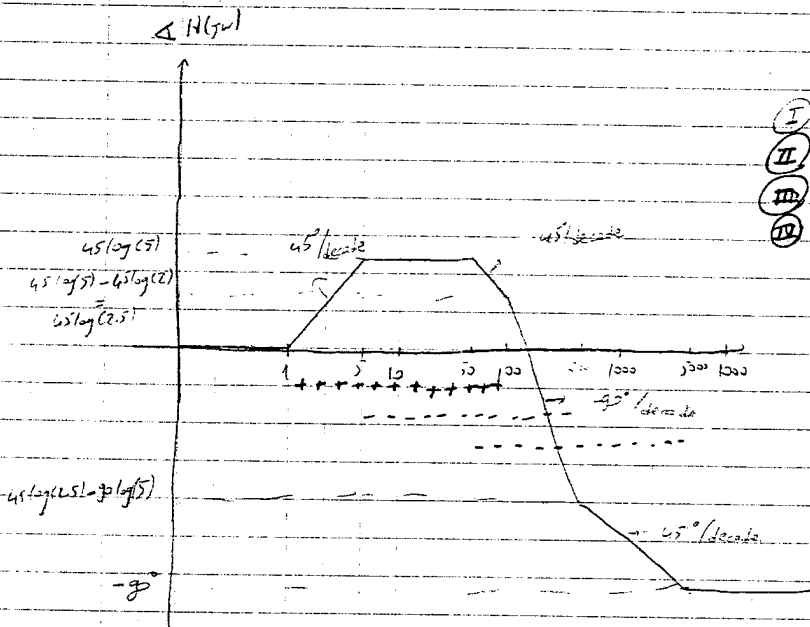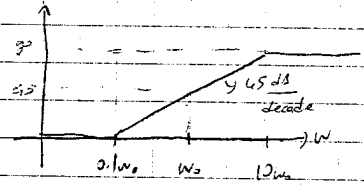I $\cdot 45$ II $\angle (1 + \frac{jw}{10})$ III $\angle (1 + \frac{jw}{50})$ IV $\angle (1 + \frac{jw}{500})$
 $\angle H(jw) = \text{I} + \text{II} + \text{III} + \text{IV}$



- I $\Rightarrow 0$
- II $\Rightarrow 45 \text{ dB/decade}$ between $[1, 100]$
- III $\Rightarrow -45 \text{ dB/decade}$ between $[5, 500]$
- IV $\Rightarrow -45 \text{ dB/decade}$ between $[50, 5000]$

27/05/2010
Perseus

Bode Plots with 2nd Order Systems

Let's examine the following form

$$A(s) = s^2 + 2\zeta\omega_n s + \omega_n^2$$

Note: $A(s)$ can be factorized as $(s + \alpha_1)(s + \alpha_2)$ (when $\zeta > 1$) (α_1, α_2 real) and then reduces $A(s)$ to the multiplication of 1st order systems.

Then assume ($\zeta < 1$); (roots are imaginary)


To start the analysis write $A(s)$ in the standard form.

$$A(s) = \omega_0^2 \left(1 + \frac{2\zeta s}{\omega_0} + \frac{s^2}{\omega_0^2} \right)$$

$$A(s) = 1 + \frac{2\zeta}{\omega_0} s + \frac{s^2}{\omega_0^2}$$

$$\sqrt{\left(1 - \frac{\omega^2}{\omega_0^2}\right)^2 + \left(\frac{2\zeta\omega}{\omega_0}\right)^2} \rightarrow 20 \log_{10} \sqrt{\left(1 - \frac{\omega^2}{\omega_0^2}\right)^2 + \left(\frac{2\zeta\omega}{\omega_0}\right)^2}$$

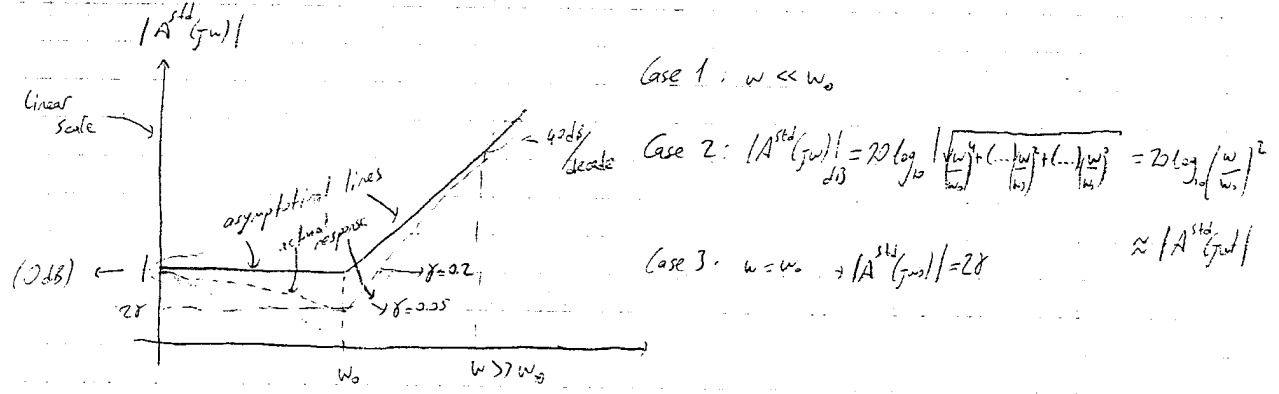
$$\tan^{-1} \left(\frac{2\zeta\omega/\omega_0}{1 - (\omega/\omega_0)^2} \right)$$



$\gamma < 1$ for imaginary roots or underdamped system

$$\omega = \frac{1}{2\zeta} ; \text{High } \omega, \text{ small } \gamma$$

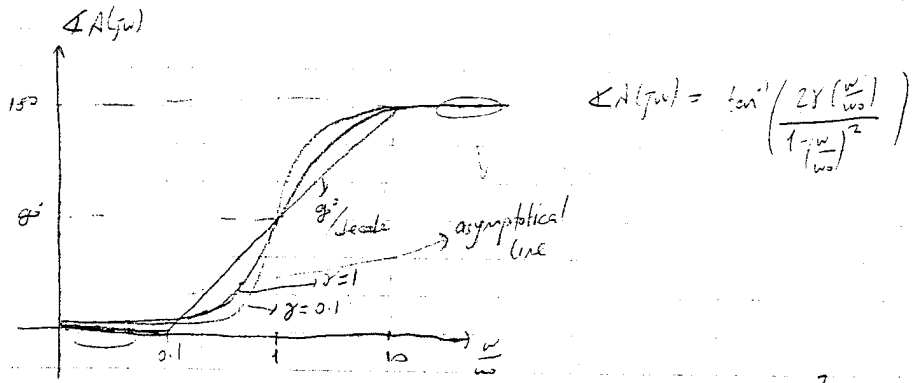
Note: $\gamma = \frac{1}{2}$; $\frac{1}{2\zeta} = 1$ actual curve passes through the intersection of asymptotes




$$Ex: H(s) = \frac{5000(s+100)}{s^2 + 625s + 500^2} = \frac{5000 \cdot 100 \left(1 + \frac{s}{100}\right)}{500^2 \left(1 + \frac{625}{500^2}s + \left(\frac{s}{500}\right)^2\right)} = \frac{2 \left(1 + \frac{s}{100}\right)}{\left(1 + \frac{s}{625} + \left(\frac{s}{500}\right)^2\right)}$$

$$\frac{s^2 + 625s + 500^2}{2 \times 500} \Rightarrow \omega_0 = 500 \quad \gamma = 0.4$$

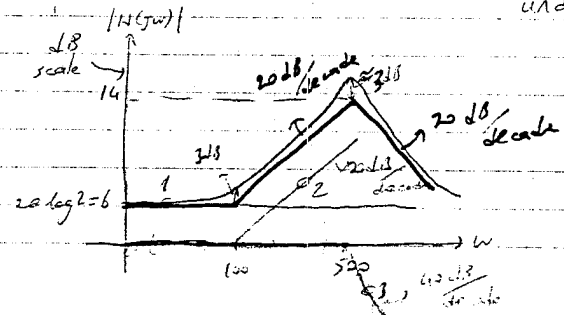underdamped (2nd order system model should be used!)




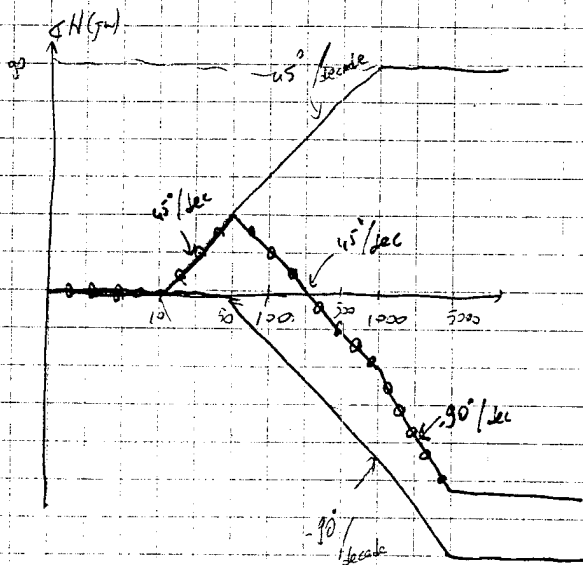

STATE EQUATIONS WITH NONLINEAR ELEMENTS

If an element is non-linear and we would like to express the circuit in the state equation form, we can do the following:

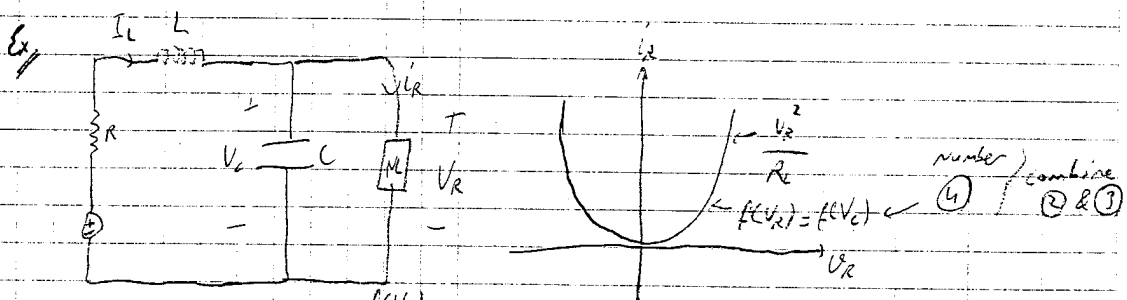- ① Check whether component current/voltage controlled
- ② Try to include the current of the non-linear component if it's current controlled (or it's voltage otherwise)
- ③ Include variables of dynamic components as state variables
- ④ Try to combine ① and ③



KCL: $C \dot{V}_C(t) = -i_R + i_L = V$ RHS contains only state variables

KVL: $-V_s(t) + R i_L + L \dot{i}_L + V_C = 0$

$L \dot{i}_L(t) = -V_C - R i_L + V_s(t) : \checkmark$

$\Rightarrow \dot{V}_C(t) = -\frac{V_C(t)}{R C} + \frac{i_L}{C}$

$\dot{i}_L(t) = -\frac{V_C(t)}{L} - \frac{R}{L} i_L(t) + \frac{V_s(t)}{L}$

Zero Input

$$V_c(0^-) = V_0 \quad \bar{I}_L(0^-) = \bar{I}_0$$

$$\dot{V}_c(t) = -\frac{V_c(t)}{RC} + \frac{\dot{I}_L(t)}{C}$$

$$\dot{I}_L(t) = -\frac{V_c(t)}{L} - \frac{R}{L} I_L(t)$$

$$V_c(t) \triangleq V_c \quad \bar{I}_L(t) \triangleq \bar{I}_L$$

$$\dot{V}_c(t) = 0 \Rightarrow -\frac{V_c^2}{RC} + \frac{\bar{I}_L}{C} = 0 \Rightarrow V_c^2 = \bar{I}_L R C \Rightarrow V_c = \pm \sqrt{R C \bar{I}_L}$$

$$\dot{I}_L(t) = 0 \Rightarrow -\frac{V_c}{L} - \frac{R}{L} \bar{I}_L = 0 \Rightarrow V_c = -R \bar{I}_L$$

