

Nezih Merve Gürel
1674159
Cağatay Candan

21.02.2010

EE201;

Analysis: Given an electrical network \rightarrow Analysis Method

Node analysis Mesh analysis

\rightarrow Simplification Tools

Parallel-Series Combination

Δ -Y
Thevenin-Norton
Source Transformation

The analysis Methods are based on;

- Conservation of energy (KVL)
- Conservation of charge (KCL)
- Components Equations

$$W_{A \rightarrow B} = q \Delta V = q (V_B - V_A)$$

Polar Coordinates:

$$\frac{1}{1+2i} = \frac{-1}{\sqrt{5} \tan^{-1}(2)} = \frac{1}{\sqrt{5}} (-\tan^{-1}(2))^{-1}$$

$$e^{i\pi/3} = \cos \pi/3 + i \sin \pi/3 \quad 1^{1/2} = \{1, -1\} \quad 1^{1/3} = (e^{2\pi j})^{1/3}; \quad 1^{1/3} = \{120^\circ, 1, -120^\circ\}$$


$$\cos \theta = \frac{e^{i\theta} + e^{-i\theta}}{2}; \quad \cos(i2) = \frac{e^{-2} + e^2}{2} = \cosh(2)$$

N^{th} Order Dynamics Circuits

Graph Theoretical Approach and Regular Approach

Graph Theoretical Approach

Node Analysis:

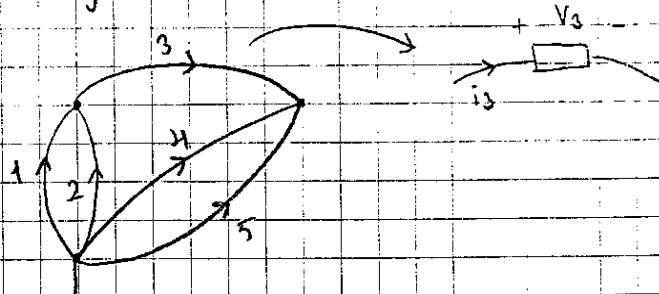

Datum = ground node


1. A: reduced Incidence Matrix (reduced: datum node is not included)

$$\underline{A} \underline{J} = \underline{0} \quad \underline{J}: \text{branch current matrix}$$

$$\begin{bmatrix} 1 & 1 & -1 & 0 & 0 \\ 0 & 0 & 1 & 1 & 1 \end{bmatrix} \begin{bmatrix} J_1 \\ J_2 \\ J_3 \\ J_4 \\ J_5 \end{bmatrix} = \begin{bmatrix} 0 \\ 0 \end{bmatrix}$$

\underline{A} \underline{J}

2- Branch Equations

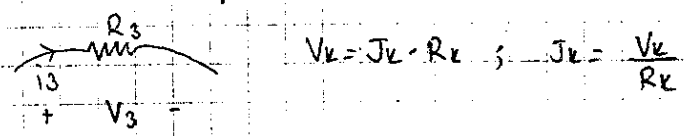

$\underline{J} = \underline{G} \underline{V} + \underline{J}_s$ → source vector

3- $\underline{V} = \underline{A}^T \underline{e}$ → node voltages



4- $\underline{A} \underline{J} = 0$ (1)

$\underline{A} \underline{J} = \underline{A} \underline{G} \underline{V} + \underline{A} \underline{J}_s = 0$


$(\underline{A} \underline{G} \underline{A}^T) \underline{e} = - \underline{A} \underline{J}_s$

Generalized Branch

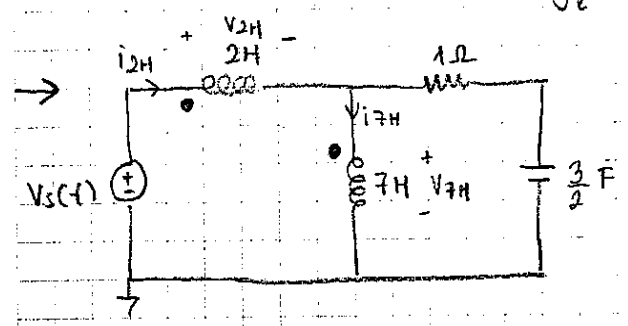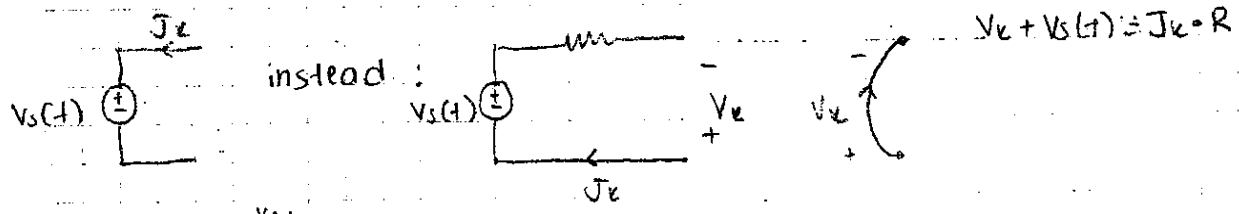In node analysis, branch currents for all components are written, but if we have an independent source (v_s): [J_k for the v_s can be written]



$\underline{A} \underline{J} = 0$

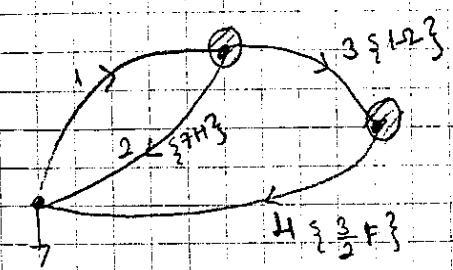

$$\begin{bmatrix} -1 & 1 & 1 & 0 \\ 0 & 0 & -1 & 1 \end{bmatrix} \begin{bmatrix} J_1 \\ J_2 \\ J_3 \\ J_4 \end{bmatrix} = \underline{A} \underline{J}$$

2.) Branch Equations

(3)

J_k : k^{th} branch current in terms of k^{th} branch voltages and possibly other branch voltages


For mutual inductor:

$$\begin{bmatrix} V_{2H}(t) \\ V_{7H}(t) \end{bmatrix} = \underbrace{\begin{bmatrix} 2 & 3 \\ 3 & 7 \end{bmatrix}}_{M(\text{given})} \frac{d}{dt} \begin{bmatrix} i_{2H}(t) \\ i_{7H}(t) \end{bmatrix} \quad d/dt = D$$

Multiply D^{-1} both sides,

$$D^{-1} D \begin{bmatrix} i_{2H}(t) \\ i_{7H}(t) \end{bmatrix} = \begin{bmatrix} 2 & 3 \\ 3 & 7 \end{bmatrix}^{-1} D^{-1} \begin{bmatrix} V_{2H}(t) \\ V_{7H}(t) \end{bmatrix} = \frac{1}{5} \begin{bmatrix} 7 & -3 \\ -3 & 2 \end{bmatrix} D^{-1} \begin{bmatrix} V_{2H}(t) \\ V_{7H}(t) \end{bmatrix}$$
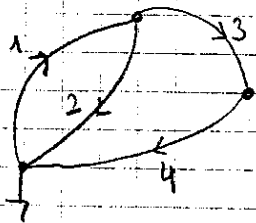
$$= \begin{bmatrix} i_{2H}(t) - i_{2H}(0) \\ i_{7H}(t) - i_{7H}(0) \end{bmatrix} = \frac{1}{5} \begin{bmatrix} 7 & -3 \\ -3 & 2 \end{bmatrix} \begin{bmatrix} \int_0^+ V_{2H}(\tau) d\tau \\ \int_0^+ V_{7H}(\tau) d\tau \end{bmatrix}$$



$$J_1 = i_{2H}(0) + \frac{7}{5} \int_0^+ V_{2H}(\tau) d\tau - \frac{3}{5} \int_0^+ V_{7H}(\tau) d\tau$$

$$J_2 = i_{7H}(0) - \frac{3}{5} \int_0^+ V_{2H}(\tau) d\tau + \frac{2}{5} \int_0^+ V_{7H}(\tau) d\tau$$

$$V_{2H} = V_1 + V_5 \quad V_{7H} = V_2 \quad J_3 = \frac{V_3}{1} \quad J_4 = C \frac{d}{dt} V_4(H) = \frac{3}{2} DV_4$$

$$\begin{bmatrix} J_1 \\ J_2 \\ J_3 \\ J_4 \end{bmatrix} = \begin{bmatrix} 7/5 D^{-1} & -3/5 D^{-1} & 0 & 0 \\ -3/5 D^{-1} & 2/5 D^{-1} & 0 & 0 \\ 0 & 0 & 1 & 0 \\ 0 & 0 & 0 & 3/2 D \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \\ V_3 \\ V_4 \end{bmatrix} + \begin{bmatrix} i_{2H}(0) \\ i_{7H}(0) \\ 0 \\ 0 \end{bmatrix} + \begin{bmatrix} 7/5 D^{-1} \\ -3/5 D^{-1} \\ 0 \\ 0 \end{bmatrix} V_5(t)$$

$$\underline{J} = \underline{G} \underline{V} + J_S$$


Node Equations: $(\underline{A} \underline{G} \underline{A}^T) \underline{e} = -\underline{A} J_S$

$$\rightarrow \begin{bmatrix} 1 & -1 & 1 & 0 \\ 0 & 0 & -1 & 0 \end{bmatrix}$$

$$\rightarrow \left[\begin{array}{c|cc} 3D^{-1} + 1 & & -1 \\ -1 & & 1 + 3/2 D \end{array} \right] \begin{bmatrix} e_A \\ e_B \end{bmatrix} = \begin{bmatrix} i_{2H}(0) - i_{7H}(0) + 2D^{-1} V_5(t) \\ 0 \end{bmatrix}$$

→ integro differential equation

At $t = 0^+$:

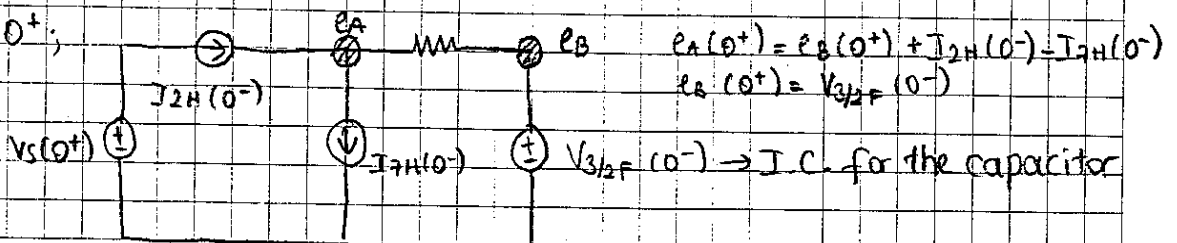


$$e_A(0^+) = e_B(0^+) + J_{2H}(0^-) - J_{7H}(0^-)$$

$$e_B(0^+) = V_{3/2F}(0^-)$$

Scanned at $t = 0^+$ da $J_{2H}(0^-)$ vs. cont. Olduğu için 0^- ya zıdık

Continued;

(4)

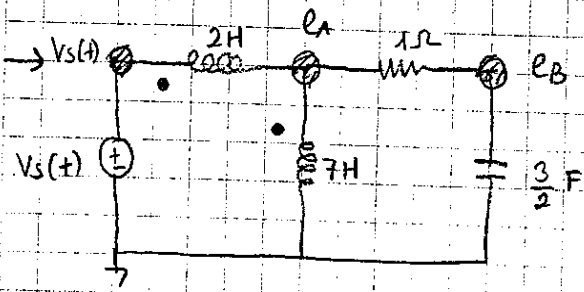

$$\text{KCL @ } e_B; \frac{e_B - e_A}{1} + \frac{3}{2} D e_B = 0$$

$$\text{KCL @ } e_A; \frac{e_A - e_B}{1} + i_{7H}(t) - i_{2H}(t) = 0$$

$$\begin{bmatrix} V_{2H}(t) \\ V_{7H}(t) \end{bmatrix} = \begin{bmatrix} 2 & 3 \\ 3 & 7 \end{bmatrix} \begin{bmatrix} d/dt I_{2H}(t) \\ d/dt I_{7H}(t) \end{bmatrix}$$

$$d/dt \begin{bmatrix} i_{2H}(t) \\ i_{7H}(t) \end{bmatrix} = \frac{1}{5} \begin{bmatrix} 7 & -3 \\ -3 & 2 \end{bmatrix} \begin{bmatrix} V_{2H}(t) \\ V_{7H}(t) \end{bmatrix}$$

$$d/dt i_{2H}(t) = 7/5 V_{2H}(t) - 3/5 V_{7H}(t)$$

$$\int_0^t (-) dt \longrightarrow i_{2H}(t) - i_{2H}(0^-) = 7/5 D^{-1} V_{2H}(t) - 3/5 D^{-1} V_{7H}(t)$$

$$\begin{aligned} \text{Multiply (-)} \rightarrow & \begin{bmatrix} i_{2H}(t) - i_{2H}(0^-) \\ i_{7H}(t) - i_{7H}(0^-) \end{bmatrix} = \begin{bmatrix} 7/5 & -3/5 \\ -3/5 & 2/5 \end{bmatrix} D^{-1} \begin{bmatrix} V_{2H}(t) \\ V_{7H}(t) \end{bmatrix} \\ \text{Multiply (+)} \rightarrow & \end{aligned}$$


$$i_{7H}(t) - i_{2H}(t) = i_{7H}(0^-) - i_{2H}(0^-) + \begin{bmatrix} -2 & 1 \end{bmatrix} D^{-1} [V_{7H}(t) - V_{2H}(t)]$$

$$V_{7H}(t) = e_A(t)$$

$$V_{2H}(t) = V_S(t) - e_A(t)$$

Also do not forget to find $e_A(0^+)$ $e_B(0^+)$ so that node equations are completed.

Mesh Analysis:

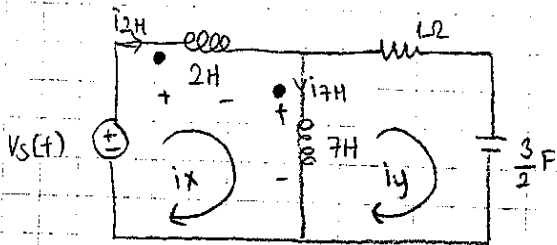

$$\begin{bmatrix} V_{2H} \\ V_{7H} \end{bmatrix} = \begin{bmatrix} 2 & 3 \\ 3 & 7 \end{bmatrix} D \begin{bmatrix} i_{2H}(t) \\ i_{7H}(t) \end{bmatrix}$$

$$\text{Mesh } i_x; -V_S(t) + V_{2H}(t) + V_{7H}(t) = 0$$

$$\text{Mesh } i_y; i_y + \frac{2}{3} D^{-1} i_y(t) - V_{7H}(t) = 0$$

Mesh i_y ; $-V_{2H}(t) + i_y + V_C(t) = 0$ (5)


$$V_C(0^-) + \frac{1}{C} \int_0^+ i_y(\tau) d\tau$$

Mesh i_x ; $-V_S(t) + 2Di_x + 3D(i_x - i_y) + 3Di_x + 7D(i_x - i_y) = 0$

$$-3Di_x - 7D(i_x - i_y) + i_y + V_C(0^-) + \frac{2}{3} D^{-1} i_y = 0$$

$$\begin{bmatrix} 15D & -10D \\ -10D & 7D + \frac{2}{3}D^{-1} + 1 \end{bmatrix} \begin{bmatrix} i_x \\ i_y \end{bmatrix} = \begin{bmatrix} V_S(t) \\ -V_C(0^-) \end{bmatrix} \quad \begin{matrix} i_x(0^+) = ? \\ i_y(0^+) = ? \end{matrix}$$


At $t=0^+$;

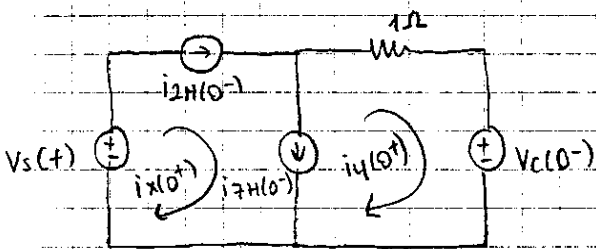

$$i_x(0^+) = I_{2H}(0^-)$$


$$i_y(0^+) = I_{2H}(0^-) - I_{7H}(0^-)$$

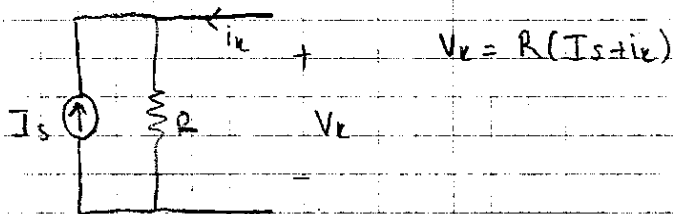If you want to use graph theoretical method for mesh analysis, then generalized branch for current sources can be required.



$$V_k = R(I_s + i_k)$$

Remember for the node analysis;

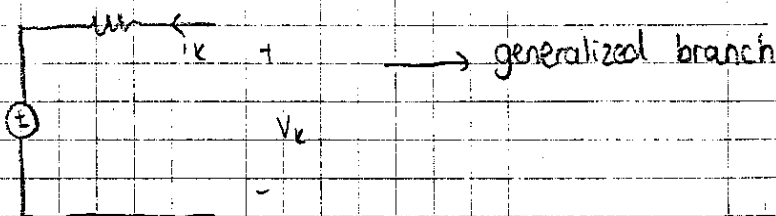

Modified Node Analysis


Previously, node analysis and mesh analysis equations are written

→ Integro differential equations (containing both D and D^{-1})

MNA: Only " D " terms, therefore differential equation set.

- MNA: 1. Assign auxiliary variables for inductors and voltage sources in general to components whose current can not be written only with "D" operator and its voltage.
2. Write node equations.
3. Write equations for each auxiliary variables.

Note: Do not forget Initial Condition.

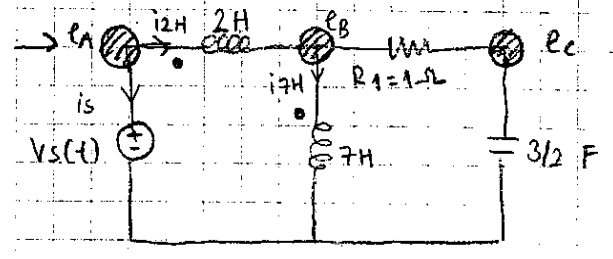


Unknowns: $\{e_A, e_B, e_C, i_s, i_{2H}, i_{7H}\}$: 6 unknowns

$$\begin{bmatrix}
 0 & 0 & 0 & 1 & 1 & 0 \\
 0 & 1/R_1 & -1/R_1 & 0 & -1 & 1 \\
 0 & -1/R_1 & 1/R_1 + 3/2 D & 0 & 0 & 0 \\
 1 & 0 & 0 & 0 & 0 & 0 \\
 1 & -1 & 0 & 0 & -2D & -3D \\
 0 & 1 & 0 & 0 & -3D & -7D
 \end{bmatrix}
 \begin{bmatrix}
 e_A \\
 e_B \\
 e_C \\
 i_s \\
 i_{2H} \\
 i_{7H}
 \end{bmatrix}
 =
 \begin{bmatrix}
 0 \\
 0 \\
 0 \\
 V_s(t) \\
 0 \\
 0
 \end{bmatrix}$$

$$\begin{bmatrix}
 V_{2H} \\
 V_{7H}
 \end{bmatrix}
 =
 \begin{bmatrix}
 2 & 3 \\
 3 & 7
 \end{bmatrix}
 D
 \begin{bmatrix}
 i_{2H} \\
 i_{7H}
 \end{bmatrix}$$

$$V_{2H} = e_A - e_B$$

$$V_{7H} = e_B$$

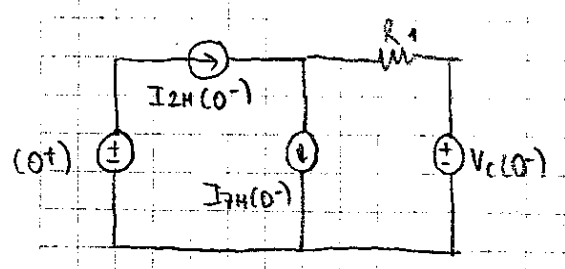

$$e_A(0^+) = V_s(0^+)$$

$$e_B(0^+) = V_c(0^-) + R_1 (i_{2H}(0^-) - i_{7H}(0^-))$$

$$e_C(0^+) = V_c(0^-)$$

$$i_{2H}(0^+) = i_{2H}(0^-); \quad i_{7H}(0^+) = i_{7H}(0^-)$$

- State equations -

Dynamics system containing N dynamic elements, there are many ways of characterizing the system

N^{th} order scalar differential equation; $(D^N + 3D^{N-1} + 2D^{N-2} + \dots + 12D + 25)x(t) = f(t) + 2Df(t)$
ext ext

Mesh } Matrix integro diff. equation
Node }

State eqn.
$$\begin{bmatrix} \dot{x}_1(t) \\ \dot{x}_2(t) \end{bmatrix} = \begin{bmatrix} 1 & 2 \\ 5 & 6 \end{bmatrix} \begin{bmatrix} x_1(t) \\ x_2(t) \end{bmatrix} + \begin{bmatrix} 1 \\ 3 \end{bmatrix} v_s(t) + \begin{bmatrix} 0 \\ 2 \end{bmatrix} i_s(t)$$

1st order matrix 2x2 differential equation

$$\dot{x}(t) = \underline{A} x(t) + \underline{B} u(t)$$

$$\begin{bmatrix} 1 & 0 \\ 0 & 2 \end{bmatrix} \begin{bmatrix} v_s(t) \\ i_s(t) \end{bmatrix}$$

\underline{B} $v(t)$


State variables = $\{v_c(t), I_L(t)\}$ (Cap voltages and inductor currents)

Solution with Laplace Transform (characteristic Eqn)

Writing State Equation


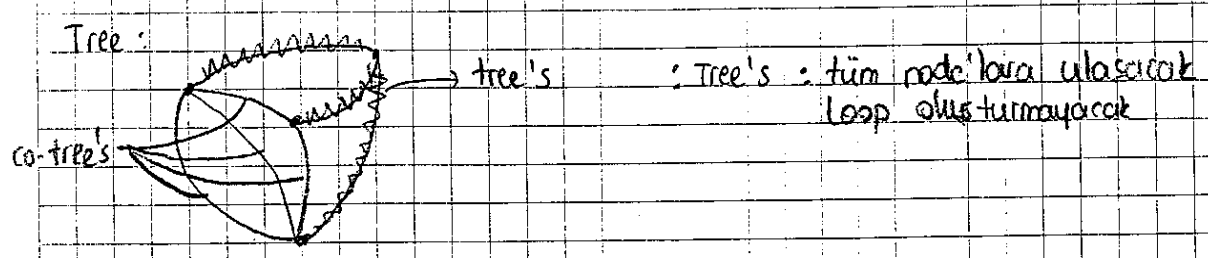
- 1.) Select a proper "tree"
 - i) All voltage sources in tree, All current sources in co-tree
 - ii) Put maximum number of capacitors in tree
 - iii) Put maximum number of inductors in co-tree
 - iv) If there is a transformer, put a branch, (only one branch) in tree, the other one in co-tree
- 2.) Write fundamental loop equations for each inductor in co-tree
- 3.) Write fundamental cut set eqn for each capacitor in tree

State Variables; $\begin{cases} \text{tree capacitors} \\ \text{co-tree inductors} \end{cases}$



Fundamental loop : A loop which contains only one co-tree
 : They're associated with a single co-tree branch

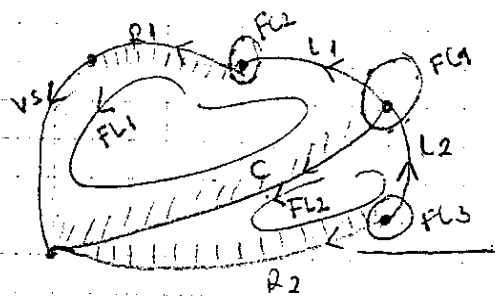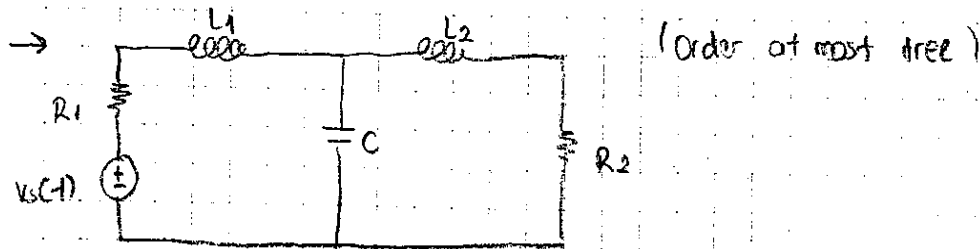Fundamental cut-set : are associated with a single tree branch.



[Inductorları tree yapmamak için R1 & R2 seçtik]
 Node'lara ulaştık böylece

- State equations Do not use generalized branches

State variables : $\{ V_c, I_{L1}, I_{L2} \}$

3 state variables \rightarrow 3rd order system

$$\begin{bmatrix} \dot{V}_c \\ \dot{I}_{L1} \\ \dot{I}_{L2} \end{bmatrix} = \begin{bmatrix} 0 & -1/C & 1/C \\ 1/L1 & -R1/L1 & 0 \\ -1/L2 & 0 & +R2/L2 \end{bmatrix} \begin{bmatrix} V_c \\ I_{L1} \\ I_{L2} \end{bmatrix} + \begin{bmatrix} 0 \\ -1/L1 \\ 0 \end{bmatrix} V_s + \begin{bmatrix} 0 \\ 0 \\ 0 \end{bmatrix} V_s$$

1.) Write fundamental cut-set for capacitor current.

FC1 \rightarrow $i_{C1} - i_{L2} = 0$
 \leftarrow $C \cdot \dot{V}_c$ \rightarrow $V_c^* = \frac{i_{L2} - i_{L1}}{C}$

2.) Write fundamental loop for L1 voltage

$$V_{L1} + V_{R1} + V_s - V_c = 0$$

$$L \dot{I}_{L1} + R_1 \cdot I_{L1} + V_s - V_c = 0$$

\rightarrow FC2 \rightarrow I_{L1}

$$\dot{I}_{L1} = \frac{1}{L1} [-R1 \cdot i_{L1} + V_c - V_s]$$

3.) Write fundamental loop for L_2 voltage

(9)

$$FL_2 \rightarrow V_{L_2} + V_c - V_{R_2} = 0$$

$$L_2 \dot{I}_{L_2} + V_c - R_2 \cdot i_{R_2} = 0 \quad ; \quad I_{L_2} = \frac{1}{L_2} \int (-V_c + R_2 i_{L_2}) dt$$

$$\rightarrow -R_2 \cdot i_{L_2}$$



And we have ; $V_c(t) = \frac{-i_{L_1} + i_{L_2}}{C}$

I.C.

$$V_c(0^+) = V_c(0^-)$$

$$I_{L_1}(0^+) = I_{L_1}(0^-)$$

$$I_{L_2}(0^+) = I_{L_2}(0^-)$$

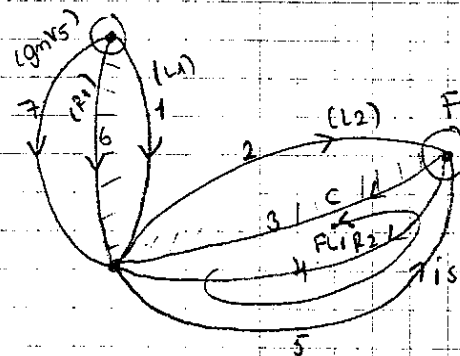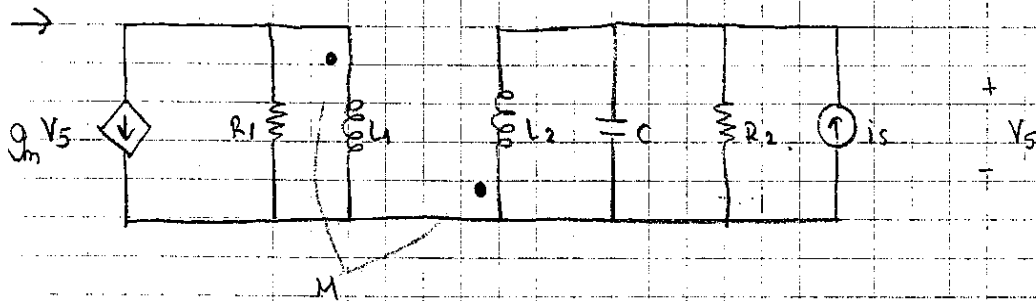

(Circuiti yeter tree)

State variables ; $\{V_c, I_{L_1}, I_{L_2}\}$

- again 3rd order system

1.) Fundamental cut-set for $i_c = i_s$;

$$FC_1 ; i_3 + i_4 - i_s - i_{L_2} = 0$$

$$C \cdot V_c - i_s + \frac{V_4}{R_2} - i_{L_2} = 0$$

$$\rightarrow V_4 = V_3 = V_c ;$$

$$C \cdot V_c - i_s + \frac{V_c}{R_2} - i_{L_2} = 0 ; \quad V_c = \frac{1}{C} \left[i_s - \frac{V_c}{R_2} + i_{L_2} \right]$$

2.) 3.) State eqn for I_{L_1} & I_{L_2}

Write mutual inductor equation:



$$\begin{bmatrix} V_{L_1} \\ V_{L_2} \end{bmatrix} = \begin{bmatrix} L_1 & M \\ M & L_2 \end{bmatrix} \begin{bmatrix} \dot{i}_{L_1} \\ \dot{i}_{L_2} \end{bmatrix}$$

V_{L1} fund. loop $V_{L1} = V_6$ terminal eqn. $i_b R_1$ fundam. cutset $(-i_{L1} - g_m V_5) R_1$

fundam. loop for V_5 $(-i_{L1} - g_m V_5) R_1$ **

V_{L2} fund. loop $-V_c = V_{L2}$ ***
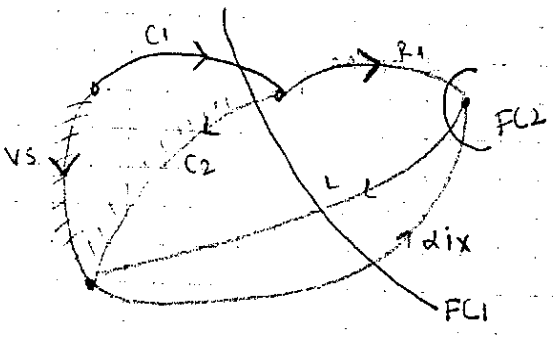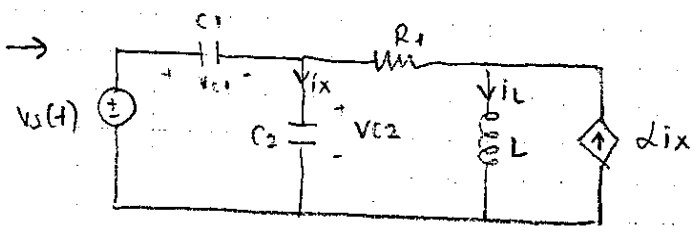
$$\begin{bmatrix} I_{L1} \\ I_{L2} \end{bmatrix} = \begin{bmatrix} L_1 & M \\ M & L_2 \end{bmatrix}^{-1} \begin{bmatrix} V_{L1} \\ V_{L2} \end{bmatrix} \begin{matrix} \rightarrow (-i_{L1} - g_m V_5) R_1 \\ \rightarrow -V_c \end{matrix}$$



Voltage sources treede omak zourde Capacitorien seasen de yeter.

state variables; $\{V_{c2}, I_L\}$ 2nd order circuit

1) Fundamental cut-set for C_2 current

$FL_1 \rightarrow -i_{c1} + i_{c2} + i_L - \alpha i_x = 0$ state variable

$i_x = C_2 \cdot V_{c2}'$

$C_1 \cdot (V_5 - V_{c2})$ fundam. loop

$C_1 \cdot V_{c1}$ $C_2 \cdot V_{c2}$

The Equation becomes; $-C_1 V_5' + C_1 V_{c2}' + C_2 V_{c2}' + i_L - \alpha C_2 V_{c2}' = 0$

$$(C_1 + C_2 - \alpha C_2) V_{c2}' = -i_L + C_1 V_5'$$



$$V_{c2}' = \frac{1}{C_1 C_2 - \alpha C_2} (-i_L + C_1 V_5')$$

2) Fundamental loop for Inductor voltage

$V_{L1} = -V_{R1} + V_{c2} = L_1 I_L' = -R_1 i_L + \alpha C_2 V_2' R_1 + V_{c2}$; $I_L' = \frac{1}{L} (-R_1 I_L + \alpha C_2 V_2' R_1 + V_{c2})$

$V_{R1} = i_{R1} \cdot R_1 = (i_L - \alpha i_x) R_1 = (i_L - \alpha C_2 V_2') R_1$

fundamental cutset 2

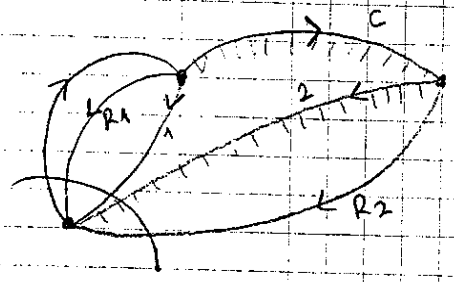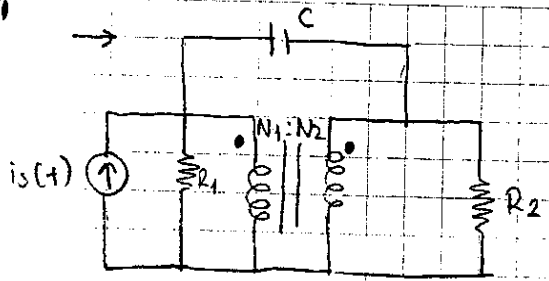

$$\frac{V_1}{V_2} = \frac{N_1}{N_2}$$

$$\frac{i_1}{i_2} = -\frac{N_2}{N_1}$$

1. Fundamental cut-set for C, V_C i.e. i_C current

$$C \cdot V_C = i_s - i_{R1} - i_1$$

$$\xrightarrow{\frac{V_{R1}}{R_1} \text{ funda. loop}} \frac{(V_C + V_2)}{R_1}$$

$$V_2 = \frac{N_2 V_1}{N_1} \xrightarrow{\text{funda. loop}} \frac{N_2 (V_C + V_2)}{N_1}; \quad * \quad V_2 = \frac{\frac{N_2 V_C}{N_1}}{\left(1 - \frac{N_2}{N_1}\right)} = \frac{N_2 V_C}{N_1 - N_2}$$

$$* \quad i_{R1} = \frac{1}{R_1} V_C \left(1 + \frac{N_2}{N_1 - N_2}\right)$$

$$* \quad i_1 = -\frac{N_2}{N_1} i_2 \xrightarrow{\text{funda. cutset}} -\frac{N_2}{N_1} (i_s - i_{R1} - i_1 - i_{R2})$$

Terminal eqn.

$$\xrightarrow{\frac{V_{R2}}{R_2} \text{ funda. loop}} \frac{V_2}{R_2}$$

$$i_1 \left(1 - \frac{N_2}{N_1}\right) = -\frac{N_2}{N_1} i_s + \frac{N_2}{N_1} i_{R1} + \frac{N_2}{N_1} \left(\frac{V_2}{R_2}\right) * \rightarrow \text{but must be!}$$

$$i_1 = \frac{i_s - \frac{V_C}{N_1 - N_2} \left(\frac{N_1}{R_1} + \frac{N_2}{R_2}\right)}{1 - \frac{N_2}{N_1}}$$

$$C V_C = i_s - i_{R1} - i_1$$


State eqn:

$$\begin{bmatrix} \dot{x}_1(t) \\ \dot{x}_2(t) \end{bmatrix} = \begin{bmatrix} a_{11} & a_{12} \\ a_{21} & a_{22} \end{bmatrix} \begin{bmatrix} x_1(t) \\ x_2(t) \end{bmatrix} + \begin{bmatrix} b_1 \\ b_2 \end{bmatrix} v_s(t) + \begin{bmatrix} c_1 \\ c_2 \end{bmatrix} v_3^*(t)$$

Solution of n^{th} order diff. equations

First, we'll examine zero-input case

i.e. Only initial conditions

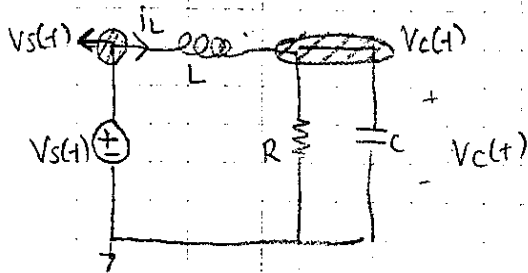

Node equations: $\frac{V_c(t)}{R} + C V_c'(t) - i_L = 0$
 $\hookrightarrow i_L(t) = i_L(0^-) + \int_0^t \underbrace{V_L(\tau)}_{V_s - V_c(\tau)} d\tau$

$$\left(\frac{1}{R} + CD\right) V_c(t) - \left[i_L(0^-) + \frac{1}{L} D^{-1} (V_s(t) - V_c(t)) \right] = 0$$


Apply $D = d/dt$ operator both sides ;

$$\left(\frac{D}{R} + CD^2\right) V_c(t) - \frac{1}{L} (V_s(t) - V_c(t)) = 0$$

$$\left(D^2 + \frac{1}{RC} D + \frac{1}{LC}\right) V_c(t) = \frac{1}{LC} V_s(t)$$

$V_c(0^+) = ?$

$V_c'(0^+) = ?$ At $t = 0^+$;

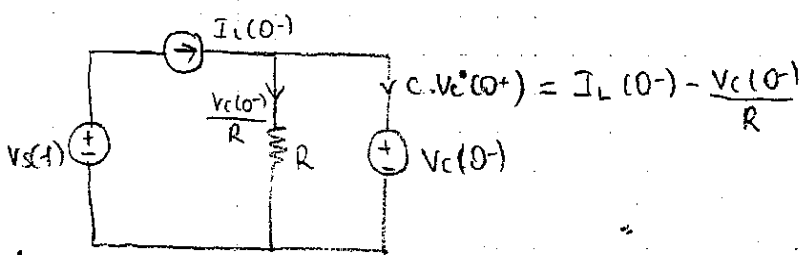

Rewriting again;

$$\left(D^2 + \frac{1}{RC} D + \frac{1}{LC}\right) V_c(t) = \frac{1}{LC} V_s(t) \quad V_c(0^+), V_c'(0^+) \text{ given}$$

[Constant coefficient diff. equation]


Solution
 ↙ particular
 ↘ homogenous

Solution
 ↙ zero input (only initial cond) sources are zero
 ↘ zero state (initial condit. are zero) sources are active

For now, let's focus on zero-input then;

$$\left(D^2 + \frac{1}{RC} D + \frac{1}{LC} \right) V_C(t) = 0 \quad V_C(0^+), V_C'(0^+) \text{ are given}$$

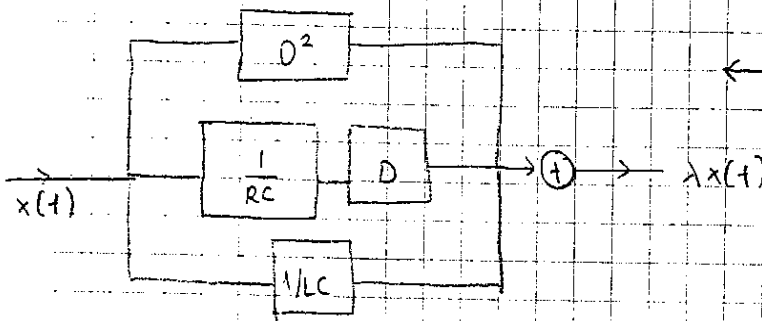For CCDE systems, the exponential functions and eigenfunctions of the system.



← definition of eigenfunction

$$\left(D^2 + \frac{1}{RC} D + \frac{1}{LC} \right) V_C(t) = 0$$

define $V_C(t) = \alpha e^{\lambda t}$

$$\alpha \left(\lambda^2 + \frac{1}{RC} \lambda + \frac{1}{LC} \right) e^{\lambda t} = 0$$

↳ $\alpha = 0$ $V_C(t) = 0$ ($V_C(0^+) \neq 0$ I.C.)

↳ $e^{\lambda t} \neq 0$

↳ $\lambda^2 + \frac{1}{RC} \lambda + \frac{1}{LC} = 0$ (set λ is equal to roots of the equation)

Example: Set $R=1/3$ $C=1$ $L=1/2$

$$(D^2 + 3D + 2) V_C(t) = 0$$

$V_C(0^+) = V_0$, $V_C'(0^+) = I_0 - 3V_0$ (hard verdi)

$$\lambda^2 + 3\lambda + 2 = 0 \quad \lambda = \{-1, -2\}$$

$V_C(t) = \{ \alpha e^{-t}, \beta e^{-2t} \}$ → natural frequencies (roots of charact eqn)

$V_C(t) = \alpha e^{-t} + \beta e^{-2t}$

Select α, β such that
I.C. at 0^+ is satisfied.

Question: (Mode excitation)

$$(D^2 + 3D + 2)V_c(t) = 0 \quad V_c(0^+) = V_0 \quad V_c'(0^+) = I_0 - 3V_0$$

$$V_c(t) = \alpha e^{-t} + \beta e^{-2t} \quad (\text{modes of the circuit})$$

Q: Excite only one mode by selecting I.C.'s (V_0, I_0) properly

$$V_c(0^+) = \alpha + \beta$$

$$V_c'(0^+) = -\alpha - 2\beta$$

To have the mode $V_c(t) = \alpha e^{-t} \rightarrow \beta = 0 \rightarrow V_c(0^+) = \alpha$

$$\begin{bmatrix} V_0 \\ I_0 \end{bmatrix} = \alpha \begin{bmatrix} 1 \\ 2 \end{bmatrix}$$

\uparrow
 $I_L(0^-)$




$$V_c'(0^+) = -\alpha$$

\swarrow
 $I_0 - 3V_0$

$$V_c(t) = \beta e^{-2t} \rightarrow \alpha = 0 \rightarrow V_c(0^+) = \beta \rightarrow \begin{bmatrix} V_0 \\ I_0 \end{bmatrix} = \beta \begin{bmatrix} 1 \\ -1 \end{bmatrix}$$

$$V_c'(0^+) = -2\beta$$

Example:

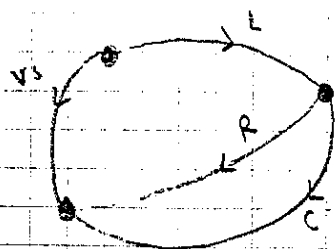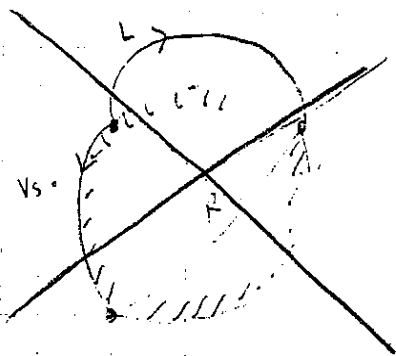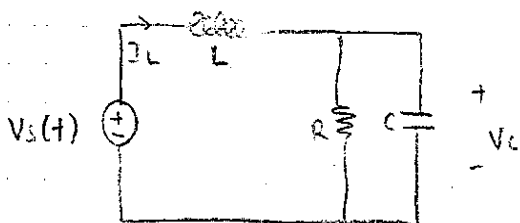

State variable: $\{V_c, I_L\}$

$$1. \quad C V_c' = -i_R + i_L = -\frac{V_c}{R} + i_L$$

$$\frac{V_R}{R} = \frac{V_c}{R}$$

$$2. \quad L I_L' = V_s - V_R = V_s - V_c$$

$$\begin{bmatrix} V_c^{\circ}(t) \\ I_L^{\circ}(t) \end{bmatrix} = \begin{bmatrix} -1/RC & 1/C \\ -1/L & 0 \end{bmatrix} \begin{bmatrix} V_c(t) \\ I_L(t) \end{bmatrix} + \begin{bmatrix} 0 \\ 1/L \end{bmatrix} V_s(t)$$

$V_c(0^+) = V_c(0^-); I_L(0^+) = I_L(0^-)$

To show that state eqn form \equiv Node Analysis form

Take derivative of $V_c^{\circ}(t) =$ _____ equation

$$V_c^{\circ\circ}(t) = \frac{-1}{RC} V_c^{\circ}(t) + \frac{1}{C} \frac{d}{dt} I_L(t) \quad \frac{-1}{L} V_c(t) + \frac{1}{L} V_s(t)$$

$(D^2 + \frac{1}{RC} D + \frac{1}{LC}) V_c(t) = \frac{1}{LC} V_s(t)$ Same as node analysis eqn.

Example: $R=1/3, C=1, L=1/2$

$$\begin{bmatrix} V_c^{\circ}(t) \\ I_L^{\circ}(t) \end{bmatrix} = \begin{bmatrix} -3 & 1 \\ -2 & 0 \end{bmatrix} \begin{bmatrix} V_c(t) \\ I_L(t) \end{bmatrix} + \begin{bmatrix} 0 \\ 2 \end{bmatrix} V_s(t)$$

$\underline{x}^{\circ}(t) = \underline{A} \underline{x}(t) + \underline{b} V_s(t)$

zero input case

$\underline{x}^{\circ}(t) = \underline{A} \underline{x}(t)$

let $\underline{x}(t) = \begin{bmatrix} \delta_1 \\ \delta_2 \end{bmatrix} e^{\lambda t}$

$\begin{bmatrix} \delta_1 \\ \delta_2 \end{bmatrix} \lambda e^{\lambda t} = \underline{A} \begin{bmatrix} \delta_1 \\ \delta_2 \end{bmatrix} e^{\lambda t}$ trivial soln, $\begin{bmatrix} \delta_1 \\ \delta_2 \end{bmatrix} = \begin{bmatrix} 0 \\ 0 \end{bmatrix}$ not suitable.

$\begin{bmatrix} \delta_1 \\ \delta_2 \end{bmatrix} = \underline{A} \begin{bmatrix} \delta_1 \\ \delta_2 \end{bmatrix}$ λ : eigenvalues of \underline{A}

$\underline{A} = \begin{bmatrix} -3 & 1 \\ -2 & 0 \end{bmatrix}$

$|\underline{A} - \lambda \underline{I}| = 0 \implies \det \begin{pmatrix} \lambda + 3 & -1 \\ 2 & \lambda \end{pmatrix} = 0; \lambda^2 + 3\lambda + 2 = 0$


$\lambda = \{-1, -2\}$ (natural frequencies)

$$e^{2t} \begin{bmatrix} 1 \\ 1 \end{bmatrix}$$

$$x(t) = \begin{bmatrix} 1 \\ 1 \end{bmatrix} e^{-2t} \quad \text{if } v_C(0^-) = 1V \\ i_L(0^-) = 1A$$

Finding Natural Frequency

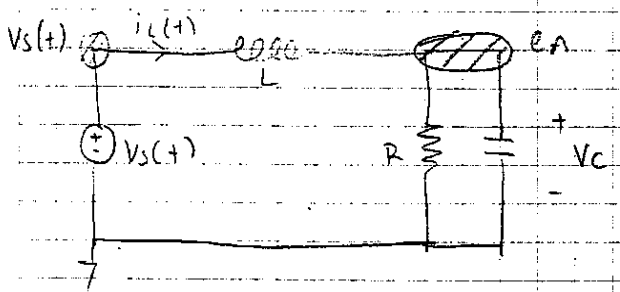- 1. Scalar Diff. Eqn.
- 2. State Eqn.
- 3. Modified Node Analysis



$i_C(t)$: auxiliary variables

$$\begin{bmatrix} 1/R + C D & -1 \\ 1 & L D \end{bmatrix} \begin{bmatrix} v_C(t) \\ i_L(t) \end{bmatrix} = \begin{bmatrix} 0 \\ v_s(t) \end{bmatrix}$$

↑
Introduced (since MNA)

$v_C(t) = L \frac{d}{dt} i_L(t)$
RHS

Zero-Input Solution RHS = 0

Guess for zero input:

$$\begin{bmatrix} v_C(t) \\ i_L(t) \end{bmatrix} = \begin{bmatrix} \alpha_1 \\ \alpha_2 \end{bmatrix} e^{\lambda t}$$

$$\begin{bmatrix} 1/R + C\lambda & -1 \\ 1 & L\lambda \end{bmatrix} \begin{bmatrix} \alpha_1 \\ \alpha_2 \end{bmatrix} e^{\lambda t} = \begin{bmatrix} 0 \\ 0 \end{bmatrix}$$

For nontrivial solution should have zero determinant

Let $R=1/3$ $C=1$ $L=1/2$

$$\begin{bmatrix} \lambda+3 & -1 \\ 1 & \lambda/2 \end{bmatrix} = 0$$

determinant

Characteristic Polynomial : $(\lambda+3) \cdot \lambda/2 + 1 = 0$

$$\lambda^2 + 3\lambda + 2 = 0 \cdot 2 = 0 \quad (\lambda+2)(\lambda+1) = 0 \quad \lambda = \{-2, -1\}$$

To only excite $\lambda = -1$ mode, what should 0^+ values of circuit variables.


$$\begin{bmatrix} e_A(t) \\ I_L(t) \end{bmatrix} = \begin{bmatrix} \alpha_1 \\ \alpha_2 \end{bmatrix} e^{-t} \leftarrow \text{desired single mode excitation}$$

$$\begin{bmatrix} \lambda+3 & -1 \\ 1 & \lambda/2 \end{bmatrix} \begin{bmatrix} \alpha_1 \\ \alpha_2 \end{bmatrix} e^{-t} = \begin{bmatrix} 0 \\ 0 \end{bmatrix}$$

$\lambda = -1$

$$\begin{bmatrix} \alpha_1 \\ \alpha_2 \end{bmatrix} \propto \begin{bmatrix} 1 \\ 2 \end{bmatrix} ; \quad \begin{bmatrix} e_A(t) \\ I_L(t) \end{bmatrix} \propto \begin{bmatrix} 1 \\ 2 \end{bmatrix} e^{-t} \rightarrow \begin{bmatrix} e_A(0^+) \\ I_L(0^+) \end{bmatrix} \propto \begin{bmatrix} 1 \\ 2 \end{bmatrix}$$

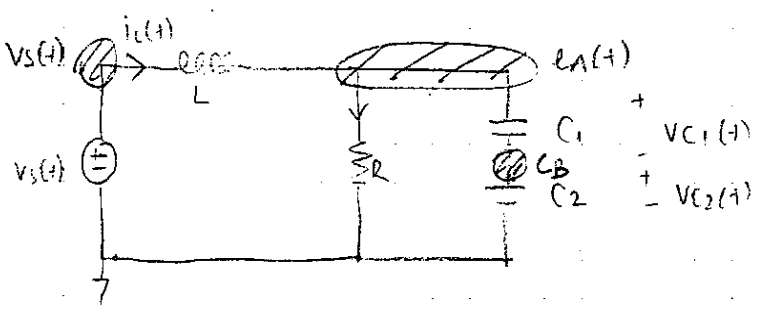4- By node Analysis (e_A, e_B, e_C, \dots)



$$\text{KCL @ } e_A: \frac{e_A}{R} + C_1(e_A - e_B) - \left[(i_L(0^-)) + \frac{1}{L} \int_0^+ (v_s(t) - e_A(t)) dt \right] = 0$$

$$\text{KCL @ } e_B: C_2 = e_B + C_1(e_B - e_A) = 0$$

$$\begin{bmatrix} 1/R + C_1 D + 1/L D^{-1} & -C_1 D \\ -C_1 D & C_1 D + C_2 D \end{bmatrix} \begin{bmatrix} e_A \\ e_B \end{bmatrix} = \begin{bmatrix} I_L(0^-) + 1/L \int_0^+ v_s(t) \\ 0 \end{bmatrix}$$

Zero input Solution: $\begin{bmatrix} e_A(t) \\ e_B(t) \end{bmatrix} = \begin{bmatrix} \alpha_1 \\ \alpha_2 \end{bmatrix} e^{\lambda t}$ (since CCDE)

In NA, we have integro diff. eqn (MNA: diff. eqn).

$$\begin{bmatrix} D/R + C_1 D^2 + 1/L & -C_1 D^2 \\ -(C_1 D) & (C_1 + C_2) D \end{bmatrix} \begin{bmatrix} e_A(t) \\ e_B(t) \end{bmatrix} = \begin{bmatrix} 1/L V_s(t) \\ 0 \end{bmatrix} \quad V_s(t) = 0 \text{ zero-input}$$

So take 1st derivative of KCL @ ea eqn.

$R = 1/3 \Omega$ $C_1 = 2 \text{ F}$ $L = 1/2 \text{ H}$
 $C_2 = 2 \text{ F}$

$$\begin{bmatrix} e_A(t) \\ e_B(t) \end{bmatrix} = \begin{bmatrix} \alpha_1 \\ \alpha_2 \end{bmatrix} e^{\lambda t}$$

$$\begin{bmatrix} 3\lambda + 2\lambda^2 + 2 & -2\lambda^2 \\ -2\lambda & 4\lambda \end{bmatrix} \begin{bmatrix} \alpha_1 \\ \alpha_2 \end{bmatrix} e^{\lambda t} = \begin{bmatrix} 0 \\ 0 \end{bmatrix}$$

$\det = 0; \rightarrow (3\lambda + 2\lambda^2 + 2) 4\lambda - 4\lambda^3 = 0$

$4\lambda(\lambda^2 + 3\lambda + 2) = 0$

$\lambda = \{0, -1, -2\}$

To only excite $\lambda = 0$;

$$\begin{bmatrix} e_A(t) \\ e_B(t) \end{bmatrix} = \begin{bmatrix} \alpha_1 \\ \alpha_2 \end{bmatrix} e^{\lambda t}$$

$$\begin{bmatrix} 3\lambda + 2\lambda^2 + 2 & -2\lambda^2 \\ -2\lambda & 4\lambda \end{bmatrix} \begin{bmatrix} \alpha_1 \\ \alpha_2 \end{bmatrix} e^{\lambda t} = \begin{bmatrix} 0 \\ 0 \end{bmatrix}$$

$\lambda = 0$

$$\begin{bmatrix} 2 & 0 \\ 0 & 0 \end{bmatrix} \begin{bmatrix} \alpha_1 \\ \alpha_2 \end{bmatrix} = \begin{bmatrix} 0 \\ 0 \end{bmatrix} \rightarrow \begin{bmatrix} \alpha_1 \\ \alpha_2 \end{bmatrix} \propto \begin{bmatrix} 0 \\ 1 \end{bmatrix}$$

$2\alpha_1 = 0$


proportional

$$\begin{bmatrix} e_A(t) \\ e_B(t) \end{bmatrix} \alpha \begin{bmatrix} 0 \\ 1 \end{bmatrix} = \begin{bmatrix} 0 \\ A \end{bmatrix}$$

$\rightarrow V_{C1}(t) + V_{C2}(t)$

\downarrow
 $V_{C2}(t)$
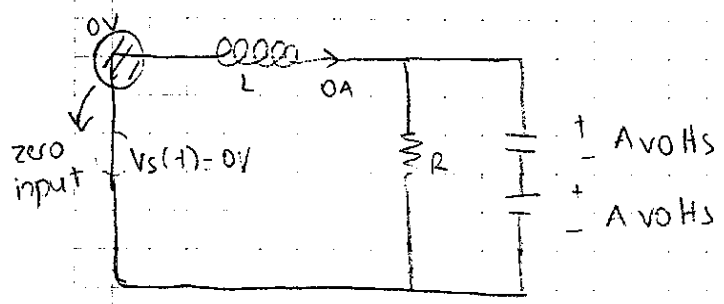
$$\begin{bmatrix} V_{C1}(t) \\ V_{C2}(t) \end{bmatrix} \alpha \begin{bmatrix} -1 \\ 1 \end{bmatrix} \begin{bmatrix} -A \\ A \end{bmatrix}$$



Note 1: We preferred modified node analysis due to presence of D' operators in node analysis. We have cancelled D' operators by an additional derivative and this cancellation operation can make natural frequency at $\lambda=0$ invisible (due to cancellations)

In this example, $\lambda=0$ mode is not cancelled (there was not any such cancellation leading to invisibility of a mode) but in general, this is possible.

- In general $\lambda=0$ mode can appear when you have series/parallel capacitors or inductors in the system.

Note 2: We prefer state eqns to the other method since

- 1 Method for eqn writing
- 2 Method for natural freq. finding $\rightarrow \text{eig}(A)$ (matlab)
- 3 Mode excitations are also available \rightarrow eigenvectors of A

Stability:




Let's focus on zero-input solution (no forcing term/external input)

Given initial cond. if initial cond. decay the zero,

We call about system "stable" system (other def. are also possible)

$$\begin{bmatrix} V_c(t) \\ I_L(t) \end{bmatrix} \longrightarrow \begin{matrix} V_c(t) = \alpha_1 e^{\lambda_1 t} + \beta_1 e^{\lambda_2 t} \\ I_L(t) = \alpha_2 e^{\lambda_1 t} + \beta_2 e^{\lambda_2 t} \end{matrix} \quad (21)$$

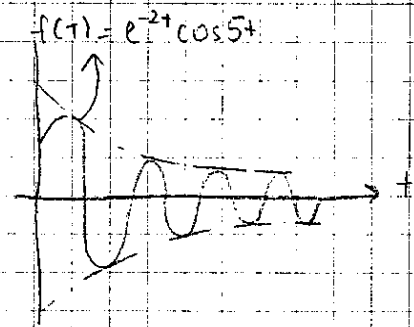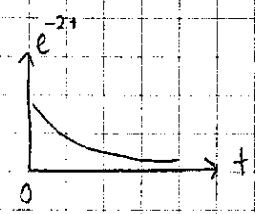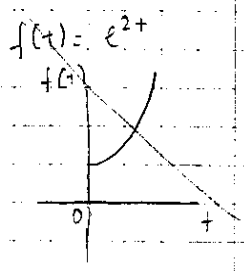For stability $\rightarrow \operatorname{Re} \{ \lambda_1 \} < 0$ natural frequencies should have negative real parts
 $\operatorname{Re} \{ \lambda_2 \} < 0$



$f(t) = e^{\lambda t}$ $\lambda = -2 + j3$
 \swarrow real argument
 \searrow complex valued function

$$f(t) = e^{(-2+j3)t} = e^{-2t} (\cos 3t + j \sin 3t)$$


$$e^{j\phi} \triangleq \cos \phi + j \sin \phi$$

$$e^{z \in t} = \sum_{k=0}^{\infty} \frac{z^k}{k!} \quad k^{\text{th}} \text{ power of complex number}$$

$\|f(t)\| \rightarrow 0$ as $t \rightarrow \infty$
 then $f(t) \rightarrow 0 \neq 0$
 $\rightarrow \infty$

Further details:

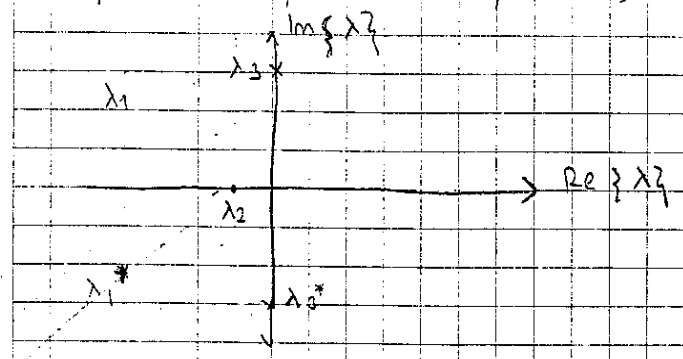- ① All λ 's have negative real parts \rightarrow asymptotically stable $f(t) \rightarrow 0$ as $t \rightarrow \infty$
- ② All λ 's have negative or zero real parts \rightarrow stable (only) $f(t) \rightarrow 5$ as $t \rightarrow \infty$
- ③ Any λ 's have positive real part \rightarrow unstable $f(t) \rightarrow \infty$



\rightarrow asymptotically stable


Solving Nth Order Circuits

Our focus is on inputs of type $f(t) = e^{s_0 t}$

s_0 is a complex number

In this part, we'll find only particular solution to $f(t) = e^{s_0 t}$

Example:

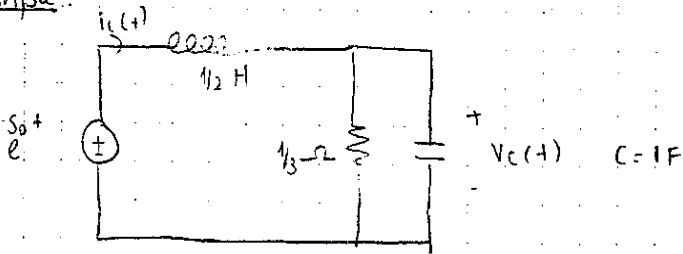

Scalar Diff. Eqn Case:

$$(D^2 + 3D + 2)V_c(t) = 2v_s(t) = 2e^{s_0 t}$$

$$V_c(t) = V_c^h(t) + V_c^p(t)$$

$$V_c^p(t) = A e^{s_0 t}$$

↓ substit into diff. eqn

$$A(s_0^2 + 3s_0 + 2)e^{s_0 t} = 2e^{s_0 t}$$

$$A = \frac{2}{s_0^2 + 3s_0 + 2} \text{ provided that } s_0^2 + 3s_0 + 2 \neq 0 \text{ or } s_0 \text{ is not natural frequency.}$$

$$\rightarrow (D^2 + 3D + 2)V_c(t) = 2v_s(t)$$

$$V_c(0^+) = V_0$$

$$V_c'(0^+) = V_0'$$

$$V_c^{\text{complete}}(t) = \alpha e^{-t} + \beta e^{-2t} + V_c^{\text{particular}}$$

Particular Solution

Let's $v_s(t) = e^{s_0 t}$ $s_0 \in \mathbb{C} \rightarrow$ complex number

$$(D^2 + 3D + 2)V_c^p(t) = 2v_s(t)$$

$$\text{Guess } V_c^p(t) = A e^{s_0 t} \rightarrow A(s_0^2 + 3s_0 + 2)e^{s_0 t} = 2e^{s_0 t}$$

$$A = \frac{2}{s_0^2 + 3s_0 + 2} \quad s_0 \neq \{-1, -2\}$$

$$s_0 \neq \{\text{natural frequency}\}$$

$$V_c^p(t) = \frac{2}{s^2 + 3s + 2} e^{5t}$$

$V_s(t)$	$V_c^p(t)$
e^{-3t}	e^{-3t}
e^{-5t}	$\frac{2}{12} e^{-5t}$
1	1
e^{-2+jt}	$\frac{2}{-2-j0} e^{-2+jt}$
$e^t (s_0=1)$	$\frac{1}{3} e^t$

$A = \frac{2}{s^2 + 3s + 2} \Big|_{s_0 = -3} = 1 \cdot e^{-3t}$

Example: Same circuit with state eqn

$$\begin{bmatrix} V_c^p(t) \\ I_L^p(t) \end{bmatrix} = \begin{bmatrix} -3 & 1 \\ -2 & 0 \end{bmatrix} \begin{bmatrix} V_c \\ I_L \end{bmatrix} + \begin{bmatrix} 0 \\ 2 \end{bmatrix} V_s(t)$$

Interest: Particular solution for exponential family of inputs ($V_s(t) = e^{s_0 t}$)

Guess: $\begin{bmatrix} V_c^p(t) \\ I_L^p(t) \end{bmatrix} = \begin{bmatrix} \alpha \\ \beta \end{bmatrix} e^{s_0 t}$

Substitute the guess into state eqn.

$$s_0 \begin{bmatrix} \alpha \\ \beta \end{bmatrix} e^{s_0 t} = \begin{bmatrix} -3 & 1 \\ -2 & 0 \end{bmatrix} \begin{bmatrix} \alpha \\ \beta \end{bmatrix} e^{s_0 t} + \begin{bmatrix} 0 \\ 2 \end{bmatrix} e^{s_0 t}$$

$$\left(s_0 \cdot I - \begin{bmatrix} -3 & 1 \\ -2 & 0 \end{bmatrix} \right) \begin{bmatrix} \alpha \\ \beta \end{bmatrix} = \begin{bmatrix} 0 \\ 2 \end{bmatrix}$$

$$\begin{bmatrix} s_0 + 3 & -1 \\ 2 & s_0 \end{bmatrix} \begin{bmatrix} \alpha \\ \beta \end{bmatrix} = \begin{bmatrix} 0 \\ 2 \end{bmatrix}$$

$$\begin{bmatrix} \alpha \\ \beta \end{bmatrix} = \frac{1}{s_0^2 + 3s_0 + 2} \begin{bmatrix} s_0 & 1 \\ -2 & s_0 + 3 \end{bmatrix} \begin{bmatrix} 0 \\ 2 \end{bmatrix} = \frac{1}{s_0^2 + 3s_0 + 2} \begin{bmatrix} 2 \\ 2(s_0 + 3) \end{bmatrix}$$

$s_0 \neq \{-1, -2\}$

$$\begin{bmatrix} V_c^p(t) \\ I_L^p(t) \end{bmatrix} = \frac{1}{s_0^2 + 3s_0 + 2} \begin{bmatrix} 2 \\ 2(s_0 + 3) \end{bmatrix} e^{s_0 t}$$

$$V_c^p(t) = \frac{2}{s_0^2 + 3s_0 + 2} e^{s_0 t}$$

Example: Same circuit with $V_s(t) = \cos 5t$

$$(D^2 + 3D + 2) V_c^p(t) = 2 \cos 5t$$

$$V_c^p(t) = A \cos 5t + B \sin 5t \quad \times 2$$

$$V_c^{p'}(t) = -5A \sin 5t + 5B \cos 5t \quad \times 3$$

$$V_c^{p''}(t) = -25A \cos 5t - 25B \sin 5t \quad \times 1$$

$$\cos 5t (2A + 15B - 25A) + \sin 5t (2B - 15A - 25B) \\ \cos 5t (-23A + 15B) + \sin 5t (-23B - 15A) = 2 \cos 5t$$

$$\begin{aligned} -23B &= 15A & -23A + 15B &= 2 & \times 15 \\ 15A + 23B &= 0 & & & \times 23 \end{aligned}$$

$$\begin{aligned} -15 \cdot 23A + 225B &= 30 \\ 15 \cdot 23A + 23^2 B &= 0 \\ (15^2 + 23^2) B &= 30 \text{ buradan } A \text{ ve } B \\ &\text{ bulunur.} \end{aligned}$$

or: $(D^2 + 3D + 2) V_c^p(t) = \underbrace{2 \operatorname{Re} \{ e^{j5t} \}}_{\cos 5t}$

2. $V_c^p(t) = \operatorname{Re} \{ A_c e^{j5t} \} \leftarrow \text{Guess}; \quad A_c \in \mathbb{C}$

3. $V_c^{p'}(t) = \operatorname{Re} \left\{ \frac{d}{dt} \{ A_c e^{j5t} \} \right\} = \operatorname{Re} \{ A_c j5 e^{j5t} \}$

1. $V_c^{p''}(t) = \operatorname{Re} \left\{ \frac{d^2}{dt^2} \{ A_c e^{j5t} \} \right\} = \operatorname{Re} \{ A_c (-25) e^{j5t} \}$


$$(D^2 + 3D + 2) V_c^p(t) = \operatorname{Re} \{ 2 A_c e^{j5t} \} + \operatorname{Re} \{ 3 A_c (j5) e^{j5t} \} + \operatorname{Re} \{ A_c (-25) e^{j5t} \} \\ = \operatorname{Re} \{ 2 e^{j5t} \}$$

$$2 A_c e^{j5t} + 3 A_c (j5) e^{j5t} + A_c (-25) e^{j5t} = 2 e^{j5t}$$

$$2A_c + 15j A_c - 25A_c = 2$$

$A_c = \frac{2}{23 + j15 - 25}$

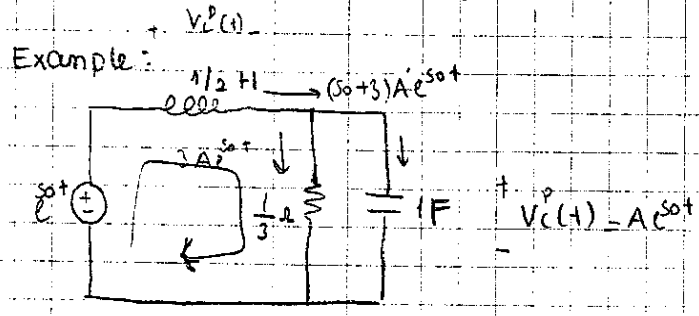$V_c^p(t) = \text{Re} \left\{ \frac{2}{23 + j15} e^{j15t} \right\}$
 $= \text{Re} \left\{ \frac{21 - 23 - j15}{23^2 + 15^2} (\cos 5t + j \sin 5t) \right\}$
 $= \frac{2}{23^2 + 15^2} (-23 \cos 5t + 15 \sin 5t)$



$V_c^p(t) = 0$

$V_c^p(t) = Ae^{s\omega t}$ $I_c(t) = C \cdot A s \omega e^{s\omega t} \Big|_{C=1} = s \omega A e^{s\omega t}$

$V_L^p(t) = L \cdot D [(s+3)Ae^{s\omega t}]$

$V_L^p(t) = L \cdot A s \omega (s+3) e^{s\omega t} = \frac{A s \omega (s+3)}{2} e^{s\omega t}$

KVL; $-e^{s\omega t} + V_L^p(t) + V_c^p(t) = 0 \rightarrow A \cdot \frac{2}{s\omega^2 + 3s\omega + 2}$

Phasors: (related to phases)

$f(t) = A e^{j\omega t}$
 ↑
 phaser quantity

$f(t) = (1+j) e^{j5t}$
 ↑ phasor = $1+j = \sqrt{2} \angle 45^\circ$

$2 \cos(\omega t + \frac{\pi}{6}) = 2 \text{Re} \left\{ e^{j(\omega t + \pi/6)} \right\}$
 $= \text{Re} \left\{ 2 e^{j\pi/6} e^{j\omega t} \right\}$ 2 $\angle 30^\circ$ phasor

$2 \cos(\omega t + 30^\circ) \xrightarrow{\text{phasor}} 2 \angle 30^\circ$

Example: $\cos \frac{(A+B)}{2} + \cos \frac{(A-B)}{2} = 2 \cos \left(\frac{A+B}{2} \right) \cos \left(\frac{A-B}{2} \right)$

$$\begin{aligned}
 &= \operatorname{Re} \left\{ e^{j(4+30^\circ)} \right\} + \operatorname{Re} \left\{ e^{j(4+60^\circ)} \right\} \\
 &= \operatorname{Re} \left\{ e^{j(4+30^\circ)} + e^{j(4+60^\circ)} \right\} \\
 &= \operatorname{Re} \left\{ e^{j4} \left(e^{j\pi/6} + e^{j\pi/3} \right) \right\} \\
 &= \operatorname{Re} \left\{ \left(\frac{\sqrt{3}}{2} + j \cdot \frac{1}{2} \right) + \left(\frac{1}{2} + j \frac{\sqrt{3}}{2} \right) \right\} \\
 &= \operatorname{Re} \left\{ e^{j4} \left(\frac{\sqrt{3}}{2} + \frac{1}{2} \right) (1+j) \right\} \\
 &= \operatorname{Re} \left\{ e^{j4} \left(\frac{\sqrt{3}+1}{2} \right) \sqrt{2} e^{j\pi/4} \right\} \\
 &= \frac{\sqrt{3}+1}{\sqrt{2}} \cos(4+45^\circ)
 \end{aligned}$$

$$\cos(4+30^\circ) \iff 1 \quad | \quad 30^\circ \quad (w=4)$$

$$\cos(4+60^\circ) \iff 1 \quad | \quad 60^\circ \quad (w=4)$$

$$\begin{aligned}
 &+ \frac{1|60^\circ + 1|30^\circ}{2} = \left(\frac{\sqrt{3}}{2} + j \frac{1}{2} \right) + \left(\frac{1}{2} + j \frac{\sqrt{3}}{2} \right) = \frac{\sqrt{3}+1}{2} (1+j) \\
 &= \frac{\sqrt{3}+1}{2} \cos(4+45^\circ) = \frac{\sqrt{3}+1}{\sqrt{2}} \quad | \quad 45^\circ
 \end{aligned}$$

Example: $\sum_{k=0}^N \cos(4t + \frac{\pi}{6}k) = \sum_{k=0}^N \operatorname{Re} \left\{ e^{j(4t + \frac{\pi}{6}k)} \right\}$

$$\begin{aligned}
 &= \operatorname{Re} \left\{ \sum_{k=0}^N e^{j(4t + \frac{\pi}{6}k)} \right\} \\
 &= \operatorname{Re} \left\{ e^{j4t} \sum_{k=0}^N e^{j\frac{\pi}{6}k} \right\}
 \end{aligned}$$

$$\sum_{k=0}^N r^k = \frac{1-r^{N+1}}{1-r}$$

$$\begin{aligned}
 &= \operatorname{Re} \left\{ e^{j4t} \frac{1 - e^{j\pi/6(N+1)}}{1 - e^{j\pi/6}} \right\} \\
 &= \operatorname{Re} \left\{ \frac{e^{j4t} (1 + e^{j\pi/6})}{\|1 - e^{j\pi/6}\|^2} \right\} \cdot (1 - e^{j\pi/6(N+1)})
 \end{aligned}$$

↓
baru similitik kosus


phasor: $\cos(\omega t + \phi) \leftarrow \rightarrow A e^{j(\omega t + \phi)}$

$(A e^{j\phi}) e^{j\omega t}$

phasor $\rightarrow A \angle \phi$
(ω not written but kept a side)

$\rightarrow A \cos(\omega t + \phi_A) + B \sin(\omega t + \phi_B) = ?$

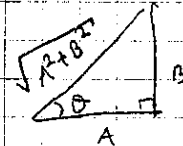$\sqrt{A^2 + B^2} \left(\frac{A}{\sqrt{A^2 + B^2}} \cos(\omega t + \phi) + \frac{B}{\sqrt{A^2 + B^2}} \sin(\omega t + \phi) \right)$



$\sqrt{A^2 + B^2} \left[\cos(\theta) \cos(\omega t + \phi) + \sin(\theta) \sin(\omega t + \phi) \right]$

$\rightarrow \sqrt{A^2 + B^2} \cos[\omega t + \phi - \tan^{-1}(B/A)]$

$\rightarrow A \cos(\omega t + \phi) \rightarrow A \angle \phi$

$B \sin(\omega t + \phi)$

$+ B \cos(\omega t + \phi - 90^\circ) \rightarrow B \angle \phi - 90$

$A \cos(\omega t + \phi) + B \sin(\omega t + \phi) \quad A \angle \phi + B \angle \phi - 90$

$= A e^{j\phi} + B e^{j(\phi - 90^\circ)} = A e^{j\phi} + B e^{j\phi} \cdot e^{-j\pi/2} = -j$


$= A e^{j\phi} - j B e^{j\phi} = e^{j\phi} (A - jB)$

$= e^{j\phi} \sqrt{A^2 + B^2} \angle -\tan^{-1} \frac{B}{A}$

$\leftarrow = \sqrt{A^2 + B^2} \angle \phi - \tan^{-1} B/A$

$\sqrt{A^2 + B^2} \cos(\omega t + \phi - \tan^{-1} \frac{B}{A})$

Example: $\frac{-5 \cos t}{1 \Omega}$

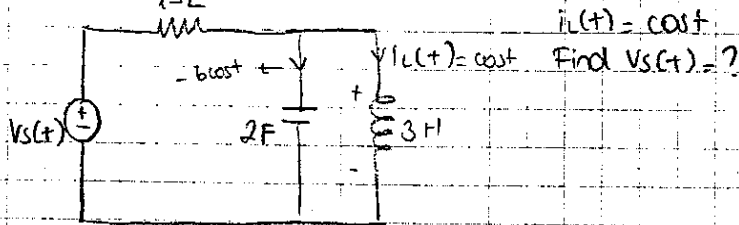


$V_{3H}(t) = L \frac{d}{dt} i_L(t) = -3 \sin(t)$

$i_C(t) = C \frac{dV_C(t)}{dt} = -6 \cos t$

$V_s(t) = -3 \sin t + (-5 \cos t)$

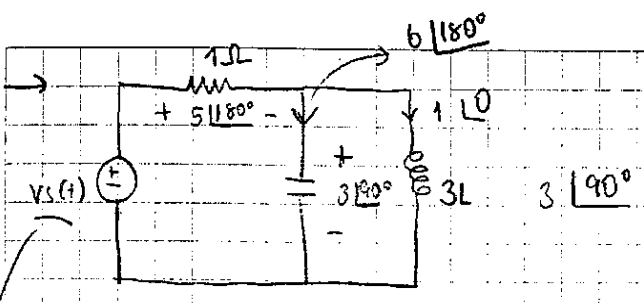$V_s(t) = \sqrt{34} \cos(t - \tan^{-1}(\frac{-3}{-5}))$



$-3\sin t$ phasor $\rightarrow (1 \angle 180^\circ) 3 \angle -90^\circ$

$3\cos(t+90^\circ)$ $\rightarrow 3 \angle 90^\circ$

$V_s(t)$ phasor $\rightarrow 5 \angle 180^\circ + 3 \angle 90^\circ$

$-5+3j = \sqrt{3.4} \angle \tan^{-1}(3/5)+180$

$= -\sqrt{3.4} \angle \tan^{-1}(3/5)$

$V_s(t) = -\sqrt{3.4} \cos(t - \tan^{-1}(3/5))$

Example: $A \cos(\omega t + \phi)$ phasor $\rightarrow A \angle \phi$

d/dt


$-A \omega \sin(\omega t + \phi)$

$A \omega \cos(\omega t + \phi + 90^\circ)$

phasor representation $A \omega \angle \phi + 90^\circ$

How phase is mapped under derivative operation


Example:

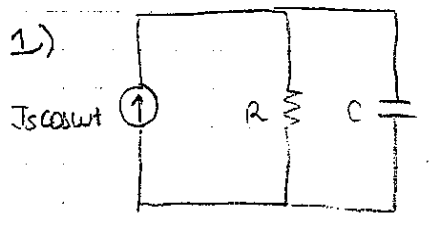

$(D + \frac{1}{RC}) V_c(t) = \frac{I_s \cos \omega t}{C}$

$V_c(0^-) = V_0$



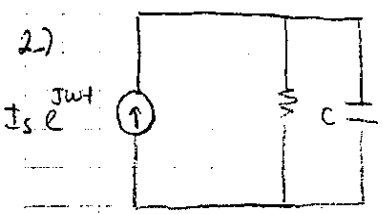
$V_I^{complete}(t) = c_1 e^{+t/RC} + A \cos \omega t + B \sin \omega t$
particular solution





$(D + \frac{1}{RC}) V_c(t) = I_s \frac{e^{j\omega t}}{C}$ $V_c(0^-) = V_0$

$V_I^{complete} = d_1 e^{+t/RC} + D e^{j\omega t}$
are complex numbers

Phasor Circuit Analysis

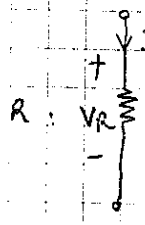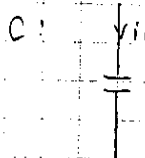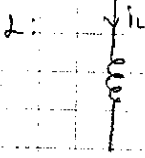
	- Time Domain -	- Phasor -
<p>R: $I_R = I_s \cos(\omega t + \phi)$</p> 	<p>$I_R = I_s \cos(\omega t + \phi)$ $V_R = I_s R \cos(\omega t + \phi)$</p> <p>Current and voltage of R are in phase</p>	<p>$I_R = I_s \angle \phi$ $V_R = R I_s \angle \phi$</p>
<p>C: $i_C(t)$</p> 	<p>$I_C(t) = I_s \cos(\omega t + \phi)$ $V_C(t) = \frac{I_s}{\omega C} \sin(\omega t + \phi)$</p>	<p>$I_C = I_s \angle \phi$ $V_C = \frac{I_s}{\omega C} \angle \phi - 90^\circ$</p>
<p>L: $i_L(t)$</p> 	<p>$I_L(t) = I_s \cos(\omega t + \phi)$ $V_L(t) = \omega L I_s (-\sin(\omega t + \phi))$ $= \omega L I_s \cos(\omega t + \phi + 90^\circ)$</p>	<p>$I_L(t) = I_s \angle \phi$ $V_L(t) = \omega L I_s \angle \phi + 90^\circ$</p>

- Phasor Domain Component -

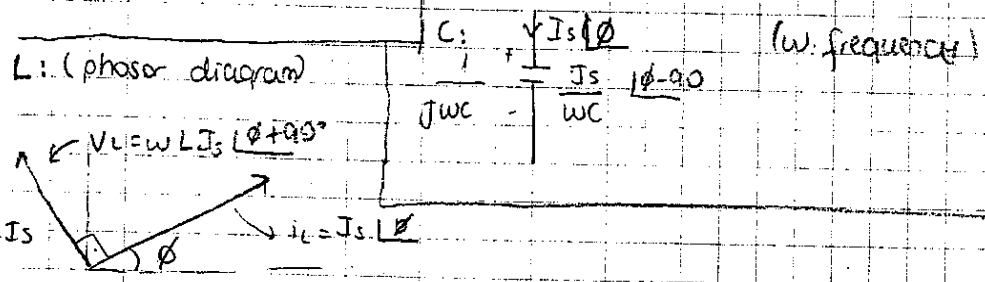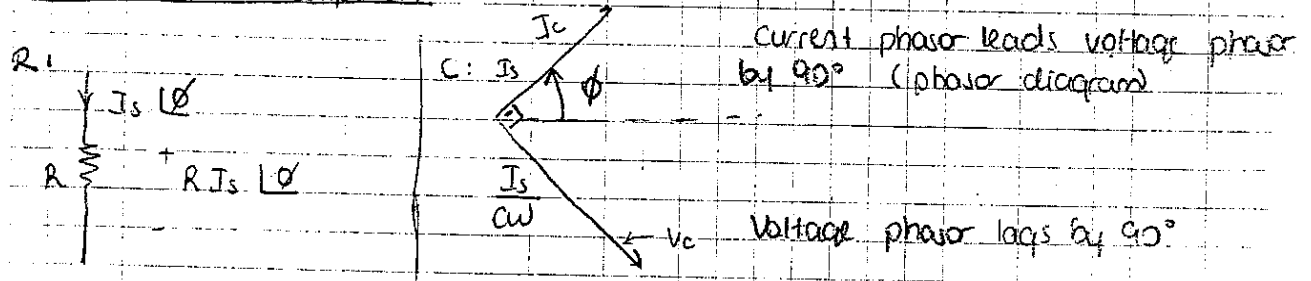

Voltage of inductor leads the current by 90°

Impedance, Admittance

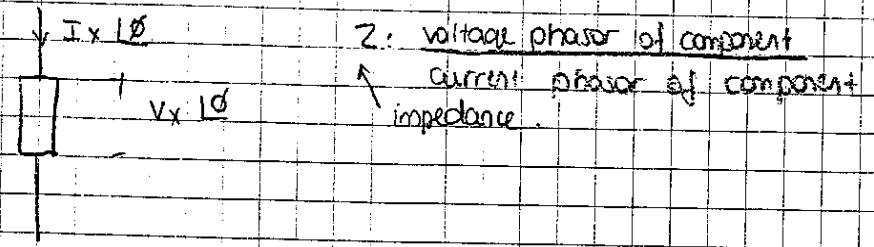

$$Z = \text{Re}\{Z\} + j \text{Im}\{Z\}$$

resistance
impedance


Y: Admittance $Y = \frac{\text{Current phasor}}{\text{Voltage phasor}} = \frac{1}{Z}$

$$= \text{Re}\{Y\} + j \text{Im}\{Y\}$$

conductance
susceptance


Impedance Combinations

1. Series

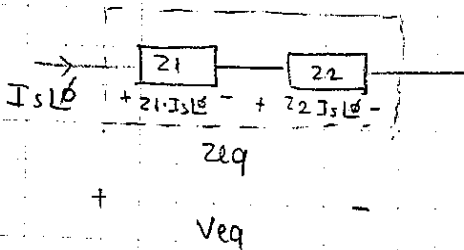

$$Z_{eq} = \frac{V_{eq}}{I_s \angle \phi} = \frac{Z_1 I_s \angle \phi + Z_2 I_s \angle \phi}{I_s \angle \phi} = Z_1 + Z_2$$

2. Parallel

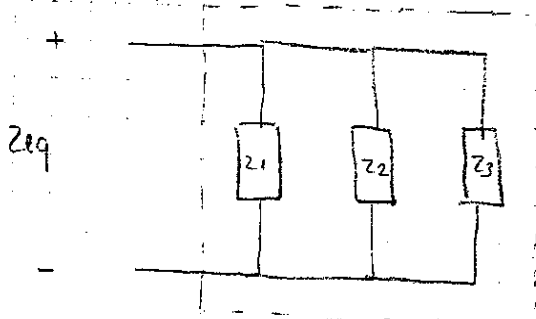

$$Y_{eq} = \sum_{k=1}^3 Z_k$$

$$Z_{eq} = \frac{1}{\sum_{k=1}^3 1/Z_k}$$

Similarly Δ -Y conversion can also be used by impedances by replaces

$$R_Y \rightarrow Z_Y$$


$$R_\Delta \rightarrow Z_\Delta$$

A.C. steady state Calculations


N^{th} order Dynamic Circuit \rightarrow particular solution
 \rightarrow homogeneous solution

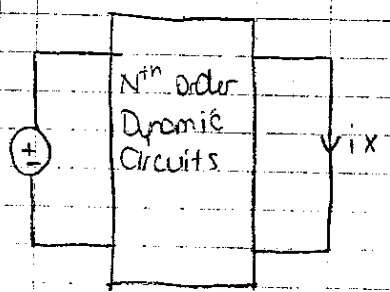zero input \rightarrow natural frequency (mode excitation)
 zero state \rightarrow mode: $C_k e^{s_k t}$
 k^{th} mode of the circuit





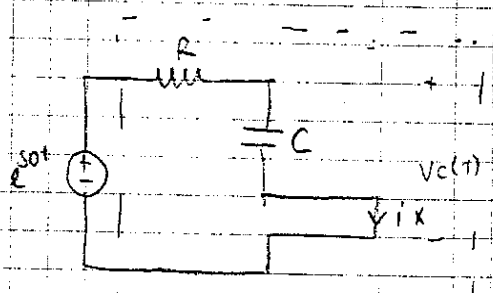$i_x(t) = ?$
 $i_x(t) = i_x^h(t) + i_x^p(t)$
 $i_x^p(t) = ?$



$i_x^p(t) = ?$

Guess: $v_c(t) = A e^{j\omega t}$ phasor

$i_c^p(t) = C \frac{d v_c}{dt} = C (A j\omega e^{j\omega t})$
 $\hookrightarrow C A j\omega$: current phasor

$v_R(t) = R i_c(t)$

$= R A C j\omega e^{j\omega t}$

$\hookrightarrow R A C j\omega$ voltage phasor for $v_R(t)$


$-e^{j\omega t} + v_R(t) + v_c^p(t) = 0$

$-e^{j\omega t} + R A C j\omega e^{j\omega t} + A e^{j\omega t} = 0$


$R A C j\omega + A - 1 = 0$

$A = \frac{1}{R C j\omega + 1} \rightarrow v_c^p(t) = A e^{j\omega t} = \frac{1}{R C j\omega + 1} e^{j\omega t}$

Sinusoidal input:


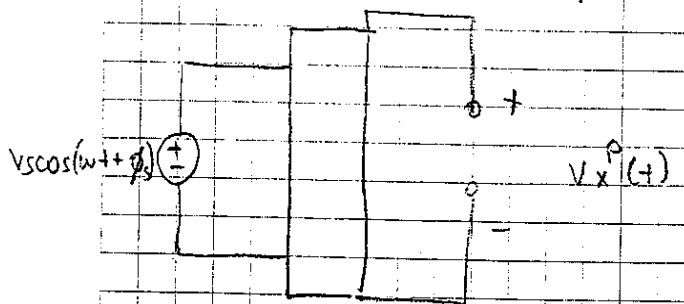


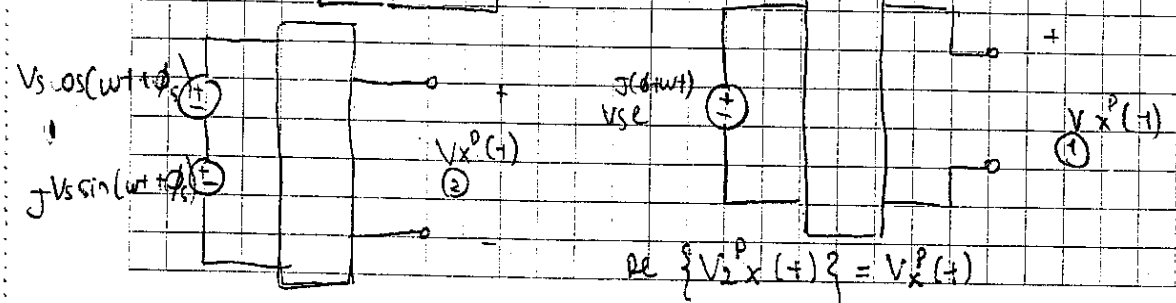Again we are interested in particular solution




$Re \{ V_x^p(t) \} = v_x^p(t)$


Phasor Domain sep. components

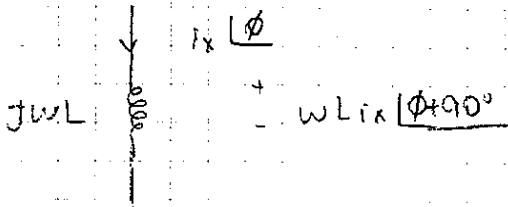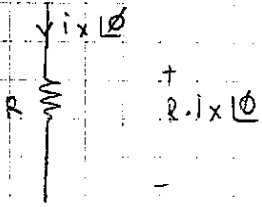

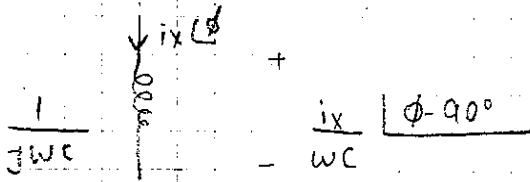→ qu'elle (+) Amplitude qu'on aura calcul.



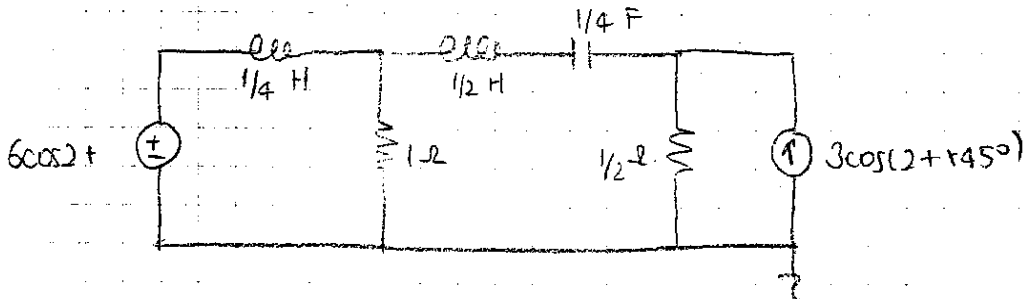
→ Node Analysis Example (we are assuming the circuits are stable)



Find steady state value for node voltages

Phasor Domain:

$\omega = 2$

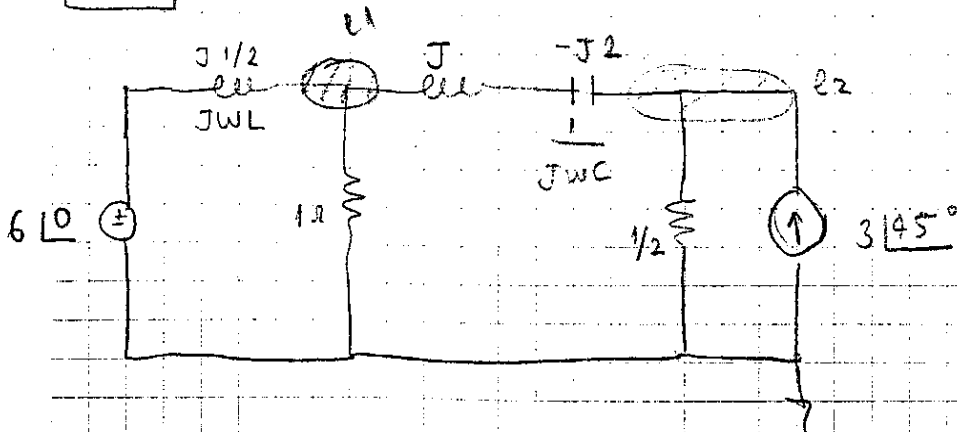

e_1, e_2 : phasor representation of node voltages.

$$\text{KCL @ } e_1: \frac{e_1 - 6}{j/2} + \frac{e_1}{1} - \frac{e_1 - e_2}{-j} = 0;$$


$$\text{KCL @ } e_2: \frac{e_2}{1/2} - 3 \angle 45^\circ + \frac{e_2 - e_1}{j} = 0$$

$$\begin{bmatrix} -j+1 & -j \\ -j & 2+j \end{bmatrix} \begin{bmatrix} e_1 \\ e_2 \end{bmatrix} = \begin{bmatrix} -12T \\ 3 \angle 45^\circ \end{bmatrix}$$


(Dependent source ohms so reciprocal circuit)

$$\begin{bmatrix} e_1 \\ e_2 \end{bmatrix} = \frac{1}{4-j} \begin{bmatrix} 2+j & j \\ j & -j+1 \end{bmatrix} \begin{bmatrix} -12T \\ 3 \angle 45^\circ \end{bmatrix} = \begin{bmatrix} ? \\ 3.63 \angle 14^\circ \end{bmatrix}$$

$\sqrt{2} \angle 45^\circ$

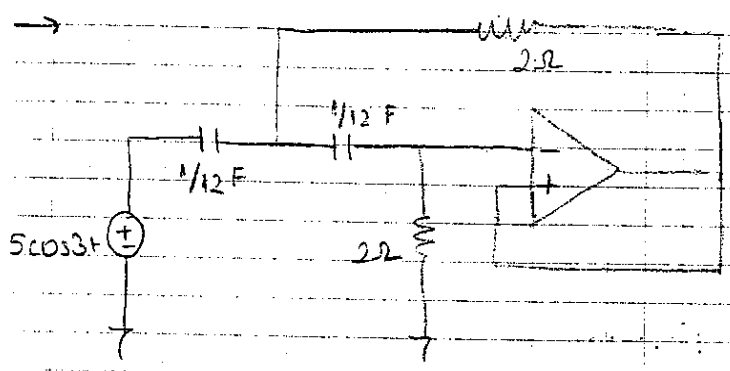

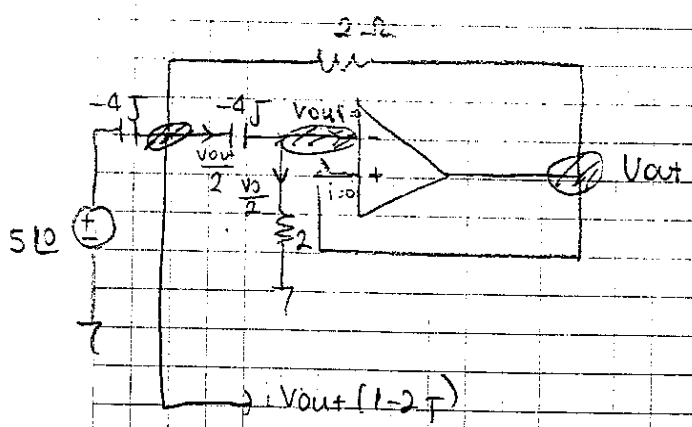Assume opamp is in linear region, find $V_{out}(t)$ steady state






$$\frac{12T}{2} = \cos(3t + 12.7^\circ)$$

$$\text{KCL @ } V_{out}(1-2T): \frac{V_{out}(1-2T) - 5}{-4T} + \frac{V_{out}}{2} + \frac{V_{out}(1-2T) - V_{out}}{2} = 0$$

$$V_{out} \left(\frac{1-2T}{-2T} + 1 - 2T \right) = \frac{5}{2}T \quad V_{out} = \frac{5/2T}{2 - \frac{3T}{2}} = \frac{5T}{5 \angle -37^\circ}$$

Mesh analysis

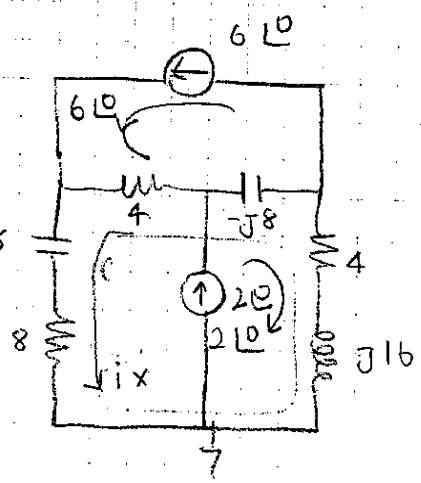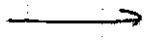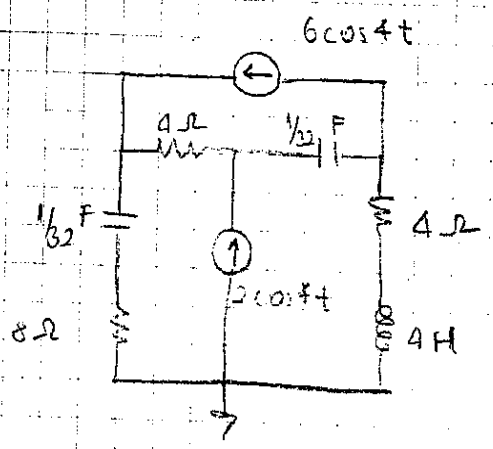

$\omega = 4$

KVL across 1 loop;


$$j32 - j32 = 2(1-j) = 2\sqrt{2} \angle -45^\circ = i_x$$

$$i_L = 2\angle 0 - i_x = 2 - 2 + 2\angle 7 = 2\angle 7$$


$i_L = 2 \angle 90^\circ$

$i_L(t) = 2 \cos(\omega t + 90^\circ)$

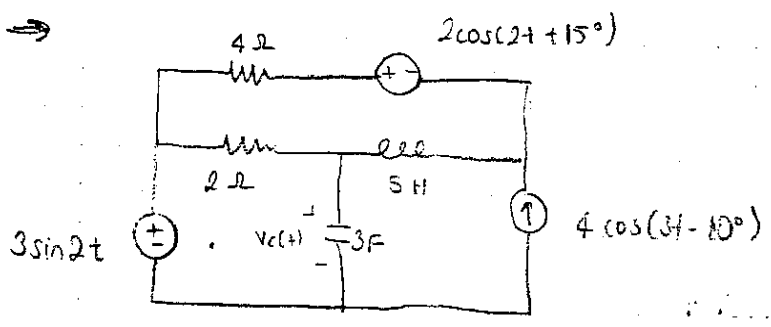Sources with different frequencies (use superposition)




$V_C^{(A)}(t) =$

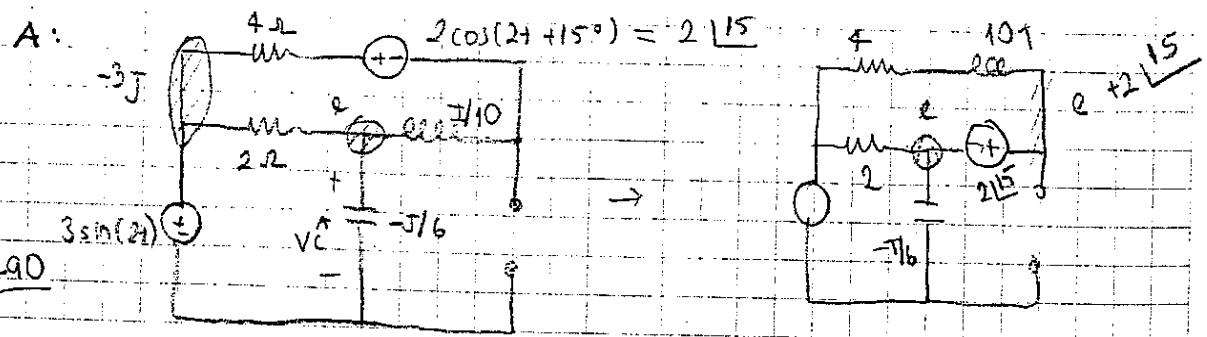


$$\frac{e - (-3T)}{2} + \frac{e}{-T/6} + \frac{(e + 2 \angle 15^\circ) - (-3T)}{4 + j\sqrt{10}} = 0 \quad e = V_{3F} \angle 0^\circ \quad (35)$$

Ass $V_{3F}(t) = V_{3F} \cos(2t + 0^\circ)$

B:

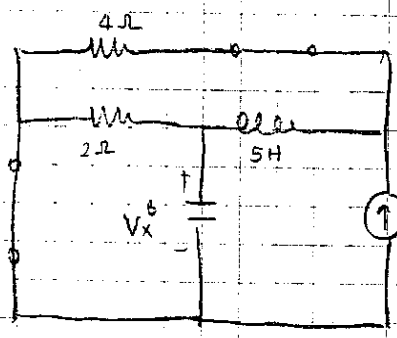

$4 \cos(3t - 10)$ phasor

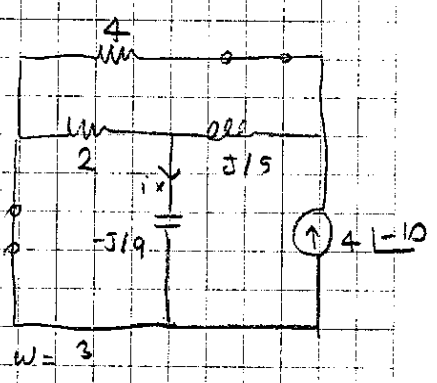


$$I_x = 4 \angle -10 \cdot \frac{4}{4 + (2 \parallel -j/9 + j15)} \cdot \frac{2}{2 \parallel (-j/9)}$$


$$V_x = I_x \left(-\frac{j}{9}\right) = V_{3F} \angle 0^\circ$$

$$V_{3p} = V_{3p} \cos(3t + 0^\circ) \text{ V}$$

$$V_{3t} = V_{3F}(t) + V_{3F}(t)$$

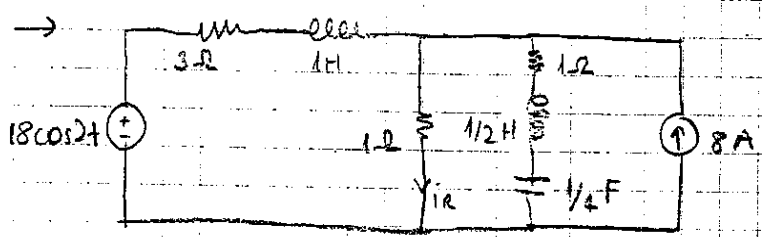

$$i_{IR}(t) = ?$$

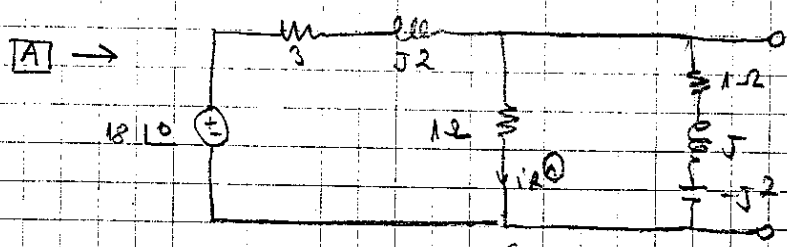


$$I_{IR} = \frac{18}{3 + j2} \cdot \frac{1/1}{1/1 + 1/3 + j2 + 1/(-j2)} = 2(1 - j)$$

\swarrow G_B \swarrow G_A \swarrow G_C

Check

$$= 2(1-j) = 2\sqrt{2} \angle -45^\circ$$
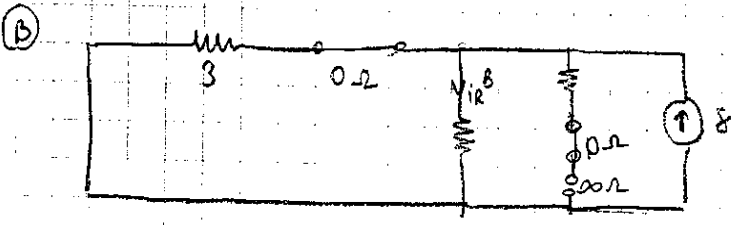
$$i_R^{ss}(t) = 2\sqrt{2} \cos(2t - 45^\circ)$$




$\omega = 0$
 $L \rightarrow j\omega L$ $C \rightarrow \frac{-j}{\omega C}$

$$i_R^{(B)} = 8 \cdot \frac{1}{1 + 1/3} = 6 \quad i_R^{ss}(t) = 6 \angle 0$$

$$i_R^{ss}(t) = i_R^{(B)} + i_R^{(A)ss}(t)$$


$$i_R(t) = 2\sqrt{2} \cos(2t - 45^\circ) + 6A$$

Thevenin - Norton Equivalents

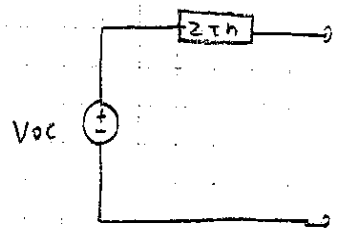


V_{oc} : phasor - open circuit voltage
 Z_{Th} : Thevenin impedance
 ↳ Their circulation is exactly the same calculation for DC circuits.

Coupled Inductors

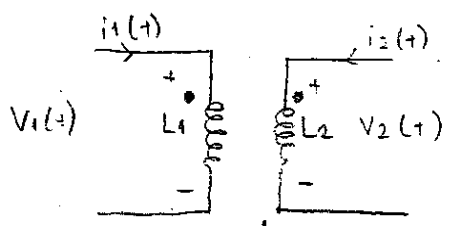

$$\begin{bmatrix} V_1(t) \\ V_2(t) \end{bmatrix} = \begin{bmatrix} L_1 & M \\ M & L_2 \end{bmatrix} \begin{bmatrix} d/dt i_1(t) \\ d/dt i_2(t) \end{bmatrix}$$


phasor

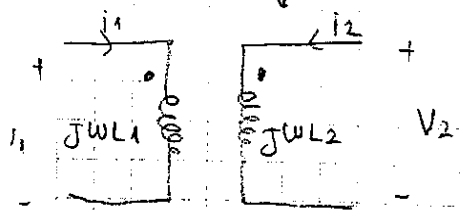

$$\begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} j\omega L_1 & j\omega M \\ j\omega M & j\omega L_2 \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \end{bmatrix}$$

phasor

Transformers

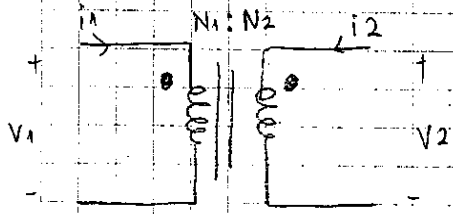


$$V_2/V_1 = N_2/N_1$$


$$i_1/i_2 = -N_2/N_1$$

The domain representation is equal phasor domain rep.

→ PPT II pr. 5

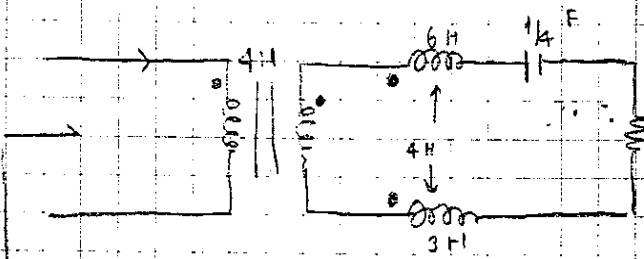

Find the input impedance

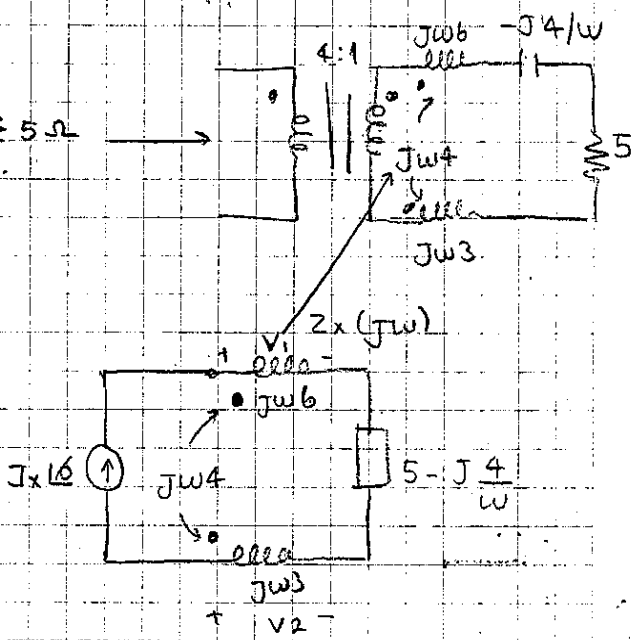

$$Z_x(j\omega) = \frac{V_1}{I_x} = \frac{V_1 + I_x(5 - j4/w) - V_2}{I_x}$$


$$\begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} jw6 & jw4 \\ jw4 & jw3 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix}$$

$I_1 \rightarrow I_x$
 $I_2 \rightarrow -I_x$

then; $V_1 - V_2 = [jw2 \quad jw1] \begin{bmatrix} I_x \\ -I_x \end{bmatrix} = (j\omega) I_x$

$$I_x(j\omega + 5 - 4j/w)$$

$$= 5 + j(\omega - \frac{4}{\omega})$$

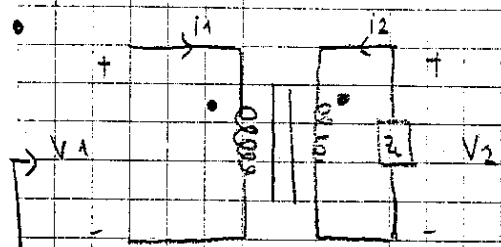

$$\left. \begin{aligned} \frac{V_1}{V_2} &= \frac{N_1}{N_2} \\ \frac{i_1}{i_2} &= -\frac{N_2}{N_1} \end{aligned} \right\} \text{transformer}$$

Load; $V_2 = Z_L(-i_2)$

$$\frac{V_1 N_2}{N_1} = -i_1 \frac{N_1}{N_2}$$

$$Z_{eq} = \left(\frac{N_1}{N_2}\right)^2 Z_L$$

$$\frac{V_1}{i_1} = Z_L \left(\frac{N_1}{N_2}\right)^2$$


derive itlik

$$Z_{j\omega} = \left(\frac{4}{1}\right)^2 Z_x(j\omega) = 16(5 + j(\omega - \frac{4}{\omega}))$$


Assume $\omega = 2 \rightarrow Z(j2) = 80$

$\omega = 3 \rightarrow Z(j3) = 80 + \frac{80}{3} j$

$\omega = 1 \rightarrow Z(j) = 80 - 48j$

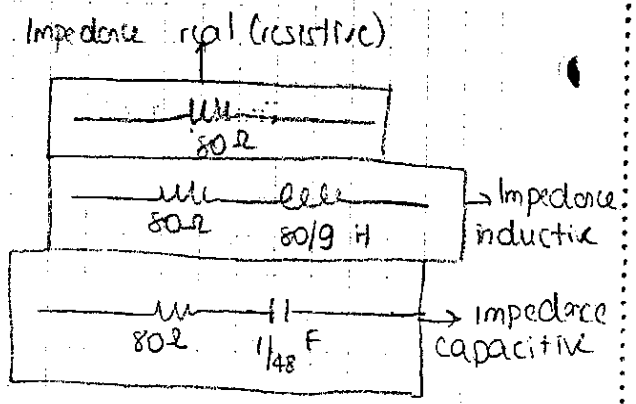


Phasor Diagram ZPS-II problem 4

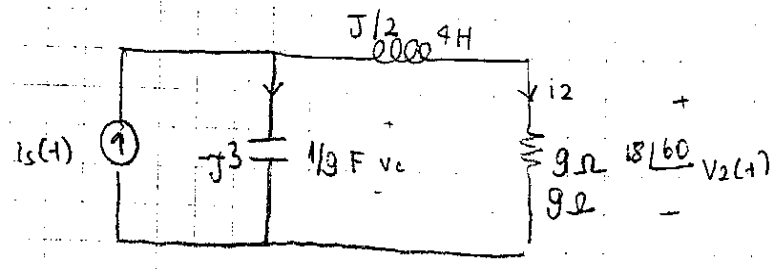


Find $i_s = ?$

$v_2(t) = 18 \cos(3t + 60^\circ)$

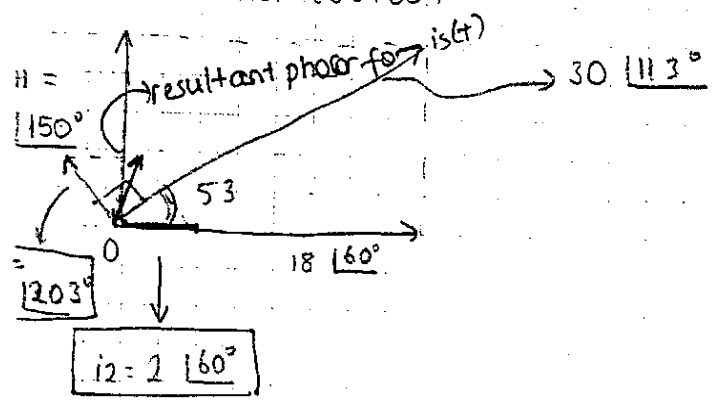

ZPS I: 12-d.)

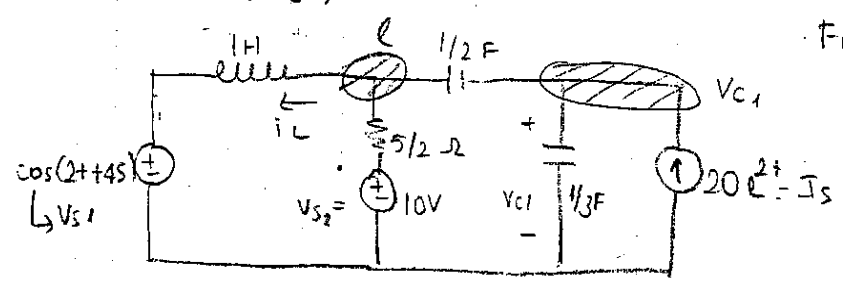

Find homogeneous, particular soln.

KCL v_c : $\frac{1}{3} Dv_c + \frac{1}{2} D(v_c - e) - i_s = 0$

KCL e : $\frac{1}{2} D(e - v_c) + (e - v_s) \cdot \frac{2}{5} + i_L(0^-) + \int_0^t (e(z) - v_s(z)) dz = 0 \quad \times 10$

$$\begin{bmatrix} 5D & -3D \\ -5D & 5D + 10 \end{bmatrix} \begin{bmatrix} v_c \\ e \end{bmatrix} = \begin{bmatrix} 6i_s \\ -10 i_L(0^-) + 4v_{s2}(t) + 10 \int v_{s1}(t) \end{bmatrix}$$

Take derivative of 2nd row

(39)

$$\begin{bmatrix} 5D & -3D \\ -5D^2 & 5D^2+4D+10 \end{bmatrix} \begin{bmatrix} V_c \\ i \end{bmatrix} = \begin{bmatrix} 6I_s \\ 4DVs_2(t) + 10Vs_1(t) \end{bmatrix}$$

zero input; RHS $\rightarrow \begin{bmatrix} 0 \\ 0 \end{bmatrix}$

$$\begin{bmatrix} V_c(t) \\ i(t) \end{bmatrix} = \begin{bmatrix} \alpha \\ \beta \end{bmatrix} e^{\lambda t} \rightarrow \begin{bmatrix} 5\lambda & -3\lambda \\ -5\lambda^2 & 10+4\lambda+5\lambda^2 \end{bmatrix} \begin{bmatrix} \alpha \\ \beta \end{bmatrix} e^{\lambda t} = \begin{bmatrix} 0 \\ 0 \end{bmatrix}$$

$$5\lambda(5\lambda^2+4\lambda+10) - 15\lambda^3 = 0 \quad \lambda = 0$$

$$5\lambda^2+4\lambda+10 - 3\lambda^2 = 2\lambda^2+4\lambda+10 \xrightarrow{1/2} \lambda^2+2\lambda+5 = 0$$

$$\frac{-b \pm \sqrt{b^2-4ac}}{2} = \frac{-2 \pm \sqrt{4-4 \cdot 1 \cdot 5}}{2} = \frac{-2 \pm 2i}{2} = -1 \pm i$$

Turn back state:

- (state variable sayisi = natural frequency sayisi) 0 zaman $\lambda=0$ 'da natural frequency vardır. (Emin olabilirsiniz buradan)

- $V_c^h(t) = c + a_1 e^t \cos 2t + a_2 e^t \sin 2t$ (only stable)

- $\begin{bmatrix} 5D & -3D \\ -5D^2 & 5D^2+4D+10 \end{bmatrix} \begin{bmatrix} V_c \\ i \end{bmatrix} = \begin{bmatrix} A_1 \\ A_2 \end{bmatrix} e^{s_0 t} \quad \left| \begin{array}{l} s_0 = 0 \\ s_0 = -1 \pm i \\ s_0 = 2 \end{array} \right.$

$$\begin{bmatrix} 5D & -3D \\ -5D^2 & 5D^2+4D+10 \end{bmatrix} \begin{bmatrix} V_c^p(t) \\ i(t) \end{bmatrix} = \begin{bmatrix} 120e^{2t} \\ 0 \end{bmatrix} \text{ by superposition (only } I_s \neq 0)$$

$$\begin{bmatrix} V_c^p \\ i^p \end{bmatrix} = \begin{bmatrix} A \\ B \end{bmatrix} e^{2t}; \quad \begin{array}{l} 10Ae^{2t} - 6Be^{2t} = 120e^{2t} \\ -20Ae^{2t} + 38Be^{2t} = 0 \end{array} \quad \begin{array}{l} 5A - 3B = 60 \\ 13B = 60 \\ B = \frac{60}{13} \end{array}$$

$$19B = 10A \quad 5A = 19B$$

$$B = \frac{120}{13} \quad A = \frac{456}{26}$$

- $V_c^{p(2)} = ?$ due to $10 \cos(2t+45) = 10 \operatorname{Re} \left\{ \sqrt{2} e^{j45} \cdot e^{j2t} \right\}$

$$A = \frac{228}{13}$$

$$\begin{bmatrix} 5D & -3D \\ -5D^2 & 5D^2+4D+10 \end{bmatrix} \begin{bmatrix} V_c \\ i \end{bmatrix} = \begin{bmatrix} 10 \\ 100 \frac{145}{\sqrt{2}} e^{j2t} \end{bmatrix} \text{ phasor representation}$$


$$\begin{bmatrix} V_c^{p(2)} \\ i^{p(2)} \end{bmatrix} = \begin{bmatrix} A^{(2)} \\ B^{(2)} \end{bmatrix} e^{j2t}$$

$$\begin{bmatrix} 5T^2 & -3T^2 \\ 5 \cdot 4 & -5 \cdot 4 + j8 + 10 \end{bmatrix} \begin{bmatrix} A^{(2)} \\ B^{(2)} \end{bmatrix} = \begin{bmatrix} 0 \\ 400/45 \end{bmatrix} \quad V_C^p(t) = \text{Re} \{ A^{(2)} e^{j2t} \} \quad (40)$$

$$= \text{Re} \{ \sqrt{10} \cos(t/3) \} \quad (j2t)$$

$$= \sqrt{10} \cos(2t + \cos^{-1}(1/3))$$

Existence of Steady State Solution

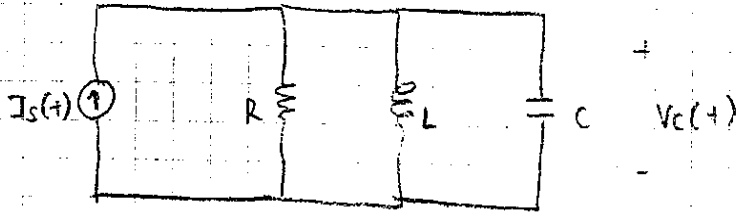

$$\left(D^2 + \frac{1}{RC} D + \frac{1}{LC} \right) V_C(t) = \frac{1}{C} \frac{d}{dt} I_S(t)$$

$$(D^2 + 2\zeta D + \omega_0^2)$$

↳ resonance frequency
↳ damping factor

Let's say we want to DE for $I_L(t)$

$$V_C(t) = L \frac{d}{dt} I_L(t) = LD I_L(t)$$

$$\left(D^2 + \frac{1}{RC} D + \frac{1}{LC} \right) LD I_L(t) = \frac{1}{C} D I_S(t) \quad \text{divide by } L$$

$$\left(D^2 + \frac{1}{RC} D + \frac{1}{LC} \right) I_L(t) = \frac{1}{LC} I_S(t)$$

$$D \cdot D' = I \rightarrow \frac{d}{dt} \left(\int_0^t f(z) dz \right) = f(t) \quad \text{Leibniz's Rule}$$

identity op.

Let set $C=1, L=1/2, R=1/3$

$$(D^2 + 3D + 2) I_L(t) = 2I_S(t)$$

Find the particular soln for;

$$a) I_S(t) = I_0 e^{-5t}$$

$$\xrightarrow{\text{make a guess}} I_L^p(t) = A e^{-5t}$$

$$I_L^p(t) = A e^{s_0 t}$$

$$s_0 = -5$$

substitute
guess
into D.E

$$A = \frac{2I_s}{s_0^2 + 3s_0 + 2} \quad | \quad s_0 = -5$$

$$I_L^p(t) = 1/6 I_s e^{-5t}$$

(41)

b. $I_s(t) = I_{s0} e^{-4t}$ → make guess

$$I_L^p(t) = A e^{s_0 t} \quad | \quad s_0 = -4$$

$$A = \frac{2I_{s0}}{s^2 + 3s + 2} \quad | \quad s_0 = -4 = \frac{1}{4} I_{s0}$$

$$I_L^p(t) = \frac{1}{4} I_{s0} e^{-4t}$$

c. $I_s(t) = I_{s0} e^{-j t}$

$$A = \frac{2I_{s0}}{s_0^2 + 3s_0 + 2} \quad | \quad s_0 = -j$$

$$I_L^p(t) = \frac{2}{1-3j} I_{s0} e^{-j t} \quad \leftarrow \quad \frac{2}{1-3j} I_{s0}$$

A

d. $I_s(t) = I_{s0} e^{-t}$

$$I_L^p(t) = A e^{s_0 t} \quad | \quad s_0 = -1$$

$$A = \frac{2I_{s0}}{s_0^2 + 3s_0 + 2} \quad | \quad s_0 = -1 = \frac{2I_{s0}}{0}$$

Wrong guess


$$I_L^p(t) = A t e^{-t} \quad \leftarrow \text{correct guess}$$

$$(D^2 + 3D + 2) I_L(t) = 2I_{s0} e^{-t}$$

$I_L^p(t) = A t e^{-t}$ → since nat frequencies are $\{-1, -2\}$ and input excites natural frequency.

d. $R \rightarrow \infty \quad G = \frac{1}{R} = 0$

(ohmic losses are zero)

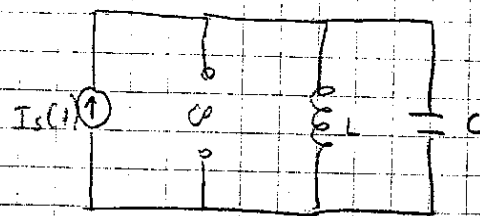

$$(D^2 + 4) I_L(t) = 4 i_s(t)$$

→ Nat. frequen = $\{+2j, -2j\}$

ii) $I_s(t) = I_{s0} \cos t \rightarrow I_L^p(t) = R$

$$= \text{Re} \{ I_{s0} e^{j t} \}$$

$$\rightarrow I_L^p(t) = \text{Re} \{ A e^{j t} \}$$

$$\rightarrow A = \frac{4I_{s0}}{s_0^2 + 4} \quad | \quad s_0 = -j$$

$$= \frac{4}{3} I_{s0}$$

i) $I_s(t) = I_{s0} e^{t} \rightarrow I_L^p(t) = A e^{t} \rightarrow A = \frac{4I_{s0}}{s^2 + 4} \Big|_{s=1} = \frac{4}{5} I_{s0}$

iii) $I_s(t) = I_{s0} \cos(2t) = \text{Re} \{ I_{s0} e^{j2t} \} \xrightarrow{\text{guess}} I_L^p(t) = \text{Re} \{ A e^{j2t} \}$

$(0^2 + 4)I_L(t) = 4I_{s0} \cos 2t$ ← wrong guess $A = \frac{4I_{s0}}{s^2 + 4} \Big|_{s=j2} = \frac{4I_{s0}}{0}$

$I_L(t) = A \cos 2t + B \sin 2t$ } Correct guess!
 $= t D \cos(2t + E)$


• Input excites the natural frequency of $\pm 2j$

$\lambda = \{ 2j, -2j \}$ and $I_s(t) = I_{s0} \cos 2t$


$= I_{s0} \frac{e^{j2t} + e^{-j2t}}{2}$

↓
 natural frequencies.

In phasor domain:

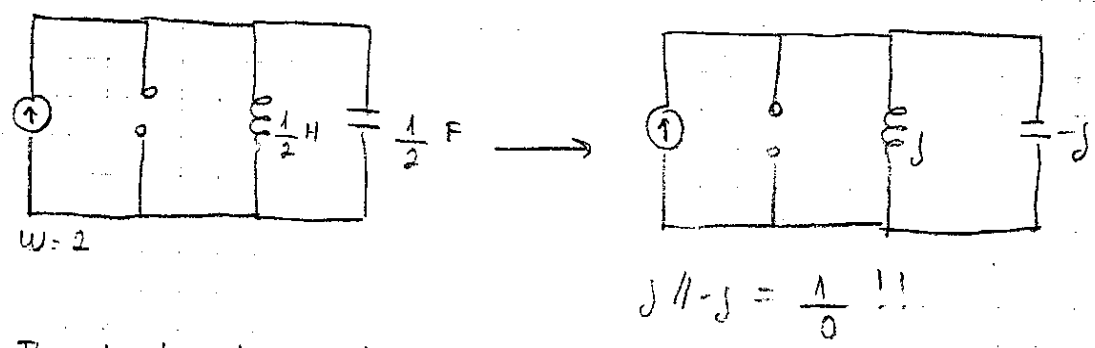

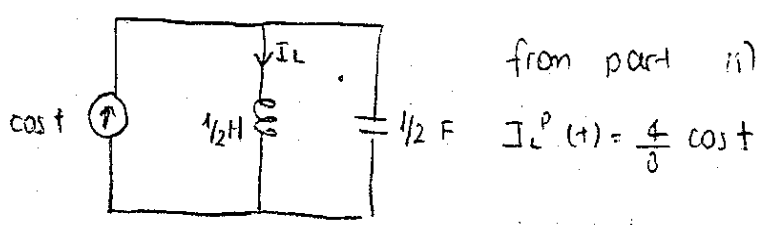• The steady state solution is the part complete solution due to input.




$I_L(0^+) = I_0$
 $I_L'(0^+) = 0$ } $I_L^n(t) = A \cos 2t + B \sin 2t$

$I_L^{comp}(t) = A \cos 2t + B \sin 2t + \frac{4}{3} \cos t$

$I_L^{comp}(t) = (I_0 - \frac{4}{3}) \cos 2t + \frac{4}{3} \cos t$ A (B=0 because t derivative)

steady state soln

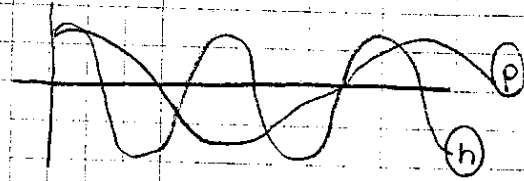

RMS (Effective Values)


md-1

$x(t)$: Periodic signal

$x(t) = x(t+T)$ for $T \neq 0$

$= x(t-kT)$ k is an integer

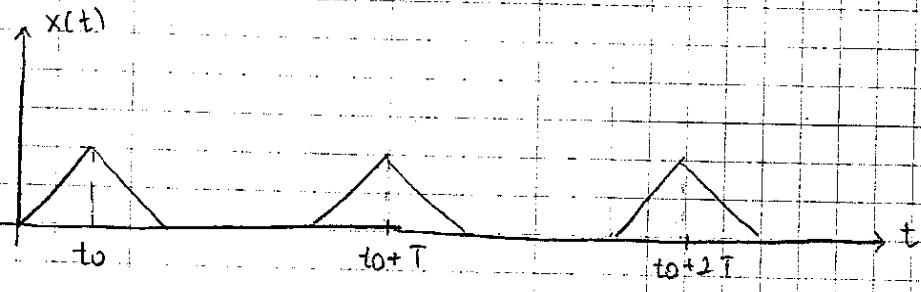T : fundamental period of the waveform $x(t)$



$$RMS = \sqrt{\frac{1}{T} \int_{t_0}^{t_0+T} [x(t')]^2 dt'}$$

integration over a full period

$$= \sqrt{\frac{1}{T} \int_0^T [x(t')]^2 dt'}$$
 in Volts

Root Mean Square


$\rightarrow x(t) = A \cos \omega t \rightarrow RMS = \sqrt{\frac{1}{T} \int_0^T A^2 \cos^2 \omega t dt} = \sqrt{\frac{A^2}{T} \int_0^T \frac{1 + \cos 2\omega t}{2} dt}$

$$= \sqrt{\frac{A^2}{T} \left\{ \int_0^T \frac{1}{2} dt + \int_0^T \frac{\cos 2\omega t}{2} dt \right\}}$$


$$\frac{A}{\sqrt{2}}$$

frequency 2ω
integration of $\cos x$ over "2" full period

→ $x(t)$: Triangular waveform

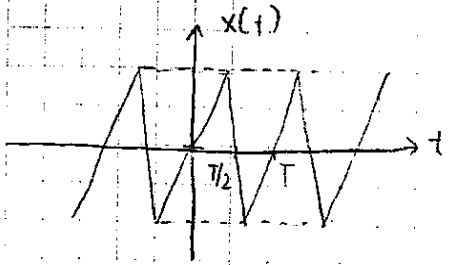


$$\begin{aligned}
 \text{RMS} &= \sqrt{\frac{1}{T} \int_0^T (x(t))^2 dt} \\
 &= \sqrt{\frac{1}{T} \int_{-T/2}^{T/2} (x(t))^2 dt} \\
 &= \sqrt{\frac{1}{T} \int_{-T/2}^{T/2} \left(\frac{2A}{T} t\right)^2 dt} \\
 &= \sqrt{\frac{4A^2}{T^3} \left. \frac{t^3}{3} \right|_{-T/2}^{T/2}} = \frac{A}{\sqrt{3}}
 \end{aligned}$$

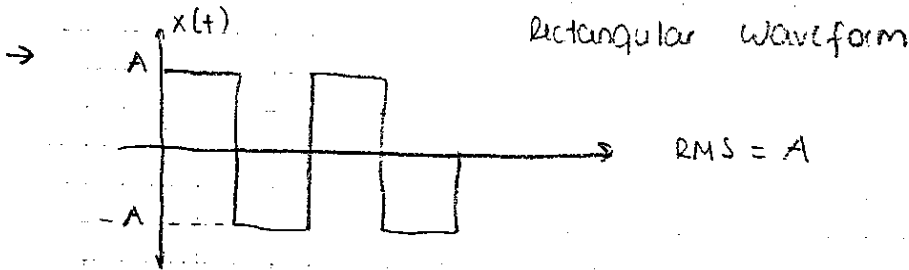

RMS = A

• why we are introducing RMS?

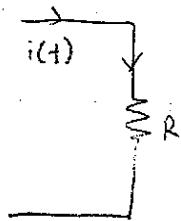

$i(t)$: periodic current waveform

Energy absorbed by $R \Rightarrow E = \int_{[0,T]} P_R(\tau) d\tau$ in $[0,T]$

$$= \int_0^T R \cdot [i(t)]^2 dt = R \int_0^T [i(t)]^2 dt = T \left(\frac{1}{T} \int_0^T [i(t)]^2 dt \right) R$$

$$= T \cdot (i_{\text{RMS}})^2 R$$

↑ ↑
RMS value of
period

Average power: (over R resistor)

① Assume $i(t)$ is periodic with T

$$P_{\text{av}} = \frac{1}{T} \int_0^T p(t) dt = \frac{1}{T} \int_0^T [i(t)]^2 R dt = \underbrace{(i_{\text{RMS}})^2}_{\text{scalar}} \cdot R$$

$p(t)$ instantaneous power $[p(t) = v(t) \cdot i(t)]$

(45)

$P_{av} = (i_{rms})^2 \cdot R$

2. If $x(t)$ is almost (not exactly) periodic ($x(t) = \cos(2\pi t) + \cos(t)$)


(okullerde periodic olarak sordere)

T = 1
2
3

T = 2π
4π
6π

- quasi periodic -

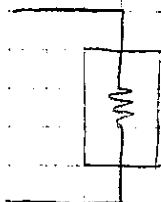$i_{rms}^2 = \lim_{T \rightarrow \infty} \frac{1}{T} \int_0^T [i(t)]^2 dt$; $P_{av} = i_{rms}^2 \cdot R$



$P_{av} = 5 \text{ Watts}$


Energy absorbed in 10 periods = $\int_0^{10T} p(t') dt'$

= $T \left(\frac{1}{T} \int_0^{10T} p(t') dt' \right)$

= $T \left(\frac{10}{T} \int_0^T p(t') dt' \right)$

= $10 P_{av} = 50 \text{ Joule}$

Average and Instantaneous Power

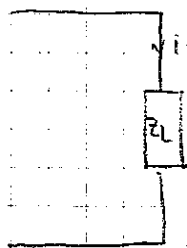

$v(t) = V_m \cos(\omega t + \theta_v)$
 $i(t) = I_m \cos(\omega t + \theta_i)$
 $\rightarrow V = V_m \angle \theta_v$
 $i = I_m \angle \theta_i$

$Z_L = \frac{V_m \angle \theta_v}{I_m \angle \theta_i}$

$p(t) = v(t) \cdot i(t) = V_m I_m \cos(\omega t + \theta_v) \cos(\omega t + \theta_i)$

= $V_m I_m \frac{\cos(\theta_v - \theta_i) + \cos(2\omega t + \theta_v + \theta_i)}{2}$

(cos A cos B acilmini kullaniladi)

$\theta_v = \theta_i + \theta_{Z_L}$

$Z_L = \frac{V_m \angle \theta_v}{I_m \angle \theta_i} = |Z_L| \angle \theta_{Z_L}$

= $\frac{V_m I_m}{2} \cos(\theta_{Z_L}) + \frac{V_m I_m}{2} \cos(2\omega t + \theta_{Z_L} + 2\theta_i)$
 $\frac{V_m I_m}{2} \cos(2\omega t + 2\theta_i) \cos(\theta_{Z_L}) - \frac{V_m I_m}{2} \sin(2\omega t + 2\theta_i) \sin(\theta_{Z_L})$

• AC de dicitur \sin θ \sin θ .

$$= \frac{V_m I_m}{2} \cos \theta_{ZL} (1 + \cos(2\omega t + 2\theta_i)) - \frac{V_m I_m}{2} \sin \theta_{ZL} \sin(2\omega t + 2\theta_i)$$

real numbers

$$P_{AV} = \frac{V_m I_m}{2} \cos(\theta_{ZL}) = \frac{V_{RMS} \sqrt{2} (I_{RMS} \sqrt{2})}{2} \cos(\theta_{ZL}) = V_{RMS} I_{RMS} \cos(\theta_{ZL})$$

WATTS

$$Z_L = |Z_L| \angle \theta_{ZL}$$


Average power consumed by load.

• Remember: For AC $\rightarrow V_{RMS} = \frac{V_m}{\sqrt{2}}$

• $Q_m = \frac{V_m I_m}{2} \sin(\theta_{ZL}) = V_{RMS} I_{RMS} \sin(\theta_{ZL})$ VAR (VOLT-AMPERE REACTIVE)

$$p(t) = P_{AV} (1 + \cos(2\omega t + 2\theta_i)) - Q \sin(2\omega t + 2\theta_i)$$
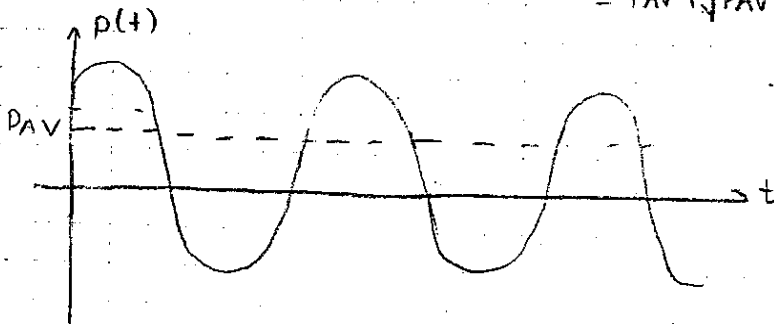
$$= P_{AV} + \sqrt{P_{AV}^2 + Q^2} \cos(2\omega t + 2\theta_i + \tan^{-1} \frac{Q}{P})$$



$$E_{abs} = \int_{t_0}^{t_0+T} p(t) dt$$

$$X = kT + r(x)$$

$$\approx X \cdot P_{AV}$$

$$T = 2 \text{ sec}$$


$$X = 5.1 \text{ sec}; \quad \bullet 5.1 \text{ sec} = 2T + 1.1 \text{ sec}$$

floor op.

$$\left\lfloor \frac{X}{T} \right\rfloor P_{AV} < E_{abs} < \left\lceil \frac{X}{T} \right\rceil P_{AV}$$


Antadm!
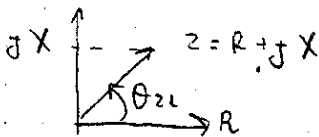
$$P_{AV} = V_{RMS} I_{RMS} \cos(\theta_{ZL})$$



Special Cases

① Resistor

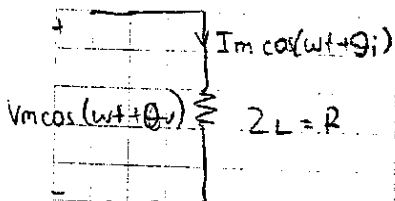


$$p(t) = \sqrt{P_{AV}^2 + Q^2} \cos(2\omega t + 2\theta_i + \tan^{-1} \frac{Q}{P})$$


$$P_{AV} = V_{RMS} I_{RMS} \cos(\theta_{ZL}) = V_{RMS} I_{RMS} = I_{RMS}^2 \frac{R}{Z_L} = I_{RMS}^2 R$$

$$Q = V_{RMS} I_{RMS} \sin(\theta_{ZL}) = 0$$

$$\theta_{ZL} = 0$$

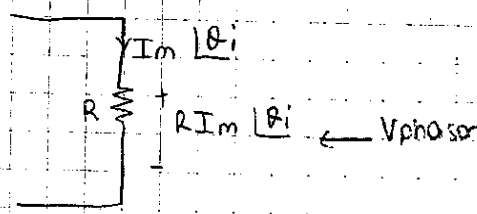


$$V_{RMS} = R I_{RMS}$$

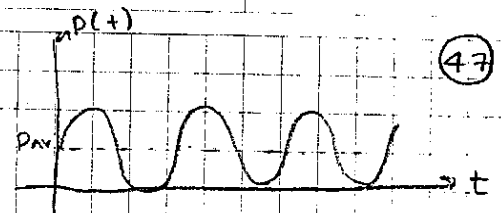

(47)

Special Case 2:

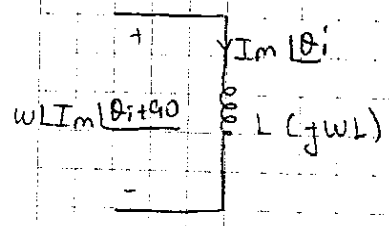


$$Z_L = j w L = w L | 90^\circ$$

$$P_{AV} = V_{RMS} I_{RMS} \cos(\theta_{ZL}) = 0 \text{ Watts}$$

$$Q = V_{RMS} I_{RMS} \sin(\theta_{ZL}) = V_{RMS} I_{RMS} \text{ VAR}$$
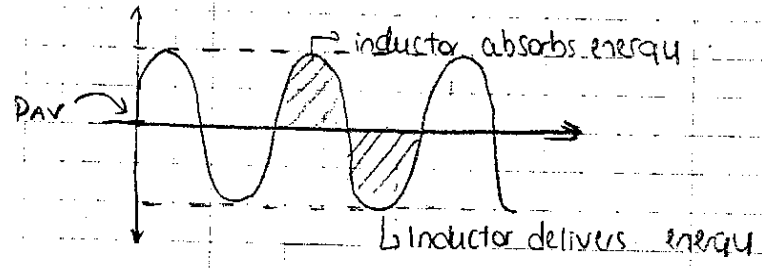
$$p(t) = Q \cos(2w t + 2\theta_i + 90^\circ)$$



Special Case 3:



$$Z_C = \frac{1}{j w C}$$

$$\theta_{ZL} = -90^\circ$$

$$P_{AV} = 0 \text{ W}$$


$$Q = -V_{RMS} I_{RMS} \text{ VAR}$$

Note: L \rightarrow P=0, Q > 0

C \rightarrow P=0, Q < 0


Meaning of Q
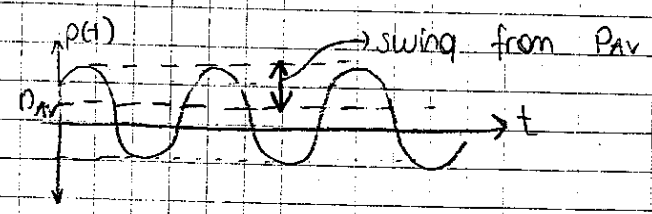
$$p(t) = P_{AV} + \sqrt{P_{AV}^2 + Q^2} \cos(2w t + 2\theta_i + \tan^{-1} \frac{Q}{P_{AV}})$$



Swing from P_{AV}:
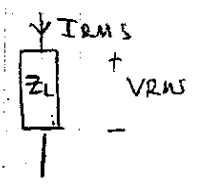
$$\sqrt{P_{AV}^2 + Q^2} = \sqrt{(V_{RMS} I_{RMS} \cos(\theta_{ZL}))^2 + V_{RMS}^2 I_{RMS}^2 \sin^2 \theta_{ZL}} = V_{RMS} I_{RMS} \text{ (apparent power)}$$



② Average Stored Energy in capacitor

$$E_{cap}(t) = \frac{1}{2} C V_c^2(t) \text{ joule} \quad \leftarrow \text{A.C. } (\omega)$$

$$E_{cap}^{average} = \frac{1}{T} \int_0^T E_{cap}(\tau) d\tau = \frac{1}{2} C \frac{1}{T} \int_0^T V_c^2(\tau) d\tau = \frac{1}{2} C V_{RMS}^2$$

$$Q^{cap} = V_{RMS} I_{RMS} \sin(\theta_Z) \quad \leftarrow -90^\circ$$

$$P^{cap} = 0$$

$$Q^{cap} = -V_{RMS} I_{RMS}$$

$$= -V_{RMS} \frac{V_{RMS}}{|Z_{cap}|} = -\omega C V_{RMS}^2$$

\uparrow
 $\frac{1}{j\omega C}$

$$J_c^{ph} = \frac{V_c^{ph}}{Z_c}$$

• $Q^{cap} = -2\omega E_{cap}^{average}$

For an Inductor:

$$E_L^{av} = \frac{1}{T} \int_0^T \frac{1}{2} L i_L^2(\tau) d\tau = \frac{1}{2} L (I_{RMS})^2$$

$$Q^{ind} = V_{RMS} I_{RMS} \sin(\theta_{ZL}) = V_{RMS} I_{RMS} \sin(90^\circ) = (I_{RMS} |Z_L|) I_{RMS}$$

\uparrow
 90°

\uparrow
 $j\omega L$

$$= \omega L I_{RMS}^2$$


• $Q^{ind} = 2\omega E_L^{av}$

Complex Power

P_{AV} , Q : reactive power (VAR: voltage Amphere reactive)
 average power


$$p(t) = P_{AV} + P_{AV} \cos(2\omega t + 2\theta_i) - Q \sin(2\omega t + 2\theta_i)$$

instantaneous power

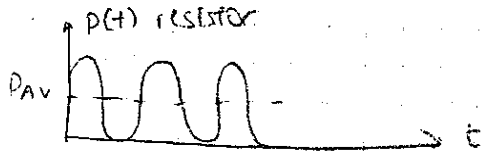

$$P_{AV} = V_{RMS} I_{RMS} \cos(\theta_z)$$

$$Q = V_{RMS} I_{RMS} \sin(\theta_z)$$

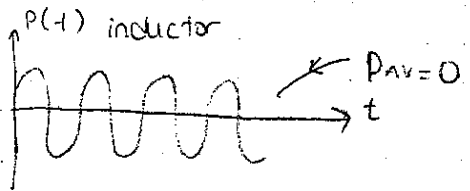


$z = j\omega L$
 $\theta_z = 90^\circ$
 $P_{AV} = 0$
 $Q = V_{RMS} I_{RMS}$

Complex Power

$$S = P + jQ = V_{RMS} I_{RMS} (\cos \theta_{zL} + j \sin \theta_{zL}) = V_{RMS} I_{RMS} e^{j\theta_{zL}}$$

Angle of load impedance

$$S = \frac{1}{2} V I^* = \frac{1}{2} |V| e^{j\theta_V} (|I| e^{j\theta_I})^* = \frac{|V|}{\sqrt{2}} \frac{|I|}{\sqrt{2}} e^{j(\theta_V - \theta_I)}$$

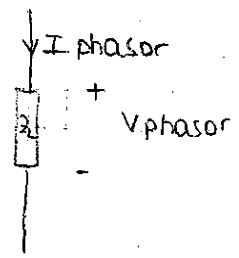


$$= V_{RMS} I_{RMS} e^{j\theta_z}$$

$$z_L = \frac{|V| \angle \theta_V}{|I| \angle \theta_I} \quad \theta_{zL} = \theta_V - \theta_I$$

$$S = \frac{1}{2} V I^* = \frac{1}{2} (z_L I) I^* = \frac{|I|^2}{2} z_L = I_{RMS}^2 z_L \rightarrow \text{load impedance } (z_L)$$


$$S = \frac{1}{2} V \left(\frac{V}{z_L} \right)^* = \frac{|V|^2}{2 z_L^*} = \frac{V_{RMS}^2}{z_L^*} \rightarrow \text{conjugate}$$

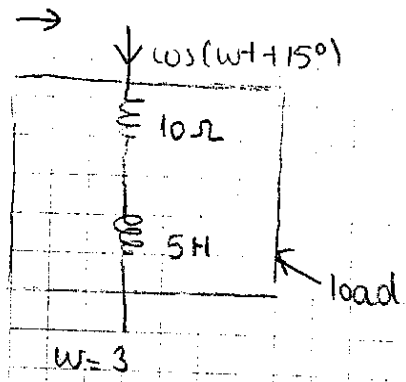

Find P_{AV} and Q of load


i.) Method 1
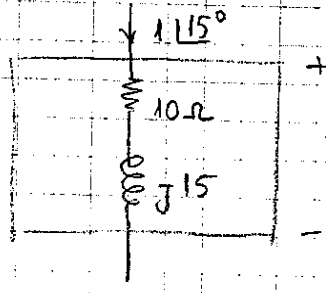
$$P_{AV} = V_{RMS} I_{RMS} \cos(\theta_{zL})$$



$$V = (10 + j15) \frac{1}{\sqrt{2}} \angle 15^\circ = 5(2 + j3) \angle 15^\circ$$

$$= 5\sqrt{13} \angle (15^\circ + \tan^{-1}(3/2))$$

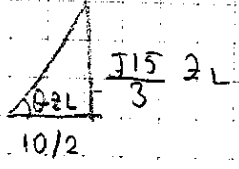

Method 1:

$$P_{AV} = V_{RMS} I_{RMS} \cos(\theta_{zL})$$

$$= \frac{5\sqrt{13}}{\sqrt{2}} \cdot \frac{1}{\sqrt{2}} \cdot \frac{2}{\sqrt{13}} = 5 \text{ Watts}$$

$$Q = V_{RMS} I_{RMS} \sin(\theta_{zL})$$

$$= \frac{5\sqrt{13}}{\sqrt{2}} \cdot \frac{1}{\sqrt{2}} \cdot \frac{3}{\sqrt{13}} = 7.5 \text{ VAR's}$$

Method 2:

$$S = \frac{1}{2} (5\sqrt{13} \angle (15^\circ + \tan^{-1}(3/2)) (1 \angle 15^\circ))$$

$$= \frac{1}{2} 5\sqrt{13} \angle (\tan^{-1}(3/2)) = \frac{5\sqrt{13}}{2} (\cos\theta_x + j\sin\theta_x) = \frac{5\sqrt{13}}{2} \left(\frac{2}{\sqrt{13}} + j\frac{3}{\sqrt{13}} \right)$$

$$= 5 + j(7.5) \text{ VA (Volt-Amperes)}$$

Method 3

$$S = I_{RMS}^2 z_L = \frac{1}{2} (10 + j15) = 5 + j(7.5) \quad I_{RMS} = \frac{1}{\sqrt{2}}$$

Method 4

$$S = \frac{V_{RMS}^2}{z_L^*} \quad \text{where } V_{RMS} = \frac{5\sqrt{13}}{\sqrt{2}}$$



$$S = \frac{25 \cdot \frac{13}{2}}{10 - j15} = \frac{5 \cdot \frac{13}{2}}{2 - j3} = \frac{5 \cdot \frac{13}{2} (2 + j3)}{13} = 5 + j(7.5)$$

Power Triangle and Impedance Triangle

$$S = I_{RMS} z_L = P + jQ$$


power Triangle (Δ)

Impedance Triangle (Δ)

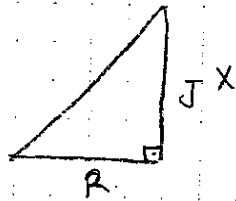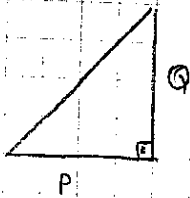

$P = I_{RMS}^2 R$

$Q = I_{RMS}^2 X$




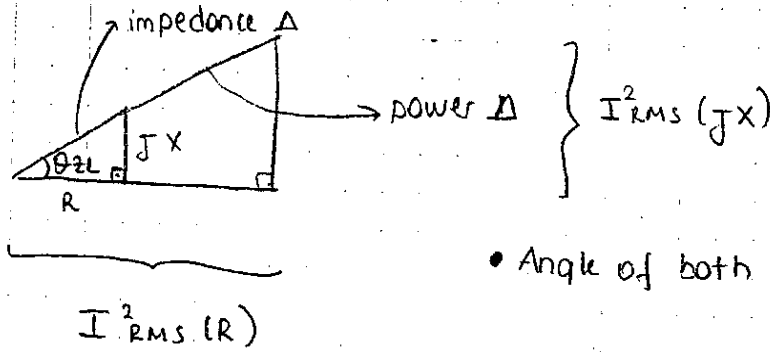


• Angle of both Δ 's are the same

Power Factor (PF)

Inductive load

Capacitive load

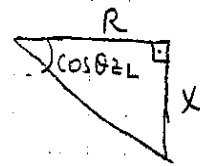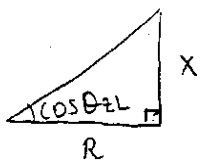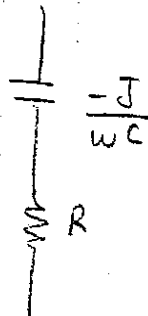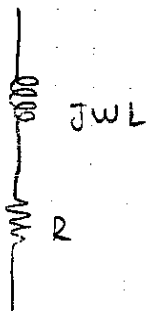

$S = P + jQ$

$S = P + jQ$

$P = I_{RMS}^2 R$ } $P > 0$

$P = I_{RMS}^2 R$ } $P > 0$

$Q = I_{RMS}^2 X$ } $Q > 0$

$Q = I_{RMS}^2 X$ } $Q < 0$


• power factor : $pf = \cos(\theta_{\pm L})$

• $pf = \cos(\theta_{\pm L})$ • leading

• lagging

ΔS (angle of S)



(Current lags the voltage = inductive)

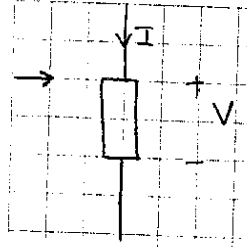

$V = 100 \text{ V (RMS)}$ (We do not need for this method)
 $P = 5 \text{ kW}$
 $\text{pf} = 0.8 \text{ lagging}$

- a.) Find VAR
- b.) Find apparent power

a.) $\phi = ?$

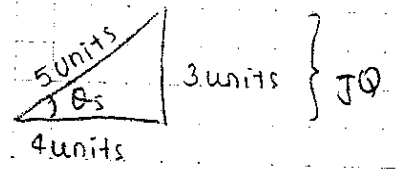
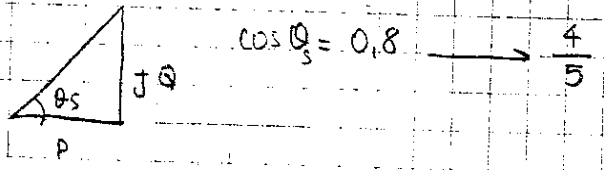


$Q = 3750 \text{ VAR}$ since lagging
 $Q = P \tan \theta_s = 5000 \cdot \frac{3}{4} = 3750$ (lagging)

b.) Apparent Power: $V_{\text{RMS}} I_{\text{RMS}}$

$S = V_{\text{RMS}} I_{\text{RMS}} (\cos \theta_{zL} + j \sin \theta_{zL})$

$|S| = V_{\text{RMS}} I_{\text{RMS}} \quad |S| = \frac{5000}{\cos(\theta_s)} = \frac{5000}{0.8} = 6250 \text{ VA}$

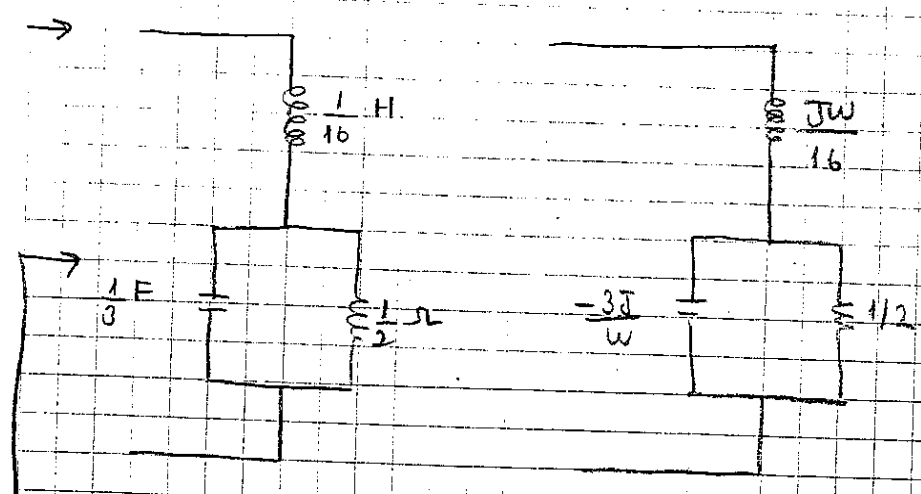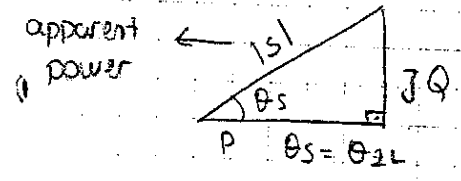

$Z(j\omega) = ?$ phasor domain

($\omega \neq 0$) Note that

$$Z(j\omega) = j\omega \frac{1}{16} + \frac{-j\omega \cdot 1}{\omega \cdot 2} = \frac{288 + j\omega(\omega^2 - 12)}{16(36 + \omega^2)} \quad \text{p. 40 of notes} \quad (54)$$

$\omega = \sqrt{12} \longrightarrow Z(j\omega) = \frac{288}{16(36+12)} = \text{purely Real } pf = 1$

 \longrightarrow cosine of angle with v

 unity power factor


$\omega < \sqrt{12} \longrightarrow \text{Im} \{ Z(j\omega) \} < 0 \longrightarrow \text{capacitive load}$

$$pf = \frac{288}{\sqrt{288^2 + (\omega(\omega^2 - 12))^2}} \quad \leftarrow \cos(\theta_{ZL}) \quad (\text{leading})$$

$\omega > \sqrt{12} \longrightarrow \text{Im} \{ Z(j\omega) \} > 0 \longrightarrow \text{Inductive load}$

$$D.f. = \frac{288}{\sqrt{288^2 + (\omega(\omega^2 - 12))^2}} \quad (\text{lagging})$$

Superposition in AC Power

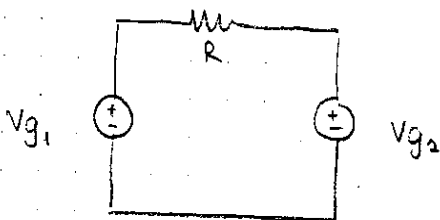

$$V_{g1} = V_1 \cos(\omega_1 t + \theta_1)$$

$$V_{g2} = V_2 \cos(\omega_2 t + \theta_2)$$

$$i(t) = I_1 \cos(\omega_1 t + \phi_1) + I_2 \cos(\omega_2 t + \phi_2) \text{ A (By superposition of } V_{g1} \text{ \& } V_{g2})$$


$$\begin{aligned}
 P_{AV} &= \frac{1}{T} \int_0^T (i(t))^2 R dt' = \frac{R}{T} \int_0^T \left[I_1^2 \cos^2(\omega_1 t + \phi_1) + I_2^2 \cos^2(\omega_2 t + \phi_2) \right. \\
 &\quad \left. + 2I_1 I_2 \cos(\omega_1 t + \phi_1) \cos(\omega_2 t + \phi_2) \right] dt' \\
 &= R \left(\underbrace{\frac{1}{T} \int_0^T \dots dt'}_{(I_{1,rms})^2} + \underbrace{\frac{1}{T} \int_0^T \dots dt'}_{(I_{2,rms})^2} + \underbrace{\frac{2}{T} \int_0^T I_1 I_2 \cos(\omega_1 t + \phi_1) \cos(\omega_2 t + \phi_2) dt'}_0 \right)
 \end{aligned}$$

Since $\omega_1 \neq \omega_2$;


$$\frac{I_1 I_2}{T} \int_0^T \left[\cos(\omega_1 - \omega_2)t' + \phi_1 - \phi_2 \right] + \left[\cos(\omega_1 + \omega_2)t' + \phi_1 + \phi_2 \right] dt'$$

$$= R_1 (I_1^{RMS})^2 + R_2 (I_2^{RMS})^2$$

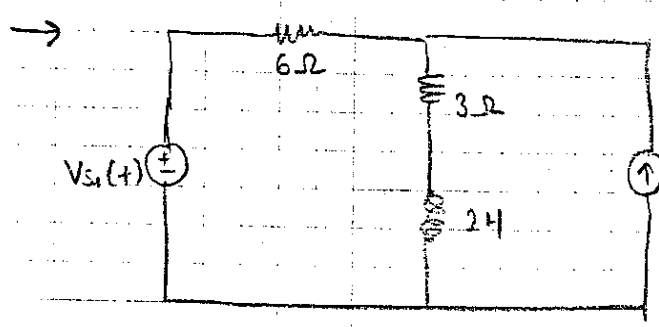Superposition in AC power is possible for inputs with different frequencies.



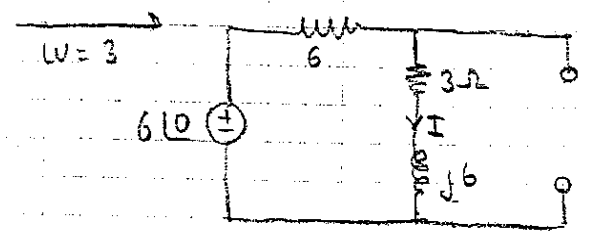
$v_{s1}(t) = 6 \cos(3t)$
 $i_{s2}(t) = 2 \cos(4t + 30^\circ) \text{ A}$
 $P_{3\Omega}^{AV} = ?$



$$I = \frac{6}{9 + j6} = \frac{2}{3 + j2} = \frac{2}{\sqrt{13} \angle \tan^{-1}(2/3)}$$

$$= \frac{2}{\sqrt{13}} \angle -\tan^{-1}(2/3)$$

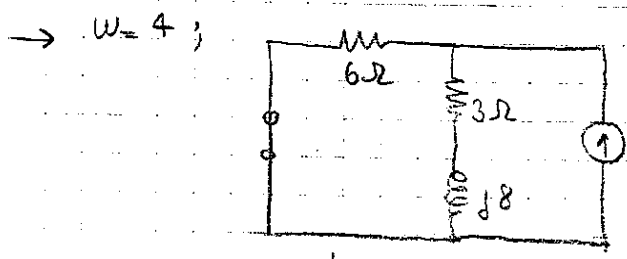$P_{3\Omega}^{AVG, \omega=3} = (I_{RMS}^{3\Omega})^2 R = \left(\frac{2}{\sqrt{2} \sqrt{13}} \right)^2 3 = \frac{2}{13} 3 = \frac{6}{13} \text{ Watts}$




$$I = 2 \angle 30^\circ \frac{1}{\frac{3 + j8}{3 + j8} + \frac{1}{6}} = 2 \angle 30^\circ \frac{6}{9 + j8} = 2 \angle 30^\circ \frac{6}{\sqrt{145} \angle \tan^{-1}(8/9)}$$

$P_{3\Omega}^{AVG, \omega=4} = (I_{RMS}^{3\Omega, \omega=4})^2 \cdot 3 = \left(\frac{2 \cdot 6}{\sqrt{2} \sqrt{145}} \right)^2 \cdot 3 = \frac{216}{145} \text{ Watts}$

$P_{3\Omega}^{AVG} = \frac{1}{2} + \frac{3}{2} = 2 \text{ Watts}$

Maximum Power Transfer

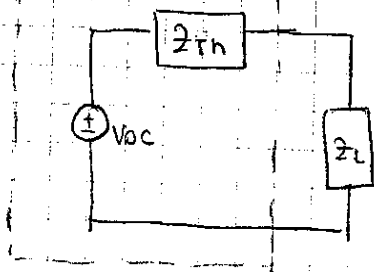

V_{oc} , Z_{Th} : fixed (given to us. (not a function of load))
 Select Z_{load} s.t. P_{AV} transferred to load is maximized.

$Z_{Th} = R_{Th} + jX_{Th}$ $Z_L = R_L + jX_L$

load Iphase = $\frac{V_{oc}}{(R_{Th} + R_L) + j(X_{Th} + X_L)}$ → $\frac{(V_{oc}^{RMS})^2}{(R_{Th} + R_L)^2 + (X_{Th} + X_L)^2} \cdot R_L$


$\frac{\partial P_{AV}}{\partial R_L} = 0$
 $\frac{\partial P_{AV}}{\partial X_L} = 0$

} Solve together →

$R_L = R_{Th}$
 $X_L = -X_{Th}$

$Z_L = Z_{Th}^*$

Example:

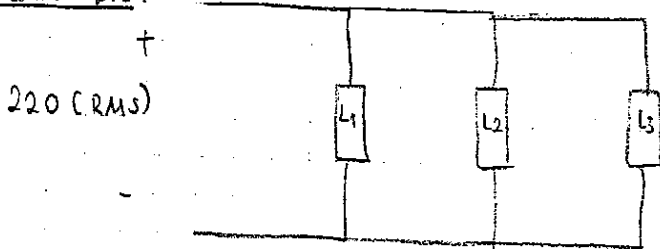

220V (RMS)



Load 1; 16 kW, 18 kVAR

Load 2; 10kVA, at pf 0.6 leading

Load 3; 8kW at unity pf

- a) Find pf at the source side.
- b) Find the impedance seen by the source.

a.)

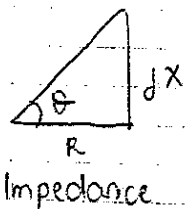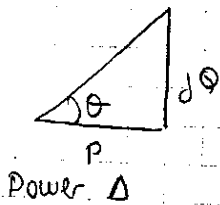


pf = cos theta

source $S_{total} = S_{L1} + S_{L2} + S_{L3}$

$S_{L1} = 16 + j18 \text{ kVA}$


$S_{L2} = 6 - j8 \text{ kVA}$
 leading

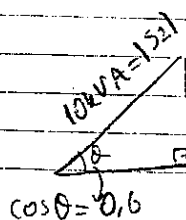

$$S_L = 8 \text{ kVA}$$

$$S_{\text{Total}} = 30 + j10 \text{ kVA}$$
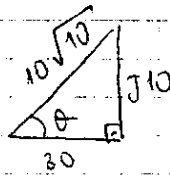
$$P.f.: \cos \theta = \frac{30}{10\sqrt{10}} = \frac{3}{\sqrt{10}} \text{ lagging}$$



(57)

$$b.) |S_{\text{Total}}| = V_{\text{Source}}^{\text{RMS}} \cdot I_{\text{Source}}^{\text{RMS}}$$

$$10\sqrt{10} = 220 \cdot I_{\text{Source}}^{\text{RMS}}$$

$$I_{\text{Source}}^{\text{RMS}} = \frac{\sqrt{10}}{22} \text{ kA (RMS)}$$

$$S_{\text{Total}} = (I_{\text{Source}}^{\text{RMS}})^2 Z_{\text{Total}}$$

$$Z_{\text{Total}} = \frac{(30 + j10)10^3}{\left(\frac{\sqrt{10}}{22}\right)^2 10^6} = \frac{22^2 (3 + j)10^4}{10^7} = 22^2 \cdot 10^{-3} (3 + j)$$

$$= 0,484 (3 + j) \Omega$$


Power Factor Compensation

Example: A mill consumes 100 kW, 220 V (RMS) at pf: 0,85

& lagging

a-) Find RMS current supplied by 220V source to mill.

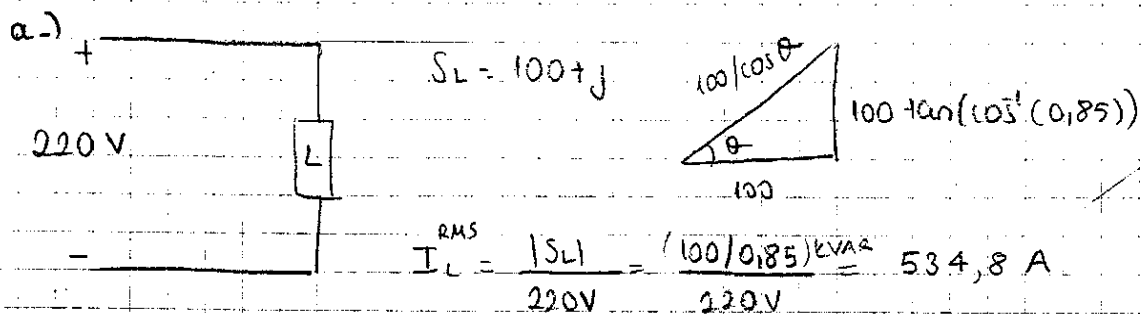
b-) Find the current RMS if pf were 0,95 lagging.



$$I_L^{\text{RMS}} = \frac{|S_L|}{220V} = \frac{10/0,95 \cdot 10^3}{220V} = 478 \text{ A}$$

Third part: c-) If there is a line connecting the source to the load & if the $R_{\text{line}} = 0,1 \Omega$; Find power loss over the line for

pf: {0,85, 0,95}

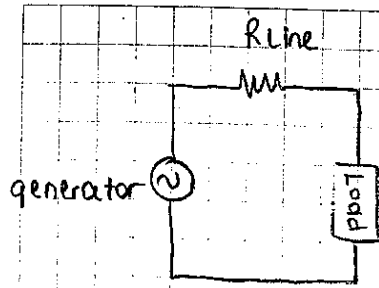

i-) $pf = 0.85 \rightarrow I_{load} = 534.8 \text{ A (RMS)}$
 220 V
 $P_{line} = I_{load, rms}^2 \times (0.1) = 28.6 \text{ kW}$


ii-) $pf = 0.95 \rightarrow P_{line} = I_{line, rms}^2 \times (0.1)$
 $468 \text{ A} \rightarrow I_{line, rms} = 468 \text{ A}$
 $= 22.9 \text{ kW}$

d-) Define efficiency as $\frac{\text{Power Delivered}}{\text{Power generated}} = \text{efficiency}$





i-) $pf : 0.85 \quad \text{eff} = \frac{100}{100 + 28.6} = 77.7\%$

ii-) $pf : 0.95 \quad \text{eff} = \frac{100}{100 + 22.9} = 82\%$

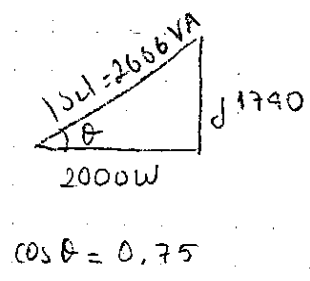Example: Load requires 2kW at 0.75 p-f. lagging at 220V (RMS). Calculate the reactive power supplied by the compensating capacitor to make pf 0.9 lagging. Find the impedance and the capacitance in Farads (Assume 220V RMS, 50 Hz line)



$S_L = 2000 + j1740$

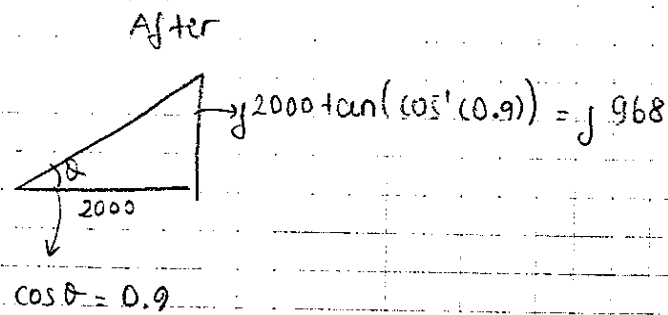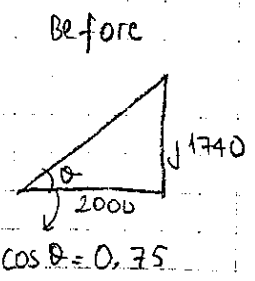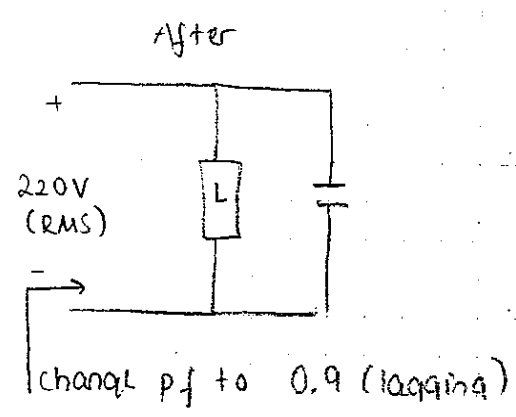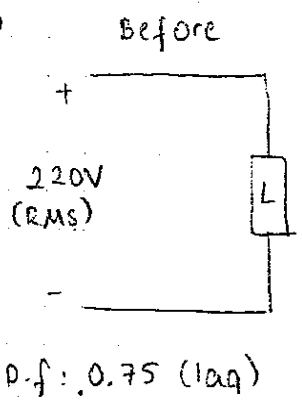


$S_{before} = 2000 + j1740$

$$S_{\text{desired after}} = 2000 + j968$$

$$S_{\text{desired}} = S_{\text{load}} + S_{\text{cap}}$$
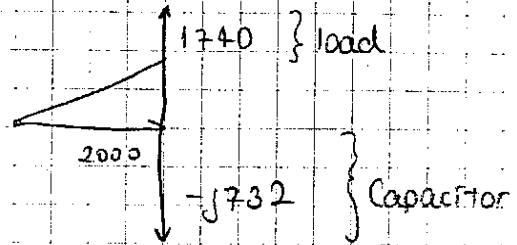
$$S_{\text{cap}} = -j(1740 - 968) = -j772$$



Impedance Calculation:

$$S_{\text{cap}} = \frac{(V_{\text{cap}}^{\text{RMS}})^2}{Z_{\text{cap}}^*} \quad -j772 = \frac{(220)^2}{Z_{\text{cap}}^*} \quad ; \quad Z_{\text{cap}}^* = \frac{48400}{772} \text{ } \Omega$$

$$Z_{\text{cap}}^* = -j61.07$$

$$Z_{\text{cap}} = \frac{-j}{\omega C_{\text{cap}}}$$


$$61.07 = \frac{1}{(2\pi 50) C_{\text{cap}}} \quad ; \quad C_{\text{cap}} = \frac{1}{100\pi (61.07)} = 52 \mu\text{F}$$

$$Z_{\text{cap}} = -j61.07$$

Volt - Ampere Method for Power Calculations

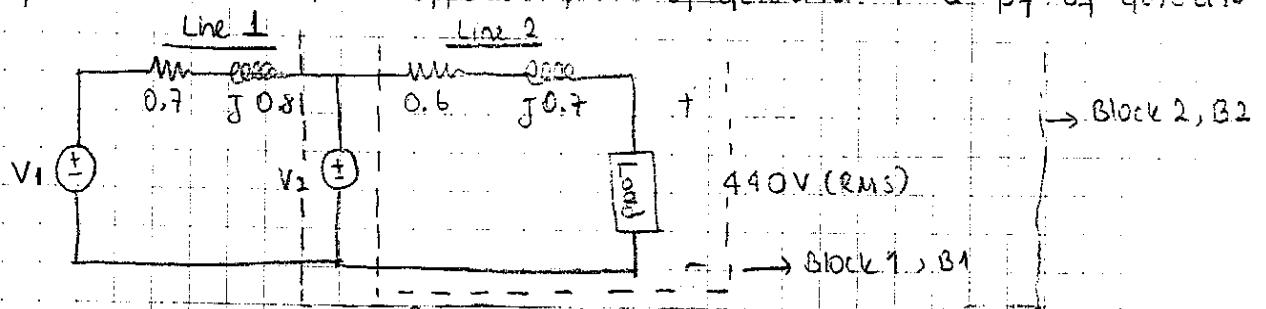Example: Two generators supply ^{to the load} 10kW at 0.8 pf lagging

The generator 2 supplies 5kW at 0.6 pf lagging. Find the voltages of V_1 & V_2 (RMS), the apparent power of generator 1 & pf of generator 2.




$$S_{\text{load}} = 10000 + j7500 \text{ VA}$$

$$S_{\text{Line, 2}} = ?$$

$$S_{\text{Line, 2}} = (I_{\text{load}}^{\text{RMS}})^2 (0.6 + j0.7) \quad I_{\text{load}}^{\text{RMS}} = \frac{|S_{\text{load}}|}{440\text{V}} = \frac{10000/0.8}{440} = 28.4 \text{ A}$$

$$S_{\text{Line, 2}} = (I_{\text{load}}^{\text{RMS}})^2 (0.6 + j0.7) = 484 + j565$$
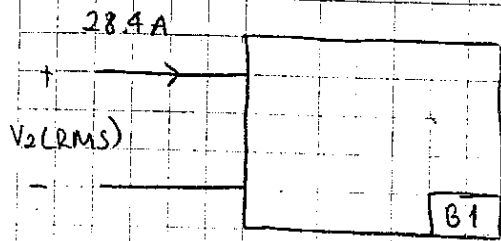
$$S_{B1} = S_{\text{Line, 2}} + S_{\text{load}} = 10,484 + j8065$$



$$|S_{B1}| = V_{B1}^{RMS} \cdot I_{B1}^{RMS}$$


$$\sqrt{(10,484)^2 + (8065)^2}$$

$$V_{B1}^{RMS} = V_2^{RMS} = 466 \text{ V (RMS)}$$

supplied

$$S_{G2} = 5000 + j 5000 \frac{4}{3} = 5000 + j 6666$$
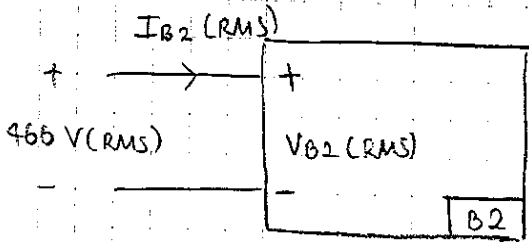
$$S_{B2} = S_{B1} - S_{G1}^{supplied} = 5484 + j 1400$$



$$|S_{B2}| = 466 I_{B2}^{RMS}$$

$$I_{B2}^{RMS} = \frac{|5484 + j 1400|}{466} = 12.14 \text{ A (RMS)}$$

$$S_{line1} = (12.14)^2 [0.7 + j 0.8] = 103 + j 1$$


supplied

$$S_{G1} = S_{line1} + S_{B2} = 5587 + j 1516$$

$$V_1 = \frac{|S_{G1}|}{12.14} = 477 \text{ V}$$


Apparent Power $V_{G1} = |S_{G1}| = 5784$

3 Phase Circuits

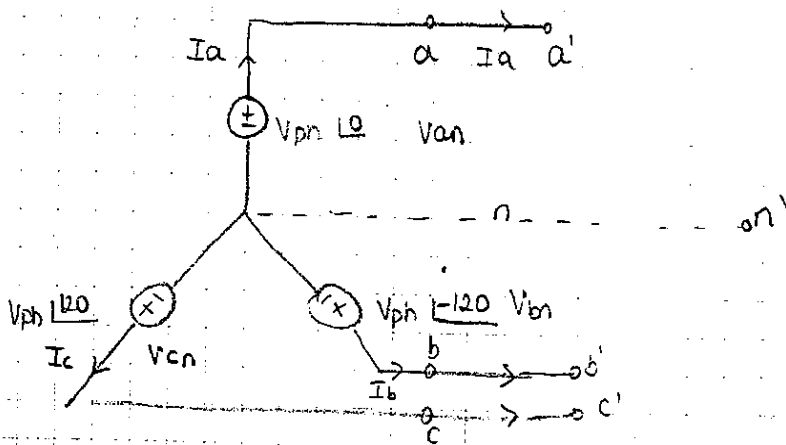

- V_{an}, V_{bn}, V_{cn} : phase voltages
- $V_{a-b}, V_{b-c}, V_{c-a}$: Phase
- I_a, I_b, I_c : phase currents
- V_{ab}, V_{ac}, V_{bc} : line voltages
- $I_{aa'}, I_{bb'}, I_{cc'}$: line

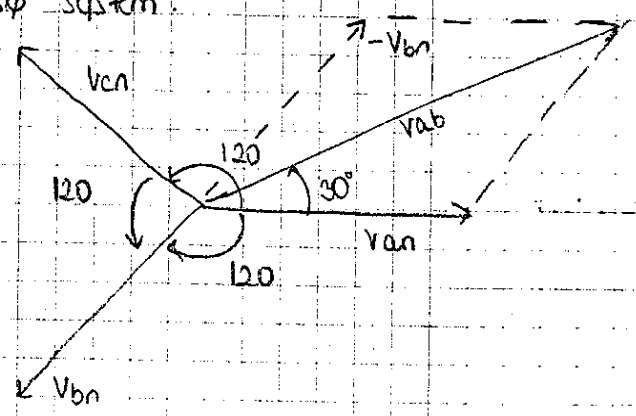In 3- ϕ systems, a, b, c are called the lines connecting to another 3 ϕ system.



phasor diagram

V_{an}, V_{bn}, V_{cn} : phase voltages

$V_{ab} = ? \quad V_a - V_b = V_{an} - V_{bn}$

$V_{ab} = \sqrt{3} V_{ph} \angle 30^\circ$

or

$$V_{ab} = V_{an} - V_{bn} = V_{ph} \angle 0^\circ - V_{ph} \angle -120^\circ$$

$$= V_{ph} \angle 0^\circ + 1 \angle 180^\circ V_{ph} \angle -120^\circ$$

$$= V_{ph} \angle 0^\circ + V_{ph} \angle 60^\circ = V_{ph} \left[1 + \frac{1}{\sqrt{2}} + j \frac{\sqrt{3}}{2} \right]$$

$$= \sqrt{3} V_{ph} \left(\frac{\sqrt{3}}{2} + j \frac{1}{2} \right) = \sqrt{3} V_{ph} \angle 30^\circ$$


$V_{ac} = \sqrt{3} V_{ph} \angle -30^\circ$

$V_{cb} = \sqrt{3} V_{ph} \angle 90^\circ$

• For Y-connected load/generator:

$I_{line} = I_{phase}$

• Δ -connected

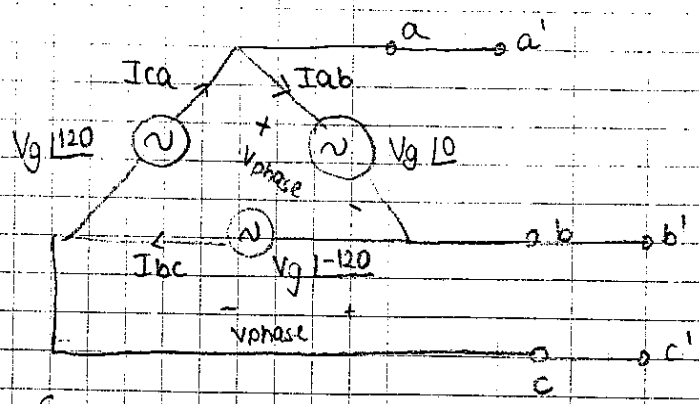


phase $\left\{ \begin{array}{l} V_{an}, V_{bn}, V_{cn} : \text{phase voltages} \\ I_{ab}, I_{ca}, I_{bc} : \text{phase currents} \end{array} \right.$

line $\left\{ \begin{array}{l} V_{ab}, V_{bc}, V_{ca} : \text{line voltages} \\ I_{aa'}, I_{bb'}, I_{cc'} : \text{line currents} \end{array} \right.$

- For Δ -load

$V_{\text{phase}} = V_{\text{line}}$


Line Current & Phase Current

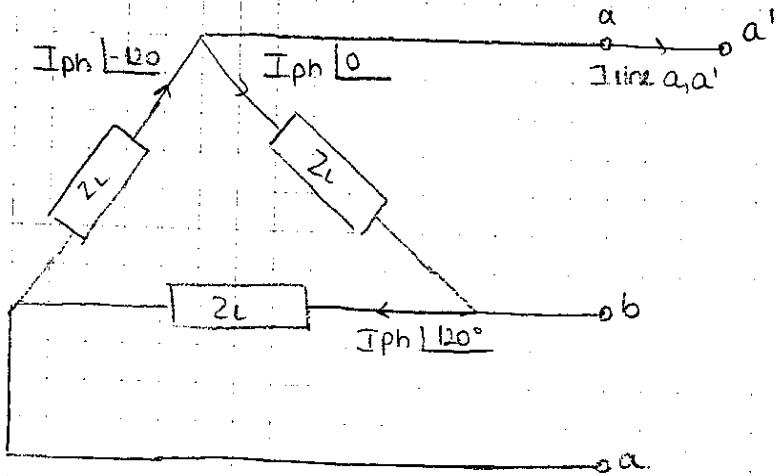


$I_{line aa'} = I_{ph} \angle -120^\circ - I_{ph} \angle 0^\circ = \sqrt{3} I_{ph} \angle 210^\circ$

$I_{line bb'} = \sqrt{3} I_{ph} \angle -30^\circ$

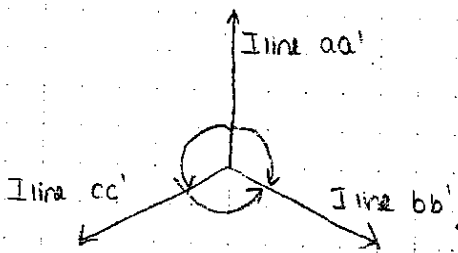$I_{line cc'} = \sqrt{3} I_{ph} \angle 90^\circ$




Mini Question:

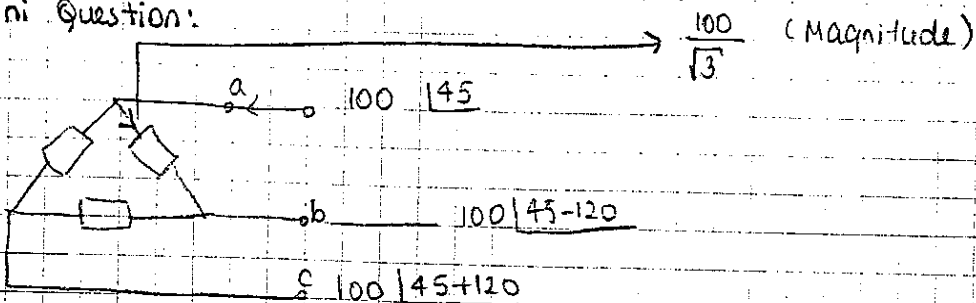


Notes:

1. Balanced 3 ϕ systems:

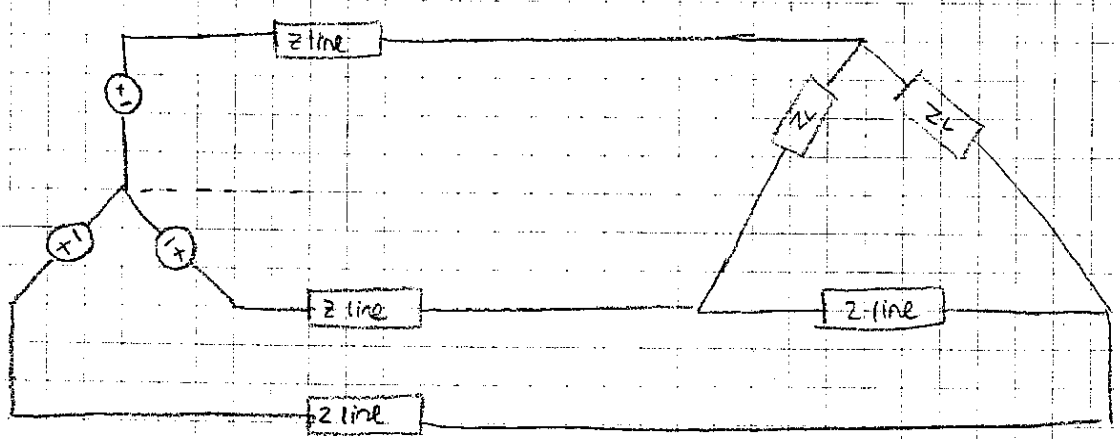


In EE 202 we only study balanced 3 ϕ systems.

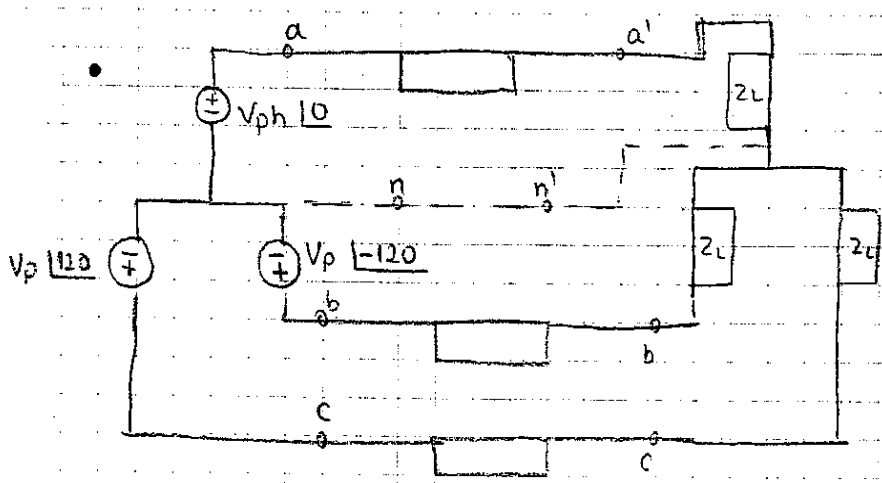
Balanced system is the system having identical components on each phase (apart from 120° of phase shift in the external input)



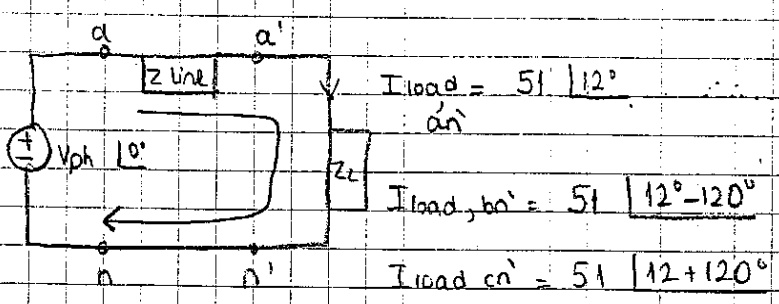
If the system is balanced, I can solve only phase a circuit (that is the circuit between a and n)



2. Neutral Connection

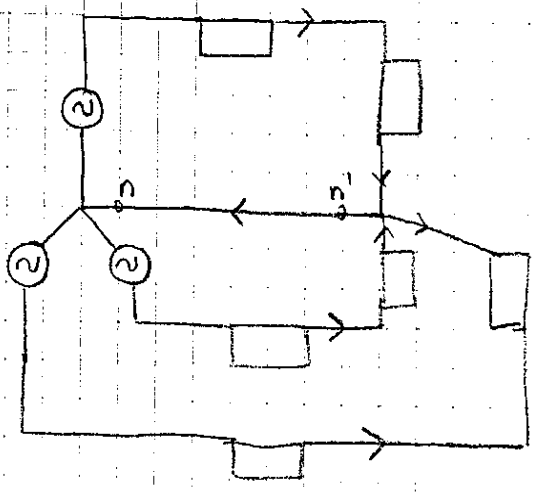

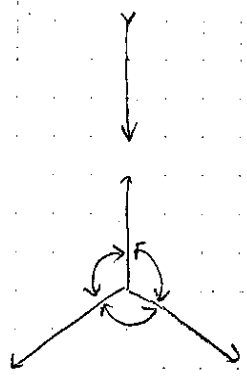
$I_{n'n} = ?$ (Assume balanced system)
 If balanced $I_{n'n} = 0A!$




phasor diagram for load currents

So, the line between n & n' carries $0A$ of current, so it can be removed without any harm to the circuit

3. Δ Connected Generators

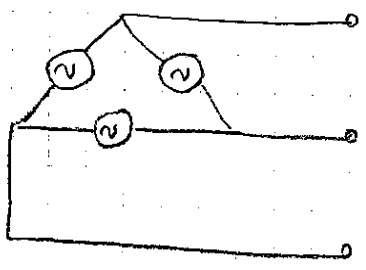

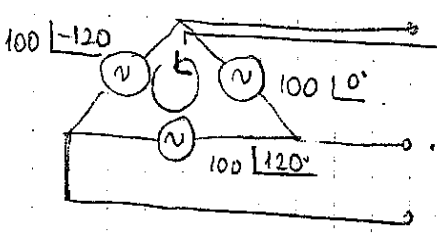
Generators aren't, in practice connected in Δ configuration. Since, if the system is even a little unbalanced.




Current can be very large.

Generators are connected in Y configuration.

4. a,b,c Sequence (positive sequence)

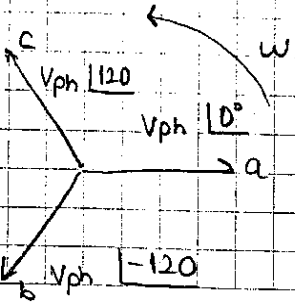


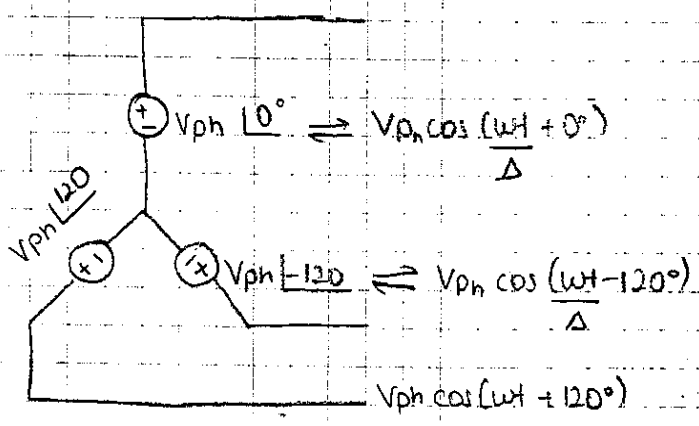a,b,c sequence (positive sequence)
 a has 0° then
 b has 0° then c has 0°




• a.c.b sequence (negative sequence)

a → c → b reaches 0° phase

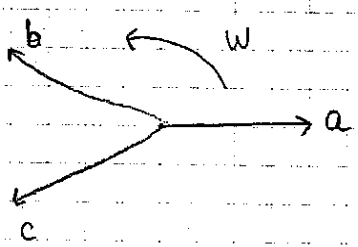

Example:

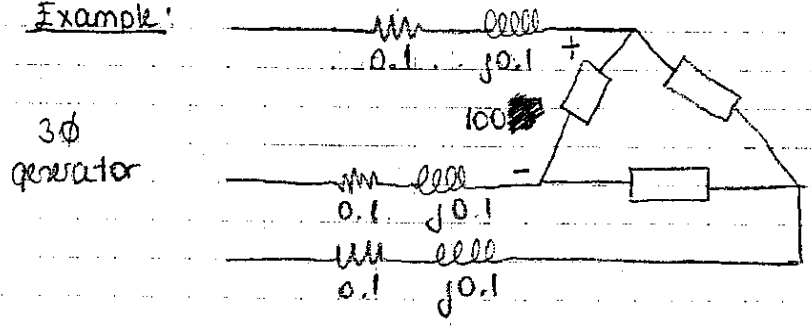

A 3φ load consumes 1200 Watts at pf 0.8

a.) Find power supplied by the generator

b.) Find V_{ph} (RMS) of the generator

i.) If generator Δ connected

ii.) If generator Y connected

a.) $S_{3\phi}^{load} = 1200 + j900$

Total complex power consumed by load

$S_{\phi} = \frac{S_{3\phi}}{3} = 400 + j300$

$$|S_{\phi}| = |V_{ph}| |I_{ph}|$$

$$500 = 100 |I_{ph}|$$

$$I_{ph, RMS} = 5A$$


$$I_{line}^{RMS} = I_{ph}^{RMS} \sqrt{3} = 5\sqrt{3} \text{ A (RMS)}$$

$$S_{\phi}^{line} = (I_{line}^{RMS})^2 (0.1 + j0.1) = 7.5 + j7.5$$

$$S_{\phi}^{line} = 22.5 + j22.5$$

a) $S^{supplied} = (1200 + j900) + (22.5 + j22.5) = 1222.5 + j922.5$

b.)

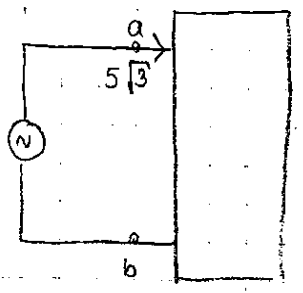

per phase power supplied: $407.5 + j307.5$


↑ Supplied

$$|S_{per\ phase\ supplied}| = 5\sqrt{3} V_{ph} \rightarrow V_{ph} = \frac{\sqrt{(407.5)^2 + (307.5)^2}}{5\sqrt{3}}$$

i) $V_{ph\Delta} = \sqrt{3} V_{phY} = \frac{\sqrt{(407.5)^2 + (307.5)^2}}{5}$

3φ power calculations

Y-connection

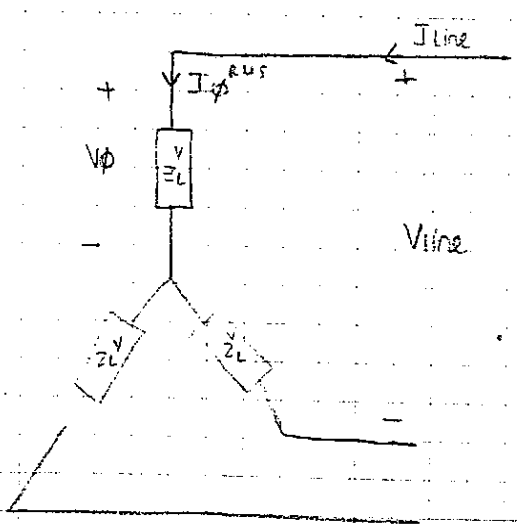


$$S_{total} = 3S_{\phi} = 3(I_{\phi}^{RMS})^2 Z_L^Y$$

$$S_{total} = 3 I_{\phi}^{RMS} \cdot I_{\phi}^{RMS} |Z_L^Y| e^{j\theta_{Z_L^Y}}$$

$$= \frac{3 I_{line}^{RMS} V_{line}^{RMS}}{\sqrt{3}} e^{j\theta_{Z_L^Y}} = \sqrt{3} I_{line}^{RMS} V_{line}^{RMS} e^{j\theta_{Z_L^Y}}$$

Δ-connection

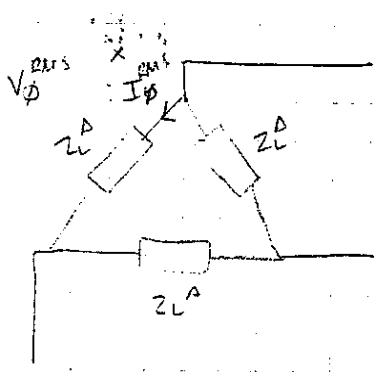

$$I_{\phi}^{RMS} = \frac{I_{line}^{RMS}}{\sqrt{3}}$$

$$S_{3\phi} = 3S_{\phi} = 3(I_{\phi}^{RMS})^2 Z_L^{\Delta}$$

$$= 3 I_{\phi}^{RMS} I_{\phi}^{RMS} |Z_L^{\Delta}| e^{j\theta_{Z_L^{\Delta}}}$$

$$= 3 I_{\phi}^{RMS} V_{\phi}^{RMS} e^{j\theta_{Z_L^{\Delta}}}$$

$$= 3 I_{line}^{RMS} V_{line}^{RMS} e^{j\theta_{Z_L^{\Delta}}}$$

$$= \sqrt{3} I_{line}^{RMS} V_{line}^{RMS} e^{j\theta_{Z_L^{\Delta}}}$$


(same as Y connection)

Cont. Y-Connection

Contn. Δ-Connection

$$P = \sqrt{3} I_{line}^{RMS} V_{line}^{RMS} \cos(\theta_{2L})$$
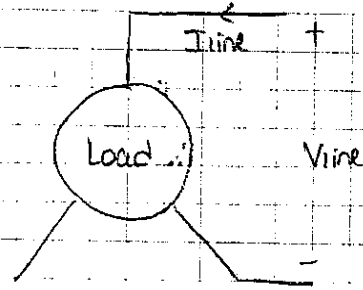
$$Q = \sqrt{3} I_{line}^{RMS} V_{line}^{RMS} \sin(\theta_{2L})$$



(67)


To calculate the total power consumed by load you need:

$$P_{3\phi} = \sqrt{3} V_{line}^{RMS} I_{line}^{RMS} \cos(\theta_L)$$


$$Q_{3\phi} = \sqrt{3} V_{line}^{RMS} I_{line}^{RMS} \sin(\theta_L)$$

You do not need the type of connection (Y or Δ)

Remember

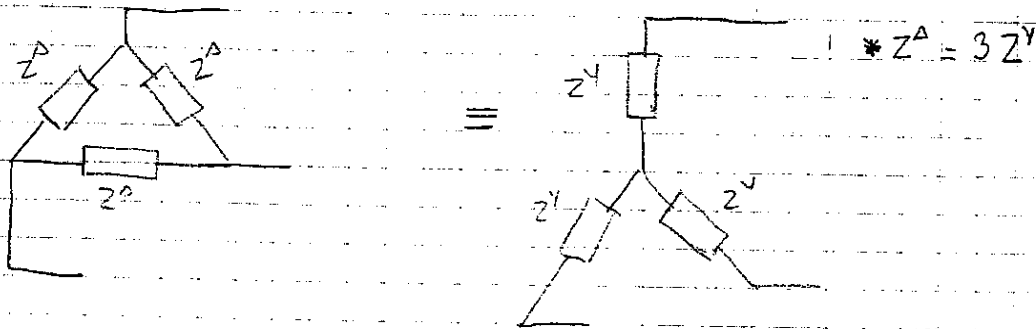

Example:

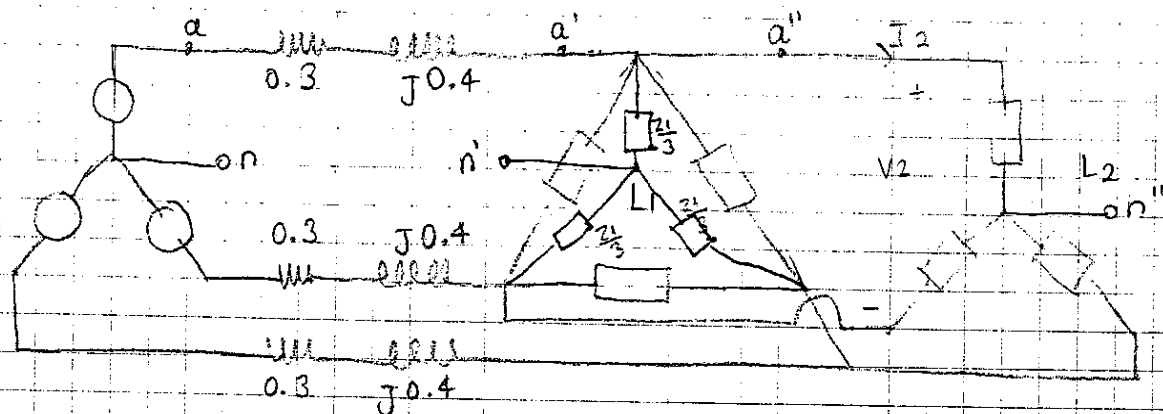


Generator produces 380 V (line to line) RMS voltage at 9 kW and 9 kVAR

L1: 6 kW at 0.6 pf lagging

Find V_2 , I_2 and power absorbed by load 2.

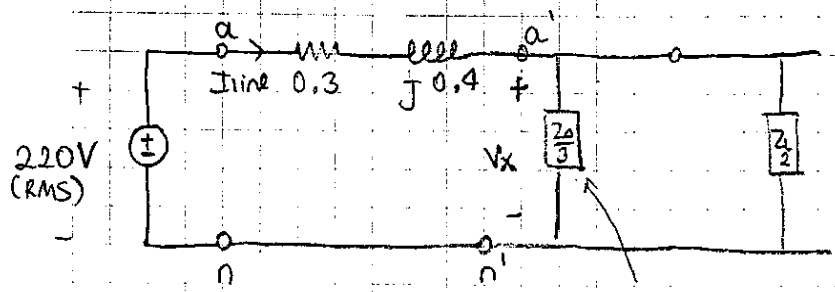Solution 1: Using single phase equivalent circuit.



L1: after $\Delta \rightarrow Y$ transformation.

$$V_{an} = \frac{380}{\sqrt{3}} = 220 \text{ V (RMS)}$$

$$S_{\text{supplied}}^{\text{gen}} = 3000 + j3000 \rightarrow |S_{\phi}^{\text{gen}}| = 220 I_{\text{line}}^{\text{RMS}} \rightarrow I_{\text{line}}^{\text{RMS}} = 19.3 \text{ A}$$

perphase power

$$S_{\phi}^{\text{line}} = (I_{\text{line}}^{\text{RMS}})^2 (0.3 + j0.4) = 112 + j149$$

$$S_{\phi}^{L1+L2} = S_{\phi}^{\text{gen}} - S_{\phi}^{\text{line}} = 2888 + j2851$$


power consumed by load #1, #2

$$|S_{\phi}^{L1+L2}| = V_x^{\text{RMS}} (19.3)$$

↓

$$V_x^{\text{RMS}} = 210.3 \text{ V}$$
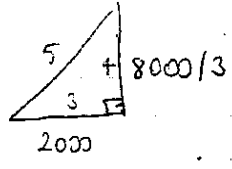
$$S_{\phi}^{L2} = S_{\phi}^{L1+L2} - S_{\phi}^{L1} \rightarrow S_{\phi}^{L1} = 888 + j187$$




$$V_2 = \sqrt{3} V_x = 364 \text{ V (RMS)}$$

$$|S_{\phi}^{L2}| = |I_{\phi,2}^{\text{RMS}}| V_x^{\text{RMS}} \rightarrow I_{2\phi}^{\text{RMS}} = \frac{907}{210.3} \rightarrow \sqrt{888^2 + 187^2}$$

$$I_{2\phi}^{\text{RMS}} = 4.3 \text{ A}$$

$$I_2 = 4.3 \text{ A}$$

Solution 2: Single line diagram

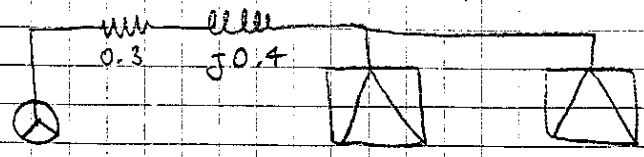

$$|S_{3\phi}^{\text{gen}}| = \sqrt{3} V_{\text{line}}^{\text{gen}} I_{\text{line}}^{\text{gen}}$$

(formula valid for both Y & Δ connection)

$$9000 \sqrt{2} = \sqrt{3} \cdot 380 I_{line}^{gen} \rightarrow I_{line}^{gen} \rightarrow I_{line}^{gen} = 19.3 \text{ A}$$

$$S_{3\phi}^{line} = 3 (19.3)^2 (0.3 + j0.4) = 336 + j447$$


$$S_{3\phi}^{L1+L2} = S_{3\phi}^{gen} - S_{3\phi}^{line} = 866.4 + j8553$$

$$|S_{3\phi}^{L1+L2}| = \sqrt{3} V_{line-line}^{L1+L2, RMS} I_{line-line}^{L1+L2, RMS}$$

$$V_{line-line}^{L1+L2} = 364 \text{ V} \rightarrow V_2$$

$$S_{3\phi}^{L2} = S_{3\phi}^{L1+L2} - S_{3\phi}^{L1} = 2664 + j561 \quad * \text{ Find } I_2 !$$

Example

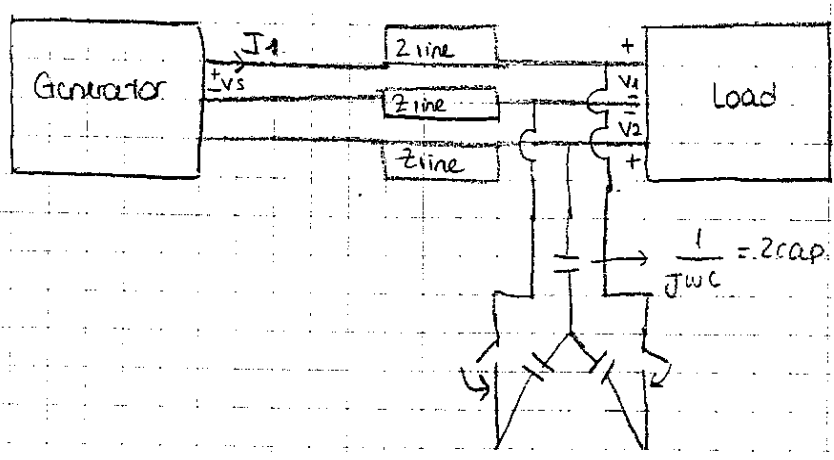

A balanced 3φ load 400 kW pf $1/\sqrt{2}$ lagging

$$V_1 = 400 \angle 30^\circ \text{ V}_{RMS} \quad Z_{line} = 0.07 + j0.16$$

$$V_2 = 400 \angle -30^\circ \text{ V}_{RMS}$$

a) Switches open find I_1 , V_s the complex power supplied by source and efficiency.

$$P_{load} = 400 \text{ kW} = \sqrt{3} V_{line}^{load} I_{line}^{load} \cos(\theta_{load})$$

$$I_{line}^{load} = \sqrt{\frac{2}{3}} \cdot 1000 \text{ A (RMS)}$$

$$= 816.5 \text{ (RMS)}$$

I_1

line-loss
 $S_{3\phi} = 3(816.5)^2(0.07 + j0.16) = 140 + j320 \text{ kVA}$

supplied
 $S_{3\phi} = (400 + j400) + (140 + j320) = 540 + j720 \text{ kVA}$

Eff: $\frac{p_{load}}{p_{supplied}} = \frac{400 \text{ kW}}{540 \text{ kW}} = 74\%$
 ↑
 watts
 watts


b.) Switches are closed and pf of the compensated load becomes 0.8 lagging.

Find the susceptance of capacitors in the bank, Vs, complex

power supplied, efficiency



Before

$S_{3\phi} = 400 + j400$

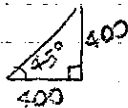

After

desired
 $S_{3\phi} = 400 + j300$

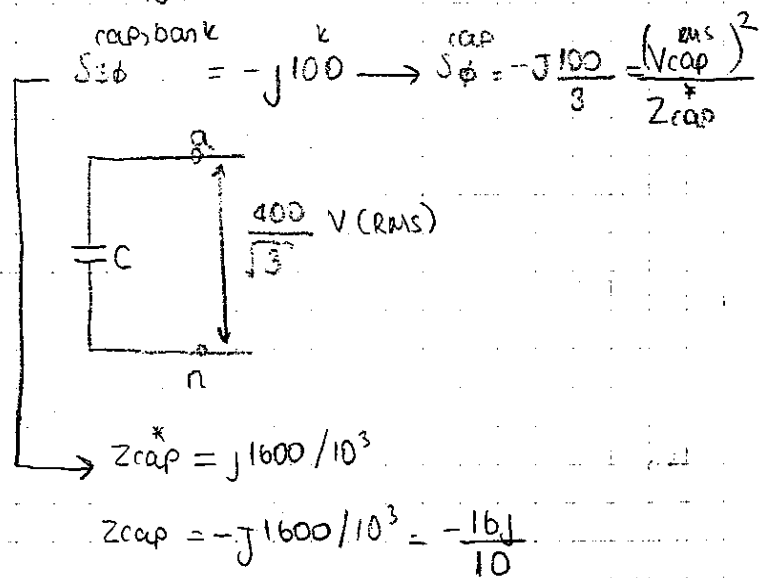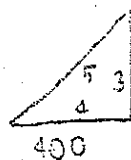

after
 $P_{load} = \sqrt{3} V_{line} I_{line}^{load} \cos(\theta_{load})$
 0.8

$400 \cdot 10^3 = \sqrt{3} \cdot 400 \cdot I_{line}^{load} \cdot 0.8$

load
 $I_{line} = 721.6 \text{ A (RMS)}$

line
 $S_{loss} = 3(721.6)^2(0.07 + j0.16) = 109 + j250$


after
 $S_{supplied} = S_{load} + (109 + j250) = (509 + j550) 10^3$

$\text{Eff} = \frac{400}{509} = 78\%$ * In p.f. compensation problems, the load voltage is assumed to be fixed!

That $V_i^{\text{RMS}} = 400\text{V}$ before and after compensation.

3 ϕ Power: (cont'd)

3 ϕ Power measurement by two watt meter

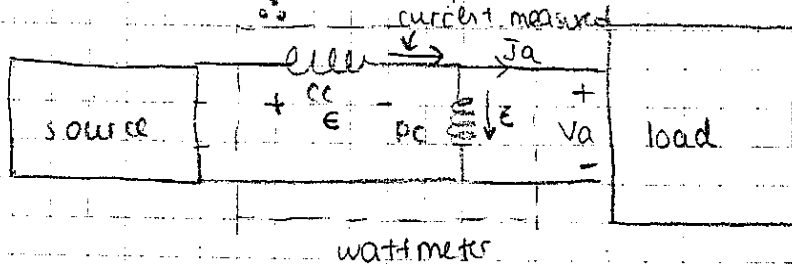


CC: Current coil (measures I_a) [Current coil has low impedance]

PC: Potential coil (measures V_a) [Potential coil has high impedance]

$S_{\text{load}} = V_a I_a^* \rightarrow P_{\text{av}} = \text{Re} \{ V_a I_a^* \}$ Everything expressed after RMS scaling
 ↑ wattmeter measures

$V_{\text{RMS}} = \sqrt{\frac{1}{T} \int_0^T v^2(t) dt}$: effective value is another name for RMS

↑
real number

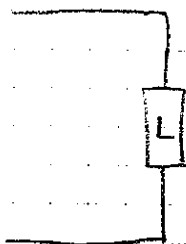

V_{ph} : phasor ← complex power

$V_{\text{ph}} = V_m \angle \theta_L$ V ← conventional phasor


$V_{\text{ph}}^{(2)} = \frac{V_m^{(2)}}{\sqrt{2}} \angle \theta_L^{(2)}$ V_{RMS} ← RMS refers to the scaling of the amplitude by $1/\sqrt{2}$

The value after scaling by $\frac{1}{\sqrt{2}}$

So $V_m^{(2)}$ is not the peak value of the phasor


but its RMS value.

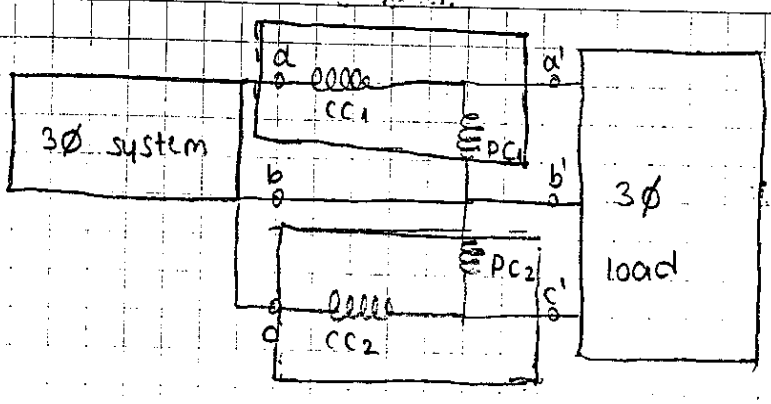$S = \frac{1}{2} V_L I_L^*$ $S = V_L I_L^*$ if V_L and I_L are expressed in RMS



Power measured by wattmeter 1: $\text{Re} \{ V_{ab'} I_{a'}^* \}$
 Wattmeter 2: $\text{Re} \{ V_{c'b'} I_{c'}^* \}$

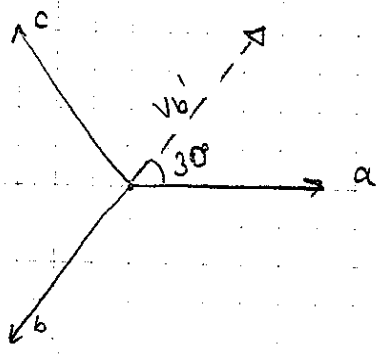• $V_{a'b'} = V_{\text{line}} \angle 30^\circ$ ← why? since we have assumed positive sequence for a-b-c lines.



← positive sequence

• $V_{c'b'} = V_{\text{line}} \angle 90^\circ$
 $I_{a'} = I_{\text{line}} \angle -\theta$
 $I_{c'} = I_{\text{line}} \angle -\theta + 120^\circ$

• $W_1 = \text{Re} \{ V_{a'b'} I_{a'}^* \} = \text{Re} \{ V_{\text{line}} \angle 30^\circ I_{\text{line}} \angle \theta \}$
 $W_2 = \text{Re} \{ V_{c'b'} I_{c'}^* \} = \text{Re} \{ V_{\text{line}} \angle 90^\circ I_{\text{line}} \angle \theta - 120^\circ \}$

$W_1 = V_{\text{line}} I_{\text{line}} \cos(\theta + 30)$


$W_2 = V_{\text{line}} I_{\text{line}} \cos(\theta - 30)$

$W_1 + W_2 = V_{\text{line}} I_{\text{line}} \{ \cos(\theta + 30) + \cos(\theta - 30) \}$
 $= \sqrt{3} V_{\text{line}} I_{\text{line}} \cos(\theta)$


$P_{3\phi}$ consumed by load;

Brief Review of Laplace Transform and s-domain Circuit Analysis:
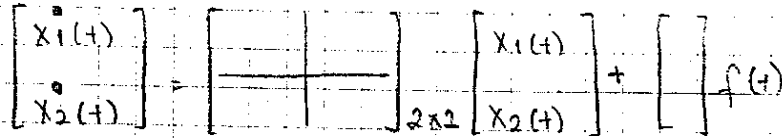
$$(D^2 + 3D + 2)x(t) = f(t) \quad \begin{matrix} x(0^-) = x_0 \\ x'(0^-) = x_0' \end{matrix}$$



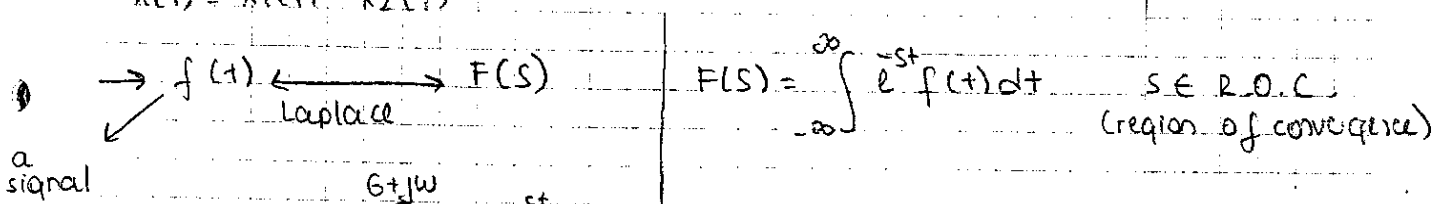
$$\begin{matrix} x(t) = x_2(t) & \text{or} \\ x(t) = x_1(t) - x_2(t) \end{matrix}$$



$$f(t) = \frac{1}{2\pi j} \int_{G-jw}^{G+jw} F(s) e^{st} ds$$

Transform domain:

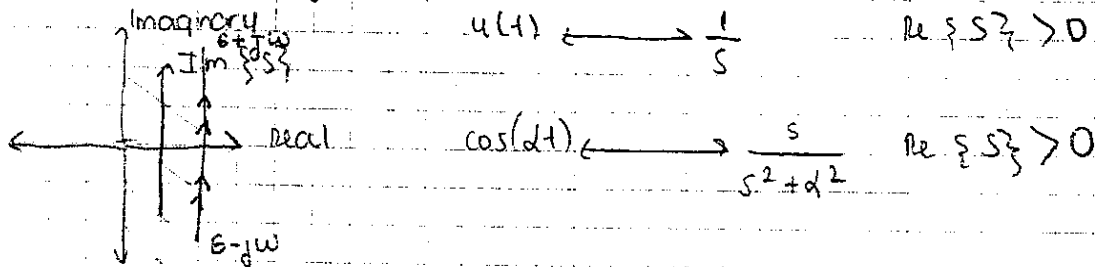

Example: $\mathcal{L}\{u(t)\} = \int_{-\infty}^{\infty} u(t) e^{-st} dt = \int_0^{\infty} 1 \cdot e^{-st} dt = \frac{e^{-st}}{-s} \Big|_{t=0}^{t=\infty}$

↑
Laplace transform

$$= \frac{1}{s} \left[e^{-st} \right]_{t=-\infty}^{t=\infty} = \frac{1}{s} \left[1 - e^{-s \cdot \infty} \right] \Big|_{t=\infty}$$

$$= \begin{cases} \frac{1}{s} [1-0] & \text{Re}\{s\} > 0 \\ -\infty & \text{Re}\{s\} < 0 \end{cases}$$

$$= \frac{1}{s} \text{ for } s \in \text{R.O.C}$$

R.O.C $\text{Re}\{s\} > 0$

$$u(t) \leftrightarrow \frac{1}{s} \quad \text{R.O.C: } \text{Re}\{s\} > 0$$

$$e^{-dt} u(t) \xrightarrow{\text{Lap}} \frac{1}{s+d} \quad \text{R.O.C: } \text{Re}\{s\} > -d$$

$$\int_0^{\infty} e^{-at} e^{-st} dt = \frac{1}{s+a} \quad \begin{matrix} \text{---} (s+a)t \text{---} \\ \downarrow t=0 \\ \downarrow t=\infty \end{matrix} \rightarrow \text{Re}\{s+a\} > 0$$

So that $e^{(s+a)t}$ will be zero
 $\downarrow t=\infty$
 $\text{Re}\{s\} > -a$

Types of Laplace Transforms

- ① Unilateral (one sided) $F(s) = \int_0^{\infty} f(t) e^{-st} dt$
 Suitable for initial value problems
 $(D^2+3D+2)x(t) = f(t)$
- ② Bilateral (two sided) $F(s) = \int_{-\infty}^{\infty} f(t) e^{-st} dt$
 Suitable for general analysis

Unilateral Transform

$$\mathcal{L}\{f'(t)\} = sF(s) - f(0^-); \quad \mathcal{L}\{f'(t)\} = \int_0^{\infty} \overset{dv}{f'(t)} \overset{u}{e^{-st}} dt$$

$$= f(t) e^{-st} \Big|_{t=0}^{t=\infty} + s \int_0^{\infty} f(t) e^{-st} dt$$

$= f(\infty) e^{-s\infty} - f(0^-) + sF(s)$ provided that $F(s)$ has R.O.C.
 to eliminate $e^{-s\infty}$, $\text{Re}\{s\} > 0$
 $= sF(s) - f(0^-)$, ROC for $\mathcal{L}\{f'(t)\} = (\text{ROC of } F(s)) \cap (\text{Re}\{s\} > 0)$

$$\begin{aligned} \rightarrow \mathcal{L}\{f''(t)\} &= \mathcal{L}\{q'(t)\} \quad q(t) = f'(t) \\ &= sG(s) - q(0) = sG(s) - f'(0) = s\mathcal{L}\{f'(t)\} - f'(0) = s(sF(s) - f(0)) - f'(0) \\ &= s^2 F(s) - sf(0) - f'(0) \end{aligned}$$

$$\rightarrow \mathcal{L}\{f^{(4)}(t)\} = s^4 F(s) - s^3 f(0) - s^2 f'(0) - s f''(0) - f'''(0)$$

Example: $(D^2+3D+2)v_c(t) = f(t)$

$v_c(0^-) = v_0$

$\dot{v}_c(0^-) = \dot{v}_0$

Assume a solution exist $V_c(t)$

Then $\mathcal{L}\{V_c(t)\} = V_c(s)$ assume a ROC also

$$\mathcal{L}\left\{\frac{d}{dt} V_c(t)\right\} = sV_c(s) - V_0$$

$$\mathcal{L}\left\{\frac{d^2}{dt^2} V_c(t)\right\} = s^2 V_c(s) - sV_0 - V_0'$$

• Then let's take Laplace transform of $(D^2 + 3D + 2)V_c(t) = f(t)$

$$\mathcal{L}\{D^2 V_c(t)\} + \mathcal{L}\{3D V_c(t)\} + \mathcal{L}\{2V_c(t)\} = F(s)$$

$$s^2 V_c(s) - sV_0 - V_0' + 3sV_c(s) - 3V_0 + 2V_c(s) = F(s)$$

$$V_c(s) [s^2 + 3s + 2] + V_0(-s - 3) - V_0' = F(s)$$

$$V_c(s) = \frac{(s+3)V_0 + V_0'}{s^2 + 3s + 2} + \frac{F(s)}{s^2 + 3s + 2} = \frac{A}{s+1} + \frac{B}{s+2} + \frac{F(s)}{s^2 + 3s + 2}$$

$$V_c(s) = \frac{2V_0 + V_0'}{s+1} + \frac{-V_0 - V_0'}{s+2} + \frac{Fs}{s^2 + 3s + 2}$$

$$\textcircled{1} V_c^{zs}(s) = \frac{F(s)}{s^2 + 3s + 2}$$

$$V_c^{zi}(s) = \frac{2V_0 + V_0'}{s+1} - \frac{-V_0 - V_0'}{s+2}$$


$$\textcircled{2} V_c(t) = \mathcal{L}^{-1}\{V_c(s)\} = (2V_0 + V_0') e^+ u(t) - (V_0 + V_0') e^{-2+} u(t) + \mathcal{L}^{-1}\left\{\frac{F(s)}{s^2 + 3s + 2}\right\}$$

$$V_c^{zi}(t) = \left[(2V_0 + V_0') e^+ - (V_0 + V_0') e^{-2+} \right] u(t)$$

to excite $\lambda = -2$ mode in $V_c^{zi}(t)$, then $V_0 + V_0' = 0$ or

$$\begin{bmatrix} V_0 \\ V_0' \end{bmatrix} \propto \begin{bmatrix} 1 \\ -1 \end{bmatrix}$$

Recitation:

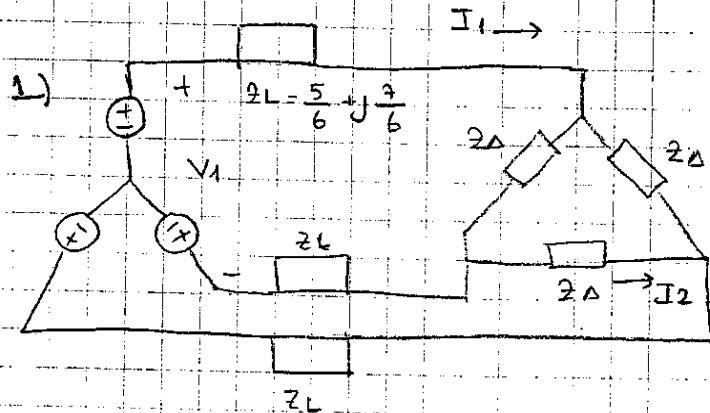

$Z_{\Delta} = ?$ $S_{Source} = ?$

$|V_{l1}| = 150\sqrt{6}$ Vrms

$|I_{21}| = 20\sqrt{3}$ Arms

The total real power

consumed by the inductive load

is 18 kW.

$|I_{l1}| = \sqrt{3} |I_{21}| = 60$ Arms

$|S_{source}| = \sqrt{3} |V_{l1}| |I_{l1}| = \sqrt{3} |V_{l1}| |I_{21}| = 27000\sqrt{2}$ VA

\downarrow $150\sqrt{6}$ \downarrow 60

$S_{source} = S_{line} + S_{load}$

$S_{line} = 3 |I_{l1}|^2 Z_{line} = 3 \cdot 60^2 \cdot \left(\frac{5}{6} + j\frac{3}{6}\right) = 9000 + j12600$ VA


$S_{load} = 18000 + jQ_L$ $Q_L > 0$

$S_{source} = 27000 + j(Q_L + 12600)$ $Q_L + 12600 = 27000$

$Q_L = 14400$ VAR $S_{source} = 27000 + j27000$ VA

$S_{load} = 18000 + j14400$ VA $S_{load, \phi} = 6000 + j4800$

$Z_{\Delta} = \frac{S_{load, \phi}}{|I_{21}|^2} = 5 + j4$

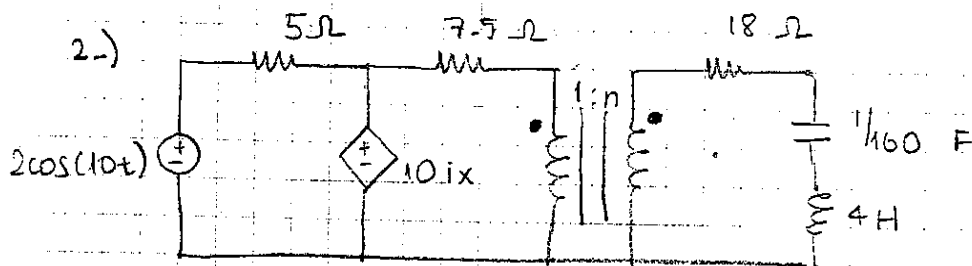


i.) Obtain the thevenin equivalent of the left side

ii.) Find n such that max average power is transferred to the load

iii.) Find the value of average power delivered to the load for the n value in part ii)

Solution:

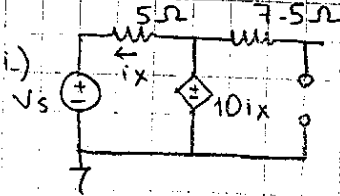


$$V_s = 5i_x$$

$$V_{oc} = 10i_x$$

$$V_{oc} = 2V_s$$

(77)

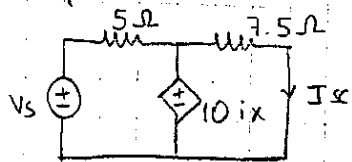


$$V_s = 5i_x$$


$$10i_x = 7.5 I_{sc}$$

$$I_{sc} = \frac{4}{15} V_s$$
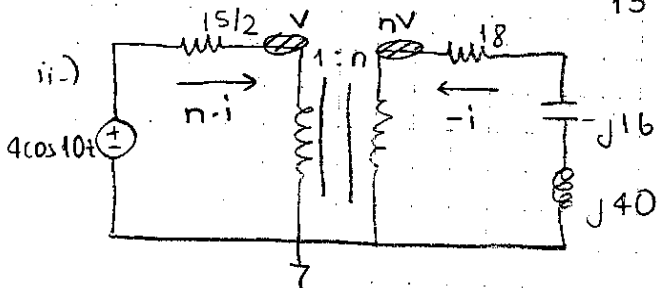
$$R_{th} = \frac{V_{oc}}{I_{sc}} = \frac{15}{2} \Omega$$


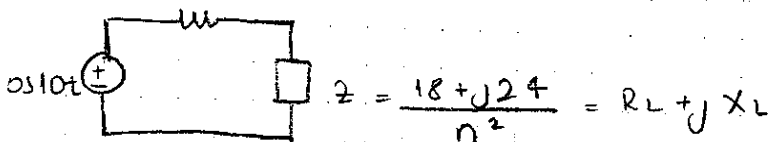
$$\frac{nV}{i} = 18 + j24 \rightarrow \frac{V}{n \cdot i} = \frac{18 + j24}{n^2}$$



$$I = \frac{V_{th}}{R_{th} + R_L + jX_L} \quad P_L = \frac{1}{2} |I|^2 \operatorname{Re}\{R_L + jX_L\}$$

$$P_L = \frac{1}{2} \frac{V_{th}^2}{(R_{th} + R_L)^2 + X_L^2} \cdot R_L \quad \frac{R_L}{(R_L + R_{th})^2 + X_L^2} \text{ must be maximum}$$

$$X_L = \frac{4}{3} R_L \rightarrow f(R_L) = \frac{R_L}{(R_{th} + R_L)^2 + \frac{16}{9} R_L^2} \text{ must be max}$$

$$f'(R_L) = 0 = (R_{th} + R_L)^2 + \frac{16}{9} R_L^2 - R_L \left[\frac{32}{9} R_L + 2(R_{th} + R_L) \right]$$

$$R_{th}^2 - \frac{50}{9} R_L^2 + \frac{25}{9} R_L^2 = 0 \quad R_{th} = \frac{5}{3} R_L$$

$$R_L = \frac{3}{5} \cdot \frac{15}{2} = \frac{9}{2}$$

$$\frac{18}{n^2} = \frac{9}{2} \Rightarrow n = 2$$

$$\text{iii) } P_L = \frac{1}{2} \frac{V_{th}^2}{(R_{th} + R_L)^2 + X_L^2} \cdot R_L$$

$$= \frac{1}{2} \frac{16}{\left(\frac{15}{2} + \frac{9}{2}\right)^2 + 6^2} \cdot \frac{9}{2} = \frac{1}{5} \text{ W}$$

Inverse Laplace Transforms

Partial Fraction Methods

$$1/s \rightarrow u(t)$$

$$1/(s+a) \rightarrow e^{-at} u(t)$$

$$1/(s+a)^2 \rightarrow t e^{-at} u(t)$$

$$k/(s+a)^r \rightarrow \frac{k t^{r-1} e^{-at}}{(r-1)!} u(t)$$

$$\frac{k}{s+a-j\beta} + \frac{k^*}{s+a+j\beta}$$

$$2|k| e^{-at} \cos(\beta t + \theta) u(t)$$

where $k = |k| e^{j\theta}$

$$k^* = |k| e^{-j\theta}$$

1) Distinct Real roots of D(s)

Example: $F(s) = \frac{96(s+5)(s+12)}{s(s+8)(s+6)} = \frac{k_1}{s} + \frac{k_2}{s+8} + \frac{k_3}{s+6}$

$$k_1 = 120, \quad k_2 = -72, \quad k_3 = 48$$

$$L^{-1}\{F(s)\} = 120 u(t) - 72 e^{-8t} u(t) + 48 e^{-6t} u(t)$$

2) Distinct Complex Roots of D(s)

$$F(s) = \frac{100(s+3)}{(s+6)(s^2+6s+25)} = \frac{k_1}{s+6} + \frac{k_2}{s+3+4j} + \frac{k_3}{s+3-4j}$$

$$F(s)(s+6) \Big|_{s=-6} = k_1 = -12$$

$$F(s)(s+3+4j) \Big|_{s=-3-4j} = k_2 = 6+8j$$

$$F(s)(s+3-4j) \Big|_{s=4j-3} = 6-8j = k_3$$

$$L^{-1}\{F(s)\} = -12 e^{-6t} u(t) + 20 e^{-3t} \cos(4t - \tan^{-1}(4/3)) u(t)$$

$\swarrow \quad \searrow \quad \rightarrow \quad \rightarrow \quad \rightarrow$
 $2|k| \quad \alpha \quad \beta \quad \theta$

3) Repeated Real Roots of D(s)

$$F(s) = \frac{100(s+25)}{s(s+5)^3} = \frac{k_1}{s} + \frac{k_2}{(s+5)^3} + \frac{k_3}{(s+5)^2} + \frac{k_4}{(s+5)}$$

$$F(s)s \Big|_{s=0} = k_1 = 20$$

$$k_3 = \frac{d}{ds} \left[F(s)(s+5)^3 \right] \Big|_{s=-5} = -100$$

$$F(s)(s+5)^3 \Big|_{s=-5} = k_2 = -400$$

$$2k_4 = \frac{d^2}{ds^2} \left[F(s)(s+5)^3 \right] \Big|_{s=-5} = -40$$

$$K_4 = -20$$

$$F(s) = \frac{20}{s} - \frac{400}{(s+5)^3} - \frac{100}{(s+5)^2} - \frac{20}{s+5}$$

$$\begin{aligned} \mathcal{L}^{-1}\{F(s)\} &= 20u(t) - \frac{400 + 2e^{-5t}}{2!} u(t) - \frac{100 + e^{-5t}}{1!} u(t) - 20e^{-5t} u(t) \\ &= 20u(t) - 200 + 2e^{-5t} u(t) - 100 + e^{-5t} u(t) - 20e^{-5t} u(t) \end{aligned}$$


4 - Repeated Complex Roots

$$F(s) = \frac{768}{(s^2 + 6s + 25)^2} = \frac{K_1}{(s+3-4j)^2} + \frac{K_2}{s+3-4j} + \frac{K_1^*}{(s+3+4j)^2} + \frac{K_2^*}{s+3+4j}$$

$$K_1 = F(s)(s+3-4j)^2 \Big|_{s=-3+4j} = -12 \quad K_1^* = -12$$

$$K_2 = \frac{d}{ds} \left[F(s)(s+3-4j)^2 \right] \Big|_{s=-3+4j} = -3j \quad K_2^* = +3j$$
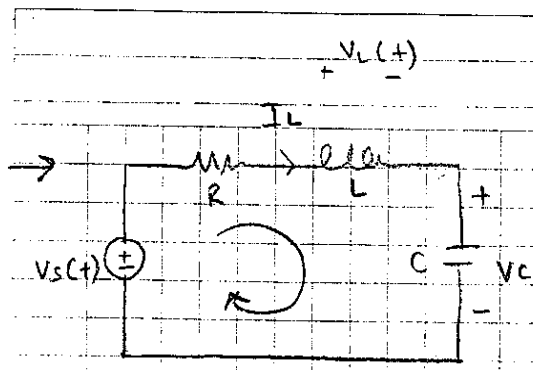
$$F(s) = -12 \left[\frac{1}{(s+3-4j)^2} + \frac{1}{(s+3+4j)^2} \right] + \frac{3 \angle -90^\circ}{s+3-4j} + \frac{3 \angle 90^\circ}{s+3+4j}$$



$V_c(0^-) = V_0$
 $I_L(0^-) = I_0$

KVL: $-V_s(t) + R I_L(t) + L \frac{dI_L(t)}{dt} + V_c(t) u(t) + \frac{1}{C} \int_{0^-}^t I_L(\tau) d\tau = 0$

Laplace Transform
 $V_c(t) \rightarrow 0$
 $V_c(t) \rightarrow 0$
 $L \{ I_L(t) \}$
 $L \{ \int_{0^-}^t I_L(\tau) d\tau \}$

$-V_s(s) + R I_L(s) + L (s I_L(s) - I_L(0^-)) + \frac{V_c(0^-)}{s} + \frac{1}{C} \frac{I_L(s)}{s} = 0$

$V_s(s) = L \{ V_s(t) u(t) \} = \int_0^+ V_s(t) u(t) e^{-st} dt$

$L \left\{ \int_{0^-}^+ x(t') dt' \right\} = \int_{t=0^-}^{\infty} \left(\int_{0^-}^+ x(t') dt' \right) e^{-st} dt$

$= \left(\int_{0^-}^+ x(t') dt' \right) \frac{e^{-st}}{-s} \Big|_{t=0^-}^{t=\infty} - \int_{0^-}^+ x(t) \frac{e^{-st}}{-s} dt$ (Integration by parts)

$= 0 - 0 + \frac{1}{s} X(s) \quad (s \in \text{ROC})$

$= \frac{X(s)}{s}$

$L \{ X'(t) \} = s X(s) - X(0^-)$

$L \{ \int_{0^-}^t x(\tau) d\tau \} = \frac{X(s)}{s}$

$I_L(s) = \frac{C s V_s(s) + s L C I_0 - C V_0}{s^2 L C + R C s + 1}$

response due to initial cond. } zero-input response

$I_L(s) = \frac{\frac{s}{L} V_s(s)}{s^2 + \frac{R}{L} s + \frac{1}{LC}} + \frac{s I_0 - V_0 / L}{s^2 + \frac{R}{L} s + \frac{1}{LC}}$

due to external input: zero state response

complete response in s domain

a- Find unit-step response; (zero state response for unit step input)

$$V_s(s) = \mathcal{L}\{u(t)\} = \frac{1}{s}$$

$$i_L(t) = \mathcal{L}^{-1}\left\{ \frac{s/L V_s(s)}{s^2 + \frac{R}{L}s + \frac{1}{LC}} \right\} \quad \downarrow V_s(s) = 1/s$$

Let $L=1H, R=6\Omega, C=\frac{4}{100}F, I_0=5A, V_0=1V$

$$= \mathcal{L}^{-1}\left\{ \frac{1}{(s+3)^2 + 16} \right\} = \frac{e^{-3t} \sin 4t}{4}$$

$$\bullet \mathcal{L}^{-1}\left\{ \frac{1}{4} \frac{4}{(s+3)^2 + 4^2} \right\} = \frac{1}{4} \mathcal{L}^{-1}\left\{ \frac{4}{(s+3)^2 + 4^2} \right\}$$

$$\bullet \mathcal{L}^{-1}\left\{ \frac{b}{(s+a)^2 + b^2} \right\} = e^{-at} \sin(bt) u(t)$$

$$\bullet \mathcal{L}^{-1}\left\{ \frac{s+a}{(s+a)^2 + b^2} \right\} = e^{-at} \cos(bt) u(t)$$

b- Impulse response (remember all responses are calculated at zero state (zero initial energy) (required due to linearity))

$$h(t) = i_L^{impulse}(t) = \mathcal{L}^{-1}\left\{ \frac{\frac{s}{L} V_s(s)}{s^2 + \frac{R}{L}s + \frac{1}{LC}} \right\} \quad \downarrow V_s(s) = \mathcal{L}\{\delta(t)\} = 1$$

$$= \mathcal{L}^{-1}\left\{ \frac{s+3-3}{(s+3)^2 + 4^2} \right\} = e^{-3t} \cos 4t - \frac{3}{4} e^{-3t} \sin 4t$$

$$= \frac{1}{4} e^{-3t} (4 \cos 4t - 3 \sin 4t) u(t)$$

$$= \frac{5}{4} e^{-3t} \cos(4t + \tan^{-1}(3/4)) u(t)$$

c- Doublet response

$$f'(t) = \text{Doublet} = \frac{d}{dt} f(t)$$


$$\mathcal{L}\{f'(t)\} = s$$

$$i_L^{\text{doublet}}(t) = \mathcal{L}^{-1} \left\{ \frac{s^2}{(s+3)^2 + 4^2} \right\} = \mathcal{L}^{-1} \left\{ 1 + \frac{-6s-25}{(s+3)^2 + 4^2} \right\} \quad (82)$$

$$= f(t) - \mathcal{L}^{-1} \left\{ \frac{6s+25}{(s+3)^2 + 4^2} \right\} = f(t) - \mathcal{L}^{-1} \left\{ \frac{6(s+3)}{(s+3)^2 + 4^2} + \frac{7}{(s+3)^2 + 4^2} \right\}$$

$$= \left(f(t) - 6e^{-3t} \cos 4t - \frac{7}{4} e^{-3t} \sin 4t \right) u(t)$$

→ (cont'd)

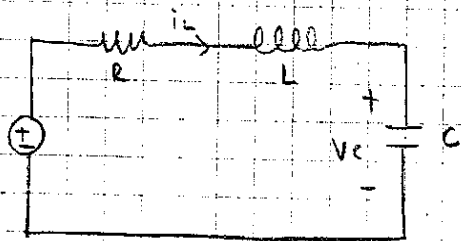

Laplace Transform

$$\begin{bmatrix} v_C(t) \\ i_L(t) \end{bmatrix} = \begin{bmatrix} 0 & 1/C \\ -1/L & -R/L \end{bmatrix} \begin{bmatrix} v_C(t) \\ i_L(t) \end{bmatrix} + \begin{bmatrix} 0 \\ 1/L \end{bmatrix} v_s(t)$$

$$\begin{bmatrix} s v_C(s) - v_C(0^-) \\ s i_L(s) - i_L(0^-) \end{bmatrix} = \begin{bmatrix} 0 & 1/C \\ -1/L & -R/L \end{bmatrix} \begin{bmatrix} v_C(s) \\ i_L(s) \end{bmatrix} + \begin{bmatrix} 0 \\ 1/L \end{bmatrix} v_s(s)$$

$$= s \begin{bmatrix} v_C(s) \\ i_L(s) \end{bmatrix} - \begin{bmatrix} v_C(0^-) \\ i_L(0^-) \end{bmatrix} = \begin{bmatrix} \underline{A} \\ \underline{b} \end{bmatrix} \begin{bmatrix} v_C(s) \\ i_L(s) \end{bmatrix} + \begin{bmatrix} 0 \\ \underline{b} \end{bmatrix} v_s(s)$$

$$(s \underline{I} - \underline{A}) \begin{bmatrix} v_C(s) \\ i_L(s) \end{bmatrix} = \begin{bmatrix} v_0 \\ i_0 \end{bmatrix} + \begin{bmatrix} \underline{b} \end{bmatrix} v_s(s)$$

$$\begin{bmatrix} v_C(s) \\ i_L(s) \end{bmatrix} = \underbrace{(s \underline{I} - \underline{A})^{-1} \begin{bmatrix} v_0 \\ i_0 \end{bmatrix}}_{\text{zero input}} + \underbrace{(s \underline{I} - \underline{A})^{-1} \underline{b} v_s(s)}_{\text{zero state}} \leftarrow \text{general form of solution}$$

Complete response
in s domain

• Let's find step response from state eqn system

Step response $\rightarrow V_o = 0, I_o = 0, V_s(s) = 1/s$

$$\begin{bmatrix} V_c(s) \\ I_L(s) \end{bmatrix} = (sI - A)^{-1} \underline{b} V_s(s) \leftarrow 1/s$$

$$A = \begin{bmatrix} 0 & 25 \\ -1 & -6 \end{bmatrix}; \quad b = \begin{bmatrix} 0 \\ 1 \end{bmatrix} \quad L=1 \quad R=6 \quad C = \frac{4}{100}$$

$$\begin{bmatrix} V_c(s) \\ I_L(s) \end{bmatrix} = \frac{1}{s} \begin{bmatrix} s & -25 \\ 1 & s+6 \end{bmatrix}^{-1} \begin{bmatrix} 0 \\ 1 \end{bmatrix} = \frac{1}{s \Delta} \begin{bmatrix} s+6 & 25 \\ -1 & s \end{bmatrix} \begin{bmatrix} 0 \\ 1 \end{bmatrix}$$

$$\Delta = s^2 + 6s + 25$$

$$\begin{bmatrix} V_c(s) \\ I_L(s) \end{bmatrix} = \frac{1}{s(s^2 + 6s + 25)} \begin{bmatrix} 25 \\ s \end{bmatrix}$$

$$V_c^{STEP}(s) = \frac{25/s}{s^2 + 6s + 25}$$


$$I_L^{STEP}(s) = \frac{1}{s^2 + 6s + 25}$$

Circuit Components in s Domain

Capacitor

time domain


s domain

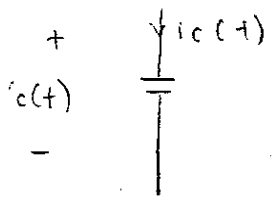

$$i_c(t) = C \frac{d}{dt} V_c(t) \rightarrow i_c(s) = C[sV_c(s) - V_c(0^-)]$$

$$V_c(t) = V_c(0^-) + \int_0^t i_c(\tau) d\tau \rightarrow V_c(s) = \frac{V_c(0^-)}{s} + \frac{I_c(s)}{Cs}$$

$$V_c(0^-) = V_o$$

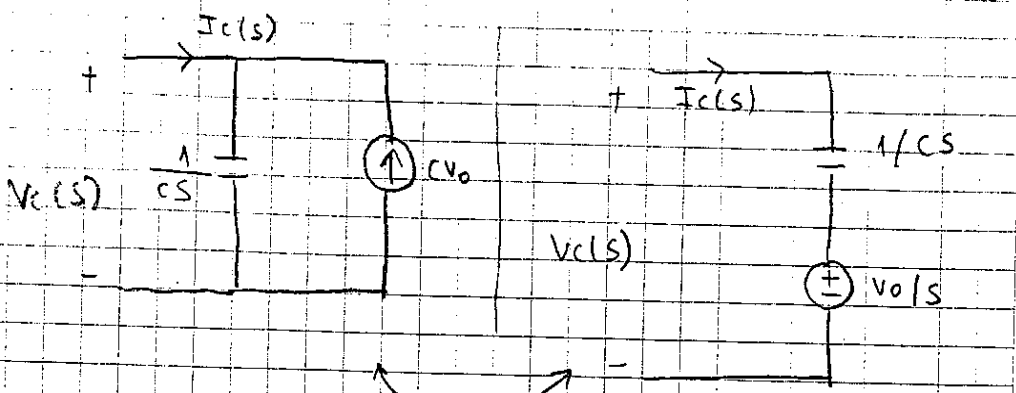


Source transformation

Inductor:

Time domain

Laplace Domain


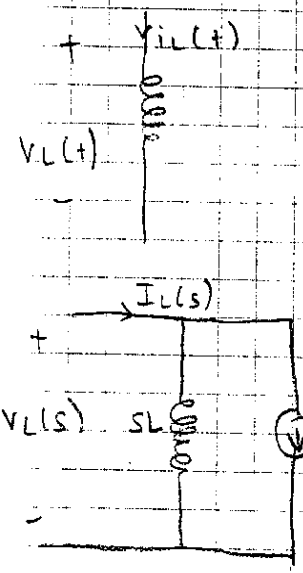


$$V_L(t) = L \frac{d}{dt} i_L(t)$$

$$i_L(0^-) = I_0$$

$$V(s) = L(sI_L(s) - I_0)$$

source transformation

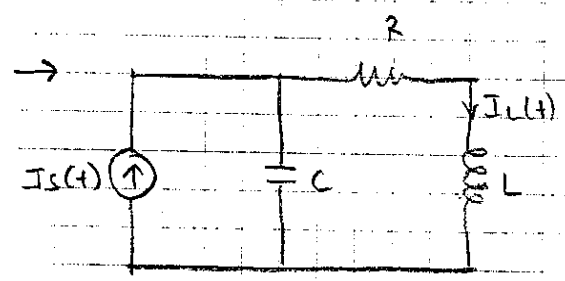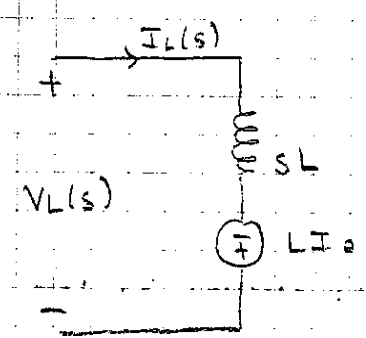


$$V_C(0^-) = V_0$$

$$I_L(0^-) = I_0$$

Find $I_L(t)$

zero state

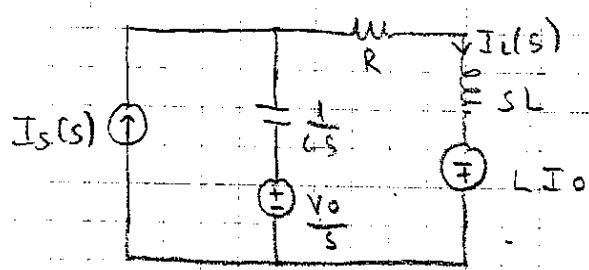

$$I_L(s) = I_S(s) \frac{1/sC}{1/sC + R + sL} +$$

$$\frac{V_0}{s} \frac{1}{R + sL + 1/sC} + LI_0 \frac{1}{R + sL + 1/sC}$$

zero input

$$V_X(s) = (R + sL) I_L(s) - LI_0$$


Note $V_X(s)$ is the branch of the capacitor so it is the cap voltage

Poles and Zeros in Sdomain

$$X(s) = K \frac{\prod_{i=1}^z (s - z_i)}{\prod_{i=1}^p (s - p_i)}$$

$$X(z_i) = 0$$

$$X(p_i) \rightarrow \infty$$

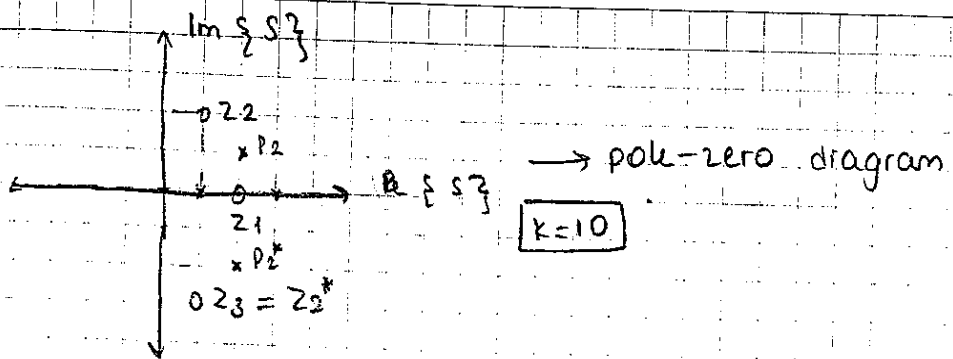

$K=10$


$P(s) = s^2 + 3s + 2 = 0$

$P(z_1) = 0 \rightarrow P(z_1)^* = 0^* = 0$


$(z_1^2 + 3z_1 + 2)^* = 0$

$P(z_1^*) = 0 \leftarrow (z_1^*)^2 + 3(z_1^*) + 2 = 0$





Interpretation of Pole-zero diagrams

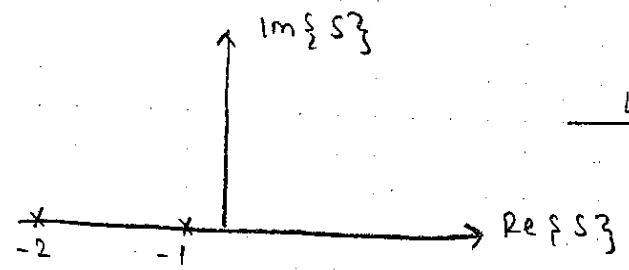

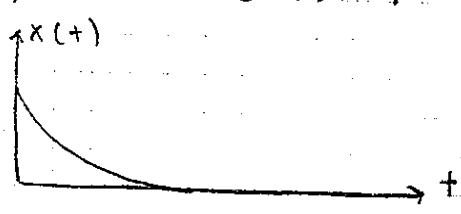$L^{-1}\{ \} \rightarrow x(t) = (Ae^{-t} + Be^{-2t})u(t)$



$x(s) = K \frac{1}{(s+1)(s+2)}$

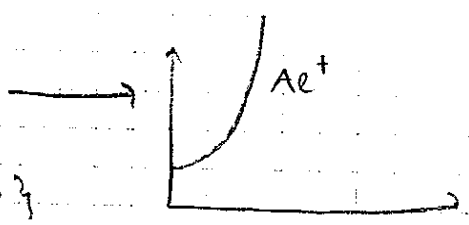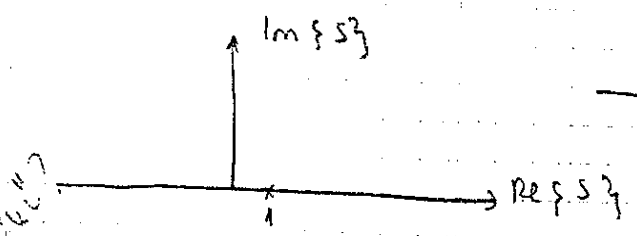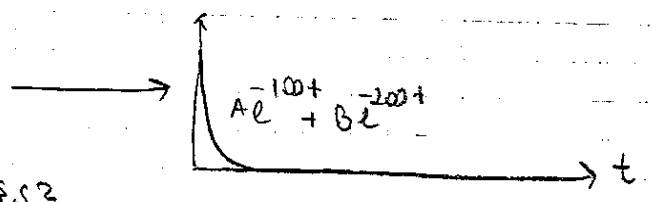
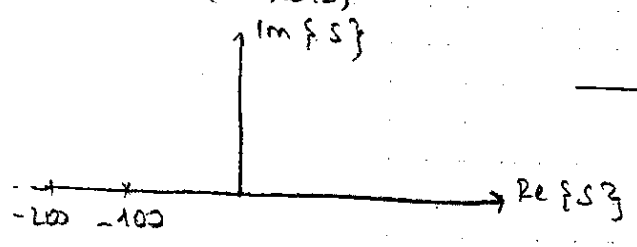


$x(s) = K \frac{1}{[s - (-1 + j2)][s - (-1 - j2)]}$


$= \frac{K}{(s+1)^2 + 4}$

$x(t) = Ae^t \cos 2t + Be^t \sin 2t$

$1, -1 \pm j2$

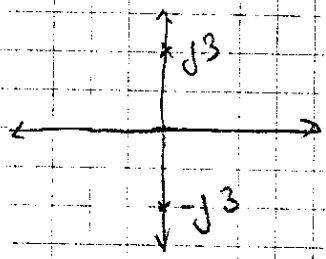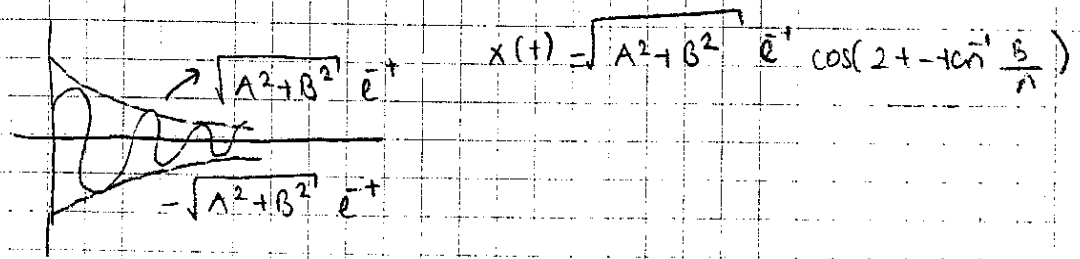


$\mathcal{L}^{-1}\{ \}$

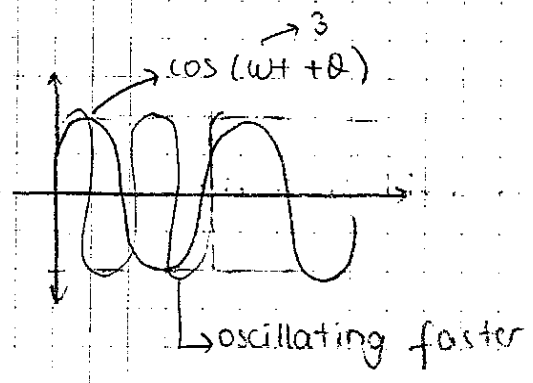


$$x(s) = k \frac{1}{s^2 + 9}$$

→ Mesh analysis in s-domain

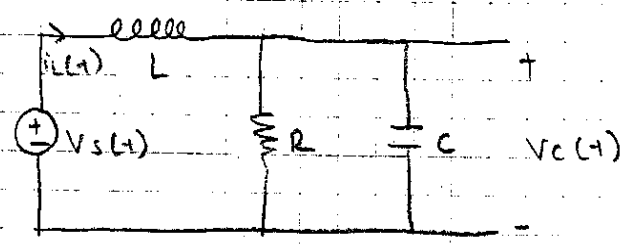

$$i_L(0^-) = I_0$$

$$V_c(0^-) = V_0$$

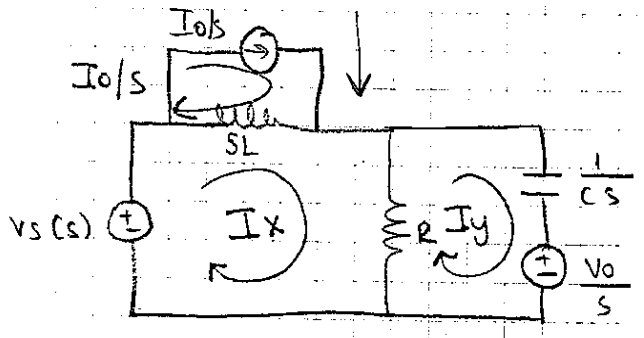

$$\begin{bmatrix} sL + R & -R \\ -R & R + \frac{1}{sC} \end{bmatrix} \begin{bmatrix} I_x(s) \\ I_y(s) \end{bmatrix} = \begin{bmatrix} I_0 L + V_s(s) \\ -\frac{V_0}{s} \end{bmatrix}$$

$$I_x(s) = \left(\frac{1}{RC} + \frac{s}{L} \right) \frac{V_s(s)}{s^2 + \frac{1}{RC}s + \frac{1}{LC}} + \frac{\frac{I_0}{RC} + \frac{V_0}{L} + sI_0}{s^2 + \frac{1}{RC}s + \frac{1}{LC}}$$

complete response

zero-state

two-input

Note: $I_x(s) = I_L(s)$ of charged inductor

$I_x(s)$: with initial energy

zero state solution; $I_L(s) = \frac{\frac{1}{RCL} + \frac{s}{L}}{s^2 + \frac{1}{RC}s + \frac{1}{LC}} V_s(s)$

$\Rightarrow \left(s^2 + \frac{1}{RC}s + \frac{1}{LC} \right) I_L(s) = \left(\frac{1}{RCL} + \frac{s}{L} \right) V_s(s)$

$\rightarrow L^{-1} \{ \} (D^2 + 1/RC D + 1/LC) i_L(t) = \frac{1}{RCL} v_s(t) + \frac{1}{L} D v_s(t)$

Powerla ilgili hatırlatma

$V_s(t) = 2 \cos(\omega t + 45^\circ) \text{ V} \rightarrow 2 \angle 45^\circ \rightarrow \sqrt{2} + j\sqrt{2} \text{ V}$

$V_s(t) = \frac{2}{\sqrt{2}} \cos(\omega t + 45^\circ) \text{ V}_{rms} \rightarrow \frac{2}{\sqrt{2}} \angle 45^\circ$


$S = \frac{1}{2} V I^* = V_{rms} I_{rms}^* = V_{rms} I_{rms}^*$

Initial Value, Final Value Theorem

Initial Value; $\lim_{t \rightarrow 0} f(t) = \lim_{s \rightarrow \infty} s F(s)$ $s \rightarrow \infty$ s should be in ROC

Final Value; $\lim_{t \rightarrow \infty} f(t) = \lim_{s \rightarrow 0} s F(s)$ $s = 0$ s should be in ROC

provided that this limit exists.

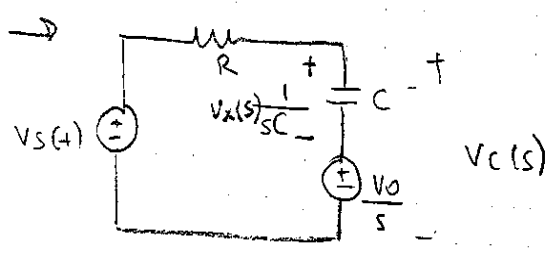

$V_c(s) = \frac{V_0}{s} + V_x(s) = \frac{V_0}{s} + \left(V_s(s) - \frac{V_0}{s} \right) \frac{1/s}{sRC + 1}$

$V_c(s) = \frac{V_0}{s} \left(1 - \frac{1}{1+sRC} \right) + \frac{1}{1+sRC} V_s(s)$

$V_c^{zi}(s) = \frac{V_0}{s} \left(1 - \frac{1}{1+sRC} \right)$; $V_c^{zs}(s) = \frac{1}{1+sRC} V_s(s)$

$\lim_{s \rightarrow \infty} s V_c^{zi} = V_0 \leftarrow V_c^{zi}(0^+)$

$V_c^{zs}(t) = \frac{1}{1+sRC} V_s(s)$; $V_s(t) = u(t) \rightarrow V_s(s) = \frac{1}{s}$

$\lim_{s \rightarrow 0} V_c^{zi}(s) = V_0 \leftarrow V_c^{zi}(0^+)$

$$\mathcal{L}\{e^{-t}\} = \frac{1}{s+1} \rightarrow f(0^+) = 1$$

$$\lim_{s \rightarrow \infty} sF(s) = 1$$



$f(t)$ $F(s)$

$$\mathcal{L}\{\cos t\} = \frac{s}{s^2+1} \rightarrow f(0^+) = 1$$

$$\lim_{s \rightarrow \infty} sF(s) = 1$$

$$\mathcal{L}\{\cos t\} = \frac{s}{s^2+1} \rightarrow f(\infty) = ?$$
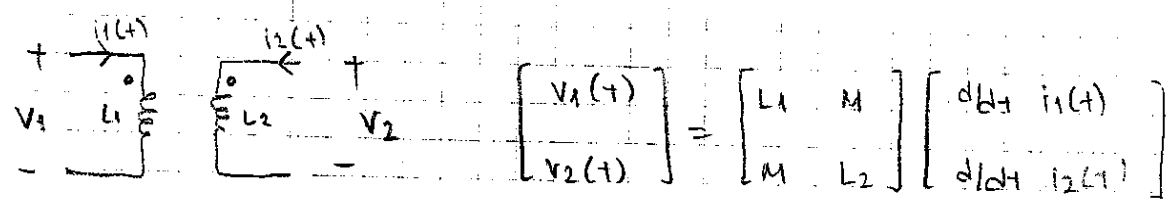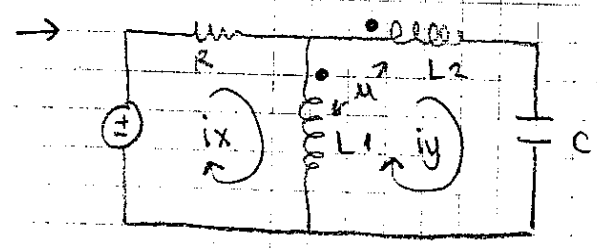
$$\lim_{s \rightarrow \infty} sF(s) = 0$$




$$\begin{bmatrix} V_1(s) \\ V_2(s) \end{bmatrix} = \begin{bmatrix} L_1 & M \\ M & L_2 \end{bmatrix} \begin{bmatrix} sI_1(s) - i_1(0^-) \\ sI_2(s) - i_2(0^-) \end{bmatrix}$$

$i_1 - i_2$ domain

KVL i_1 ; $-V_s(s) + R i_1(s) + V_1(s) = 0$


KVL i_2 ; $\frac{1}{sC} i_2(s) - V_1(s) + V_2(s) = 0$

Network Functions:
Linear time invariant

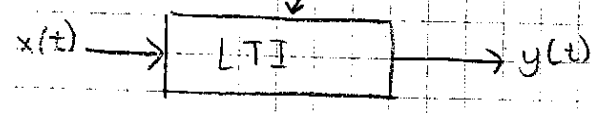

$$H(s) = \frac{\mathcal{L}\{y^{zs}(t)\}}{\mathcal{L}\{x(t)\}}$$

zerostate

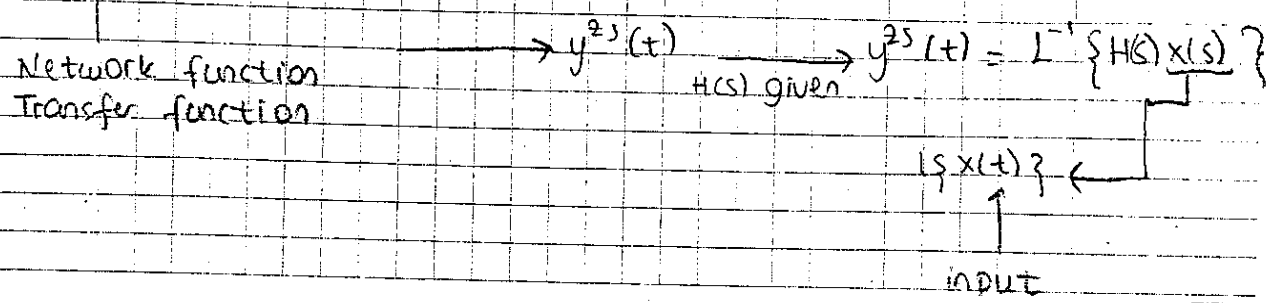


* zero state responses

$$H(s) = \frac{I_L^{zs}(s)}{V_s(s)} = \frac{s}{s+1} \text{ is given}$$

$$(s+1)I_L^{zs}(s) = sV_s(s)$$

$L^{-1}\{ \}$
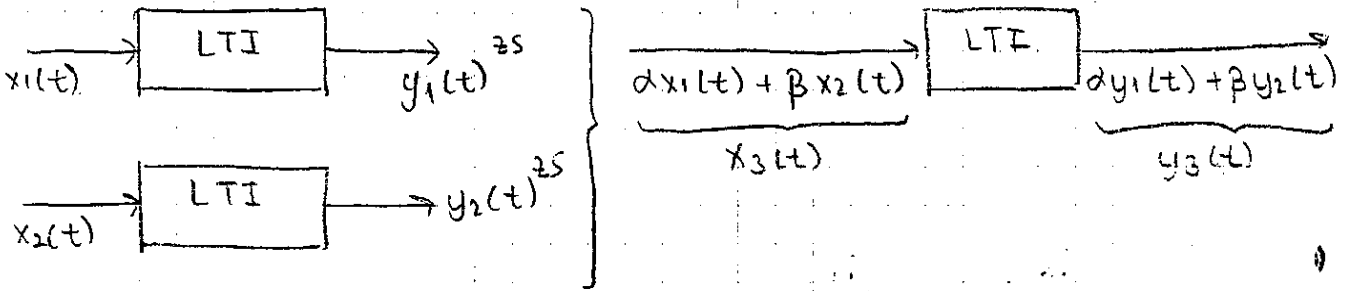
$$\frac{d}{dt} I_L^{zs}(t) + I_L^{zs}(t) = \frac{d}{dt} V_s(t) \quad \rightarrow \text{Note that: ICs are zero.}$$




$$Y_3^{zs}(s) = H(s) X_3(s)$$

proportionality "constant"


$$= H(s) [\alpha X_1(s) + \beta X_2(s)] = \alpha Y_1^{zs}(s) + \beta Y_2^{zs}(s)$$

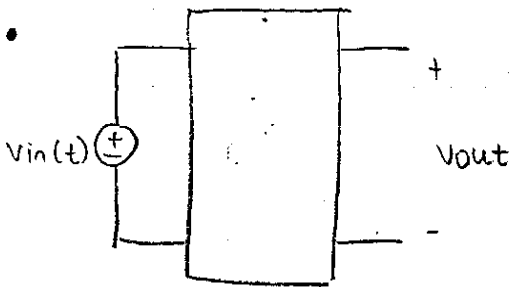"Superposition is only valid in zero state responses"




$$H_v(s) = \frac{V_{out}(s)}{V_{in}(s)}$$

voltage transfer function

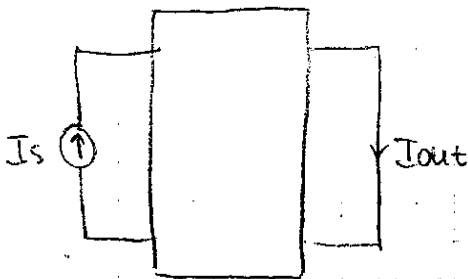



$$\frac{I_{out}(s)}{I_{in}(s)}$$

current transfer function

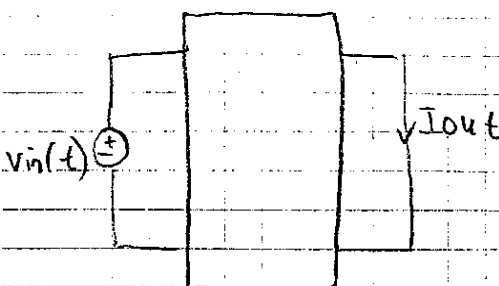

$$\frac{I_{out}(s)}{V_{in}(s)}$$

transfer admittance

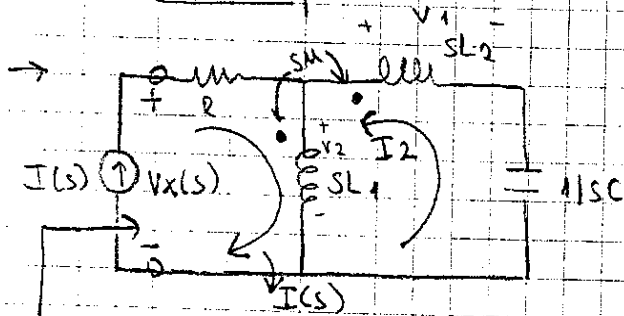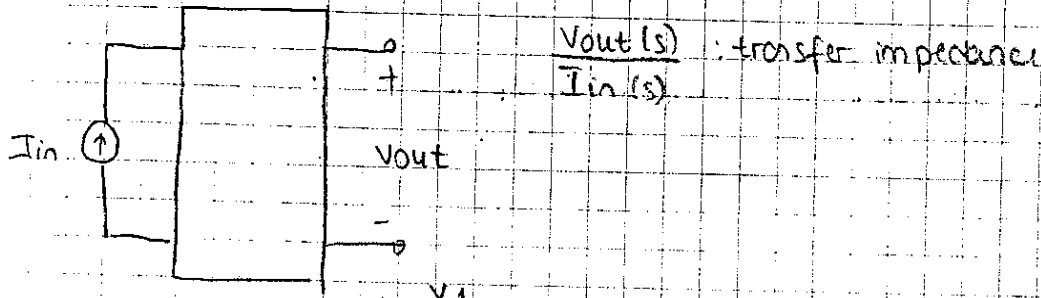

$Z(s)$: transfer impedance (All initial conditions are zero) \downarrow
demek

$$Z(s) = \frac{V_x(s)}{I_{in}(s)}$$

KVL around I_2 loop:

$$I_2 \frac{1}{sC} - V_1(s) + V_2(s) = 0$$

$$\begin{bmatrix} V_1(s) \\ V_2(s) \end{bmatrix} = \begin{bmatrix} sL_1 & sM \\ sM & sL_2 \end{bmatrix} \begin{bmatrix} -I_2(s) \\ I_2(s) + I_{in}(s) \end{bmatrix}$$

$$V_2(s) - V_1(s) = -sM I_2(s) + sL_2 [I_2(s) + I_{in}(s)] + sL_1 I_2(s) - sM [I_2(s) + I_{in}(s)]$$

$$= s [I_2(s) + I_{in}(s)] (L_2 - M) + I_2(s) s (L_1 - M)$$

$$= I_2(s) [s(L_1 + L_2 - 2M)] + I_{in}(s) \cdot s(L_2 - M)$$

Putting KVL equation;

$$I_2(s) \left[\frac{1}{sC} + s(L_1 + L_2 - 2M) \right] + I_{in}(s) \cdot s(L_2 - M) = 0$$


$$I_2(s) = \frac{s(M - L_2) I_{in}(s)}{\frac{1}{sC} + s(L_1 + L_2 - M)} = \frac{s(L_2 - M) I_2}{I_{in}} \cdot \frac{s(M - L_2)}{s(M - L_2)}$$

$$V_x(s) = I_{in}(s) R + V_2(s)$$

$$= I_{in}(s) R + s I_2(s) (L_2 - M) + s L_2 I_{in}(s)$$

$$\frac{V_x(s)}{I_{in}(s)} = \frac{R + sL_2}{s^2(L_2 - M)^2} = \frac{1}{sC + s(L_1 + L_2 - 2M)}$$


Network Function and Impulse Response

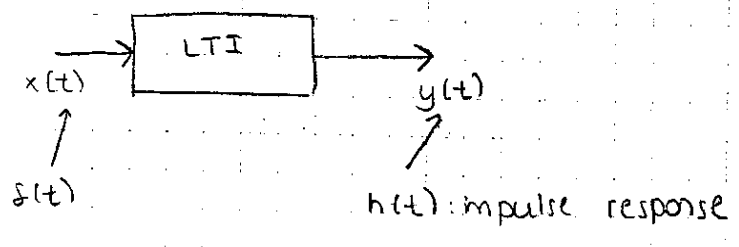

$$\frac{Y^{zs}(s)}{X(s)} = H(s) = \frac{\mathcal{L}\{y^{zs}(t)\}}{\mathcal{L}\{x(t)\}} = \frac{\mathcal{L}\{h(t)\}}{1}$$

↓
δ(t)

• $h(t) = \mathcal{L}^{-1}\{H(s)\}$

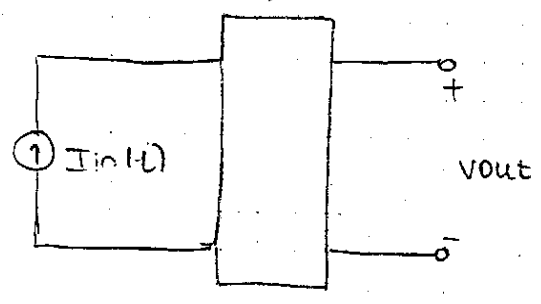

$$v_{out}(s) = H(s) \cdot I_{in}(s)$$

↓ $\mathcal{L}^{-1}\{\}$


$$v_{out}(t) = \int_{-\infty}^{\infty} h(\tau) I_{in}(t-\tau) d\tau$$

convolution operator
convolution integral

$h(t) * I_{in}(t)$
↳ convolution operator


About convolution integral;

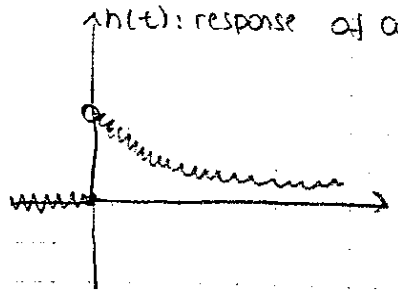$h(t)$: response of an LTI circuit to $\delta(t)$



$$h(t) = \begin{cases} 0 & t < 0 \\ \dots & t > 0 \end{cases}$$

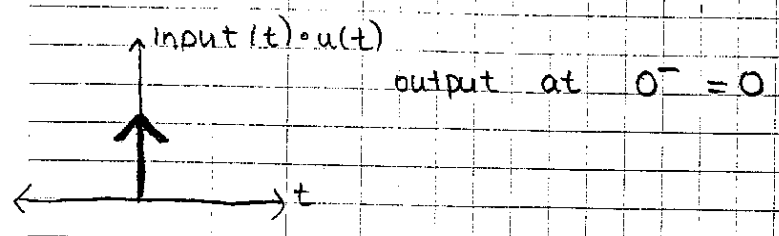Systems with $h(t) = 0$ for $t > 0$ are called causal systems.



$$V_{out}(t) = \left(\int_{-\infty}^0 + \int_0^t + \int_t^{\infty} \right)$$

$$\int_{-\infty}^0 h(\tau) I_{in}(t-\tau) d\tau = 0$$

↓ (causality)

$$\int_t^{\infty} h(\tau) I_{in}(t-\tau) d\tau =$$


↓
I_{in}(negative argument)
or zero

$$I_{in}(t) = f(t) u(t)$$

$$\int_t^{\infty} h(\tau) I_{in}(t-\tau) u(t-\tau) d\tau = 0$$

$$V_{out}(t) = \int_0^t h(\tau) I_{in}(t-\tau) d\tau \quad \text{for causal systems}$$

Step Response:

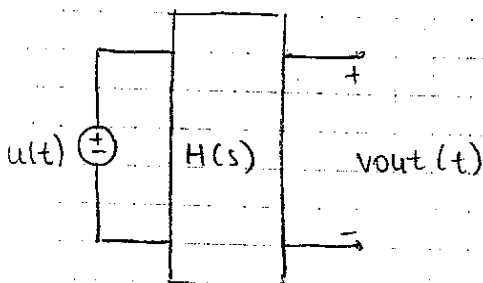


$$\overset{\text{step}}{V_{out}(s)} = V_{out}(s) = H(s) \cdot \frac{1}{s}$$

$$\overset{\text{step}}{V_{out}(t)} = \int_{-\infty}^t h(\tau) d\tau = \int_0^t h(\tau) d\tau$$

$$\overset{\text{step}}{V_{out}(t)} = \int_0^t h(\tau) \underbrace{V_{in}(t-\tau)}_{u(t-\tau)=1} d\tau = \int_0^t h(\tau) d\tau$$

(convolution)

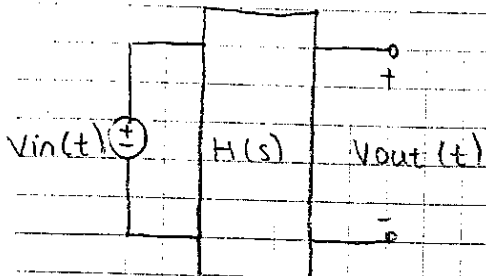Sinusoidal Steady-State Response and H(s):



$$H(s) = \frac{V_{out}(s)}{I_{in}(s)} \rightarrow V_{out}(s) = H(s) I_{in}(s)$$

$$V_{out} = ?$$

(I am only interested in the steady

$$V_{in}(t) = A \cos(\omega t + \phi)$$

state part of $V_{out}(t)$)

$$L\{v_{in}(t)\} = L\{A(\cos\omega t \cos\phi - \sin\omega t \sin\phi)\}$$

$$= A \frac{s \cos\phi - \omega \sin\phi}{s^2 + \omega^2}$$

$$V_{out}(s) = H(s) A \frac{s \cos\phi - \omega \sin\phi}{s^2 + \omega^2}$$

$$= \underbrace{\left(\frac{K}{s-j\omega} + \frac{K^*}{s+j\omega} \right)}_{\text{steady state response due to cosine}} + \left(\frac{A_1}{s-\lambda_1} + \frac{A_2}{s-\lambda_2} + \dots + \frac{A_n}{s-\lambda_n} \right)$$

(natural frequency of poles of H(s))
 $\text{Re}\{\lambda\} < 0$

$$K = H(s) A \frac{s \cos\phi - \omega \sin\phi}{s^2 + \omega^2} \Big|_{s=j\omega}$$

$$K = H(j\omega) \frac{j\omega \cos\phi - \omega \sin\phi}{2j\omega} A$$

$$K = H(j\omega) \frac{A}{2} (\cos\phi + j \sin\phi) = H(j\omega) \frac{A}{2} e^{j\phi}$$

$$V_{out}(t) = L^{-1} \left\{ \frac{K}{s-j\omega} + \frac{K^*}{s+j\omega} \right\}$$


$$= K e^{j\omega t} + K^* e^{-j\omega t}$$

$$= 2 \text{Re} \left\{ K e^{j\omega t} \right\}$$

$$= 2 \text{Re} \left\{ |K| e^{j\Delta} e^{j\omega t} \right\} = 2 \text{Re} \left\{ \|H(j\omega)\| \frac{A}{2} e^{j(\omega t + \Delta + H(j\omega) + \phi)} \right\}$$

$$V_{out}(t) = \text{Re} \left\{ \|H(j\omega)\| A e^{j(\omega t + \Delta + H(j\omega) + \phi)} \right\}$$

If I have;

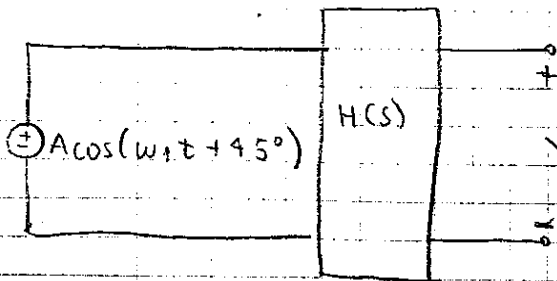


$$H(s) = \frac{1}{s+1} \quad | \quad H(j\omega)$$

$$= \frac{1}{j\omega + 1}$$

$$\|H(j\omega)\| \cos(\omega t + 45 + \Delta + H(j\omega))$$

Frequency Response:

94

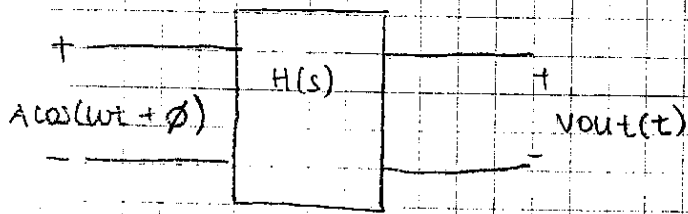

$$v_{out} = \underbrace{A |H(j\omega)|}_{\text{amplitude of the output}} \cos(\omega t + \phi + \underbrace{\angle H(j\omega)}_{\text{phase of the output}})$$



$$\text{Gain} = |H(j\omega)|$$

↑ amplitude gain/loss


$\angle H(j\omega)$ = phase response

Types of Filters:

$|H(j\omega)|$: magnitude response

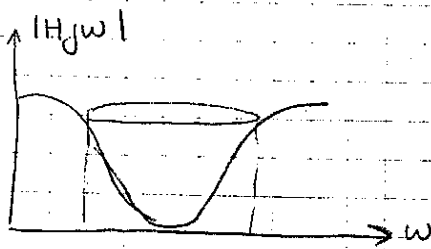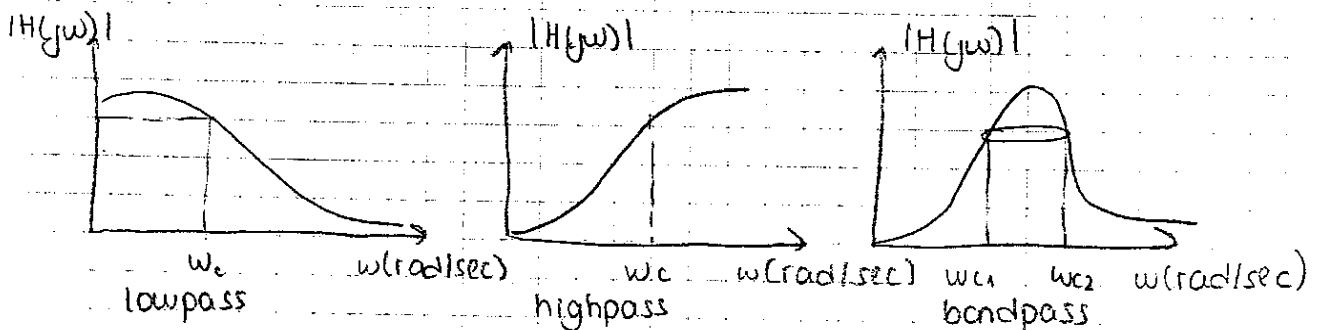


Band stop

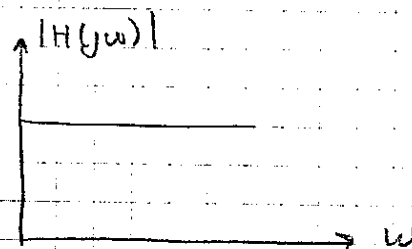


All pass

Decibel:

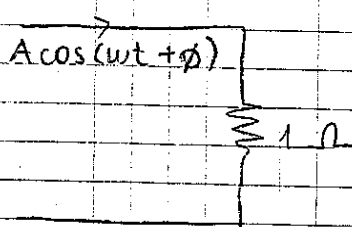
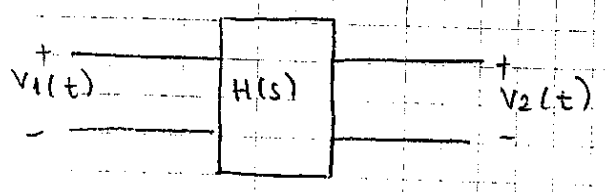
$$P_{1\Omega} = \frac{A^2}{2} R \rightarrow 1 \Omega$$




Power at the input and output is at interest

Decibel: $10 \log_{10} \frac{\text{Power at the input}}{\text{Power at the output}} = 10 \log |H(j\omega)|^2$

can be written as $20 \log |H(j\omega)|$

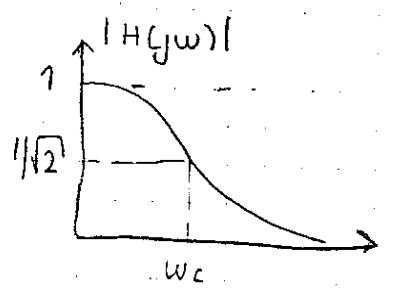Decibel is a relation between powers at input and output
(Decibel is about power)




Lowpass critical frequency, half power freq, cut off frequency
3dB frequency

$ H(j\omega) ^2$	$10 \log_{10} H(j\omega) ^2$
1	0
2	3 dB
3	4.77 dB
4	6 dB
5	7 dB
6	7.77
7	8.45
8	9 dB
9	9.54
10	10

$10 \log 2 = 3$


$10 \log (1/2) = -3 \text{ dB}$

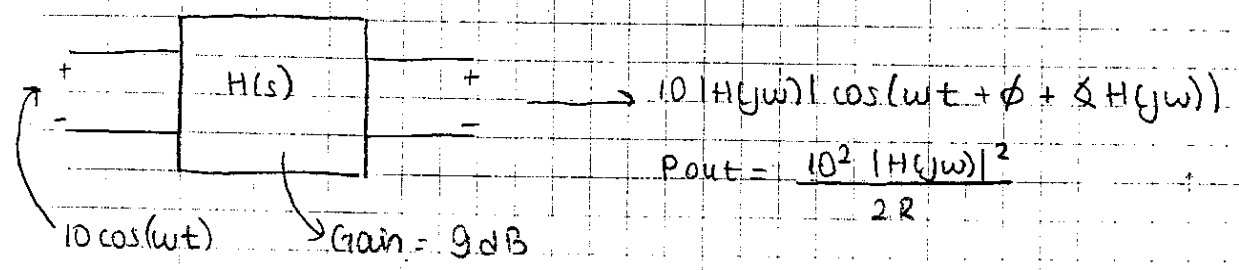

$|H(j\omega)|^2 = 5 \text{ dB} = 3.5$ $|H(j\omega)| = \sqrt{3.5}$


$P_{in} = \frac{10^2}{2R} = 50 \text{ watts} = 17 \text{ dB}$

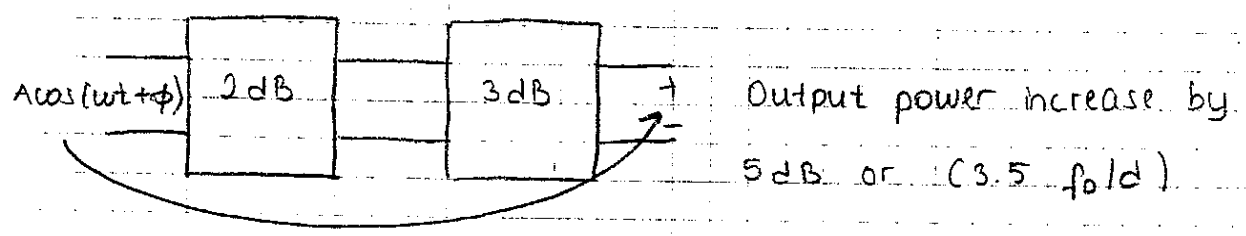$(P_{out})_{dB} = (P_{in})_{dB} + (\text{gain})_{dB}$



Frequency Response of 1st Order Systems

a.) Lowpass

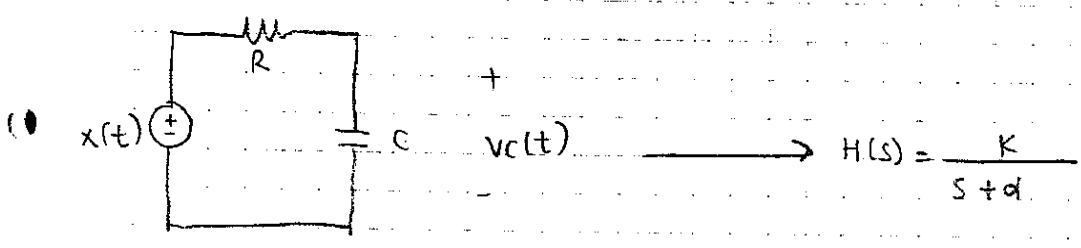

$H(s) = \frac{1/sC}{1/sC + R} = \frac{1}{1 + sCR} = \frac{1/RC}{s + 1/RC}$


where $K = 1/RC$ and $d = 1/RC$

$|H(j\omega)| = ? \rightarrow |H(j\omega)| = \frac{|K|}{\sqrt{d^2 + \omega^2}}$
 $\angle H(j\omega) \rightarrow \angle K - \tan^{-1}(\omega/d)$

when $K < 0 \rightarrow \angle K = 180$

$K > 0 \rightarrow \angle K = 0$


$$|H(j\omega)| = \frac{|K|}{\omega \sqrt{\left(\frac{\omega}{d}\right)^2 + 1}} = \frac{|K|}{d \sqrt{1 + \left(\frac{\omega}{d}\right)^2}}$$

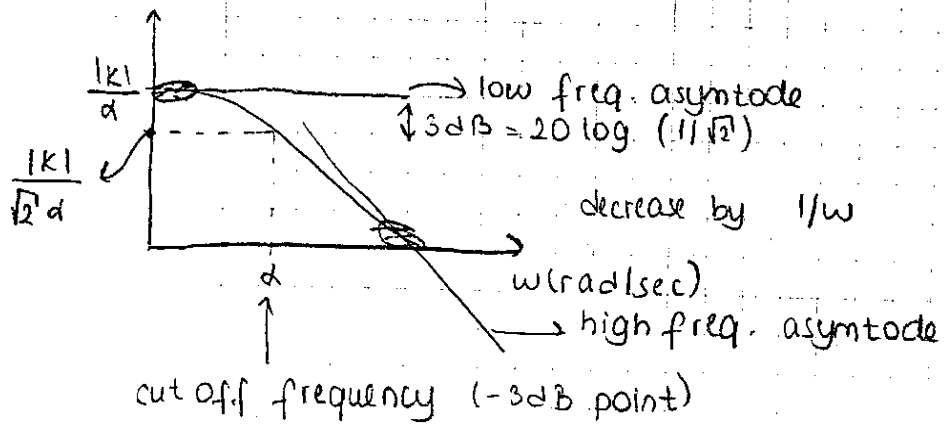


i-) $\frac{\omega}{d} \ll 1 \rightarrow (\omega \ll d)$

ii-) $\frac{d}{\omega} \ll 1 \rightarrow |H(j\omega)| \approx \frac{|K|}{\omega}$

Two asymptotes meet at $\frac{|K|}{d} = \frac{|K|}{\omega} \rightarrow \omega = d$


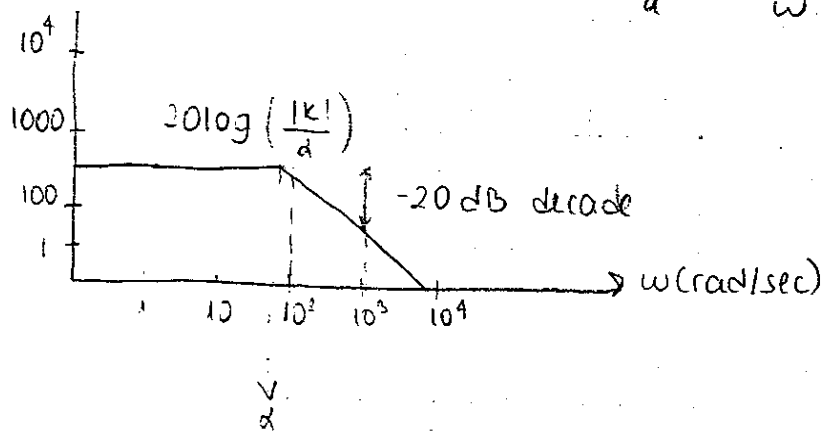


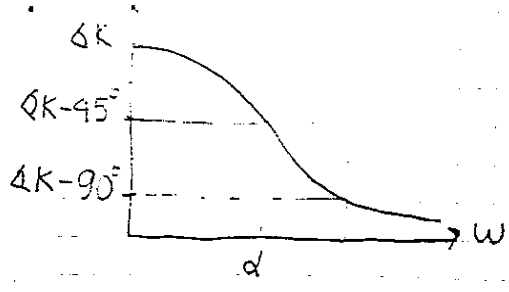$\angle H(j\omega) \Rightarrow \angle K - \tan^{-1} \omega/d$





$K > 0 \quad \angle K = 0$
 $K < 0 \quad \angle K = \mp 180^\circ$

Review: $H(s) = \frac{K}{s+d}$

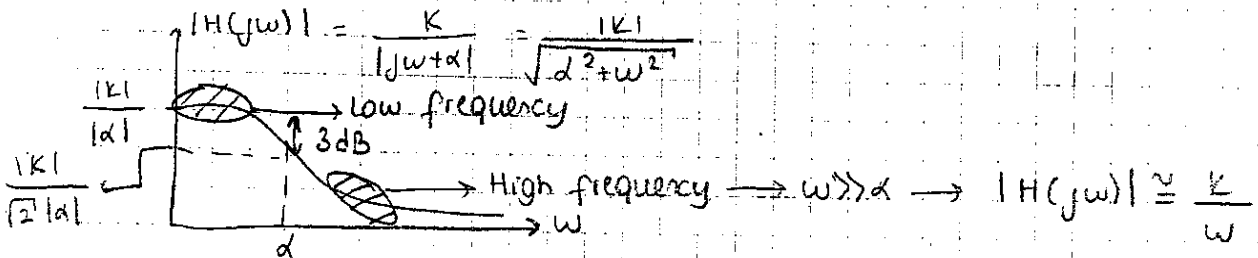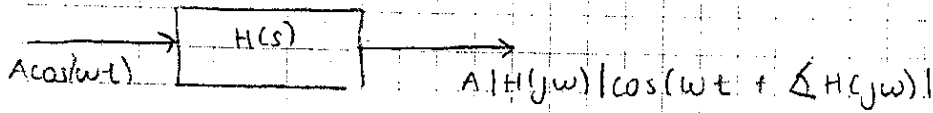

Two asymptotes meet at $\frac{|K|}{|d|} = \frac{|K|}{\omega} \rightarrow \omega = d$

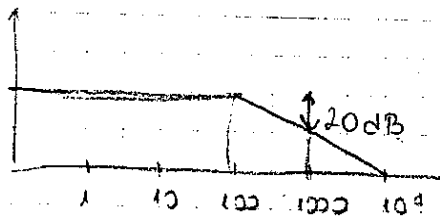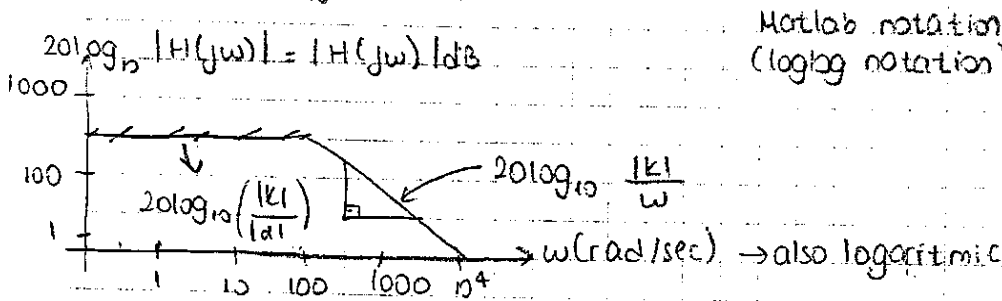
$\downarrow -3dB = 20 \log_{10} (1/\sqrt{2})$




let's cover $\angle H(j\omega) = ? \rightarrow \angle K - \tan^{-1}(\frac{d}{j\omega})$ $\omega \rightarrow \infty \frac{\tan^{-1} \frac{d}{j\omega}}{j\omega} = \pi/2$

$K > 0 \rightarrow \angle K = 0$ $\omega \rightarrow 0 \frac{\tan^{-1} \frac{d}{j\omega}}{j\omega} = 0$

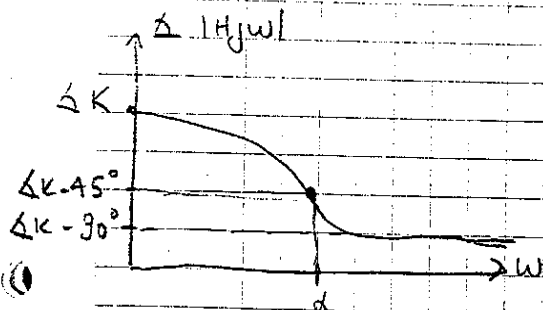$K < 0 \rightarrow \angle K = \mp 180^\circ$



Example: $H(s) = \frac{100}{s+20}$

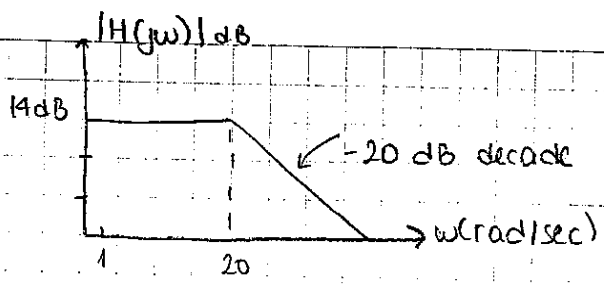

$$H(j\omega) = \frac{100}{j\omega + 20}$$

$$|H(j\omega)| = \frac{100}{\sqrt{20^2 + \omega^2}}$$


Highpass Filters:

$$H(s) = \frac{Ks}{s+a}$$


$$H(j\omega) = \frac{Kj\omega}{j\omega + a}$$

$$\lim_{\omega \rightarrow \infty} H(j\omega) = K$$

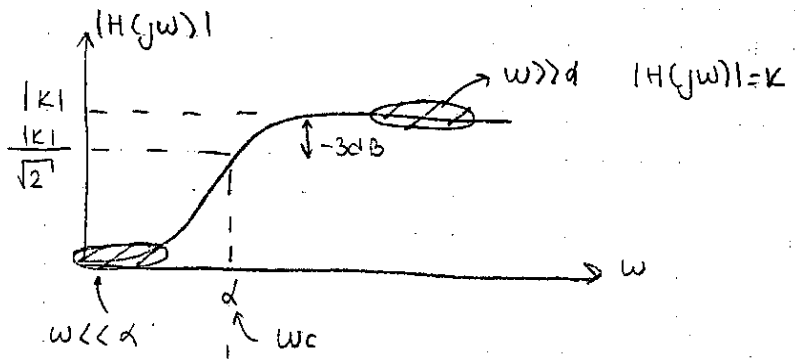
$$\lim_{\omega \rightarrow 0} H(j\omega) = 0$$



$$H(j\omega) \approx \frac{K}{a} j\omega \rightarrow |H(j\omega)| = \left| \frac{K}{a} \right| \omega$$

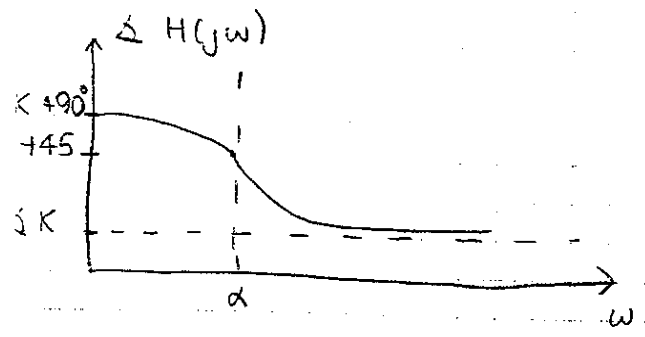

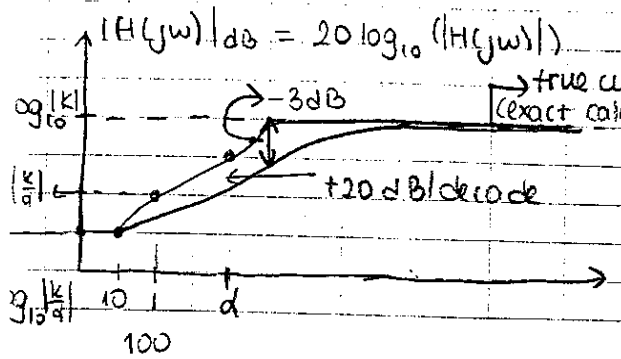
$$\angle H(j\omega) = \angle K + 90^\circ - \tan^{-1}(\omega/a)$$



Let's check the intersection point of low frequency and high-frequency asymptotes.


$$20 \log_{10} |K| = 20 \log_{10} \left(\frac{|K| \omega}{\alpha} \right)$$

high frequency
low frequency

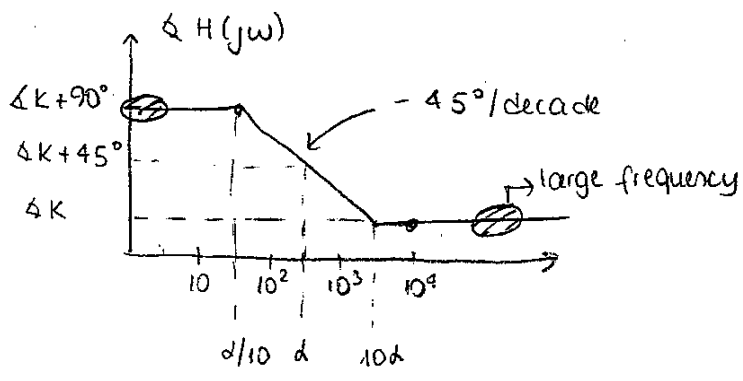



Bandpass - Bandstop Filters using 1st Order Circuits

Bandpass system:

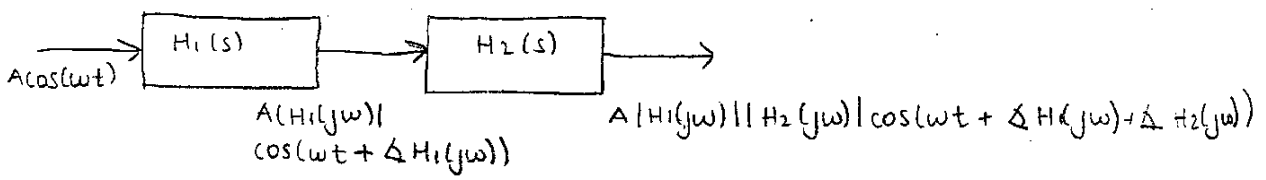


We note that first system does not have a loading effect on 2nd system

$$H(s) = H_1(s) H_2(s)$$

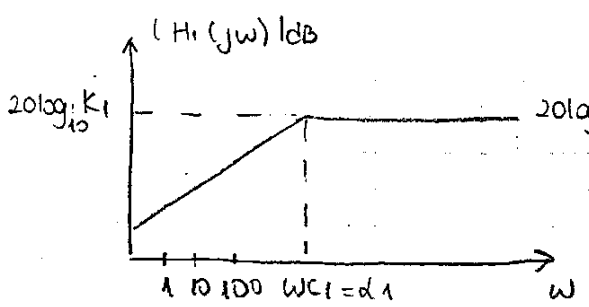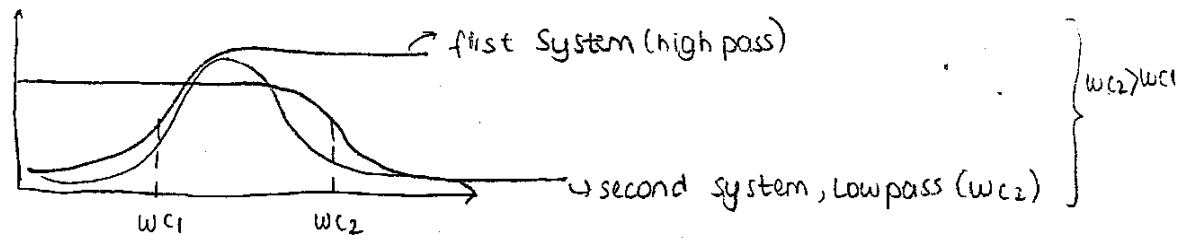

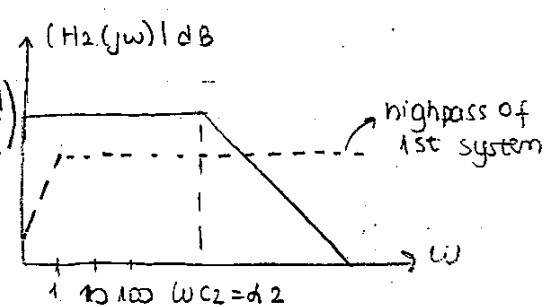
$$H_1(s) = \frac{K_1 s}{\dots} \text{ highpass}$$





$$H_2(s) = \frac{K_2}{\dots} \text{ lowpass}$$

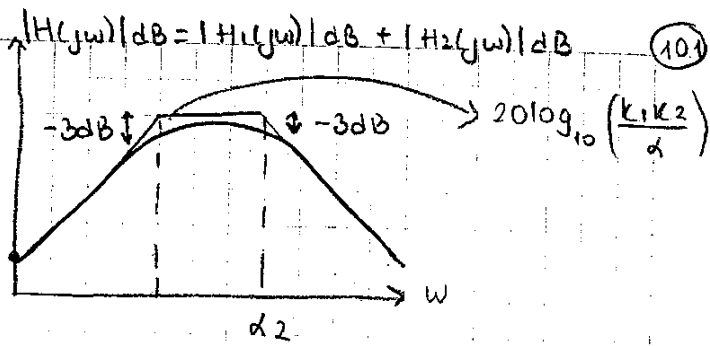
$$H(s) = \frac{k_1 k_2 s}{(s+d_1)(s+d_2)}$$




Bandstop Filter:

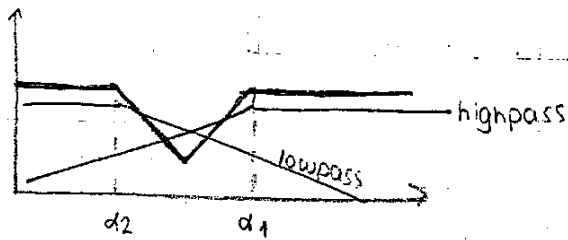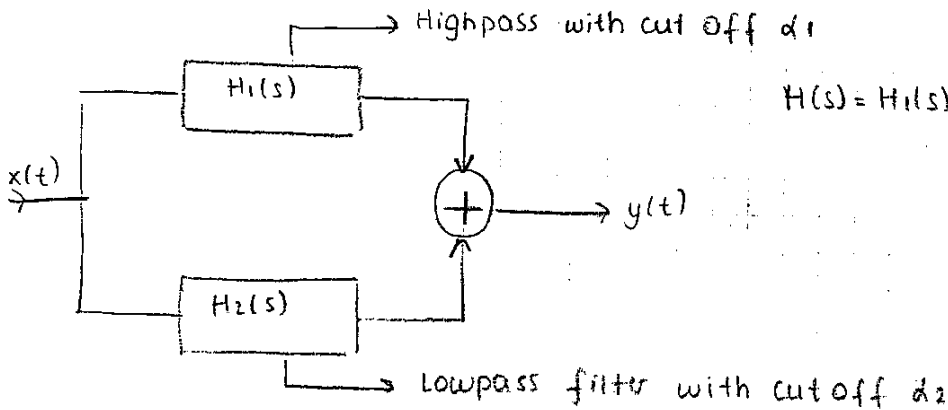

All pass filter but $d_2 > d_1$

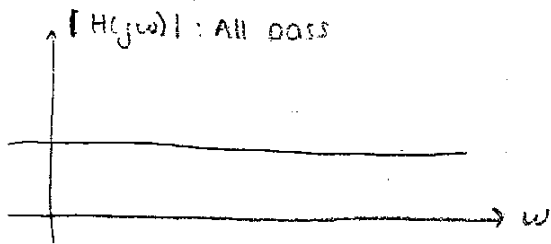

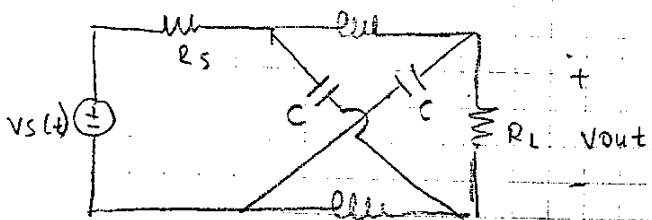Example: All pass constructed from 1st Order Filters



$$\frac{L}{C} = R_L^2 \rightarrow H(j\omega) = \frac{R_L}{R_L + R_S} \frac{1 - j\omega C R_L}{1 + j\omega C R_L}$$


$$|H(j\omega)| = \frac{R_L}{R_L + R_S}$$

Second Order System

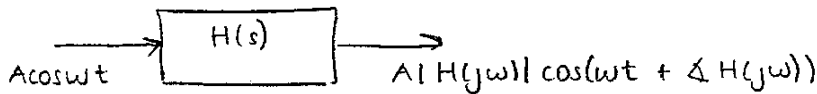(102)

1 Bandpass Systems:

$$H(s) = \frac{Ks}{s^2 + 2\gamma\omega_0 s + \omega_0^2}$$



Pole locations: $s^2 + 2\gamma\omega_0 s + \omega_0^2 = 0 \longrightarrow (s + \gamma\omega_0)^2 = \omega_0^2(\gamma^2 - 1)$


$$s_{1,2} = \left\{ -\gamma\omega_0 \mp \omega_0 \sqrt{\gamma^2 - 1} \right\}$$

Ⓐ $\gamma = 1 \longrightarrow s_{1,2} = \{-\omega_0\} \longrightarrow$ Double root at $s = -\omega_0 \longrightarrow$ Critically damped

Ⓑ $\gamma > 1 \longrightarrow s_{1,2} \longrightarrow$ 2 distinct real roots \longrightarrow overdamped


Ⓒ $\gamma < 1 \longrightarrow s_{1,2} \longrightarrow$ complex conjugate roots \longrightarrow underdamped
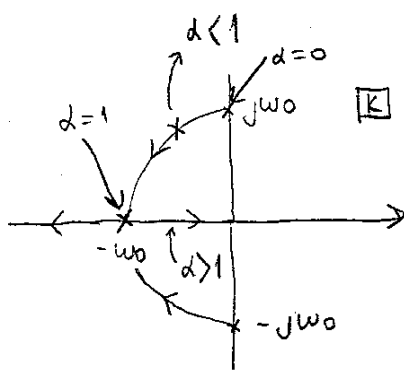
$$s_{1,2} = \left\{ -\gamma\omega_0 \mp j\omega_0 \sqrt{1 - \gamma^2} \right\}$$




Pole-zero diagram for $H(s)$

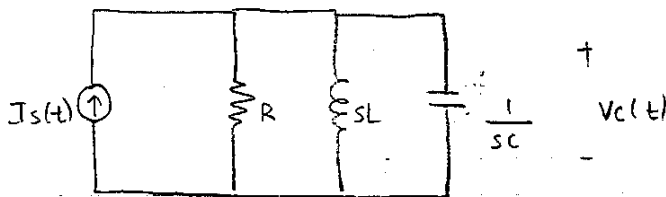Damping in electrical circuits is related to how long is "R" in the circuit




$$\frac{V_c(s)}{I_s(s)} = H(s) = \frac{1}{1/R + 1/sL + sC} = \frac{sLR}{sL + R + s^2 RCL} = \frac{s/C}{s^2 + \frac{1}{LC} + \frac{s}{RC}}$$

$$H(s) = \frac{Ks}{(s-p_1)(s-p_2)} \quad |H(j\omega)| = \frac{|K| |\omega|}{|j\omega - p_1| |j\omega - p_2|}$$

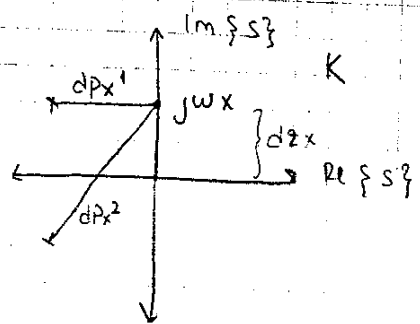

$$|H(j\omega x)| = \frac{|K| dz_x}{dp_x^1 dp_x^2}$$

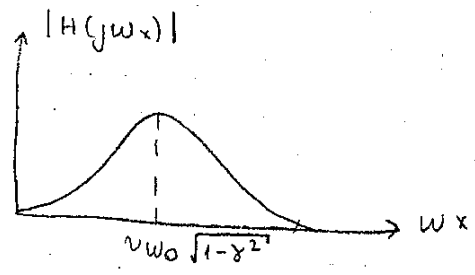

Algebraic Approach for $|H(j\omega)|$ and $\Delta H(j\omega)$

$$H(s) = \frac{Ks}{s^2 + 2\gamma\omega_0 s + \omega_0^2}$$

$$H(j\omega) = \frac{Kj\omega}{-\omega^2 + \omega_0^2 + j2\gamma\omega\omega_0} \quad \text{divide by } j\omega \text{ both sides}$$

$$= \frac{K}{j\frac{(\omega^2 - \omega_0^2)}{\omega} + 2\gamma\omega_0} = \frac{K}{\omega_0(2\gamma + j[\frac{\omega}{\omega_0} - \frac{\omega_0}{\omega}])}$$


$$|H(j\omega)| = \frac{|K|}{\omega_0 [(2\gamma)^2 + (\frac{\omega}{\omega_0} - \frac{\omega_0}{\omega})^2]^{1/2}}$$

$$\Delta H(j\omega) = \angle K - \tan^{-1} \left[\left(\frac{\omega}{\omega_0} - \frac{\omega_0}{\omega} \right) \cdot \frac{1}{2\gamma} \right]$$

$$|H(j\omega)| \rightarrow \max |H(j\omega)| = 1 \quad \text{at } \omega = \omega_0 \rightarrow |H(j\omega)| = \frac{|K|}{\omega_0 [(2\gamma)^2 + 0^2]^{1/2}} = \frac{|K|}{\omega_0 2|\gamma|}$$

$$\text{at } \omega = \omega_0 \rightarrow |H(j\omega)| = \frac{|K|}{\omega_0 [(2\gamma)^2 + 0^2]^{1/2}} \rightarrow |H(j\omega)| \sim \frac{|K|\omega}{\omega_0^2}$$


$$\textcircled{3} \omega \gg \omega_0 \rightarrow |H(j\omega)| \sim \frac{|K|}{\omega}$$

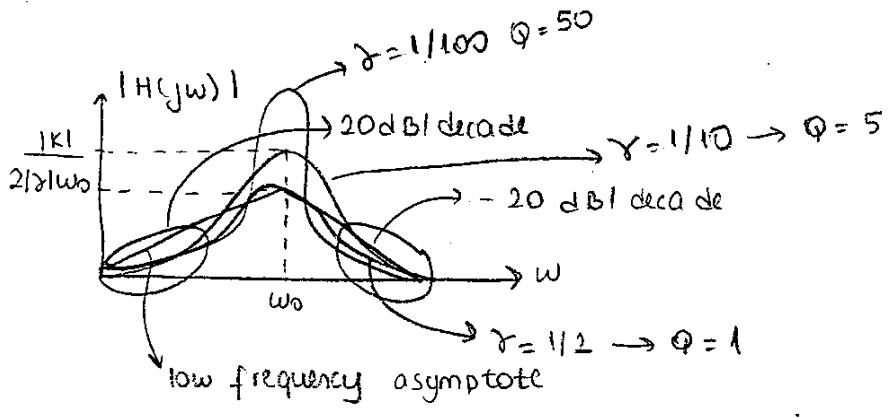

4.2) Intersection of asymptotes:

$$|K| \frac{w}{w^2} = \frac{|K|}{w} \longrightarrow w = w_0$$

low frequency high frequency

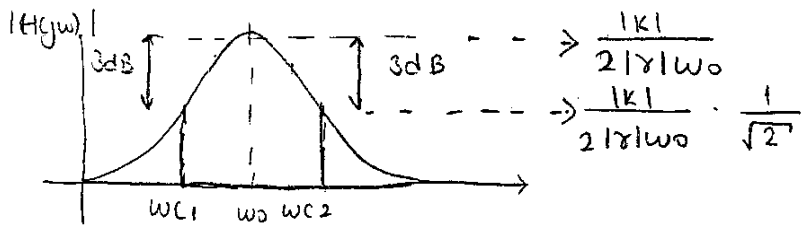

If $\left(\frac{w}{w_0} - \frac{w_0}{w}\right) = \pm 2\gamma \longrightarrow w$ is a cut-off frequency

For w_{c2} ($w_{c2} > w_0$) $\longrightarrow \left(\frac{w}{w_0} - \frac{w_0}{w}\right) = 2\gamma \longrightarrow$

$$w_{c2}^2 - (2\gamma w_0) w_{c2} - w_0^2 = 0$$

$$w_{c2} = w_0 \left(\gamma + \sqrt{1 + \gamma^2} \right) \longrightarrow w_0 \left(\frac{1}{2Q} + \sqrt{1 + \frac{1}{4Q^2}} \right)$$

plus or minus
(we choose plus)

For w_{c1} ($w_{c1} < w_0$) $\longrightarrow \left(\frac{w_{c1}}{w_0} - \frac{w_0}{w_{c1}}\right) = -2\gamma \longrightarrow$

$$w_{c1} = w_0 \left(-\gamma + \sqrt{1 + \gamma^2} \right)$$


$BW = w_{c2} - w_{c1} = 2 w_0 \gamma$ (Bandwidth)

$$H(s) = \frac{Ks}{s^2 + \underbrace{(2\gamma w_0)}_{BW} s + w_0^2} \longrightarrow \text{resonance frequency}$$

$$Q = \frac{w_0}{BW} \xrightarrow{\text{center frequency}} = \frac{1}{2\gamma} \left[\begin{array}{l} Q = 1/2\gamma \\ \gamma = 1/2Q \end{array} \right] \xrightarrow{\text{bandwidth}}$$

$\rightarrow \sqrt{w_{c1} w_{c2}} = w_0$

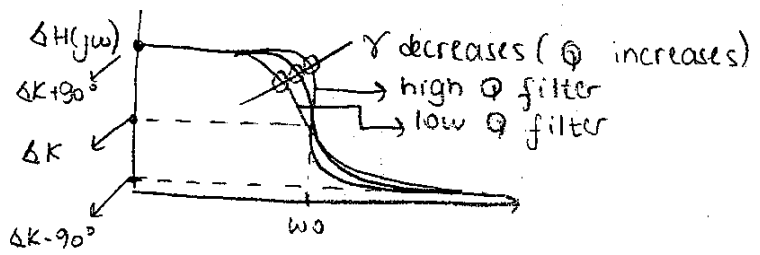$\angle H(jw) = \Delta K - \tan^{-1} \left(\frac{(w/w_0) - (w_0/w)}{2\gamma} \right)$




Second Order Lowpass Systems

$H(s) = \frac{K}{s^2 + 2\gamma w_0 s + w_0^2}$

$|H(jw)|$: Mag response
 $\angle H(jw)$: Phase response

$H(jw) \Big|_{\omega=0, s=0} = K/w_0^2$

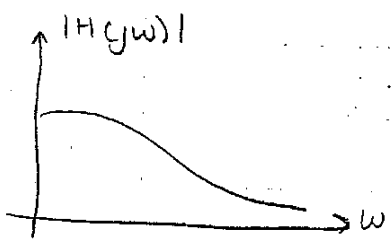
$\lim_{w \rightarrow \infty} H(jw) = 0$ with K/s^2
 ($s \rightarrow \infty$)



$H(jw) = \frac{K}{w_0^2 - w^2 + j 2\gamma w_0 w}$


$|H(jw)| = \frac{|K|}{[(w_0^2 - w^2)^2 + (2\gamma w_0 w)^2]^{1/2}} = \frac{K}{w_0^2 \left[\left(1 - \left(\frac{w}{w_0}\right)^2\right)^2 + \left(2\gamma \frac{w}{w_0}\right)^2 \right]^{1/2}}$

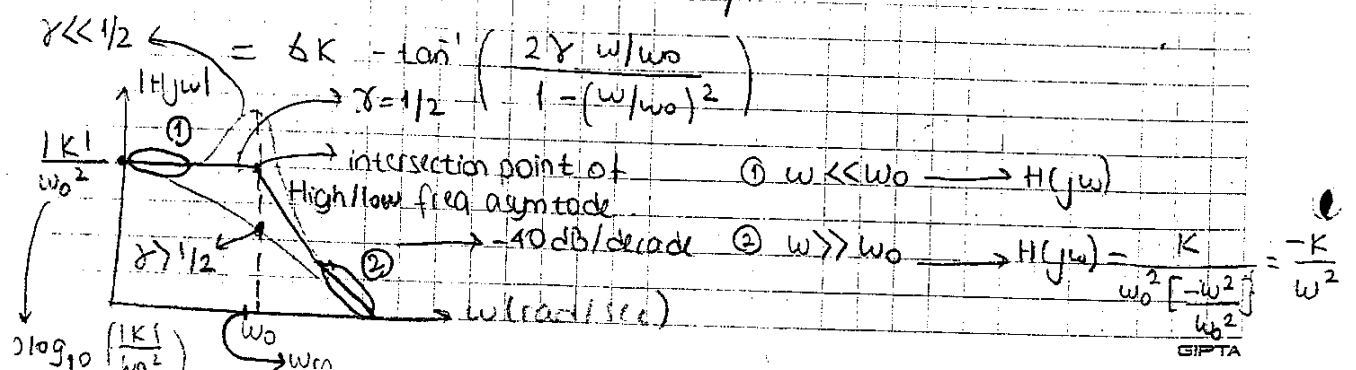$\angle H(jw) = \Delta K - \tan^{-1} \left(\frac{2\gamma w_0 w}{w_0^2 - w^2} \right)$



$|H(j\omega)|_{dB} = -40 \text{ dB/dec}$
 $20 \log_{10} |H(j\omega)|$

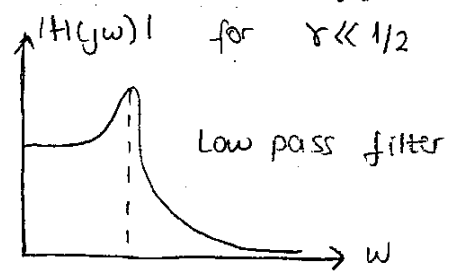3- $H(j\omega) = \frac{K}{\omega^2 (j 2\gamma \frac{\omega_0}{\omega})}$



- 2nd Order $\gamma > 1/2$ Overdamped
- $\gamma < 1/2$ Underdamped \rightarrow Two complex conjugate poles

4- What is the peak value of $|H(j\omega)| = ?$

(Is the peak located at $\omega = \omega_0$) \rightarrow acılyla ilgisi yok

$\text{Argmax}_{\omega} |H(j\omega)| = \omega_{\text{max}} = \text{argmin}_{\omega} \left(\left(1 - \frac{\omega^2}{\omega_0^2}\right)^2 + \left(2\gamma \frac{\omega}{\omega_0}\right)^2 \right)$


$f(x) = (1-x^2)^2 + (2\gamma x)^2 ; x = \frac{\omega}{\omega_0}$

$f'(x) = -4x(1-x^2) + 2(2\gamma)^2 x = 0$

$x = \sqrt{1-2\gamma^2} \quad \omega_m = \omega_0 \sqrt{1-2\gamma^2}$

$\gamma = 1/2Q$ where $Q = \text{quality factor}$

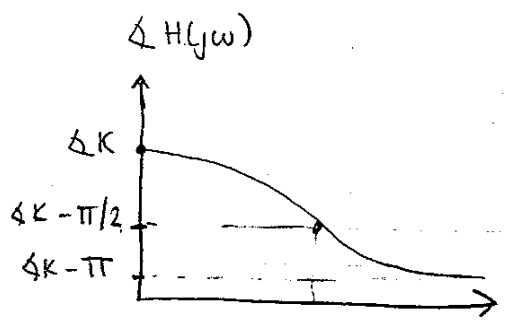$\omega_m = \omega_0 \sqrt{1 - \frac{1}{2Q^2}}$ provided that $Q > \frac{1}{\sqrt{2}}$ $\gamma < \frac{1}{\sqrt{2}}$



$H(j\omega) = \frac{K}{(\omega_0^2 - \omega^2) + j(2\gamma\omega_0)\omega}$
 $= \frac{K((\omega_0^2 - \omega^2) - j(2\gamma\omega_0)\omega)}{(\omega_0^2 - \omega^2)^2 + (2\gamma\omega_0\omega)^2}$


Second Order High Pass System

$$H(s) = \frac{K s^2}{s^2 + 2\gamma \omega_0 s + \omega_0^2}$$

$$H(j\omega) \approx \begin{matrix} K & \omega \rightarrow \infty \\ 0 & \omega \rightarrow 0 \end{matrix}$$

$$H(j\omega) = \frac{K - \omega^2}{\omega_0^2 - \omega^2 + j 2\gamma \omega_0 \omega}$$

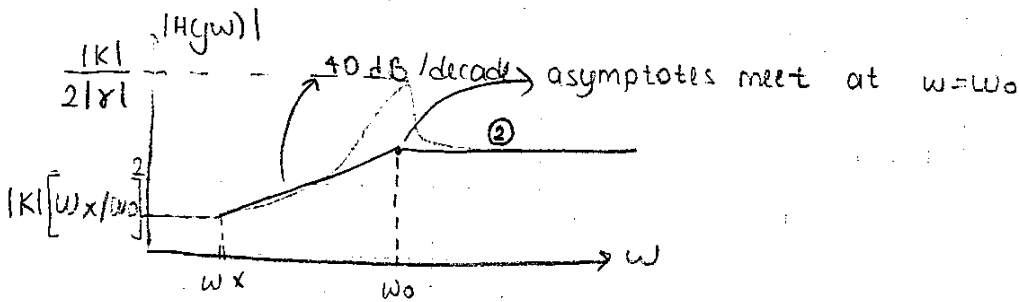
$$= -K \frac{(\omega/\omega_0)^2}{1 - (\omega/\omega_0)^2 + j 2\gamma (\omega/\omega_0)}$$



① $\omega/\omega_0 \ll 1$ $\omega_x/\omega_0 \ll 1$ ($\omega_x = 10^{-6} \omega_0$)

② $\omega/\omega_0 \gg 1$ $\rightarrow H(j\omega) \sim -K (\omega/\omega_0)^2$

$\rightarrow H(j\omega) \approx +K$

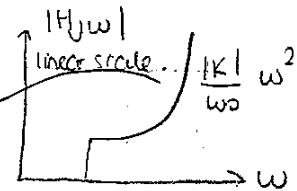


③ $H(j\omega_0) = \frac{-K}{j 2\gamma}$


$$H(j\omega) = |H(j\omega)| e^{j\angle H(j\omega)}$$

$$H(j\omega) = \frac{-K (\omega/\omega_0)^2}{\left[1 - (\frac{\omega}{\omega_0})^2 \right]^2 + \left[2\gamma (\frac{\omega}{\omega_0}) \right]^2} \left(1 - (\frac{\omega}{\omega_0})^2 - j 2\gamma (\frac{\omega}{\omega_0}) \right)$$

real

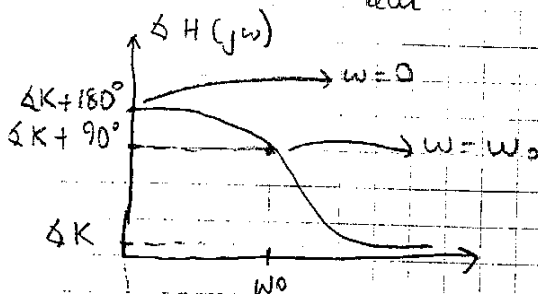

Example:

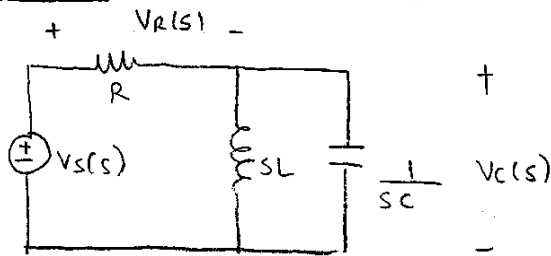

$$H(s) = \frac{s/R C}{s^2 + s/R C + 1/LC}$$

$$H_2(s) = \frac{V_R(s)}{V_S(s)} = 1 - H_1(s)$$


Bandstop

$$L = 1/4 \text{ H} \quad R = 1 \text{ k}\Omega \quad C = 1 \mu\text{F}$$


$$H_1(s) = \frac{s \cdot 1000}{s^2 + 1000s + (2000)^2} = \frac{K s}{s^2 + 2\gamma\omega_0 s + \omega_0^2}$$

$$\gamma = 1000 \quad \omega_0 = 2000$$
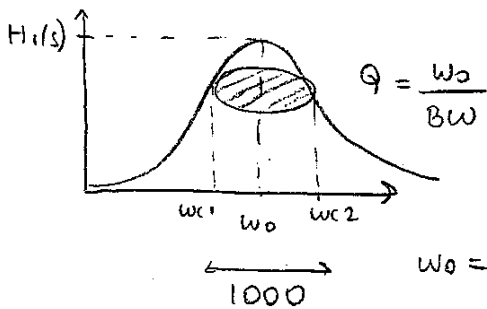
$$\gamma = \frac{1000}{2\omega_0} = 1/4 \rightarrow Q = 2 \left(= \frac{1}{2\gamma} \right)$$



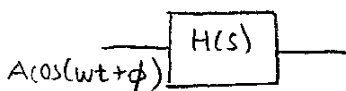
Example: Active filters: Filters with active components



$$H(s) = \frac{s+1}{s^2+2s+5}$$

$|H(j\omega)| > 1$ ise;
active filters
Adi üstünde amplif. var

$$A |H(j\omega)| \cos(\omega t + \phi + \Delta H(j\omega))$$

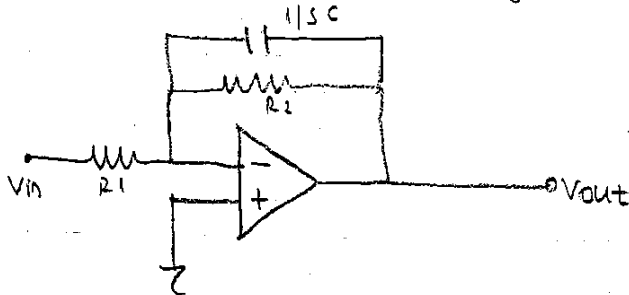


$$H(s) = \frac{V_{out}(s)}{V_{in}(s)} = -\frac{R_2}{R_1} \frac{1}{1+sR_2C}$$


operating in linear region
(ideal op-amp)

scaling:

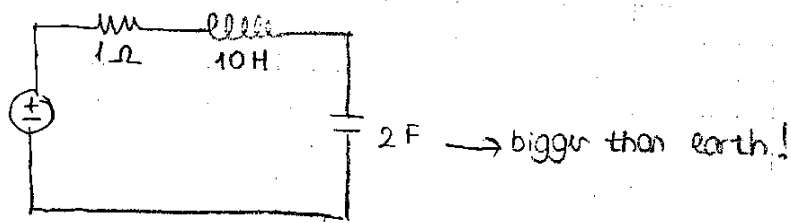- ① Magnitude scaling
- ② Frequency scaling



① Magnitude scaling:

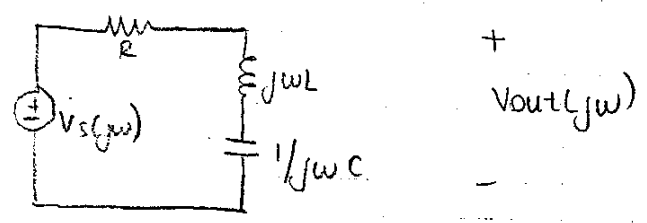




$$H(j\omega) = \frac{j\omega L + 1/j\omega C}{R + j\omega L + 1/j\omega C} = \frac{Z_2(j\omega) + Z_3(j\omega)}{Z_1(j\omega) + Z_2(j\omega) + Z_3(j\omega)}$$

- $R \rightarrow k_m R$ (replace) $\longrightarrow z_1(j\omega)$ scaled by k_m
 - $L \rightarrow k_m L$ $\longrightarrow z_2(j\omega)$ scaled by k_m
 - $C \rightarrow C/k_m$ $\longrightarrow z_3(j\omega)$ scaled by k_m
- } $H(j\omega)$ remains the same.

For example: $z_1(j\omega)$ replaced by $k_m z_1(j\omega)$

② Frequency scaling:

Previous example:

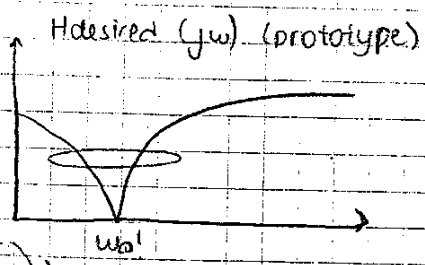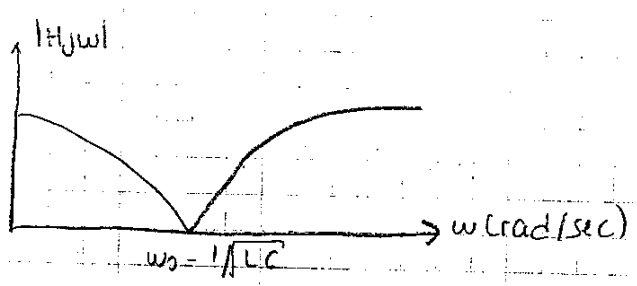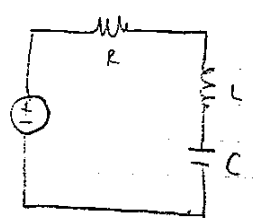

$$H(j\omega)_{desired} = H(j\omega \cdot \frac{\omega_0}{\omega_0'}) \text{ prototype}$$

$\omega_0 \rightarrow$ scalar

ω_0' : desired null frequency

$$H_{pro}(j\omega) = \frac{j\omega L + 1/j\omega C}{R + j\omega L + 1/j\omega C}$$

$$R \rightarrow R$$



$$L \rightarrow L/k_f$$

$$C \rightarrow C/k_f$$

$$\left. \begin{array}{l} H(j\omega) \text{ after } k_f \\ \text{scaling} = \frac{j\omega L/k_f + k_f/j\omega C}{R + j\frac{\omega}{k_f}L + \frac{k_f}{j\omega C}} \end{array} \right\} = H_{pro}\left(\frac{j\omega}{k_f}\right)$$


So to scale the null from $\omega_0 \rightarrow \omega_0'$
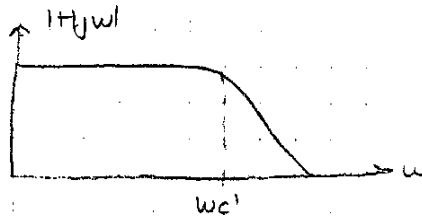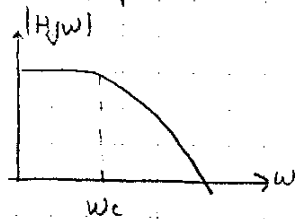
$$H_{pro}\left(j\frac{\omega}{k_f}\right) = H\left(j\omega \frac{\omega_0}{\omega_0'}\right) \rightarrow k_f = \frac{\omega_0'}{\omega_0} \left\{ \begin{array}{l} \leftarrow \text{new frequency} \\ \leftarrow \text{old frequency} \end{array} \right.$$



lowpass example

Example:

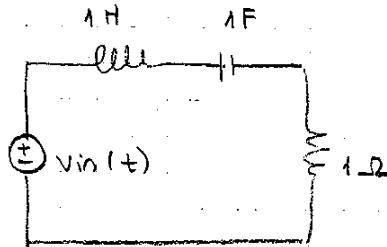

Scale the circuit such that the resonant freq is not 500 Hz and use a 2μF cap.

$$\omega_0 = \frac{1}{\sqrt{LC}} = 1 \text{ rad/sec}$$

$$BW = 2\gamma\omega_0 = \frac{R}{L} = 1 \text{ rad/sec}$$

$$Q = \frac{\omega_0}{BW} = 1$$

$$\omega_0' = 2\pi 500 = 1000\pi, \text{ Use } 2\mu\text{F cap}$$


$$R \rightarrow R_{km} \rightarrow R_{km} \rightarrow 160 \Omega$$

$$L \rightarrow L_{km} \rightarrow L_{km}/k_f \rightarrow 50 \text{ mH}$$

$$C \rightarrow C/k_m \rightarrow C/k_m k_f \rightarrow 2\mu\text{F}$$

$$k_f = \frac{\omega_0'}{\omega_0} = 1000\pi \quad k_m = ?$$
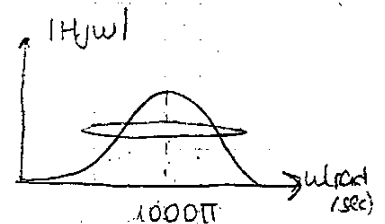
$$\frac{C}{k_m k_f} = 2\mu\text{F} \rightarrow k_m = \frac{1}{2 \cdot 10^3 \pi} \approx .160$$



$$BW \text{ after: } \frac{R_{\text{after}}}{L_{\text{after}}} = k_f BW \text{ before} = 1000\pi$$

$$Q = \frac{1000\pi}{1000\pi} = 1 \text{ (remains the same)}$$

(111)

Example: $H(s) = 12500 \frac{s+10}{(s+50)(s+500)}$

① Bring $H(s)$ into standard form: (all polynomials should be expressed as $(1 + \frac{s}{\alpha_1})$)

constant term = 1



$$H(s) = 12500 \frac{10(1+s/10)}{50(1+s/50)500(1+s/500)} = 5 \frac{(1+s/10)}{(1+s/50)(1+s/500)}$$

② Express $|H(j\omega)|_{dB}$ & $\angle H(j\omega)$

$$H(j\omega) = 5 \frac{1+j\omega/10}{(1+j\omega/50)(1+j\omega/500)}$$


$$20\log_{10} |H(j\omega)| = 20\log_{10} 5 + 20\log_{10} \left\| 1 + \frac{j\omega}{10} \right\| - 20\log_{10} \left\| 1 + \frac{j\omega}{50} \right\| - 20\log_{10} \sqrt{1 + \frac{\omega^2}{500^2}}$$

Let's focus on $20\log_{10} \left\| 1 + \frac{j\omega}{\alpha_1} \right\| = 20\log_{10} \sqrt{1 + \frac{\omega^2}{\alpha_1^2}}$

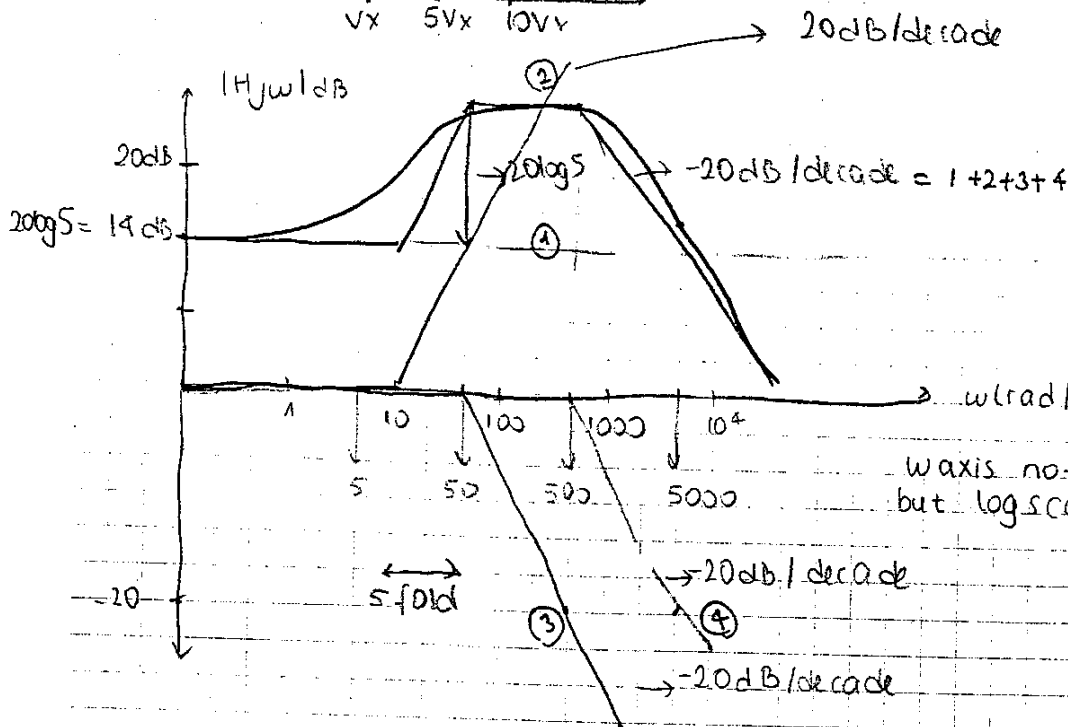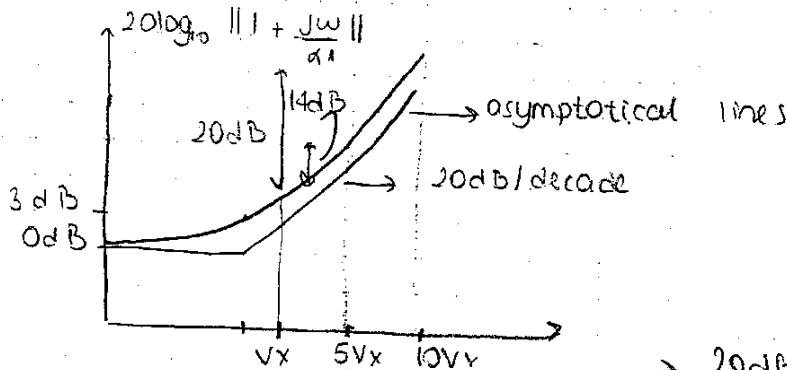

Note that: at every critical frequency $(1 + \frac{s}{d_1})$, such as d_1 , there is an increasing or decreasing 20 dB/dec slope.

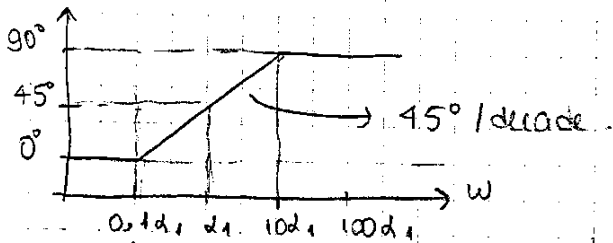
Phase Resp $\angle (1 + j \frac{\omega}{d_1}) = \tan^{-1}(\omega/d_1)$



Annotations for the graph:
 - 10 times critical frequency (from d1 to 10d1)
 - critical frequency (at d1)
 - 10% of critical freq. (at 0.1d1)

$$H(j\omega) = 5 \frac{(1 + j\omega/10)}{(1 + j\omega/50)(1 + j\omega/50)}$$

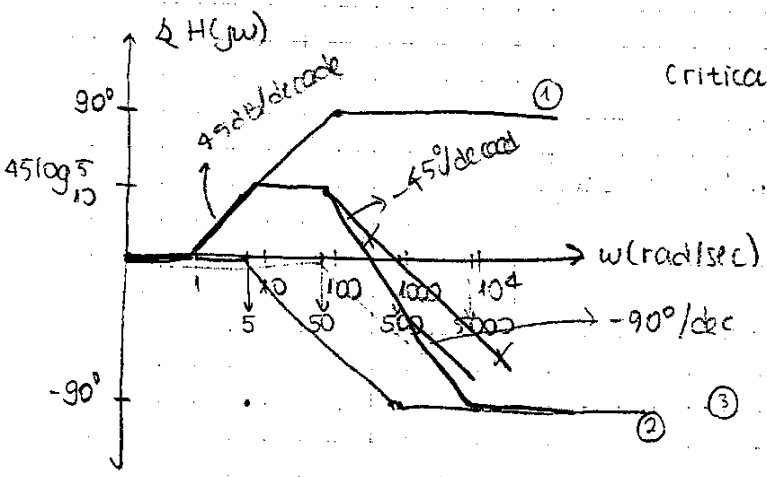$\rightarrow \Delta H(j\omega) = \Delta 5 + \Delta (1 + j\omega/10)$
 $- \Delta (1 + j\omega/50) - \Delta (1 + j\omega/50)$



critical freq: { 10, 50, 500 }

Bode Plots with 2nd Order System

$$H(s) = \frac{(s+1)}{(s+2)(s+3)(s^2+4s+5)}$$

↳ does not have a real root

$$A(s) = s^2 + 2\gamma\omega_0 s + \omega_0^2 \quad (\text{divide by } \omega_0^2)$$


Bring the $A(s)$ into standard form $\rightarrow \left(\frac{s}{\omega_0}\right)^2 + \frac{2\gamma}{\omega_0} s + 1 = A^{\text{std}}(s)$

$$H(s) = \frac{(1+s)}{2(1+s/2) \cdot 3(1+s/3) \cdot 5(1+s \frac{4}{5} + \frac{s^2}{5})}$$

the constant term

$$H(s) = \frac{1}{30} \frac{(1+s)}{(1+s/2)(1+s/3)(1+s \frac{4}{5} + \frac{s^2}{5})}$$
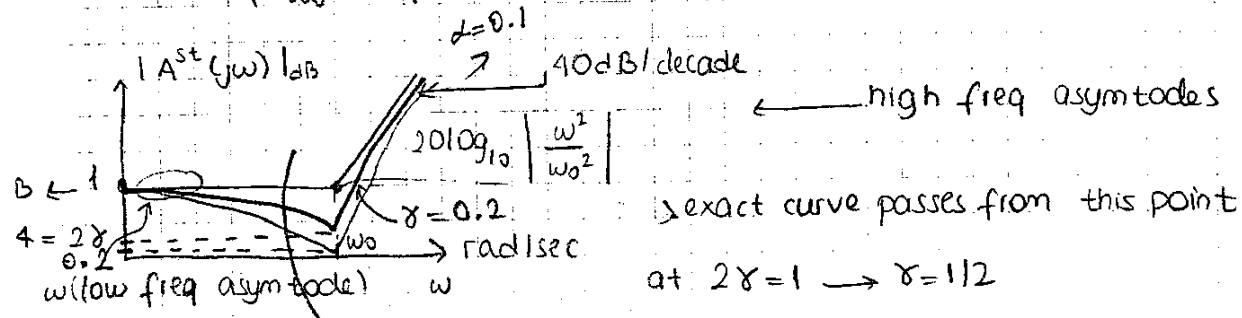
$$A^{std}(j\omega) = \left(-\frac{\omega^2}{\omega_0^2} + 1 \right) + j \left(2\zeta \frac{\omega}{\omega_0} \right)$$



$$A^{std}(j\omega_0) = j 2\zeta$$

When $\zeta < 1$ ($Q > 1/2$) underdamped


$\zeta = 1$ ($Q = 1/2$) critically damped

$\zeta > 1$ ($Q < 1/2$) overdamped → This case can be factored as multiplication of two first order


$(1 + \frac{s}{d_1})(1 + \frac{s}{d_2})$ type polynomials

$Q = 1/2\zeta$ (quality factor)

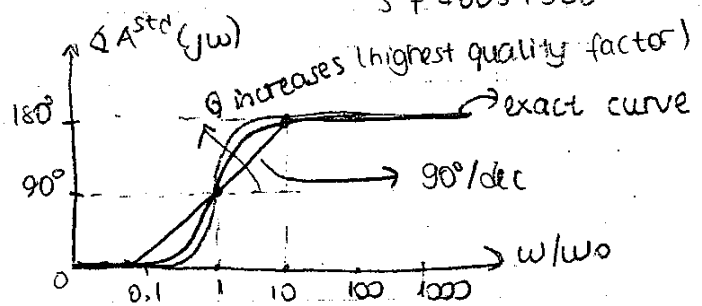Example: $H(s) = 5000 \frac{(s+100)}{s^2 + 400s + 500^2}$


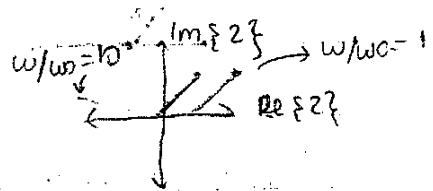
$$A^{std}(j\omega) = \left[-\left(\frac{\omega}{\omega_0}\right)^2 + 1 \right] + j 2\zeta \left(\frac{\omega}{\omega_0}\right)$$




$$H(s) = 5000 \frac{(s+100)}{s^2 + 400s + 500^2} = 5000 \frac{100(1+s/100)}{500^2 \left(1 + \frac{400}{500^2}s + \frac{s^2}{500^2} \right)}$$

two complex roots

$$H(s) = \underbrace{K}_{I} \underbrace{\left(1 + \frac{s}{d_1} \right)}_{II} \underbrace{\left(\frac{1 + 2\zeta \frac{s}{\omega_0} + \frac{s^2}{\omega_0^2}}{\omega_0^2} \right)}_{III}$$


$\omega_0 = 500$
 $\zeta = 2/5$

Critical freq; = {100, 500}

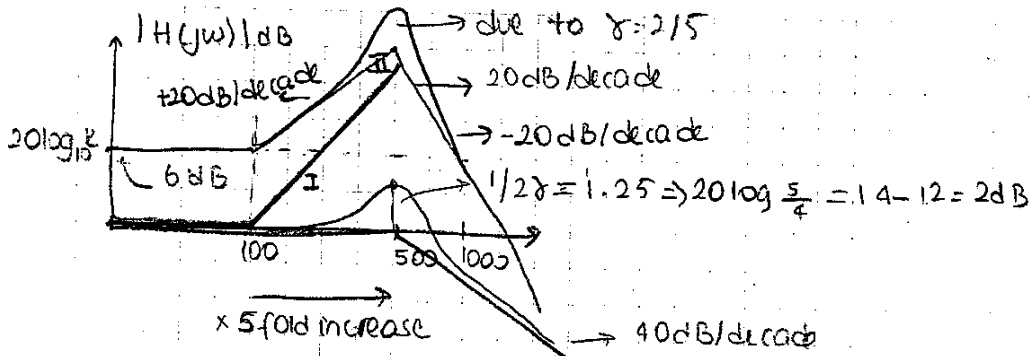


$\gamma \rightarrow 0$ sharper, peak ∞ 'da dir ;

Phase response:

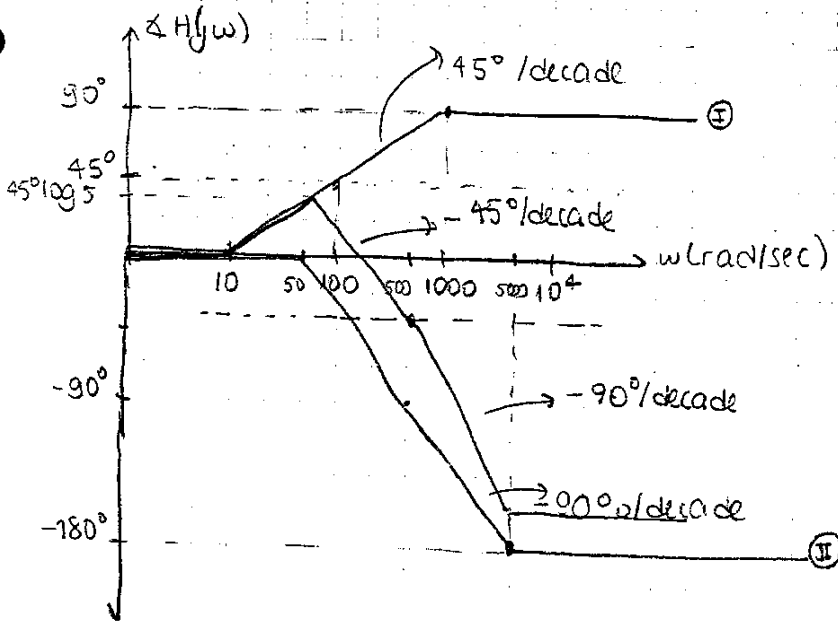

State equation with Non-linear Elements:

Example:

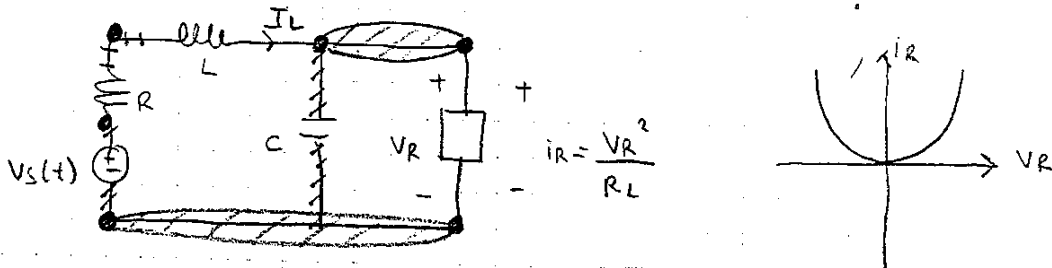

$\{I_L(t), V_C(t)\}$

Fundamental cut-set: $\rightarrow C V_C' = I_L - I_{NL} = I_L - \frac{V_C^2(t)}{R_L}$ ✓

Fundamental loop $\rightarrow L I_L' = -I_L R + V_S(t) - V_C(t)$ ✓

[DC outputlarını kabul ediyoruz]

$$V_c'(t) = -\frac{V_c(t)}{R_L C} + \frac{I_L}{C}$$

$$I_L'(t) = -V_c(t) \cdot \frac{1}{L} - \frac{R}{L} I_L(t) + \frac{V_s(t)}{L}$$

Zero-input solution $V_c(0^-) = V_0$ $I_L(0^-) = I_0$ $V_s(t) = 0$



If there is a solution, then $V_c'(t) = 0$ } when we reach the steady state
 $I_L'(t) = 0$ } solution.

$$t \rightarrow \infty \quad V_c(t) \rightarrow V_c^\infty$$

$$I_L(t) \rightarrow I_L^\infty$$

$$\text{As } t \rightarrow \infty \quad 0 = -\frac{(V_c^\infty)^2}{R_L C} + \frac{I_L^\infty}{C} \rightarrow (V_c^\infty)^2 = R_L \cdot I_L^\infty$$
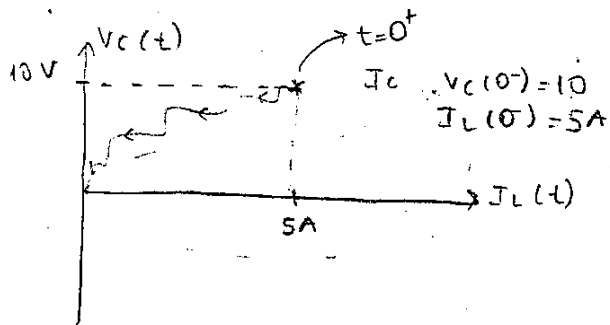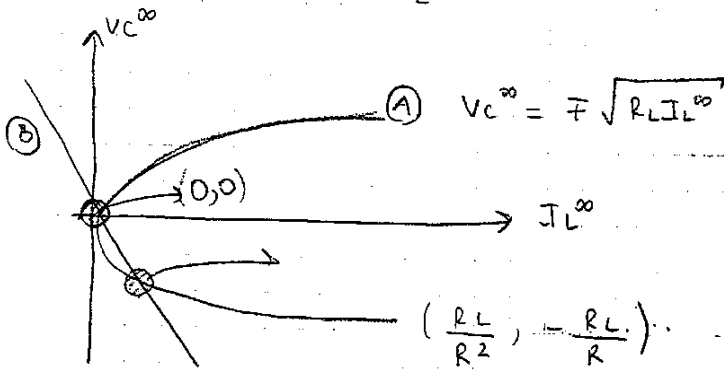
$$0 = -\frac{V_c^\infty}{L} - \frac{R}{L} I_L^\infty \quad V_c^\infty = -R I_L^\infty$$



phase plane
 phase portrait