

Average Energy Stored in a Mutual Inductor at AC Steady State

Onur Memioğlu

April 22, 2013


Abstract: The formula for the average stored energy in mutual inductors under AC excitation is derived in two different ways. ¹

First Method:

Firstly, we compute the instantaneous power of a mutual inductor. Instantaneous power of a component is equal to:

$$p(t) = i(t) \cdot v(t)$$

For mutual inductor:

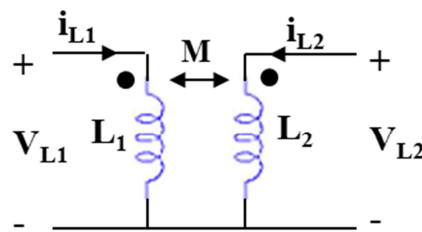

$$p(t) = i(t) \cdot v(t)$$

$$p(t) = i_1(t) \cdot v_1(t) + i_2(t) \cdot v_2(t)$$

$$p(t) = \begin{pmatrix} i_1(t) & i_2(t) \end{pmatrix} \cdot \begin{pmatrix} v_1(t) \\ v_2(t) \end{pmatrix}$$

By mutual inductance equation:

$$\begin{pmatrix} v_1(t) \\ v_2(t) \end{pmatrix} = \begin{pmatrix} L_1 & M \\ M & L_2 \end{pmatrix} \cdot \begin{pmatrix} di_1(t)/dt \\ di_2(t)/dt \end{pmatrix}$$

¹ Notes are prepared to assist EE 202 course of Department of Electrical-Electronics Engineering, Middle East Technical University (METU), Ankara, Turkey. The author is a second year undergraduate student taking the course in Spring 2012-13 semester.

$p(t)$ becomes:

$$p(t) = \begin{pmatrix} i_1(t) & i_2(t) \end{pmatrix} \cdot \begin{pmatrix} L_1 & M \\ M & L_2 \end{pmatrix} \cdot \begin{pmatrix} di_1(t)/dt \\ di_2(t)/dt \end{pmatrix}$$

$$p(t) = \begin{pmatrix} i_1(t) \cdot L_1 + M \cdot i_2(t) & i_1(t) \cdot M + i_2(t) \cdot L_2 \end{pmatrix} \cdot \begin{pmatrix} di_1(t)/dt \\ di_2(t)/dt \end{pmatrix}$$

$$p(t) = i_1(t) \cdot L_1 \cdot \frac{di_1(t)}{dt} + M \cdot i_2(t) \cdot \frac{di_1(t)}{dt} + i_1(t) \cdot M \cdot \frac{di_2(t)}{dt} + i_2(t) \cdot L_2 \cdot \frac{di_2(t)}{dt}$$

The terms that include M can be arranged as

$$M \cdot i_2(t) \cdot \frac{di_1(t)}{dt} + i_1(t) \cdot M \cdot \frac{di_2(t)}{dt} = M \cdot \frac{d(i_1(t) \cdot i_2(t))}{dt}$$

(Multiplication rule of the derivative)

Therefore $p(t)$ becomes:

$$p(t) = i_1(t) \cdot L_1 \cdot \frac{di_1(t)}{dt} + M \cdot \frac{d(i_1(t) \cdot i_2(t))}{dt} + i_2(t) \cdot L_2 \cdot \frac{di_2(t)}{dt}$$

From this equation total energy can be computed by integrating the instantaneous power from $-\infty$ to an arbitrary time t .

$$E(t) = \int_{-\infty}^t P(t') \cdot dt' = \int_{-\infty}^t \left(i_1(t') \cdot L_1 \cdot \frac{di_1(t')}{dt'} + M \cdot \frac{d(i_1(t') \cdot i_2(t'))}{dt'} + i_2(t') \cdot L_2 \cdot \frac{di_2(t')}{dt'} \right) \cdot dt'$$

dt' terms cancel inside the integration:

$$E(t) = \int_{-\infty}^t i_1(t') \cdot L_1 \cdot di_1(t') + \int_{-\infty}^t i_2(t') \cdot L_2 \cdot di_2(t') + \int_{-\infty}^t M \cdot d(i_1(t') \cdot i_2(t'))$$

At $-\infty$, $i_1(t)$ and $i_2(t)$ are equal to zero. Therefore $E(t)$ becomes:

$$E(t) = \frac{L_1 \cdot i_1^2(t)}{2} + \frac{L_2 \cdot i_2^2(t)}{2} + M \cdot i_1(t) \cdot i_2(t)$$

Average stored energy in the mutual inductor becomes:

$$\begin{aligned}\bar{E} &= \frac{1}{T} \int_0^T E(t) \cdot dt = \frac{1}{T} \int_0^T \left(\frac{L_1 \cdot i_1^2(t)}{2} + \frac{L_2 \cdot i_2^2(t)}{2} + M \cdot i_1(t) \cdot i_2(t) \right) \cdot dt \\ &= \frac{1}{T} \left(\int_0^T \frac{L_1 \cdot i_1^2(t)}{2} \cdot dt + \int_0^T \frac{L_2 \cdot i_2^2(t)}{2} \cdot dt + \int_0^T M \cdot i_1(t) \cdot i_2(t) \cdot dt \right)\end{aligned}$$

Assume $i_1(t) = I_1 \cdot \cos(\omega t + \theta_1)$

$i_2(t) = I_2 \cdot \cos(\omega t + \theta_2)$

$$\begin{aligned}&= \frac{L_1}{2} \cdot \left(\sqrt{\frac{1}{T} \int_0^T i_1^2(t) \cdot dt} \right)^2 + \frac{L_2}{2} \cdot \left(\sqrt{\frac{1}{T} \int_0^T i_2^2(t) \cdot dt} \right)^2 \\ &\quad + \frac{1}{T} \int_0^T M \cdot I_1 \cdot I_2 \cdot \cos(\omega t + \theta_1) \cdot \cos(\omega t + \theta_2) \cdot dt\end{aligned}$$

The terms in square root are equal to the RMS values of the inductor branch currents. For the third integral, we can convert multiplication of two cosines into addition of two cosines by the following formula:

$$\cos(a) \cdot \cos(b) = \frac{1}{2} \cdot (\cos(a + b) + \cos(a - b))$$

The average stored energy becomes:

$$= \frac{L_1}{2} \cdot I_{1,RMS}^2 + \frac{L_2}{2} \cdot I_{2,RMS}^2 + \frac{M \cdot I_1 \cdot I_2}{2 \cdot T} \cdot \int_0^T (\cos(2\omega t + \theta_1 + \theta_2) + \cos(\theta_1 - \theta_2)) \cdot dt$$

Integration of $\cos(2\omega t + \theta_1 + \theta_2)$ over the whole period is zero because cosine is a periodic function. The only remaining term is $\cos(\theta_1 - \theta_2)$.

$$\bar{E} = \frac{L_1}{2} \cdot I_{1,RMS}^2 + \frac{L_2}{2} \cdot I_{2,RMS}^2 + \frac{M \cdot I_1 \cdot I_2}{2 \cdot T} \cdot \int_0^T \cos(\theta_1 - \theta_2) \cdot dt$$

$$\bar{E} = \frac{L_1}{2} \cdot I_{1,RMS}^2 + \frac{L_2}{2} \cdot I_{2,RMS}^2 + \frac{M \cdot I_1 \cdot I_2}{2 \cdot T} \cdot \cos(\theta_1 - \theta_2) \cdot T$$

$$\bar{E} = \frac{L_1}{2} \cdot I_{1,RMS}^2 + \frac{L_2}{2} \cdot I_{2,RMS}^2 + \frac{M \cdot I_1 \cdot I_2}{2} \cdot \cos(\theta_1 - \theta_2)$$

$$\bar{E} = \frac{L_1}{2} \cdot I_{1,RMS}^2 + \frac{L_2}{2} \cdot I_{2,RMS}^2 + M \cdot I_{1,RMS} \cdot I_{2,RMS} \cdot \cos(\theta_1 - \theta_2)$$

In the end result we can see that the average energy stored in the mutual inductor at the AC steady state depends only on the RMS values of the currents and the cosine of the relative phase between the currents. If the phase difference is equal to zero then the relation simply drops to:

$$\bar{E} = \frac{L_1}{2} \cdot I_{1,RMS}^2 + \frac{L_2}{2} \cdot I_{2,RMS}^2 + M \cdot I_{1,RMS} \cdot I_{2,RMS}$$

Second Method:

By computing the complex power of the system:

$$S = P + jQ$$

Since, $Q_{mutual\ inductor} = 2 \cdot \omega \cdot E_{avg}$

By finding the Q in the complex power, we can eventually solve for the average energy stored in the mutual inductor.

For any component power can be written as:

$$S = P + jQ = \frac{1}{2} \cdot I^* \cdot V$$

in phasor domain. (note that V and I are voltage and current phasors, respectively; and star (*) indicates the conjugate of the current)

From the mutual inductor equation:

$$P + jQ = \frac{1}{2} \cdot (I_1^* \quad I_2^*) \cdot j \cdot \omega \cdot \begin{pmatrix} L_1 & M \\ M & L_2 \end{pmatrix} \cdot \begin{pmatrix} I_1 \\ I_2 \end{pmatrix}$$

$$P + jQ = \frac{1}{2} \cdot j \cdot \omega \cdot (I_1^* \cdot L_1 + M \cdot I_2^* \quad I_1^* \cdot M + I_2^* \cdot L_2) \cdot \begin{pmatrix} I_1 \\ I_2 \end{pmatrix}$$

$$P + jQ = \frac{1}{2} \cdot j \cdot \omega \cdot (I_1 \cdot I_1^* \cdot L_1 + M \cdot I_1^* \cdot I_2 + I_1 \cdot I_2^* \cdot M + I_2 \cdot I_2^* \cdot L_2)$$

$$I_1 \cdot I_1^* = |I_1|^2$$

$$I_2 \cdot I_2^* = |I_2|^2$$

$$I_1 \cdot I_2^* = |I_1| \cdot |I_2| \cdot e^{j(\theta_1 - \theta_2)}$$

$$I_2 \cdot I_1^* = |I_1| \cdot |I_2| \cdot e^{j(\theta_2 - \theta_1)}$$

By inserting these values we obtain:

$$P + jQ = \frac{1}{2} \cdot j \cdot \omega \cdot (|I_1|^2 \cdot L_1 + M \cdot |I_1| \cdot |I_2| \cdot e^{j(\theta_1 - \theta_2)} + M \cdot |I_1| \cdot |I_2| \cdot e^{j(\theta_2 - \theta_1)} + |I_2|^2 \cdot L_2)$$

The terms that have M can be arranged as:

$$M \cdot |I_1| \cdot |I_2| \cdot (e^{j(\theta_1 - \theta_2)} + e^{-j(\theta_1 - \theta_2)})$$

Sum of the exponential terms is equal to:

$$(e^{j(\theta_1 - \theta_2)} + e^{-j(\theta_1 - \theta_2)}) = 2 \cdot \cos(\theta_1 - \theta_2)$$

By combining these values:

$$P + jQ = \frac{1}{2} \cdot j \cdot \omega \cdot (|I_1|^2 \cdot L_1 + 2 \cdot M \cdot |I_1| \cdot |I_2| \cdot \cos(\theta_1 - \theta_2) + |I_2|^2 \cdot L_2)$$

As we can see, the right hand side does not have a real component. Therefore, P is equal to zero.

$$jQ = \frac{1}{2} \cdot j \cdot \omega \cdot (|I_1|^2 \cdot L_1 + 2 \cdot M \cdot |I_1| \cdot |I_2| \cdot \cos(\theta_1 - \theta_2) + |I_2|^2 \cdot L_2)$$

$$\frac{Q}{2 \cdot \omega} = \frac{1}{2} \cdot \frac{1}{2} \cdot (|I_1|^2 \cdot L_1 + 2 \cdot M \cdot |I_1| \cdot |I_2| \cdot \cos(\theta_1 - \theta_2) + |I_2|^2 \cdot L_2)$$

By distributing one of the 1/2 coefficients inside the equation, we obtain RMS values for each current component. Then,

$$\frac{Q}{2 \cdot \omega} = \frac{1}{2} \cdot (I_{1,RMS}^2 \cdot L_1 + 2 \cdot M \cdot I_{1,RMS} \cdot I_{2,RMS} \cdot \cos(\theta_1 - \theta_2) + I_{2,RMS}^2 \cdot L_2)$$

From, $Q_{mutual\ inductor} = 2 \cdot \omega \cdot E_{avg}$

$$E_{avg} = \frac{Q}{2 \cdot \omega} = \frac{1}{2} \cdot (I_{1,RMS}^2 \cdot L_1 + I_{2,RMS}^2 \cdot L_2 + 2 \cdot M \cdot I_{1,RMS} \cdot I_{2,RMS} \cdot \cos(\theta_1 - \theta_2))$$

Hence we obtained the same result with the first method:

$$\bar{E} = \frac{L_1}{2} \cdot I_{1,RMS}^2 + \frac{L_2}{2} \cdot I_{2,RMS}^2 + M \cdot I_{1,RMS} \cdot I_{2,RMS} \cdot \cos(\theta_1 - \theta_2)$$