

1) Given the system function $H(s) = \frac{30(s+1)}{s^2+8s+15}$.

- (a) Plot the pole/zero diagram.
(b) Sketch the magnitude and phase characteristics.

2) Given the transfer admittance $Y_T(s) = \frac{s^2+9}{s^2+10s+16} \text{ v.}$



- (a) Plot the pole/zero diagram.
(b) Sketch the magnitude and phase characteristics.
(c) Find the steady-state response to the excitation

$$24 + 6 \cos(3t + 15^\circ) - 5 \sin(4t - 72^\circ) \text{ V.}$$

3)(a) Obtain the transfer voltage ratio.

(b) Plot the pole/zero diagram.

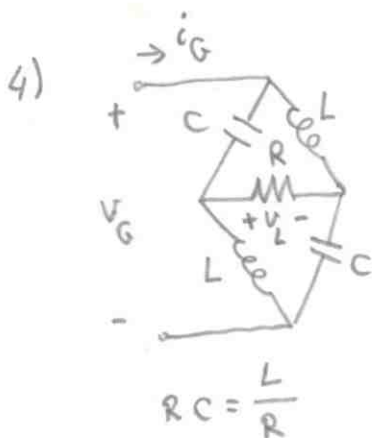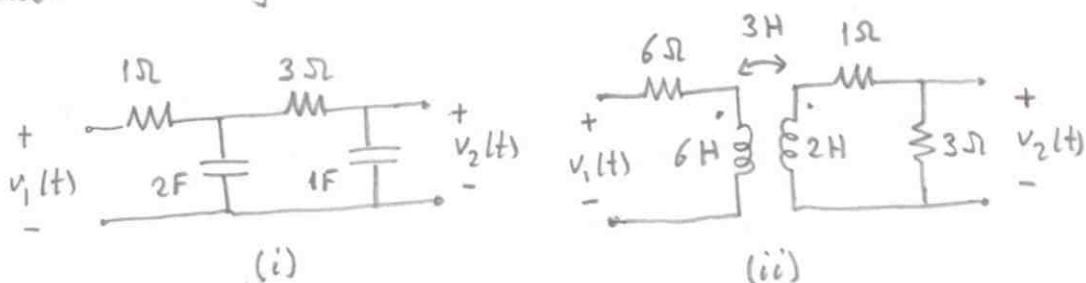(c) Sketch the magnitude and phase characteristics.



(a) Find the natural frequencies.


(b) Obtain the input admittance $Y_{in}(s) = \frac{I_G(s)}{V_G(s)}$.

(c) Obtain the transfer voltage ratio $H(s) = \frac{V_L(s)}{V_G(s)}$.

Plot the pole/zero diagram.

Sketch the magnitude and phase characteristics.


5)

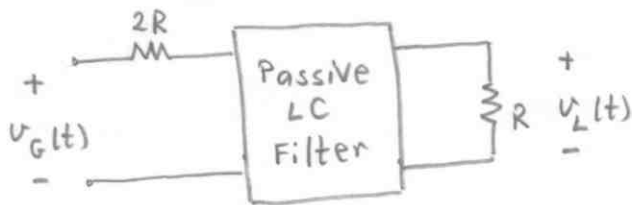

$H(s) = \frac{V_L(s)}{V_G(s)}$ is a second order bandpass transfer function.

- (a) Let $R=1 \Omega$. Provide two filter structures and determine the element values so that the peak frequency is 1 rad/sec and the half-power bandwidth is 0.5 rad/sec .
- (b) Sketch the magnitude and phase characteristics.
- (c) Scale the circuits so that the peak frequency is 4 KHz and $R=2 \text{ K}\Omega$.
- (d) Compare the two structures. Comment.

6)

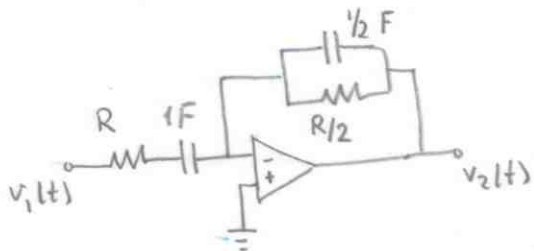

- (a) Let $R=2 \Omega$. Obtain the transfer function $H(s) = V_2(s)/V_1(s)$. Plot the pole/zero diagram. Sketch the magnitude and phase characteristics.
- (b) Scale the circuit so that $R=10 \text{ K}\Omega$ and the magnitude response function peaks at 4 Krad/sec .


7) The magnitude response function of the n th order ($n=1,2,3,\dots$) lowpass Butterworth filter of cutoff frequency ω_0 is

$$|H(j\omega)| = 1 / \sqrt{1 + (\omega/\omega_0)^{2n}}$$

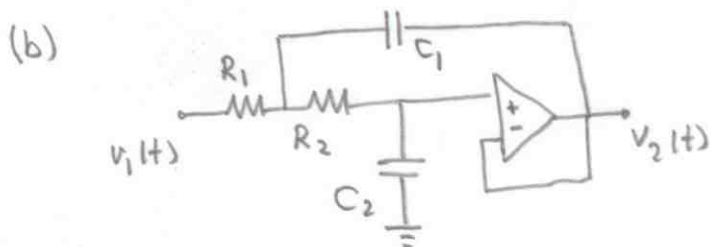
(a) The transfer function of a second order lowpass Butterworth filter is

$$H(s) = \frac{\omega_0^2}{s^2 + 2\alpha s + \omega_0^2}$$


Find the $Q = \frac{\omega_0}{2\alpha}$ of this filter.



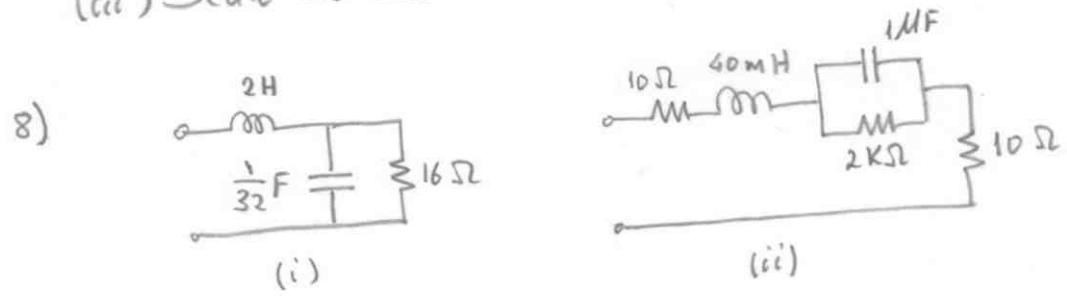- (i) Obtain the transfer function $H(s) = V_2(s)/V_1(s)$.
- (ii) Design the circuit so that $H(s)$ is the second order lowpass Butterworth filter transfer function with $\omega_0 = 1$ rad/sec.
- (iii) Scale the circuit so that $R_1 = 10$ k Ω and $\omega_0 = 2\pi \cdot 10^3$ rad/sec.



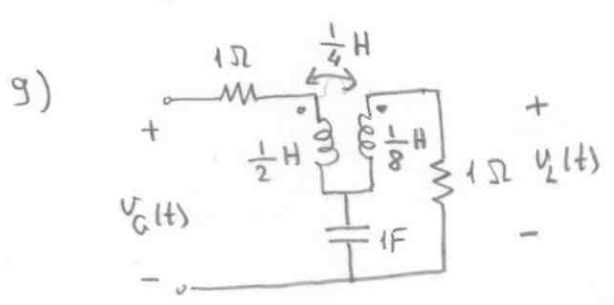- (a) Obtain the input impedance. Plot the pole/zero diagram.
- (b) Find the resonant frequency ω_0 .
- (c) Sketch the approximate magnitude and phase characteristics.
- (d) For the input voltage $V_m \cos(\omega_0 t + \theta_s)$, P is the average power input and E is the sum of the average stored energies in the dynamic elements. Compute $\omega_0 E/P$. Discuss.



- (a) Obtain the transfer function $H(s) = \frac{V_2(s)}{V_0(s)}$.
- (b) Plot the pole/zero diagram.
- (c) Sketch the magnitude and phase characteristics.
- (d) Obtain the magnitude and phase Bode plots.

10) Plot the pole/zero diagram. Obtain the magnitude and phase Bode plots.

(a) $H(s) = \frac{100s(s+200)}{(s+20)(s+1000)}$, (b) $H(s) = \frac{40s^2}{(s+20)(s^2+s+4)}$, (c) $H(s) = \frac{s^2+100s+10^4}{(s+10)^2}$