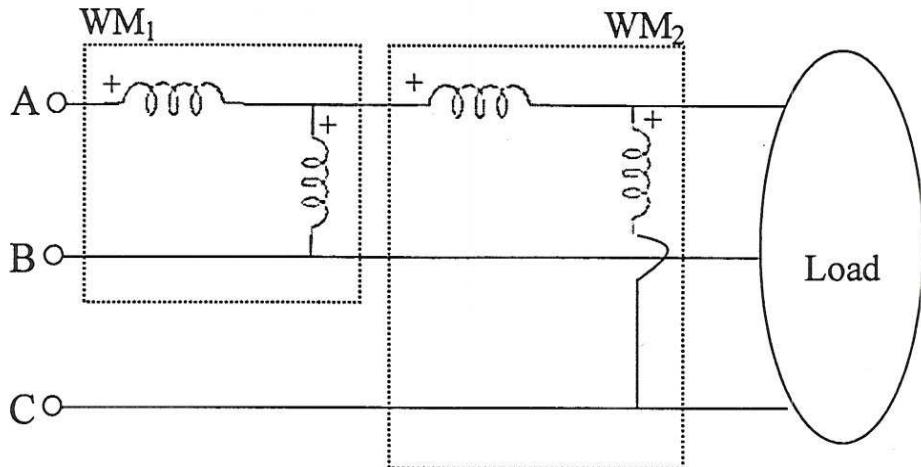


Question 4 (17 pts) Given the following balanced 3-phase system with positive phase sequence, express the readings of wattmeters WM₁ and WM₂ in terms of the total real power P and the total reactive power Q of the load.



$$V_{An} = |V_m| \angle 0^\circ \quad V_{rms}$$

$$I_A = |I_m| \angle -\theta \quad A_{rms}$$

$$V_{Bn} = |V_m| \angle -120^\circ \quad V_{rms}$$

$$V_{Cn} = |V_m| \angle +120^\circ \quad V_{rms}$$

$$P = 3 |V_m| |I_m| \cos \theta \quad \& \quad Q = 3 |V_m| |I_m| \sin \theta$$

$$W_1 = Re \{ V_{AB} I_A^* \}$$

$$= Re \{ \sqrt{3} |V_m| \angle 30^\circ |I_m| \angle \theta \}$$

$$= \sqrt{3} |V_m| |I_m| \cos(\theta + 30^\circ)$$

$$= \sqrt{3} |V_m| |I_m| \{ \cos \theta \cos 30^\circ - \sin \theta \sin 30^\circ \}$$

$$= \frac{3}{2} |V_m| |I_m| \cos \theta - \frac{\sqrt{3}}{2} |V_m| |I_m| \sin \theta$$

$$= \frac{1}{2} P - \frac{1}{2\sqrt{3}} Q$$

$$W_2 = Re \{ V_{AC} I_A^* \}$$

$$= Re \{ \sqrt{3} |V_m| \angle -30^\circ |I_m| \angle \theta \}$$

$$= \sqrt{3} |V_m| |I_m| \cos(\theta - 30^\circ)$$

$$= \sqrt{3} |V_m| |I_m| \{ \cos \theta \cos 30^\circ + \sin \theta \sin 30^\circ \}$$

$$= \frac{3}{2} |V_m| |I_m| \cos \theta + \frac{\sqrt{3}}{2} |V_m| |I_m| \sin \theta$$

$$= \boxed{\frac{1}{2} P + \frac{1}{2\sqrt{3}} Q}$$