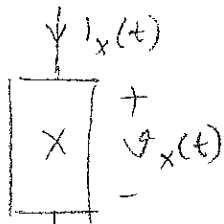


EE 202

EE 201 Review

Components: R, L, C, diode, op-amp, transformer etc.




$$i_c(t) = C \frac{d}{dt} v_c(t)$$



capacitance

$$v_c(t) = v_c(t_0^-) + \frac{1}{C} \int_{t_0^-}^t i_c(t) dt$$


Tau

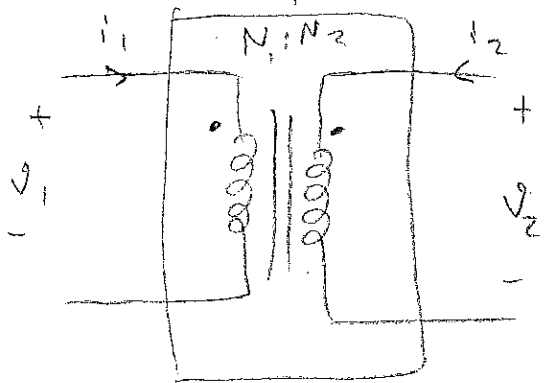

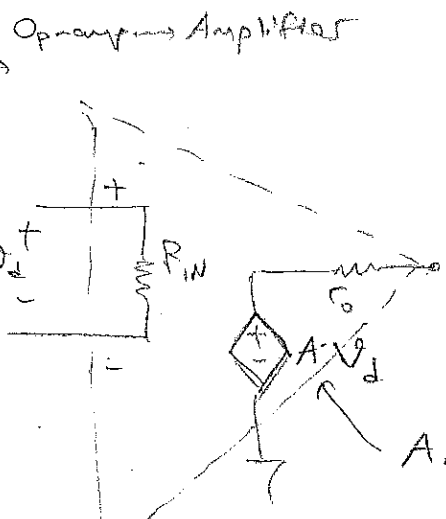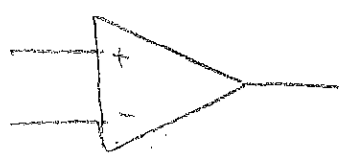
$$\frac{v_1}{v_2} = \frac{N_1}{N_2} ; \frac{i_1}{i_2} = -\frac{N_2}{N_1}$$



ideal diode

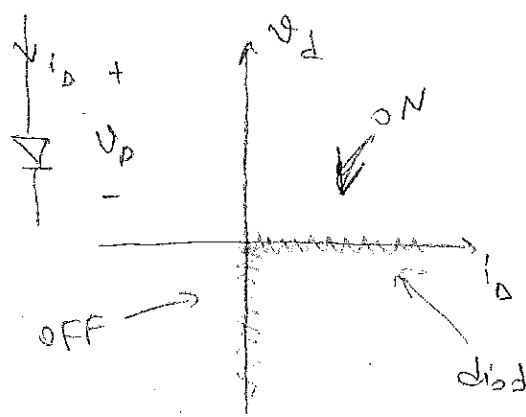


diode's allowable operating points

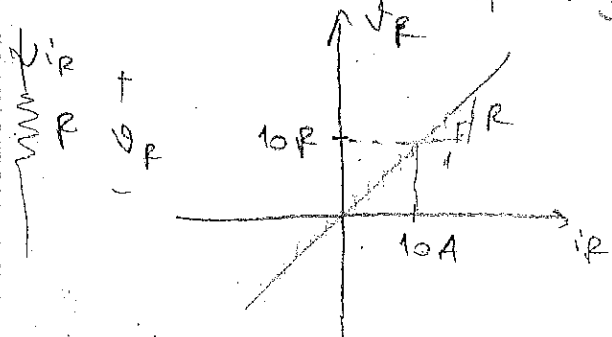

Circuits as Natural of Components




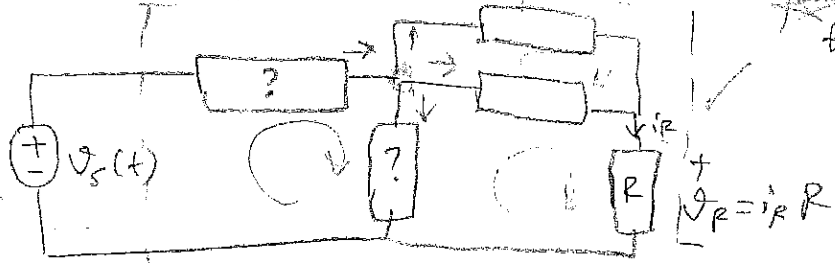
★ Don't forget the passive sign convention



External input: microphone, output of another system, thermometer reader...


Analysis problems: we need to satisfy

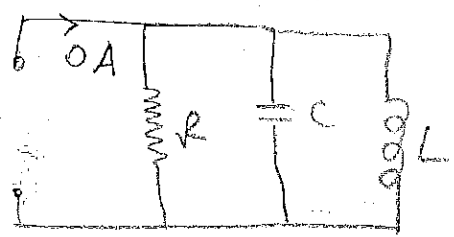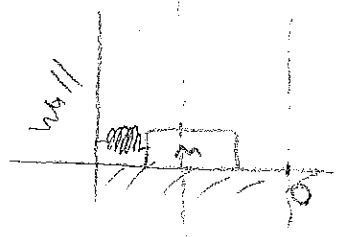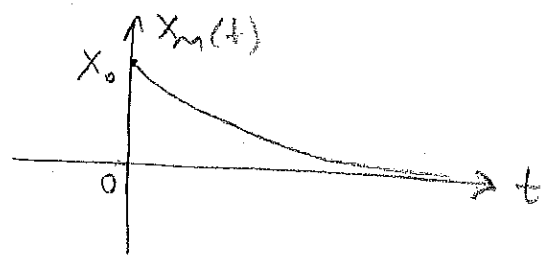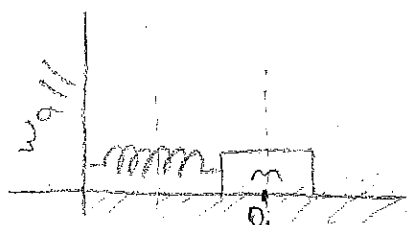- ① Component equation (terminal equation) of every branch.
- ② KVL - (Energy conservation)
- ③ KCL - (Charge conservation)



$$i_L(0^-) = I_0$$

$$V_C(0^-) = V_0$$

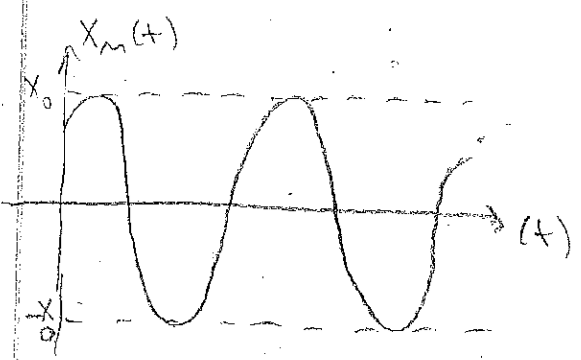


$$\left(D^2 + \frac{1}{RC} D + \frac{1}{LC} \right) V_C(t) = \frac{D}{LC} \{ V_S(t) \}$$


$$F_{\text{net}} = m \ddot{x}(t)$$

$$-F_{\text{spring}} + F_{\text{ext}} - F_{\text{fric}} = m \cdot \frac{d^2 x(t)}{dt^2}$$

\downarrow $k \cdot x(t)$

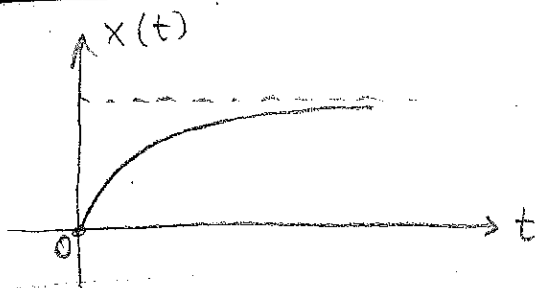

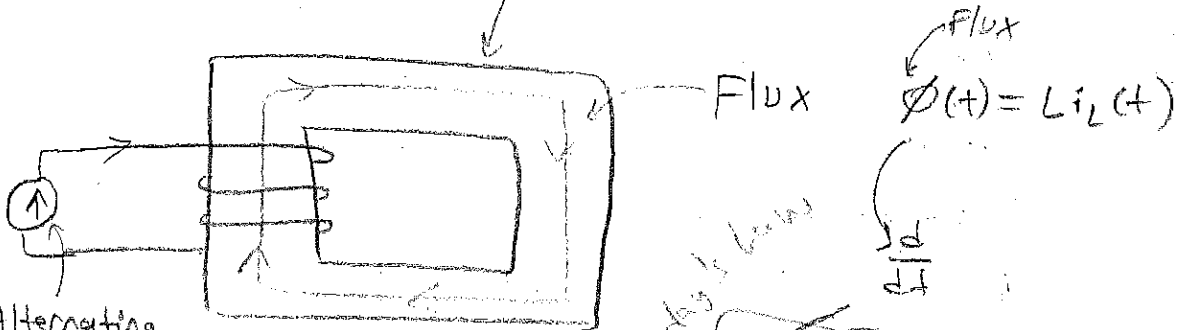Mutual Inductors Iron core (μ ; permeability is high)



Alternating current

Faraday's Law

$$\dot{\phi}(t) = \frac{d}{dt} (L(t) i_2(t))$$


$$V_L(t) = \left(\frac{d}{dt} L(t) \right) i_2(t) + L(t) \frac{d}{dt} i_2(t)$$

Special case; LTI inductor, $L(t) = L$

$$V_L(t) = L \frac{d}{dt} i_2(t)$$

Self-inductor; (classical inductor definition)

Mutual Inductor:

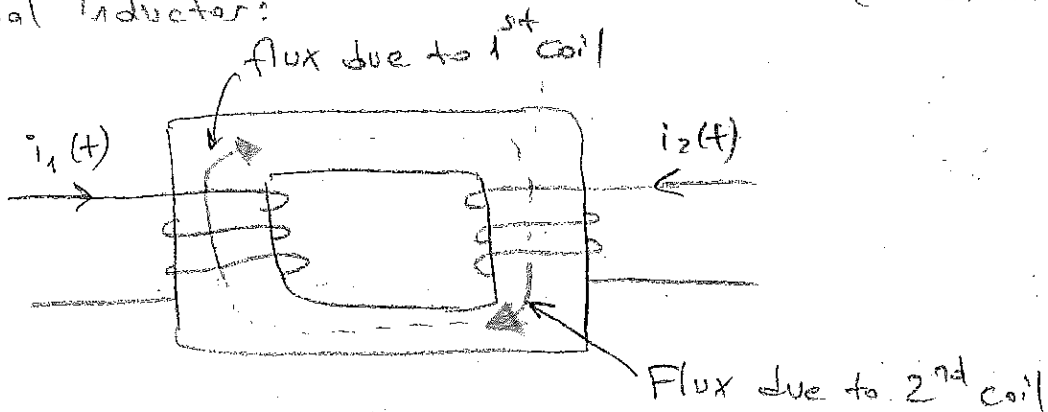

$$\phi_1 = L_1 \cdot i_1(t) + (M) i_2(t)$$

Total flux intercepted by 1st coil

Self inductance (H)

Mutual inductance (H)

the same number

$$\phi_2(t) = (M) i_1(t) + L_2 i_2(t)$$

Total flux intercepted by 2nd coil


$$\begin{bmatrix} \phi_1(t) \\ \phi_2(t) \end{bmatrix} = \begin{bmatrix} L_1 & M \\ M & L_2 \end{bmatrix} \begin{bmatrix} i_1(t) \\ i_2(t) \end{bmatrix}$$

$\frac{d}{dt}$

$$\begin{bmatrix} v_{L_1}(t) \\ v_{L_2}(t) \end{bmatrix} = \begin{bmatrix} L_1 & M \\ M & L_2 \end{bmatrix} \begin{bmatrix} \frac{d}{dt} i_1(t) \\ \frac{d}{dt} i_2(t) \end{bmatrix}$$


Mutual inductor terminal equation

it is mutual inductor

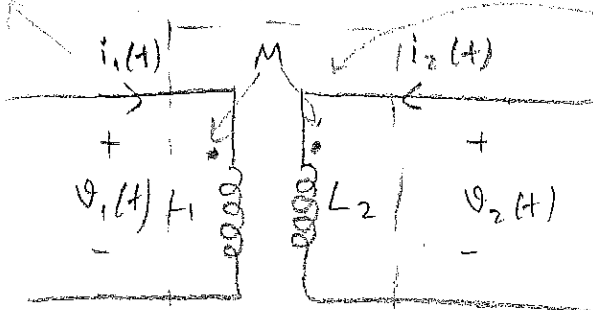


$$\begin{bmatrix} v_{L_1}(t) \\ v_{L_2}(t) \end{bmatrix} = \begin{bmatrix} L_1 & M \\ M & L_2 \end{bmatrix} \begin{bmatrix} \frac{d}{dt} i_{L_1}(t) \\ \frac{d}{dt} i_{L_2}(t) \end{bmatrix}$$

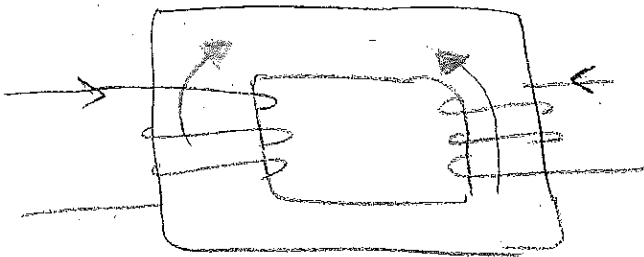Positive polarity of v_{L_1} and v_{L_2} is aligned with dot and $i_{L_1}(t)$ & $i_{L_2}(t)$ are entering L_1 to the dot.



Ex: (Series combination)

Passive sign convention!!

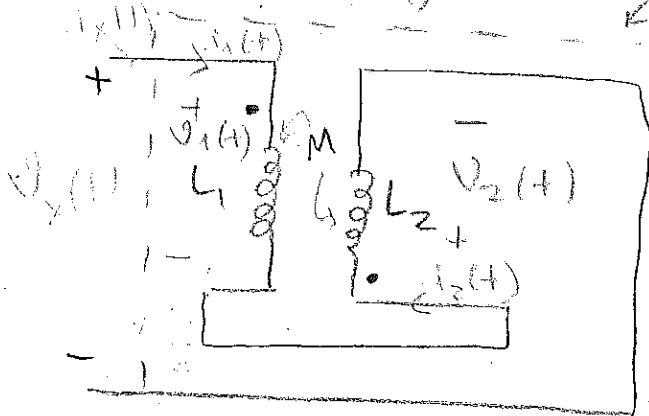

M: mutual inductance

$$\begin{bmatrix} v_{L_1}(t) \\ v_{L_2}(t) \end{bmatrix} = \begin{bmatrix} L_1 & M \\ M & L_2 \end{bmatrix} \begin{bmatrix} \frac{d}{dt} i_1(t) \\ \frac{d}{dt} i_2(t) \end{bmatrix} \quad (*)$$

Note! (1) $V_x(t) = V_{L_1}(t) + V_{L_2}(t)$

(2) $i_x(t) = i_1(t)$
 $i_x(t) = i_2(t)$

Then multiply from left of (*) by [1 1]

$$\begin{bmatrix} 1 & 1 \end{bmatrix} \begin{bmatrix} V_{L_1} \\ V_{L_2} \end{bmatrix} = \begin{bmatrix} 1 & 1 \end{bmatrix} \begin{bmatrix} L_1 & M \\ M & L_2 \end{bmatrix} \begin{bmatrix} \frac{d}{dt} i_x(t) \\ \frac{d}{dt} i_x(t) \end{bmatrix}$$

The 1-part is equivalent to an inductor with $(L_1 + L_2 + 2M)$ theory ???

$$V_x(t) = (L_1 + L_2 + 2M) \frac{d}{dt} i_x(t)$$

$$\underbrace{V_{L_1} + V_{L_2}}_{V_x(t)} = (L_1 + L_2 + 2M) \frac{d}{dt} i_x(t)$$


- If the dot were on the other side:

$$V_x(t) = V_{L_1}(t) - V_{L_2}(t)$$


$$i_x(t) = -i_2(t)$$

$$V_x(t) = (L_1 + L_2 - 2M) \frac{d}{dt} i_x(t)$$
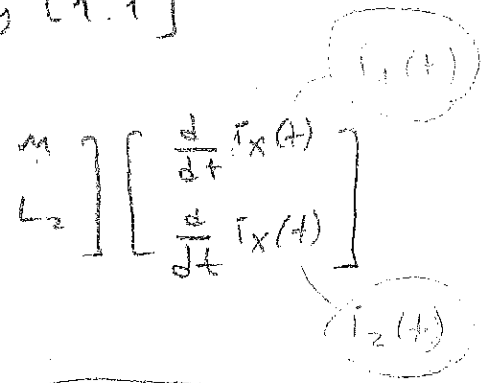
$$\underbrace{V_{L_1} + V_{L_2}}_{V_x(t)} = (L_1 + L_2 - 2M) \frac{d}{dt} i_x(t)$$




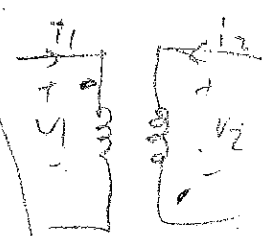
$$\begin{bmatrix} V_1(t) \\ V_2(t) \end{bmatrix} = \begin{bmatrix} L_1 & M \\ M & L_2 \end{bmatrix} \begin{bmatrix} \frac{d}{dt} i_1(t) \\ \frac{d}{dt} i_2(t) \end{bmatrix}$$



$$\begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} L_1 - M & M \\ M & L_2 \end{bmatrix} \begin{bmatrix} \frac{d}{dt} i_1 \\ \frac{d}{dt} i_2 \end{bmatrix}$$

Telecom

Mutual Inductance

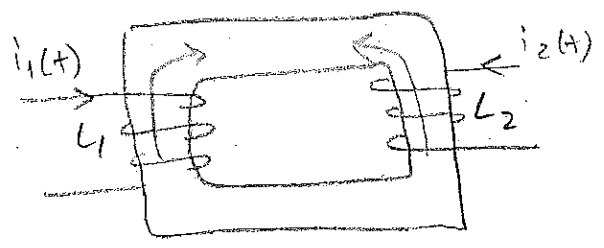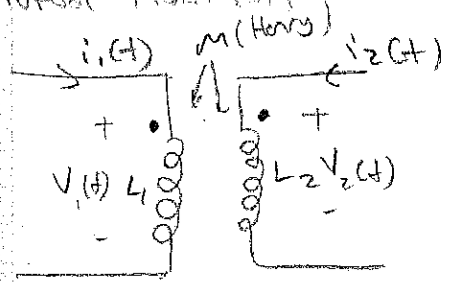



Circuit symbol

The dots are related to the winding directions: if the dots are on the same side the fluxes are constructive ($L_1 \dots + M \dots$)
 if dots are on opposite direction the fluxes are destructive ($L_1 \dots - M \dots$)

$$\begin{bmatrix} V_{L_1}(t) \\ V_{L_2}(t) \end{bmatrix} = \begin{bmatrix} L_1 & M \\ M & L_2 \end{bmatrix} \begin{bmatrix} \frac{d}{dt} i_{L_1}(t) \\ \frac{d}{dt} i_{L_2}(t) \end{bmatrix}$$

↳ only valid if incoming currents are coming to the dots.

3-coil Mutual Inductance

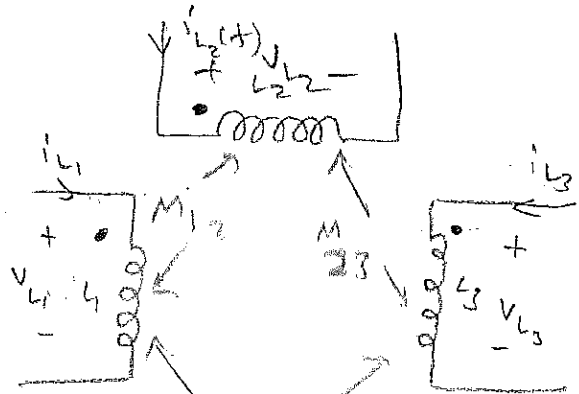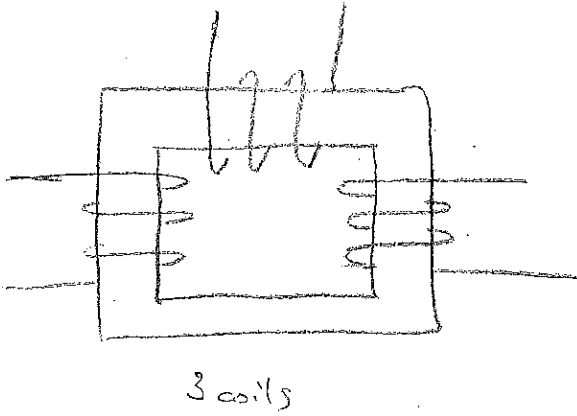


$$\begin{bmatrix} V_{L_1}(t) \\ V_{L_2}(t) \\ V_{L_3}(t) \end{bmatrix} = \underbrace{\begin{bmatrix} L_1 & M_{12} & M_{13} \\ M_{12} & L_2 & M_{23} \\ M_{13} & M_{23} & L_3 \end{bmatrix}}_L \begin{bmatrix} \frac{d}{dt} i_{L_1}(t) \\ \frac{d}{dt} i_{L_2}(t) \\ \frac{d}{dt} i_{L_3}(t) \end{bmatrix}$$


$L =$

L : symmetric matrix

$$(L^T = L)$$

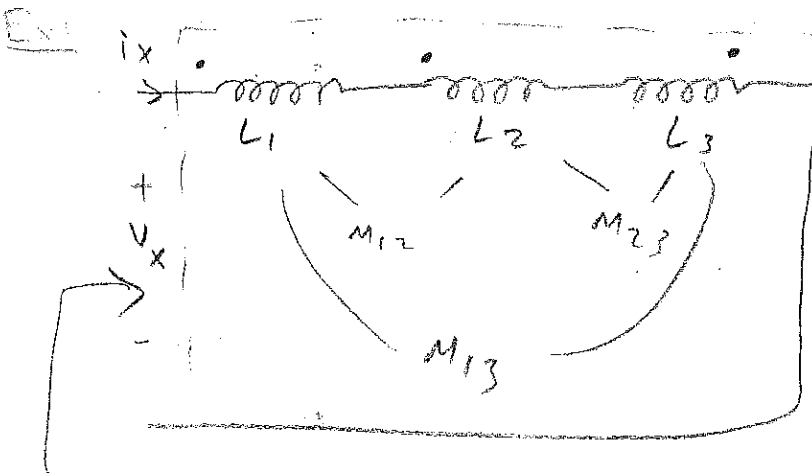


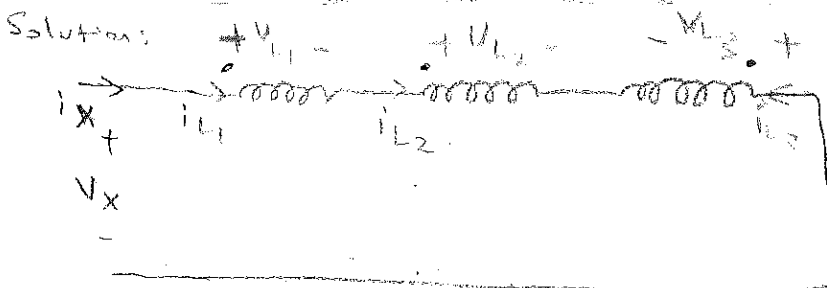What is the relation between V_x and i_x ?



$$V_x = -V_{L3} + V_{L2} + V_{L1}$$
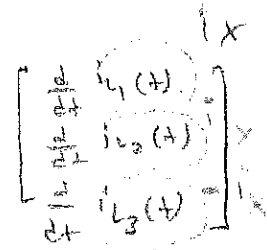
$$= [1 \ 1 \ -1] \begin{bmatrix} V_{L1} \\ V_{L2} \\ V_{L3} \end{bmatrix} = [1 \ 1 \ -1] L \frac{d}{dt} \begin{bmatrix} i_1(t) \\ i_2(t) \\ i_3(t) \end{bmatrix}$$



Mutual inductance terminal equations

$$V_x = [1 \ 1 \ -1] L \frac{d}{dt} i_x(t)$$


$$V_x = [(L_1 + M_{21} - M_{31}) + (L_2 + M_{12} - M_{32}) + (L_3 - M_{13} - M_{23})] \frac{d}{dt} i_x(t)$$

equivalent inductance value

★ If all mutual inductance ($M_{12}, M_{13}, M_{23}, \dots$) are 0 the answer must be equal to:

$$(L_1 + L_2 + L_3) \dots$$

Power and Energy Relations

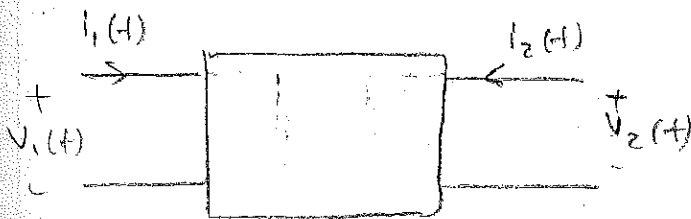

General formula for 2-ports

$$P(t) = i_1(t) V_1(t) + i_2(t) V_2(t)$$

$$= \begin{bmatrix} i_1(t) & i_2(t) \end{bmatrix} \begin{bmatrix} V_1(t) \\ V_2(t) \end{bmatrix}$$

$$= \underline{i(t)}^T \underline{V(t)}$$

$V(t)$

Notes: $\underline{x} = \begin{bmatrix} 1 \\ 2 \\ 3 \end{bmatrix}$ Under bar denotes a column vector.

$A = \begin{bmatrix} - & - & - \\ - & - & - \\ - & - & - \end{bmatrix}$ matrix

For mutual inductor:

$$P = (\underline{i(t)})^T \underline{V(t)} \quad \leftarrow \text{terminal equation for mutual inductors}$$

$$= \underline{i(t)}^T \cdot L \frac{d}{dt} \underline{i(t)}$$

$$L = \begin{bmatrix} L_1 & M \\ M & L_2 \end{bmatrix}$$

case:

$$P(t) = [i_1 \ i_2] \begin{bmatrix} L_1 & M \\ M & L_2 \end{bmatrix} \begin{bmatrix} \frac{d}{dt} i_1 \\ \frac{d}{dt} i_2 \end{bmatrix}$$


$$P(t) = L_1 i_1(t) \frac{d}{dt} i_1(t) + L_2 i_2(t) \frac{d}{dt} i_2(t)$$

$$+ M i_1(t) \frac{d}{dt} i_2(t) + M i_2(t) \frac{d}{dt} i_1(t)$$

$$P(t) = L_1 i_1(t) \frac{d}{dt} i_1(t) + L_2 i_2(t) \frac{d}{dt} i_2(t) + M \frac{d}{dt} (i_1 i_2)$$

Energy: work = $\Delta E = \int_{-\infty}^t P(z) dz$

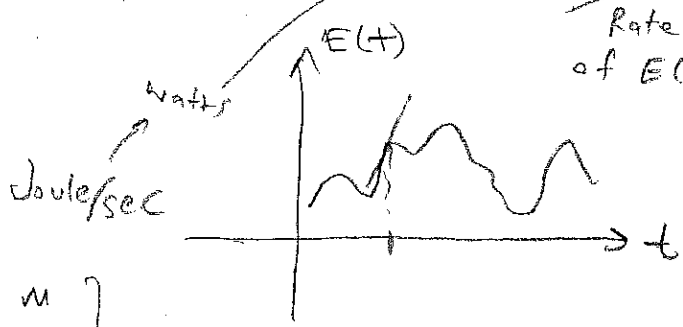$P(t) = \frac{d}{dt} E(t)$
Rate of change of $E(t)$



Case of $L = \begin{bmatrix} L_1 & M \\ M & L_2 \end{bmatrix}$

we assume at $-\infty$ the energy is 0 (zero)

$E(t) = \int_{-\infty}^t P(z) dz = \frac{1}{2} L_1 (i_{L_1}(t))^2 + \frac{1}{2} L_2 (i_{L_2}(t))^2 + M i_1(t) i_2(t)$

Joules

General case for $N \times N$ \underline{L} matrix:

$E(t) = \frac{1}{2} (\underline{i}(t))^T \underline{L} \underline{i}(t)$ Joules

Properties of \underline{L} matrix: coupling coefficient and all coupled inductor

① Mutual inductor is a passive component.

$E(t)_{mut ind.} \geq 0, \forall(t)$

$\frac{1}{2} (\underline{i}(t))^T \underline{L} \underline{i}(t) \geq 0, \forall(t)$ and $\forall i(t)$ vector function.

In mathematics,

If $\underline{x}^T \underline{A} \underline{x} \geq 0 \forall \underline{x}$, condition is satisfied

then \underline{A} matrix is called positive semi-definite matrix.

Then, \underline{L} is a positive semi-definite matrix.

For 2×2 \underline{L} matrices, that is $\underline{L} = \begin{bmatrix} L_1 & M \\ M & L_2 \end{bmatrix}$

positive semi-definiteness is equivalent to

- ① $L_1 \geq 0$
- ② $L_2 \geq 0$
- ③ $\det(\underline{L}) \geq 0$

these 3 conditions are satisfied.

$\rightarrow L_1 L_2 - M^2 \geq 0$


$M \leq \sqrt{L_1 L_2}$

Coupling coefficient: $k = \frac{M}{\sqrt{L_1 L_2}}$, clearly $0 \leq k \leq 1$
 Coupling coefficient

Mutual inductors are said to be fully coupled if $k=1$

Ideal Transformers

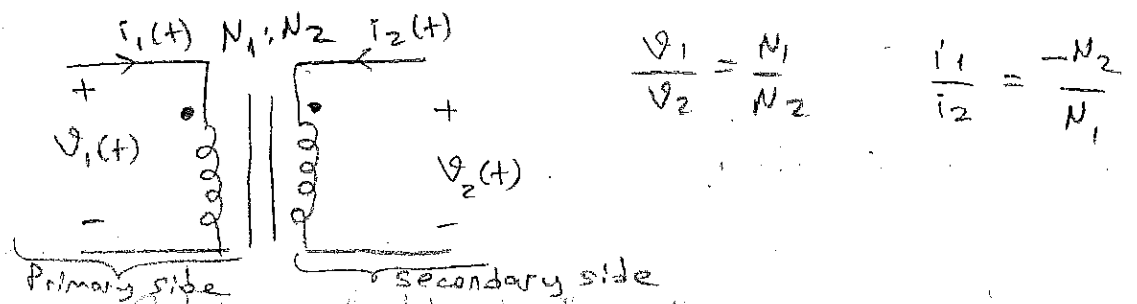Ideal transformers are mutual inductors with fully coupled inductors ($k=1$) and there is no ohmic loss in the ideal transformer.



$$\frac{V_1}{V_2} = \frac{N_1}{N_2} \quad \frac{i_1}{i_2} = -\frac{N_2}{N_1}$$

Power Relation of Ideal Transformer


$$P(t) = \sum_{k=1}^2 i_k(t) V_k(t) = i_1 V_1 + i_2 V_2$$

$$= i_1 V_1 + \left(-\frac{N_1}{N_2} i_1\right) \left(\frac{N_2}{N_1} V_1\right)$$

$$= 0$$

$P(t) = 0$ Watts
 for ideal transformer!

Resistance Reflection

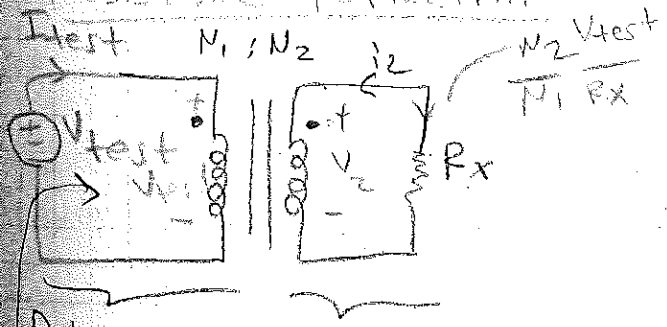

R_{in} : resistance seen from primary side.

$$R_{in} = \frac{V_{test}}{I_{test}}$$

Primary side

Secondary side

$$V_2 = \frac{N_2}{N_1} V_{test} \quad i_2 = -\frac{N_2}{N_1} \frac{V_{test}}{R_x}$$


$R_{in} = ?$

$$R_{in} = \frac{V_{test}}{I_{test}} = \frac{V_{test}}{-\frac{N_2}{N_1} \left(-\frac{N_2}{N_1} \frac{V_{test}}{R_x}\right)}$$


$$i_1 = -\frac{N_2}{N_1} i_2$$

$$R_{in} = R_x \left(\frac{N_1}{N_2}\right)^2$$

Ex:

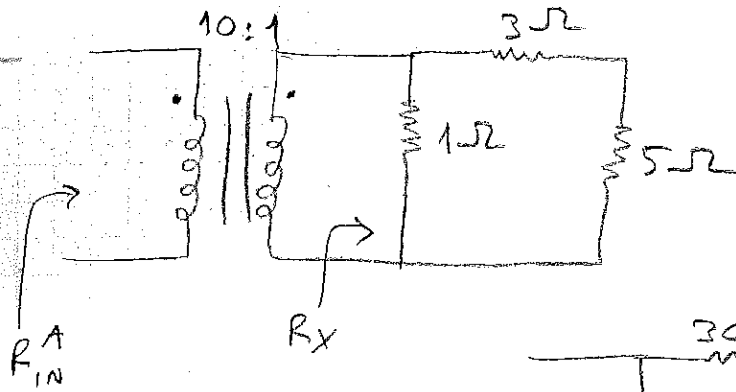

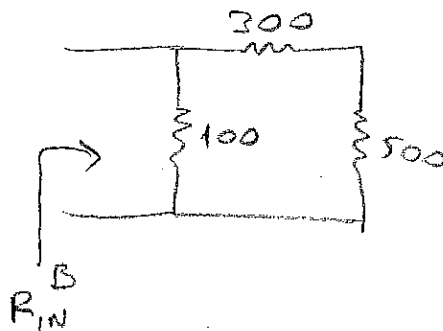
It should be clear that $R_{IN}^A = R_{IN}^B$



Use of Transformers

Pls. check Sadiku's book on transformers/mutual inductors and their applications.


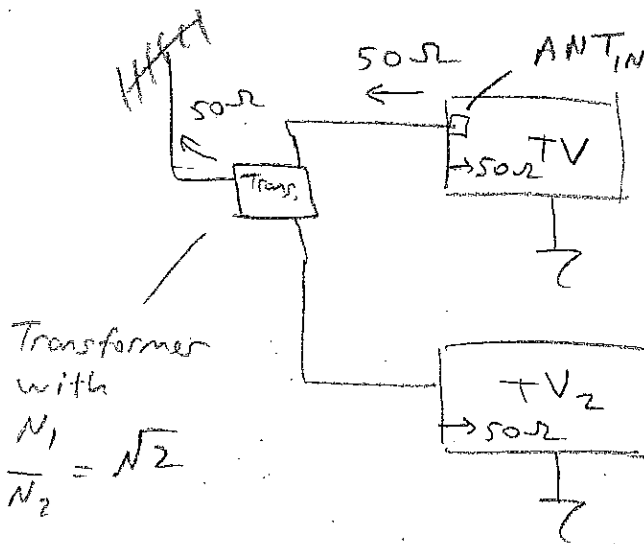
1) Impedance (Resistive) Matching (Active max. power transfer)



Transformer with $\frac{N_1}{N_2} = \sqrt{2}$

2) Electrical and Magnetic Decoupling

Coupling is through magnetic flux

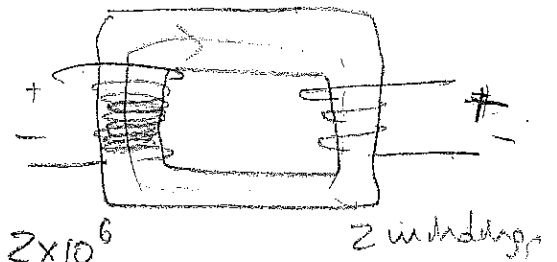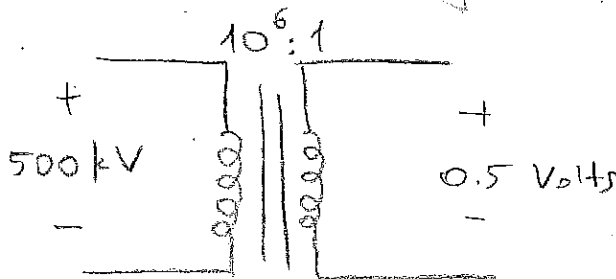


$\frac{N_1}{N_2} = 10^6$

★ Check Sadiku's book for more uses of transformers.

There is no electrical connection between two sides.

State Equations

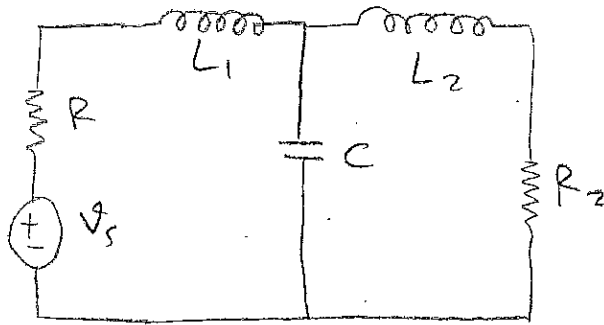The order of the circuit \leq the number of dynamic elements.



Goal: Analysis of N^{th} order circuits.

Assume that the variable of interest is $v_c(t)$, then given the input ($v_s(t)$) and initial conditions I need to find the solution of a differential equation for the unknown $v_c(t)$.

For a 3rd order circuit, a possible differential equation is

Scalar differentiation for $v_c(t)$

$$(D^3 + 3D^2 + 2D + 1)v_c(t) = 4v_s(t) \leftarrow \text{differential equation for } v_c(t)$$

Initial condition set

$$v_c(0^-) = v_0$$

$$\dot{v}_c(0^-) = \dot{v}_0$$

$$\ddot{v}_c(0^-) = \ddot{v}_0$$

State equation:

$$\dot{X} = \begin{bmatrix} v_c(t) \\ I_{L_1}(t) \\ I_{L_2}(t) \end{bmatrix} \leftarrow \text{state vector}$$

3rd order matrix differential equation

$$\begin{bmatrix} \dot{v}_c(t) \\ \dot{I}_{L_1}(t) \\ \dot{I}_{L_2}(t) \end{bmatrix} = \begin{bmatrix} \cdot & \cdot & \cdot \\ \cdot & \cdot & \cdot \\ \cdot & \cdot & \cdot \end{bmatrix} \begin{bmatrix} v_c(t) \\ I_{L_1}(t) \\ I_{L_2}(t) \end{bmatrix} + \begin{bmatrix} \cdot \\ \cdot \\ \cdot \end{bmatrix} v_s(t)$$

Set of initial I.C. (conditions)


$$\begin{bmatrix} v_c(0^-) \\ I_{L_1}(0^-) \\ I_{L_2}(0^-) \end{bmatrix} = \begin{bmatrix} v_0 \\ I_{L_1} \\ I_{L_2} \end{bmatrix}$$

Goal: Expressing the circuit as

$$\dot{X}(t) = \underline{A} X(t) + \underline{b} v_s(t) \left\} \text{state equation}$$

$$X(0^-) = X_0$$

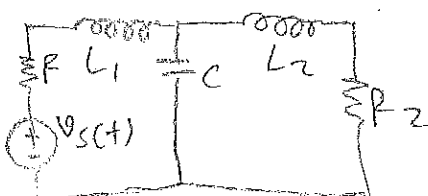
Ex: Let's find the state equation for the given circuit.



State variables = $\{v_c(t), I_{L_1}(t), I_{L_2}(t)\}$

1st row of $\rightarrow \dot{V}_c(t) = ? \cdot V_c(t) + ? \cdot i_{L_1}(t) + ? \cdot i_{L_2}(t) + ? \cdot V_s(t)$

$$\dot{X}(t) = A X(t) + b V_s(t)$$

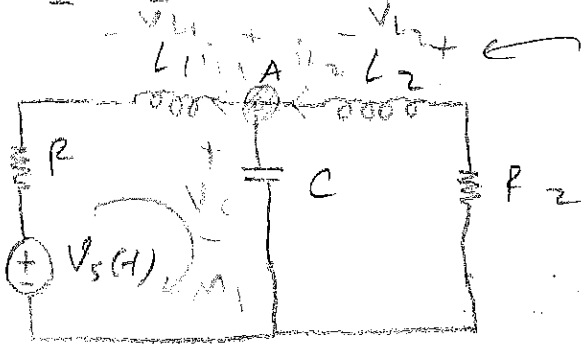

we assign the directions randomly.

$$\text{KCL at A: } C \dot{V}_c(t) = -i_{L_1}(t) + i_{L_2}(t)$$

state variable derivative


a linear combination state variable

$$\text{KVL at } \mathcal{M}_1: -V_s(t) + (-R i_{L_1}) - \underbrace{V_{L_1}(t)}_{L_1 \dot{I}_{L_1}(t)} + V_c = 0$$

$$\text{Mesh } \mathcal{M}_2: -V_c - \underbrace{V_{L_2}(t)}_{L_2 \dot{I}_{L_2}(t)} + R_2 (-i_{L_2}) = 0$$

$$\begin{bmatrix} \dot{V}_c(t) \\ \dot{I}_{L_1}(t) \\ \dot{I}_{L_2}(t) \end{bmatrix} = \begin{bmatrix} 0 & -1/C & 1/C \\ 1/L_1 & -R/L_1 & 0 \\ -1/L_2 & 0 & -R_2/L_2 \end{bmatrix} \begin{bmatrix} V_c(t) \\ I_{L_1}(t) \\ I_{L_2}(t) \end{bmatrix} + \begin{bmatrix} 0 \\ -1/L_1 \\ 0 \end{bmatrix} V_s(t)$$

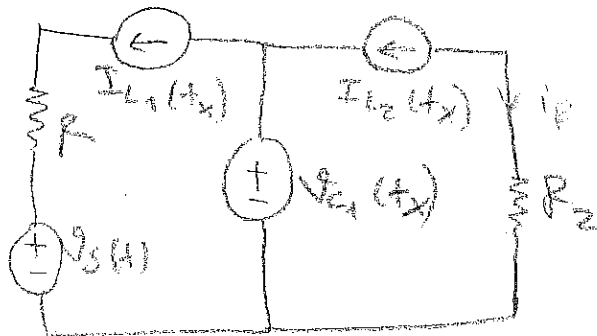Note: If the value of the state variables at time "t" is known, then all other circuit variables related with all other branches are a linear combination of state variables and input! for time "t"



At $t=t_x$

$$X(t_x) = \begin{bmatrix} 1 \text{ Volt} \\ 2 \text{ A} \\ 3 \text{ A} \end{bmatrix}$$

$$v_{R_2}(t_x) = \alpha_1 V_c(t_x) + \alpha_2 I_{L_1}(t_x) + \alpha_3 I_{L_2}(t_x) + \beta V_s(t_x)$$

linear combination coefficients

How to write state equations

- ① Select a proper tree (including dependent and independent sources)
- i) Put all voltage sources on the tree and put all current sources on the co-tree.



ii) If there's a transformer, place one port in the tree, the other port in the co-tree.

iii) Put maximum number of cap. on the tree. Put max. number of Ind. on co-tree.

② Write the fundamental loop equations for each inductor in co-tree.

③ Write the fun. cut-set equations for each cap. in the tree.

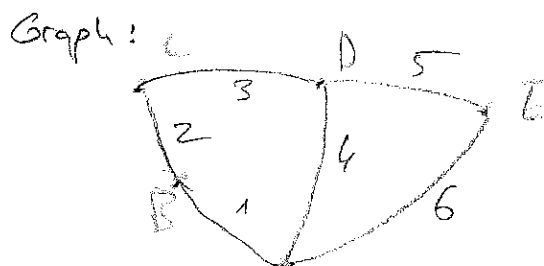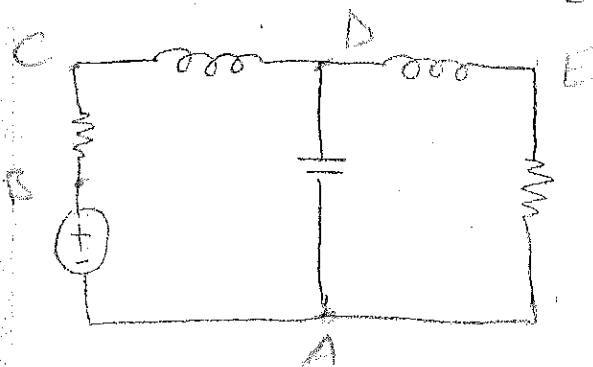State variables = $\left\{ \begin{array}{l} \text{Tree cap. voltages} \\ \text{Co-tree inductor currents} \end{array} \right\}$



Tree: A set of branches that
 ① does not form a loop

- ② reaches all the nodes.
- ③ Connected single piece

Co-tree = {2, 6}
 Tree = {4, 5, 3, 1}

(another) tree = {1, 2, 3, 5}
 Co-tree = {4, 6}

Fundamental loop: A loop whose all branches are from tree and a single branch from co-tree.

Link: A branch of co-tree

Co-tree: Remaining branches from tree.

Tree = {4, 5, 3, 1}, Co-tree = {2, 6}


For co-tree branch 2: Fun-loop: {1, 2, 3, 4}

" " " 6: " " : {4, 5, 6}

tree branch | Co-tree branch

Fundamental cut-set: A cut-set whose elements are all from co-tree except a single element from tree.


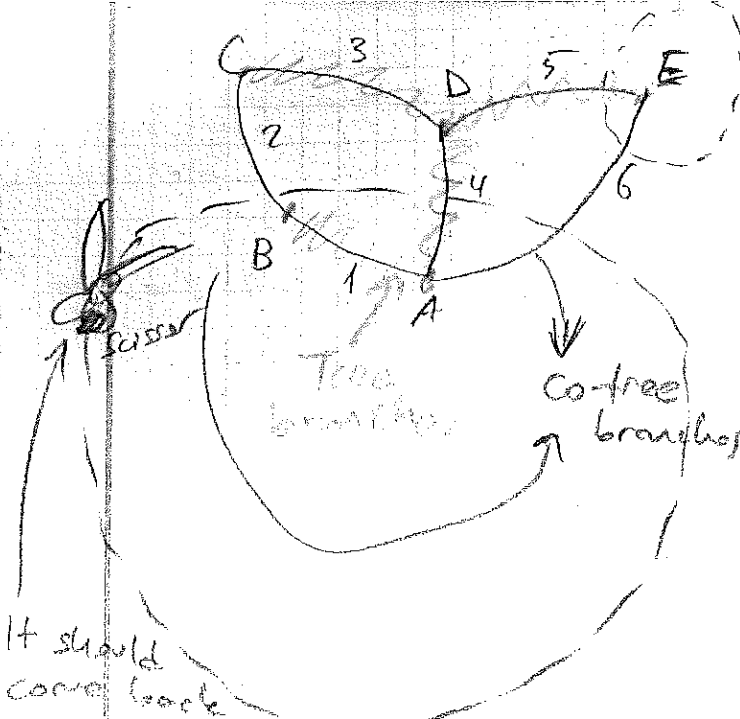
Cut-set: A set of branches whose removal separates the graph into two.



Fun. cut-set: Tree: $\{1, 3, 4, 5\}$
 Fun. cut-set for branch 1: $\{1, 2\}$
 " 3: $\{2, 3\}$
 " 4: $\{2, 4, 6\}$
 " 5: $\{5, 6\}$
 tree branches
 Co-tree branches

It should cover back to original place. It shouldn't cut the same branch twice.

Ex:

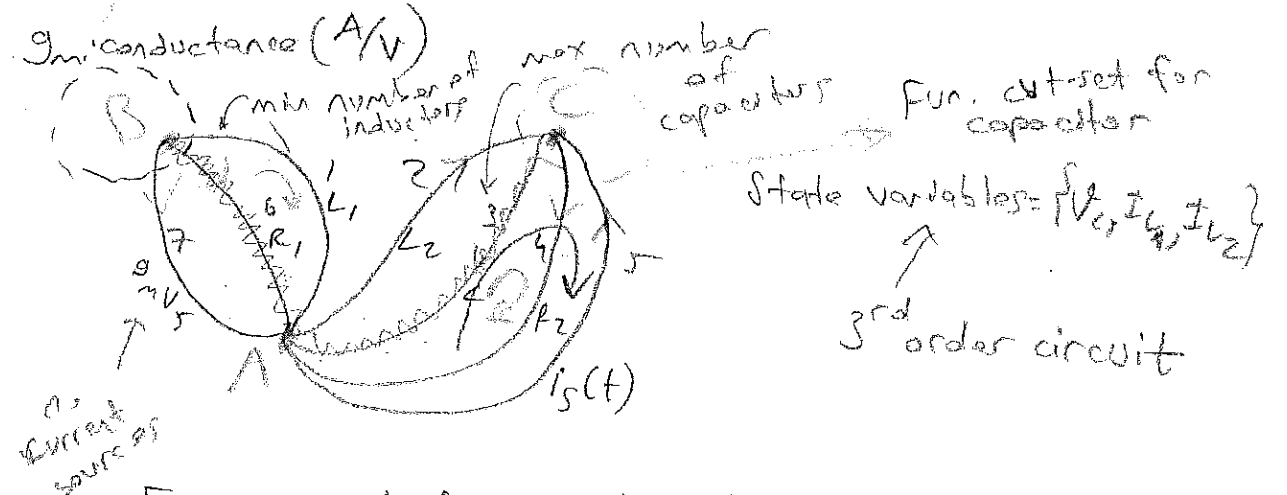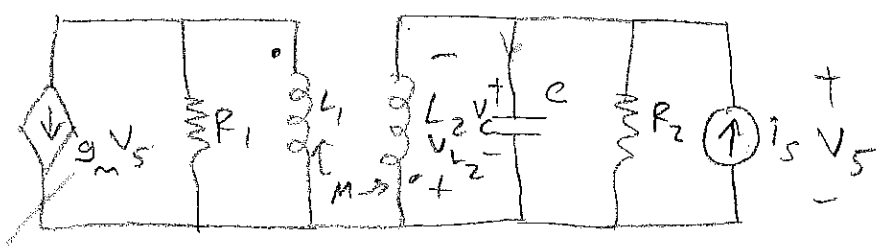

Fund. cut-set for cap. branch:

$$C \dot{V}_C(t) + i_{R2} - i_s(t) - i_{L2} = 0$$

↑ state variable
 ↓ Not a state variable

$$i_{R2} = \frac{V_{R2}}{R2} = \frac{V_C}{R2}$$

1st state equation →

$$\dot{V}_C(t) = \frac{1}{C} \left[-\frac{V_C}{R2} + I_{L2} + i_s(t) \right]$$

Fund. loop

State equations for I_{L1} and I_{L2} }
$$\begin{bmatrix} \dot{V}_{L1}(t) \\ \dot{V}_{L2}(t) \end{bmatrix} = \begin{bmatrix} L_1 & M \\ M & L_2 \end{bmatrix}^{-1} \begin{bmatrix} \frac{d}{dt} I_{L1}(t) \\ \frac{d}{dt} I_{L2}(t) \end{bmatrix}$$

Not a state variable

$$\begin{bmatrix} \dot{I}_{L1}(t) \\ \dot{I}_{L2}(t) \end{bmatrix} = \begin{bmatrix} L_1 & M \\ M & L_2 \end{bmatrix}^{-1} \begin{bmatrix} \dot{V}_{L1}(t) \\ \dot{V}_{L2}(t) \end{bmatrix}$$

F.L. F.C.

$$\dot{V}_{L1}(t) = \dot{V}_{R1} = R_1 \cdot \dot{i}_{R1} = R_1 (-g_m V_5 - i_{L1}) = R_1 (-g_m V_C - i_{L1})$$

Component eqn. (Ohm's Law)

$$V_5 = V_C$$

Fun loop

V_{L1} is in terms of state variables

F-loop


$$\dot{V}_{L2}(t) = -\dot{V}_C$$

$$\begin{bmatrix} \dot{V}_C(t) \\ \dot{I}_{L1}(t) \\ \dot{I}_{L2}(t) \end{bmatrix} = \begin{bmatrix} -\frac{1}{CR_2} & 0 & \frac{1}{C} \\ -\Gamma_1 R_1 g_m - \Gamma_1 R_1 & 0 & 0 \\ -\Gamma_2 & 0 & 0 \\ -\Gamma_3 R_1 g_m - \Gamma_3 R_1 & 0 & 0 \\ -R_4 & 0 & 0 \end{bmatrix} \begin{bmatrix} V_C(t) \\ I_{L1}(t) \\ I_{L2}(t) \end{bmatrix} + \begin{bmatrix} \frac{1}{C} \\ 0 \\ 0 \end{bmatrix} i_s(t)$$


$$\begin{bmatrix} \dot{I}_{L1}(t) \\ \dot{I}_{L2}(t) \end{bmatrix} = \begin{bmatrix} L_1 & M \\ M & L_2 \end{bmatrix}^{-1} \begin{bmatrix} -R_1 (g_m V_C + I_{L1}) \\ -V_C \end{bmatrix}$$

$$= \begin{bmatrix} \Gamma_1 & \Gamma_2 \\ \Gamma_3 & \Gamma_4 \end{bmatrix} \begin{bmatrix} -R_1 (g_m V_C + I_{L1}) \\ -V_C \end{bmatrix}$$

State Equations (cont'd)

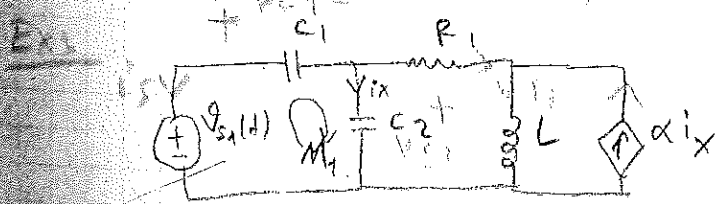

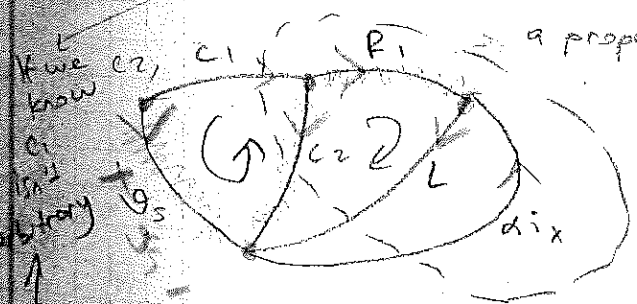Number of dynamic components = 3 = max possible order of the circuit



We know C_2, C_1, R_1 are not state variables

a proper tree (for state equation)

Another proper tree = $\{V_s, C_1, R_1\}$


State variables = $\{V_{C2}, I_L\}$

$$X(t) = \begin{bmatrix} V_{C2}(t) \\ I_L(t) \end{bmatrix}$$

$$\dot{X}(t) = A X(t) + b V_s(t) + \gamma \dot{V}_s(t)$$

We can see it by giving $V_{S1}(t) = 0V$

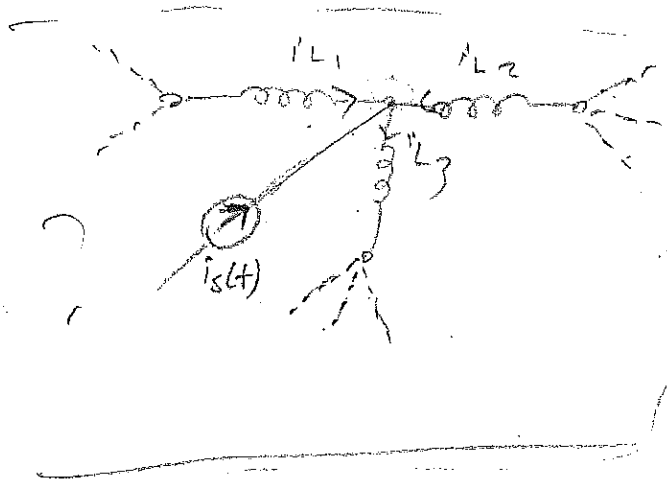Capacitive loops (such as in Mesh M_1) and inductive out-set results in the combination dynamic components and order of the circuit is related with the number of dynamic components after combination.



Finding $\dot{V}_{C_2}(t)$ in terms of state variables and input:

Fund. Cut-set for C_2 branch

$$\dot{I}_{C_2} = i_{C_1} - i_L + \alpha i_X$$

$C_2 \dot{V}_{C_2}$

$$i_X = C_2 \dot{V}_{C_2} \quad \checkmark$$

$$i_{C_1} = C_1 \dot{V}_{C_1} = C_1 (\dot{V}_S - \dot{V}_{C_2})$$

Component equation Fun. loop

$$C_2 \dot{V}_{C_2} = C_1 \dot{V}_S - C_1 \dot{V}_{C_2} - i_L + \alpha C_2 \dot{V}_{C_2}$$

$$\dot{V}_{C_2} = \frac{1}{(1-\alpha)C_2 + C_1} [-i_L + C_1 \dot{V}_S(t)]$$

First equation we need one for i_L too.

Finding $\dot{I}_L(t)$

Fund. loop for L branch:

$$V_L = -V_{R_1} + V_{C_2}$$

$L \cdot \dot{I}_L(t)$

$$V_{R_1} = R_1 \cdot i_{R_1} = R_1 (i_L - \alpha i_X)$$



Comp. Law.

$$L \dot{I}_L = -R_1 I_L + \alpha R_1 C_2 \dot{V}_{C_2} + V_{C_2}$$

After substitution

$\dot{I}_L(t)$ is expressed in terms of state variables (and input)

Ex:

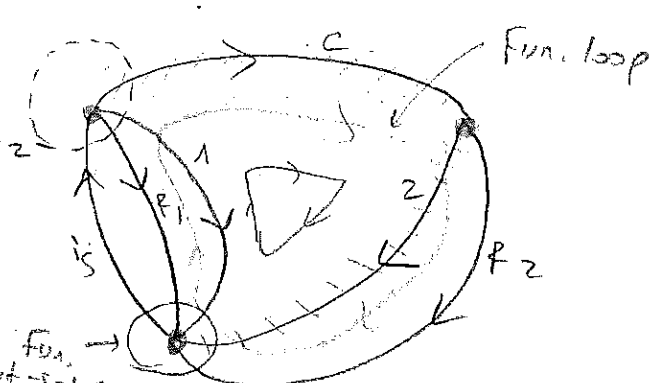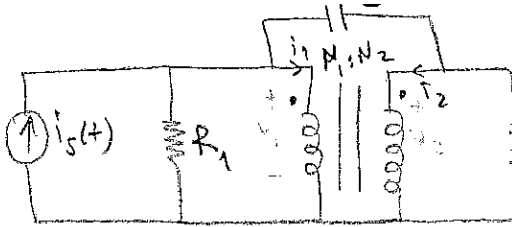

State variable = $\{V_c\}$

$\dot{V}_c(t)$

Fun. cut-set for C branch to find

$i_{R1} = ?$ (in terms of state variables)

$$i_{R1} = \frac{V_{R1}}{R1} = \frac{V_c + V_2}{R1}$$

$$i_c = i_s - i_{R1} - i_1$$

$$V_2 = \frac{N_2}{N_1} V_1 = \frac{N_2}{N_1} (V_c + V_2) \rightarrow V_2 = \frac{N_2}{N_1 - N_2} V_c$$

$$\frac{V_2}{V_1} = \frac{N_2}{N_1}$$

$$\frac{i_2}{i_1} = \frac{-N_1}{N_2}$$

$$i_{R1} = \frac{V_c}{R1} + \left(\frac{N_2}{N_1 - N_2} \right) \frac{1}{R1} V_c$$

$i_1 = ?$ (in terms of V_c)

$$i_1 = \frac{-N_2}{N_1} i_2 = \frac{-N_2}{N_1} (-i_{R2} + i_s - i_{R1} - i_1)$$

comp. law

$$(N_1 - N_2) i_1 = -N_2 (i_s - i_{R2} - i_{R1})$$

$$\dot{V}_c = i_s + \frac{-N_1}{N_1 - N_2} \left(\frac{V_c}{R1} + \left(\frac{N_2}{N_1 - N_2} \right) \frac{1}{R1} V_c \right) + \frac{N_2}{N_1 - N_2} \left(i_s - \frac{N_2}{(N_1 - N_2) R2} V_c \right)$$

already expressed in terms of V_c

$$i_{R2} = \frac{V_{R2}}{R2} = \frac{V_2}{R2} = \frac{N_2}{(N_1 - N_2) R2} V_c$$


1st order diff. eqn.

Suggested Problems

ZPS-1: State equations: 1a, 1b, 1c, 1d

Solution of State Equations

Ex2

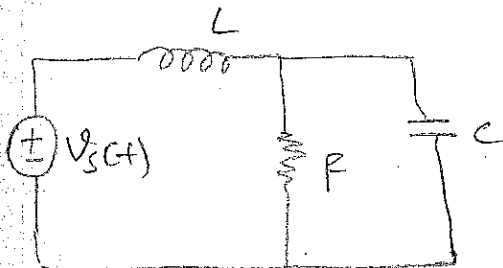

$$R = \frac{1}{3} \Omega, C = 1F, L = \frac{1}{2} H$$

$$\begin{bmatrix} \dot{V}_c(t) \\ \dot{I}_L(t) \end{bmatrix} = \begin{bmatrix} -3 & 1 \\ -2 & 0 \end{bmatrix} \begin{bmatrix} V_c(t) \\ I_L(t) \end{bmatrix} + \begin{bmatrix} 0 \\ 2 \end{bmatrix} V_s(t)$$

Note: The scalar differential equation for V_c can be written from state equations as:

$$\ddot{V}_c = -3\dot{V}_c + \dot{I}_L$$

$$\hookrightarrow -2\dot{V}_c + 2\dot{V}_s(t)$$

$$(\ddot{V}_c + 3\dot{V}_c + 2V_c) = 2V_s(t)$$

$$V_c(0^-) = \dots \quad 2^{\text{nd}} \text{ order scalar}$$

$$\dot{V}_c(0^-) = \dots \quad \text{dif. eq. for } V_c$$

Similarly

$$\ddot{I}_L = -2\dot{V}_c + 2\dot{V}_s$$

$$= -2(-3V_c + I_L)$$

$$\hookrightarrow V_c = -\frac{I_L}{2}$$

\uparrow
2nd state eqn.

So, I can also find a 2nd order dif. eqn. for I_L .

Case of zero-input solution:

$$V_s(t) = 0 \quad (\text{External input is not present anymore})$$

So, there is only initial energy stored in the circuit, and responses is due to the initial energy.

$$\text{Given: } \begin{bmatrix} V_c(0^-) \\ I_L(0^-) \end{bmatrix} = \begin{bmatrix} V_0 \\ I_0 \end{bmatrix} \xrightarrow{\text{guess}} \begin{bmatrix} V_c(t) \\ I_L(t) \end{bmatrix} = \begin{bmatrix} \alpha_1 e^{\lambda t} \\ \alpha_2 e^{\lambda t} \end{bmatrix}$$

For the guess to be correct, it should satisfy differential equation:

$$\dot{X}(t) = \begin{bmatrix} -3 & 1 \\ -2 & 0 \end{bmatrix} X(t) + \begin{bmatrix} 0 \\ 2 \end{bmatrix} V_s(t)$$

$$\lambda \begin{bmatrix} \alpha_1 \\ \alpha_2 \end{bmatrix} = \underbrace{\begin{bmatrix} -3 & 1 \\ -2 & 0 \end{bmatrix}}_A \begin{bmatrix} \alpha_1 \\ \alpha_2 \end{bmatrix} e^{\lambda t}$$

$$\lambda I \begin{bmatrix} \alpha_1 \\ \alpha_2 \end{bmatrix} = A \begin{bmatrix} \alpha_1 \\ \alpha_2 \end{bmatrix}$$

$$\begin{bmatrix} 1 & 0 \\ 0 & 1 \end{bmatrix}$$

$$(\lambda I - A) \begin{bmatrix} \alpha_1 \\ \alpha_2 \end{bmatrix} = \begin{bmatrix} 0 \\ 0 \end{bmatrix}$$

Note: If $(\lambda I - A)$ matrix is invertible.

$(\lambda I - A)^{-1}$ exists, then

$$\begin{bmatrix} \alpha_1 \\ \alpha_2 \end{bmatrix} = (\lambda I - A)^{-1} \begin{bmatrix} 0 \\ 0 \end{bmatrix} = \begin{bmatrix} 0 \\ 0 \end{bmatrix}$$

$$\begin{bmatrix} V_c(t) \\ I_L(t) \end{bmatrix} = \begin{bmatrix} 0 \\ 0 \end{bmatrix} e^{\lambda t} = \begin{bmatrix} 0 \\ 0 \end{bmatrix}$$

trivial

soln. \Rightarrow does not satisfy I.C. unless $V_0 \neq 0, I_0 \neq 0$

For non-trivial soln.

$(\lambda I - A)$ should not be invertible.

Then $\det(\lambda I - A) = 0 \rightarrow |\lambda I - A| = 0$

$$\left| \begin{bmatrix} \lambda & 0 \\ 0 & \lambda \end{bmatrix} - \begin{bmatrix} -3 & 1 \\ -2 & 0 \end{bmatrix} \right| = 0 \rightarrow \left| \begin{bmatrix} \lambda+3 & -1 \\ 2 & \lambda \end{bmatrix} \right| = 0$$

$$\lambda^2 + 3\lambda + 2 = 0 \leftarrow \text{characteristic polynomial}$$


$$\lambda = \{-1, -2\}$$

Then non-trivial soln. exists for only special values of λ , which are called natural frequencies.

$$X(t) = \text{span} \left\{ \begin{bmatrix} \alpha_1 \\ \alpha_2 \end{bmatrix} e^{-t} + \begin{bmatrix} \beta_1 \\ \beta_2 \end{bmatrix} e^{-2t} \right\}$$

Solution of state eqns: (continued)

9) zero-input (continued)

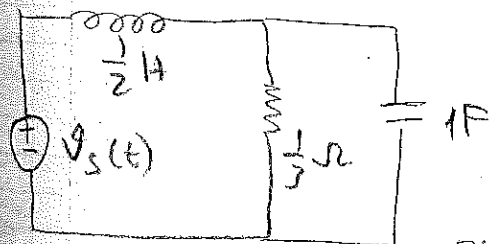

State equations

$$\begin{bmatrix} \dot{V}_c(t) \\ \dot{I}_L(t) \end{bmatrix} = \begin{bmatrix} -3 & 1 \\ -2 & 0 \end{bmatrix} \begin{bmatrix} V_c(t) \\ I_L(t) \end{bmatrix} + \begin{bmatrix} 0 \\ 2 \end{bmatrix} V_s(t)$$

$$\begin{bmatrix} V_c(0^-) \\ I_L(0^-) \end{bmatrix} = \begin{bmatrix} V_0 \\ I_0 \end{bmatrix}$$

$f(t)$: forcing term

State variables

Assume $v_3(t) = 0$ (zero-input)

then:

$$\begin{bmatrix} \dot{v}_c(t) \\ \dot{I}_L(t) \end{bmatrix} = \begin{bmatrix} -3 & 1 \\ -2 & 0 \end{bmatrix} \begin{bmatrix} v_c(t) \\ I_L(t) \end{bmatrix}$$

We need to solve this

$$\begin{bmatrix} v_c(0) \\ I_L(0) \end{bmatrix} = \begin{bmatrix} v_0 \\ I_0 \end{bmatrix}$$

Solution:

Guess: $\begin{bmatrix} v_c^{zi}(t) \\ I_L^{zi}(t) \end{bmatrix} = \begin{bmatrix} k_1 \\ k_2 \end{bmatrix} e^{\lambda t}$

$$\lambda \begin{bmatrix} k_1 \\ k_2 \end{bmatrix} e^{\lambda t} = A \begin{bmatrix} k_1 \\ k_2 \end{bmatrix} e^{\lambda t}$$

$$(A - \lambda I) \begin{bmatrix} k_1 \\ k_2 \end{bmatrix} = \begin{bmatrix} 0 \\ 0 \end{bmatrix}$$

$\det(A - \lambda I) \neq 0 \rightarrow \begin{bmatrix} k_1 \\ k_2 \end{bmatrix} = \begin{bmatrix} 0 \\ 0 \end{bmatrix}$ i.e. $(A - \lambda I)$ is invertible

So trivial solution cannot be the solution we are looking for unless initial conditions are all zero.

trivial solution $\rightarrow \begin{bmatrix} v_c^{zi}(t) \\ I_L^{zi}(t) \end{bmatrix} = \begin{bmatrix} k_1 \\ k_2 \end{bmatrix} e^{\lambda t} = \begin{bmatrix} 0 \\ 0 \end{bmatrix}$

$$\det(A - \lambda I) = 0 \rightarrow \lambda^2 + 3\lambda + 2 = 0 \rightarrow \lambda = \{-1, -2\}$$

characteristic polynomial

natural frequency

Then for $\lambda = \{-1, -2\}$, a non-trivial solution can exist.

$$(A - \lambda I) \begin{bmatrix} k_1 \\ k_2 \end{bmatrix} = \begin{bmatrix} 0 \\ 0 \end{bmatrix} \text{ has a solution } \begin{bmatrix} k_1 \\ k_2 \end{bmatrix} \neq \begin{bmatrix} 0 \\ 0 \end{bmatrix}$$

$\lambda = \{-1, -2\}$
for our problem

$$A \begin{bmatrix} k_1 \\ k_2 \end{bmatrix} = \lambda \begin{bmatrix} k_1 \\ k_2 \end{bmatrix} \leftarrow \text{eigenvalue-eigenvector equation system}$$

$$\lambda = -1 \rightarrow \underline{(A - \lambda I)} \begin{bmatrix} k_1 \\ k_2 \end{bmatrix} = \begin{bmatrix} 0 \\ 0 \end{bmatrix}$$

$$\begin{bmatrix} -2 & 1 \\ -2 & 1 \end{bmatrix} \begin{bmatrix} k_1 \\ k_2 \end{bmatrix} = \begin{bmatrix} 0 \\ 0 \end{bmatrix} \rightarrow \begin{bmatrix} k_1 \\ k_2 \end{bmatrix} \propto \begin{bmatrix} 1 \\ 2 \end{bmatrix}$$

$$\begin{matrix} (A - \lambda I) \\ \uparrow \\ \lambda = -1 \end{matrix}$$

Proportional to

$$\beta \begin{bmatrix} 1 \\ 2 \end{bmatrix} \quad \beta \in \mathbb{R}$$

$$\lambda = -2 \rightarrow \begin{bmatrix} -1 & 1 \\ -2 & 2 \end{bmatrix} \begin{bmatrix} k_1 \\ k_2 \end{bmatrix} = \begin{bmatrix} 0 \\ 0 \end{bmatrix} \rightarrow \begin{bmatrix} k_1 \\ k_2 \end{bmatrix} \propto \begin{bmatrix} 1 \\ 1 \end{bmatrix} \quad \alpha \in \mathbb{R}$$

$$(*) \begin{bmatrix} V_C^{zi}(t) \\ I_L^{zi}(t) \end{bmatrix} = \alpha \begin{bmatrix} 1 \\ 2 \end{bmatrix} e^{-t} + \beta \begin{bmatrix} 1 \\ 1 \end{bmatrix} e^{-2t} \quad \begin{matrix} \alpha \in \mathbb{R} \\ \beta \in \mathbb{R} \end{matrix}$$

any α and β satisfies the diff. eqn. given.

$$\text{Guess: } \begin{bmatrix} k_1 \\ k_2 \end{bmatrix} e^{\lambda t} \quad \lambda = -1$$

Now, only thing that we need to check whether I.Cs are satisfied or not.

$$\begin{bmatrix} V_C^{zi}(0^+) \\ I_L^{zi}(0^+) \end{bmatrix} = \begin{bmatrix} V_C^{zi}(0^-) \\ I_L^{zi}(0^-) \end{bmatrix} = \begin{bmatrix} V_0 \\ I_0 \end{bmatrix}$$

Then inserting $t=0^+$ into (*)

$$\begin{bmatrix} V_0 \\ I_0 \end{bmatrix} = \begin{bmatrix} 1 \\ 2 \end{bmatrix} \alpha + \begin{bmatrix} 1 \\ 1 \end{bmatrix} \beta \rightarrow \begin{bmatrix} V_0 \\ I_0 \end{bmatrix} = \begin{bmatrix} 1 & 1 \\ 2 & 1 \end{bmatrix} \begin{bmatrix} \alpha \\ \beta \end{bmatrix}$$

Inverse

$$\begin{bmatrix} \alpha \\ \beta \end{bmatrix} = \frac{1}{-1} \begin{bmatrix} 1 & -1 \\ -2 & 1 \end{bmatrix} \begin{bmatrix} V_0 \\ I_0 \end{bmatrix} \rightarrow \begin{bmatrix} \alpha \\ \beta \end{bmatrix} = \begin{bmatrix} I_0 - V_0 \\ 2V_0 - I_0 \end{bmatrix}$$

$$\text{Finally, } \begin{bmatrix} V_C^{zi}(t) \\ I_L^{zi}(t) \end{bmatrix} = (I_0 - V_0) \begin{bmatrix} 1 \\ 2 \end{bmatrix} e^{-t} + (2V_0 - I_0) \begin{bmatrix} 1 \\ 1 \end{bmatrix} e^{-2t}, \quad t \geq 0$$

What we've learned:

① From state equations

$$\dot{\underline{x}}(t) = \underline{A} \underline{x}(t) + b v_s(t)$$

The natural frequencies (λ) are eigen values of \underline{A} matrix.

② The zero-input solution is in the form:

zero input solution $\leftarrow \dot{\underline{x}}(t) = \text{span} \left\{ e_1 e^{\lambda_1 t}, e_2 e^{\lambda_2 t}, \dots, e_n e^{\lambda_n t} \right\}$

$e_k = k^{\text{th}}$ eigenvector of the matrix \underline{A}

that is

$$\underline{A} e_k = \lambda_k e_k$$

In our example

$$\begin{bmatrix} V_C^{z'} \\ I_L^{z'} \end{bmatrix} = \alpha \begin{bmatrix} 1 \\ 2 \end{bmatrix} e^{-t} + \beta \begin{bmatrix} 1 \\ 1 \end{bmatrix} e^{-2t} = \text{span} \left\{ \begin{bmatrix} 1 \\ 2 \end{bmatrix} e^{-t}, \begin{bmatrix} 1 \\ 1 \end{bmatrix} e^{-2t} \right\}$$

$$\alpha, \beta \in \mathbb{R}$$

③ The components zero-input solution such as

$e_k e^{\lambda_k t} \leftarrow k^{\text{th}}$ component in the span expansion

is called the mode of the circuit.

In our example, the circuit has two modes:

$$\begin{bmatrix} 1 \\ 2 \end{bmatrix} e^{-t} \text{ and } \begin{bmatrix} 1 \\ 1 \end{bmatrix} e^{-2t}$$

Hence we can repeat note ② as the zero input solution is a linear combination of the modes.


In our examples let $V_s = 10V$
 $I_s = 5A$

$$\begin{bmatrix} V_C^{z'}(t) \\ I_L^{z'}(t) \end{bmatrix} = -5 \begin{bmatrix} 1 \\ 2 \end{bmatrix} e^{-t} + 15 \begin{bmatrix} 1 \\ 1 \end{bmatrix} e^{-2t} = \begin{bmatrix} -5e^{-t} + 15e^{-2t} \\ -10e^{-t} + 15e^{-2t} \end{bmatrix}$$

slow mode

fast mode

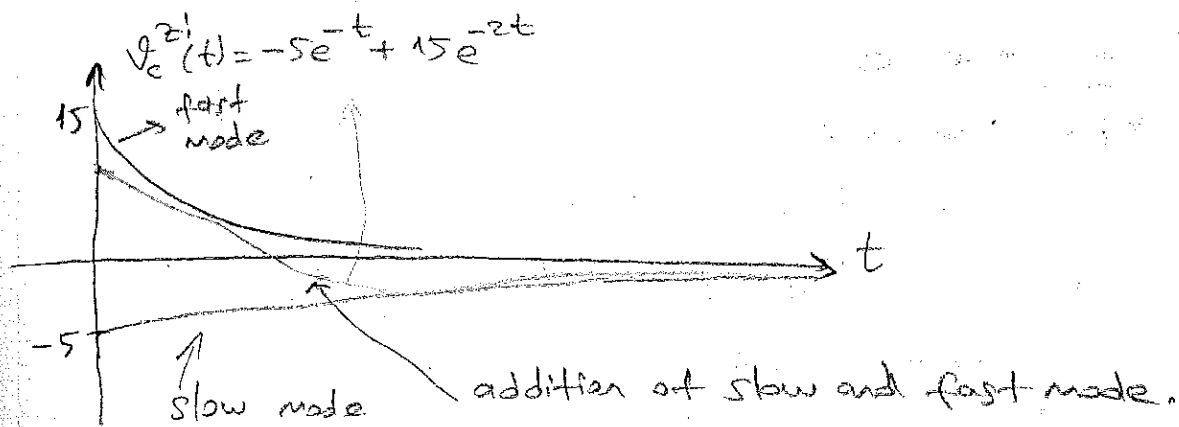(since e^{-2t} decays much faster than e^{-t})



(4) Mode excitation

The I.C.'s resulting in a single mode for the zero input solution are called mode exciting Initial conditions.

$$\dot{x}(t) = Ax(t) + b V_s(t) \quad (\text{zero-input})$$

$$x(0) = x_0$$

↑ a special I.C. such that

$$x^{zi}(t) = \begin{bmatrix} \vdots \\ \vdots \\ \vdots \end{bmatrix} e^{\lambda t}$$

↑ only a single mode present in the x^{zi} solution.

Conclusion: If the initial condition vector is proportional to an eigenvector of A , say e_k , then that I.C. excites k^{th} mode, i.e.

$$\begin{bmatrix} V_c^{zi}(t) \\ I_L^{zi}(t) \end{bmatrix} = \beta \begin{bmatrix} 1 \\ 1 \end{bmatrix} e^{-2t} \quad \left\{ \begin{bmatrix} V_c^{zi}(0) \\ I_L^{zi}(0) \end{bmatrix} = \beta \begin{bmatrix} 1 \\ 1 \end{bmatrix} \right. \quad \begin{array}{l} \checkmark \text{ for} \\ \text{eigenvector} \\ \lambda = -2 \end{array}$$

(initial condition) ↑ I.C. exciting fast mode.

(5) State Transition Matrix and Mode Excitation

Let's assume that the initial cond. is expressed as a linear combination of eigenvectors of A .

$$x_0 = \alpha_1 e_1 + \alpha_2 e_2 + \dots + \alpha_N e_N$$

I.C. ↑

↑ eigenvectors

$$A e_k = \lambda_k e_k$$

Then

$$x(t) = \alpha_1 e_1 e^{\lambda_1 t} + \alpha_2 e_2 e^{\lambda_2 t} + \dots + \alpha_N e_N e^{\lambda_N t}$$

↑ the zero-input solution of $\dot{x}(t) = Ax(t)$

$$\underline{x}(t) = \underbrace{[e_1 \ e_2 \ \dots \ e_N]}_{\underline{E}} \begin{bmatrix} e^{\lambda_1 t} & & & \\ & e^{\lambda_2 t} & & 0 \\ & & \ddots & \\ 0 & & & e^{\lambda_N t} \end{bmatrix} \begin{bmatrix} \alpha_1 \\ \alpha_2 \\ \vdots \\ \alpha_N \end{bmatrix}$$

$$\underline{x}(t) = \underline{E} \text{diag}(e^{\lambda_1 t}, \dots, e^{\lambda_N t}) \underline{E}^{-1} \underline{x}(0)$$

$\Phi(t, 0)$

$\begin{bmatrix} \alpha_1 \\ \alpha_2 \\ \vdots \\ \alpha_N \end{bmatrix}$

$\begin{bmatrix} e^{\lambda_1 t} \alpha_1 \\ e^{\lambda_2 t} \alpha_2 \\ \vdots \\ e^{\lambda_N t} \alpha_N \end{bmatrix}$

$\underline{x}(t) = \underline{\Phi}(t, 0) \underline{x}(0)$

$$= \underline{E} \text{diag}(e^{\lambda_1 t}, \dots, e^{\lambda_N t}) \underline{E}^{-1}$$

$\underline{\Phi}(t, 0)$ is called state-transition matrix

This is a powerful result, since

$\dot{\underline{x}}(t) = \underline{A} \underline{x}(t)$ diff. eqn. has the solution

$$\underline{x}(t) = \underline{\Phi}(t, 0) \underline{x}_0$$

↑
I.C.

→ State transition matrix which may be calculated from \underline{A} matrix.


$\underline{\Phi}(t, 0) = \underline{E} \text{diag}(e^{\lambda_1 t}, \dots, e^{\lambda_N t}) \underline{E}^{-1}$

↑ eigenvalues

\underline{E} has columns as the eigenvectors of \underline{A} .

Particular Solution - A State Equation System

Ex:

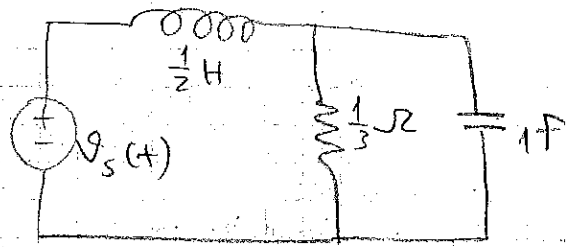

$V_s(t) = e^{s_0 t}$
 $s_0 \neq$ natural frequency of the circuit
 s is a complex number

Q: Find the particular solution.

$$\begin{bmatrix} \dot{V}_c \\ \dot{I}_L \end{bmatrix} = \begin{bmatrix} -3 & 1 \\ -2 & 0 \end{bmatrix} \begin{bmatrix} V_c(t) \\ I_L(t) \end{bmatrix} + \begin{bmatrix} 0 \\ 2 \end{bmatrix} V_s(t) = e^{s_0 t}$$

Char. eqn: $\lambda^2 - \text{trace}\{\underline{A}\}\lambda + |\underline{A}| = 0$

$$\begin{bmatrix} V_c(0^-) \\ I_L(0^-) \end{bmatrix} = \begin{bmatrix} V_0 \\ I_0 \end{bmatrix}$$

Particular solution:
Guess:

method of undetermined coefficients

$$\begin{bmatrix} V_C(t) \\ I_L(t) \end{bmatrix} = \begin{bmatrix} k_1 \\ k_2 \end{bmatrix} e^{s_0 t}$$

Insert into Eqn.

$$s_0 \mathbb{I} \begin{bmatrix} k_1 \\ k_2 \end{bmatrix} e^{s_0 t} = \begin{bmatrix} -3 & 1 \\ -2 & 0 \end{bmatrix} \begin{bmatrix} k_1 \\ k_2 \end{bmatrix} e^{s_0 t} + \begin{bmatrix} 0 \\ 2 \end{bmatrix} e^{s_0 t}$$

$$\left(s_0 \mathbb{I} - \begin{bmatrix} -3 & 1 \\ -2 & 0 \end{bmatrix} \right) \begin{bmatrix} k_1 \\ k_2 \end{bmatrix} = \begin{bmatrix} 0 \\ 2 \end{bmatrix} \rightarrow \begin{bmatrix} s_0+3 & -1 \\ 2 & s_0 \end{bmatrix} \begin{bmatrix} k_1 \\ k_2 \end{bmatrix} = \begin{bmatrix} 0 \\ 2 \end{bmatrix}$$

$$\begin{bmatrix} k_1 \\ k_2 \end{bmatrix} = \frac{1}{s_0^2 + 3s_0 + 2} \begin{bmatrix} s_0 & 1 \\ -2 & s_0+3 \end{bmatrix} \begin{bmatrix} 0 \\ 2 \end{bmatrix}$$

$$\begin{bmatrix} k_1 \\ k_2 \end{bmatrix} = \frac{1}{s_0^2 + 3s_0 + 2} \begin{bmatrix} 2 \\ 2s_0 + 6 \end{bmatrix}$$

k_1 and k_2 values required to finalize the particular solution to the input $e^{s_0 t}$.

Particular soln. of whole equation (continued)

$$\begin{cases} \dot{X}(t) = \underline{A}x(t) + bV_s(t) \\ X(0) = X_0 \end{cases}$$

Assume $V_s(t) = M e^{s_0 t}$, s_0 can be an exponential input $\{1, -2, 1+j, \dots\}$

Goal: Finding the particular solution to the exponential input.

s_0 is not a natural frequency of the circuit. \uparrow i.e. $s_0 \notin$ complex field

Note:

$$Ae^{s_0 t} \xrightarrow{s_0=0} A$$

$$Ae^{s_0 t} \xrightarrow{s_0=-1} Ae^{-t}$$

$$Ae^{s_0 t} \xrightarrow{s_0=2j} Ae^{2jt} = A[\cos(2t) + j\sin(2t)]$$

(or $Me^{s_0 t}$)

s_0 exponential input family is quite general and includes many inputs of interest

$$\underline{X}^p(t) = \begin{bmatrix} k_1 \\ k_2 \\ \vdots \\ k_n \end{bmatrix} e^{s_0 t}$$

\underline{k}

Guess for particular solution

For the guess to be correct, the dif. eqn. should be satisfied:

$$\dot{X}^p(t) = \underline{A}X^p(t) + bV_s(t)$$

$$s_0 \underline{k} e^{s_0 t} = \underline{A} \underline{k} e^{s_0 t} + b M e^{s_0 t} \rightarrow (s_0 \mathbb{I} - \underline{A}) \underline{k} = b M$$

Identity matrix

$$\underline{k} = [(-s_0 I - A)^{-1} b] M$$

↑
Unknown k vector is found since $(s_0 I - A)$ is invertible, I have calculated \underline{k} by

Simply inverting the matrix.

The earlier numerical example:

$$\begin{bmatrix} \dot{V}_c(t) \\ \dot{I}_L(t) \end{bmatrix} = \begin{bmatrix} -3 & 1 \\ -2 & 0 \end{bmatrix} \begin{bmatrix} V_c(t) \\ I_L(t) \end{bmatrix} + \begin{bmatrix} 0 \\ 2 \end{bmatrix} V_s(t)$$

$$V_s(t) = e^{s_0 t}$$

$$\hookrightarrow \text{Guess: } \begin{bmatrix} V_c^p(t) \\ I_L^p(t) \end{bmatrix} = \begin{bmatrix} k_1 \\ k_2 \end{bmatrix} e^{s_0 t} \rightarrow (s_0 I - \begin{bmatrix} -3 & 1 \\ -2 & 0 \end{bmatrix}) \begin{bmatrix} k_1 \\ k_2 \end{bmatrix} = \begin{bmatrix} 0 \\ 2 \end{bmatrix}$$

$$\rightarrow \begin{bmatrix} s_0 + 3 & -1 \\ 2 & s_0 \end{bmatrix} \begin{bmatrix} k_1 \\ k_2 \end{bmatrix} = \begin{bmatrix} 0 \\ 2 \end{bmatrix} \rightarrow \begin{bmatrix} k_1 \\ k_2 \end{bmatrix} = \frac{1}{(s_0^2 + 3s_0 + 2)} \begin{bmatrix} s_0 & 1 \\ -2 & s_0 + 3 \end{bmatrix} \begin{bmatrix} 0 \\ 2 \end{bmatrix}$$

$$\det(s_0 I - A)$$

Since $s_0 \neq \text{not. freq.}$

Remember not. freq. for this example = $\{-1, -2\}$

$$\rightarrow s_0^2 + 3s_0 + 2 \neq 0$$

$$\begin{bmatrix} k_1 \\ k_2 \end{bmatrix} = \frac{1}{s_0^2 + 3s_0 + 2} \begin{bmatrix} 2 \\ 2(s_0 + 3) \end{bmatrix}$$

$$\begin{bmatrix} V_c^p(t) \\ I_L^p(t) \end{bmatrix} = \begin{bmatrix} k_1 \\ k_2 \end{bmatrix} e^{s_0 t} = \frac{1}{s_0^2 + 3s_0 + 2} \begin{bmatrix} 2 \\ 2(s_0 + 3) \end{bmatrix} e^{s_0 t}$$

$$V_c^p(t) = \frac{2}{s_0^2 + 3s_0 + 2} e^{s_0 t}$$

$$s_0 = 0$$

$$V_s(t) = e^{s_0 t}$$


$$V_c^p(t)$$

$$s_0 = 0 \rightarrow V_s(t) = 1$$

$$V_c^p(t) = 1$$

$$s_0 = 1 \rightarrow V_s(t) = e^t$$

$$V_c^p(t) = \frac{1}{3} e^t$$

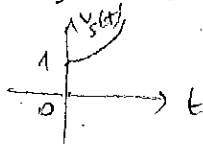


$$V_s(t) = e^{s_0 t}$$

$$s_0 = 2j \rightarrow V_s(t) = e^{2jt}$$

$$V_s(t) = \begin{pmatrix} \cos(2t) \\ + \\ j \sin(2t) \end{pmatrix}$$

$$V_c^P(t) = \frac{2}{(2j)^2 + 3(2j) + 2} e^{2jt}$$

$$= \frac{1}{-1 + 3j} e^{2jt}$$

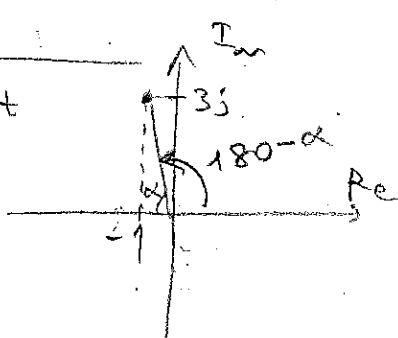

$$\frac{1}{1+j} = \frac{1-j}{1+j} = \frac{1-j}{2}$$

$$(1-j)$$

$$\frac{1}{1+j} = \frac{1}{\sqrt{2} \angle 45^\circ} = \frac{1}{\sqrt{2}} \angle -45^\circ$$

$$= \frac{1}{\sqrt{2}} (\cos 45^\circ - j \sin 45^\circ)$$

$$= \frac{1}{2} - \frac{j}{2}$$

$$= \frac{1}{\sqrt{10}} \angle (180^\circ - \tan^{-1}(3)) e^{2jt}$$

$$= \frac{1}{\sqrt{10}} e^{j(180^\circ - \tan^{-1}(3)) 2jt}$$


$$= \frac{1}{\sqrt{10}} e^{j(2t - 180^\circ + \tan^{-1}(3))}$$

$$= \frac{1}{\sqrt{10}} \left[\cos(2t - 180^\circ + \tan^{-1}(3)) + j \sin(2t - 180^\circ + \tan^{-1}(3)) \right]$$

$V_c^P(t)$ for e^{2jt} input

$$\boxed{e^{j\theta} = \cos\theta + j\sin\theta}$$

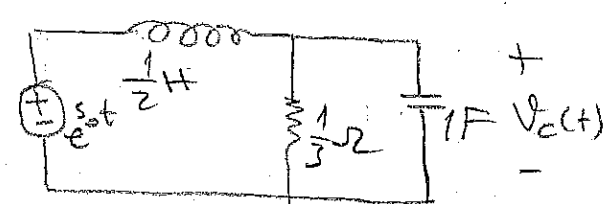Now, let's go back and examine the circuit one more time:




Let's try to find particular solution from the circuit:

I know that $V_c^P(t) = \frac{2}{s_0^2 + 3s_0 + 2} e^{s_0 t}$

we will verify this result one more time.

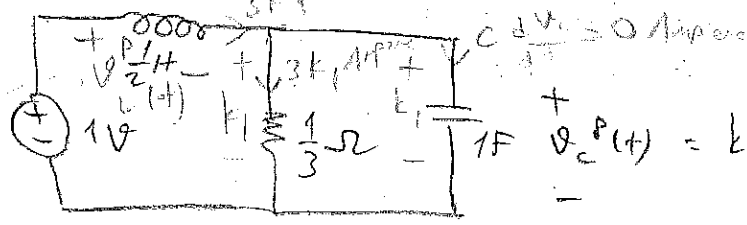Before general verification, let's do $s_0 = 0$ special case:



$$V_L(t) = L \frac{di}{dt} = 0$$

$$V_c^P(t) = k_1 e^{s_0 t} = k_1$$


$$s_0 = 0$$

$k_1 = 1V$

↑ by KVL


= 0 V

$V_s(t) = 1V$ is DC input

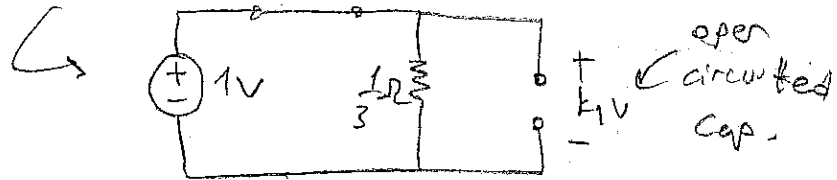

$t \rightarrow \infty$

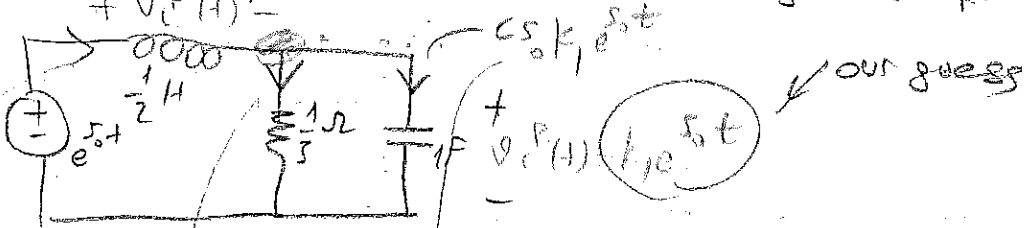Let's find the particular solution for the general input $e^{s_0 t}$



$$= I_C^P(t) = C \dot{V}_C^P(t)$$

by KCL

$$3 \cdot k_1 e^{s_0 t} = I_R^P(t)$$

$$k_1 e^{s_0 t} (3 + Cs_0) \quad V_L^P(t) = L \frac{d}{dt} I_L^P(t)$$

$$= L k_1 (3 + s_0 C) s_0 e^{s_0 t}$$

Finally, KVL: $-e^{s_0 t} + V_C^P(t) + V_L^P(t) = 0$

$$-e^{s_0 t} + L k_1 (3 + s_0 C) s_0 e^{s_0 t} + k_1 e^{s_0 t} = 0$$

$$k_1 = \frac{1}{s_0^2 CL + L3s_0 + 1}$$

$$k_1 = \frac{1}{s_0^2 \frac{1}{2} + \frac{3s_0}{2} + 1}$$

$$k_1 = \frac{2}{s_0^2 + 3s_0 + 2}$$

$$V_C^P(t) = \frac{2}{s_0^2 + 3s_0 + 2} e^{s_0 t}$$

Final answer for particular solution

Notes: (1) For the exponential input in the form $Ke^{s_0 t}$ the branch voltages and currents have the particular solution in the form:

$$\text{pth branch} \left\{ \begin{aligned} V_k &= A_k e^{s_0 t} \\ I_k &= B_k e^{s_0 t} \end{aligned} \right.$$

Variables

The goal of particular soln. is to find the coefficients A_k and B_k for the k^{th} branch and all the other branches.

② The general solution of an LTI circuit is in the form:

$$v_k(t) = \underbrace{v_k^h(t)}_{\text{homogeneous}} + \underbrace{v_k^p(t)}_{\text{particular}}$$

Homogeneous solution: $v_k^h(t) = \alpha_1 e^{\lambda_1 t} + \alpha_2 e^{\lambda_2 t} + \dots + \alpha_N e^{\lambda_N t}$




λ_k : natural frequency
 char. eqn: $\det(\lambda I - A) = 0$
 roots of char. eqn. are nat. frequency

Particular solution (for $Ae^{s_0 t}$ input): $v_k^p(t) = k_1 e^{s_0 t}$

$$v_k^{\text{complete}}(t) = v_k^h(t) + v_k^p(t) = \left(\sum_{k=1}^N \alpha_k e^{\lambda_k t} \right) + k_1 e^{s_0 t}$$

If all λ_k 's are real and negative valued, then as $t \rightarrow \infty$, $v_k^h(t) \rightarrow 0$ (homogeneous solution vanishes as t increases)

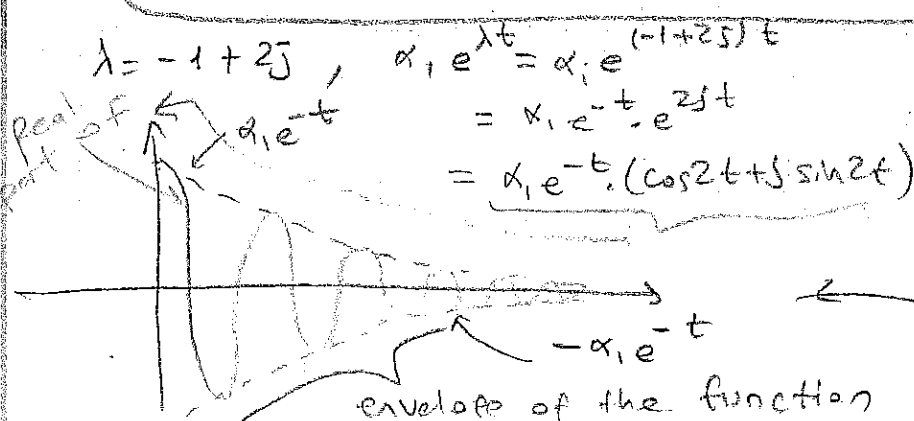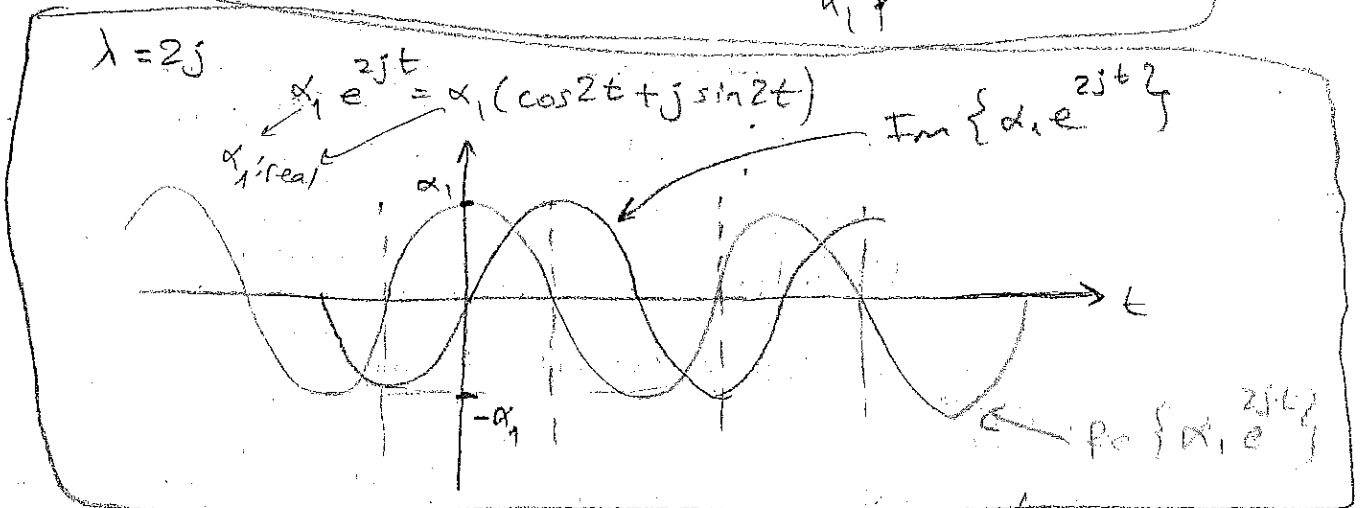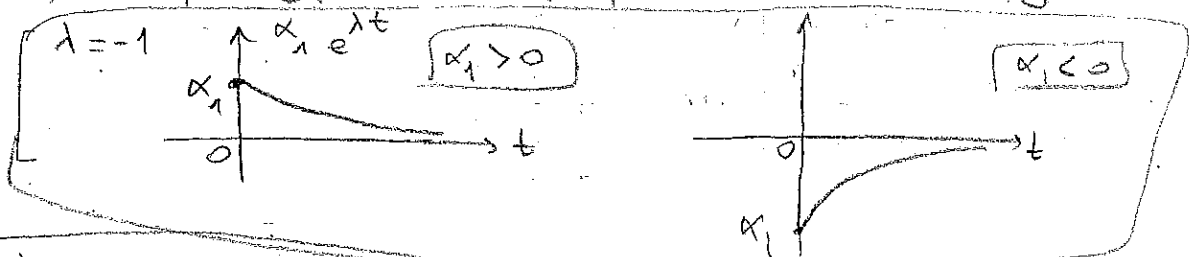A circuit is called stable if $\text{Re}\{\lambda_k\} < 0$ $k = \{1, \dots, N\}$ that is, real part of natural frequencies should be negative.



clearly the function does not decay


clearly we see a decaying function

So for stable circuits as $t \rightarrow \infty$ the complete solution \rightarrow particular solution,

(approaches)

In other words,
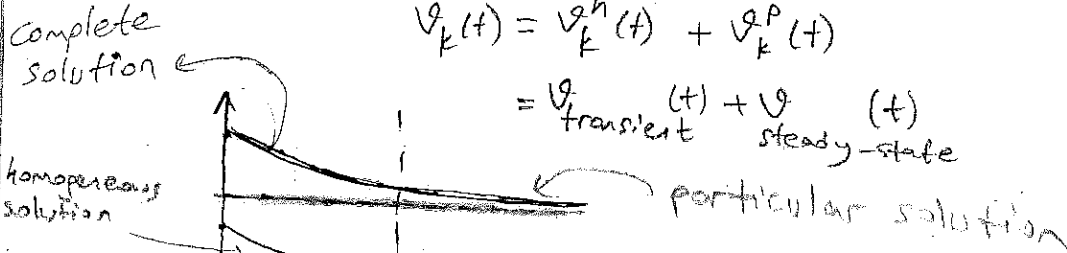
$$V_k(t) = V_k^h(t) + V_k^p(t) \\ = V_{\text{transient}}(t) + V_{\text{steady-state}}(t)$$



Transient Steady-state


Transient part of the solution has the non-diminished effects of homogeneous solution,

as $t \rightarrow \infty$ the complete solution becomes identical to the particular solution

Zero input the homogeneous variables for balanced

Other Analysis Methods for Dynamic Circuits

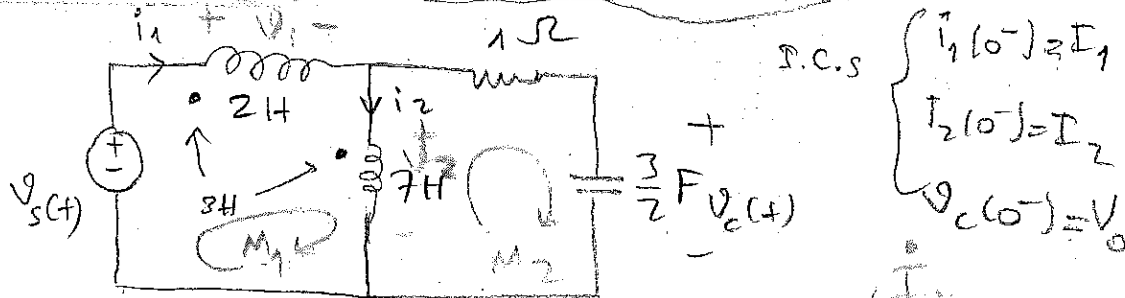① Mesh Analysis \rightarrow only for planar circuits



the order of the circuit

$$\begin{bmatrix} V_1(t) \\ V_2(t) \end{bmatrix} = \begin{bmatrix} 2 & 3 \\ 3 & 7 \end{bmatrix} \begin{bmatrix} I_1(t) \\ I_2(t) \end{bmatrix} \quad \frac{d}{dt} \begin{bmatrix} I_1(t) \\ I_2(t) \end{bmatrix}$$

KVL $\mathcal{M}_1: -V_s(t) + V_1 + V_2 = 0$
 $-V_s(t) + 5I_1(t) + 10I_2(t) = 0$

$-V_s(t) + 15I_x(t) - 10I_y(t) = 0$

mesh equation aims to do analysis with mesh currents, so every equation should have mesh currents I_x and I_y as unknowns.

Mesh eq #1:

KVL $\mathcal{M}_2: -\frac{V_c}{2} + 1 \cdot I_y + V_c(t) = 0 \rightarrow V_c(0^-) + \frac{1}{C} \int_0^t i_{\text{cap}}(\tau) d\tau$

$$-10I_x(t) + 7I_y(t)$$

$D = \frac{d}{dt}, D^{-1} = \int_0^t (\cdot) d\tau$ $D^{-1} \{ f(t) \} = \int_0^t f(\tau) d\tau$

Mesh eq #2: $-10I_x + 7I_y + I_y + V_0 + \frac{1}{C} D^{-1} \{ I_y \} = 0$

We can take derivative for all $t > 0$

$$\begin{bmatrix} 15D & -10D \\ -10D & 7D + \frac{2}{3}D + 1 \end{bmatrix} \begin{bmatrix} I_x(t) \\ I_y(t) \end{bmatrix} = \begin{bmatrix} V_s(t) \\ -V_o \end{bmatrix}$$

Mesh eq. set

we can take derivative of this side

Finding Natural Frequencies

$$V_c(t) = \alpha_1 e^{\lambda_1 t} + \alpha_2 e^{\lambda_2 t} + \alpha_3 e^{\lambda_3 t} + \text{Particular solution}$$

Complete solution

homogeneous solution

(for capacitor) Find $\lambda_1, \lambda_2, \lambda_3$:

Assume $V_c(t) = 0 \rightarrow \begin{bmatrix} I_x \\ I_y \end{bmatrix} = \begin{bmatrix} \alpha \\ \beta \end{bmatrix} e^{\lambda t}$

$$\Rightarrow \begin{bmatrix} 15\lambda & -10\lambda \\ -10\lambda^2 & 7\lambda + \frac{2}{3}\lambda + 1 \end{bmatrix} \begin{bmatrix} \alpha \\ \beta \end{bmatrix} e^{\lambda t} = \begin{bmatrix} 0 \\ 0 \end{bmatrix}$$

Guess for zero-input solution

Insert guess into differential equation

$\rightarrow \begin{bmatrix} \alpha \\ \beta \end{bmatrix} = \begin{bmatrix} 0 \\ 0 \end{bmatrix} \rightarrow \text{trivial soln.}$ $\begin{bmatrix} I_x(t) \\ I_y(t) \end{bmatrix} = \begin{bmatrix} 0 \\ 0 \end{bmatrix} e^{\lambda t} = \begin{bmatrix} 0 \\ 0 \end{bmatrix}$

Non-trivial solutions:

$$\det(M(\lambda)) = 0 \rightarrow 15\lambda(7\lambda^2 + \frac{2}{3}\lambda + 1 - 100\lambda^3) = 0$$

roots of this polynomial = net frequencies

$$\begin{bmatrix} 1 & 2 \\ 3 & 4 \end{bmatrix} \begin{bmatrix} x \\ y \end{bmatrix} = \begin{bmatrix} 0 \\ 0 \end{bmatrix}$$

$$\underline{A} \underline{x} = \underline{b} \quad \underline{A}^{-1} \underline{A} \underline{x} = \underline{A}^{-1} \underline{b}$$

If $\det A = 0$


$$\underline{x} = \underline{A}^{-1} \underline{b}$$

\rightarrow there is no inverse

$$\lambda = \{0, -1, -2\}$$



2) Node Analysis

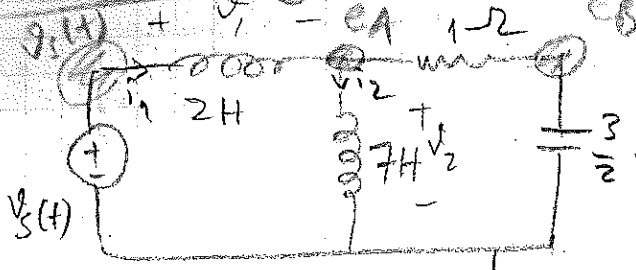

I.C.s $\begin{cases} i_1(0^-) = I_1 \\ i_2(0^-) = I_2 \\ v_c(0^-) = v_0 \end{cases}$

KCL at eA:

$$\frac{e_A - e_B}{1} + i_2 - i_1 = 0$$

$$\begin{bmatrix} v_1 \\ v_2 \end{bmatrix} = \begin{bmatrix} 2 & 3 \\ 3 & 7 \end{bmatrix} \begin{bmatrix} \frac{d}{dt} i_1 \\ \frac{d}{dt} i_2 \end{bmatrix}$$

$$\begin{bmatrix} 2 & 3 \\ 3 & 7 \end{bmatrix}^{-1} \begin{bmatrix} v_1 \\ v_2 \end{bmatrix} = \begin{bmatrix} D i_1 \\ D i_2 \end{bmatrix}$$

$$D^{-1} \begin{bmatrix} 7 & -3 \\ -3 & 2 \end{bmatrix} \begin{bmatrix} v_1 \\ v_2 \end{bmatrix} = \begin{bmatrix} -1 & D i_1 \\ D & D i_2 \end{bmatrix} \rightarrow \begin{bmatrix} i_1 - i_1(0^-) \\ i_2 - i_2(0^-) \end{bmatrix} = \begin{bmatrix} I_1 \\ I_2 \end{bmatrix}$$

- ① $D \cdot D^{-1} \{f(t)\} = \frac{d}{dt} \int_{0^-}^t f(\tau) d\tau = f(t)$
- ② $D^{-1} \cdot D \{f(t)\} = \int_{0^-}^t f(\tau) d\tau = f(t) - f(0^-)$

$$\frac{e_A - e_B}{1} + I_2 - I_1 + \frac{D^{-1}(-10v_1 + 5v_2)}{5} = 0$$

Node eq. #1: $\frac{e_A - e_B}{1} + I_2 - I_1 - 2D^{-1}\{v_s\} + 2D^{-1}\{e_A\} + D^{-1}\{e_A\} = 0$

KCL at eB: $\frac{e_B - e_A}{1} + \frac{3}{2} \dot{e}_B = 0$

Node eq. #2: $e_B - e_A + \frac{3}{2} D \{e_B\} = 0$

$$\begin{bmatrix} 1 + 3D^{-1} & -1 \\ -1 & 1 + \frac{3}{2}D \end{bmatrix} \begin{bmatrix} e_A(t) \\ e_B(t) \end{bmatrix} = \begin{bmatrix} 2D^{-1}\{v_s(t)\} + I_1 - I_2 \\ 0 \end{bmatrix}$$

Integral differential equation

Finding Natural Frequencies

(1) Take derivative of 1st Node equation to make it D^{-1} free

$$\begin{bmatrix} (D+3) & -D \\ -1 & 1+\frac{3}{2}D \end{bmatrix} \begin{bmatrix} e_A \\ e_B \end{bmatrix} = \begin{bmatrix} 2v_S(t) \\ 0 \end{bmatrix}$$

Make a guess for homogeneous solution ($v_S(t) = 0$):

$$\begin{bmatrix} e_A \\ e_B \end{bmatrix} = \begin{bmatrix} \alpha \\ \beta \end{bmatrix} e^{\lambda t}$$

trivial solution

non-trivial soln.

If we take derivative one more time λ will be added, $\lambda=0$ will be a solution.

$$\begin{vmatrix} \lambda+3 & -\lambda \\ -1 & 1+\frac{3}{2}\lambda \end{vmatrix} = 0$$

$$\rightarrow (\lambda+3)\left(\frac{3\lambda}{2}+1\right) - \lambda = 0$$

$$\frac{3\lambda^2}{2} + \frac{9\lambda}{2} + \lambda + 3 - \lambda = 0$$

$$\lambda^2 + 3\lambda + 2 = 0$$

$$\lambda = \{-1, -2, 0\}$$

Comments: (1) State equations result in correct number of nat. frequencies and their values.

(2) Mesh/Node Analysis results in all natural frequency, but the ones with $\lambda=0$ can be missing or can appear without any physical meaning.



(MNA)

Modified Node Analysis:

Node or Mesh analysis may result in a set of integro-differential equations, that is an equation system containing both $D = \frac{d}{dt}$ and $D^{-1} = \int (\) dt$ operators.


MNA aims to write a differentiation, as in state equations, describing the circuit.

In general MNA equations are much simpler to write, but they may contain many more equations than Node/Mesh analysis.

MNA recipe:

Auxiliary variables

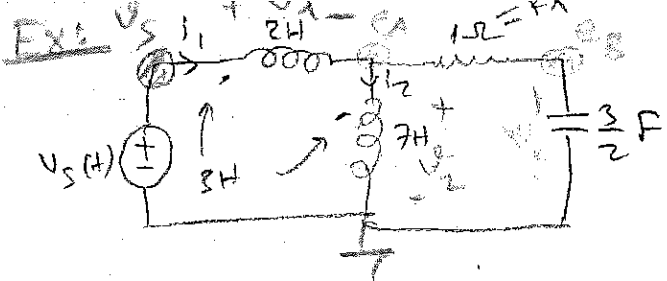- (1) Introduce current variables for inductor currents.
- (2) Introduce current variables for transformer primary/secondary side currents.
- (3) If there's a need, introduce current variables for voltage source currents.
- (4) Write KCL equations as in Node Analysis.
- (5) Write a component equation for each introduced auxiliary variables such that at the end, we have "N" equations for "N" unknowns.



$$\begin{bmatrix} \varphi_1(t) \\ \varphi_2(t) \end{bmatrix} = \begin{bmatrix} 2 & 3 \\ 3 & 7 \end{bmatrix} \begin{bmatrix} D i_1 \\ D i_2 \end{bmatrix}$$

KCL @ e_A : $\frac{1}{R_1} \quad -\frac{1}{R_1} \quad -1 \quad 1$

KCL @ e_B : $-\frac{1}{R_1} \quad \frac{1}{R_1} + \frac{3}{2} D \quad 0 \quad 0$

Mat. Inductors: $\begin{bmatrix} 1 & 0 & 2D & 3D \\ -1 & 0 & 3D & 7D \end{bmatrix} \begin{bmatrix} e_A \\ e_B \\ i_1 \\ i_2 \end{bmatrix} = \begin{bmatrix} 0 \\ 0 \\ \varphi_1(t) \\ 0 \end{bmatrix}$

Note that I've only $D = \frac{d}{dt}$ in my equations!
 So, diff. equation

To find nat. freqs: $M(D) \begin{bmatrix} e_A \\ e_B \\ i_1 \\ i_2 \end{bmatrix} = \begin{bmatrix} 0 \\ 0 \\ \varphi_1(t) \\ 0 \end{bmatrix}$

Assume $\varphi_1(t) = 0$

Guess: $\begin{bmatrix} e_A \\ e_B \\ i_1 \\ i_2 \end{bmatrix} = \begin{bmatrix} \alpha_1 \\ \alpha_2 \\ \alpha_3 \\ \alpha_4 \end{bmatrix} e^{\lambda t}$

Insert guess into diff. eqn:

$$M(D) \begin{bmatrix} \alpha_1 \\ \alpha_2 \\ \alpha_3 \\ \alpha_4 \end{bmatrix} e^{\lambda t} = \begin{bmatrix} 0 \\ 0 \\ 0 \\ 0 \end{bmatrix}$$

We substitute λ into D .

$$M(\lambda) \begin{bmatrix} \alpha_1 \\ \alpha_2 \\ \alpha_3 \\ \alpha_4 \end{bmatrix} e^{\lambda t} = \begin{bmatrix} 0 \\ 0 \\ 0 \\ 0 \end{bmatrix}$$

trivial
non-trivial solution

For non-trivial solution $\det(M(\lambda)) = 0$

char poly. and roots of char. poly. are the nat. freq.



Check the course website!

Solution of Diff. Eqn. Systems with Laplace Transform

$$f(t) \xleftrightarrow{\text{Laplace Transform}} F(s)$$

$$F(s) = \int_0^{\infty} f(t) e^{-st} dt$$

s : a complex number selected such that the integral does not diverge!

$F(s) = \mathcal{L}\{f(t)\}$
another notation

$$f(t) = \frac{1}{2\pi j} \int_{\sigma-j\infty}^{\sigma+j\infty} F(s) e^{st} ds, \text{ where } \sigma \in \text{R.O.C. of } F(s)$$

$$j = i = \sqrt{-1}$$

Inverse Laplace transform

We won't use inverse Laplace transform formula in this course.

region of convergence

Laplace Transform Pairs

① $f(t) = u(t)$

Step function

$$\begin{aligned} \mathcal{L}\{u(t)\} &= \int_0^{\infty} u(t) e^{-st} dt = \int_0^{\infty} 1 \cdot e^{-st} dt \\ &= \left. \frac{e^{-st}}{-s} \right|_0^{\infty} = \frac{e^{-s\infty}}{-s} + \frac{1}{s} \end{aligned}$$

for $s > 0 \rightarrow$ (this term) vanishes

$$\mathcal{L}\{u(t)\} = \frac{1}{s}$$

② $f(t) = e^{\alpha t} u(t) \leftrightarrow \frac{1}{s-\alpha} = \int_0^{\infty} e^{\alpha t} e^{-st} dt = \frac{1}{s-\alpha}$

Property

if $f(t) \leftrightarrow F(s)$

then $f(t) e^{\alpha t} \leftrightarrow F(s-\alpha)$ ★

Euler's formula

③ $f(t) = \sin \omega t \leftrightarrow e^{j\omega t} = \cos \omega t + j \sin \omega t$

$$- e^{-j\omega t} = \cos \omega t - j \sin \omega t$$

$$\frac{e^{j\omega t} - e^{-j\omega t}}{2j} = \sin \omega t \leftrightarrow F(s) = \mathcal{L}\left\{ \frac{e^{j\omega t} - e^{-j\omega t}}{2j} \right\}$$

$$= \frac{1}{2j} \left[\mathcal{L}\{e^{j\omega t}\} - \mathcal{L}\{e^{-j\omega t}\} \right]$$

$$= \frac{1}{2j} \left[\frac{1}{s-j\omega} - \frac{1}{s+j\omega} \right] = \frac{\omega}{s^2 + \omega^2}$$

$$(4) \cos \omega t \leftrightarrow \frac{s}{s^2 + \omega^2}$$

$$(5) t e^{-at} \leftrightarrow \frac{-d}{ds} \mathcal{L}(e^{-at}) = -\frac{d}{ds} \left(\frac{1}{s+a} \right) = \frac{1}{(s+a)^2}$$

Property if $f(t) \leftrightarrow F(s)$

then $t f(t) \leftrightarrow \frac{-d}{ds} F(s)$

$$= -\frac{d}{ds} \int_0^{\infty} f(t) e^{-st} dt$$


$$\mathcal{L}\{t f(t)\} = \int_0^{\infty} f(t) \frac{d}{ds} e^{-st} dt$$

$$= \int_0^{\infty} t f(t) e^{-st} dt$$

$$(6) \delta(t) \leftrightarrow 1$$

$$\int_0^{\infty} \delta(t) e^{-st} dt = \int_0^{\infty} \delta(t) e^{-s \cdot 0} dt = \int_0^{\infty} \delta(t) \cdot 1 \cdot dt = 1 \cdot \int_0^{\infty} \delta(t) dt = 1$$

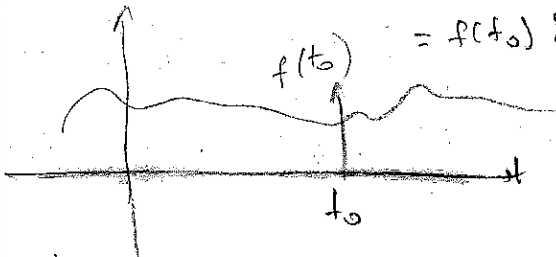
Since $f(t) \delta(t-t_0)$
 $= f(t_0) \delta(t-t_0)$



$$(7) \delta(t-t_0) \leftrightarrow ?$$

Property if $f(t) u(t) \leftrightarrow F(s)$
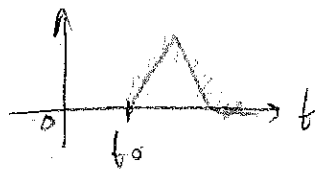
$$f(t-t_0) u(t-t_0) \leftrightarrow e^{-st_0} F(s)$$



$$\mathcal{L}\{f(t-t_0) u(t-t_0)\} = \int_0^{\infty} f(t-t_0) u(t-t_0) e^{-st} dt$$

$$= \int_{t=t_0}^{\infty} f(t-t_0) e^{-st} dt = e^{-st_0} \int_{\tau=0}^{\infty} f(\tau) e^{-s\tau} d\tau$$

$$= e^{-st_0} F(s)$$

⑧ Integration and Differentiation Property

$f(t) \leftrightarrow F(s)$

$\frac{d}{dt} f(t) \leftrightarrow sF(s) - f(0^-)$

Proof: Put this and use integration by parts

$D^{-1} = \int_0^+ (\cdot) dt \left(\begin{matrix} f(t) \leftrightarrow F(s) \\ \int_0^+ f(\tau) d\tau \leftrightarrow \frac{F(s)}{s} \end{matrix} \right)$

function of time
 ↓
 area between $[0, t]$ of argument

slider
 cosine horf

Ex: Use Laplace Transform to solve:

$(D^2 + 3D + 2)V_c(t) = f(t) \quad (*)$

$V_c(0) = V_0$

$\dot{V}_c(0^-) = \dot{V}_0$

$t > 0^-$ Let $\mathcal{L}\{V_c(t)\} = V_c(s)$

then $\mathcal{L}\left\{\frac{d}{dt} V_c(t)\right\} = sV_c(s) - V_c(0)$

If (*) holds for all $t > 0^-$ then I can multiply both LHS and RHS by e^{-st} and then integrate from $t=0^-$ to $t=\infty \rightarrow$ after this operation equality should still hold.

$\mathcal{L}\left\{\frac{d^2}{dt^2} V_c(t)\right\} = s^2 V_c(s) - sV_c(0^-) - \dot{V}_c(0^-)$

Known I.C. Values

$\mathcal{L}\{D^2 V_c(t)\} + 3\mathcal{L}\{D V_c(t)\} + 2\mathcal{L}\{V_c(t)\} = \mathcal{L}\{f(t)\}$

$V_c(s)(s^2 + 3s + 2) - sV_0 - \dot{V}_0 - 3V_0 = F(s)$

$V_c(s) = \frac{F(s) + (s+3)V_0 + \dot{V}_0}{(s^2 + 3s + 2)}$

$V_c(s) = \frac{(s+3)V_0 + \dot{V}_0}{(s+2)(s+1)} + \frac{F(s)}{(s+2)(s+1)}$

Complete solution in Laplace domain

part related with I.C.
 //
 zero input part

part related with //
 zero-state part

$f(t) \leftrightarrow$ external input
 ↑
 forcing term

Let's focus on

external input

① zero-input part ($f(t) = 0$)

$$V_c^{z.i.}(s) = \frac{(s+3)V_0 + \dot{V}_0}{(s+2)(s+1)}$$

I need $V_c^{z.i.}(t)$ ← time domain

$$V_c^{z.i.}(t) = \mathcal{L}^{-1} \left\{ V_c^{z.i.}(s) \right\} = \mathcal{L}^{-1} \left\{ \frac{(s+3)V_0 + \dot{V}_0}{(s+2)(s+1)} \right\}$$

$$\frac{A}{s+2} + \frac{B}{s+1}$$

$$\frac{(-2+3)V_0 + \dot{V}_0}{(-2+1)} = \frac{V_0 + \dot{V}_0}{-1}$$

$$(s+1) \frac{(s+3)V_0 + \dot{V}_0}{(s+2)(s+1)} = \frac{A(s+1)}{s+2} + \frac{B(s+1)}{s+1}$$

insert $s = -1$

$$\frac{2V_0 + \dot{V}_0}{1} = \frac{A \cdot 0}{2} + B$$

$$B = \frac{2V_0 + \dot{V}_0}{1}$$

$$V_c^{z.i.}(s) = \frac{-V_0 - \dot{V}_0}{s+2} + \frac{2V_0 + \dot{V}_0}{s+1}$$

$\mathcal{L}^{-1} \{ \}$

$$V_c^{z.i.}(t) = (-V_0 - \dot{V}_0) e^{-2t} u(t) + (2V_0 + \dot{V}_0) e^{-t} u(t)$$

Check Sadiku's book
Laplace transform
partial fraction
expressions

② zero-state solution

→ state-variables take 0 value, that is all I.C. are zero, or zero initial energy.

$$V_c^{z.s.}(s) = \frac{F(s)}{(s+2)(s+1)}$$

Case of $f(t) = u(t) \rightarrow F(s) = \frac{1}{s}$, $V_c^{z.s.}(s) = \frac{1/s}{(s+2)(s+1)}$

Step response

$$= \frac{A}{s} + \frac{B}{s+1} + \frac{C}{s+2}$$

$$A = \frac{1}{2}; B = -1; C = \frac{1}{2}$$

$$V_c^{z.s.}(s) = \frac{1}{s(s+1)(s+2)} = \frac{1/2}{s} + \frac{-1}{s+1} + \frac{1/2}{s+2}$$

$$\mathcal{L}^{-1}\left\{ \right\} \rightarrow V_c^{step}(t) = \frac{1}{2} u(t) - e^{-t} u(t) + \frac{1}{2} e^{-2t} u(t)$$

Case of $f(t) = \delta(t)$

(impulse response)

$$F(s) = 1 \rightarrow V_c^{z.s.}(t) = \frac{1}{(s+2)(s+1)} = \frac{-1}{s+2} + \frac{1}{s+1}$$

$$V_c^{impulse}(t) = (-e^{-2t} + e^{-t}) u(t)$$

Case of $f(t) = 3e^{-t} u(t)$

$$F(s) = \frac{3}{s+1} \rightarrow V_c^{z.s.}(t) = \frac{3}{(s+1)^2(s+2)}$$

$$= \frac{A}{s+2} + \frac{B}{s+1} + \frac{C}{(s+1)^2}$$

Note: When we write this equation we implicitly assume that A, B, C are scalars, i.e. numbers!

Important Note: Make sure that A, B, C is indeed a scalar, not something else.

$$A = \frac{3}{(-1)^2} = 3$$

$$B = \dots$$

$$C = \frac{3}{1} = 3$$

$$\frac{C(s+1)}{(s+1)^2}$$

$$\frac{C(s+1-1)+D}{(s+1)^2} = \frac{C(s+1-1)+D}{(s+1)^2}$$

(C(s+1)+D) derivative gives you

★ How to find B (when we have repeated poles in Laplace domain) singularities

$$\frac{3}{(s+1)^2(s+2)} = \frac{3}{s+2} + \frac{B}{s+1} + \frac{3}{(s+1)^2}$$

$$B = -3$$

put $s=0$ (or any number) $\frac{3}{2} = \frac{3}{2} + \frac{B}{1} + \frac{3}{1}$


- Steps
- ① Multiply by $(s+1)^2 \rightarrow \frac{3}{s+2} = A \frac{(s+1)^2}{s+2} + B(s+1) + C$
 - ② Take derivative of both parts $\rightarrow \frac{-3}{(s+2)^2} = A \frac{d}{ds} \left(\frac{(s+1)^2}{s+2} \right) + B$
 - ③ Evaluate at $s=-1 \rightarrow \frac{-3}{1} = A \frac{2}{1} + B$

Pls check Sadiku's book notes are also on the web!

$$\boxed{B = -3}$$

$$V_c^{z.s.}(t) = (3e^{-2t} - 3e^{-t} + 3e^{-t}) u(t)$$

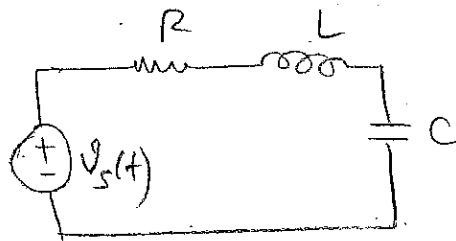Laplace Domain Analysis of State Equation System



$$\begin{bmatrix} \dot{V}_c(t) \\ \dot{I}_L(t) \end{bmatrix} = \begin{bmatrix} 0 & 1/C \\ -1/L & -R/L \end{bmatrix} \begin{bmatrix} V_c(t) \\ I_L(t) \end{bmatrix} + \begin{bmatrix} 0 \\ 1/L \end{bmatrix} V_s(t)$$

$$\begin{bmatrix} V_c(0^-) \\ I_L(0^-) \end{bmatrix} = \begin{bmatrix} V_0 \\ I_0 \end{bmatrix} \quad t > 0^-$$

Apply Laplace transfer to both parts

$$\begin{bmatrix} sV_c(s) - V_0 \\ sI_L(s) - I_0 \end{bmatrix} = \underbrace{\begin{bmatrix} | & | \\ \hline & \\ \hline | & | \end{bmatrix}}_A \begin{bmatrix} V_c(s) \\ I_L(s) \end{bmatrix} + \underbrace{\begin{bmatrix} | \\ | \end{bmatrix}}_b V_s(s)$$

capital letter

$$s \underline{I} \begin{bmatrix} V_c(s) \\ I_L(s) \end{bmatrix} - A \begin{bmatrix} V_c(s) \\ I_L(s) \end{bmatrix} = \underline{b} V_s(s) + \begin{bmatrix} V_0 \\ I_0 \end{bmatrix}$$

$$(s \underline{I} - A) \begin{bmatrix} V_c(s) \\ I_L(s) \end{bmatrix} = \underline{b} V_s(s) + \begin{bmatrix} V_0 \\ I_0 \end{bmatrix}$$

$$\begin{bmatrix} V_c(s) \\ I_L(s) \end{bmatrix} = (s \underline{I} - A)^{-1} \begin{bmatrix} V_0 \\ I_0 \end{bmatrix} + (s \underline{I} - A)^{-1} \underline{b} V_s(s)$$

L=1H
R=6Ω
C=4/100 F

$$[s \underline{I} - A]^{-1} = \begin{bmatrix} s & -25 \\ -1 & s+6 \end{bmatrix}^{-1} = \frac{1}{\Delta} \begin{bmatrix} s+6 & 25 \\ -1 & s \end{bmatrix}$$

Let's focus on zero-input solution ($V_s(t) = 0$)

$$\Delta = s(s+6) + 25 = s^2 + 6s + 25$$


$$\begin{bmatrix} V_c^{z.i.}(s) \\ I_L^{z.i.}(s) \end{bmatrix} = \frac{1}{s^2 + 6s + 25} \begin{bmatrix} s+6 & 25 \\ -1 & s \end{bmatrix} \begin{bmatrix} V_0 \\ I_0 \end{bmatrix}$$

$$\begin{bmatrix} V_c^{z.i.}(s) \\ \dots \\ I_L^{z.i.}(s) \end{bmatrix} = \begin{bmatrix} \frac{sV_0 + 6V_0 + 25I_0}{s^2 + 6s + 25} \\ \dots \\ \frac{sI_0 + V_0}{s^2 + 6s + 25} \end{bmatrix} = \begin{bmatrix} \frac{(s+3)V_0 + 3V_0 + 25I_0}{(s+3)^2 + 4^2} \\ \dots \\ \frac{(s+3)I_0 - 3I_0 - V_0}{(s+3)^2 + 4^2} \end{bmatrix}$$

$$\begin{bmatrix} v_c^{z.i.}(t) \\ \dots \\ i_L^{z.i.}(t) \end{bmatrix} = \begin{bmatrix} V_0 e^{-3t} \cos 4t + \frac{3V_0 + 25I_0}{4} e^{-3t} \sin 4t \\ I_0 e^{-3t} \cos 4t + \frac{(-3I_0 - V_0)}{4} e^{-3t} \sin 4t \end{bmatrix}$$

$$\mathcal{L}^{-1} \left\{ \frac{s \omega}{s^2 + \omega^2} \right\} = \sin \omega t$$
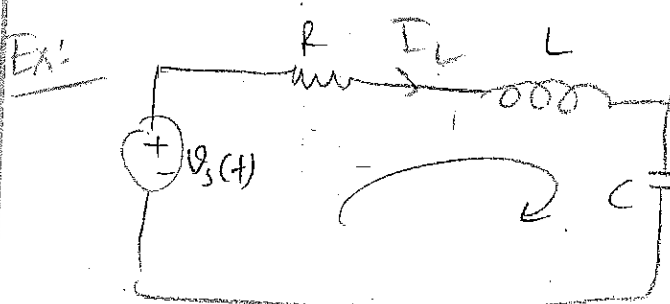
$$\mathcal{L}^{-1} \left\{ \frac{s}{s^2 + \omega^2} \right\} = \cos \omega t$$



Apply mesh analysis and transform the mesh equations to Laplace domain.

Mesh 2: $-v_s(t) + R i_L(t) + L \frac{d}{dt} i_L(t) + v_c(t) + \frac{1}{C} \int_0^t i_L(\tau) d\tau = 0$

$$\mathcal{L}\{ \dots \} \rightarrow -V_s(s) + R I_L(s) + L(s I_L(s) - I_0) + \frac{V_0}{s} + \frac{1}{C} \frac{I_L(s)}{s} = 0$$

$$I_L(s) = \frac{V_s(s) - V_0/s + I_0}{R + sL + \frac{1}{Cs}} = \frac{\frac{s}{L} (-\frac{V_0}{s} + I_0)}{s^2 + \frac{R}{L}s + \frac{1}{LC}} + \frac{\frac{s}{L} V_s(s)}{s + \frac{R}{L}s + \frac{1}{LC}}$$

phasor

A.C. Circuit Analysis

① Phasor Concept:

$$v(t) = V_m \cos(\omega t + \phi) = \text{Re} \{ V_m e^{j(\omega t + \phi)} \} = \text{Re} \{ V_m e^{j\phi} e^{j\omega t} \}$$

Phasors help us to reduce the computations with trigonometric functions.

Euler's Formula: $e^{j\theta} = \cos \theta + j \sin \theta$

$$\cos \theta = \frac{e^{j\theta} + e^{-j\theta}}{2}$$

$$\sin \theta = \frac{e^{j\theta} - e^{-j\theta}}{2j}$$

$$j = \sqrt{-1}$$

phasor: $\text{Re} \{ e^{j\theta} \} = \cos \theta$

$$A \cos(\omega t + \phi) = A \text{Re} \{ e^{j(\omega t + \phi)} \} \longleftrightarrow A \angle \phi$$

phasor

Note that frequency (ω) is missing in $A \angle \phi$ representation

Ex: $f_1(t) = A_1 \cos(\omega t + \phi_1)$


$$f_2(t) = A_2 \cos(\omega t + \phi_2) \quad \mathcal{F}_1: f_1(t) + f_2(t) = ?$$

$$\hookrightarrow \text{Re} \{ A_1 e^{j(\omega t + \phi_1)} \} + \text{Re} \{ A_2 e^{j(\omega t + \phi_2)} \} = \text{Re} \{ A_1 e^{j(\omega t + \phi_1)} + A_2 e^{j(\omega t + \phi_2)} \}$$

$$= \operatorname{Re} \left\{ (A_1 e^{j\phi_1} + A_2 e^{j\phi_2}) e^{j\omega t} \right\} = \operatorname{Re} \left\{ \|X\| e^{j\Delta X} \cdot e^{j\omega t} \right\}$$

$$= \|X\| \cdot \operatorname{Re} \left\{ e^{j(\omega t + \Delta X)} \right\} \quad \begin{array}{l} \text{polar coord.} \\ \text{rep. } \phi \end{array}$$

$$= \|X\| \cos(\omega t + \Delta X)$$

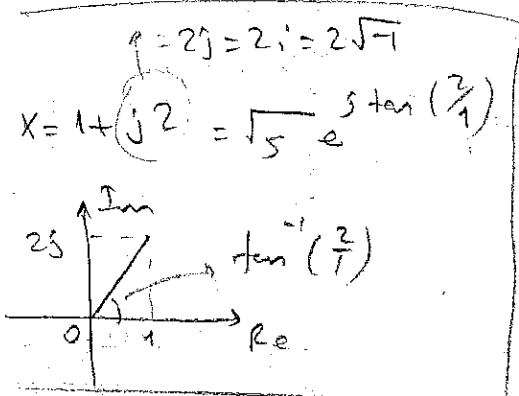

$$(1+2j) + (5+3j) = 6 + j5$$

$$(1+2j)(5+3j) = (5-6) + j(10+3)$$

$$\sqrt{5} e^{j \tan^{-1}(2)} \cdot \sqrt{34} e^{j \tan^{-1}(3/5)} = \sqrt{170} e^{j(\tan^{-1} 2 + \tan^{-1} 3/5)}$$

Ex: $3 \cos(\omega t) + 4 \sin(\omega t) = ?$

$$= \operatorname{Re} \left\{ 3e^{j\omega t} + 4e^{j(\omega t - 90^\circ)} \right\} = \operatorname{Re} \left\{ e^{j\omega t} (3 - 4j) \right\}$$

$$= \operatorname{Re} \left\{ e^{j\omega t} (3 - 4j) \right\}$$

\swarrow
 $5 e^{-j \tan^{-1}(4/3)}$

$$= 5 \cos(\omega t - \tan^{-1}(4/3))$$

$$3 \cos(2t) + 4 \sin(2t) = ?$$

Phasor

Phasor



$$3 \angle 0^\circ + 4 \angle -90^\circ \quad (\omega = 2 \text{ rad/sec})$$

$$= 3 - 4j$$

$$= 5 \angle -\tan^{-1}(4/3)$$

Phasor

$$5 \cos(2t - \tan^{-1}(4/3))$$

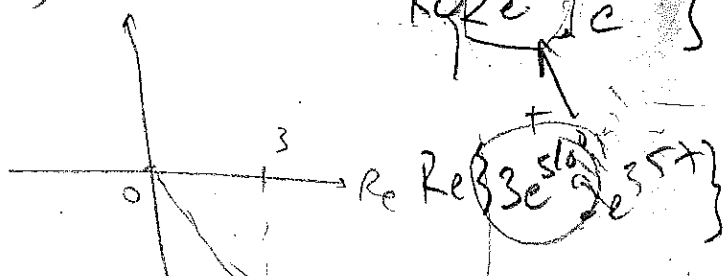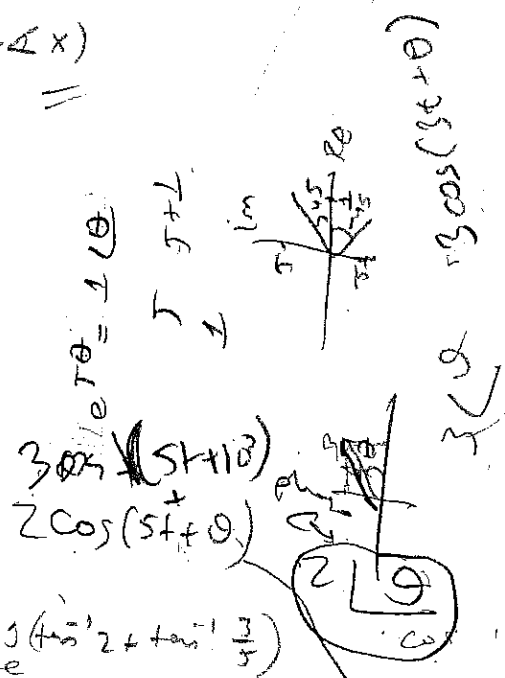

$$= \operatorname{Re} \left\{ (2e^{j0} + 3e^{j10}) e^{j5t} \right\}$$


Phasor

$$\begin{aligned} e^j &= \cos(\omega t) + j \sin(\omega t) \\ e^{-j} &= \cos(\omega t) - j \sin(\omega t) \\ \frac{e^j + e^{-j}}{2} &= \cos(\omega t) \end{aligned}$$

Ex 1 $\sum_{k=1}^{10} \cos(\omega t + \frac{2\pi}{10} k) = ?$

$= \text{Re} \left\{ e^{j\omega t} \left(\sum_{k=1}^{10} e^{j \frac{2\pi}{10} k} \right) \right\}$
 $= 0$

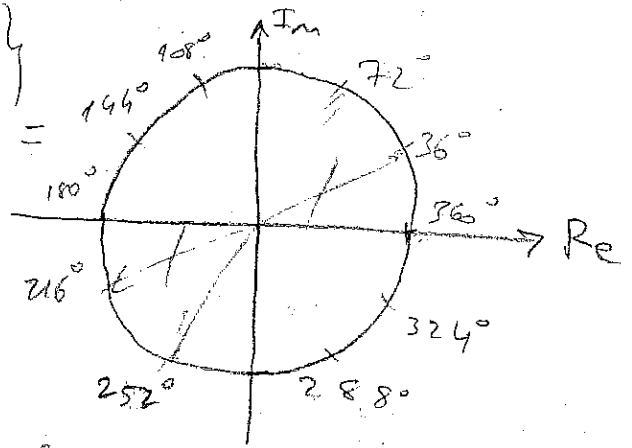$\sum_{k=1}^N \text{Re} \left\{ e^{j\omega t} e^{j \frac{2\pi}{10} k} \right\}$



Ex 2 $f(t) = 3 \cos(5t + 30^\circ)$

$\dot{f}(t) = \frac{df(t)}{dt} = -15 \sin(5t + 30^\circ)$

frequencies are the same!

$f(t) + \dot{f}(t) = ?$

$3 \cos 30^\circ - 15 \sin(30^\circ - 90^\circ) \quad (\omega = 5)$

$3 \cos 30^\circ - 15 \sin(-60^\circ) \quad (\omega = 5)$

$= 3 \left(\frac{\sqrt{3}}{2} + j \frac{1}{2} \right) - 15 \left(\frac{1}{2} - j \frac{\sqrt{3}}{2} \right)$

$= \left(\frac{3\sqrt{3} - 15}{2} \right) + j \left(\frac{3 + 15\sqrt{3}}{2} \right)$

$\left(\frac{3\sqrt{3} - 15}{2} \right) \cos(5t) + \left(\frac{3 + 15\sqrt{3}}{2} \right) \sin(5t)$

$= \frac{3\sqrt{3} - 15}{2} \cos(5t) + \frac{3 + 15\sqrt{3}}{2} \sin(5t)$

$= \cos(5t + 0^\circ)$

$\text{Re} \left\{ 3 e^{j5t} e^{j30^\circ} \right\}$

$\text{Re} \left\{ e^{j5t} \left(3e^{j30^\circ} - 15e^{j(30^\circ - 90^\circ)} \right) \right\}$


$90^\circ - (30^\circ + 5t)$
 $\cos(60^\circ - 5t) = \cos(5t - 60^\circ)$

$M \angle \phi \leftrightarrow \text{Re} \left\{ M e^{j(\omega t + \phi)} \right\} \leftrightarrow M \cos(\omega t + \phi)$

$M e^{j\phi} = M(\cos \phi + j \sin \phi)$

Euler's formula

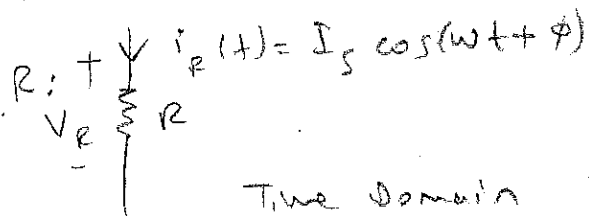Phasor Circuit Analysis and KVL in phasor Domain



Time Domain

$$i_R(t) = I_S \cos(\omega t + \phi)$$



$$V_R = R I_S \cos(\omega t + \phi)$$

Phasor Domain

$$I_R = I_S \angle \phi$$

$$V_R = R I_S \angle \phi$$

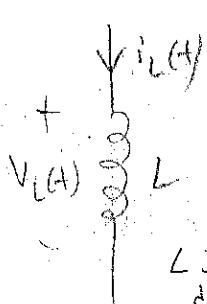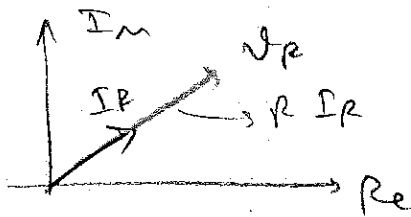(Resistance scales current phasor by R .)



Time Domain

$$i_L(t) = I_S \cos(\omega t + \phi)$$

$$V_L(t) = -L I_S \omega \sin(\omega t + \phi)$$

$$L \frac{d}{dt} i_L(t) = -L I_S \omega \cos(\omega t + \phi - 90^\circ)$$

$$= L I_S \omega \cos(\omega t + \phi - 90^\circ + 180^\circ)$$

$$= \omega L I_S \cos(\omega t + \phi + 90^\circ)$$


Phasor Domain

$$I_L = I_S \angle \phi$$


$$V_L = \omega L I_S \angle \phi + 90^\circ$$

$$= j \omega L I_S \angle \phi$$

(Remember $j = 1 \angle 90^\circ$)

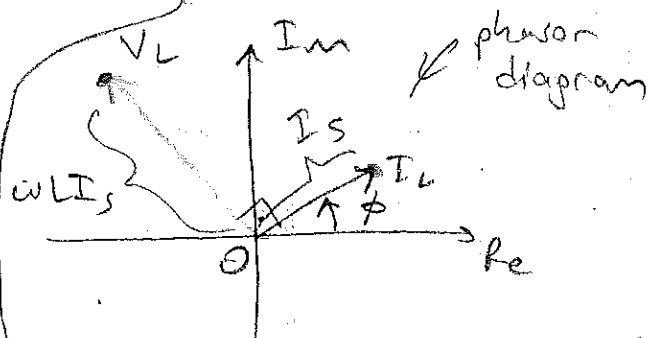

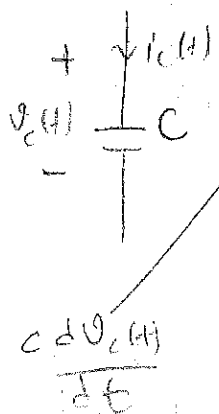Voltage phasor leads current phasor by 90° for the inductor.



Time Domain

$$i_C(t) = I_S \cos(\omega t + \phi)$$

$$V_C(t) = \frac{I_S}{\omega C} \sin(\omega t + \phi)$$

$$= \frac{I_S}{\omega C} \cos(\omega t + \phi - 90^\circ)$$


Phasor Domain

$$I_C = I_S \angle \phi$$

$$V_C = \frac{I_S}{\omega C} \angle \phi - 90^\circ$$

$$= \left(\frac{I_S}{\omega C} \angle \phi \right) (1 \angle -90^\circ)$$
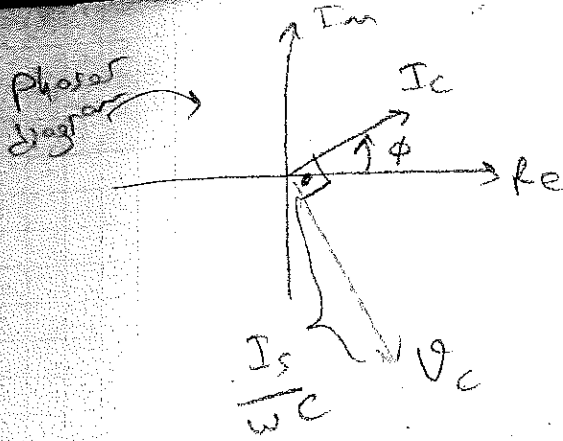
$$= \frac{1}{j \omega C} I_S \angle \phi$$



V_{cap} lags i_{cap} by 90°

Impedance: The ratio of voltage phasor over current phasor.


$$Z = \frac{\text{Voltage phasor}}{\text{current phasor}}$$

Complex number division result

Impedance

Phasor domain representation


Arbitrary Digital

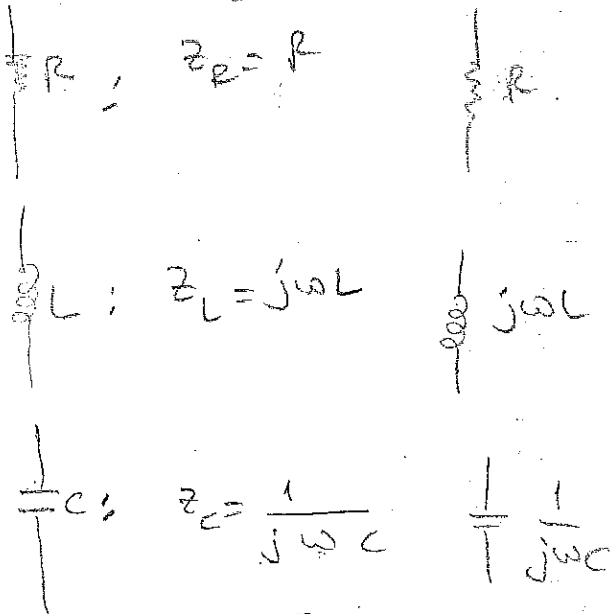

Digital Signal
↓
bitap


362
Logic
Oder bin Map
Wichtig
für Studenten

Ex:

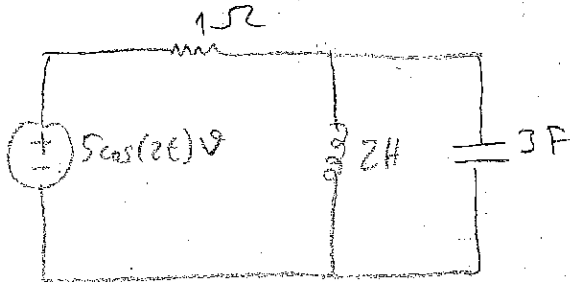

Find $i_s(t)$ at steady-state

Phasor domain circuit

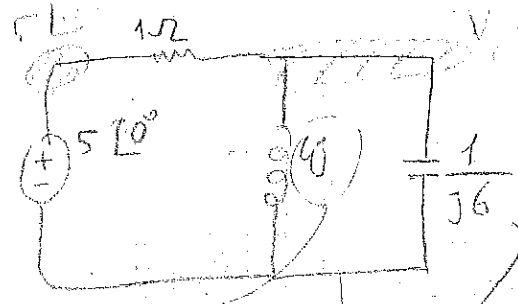

$(\omega=2)$

$$Z_L = j\omega L = j2 \cdot 2 = j4$$

$$Z_C = \frac{1}{j\omega C} = \frac{1}{j2 \cdot 3} = \frac{1}{j6}$$

KCL at V_c node

$$\frac{V_c - 5 \angle 0^\circ}{1} + \frac{V_c}{j4} + \frac{V_c}{1/j6} = 0$$

$$V_c \left(1 + \frac{j}{4} + 6j \right) = 5 \angle 0^\circ$$

$$V_c = \frac{5 \angle 0^\circ}{1 + j5.75}$$

$$V_c = \frac{5}{1 + j \frac{23}{4}} = \frac{5}{\sqrt{1 + \left(\frac{23}{4}\right)^2}} \angle -\tan^{-1}\left(\frac{23}{4}\right)$$


$$v_c^{s.s.}(t) = \frac{5}{\sqrt{1 + \left(\frac{23}{4}\right)^2}} \cos\left(2t - \tan^{-1}\left(\frac{23}{4}\right)\right)$$

AC Steady State Analysis Review

Phasor: A complex number referring to amplitude and phase of a cosine waveform.

Ex: $3 \cos(2t + 15^\circ) \xleftrightarrow[\text{phasor domain}]{\frac{\pi}{12} \text{ radians}} 3e^{j15^\circ} = 3(\cos 15^\circ + j \sin 15^\circ)$
 (Another notation: $3 \angle 15^\circ$)

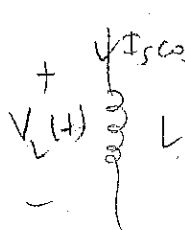Impedance: The ratio of Voltage phasor over current phasor of a circuit component.



$$Z_L = j\omega L$$

Impedance of $L = \frac{\text{Voltage phasor}}{\text{Current phasor}}$

$$= \frac{\omega L I_s \angle (90^\circ + \phi)}{I_s \angle \phi} = \frac{j\omega L I_s \angle \phi}{I_s \angle \phi} = j\omega L$$



$$Z_R = R$$



$$Z_C = \frac{1}{j\omega C}$$

Complex

① $Z = R + jX$ a) Z_L has the units Ω (ohm) as in ordinary resistors.

b) $Re\{Z\} = R$ ← Resistance

$Im\{Z\} = X$ ← Reactance

② $Y = \frac{1}{Z} \rightarrow Re\{Y\}$ is called conductance (G)
 $Im\{Y\}$ is called susceptance.

Admittance

A funny mistake: A component has resistance of 4 ohms and reactance of 5 ohms. What's its conductance and susceptance?

Soln: $Z = 4 + j5$ Then $Y = \frac{1}{Z} = \frac{1}{4 + j5} = \frac{4 - j5}{(4 - j5)(4 + j5)}$

$Re\{Y\} = \text{conductance} = \frac{4}{41}$


$Im\{Y\} = \text{susceptance} = \frac{-5}{41}$

~~conductance $\neq \frac{1}{4}$~~

~~susceptance $\neq \frac{1}{5}$~~

Combination of Impedance

① Series Combination

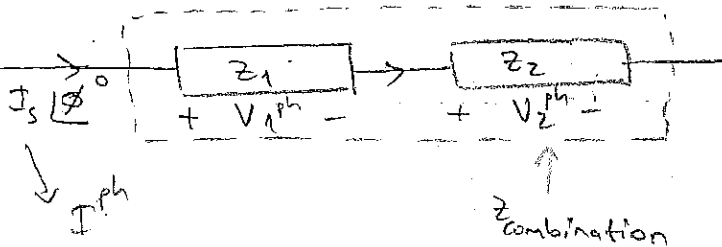

$V_1^{ph} = (Z_1) I_s \angle \phi$


$V_2^{ph} = (Z_2) I_s \angle \phi$

$V_1^{ph} + V_2^{ph} = (Z_1 + Z_2) I_s \angle \phi$

$\rightarrow Z_{\text{combination}} = \frac{V_{\text{combination}}^{ph}}{I_{\text{combination}}^{ph}}$

$= Z_1 + Z_2$

② Parallel Combination

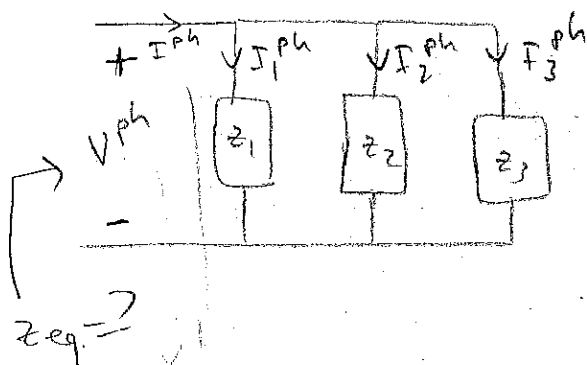

All are cosine.

$I^{ph} = I_1^{ph} + I_2^{ph} + I_3^{ph}$

$= \frac{V^{ph}}{Z_1} + \frac{V^{ph}}{Z_2} + \frac{V^{ph}}{Z_3}$


$= \left(\frac{1}{Z_1} + \frac{1}{Z_2} + \frac{1}{Z_3} \right) V^{ph}$

$\rightarrow \frac{V^{ph}}{I^{ph}} = \left(\frac{1}{Z_1} + \frac{1}{Z_2} + \frac{1}{Z_3} \right)^{-1}$


A.C. Steady State Analysis is identical to earlier resistive LTI circuit analysis methods with the introduction of phasor and Impedance concepts.

So, Thevenin Equivalents, Δ -Y conversions, Source Transformations, Mesh/Node analysis etc. are applicable as they are with the replacement of resistances with Impedances.

Ex: Mesh Analysis

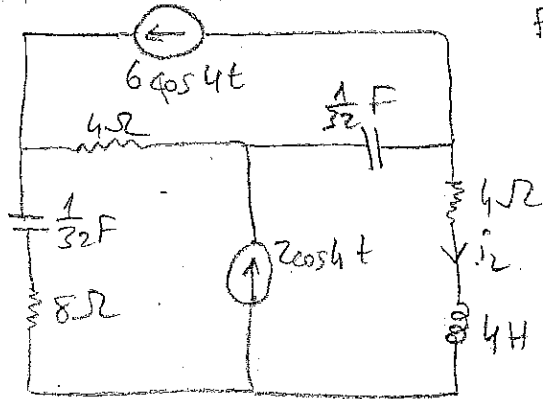

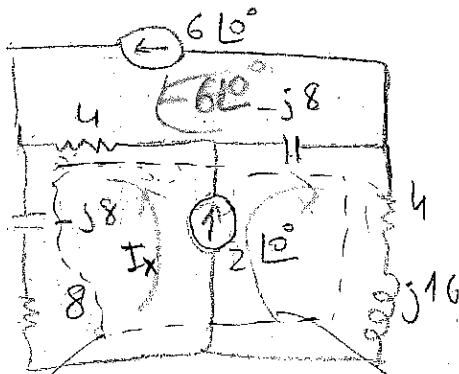Find $i_L^{ss}(t)$
 → steady state current of inductor L.
 → phasor domain



phasor domain circuit
 $(\omega = 4 \text{ rad/sec})$
 $2\angle 0^\circ - I_x$

Supermesh

$$\text{KVL: } 4(6\angle 0^\circ - I_x) - j8(6\angle 0^\circ + 2\angle 0^\circ - I_x) + (4 + j16)[2\angle 0^\circ - I_x] + (8 - j8)(-I_x) = 0$$

$$I_x = \frac{-(24 - j64 + 8 + j32)}{-4 + j8 - 4 - j16 - 8 + j8} \quad I_x = \frac{32 - j32}{16}$$


$$I_L = 2\angle 0^\circ - I_x = \frac{j32}{16} = j2$$

← phasor value of $i_L^{ss}(t)$


$$I_L^{ph} = j2 = 2\angle 90^\circ$$

$$i_L^{ss}(t) = 2\cos(4t + 90^\circ) \text{ A}$$

Ex:

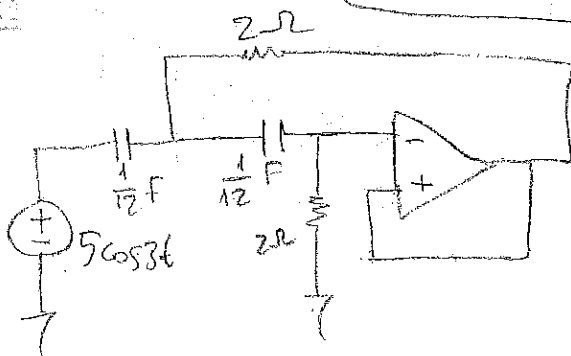

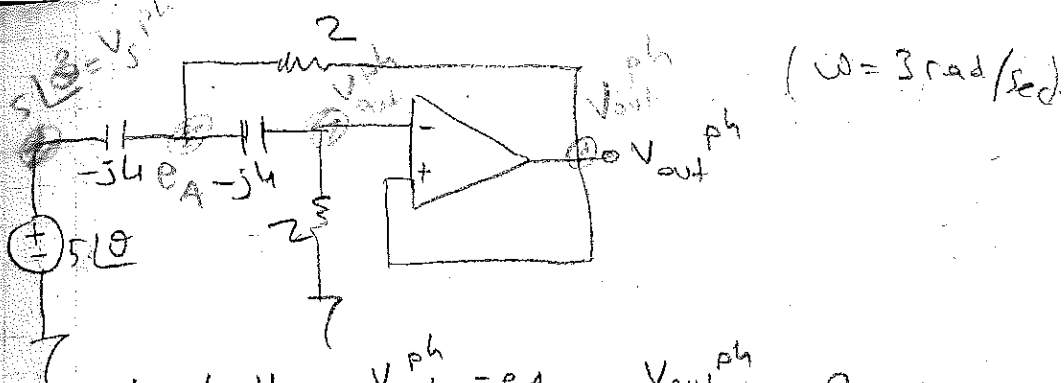Find $V_{out}(t)$
 at steady-state
 (Assume op-amp is an ideal op-amp in linear region)



KCL at V_- : $\frac{V_{out}^{ph} - e_A}{-j4} + \frac{V_{out}^{ph}}{2} = 0 \rightarrow$

$e_A = (1 - j2) V_{out}^{ph}$

KCL at e_A : $\frac{e_A - 5\angle\theta}{-j4} + \frac{e_A - V_{out}^{ph}}{2} + \frac{e_A - V_{out}^{ph}}{-j4} = 0$
 $(1 - j2 + 1)e_A + (j2 - 1)V_{out}^{ph} = 5\angle\theta$

$(1 - j2)V_{out}^{ph}$

$[(2 - j2)(1 - j2) + (2j - 1)]V_{out}^{ph} = 5\angle\theta$

$(1 - j2)(1 - j2) = (1 - j2)^2$

$= -3 - j4$

$V_{out}^{ph} = \frac{5\angle\theta}{-3 - j4} = \frac{5\angle\theta}{5 \sqrt{\tan^{-1} \frac{4}{3} + 180^\circ}}$


$\rightarrow V_{out}^{ph} = 1 \angle \theta - \tan^{-1} \frac{4}{3} - 180^\circ$

$V_{out}^{ss}(t) = 1 \cos(3t + \theta - \tan^{-1} \frac{4}{3} - 180^\circ)$ Volts


→ the particular solution.

General solution $\pm V_{out}^{ss}(t) + A_1 e^{s_1 t} + A_2 e^{s_2 t}$

Node Analysis:

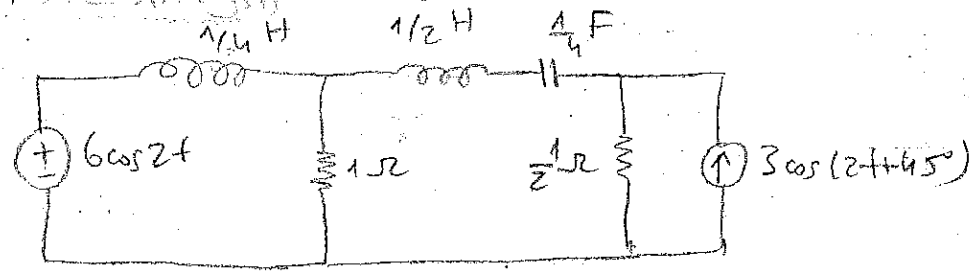

Find s.s. (steady state) node voltages.

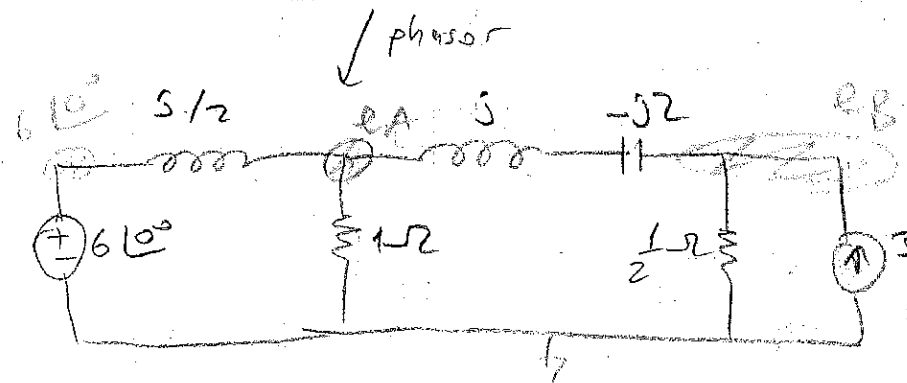

($\omega = 2$ rad/sec)

KCL at e_A :

$$\frac{e_A - 6 \angle 0^\circ}{j/2} + \frac{e_A}{1} + \frac{e_A - e_B}{-j} = 0$$

KCL at e_B :



$$\frac{e_B - e_A}{-j} + \frac{e_B}{1/2} - 3 \angle 45^\circ = 0$$

$$\begin{bmatrix} -j2 + j & -j \\ -j & j + \frac{1}{2} \end{bmatrix} \begin{bmatrix} e_A \\ e_B \end{bmatrix} = \begin{bmatrix} -j/2 \\ 3 \angle 45^\circ \end{bmatrix}$$



$\begin{bmatrix} e_A \\ e_B \end{bmatrix} = \begin{bmatrix} 5.82 \angle -51^\circ \\ 3.93 \angle 14^\circ \end{bmatrix}$
 $e_A^{ss}(t) = 5.82 \cos(2t - 51^\circ) \text{ V}$
 $e_B^{ss}(t) = 3.13 \cos(2t - 14^\circ) \text{ V}$

AC Analysis (cont'd)

Source with different frequencies

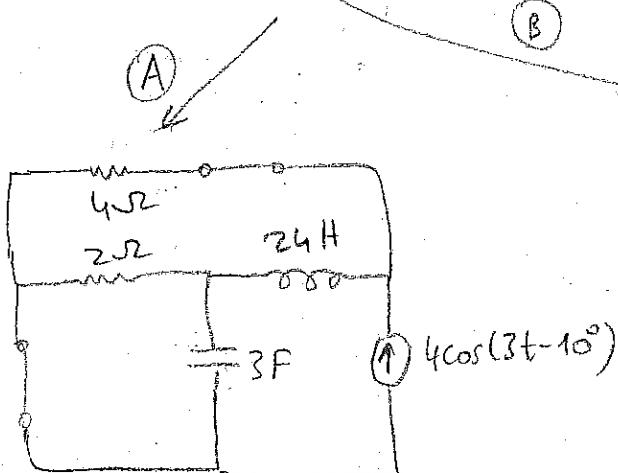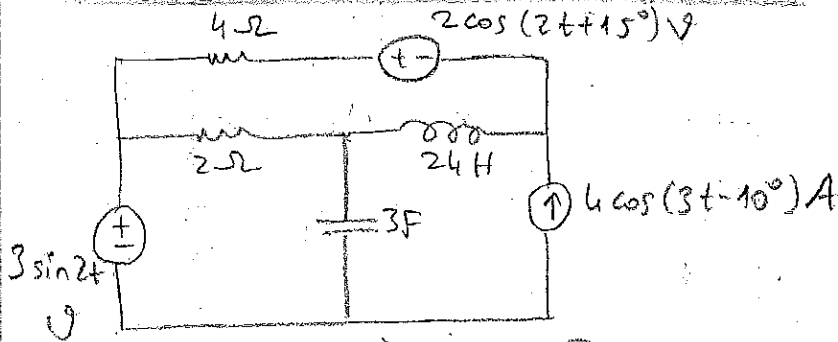

($\omega = 3$) phasor domain

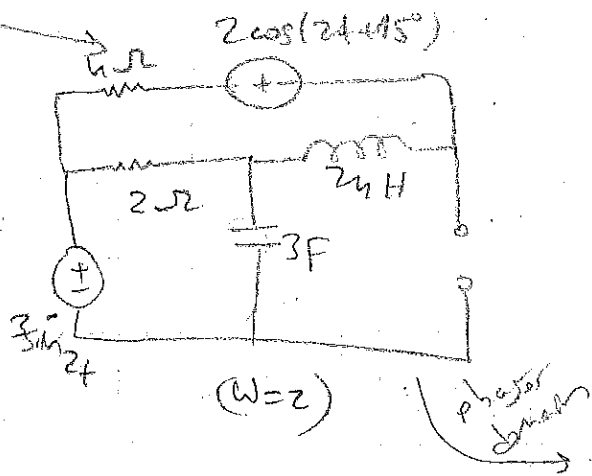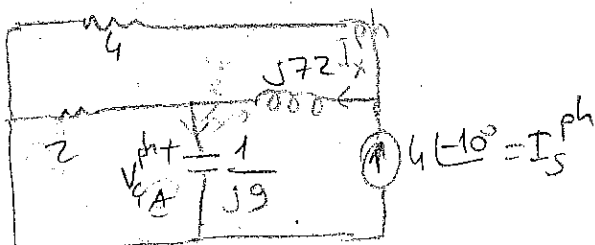

$$2 \parallel \frac{-j}{9} = \frac{-2j/9}{2 - j/9} = \frac{-2j}{18 - j}$$


$$I_x^{ph} = I_s^{ph} \frac{4}{4 + \frac{-2j}{18-j} + j72}$$

$$I_y^{ph} = I_x^{ph} \frac{2}{2 - \frac{j}{9}}$$


$$V_{C(A)}^{ph} = I_y^{ph} \cdot \frac{1}{j9} = \frac{16}{45} \angle -100^\circ$$

$$V_{C(A)}^{s.s.}(t) = \frac{16}{45} \cos(3t - 100^\circ) \text{ Volts}$$

phasor domain (B)

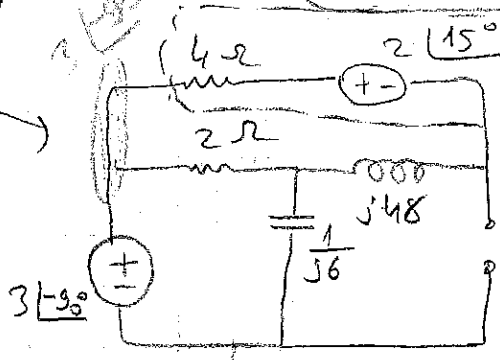

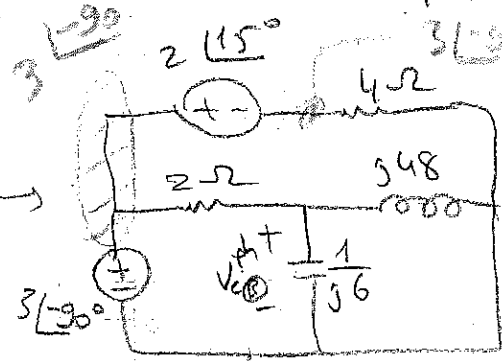We can change the places of V.C. and the 4Ω resistor.



KCL at $V_{C(B)}^{ph}$:


$$\frac{V_{C(B)}^{ph}}{\frac{1}{j6}} + \frac{V_{C(B)}^{ph} - 3\angle -90^\circ}{2} + \frac{V_{C(B)}^{ph} - (3\angle -90^\circ - 2\angle 15^\circ)}{4 + j48} = 0$$

$$V_{C(B)}^{ph} = M_{(B)} \angle \theta_{(B)} \rightarrow V_{C(B)}^{s.s.}(t) = M_{(B)} \cos(2t + \theta_{(B)}) \text{ Volts}$$

Final answer:

$$V_C^{s.s.}(t) = V_{C(A)}^{s.s.}(t) + V_{C(B)}^{s.s.}(t) = \frac{16}{45} \cos(3t - 100^\circ) + M_{(B)} \cos(2t + \theta_{(B)}) \text{ Volts}$$


Ex:

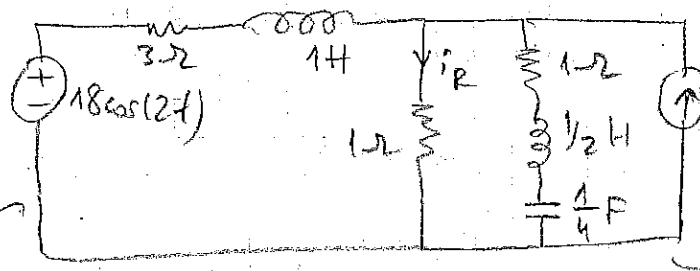

Find $i_R^{s.s.}(t)$

$$8 \cos(\omega t + 0^\circ) \downarrow = 8$$


ω = 0

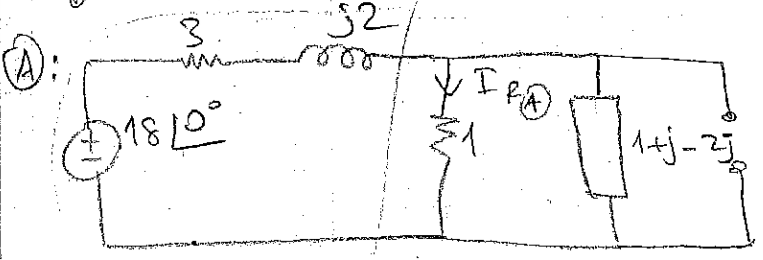


(ω = 2)

Source transformation → current division
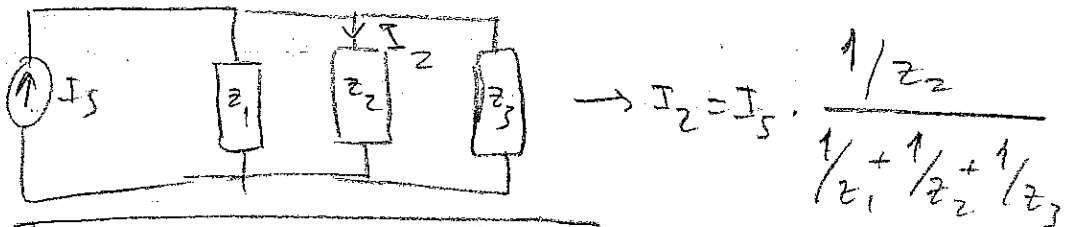
$$I_{R(A)} = \frac{18 \angle 0^\circ}{3 + j2} \cdot \frac{1}{\frac{1}{1} + \frac{1}{(3 + j2) + (1 - j)}} = 2(1 - j) = 2\sqrt{2} \angle -45^\circ$$



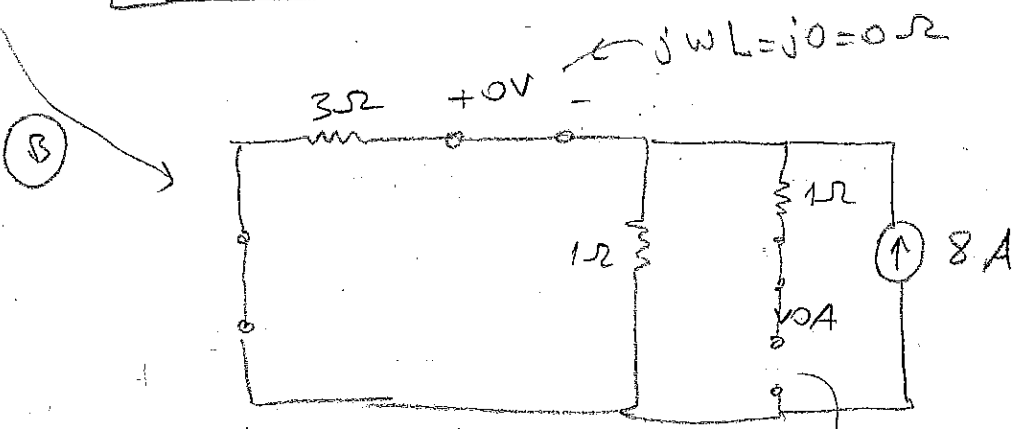$i_{RA}^{ss}(t) = 2\sqrt{2} \cos(2t - 45^\circ) \text{ A}$



$I_{R_1} = 8 \frac{1/1}{1/1 + 1/3} = 6 \text{ A}$


cap: $Z_c = \frac{1}{j\omega C} = \infty$
 $\omega = 0$

$i_{R_1}^{ss} = 6 \text{ A}$


Final answer:
 $i_e^{ss}(t) = i_e^{ss}(t) + i_e^{ss}(t)$
 $i_e^{ss}(t) = 2\sqrt{2} \cos(2t - 45^\circ) + 6, \text{ A}$

Thevenin - Norton Equivalents

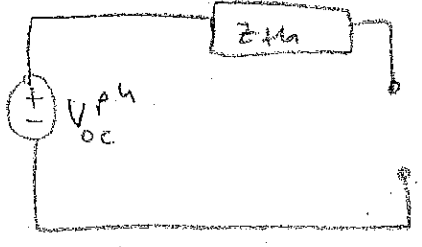The method for Thevenin-Norton equivalent finding applies with no changes in phasor domain. The only difference is, we have Z_{Th} (Thevenin impedance) instead of R_{Th} . So, the Thevenin equivalent in phasor domain is




Thevenin Eq.

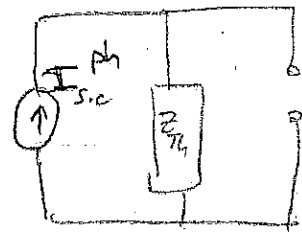

Norton Eq.

Homework Please check:

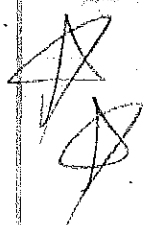


- Sadiku 4th edition
- Ex 9.10 p. 393
 - Ex 9.11 p. 394
 - Ex 10.1 p. 414
 - Ex 10.4 p. 414
 - Ex 10.10 p. 429

- Sadiku
- P. 10.56 p. 449
 - 10.25 p. 445
 - 10.31 p. 446
 - 10.55 p. 449
 - 10.62 p. 450

Answers are at the back of the book

Also check the web-site. HW-3 is on the web! ✈

Mutual Inductor in Phasor Domain

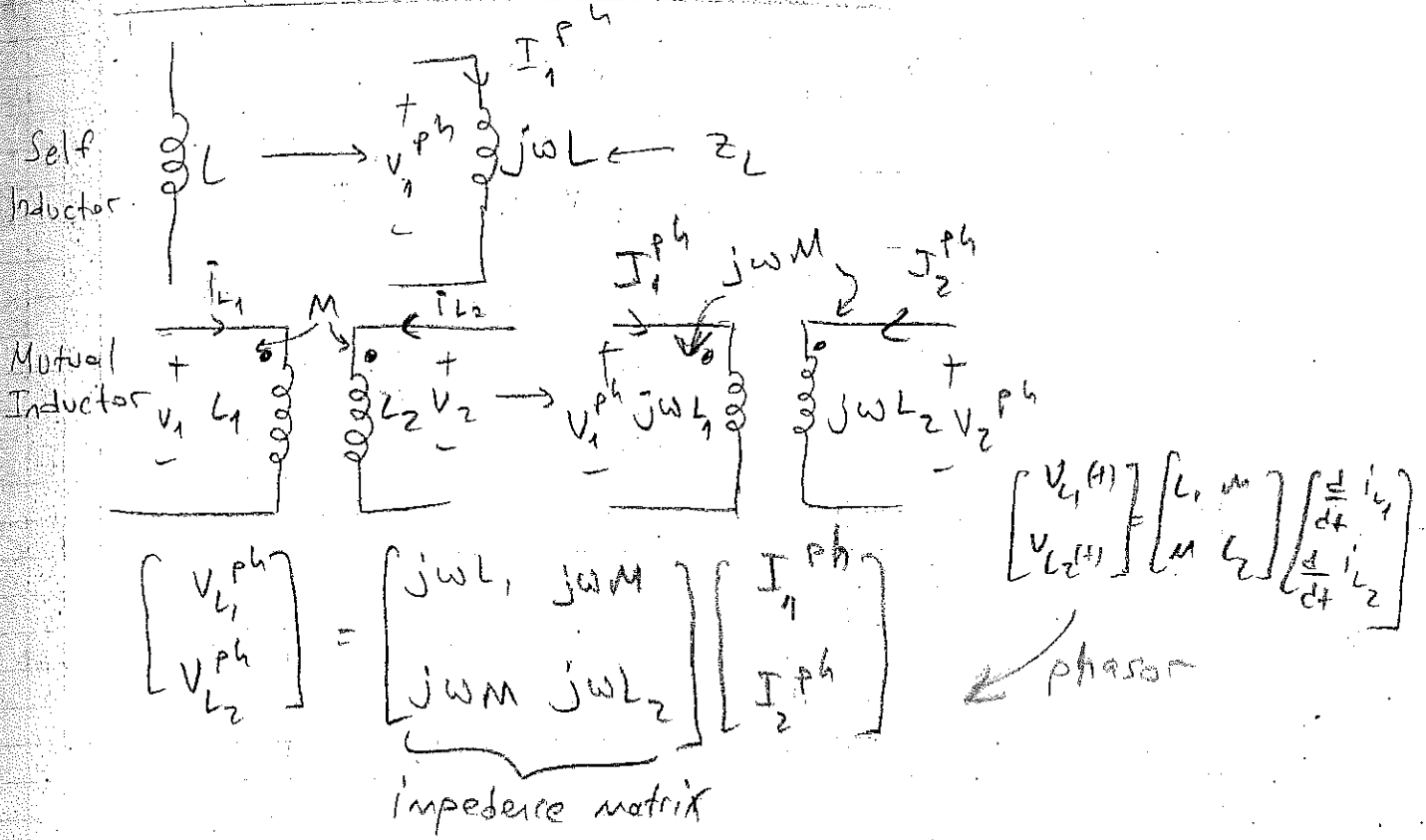


$i_{L1}(t) = A \cos(\omega t + \theta_A)$, $i_{L2}(t) = B \cos(\omega t + \theta_B)$

$I_{L1}^{ph} = A \angle \theta_A$

$I_{L2}^{ph} = B \angle \theta_B$


Transformers

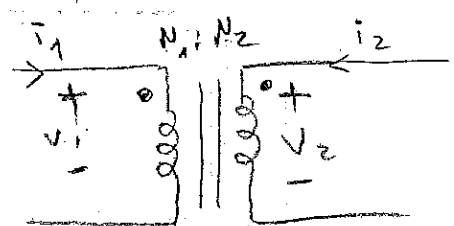


$\frac{V_1}{V_2} = \frac{N_1}{N_2}$ | $\frac{i_1}{i_2} = -\frac{N_2}{N_1}$

remains exactly the same in phasor domain

Ex: (ZPS-II Pr: 5)

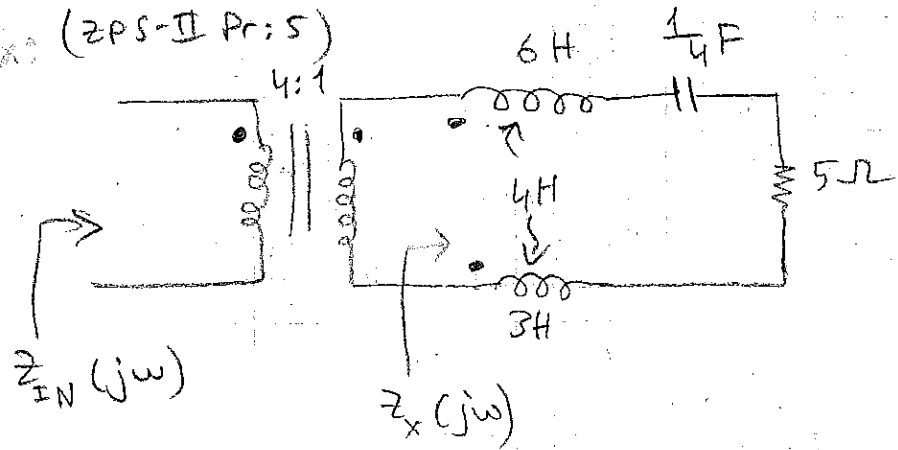

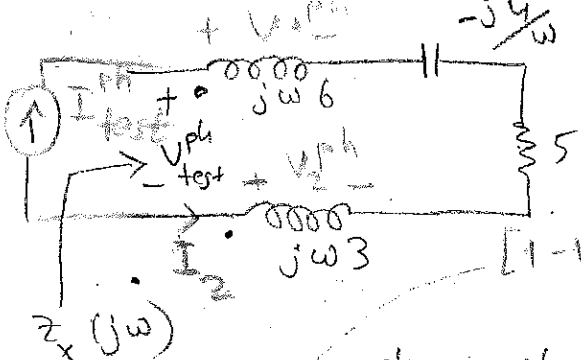

$$Z_x(j\omega) = \frac{V_{test}^{ph}}{I_{test}^{ph}}$$

$$\begin{bmatrix} V_1^{ph} \\ V_2^{ph} \end{bmatrix} = \begin{bmatrix} j\omega 6 & j\omega 4 \\ j\omega 4 & j\omega 3 \end{bmatrix} \begin{bmatrix} I_1^{ph} \\ I_2^{ph} \end{bmatrix}$$


KVL: $-V_{test}^{ph} + V_1^{ph} + (5 - \frac{j4}{\omega}) I_{test}^{ph} - V_2^{ph} = 0$

To obtain this: $V_1^{ph} - V_2^{ph} = [j\omega 2 \quad j\omega] \begin{bmatrix} I_1^{ph} \\ I_2^{ph} \end{bmatrix} = I_{test}^{ph}$

$$V_{test}^{ph} = (j\omega + 5 - \frac{j4}{\omega}) I_{test}^{ph} = -I_{test}^{ph}$$

$$Z_x(j\omega) = \frac{V_{test}^{ph}}{I_{test}^{ph}} = 5 + j(\omega - \frac{4}{\omega})$$

Now:

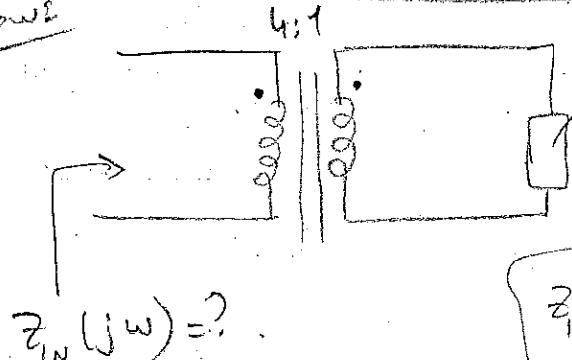

Resistance reflection formula for ideal transformers

$$Z_{in}(j\omega) = (\frac{4}{1})^2 \cdot Z_x(j\omega)$$

$$Z_{in}(j\omega) = 16(5 + j(\omega - \frac{4}{\omega})) \Omega$$


Comments on last example:

$$Z_{in}(j\omega) = 16(5 + j(\omega - \frac{4}{\omega}))$$

$$\omega = 2 \rightarrow Z_{in}(j2) = 80$$

$$\omega = 3 \rightarrow Z_{in}(j3) = 80 + \frac{j80}{3}$$

$$\omega = 1 \rightarrow Z_{in}(j1) = 80 - j48$$

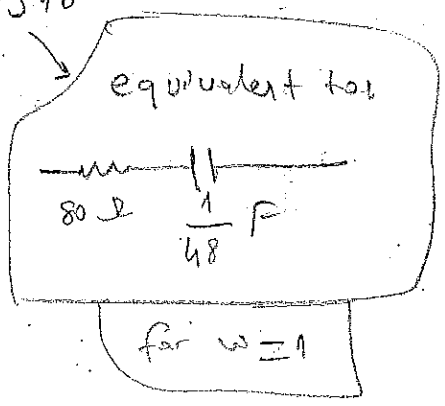

MT 13
AC analysis in
Savara. Kadar
Power - RMS
yok
(0 + j30 + j2) I_c H = 200
(I_c H) = I_o
only responsible for
solution of this

$$(D^2 + 3D + 2) I_L(t) = 2v(t)$$

$$I_L(0^-) = I_0$$

$$\dot{I}_L(0^-) = F_1$$

$$(s^2 + 3s + 2) I_L(s) + (-sI_0 - I_1) - 3I_0 = 2 \cdot \frac{1}{s}$$

$$\hookrightarrow I_L(s) = \frac{2/s + sI_0 + I_1 + 3I_0}{(s^2 + 3s + 2)}$$

$$\lambda = 0$$

$$= \frac{A}{s+1} + \frac{B}{s+2} + \frac{C}{s}$$

① Check the number of the natural frequencies by finding the # of state variables (graphical/tree method)

Existence of Steady-state Solutions

Phasor domain analysis gives us the particular solution to an LTI circuit composed of dynamic components.

We should remember that the complete solution of the circuit, say for the k^{th} branch voltage is

$$V_k^{comp}(t) = \underbrace{A_1 e^{\lambda_1 t} + A_2 e^{\lambda_2 t} + \dots + A_N e^{\lambda_N t}}_{\text{homogeneous solution}} + \underbrace{V_k^{part}(t)}_{\text{particular solution}}$$

If the circuit is stable, that is λ_k 's have negative real parts, then homogeneous solution decays to 0 as $t \rightarrow \infty$

$$\text{Re} \{ \lambda_k \} < 0 \quad \forall k$$

$$(D^2 + 3D + 2) V_k^{ph} = 0$$

$$\lambda = \{-1, -2\}$$

Then for stable circuits,

$$V_k^{comp}(t) \rightarrow V_k^{part}(t) \quad \text{as } t \rightarrow \infty$$

that's the phasor domain solution is the steady state solution ($t \rightarrow \infty$) for stable circuits.


RMS Values

Periodic Functions: $f(t) = f(t - T) \quad \forall t, T \neq 0$ T : Period (Sec)

T : Period of the function.


$$f = \frac{1}{T} \quad \left(\frac{1}{\text{sec}}, \text{Hz} \right)$$

frequency

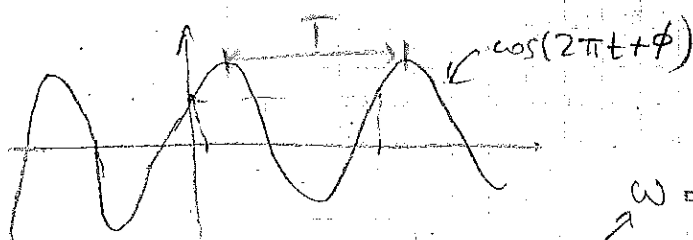

$$\omega = \frac{2\pi}{T} = 2\pi f \quad (\text{rad/sec})$$

(omega) radial frequency

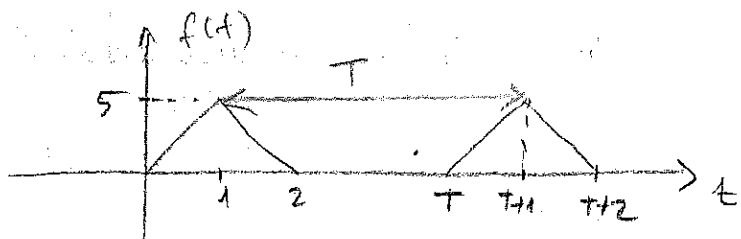

Simple fact: If $f(t)$ is periodic by T , it is also periodic by $2T, 3T, \dots$ in general kT .

The smallest period among all periods is called the fundamental period. $k \in \mathbb{Z}$

In EE301

$$f(t) = \sum_{k=0}^{\infty} a_k \cos\left(\frac{2\pi}{T} kt\right) + b_k \sin\left(\frac{2\pi}{T} kt\right)$$

$f(t)$ has fundamental period of T

RMS: (Root Mean Square)

$f(t)$: Periodic by T

$$f_{RMS} = \sqrt{\frac{1}{T} \int_0^T (f(t))^2 dt}$$

also called effective value

Ex: $f(t) = A \cos(\omega t + \theta)$

$$f_{RMS} = \sqrt{\frac{1}{T} \int_0^T [A \cos(\omega t + \theta)]^2 dt}$$



$$A^2 \cos^2(\omega t + \theta) = \frac{A^2}{2} [\cos(2(\omega t + \theta)) + 1]$$

$$= \sqrt{\frac{1}{T} \int_0^T \frac{A^2}{2} dt + \frac{1}{T} \int_0^T \frac{A^2}{2} \cos(2\omega t + 2\theta) dt}$$

periodic by $\frac{T}{2}$


$$f_{RMS} = \frac{A}{\sqrt{2}}$$

$$\sqrt{\frac{A^2}{2}}$$

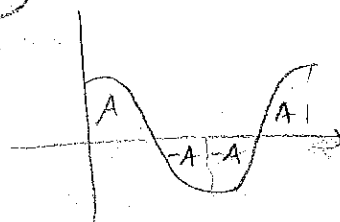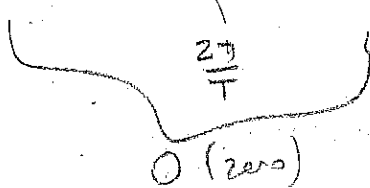

Mean of a Periodic Function

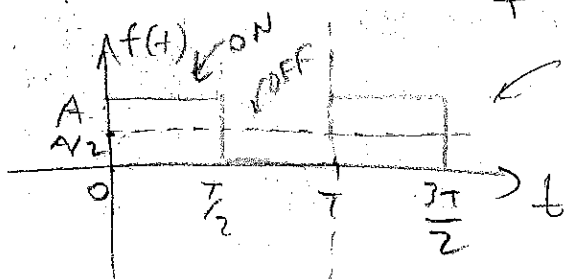
$$\langle f(t) \rangle = \text{mean value} = \frac{1}{T} \int_0^T f(t) dt$$



Square wave with 50% duty cycle.

ON interval is 50% of period.

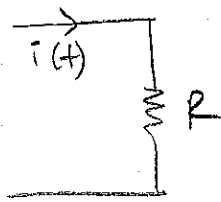Let's find the mean value of Power dissipated over resistor R whose current is periodic.



$$P(t) = R [i(t)]^2$$

Instantaneous power,

$$\langle P(t) \rangle = \frac{1}{T} \int_0^T R [i(t)]^2 dt$$

$$= R (i_{RMS})^2$$

effective value of periodic $i(t)$

$$\Delta E = \int_0^{1 \text{ hour}} P(t) dt$$

work (Joule)

$$= \int_0^{3600 \text{ sec}} R [i(t)]^2 dt$$

$\langle \rangle$ means average

$$T = 20 \text{ msec}$$

$$f = 50 \text{ Hz}$$

$$\frac{3600 \text{ sec}}{20 \text{ msec}} = 180000 \text{ oscillations}$$

$$= 180 \times 10^3 \text{ Energy dissipation per period}$$

$$= 180 \times 10^3 (T P_{AVG})$$



Period

$$= (180 \times 10^3) (20 \text{ msec } (R i_{RMS}^2))$$

$$= 3600 \text{ sec } P_{AVG} \text{ Joule/sec } = (\text{Watt})$$




Ex:

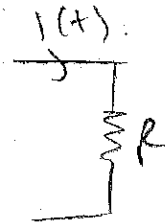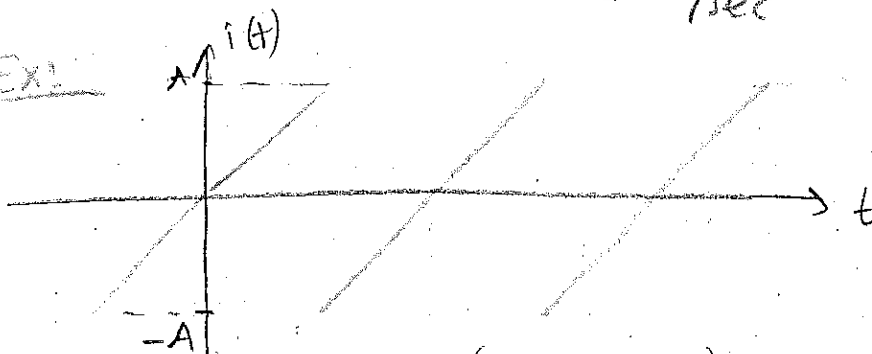

$$\text{Energy dissipated in an hour} = (3600 \text{ sec.}) P_{AVG}$$

$$= (3600 \text{ sec}) R (i_{RMS})^2$$

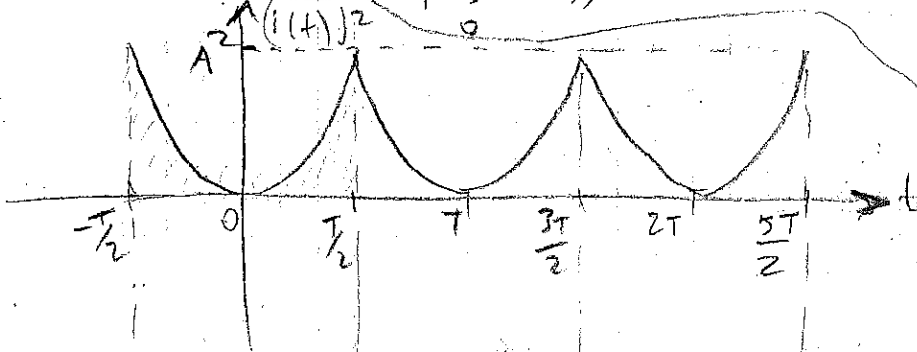
$$i_{RMS} = \sqrt{\frac{1}{T} \int_0^T (i(t))^2 dt} = \sqrt{\frac{1}{T} \int_{-T/2}^{T/2} (A \frac{t}{T})^2 dt}$$



$$= \sqrt{\frac{A^2}{T^3} \int_{-T/2}^{T/2} t^2 dt}$$

$$= \sqrt{\frac{A^2 \cdot \frac{2}{3} T^3}{T^3 \cdot 12/3}}$$

$$i_{RMS} = \frac{A}{\sqrt{3}}$$

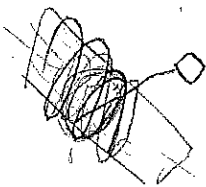

T
24

Since $\langle P \rangle = P_{AVG} = R (i_{rms})^2$

value of i_{rms} can be considered as the equivalent (effective) value of a hypothetical DC source providing the same average power!

RMS values: (continued)



$f(t)$: periodic waveform with period T .

Digital multimeter calculates this.

$$f_{rms} = \sqrt{\frac{1}{T} \int_0^T (f(t))^2 dt} = \sqrt{\lim_{T_x \rightarrow \infty} \frac{1}{T_x} \int_0^{T_x} (f(t))^2 dt}$$

$f(t) = A \cos(\omega t)$ Volt $\rightarrow f_{rms} = \frac{A}{\sqrt{2}}$ Volts

↑ effective value

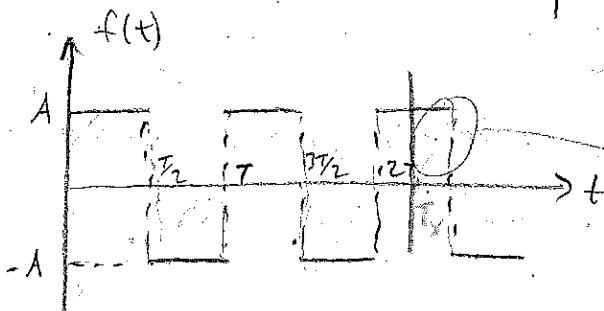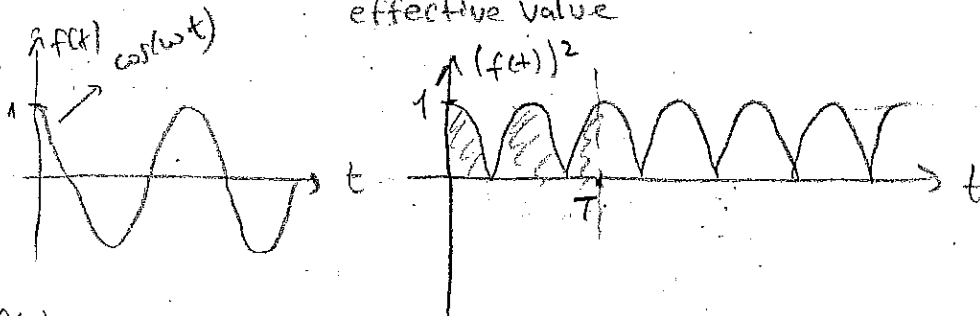

$T = 20$ msec ($f = 50$ Hz)

$T_x = 10$ sec \rightarrow 500 periods

As T_x increases, this additional integral ($T_x - 2T$ in this case) becomes insignificant.

Ex: $f(t) = A_1 \cos\left(\frac{2\pi t}{T_1} + \theta_1\right) + A_2 \cos\left(\frac{2\pi t}{T_2} + \theta_2\right)$ Volts

$T = \text{LCM}(T_1, T_2)$

Lowest common multiple

More significant

$$f_{rms} = \sqrt{\lim_{T_x \rightarrow \infty} \frac{1}{T_x} \int_0^{T_x} (f(t))^2 dt}$$

$$A_1^2 \left(\frac{1 + \cos(2\omega_1 t + 2\theta_1)}{2} \right)$$

$$A_2^2 \left(\frac{1 + \cos(2\omega_2 t + 2\theta_2)}{2} \right)$$

$$A_1^2 \cos^2(\omega_1 t + \theta_1) + A_2^2 \cos^2(\omega_2 t + \theta_2)$$

$$+ 2A_1 A_2 \left[\cos(\omega_1 + \omega_2)t + \theta_1 + \theta_2 + \cos(\omega_1 - \omega_2)t + \theta_1 - \theta_2 \right]$$

2

$$f_{rms} = \sqrt{\frac{A_1^2}{2} + \frac{A_2^2}{2}}$$


So, if $f(t) = A_1 \cos(\omega_1 t) + A_2 \cos(\omega_2 t)$ ($\omega_1 \neq \omega_2$)

$$f_{rms}^2 = f_{rms1}^2 + f_{rms2}^2$$

$$f_{rms1} = \frac{A_1}{\sqrt{2}}$$

$$f_{rms2} = \frac{A_2}{\sqrt{2}}$$

Average and Instantaneous Power

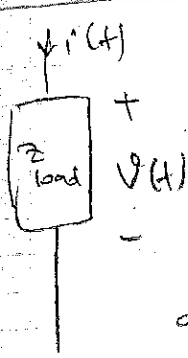

$$v(t) = V_m \cos(\omega t + \theta_v) \rightarrow V^{Ph} = V_m \angle \theta_v$$

$$i_m(t) = I_m \cos(\omega t + \theta_i) \rightarrow I^{Ph} = I_m \angle \theta_i$$

$$Z_{load} = \frac{V^{Ph}}{I^{Ph}} = \frac{V_m}{I_m} \angle \theta_v - \theta_i$$

Goal: Find instantaneous power and its average $P_{AVG} = \langle P(t) \rangle$

Instantaneous power $= |Z_{load}| \angle \theta_{load}$

$$P(t) = v(t) \cdot i(t) = V_m I_m \cos(\omega t + \theta_v) \cos(\omega t + \theta_i)$$

$$\cos(2\omega t + \theta_v + \theta_i) + \cos(\theta_v - \theta_i)$$

$$P_{AVG} = \langle P(t) \rangle = \lim_{T_x \rightarrow \infty} \frac{1}{T_x} \int_0^{T_x} P(t) dt$$

$$P(t) = \frac{V_m I_m}{2} \left[\cos(\theta_{load}) + \cos(2\omega t + 2\theta_i + \theta_{load}) \right]$$

If average approaches to zero.

$$\cos(2\omega t + 2\theta_i) \cos(\theta_{load}) - \sin(2\omega t + 2\theta_i) \sin(\theta_{load})$$

$$P(t) = \frac{V_m I_m}{2} \cos(\theta_{load}) [1 + \cos(2\omega t + 2\theta_i)] - \frac{V_m I_m}{2} \sin(\theta_{load}) [\sin(2\omega t + 2\theta_i)]$$

$$\langle P(t) \rangle = P_{AVG} = \frac{V_m I_m}{2} \cos(\theta_{load}) = V_{RMS}^{load} I_{RMS}^{load} \cos(\theta_{load}) \text{ Watts}$$


If average approaches to zero.

$$Q = \frac{V_m I_m}{2} \sin(\theta_{load}) = V_{RMS}^{load} I_{RMS}^{load} \sin(\theta_{load})$$

Reactive Power

$$P(t) = P_{AVG} + P_{AVG} \cos(2\omega t + 2\theta_i) - Q \sin(2\omega t + 2\theta_i)$$
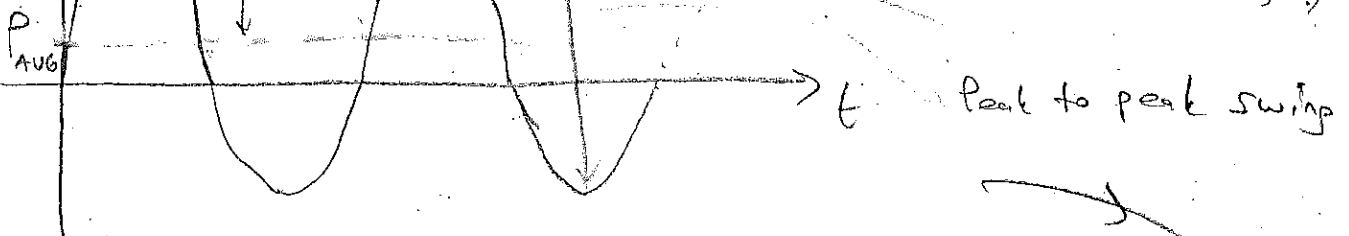
$$= P_{AVG} + \sqrt{P_{AVG}^2 + Q^2} \cos(2\omega t + 2\theta_i + \tan^{-1} \frac{Q}{P_{AVG}})$$




p(t) oscillates with double frequency of voltage and current waveforms (oscillates at 2ω) and its mean/average value is $P_{AVG} = V_{RMS} I_{RMS} \cos(\theta_{Load})$ and it has a peak-to-peak swing value of $2\sqrt{P_{AVG}^2 + Q_{AVG}^2}$ Watts

Notes: Q (Reactive Power) affects peak-to-peak swing of instantaneous power around the average value.

Special Cases

① Load is a Resistor

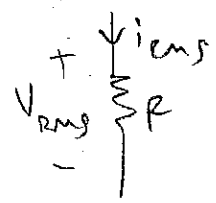

$Z_L = R$

- $P_{AVG} = V_{RMS} I_{RMS} \cos(\theta_{Load})$
- $Q = V_{RMS} I_{RMS} \sin(\theta_{Load})$
- $|Z_L| = R$
- $\angle Z_L = 0^\circ$
- Load (not inductor)
- $1 = V_{RMS} I_{RMS}$ Watts
- 0°
- VAR's
- Volt Ampere Reactive

Remember

$$Z_{load} = \frac{V_{load}^{ph}}{I_{load}^{ph}}$$

$$|Z_{load}| = \frac{|V_{load}^{ph}|}{|I_{load}^{ph}|} \rightarrow |V_{Load}^{ph}| = |Z_{Load}| \cdot |I_{Load}^{ph}|$$

$$V_{Load}^{RMS} \triangleq \frac{\text{Amplitude } V_{Load}}{\sqrt{2}}$$


A.C. signals

$$V_{Load}^{RMS} = |Z_{Load}| I_{Load}^{RMS}$$

→

$$\begin{aligned}
 P_{AVG} &= V_{RMS} I_{RMS} \cos(\theta_{Load}) \rightarrow 1 \text{ for } Z_{Load} = R \\
 &= V_{RMS} I_{RMS} \\
 &= (R I_{RMS}) (I_{RMS}) = R I_{RMS}^2 = \frac{V_{RMS}^2}{R}
 \end{aligned}$$

② Load is Inductor

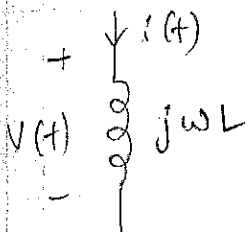


$$Z_{load} = j\omega L = \omega L \angle 90^\circ$$

$$P_{AVG} = V_{RMS} I_{RMS} \cos(\theta_{Load})$$

$$Q = V_{RMS} I_{RMS} \sin(\theta_{Load}) = V_{RMS} I_{RMS}$$

Also absorbed by R is P_{AVG}
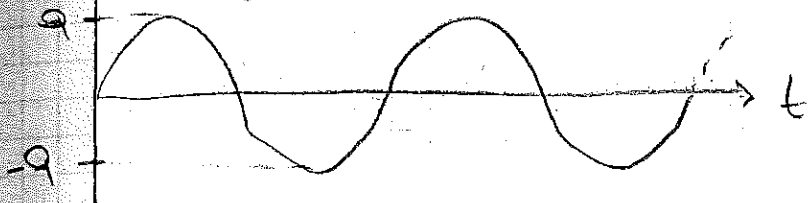
$$p(t) = P_{AVG} + \sqrt{P_{AVG}^2 + Q^2} \cos(2\omega t + 2\theta_i + \tan^{-1} \frac{Q}{P_{AVG}})$$




$$E_{absorbed} = \int_0^{tA} p(t) dt$$

$0 \rightarrow t$

$p(t)$ oscillates between $Q = V_{RMS} I_{RMS}$ and $-Q$

The instantaneous power for $Z_L = R$ is:

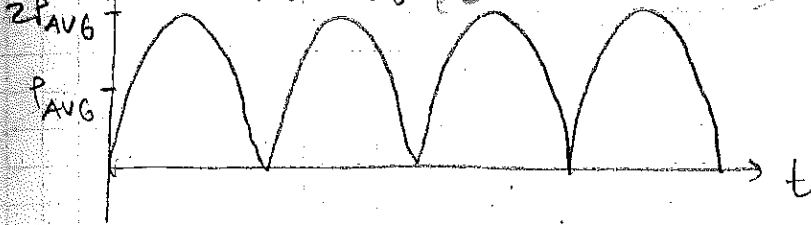
$$p(t) = P_{AVG} + \sqrt{P_{AVG}^2 + Q^2} \cos(2\omega t + 2\theta_i + \tan^{-1} \frac{Q}{P_{AVG}})$$



$$P_{AVG} = V_{RMS} I_{RMS} \cos(\theta_{Load}) = 0$$

$$Q = V_{RMS} I_{RMS} \sin(\theta_{Load}) = -V_{RMS} I_{RMS}$$


③ Load is Capacitor

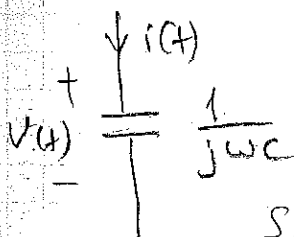

$$Z_{Load} = \frac{1}{j\omega C} = \frac{1}{\omega C} \angle -90^\circ$$

$$Q = V_{RMS} I_{RMS} \sin(\theta_{Load}) = -V_{RMS} I_{RMS}$$

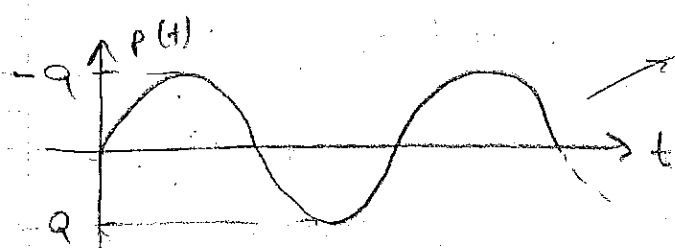Similar to the inductor case capacitor does not consume any power on the average but it may absorb power and store it as energy and then release at a later time.



Instantaneous power of capacitor under AC input at steady state

Note: $Q_{inductor} > 0$
 $Q_{capacitor} < 0$

?

$$A \cos(\omega t) + B \sin(\omega t) = \sqrt{A^2 + B^2} \cos(\omega t - \tan^{-1} \frac{B}{A})$$

1st way

$$A \angle 0^\circ + B \angle -90^\circ = A + (-jB)$$

$$= \sqrt{A^2 + B^2} \angle -\tan^{-1} \frac{B}{A}$$


2nd way

$$A \cos \omega t + B \sin \omega t = ?$$

$$\sqrt{A^2 + B^2} \left[\frac{A}{\sqrt{A^2 + B^2}} \cos(\omega t) + \frac{B}{\sqrt{A^2 + B^2}} \sin(\omega t) \right] = ?$$



$$= \sqrt{A^2 + B^2} [\cos \phi \cos \omega t + \sin \phi \sin \omega t]$$
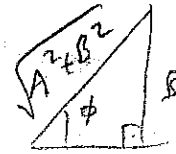
$$\cos(\omega t - \phi) = \cos(\omega t - \tan^{-1} \frac{B}{A})$$



Meaning of Q

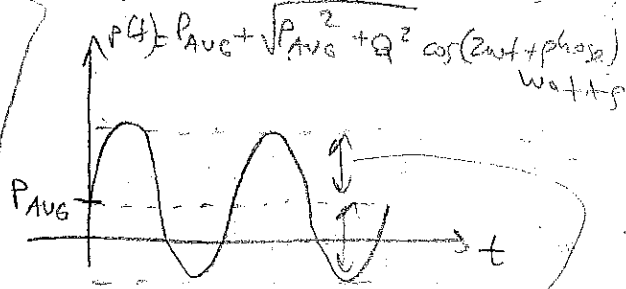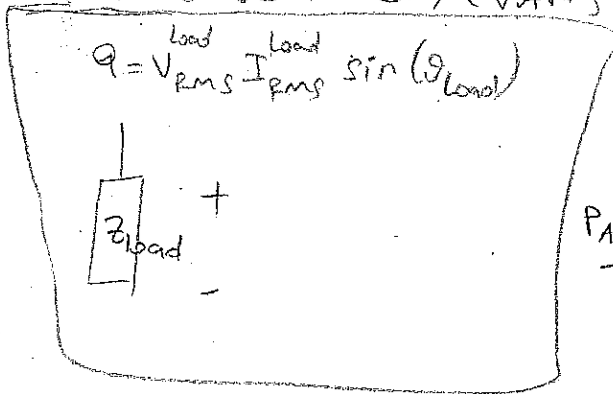Q: Reactive Power, (VAR's) → (Volt-Ampere Reactive)



So Q affects the swing in the instantaneous power from the average power level.

Swing from P_AVG is

$$\sqrt{P_{AVG}^2 + Q^2}$$

$$\text{Apparent Power} \triangleq V_{RMS} I_{RMS} = \sqrt{P_{AVG}^2 + Q^2}$$

Note: The swing amount is identical to the apparent power.

2) Avg and Average Stored Energy in a Cap/Inductor For Capacitor

$$E_{cap}(t) = \frac{1}{2} C V_c^2(t)$$

$$E_{cap}^{AVG} = \langle E_{cap}(t) \rangle = \frac{1}{2} C \langle V_c^2(t) \rangle = \frac{1}{2} C \left[\frac{1}{T} \int_0^T V_c^2(t) dt \right] = \frac{1}{2} C (V_c^{RMS})^2$$

$$E_{cap}^{AVG} = \frac{1}{2} C (V_c^{RMS})^2 \quad (1)$$

$$Q_{cap} = ? \longrightarrow$$

$$Z_{cap} = \frac{1}{j\omega C} = \frac{1}{\omega C} \angle -90^\circ$$

$$Q_{cap} = V_{RMS} I_{RMS} \sin(\theta_{Load})$$

$$= -V_{RMS}^{cap} I_{RMS}^{cap} = -V_{RMS}^{cap} (V_{RMS}^{cap} \omega C)$$

$$Q_{cap} = -\omega C (V_{RMS}^{cap})^2 \quad (2)$$

Then combining (1) with (2)

we get $E_{cap}^{AVG} = \frac{-Q_{cap}}{2\omega}$

$$Q_{cap} = -2\omega E_{cap}^{AVG}$$

$$Z = \frac{1}{\omega C} \angle -90^\circ$$

Q of capacitor is proportional to the average energy stored in the capacitor.

For Inductor

$$E_{ind}^{AVG} = \langle \frac{1}{2} L I_L^2(t) \rangle = \frac{1}{2} L (I_{RMS}^{ind})^2 \quad (1)$$

$$Q_{inductor} = V_{RMS}^{ind} I_{RMS}^{ind} \sin(\theta_{ind})$$

$$\begin{aligned} 90^\circ &= V_{RMS}^{ind} I_{RMS}^{ind} \\ &= (\omega L I_{RMS}^{ind}) I_{RMS}^{ind} \\ &= \omega L I_{RMS}^2 \end{aligned}$$


Combine (1) and (2);

$$Q_{ind} = \omega L I_{RMS}^2 \quad (2)$$

$$Q_{ind} = 2\omega E_{ind}^{AVG}$$

Conservation of P and Q

$$(-P = P_{AVG})$$

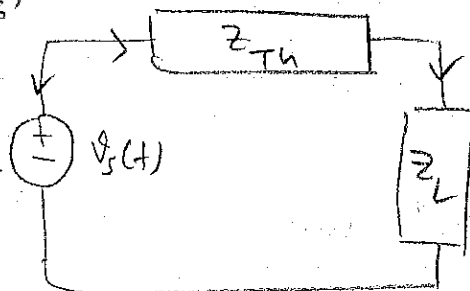


A.C. steady state conditions

$$V_1(t) i_1(t) + V_2(t) i_2(t) + V_3(t) i_3(t) = 0$$

absorbed absorbed absorbed

$$V_2(t) i_2(t) + V_3(t) i_3(t) = -V_1(t) i_1(t), \forall t$$

delivered power (with minus sign)

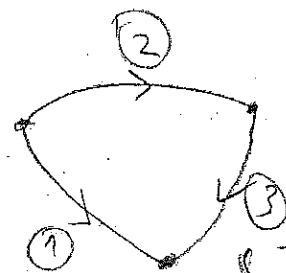

$$\sum_{k=1}^3 P_k(t) = 0$$

Tellegen's Theorem

Conservation of power

$$\sum_{k=1}^3 V_k(t) i_k(t) = 0$$

$$\sum_{k=1}^3 V_k(t) i_k(t) = 0$$

$$i_k(t) = 0$$

Another circuit with the same graph

$$P_k(t) = V_k(t) i_k(t) = P_k + \sqrt{P_k^2 + Q_k^2} \cos(2\omega t + \theta_i + \tan^{-1} \frac{Q_k}{P_k})$$

$$= P_k (1 + \cos(2\omega t + 2\theta_i)) - Q_k \sin(2\omega t + 2\theta_i)$$

$$P_2(t) + P_3(t) = -P_1(t)$$

$k = \{1, 2, 3\}$
 $\forall t$

$$P_{AVG}^{(2)} + P_{AVG}^{(3)} \cos(2\omega t + 2\theta_i) - Q^{(1)} \sin(2\omega t + 2\theta_i)$$

$$P_{AVG}^{(2)} + P_{AVG}^{(3)} \cos(2\omega t + 2\theta_i) - Q \sin(2\omega t + 2\theta_i)$$

$$P_{AVG}^{(2)} + P_{AVG}^{(3)} = -P_{AVG}^{(1)}$$


$$Q^{(2)} + Q^{(3)} = -Q^{(1)}$$

$$-P_{AVG}^{(1)}$$

So, not only instantaneous power but its average P_{AVG} and Q is also conserved.

Complex Power

$$S = P + jQ$$

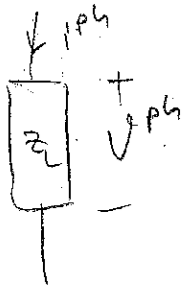

$$P = \frac{|V^{ph}| \cdot |I^{ph}| \cos(\theta_L)}{2} = V_{RMS} I_{RMS} \cos(\theta_L)$$

$\leftarrow (I_1 \cdot I_2)$

$$Q = \frac{|V^{ph}| \cdot |I^{ph}| \sin(\theta_L)}{2} = V_{RMS} I_{RMS} \sin(\theta_L)$$

$$S = P + jQ = V_{RMS} I_{RMS} \cos(\theta_L) + j V_{RMS} I_{RMS} \sin(\theta_L)$$


complex power

Clearly, complex power S is also conserved that is

branches


$$\sum_{k=1} S_k = 0$$

S has the unit of VA (Volt-Ampere)

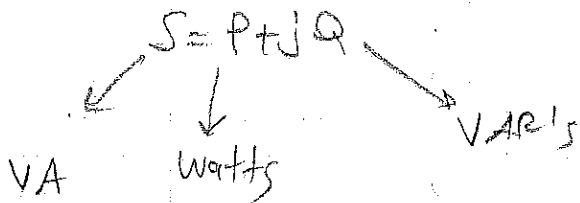

Alternative forms of Complex Power:

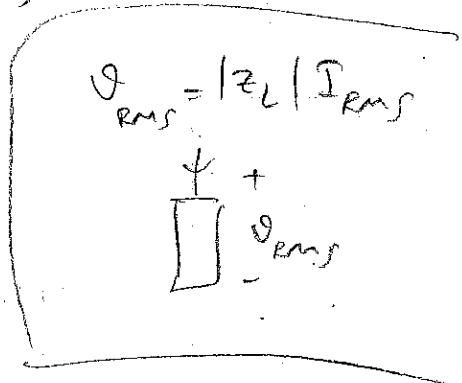
- ① $S = V_{RMS} I_{RMS} (\cos \theta_{Z_L} + j \sin \theta_{Z_L}) = V_{RMS} I_{RMS} e^{j\theta_{Z_L}}$
- ② $S = \frac{1}{2} V^{ph} (I^{ph})^*$ ← Conjugate
- ③ $S = I_{RMS}^2 Z_L$
- ④ $S = \frac{V_{RMS}^2}{(Z_L)^*}$ ← Conjugate!



Complex Power (continued)

$S = P + jQ$

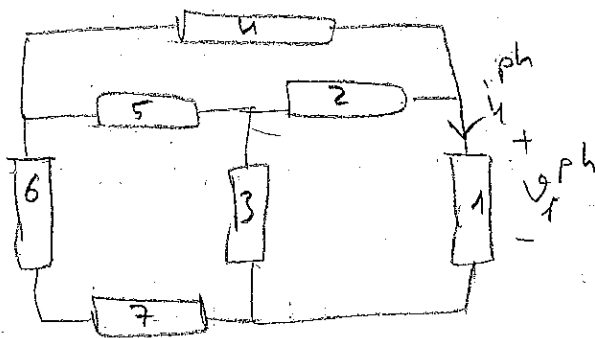Complex Power (VA) Average Power (Watts) Reactive Power (VAR's)



$$\sum_{k=1}^7 P_k = 0 \quad \Bigg| \quad \sum_{k=1}^7 Q_k = 0 \quad \Bigg| \quad S_k = P_k + jQ_k$$

How to Calculate Complex Power

$$P = V_{RMS} I_{RMS} \cos(\theta_{Load}) \quad Q = V_{RMS} I_{RMS} \sin(\theta_{Load})$$

$$① S = V_{RMS} I_{RMS} e^{j\theta_{Load}}$$

$$(Since S = \underbrace{V_{RMS} I_{RMS} \cos(\theta_L)}_P + j \underbrace{V_{RMS} I_{RMS} \sin(\theta_L)}_Q)$$

$$② S = \frac{1}{2} V^{ph} (I^{ph})^* \leftarrow \text{conjugate}$$

$$(Since S = \frac{1}{2} |V^{ph}| e^{j\Delta V^{ph}} \cdot (|I^{ph}| e^{j\Delta I^{ph}})^* = V_{RMS} I_{RMS} e^{j(\Delta V^{ph} - \Delta I^{ph})} = V_{RMS} I_{RMS} e^{j\theta_L})$$

$$③ S = I_{RMS}^2 Z_L$$

Use this one because it's easy.


$$(Since S = I_{RMS} I_{RMS} Z_L = I_{RMS} I_{RMS} |Z_L| e^{j\theta_L} = I_{RMS} V_{RMS} e^{j\theta_L})$$

$$|Z_{Load}| = \frac{|V_{Load}^{ph}|}{|I_{Load}^{ph}|}$$

$$= I_{RMS} V_{RMS} e^{j\theta_L}$$


(4) $S = \frac{V_{rms}^2}{(z_L)^*}$ - conjugate (since $S = V_{rms} \cdot I_{rms}$)
 $= V_{rms} I_{rms} e^{j\angle z_L}$ $(|z_L| e^{j\angle z_L})^*$

Ex: $\cos(3t+15^\circ)$ Find S_{Load}

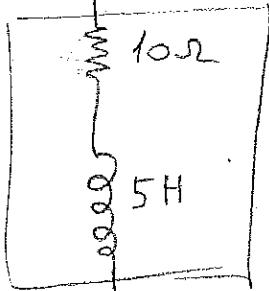

Load

Phasor!

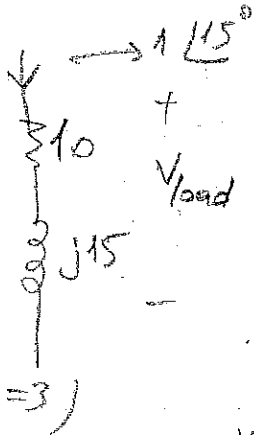

$$V_{Load}^{ph} = 1 \angle 15^\circ \cdot 5(2+j3)$$

$$= 5\sqrt{13} \angle [15^\circ + \tan^{-1} \frac{3}{2}]$$

$$I^{ph} = 1 \angle 15^\circ$$

$$z_{load} = 10 + j15$$

$$= 5\sqrt{13} \angle \tan^{-1} \frac{3}{2}$$

($\omega = 3$)


$$\textcircled{1} S = V_{rms} I_{rms} e^{j\theta_{Load}}$$

$$= \frac{5\sqrt{13}}{\sqrt{2}} \cdot \frac{1}{\sqrt{2}} \cdot e^{j \tan^{-1}(\frac{3}{2})}$$

$$= \frac{5\sqrt{13}}{2} (\cos \theta_L + j \sin \theta_L)$$

$$= \frac{5\sqrt{13}}{2} \left(\frac{2}{\sqrt{13}} + j \frac{3}{\sqrt{13}} \right)$$
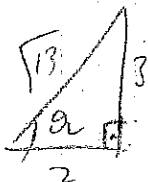
$$\textcircled{2} S = \frac{1}{2} V^{ph} (I^{ph})^*$$



$$= \frac{1}{2} 5\sqrt{13} \angle [15^\circ + \tan^{-1} \frac{3}{2}] \cdot 1 \angle -15^\circ$$

$$= \frac{5\sqrt{13}}{2} \angle \tan^{-1} \frac{3}{2} = 5 + j7.5$$

$$= \underbrace{5}_{P_{Load}} + j \underbrace{7.5}_{Q_{Load}} \text{ VA}$$

$$\textcircled{3} S = I_{rms}^2 z_L = \left(\frac{1}{\sqrt{2}}\right)^2 (10 + j15) = 5 + j7.5 \text{ (VA)}$$

$$\textcircled{4} S = \frac{V_{rms}^2}{z_L^*} = \frac{(5\sqrt{13}/\sqrt{2})^2}{5\sqrt{13} \angle -\tan^{-1}(\frac{3}{2})} = \frac{5\sqrt{13}}{2} \angle \tan^{-1}(\frac{3}{2}) = 5 + j7.5 \text{ (VA)}$$

Important Note: Before finding S , look at the phasor domain component and see whether $Q > 0$ or $Q < 0$.

Remember $Q > 0 \rightarrow$ Inductive components
 $Q < 0 \rightarrow$ Capacitive

Power Factor Definitions:



power factor = $\cos(\theta_{Load})$

Question: Can you uniquely find θ_{Load} , given that p.f. of the load is $\frac{\sqrt{2}}{2}$?

Answer: No.

$\cos(\theta_{Load}) = \frac{\sqrt{2}}{2} \rightarrow \theta_{Load} = \{45^\circ, -45^\circ\}$

For inductive loads, that is $Z_L = R + jX$ and $X > 0$ p.f. is said to be lagging ($\theta_{Load} > 0$).

For capacitive loads, that is $Z_L = R + jX$, $X < 0$, p.f. is said to be leading ($\theta_{Load} < 0$).

Q: Find θ_{Load} for p.f. $\frac{1}{\sqrt{2}}$ lagging.


A. θ_{Load} is positive, since Load is inductive.

$\theta_{Load} = 45^\circ$

$P = V_{RMS} I_{RMS} \cos(\theta_{Load})$

$|H(j\omega)| = \frac{V_{out}(j\omega)}{V_{in}(j\omega)}$

Lagging and leading concept

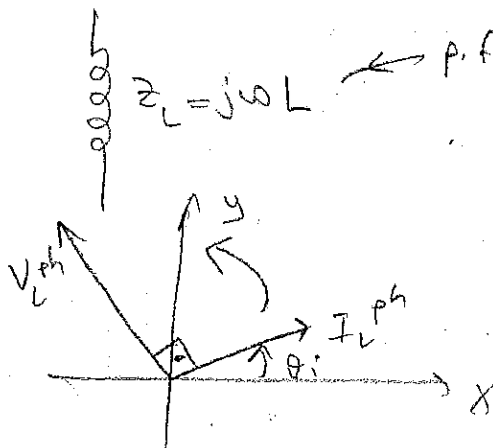

p.f. lagging $I_{ph} = I_m \angle \theta_i$

$V_{ph} = Z_L I_{ph} = \omega L \angle \theta_i + 90^\circ$


phasor diagram

Current is lagging voltage by 90° .


Impedance Triangle and Power Triangle

$S_{Load} = (I_{Load}^{RMS})^2 Z_{Load}$

$Z_L = R + jX \rightarrow S_L = (I_{Load}^{RMS})^2 [R + jX]$

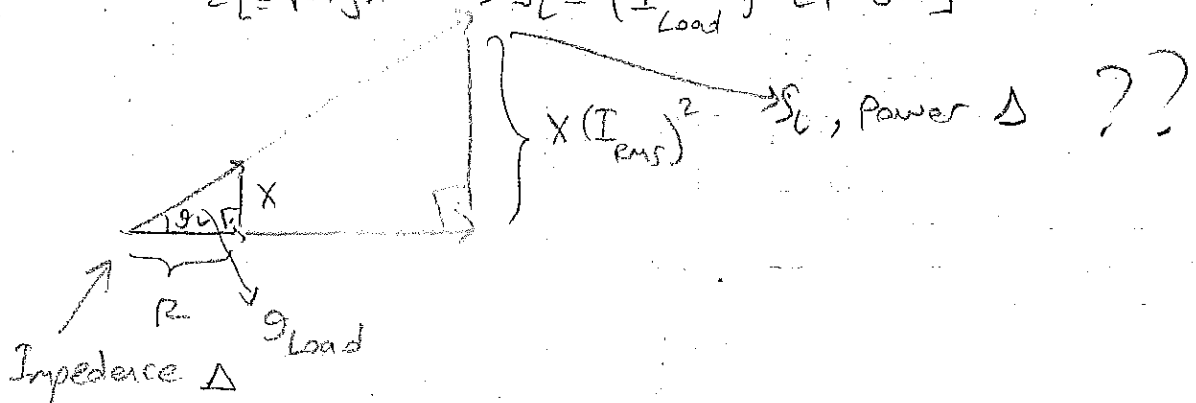

Ex 1

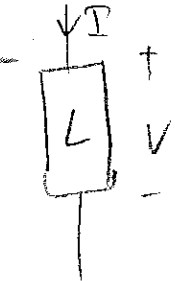

$V = 100 \text{ V (RMS)}$



$P = 5 \text{ kW}$

$\text{p.f.} = 0.8 \text{ lagging}$

a) Find VAR of Load.

b) Find Apparent Power.

lagging info \rightarrow inductive load

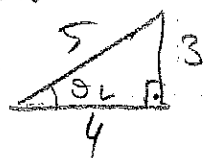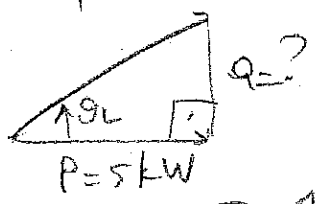

$Q > 0$

$Q = (5000) \cdot \tan(\theta_L) = 3750 \text{ VAR's}$

b) Apparent Power $\triangleq V_{\text{RMS}} I_{\text{RMS}} \triangleq |S|$

$S = P + jQ$


$= 5000 + j3750$

Since

$S = V_{\text{RMS}} I_{\text{RMS}} e^{j\theta_L}$

Apparent power $= \sqrt{5000^2 + 3750^2} = \frac{5000}{\cos(\theta_L)} = \frac{5000}{4/5} = 6250$

Superposition in AC Power

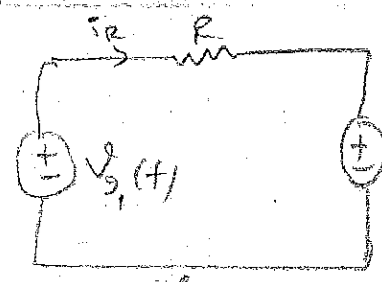

$V_{g1} = V_1 \cos(\omega_1 t + \theta_1) \text{ Volts}$

$V_{g2} = V_2 \cos(\omega_2 t + \theta_2) \text{ Volts}$

$i_R(t) = \frac{V_{g1}}{R} - \frac{V_{g2}}{R} = \frac{1}{R} (V_1 \cos(\omega_1 t + \theta_1) - V_2 \cos(\omega_2 t + \theta_2)) \text{ A}$

$\langle P_R(t) \rangle = \langle P(i_R^2(t)) \rangle = R \langle i_R^2(t) \rangle = R \lim_{T \rightarrow \infty} \frac{1}{T} \int_{-T/2}^{T/2} i_R^2(t) dt$

$\lim_{T \rightarrow \infty} \frac{1}{T} \int_{-T/2}^{T/2} \frac{1}{R} [V_1^2 \cos^2(\omega_1 t + \theta_1) - 2V_1 V_2 \cos(\omega_1 t + \theta_1) \cos(\omega_2 t + \theta_2) + V_2^2 \cos^2(\omega_2 t + \theta_2)] dt = P_{AV}$

$= \frac{1}{R} \left(\lim_{T \rightarrow \infty} \frac{1}{T} \int_{-T/2}^{T/2} V_1^2 \cos^2(\omega_1 t + \theta_1) dt \right) + \frac{1}{R} \left(\lim_{T \rightarrow \infty} \frac{1}{T} \int_{-T/2}^{T/2} V_2^2 \cos^2(\omega_2 t + \theta_2) dt \right)$

$- \frac{2}{R} \left(\lim_{T \rightarrow \infty} \frac{1}{T} \int_{-T/2}^{T/2} V_1 V_2 \cos(\omega_1 t + \theta_1) \cos(\omega_2 t + \theta_2) dt \right)$

$= \frac{(V_{g1}^{\text{RMS}})^2}{2} + \frac{(V_{g2}^{\text{RMS}})^2}{2} - \frac{2}{R} (\text{Bracket}) (V_{g2}^{\text{RMS}})^2$

Bracket = 0 if $\omega_1 \neq \omega_2$

$\frac{\cos((\omega_1 + \omega_2)t + \theta_1 + \theta_2) + \cos((\omega_1 - \omega_2)t + (\theta_1 - \theta_2))}{2}$

Note: (Bracket) = 0 if $\omega_1 \neq \omega_2$ but

but (Bracket) $\neq 0$ if $\omega_1 = \omega_2$

$$\hookrightarrow (\text{Bracket}) = \frac{\cos(\theta_1 - \theta_2)}{2} V_1 V_2$$

Conclusion

If we have two sources with different frequencies, average power dissipated over a component is

$$P_{AVG} = P_{AVG}^{\text{source } \textcircled{1}} + P_{AVG}^{\text{source } \textcircled{2}}$$


↑
↑

Avg. Power consumption due to source $\textcircled{1}$
to source $\textcircled{2}$

So power can be superposed only if the sources have different frequencies!!!

A.C. Power Analysis (cont'd)

EX:

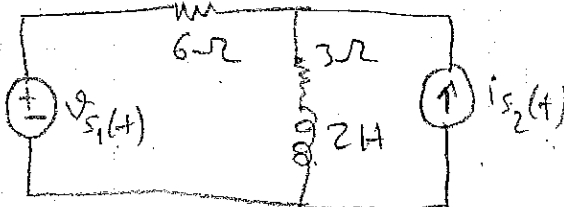


$$v_{s_1}(t) = 6 \cos(3t) \text{ Volts}$$

$$i_{s_2}(t) = 2 \cos(4t + 30^\circ) \text{ A}$$

Find average power consumed by 3 ohm resistor.

$$P_{AVG} = P_{AVG}^{\text{source with freq } \omega_1} + P_{AVG}^{\text{source with freq } \omega_2} \quad \text{provided that } \omega_1 \neq \omega_2$$

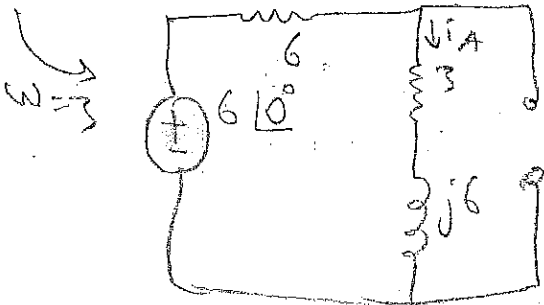
Superposition in A.C. s.s. power calculations (only valid when sources have different frequencies)



$$\rightarrow i_A = \frac{2}{6 + j6} = \frac{2(3 - 3j)}{13} = \frac{2}{13} \sqrt{13} \angle -\tan^{-1} \frac{2}{3}$$

$$\rightarrow i_A^{ss}(t) = \frac{2}{\sqrt{13}} \cos(3t - \tan^{-1} \frac{2}{3}) \text{ A}$$
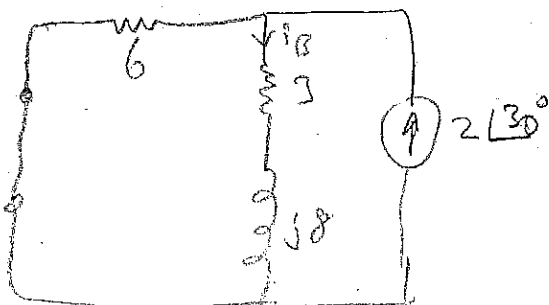
$$\rightarrow P_{3\Omega}^{RMS} = \left(\frac{2}{13} \right)^2 \cdot 3 = \frac{6}{13} \text{ watts}$$



$$\rightarrow i_B = 2 \angle 30^\circ \cdot \frac{6}{9 + j8} = \frac{12 \angle 30^\circ}{\sqrt{145} \angle \tan^{-1} \frac{8}{9}}$$


$$\rightarrow i_B^{ss}(t) = \frac{12}{\sqrt{145}} \cos(4t + 30^\circ - \tan^{-1} \frac{8}{9})$$

$$P_{3\Omega} = \left(\frac{12}{\sqrt{145}} \right)^2 \cdot 3 \approx 1.5 \text{ watts}$$

$$i_{3R}(t) = \frac{1}{3}i_1(t) + \frac{1}{3}i_2(t) = \sqrt{\quad} + \sqrt{\quad} A$$

$$P_{3R} = P_{3R}^{(A)} + P_{3R}^{(B)} = \frac{6}{13} + 1.5 \approx 2 \text{ watts}$$


Ex: A silly but important example

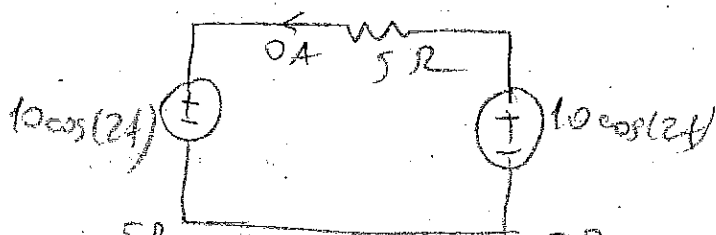

$$P_{5R}^{AVG} = ? \quad \text{Trivially } P_{5R}^{AVG} = 0, \text{ since } i_{5R}(t) = 0 \quad \forall t$$

→ You cannot apply superposition of A.C. powers when sources have the same frequency.

Maximum Power Transfer

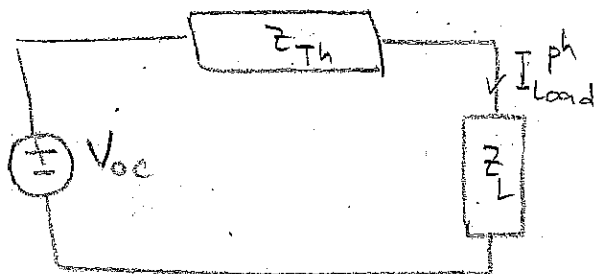

V_{oc} and Z_{Th} is fixed (we're not allowed to set their values) and we would like to adjust Z_L s.t. power delivered to Z_L is maximized.

$$I_{Load}^{ph} = \frac{V_{oc}^{ph}}{Z_{Th} + Z_L} = \frac{V_{oc}^{ph}}{(R_{Th} + R_L) + j(X_{Th} + X_L)}$$

$$R_{Th} + jX_{Th}$$

$$R_L + jX_L$$

$$P_{AVG}^{Load} = \left(\frac{|I_{Load}^{ph}|}{\sqrt{2}} \right)^2 R_L = \frac{|V_{oc}^{ph}|^2}{2} \frac{R_L}{(R_{Th} + R_L)^2 + (X_{Th} + X_L)^2}$$

Q: Maximize $P_{AVG}^{Load}(R_L, X_L)$.

$$A. \quad \frac{\partial P_{AVG}^{Load}}{\partial R_L} = 0 \quad \Bigg| \quad \frac{\partial P_{AVG}^{Load}}{\partial X_L} = 0$$

$$X_L = -X_{Th}$$


$$R_L = R_{Th}$$

$$\rightarrow \boxed{Z_L = R_{Th} - jX_{Th} = (Z_{Th})^*}$$

optimum impedance for maximum power transfer


\uparrow
 $P_{AVG}^{Load}(R_L, X_L)$

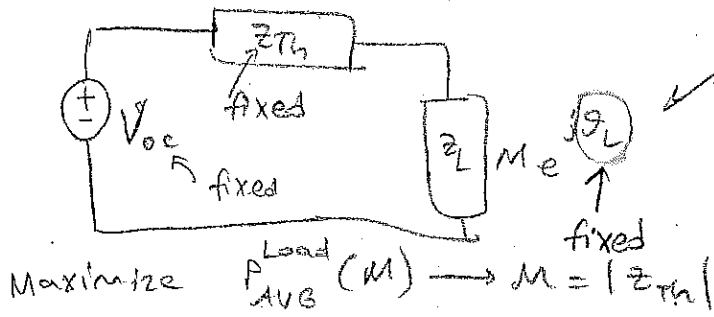Some other maximum power transfer condition.



You can only change M but not the angle of the load.

Ex:

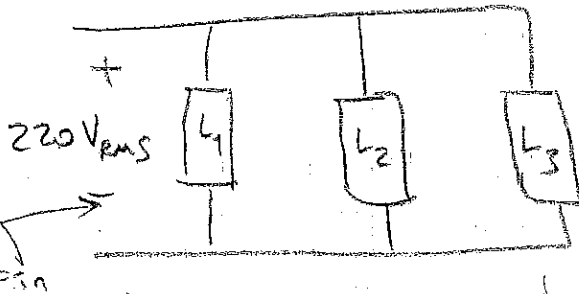

$L_1: 16 \text{ kW}, 18 \text{ kVAR}$

$L_2: 10 \text{ kVA at } 0.6, \text{ p.f. leading}$

$L_3: 8 \text{ kW at unity p.f.}$

a) Find p.f. at the source side.

b) Find apparent power at the source side.


c) Find the impedance seen by the source.

$$S_1 = 16 + j18 \text{ kVA}$$

$$S_2 = 6 - j8 \text{ kVA}$$

$$S_3 = 8 \text{ kVA}$$

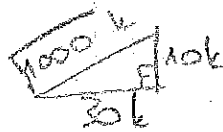a) $S_{Total} = S_1 + S_2 + S_3$
 $= 30 + j10 \text{ kVA}$



p.f. of source

$$\text{side} = \cos(\theta_{\epsilon}) = \frac{3}{110} \text{ (lagging)}$$

b) Apparent Power = $(220 \text{ V}_{RMS}) I_{RMS} = |S_{Total}|$
 at source side $= 10\sqrt{10} \text{ kVA}$

c) $S_{total} = (I_{RMS})^2 Z_{in}$



$$I_{RMS} = \frac{|S_{total}|}{220 \text{ V}_{RMS}} = \frac{10\sqrt{10} \times 10^3}{220} = \frac{10^3 \sqrt{10}}{22}$$

$$Z_{in} = \frac{S_{total}}{(I_{RMS})^2}$$

$$= \frac{10 \cdot 10^6}{(22)^2} = (30 + j10) \cdot 10^3$$

Ex 1 A mill consumes 100 kW, 220 V (RMS) at p.f. 0.85, lagging.

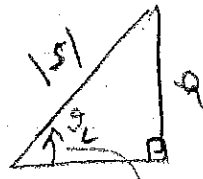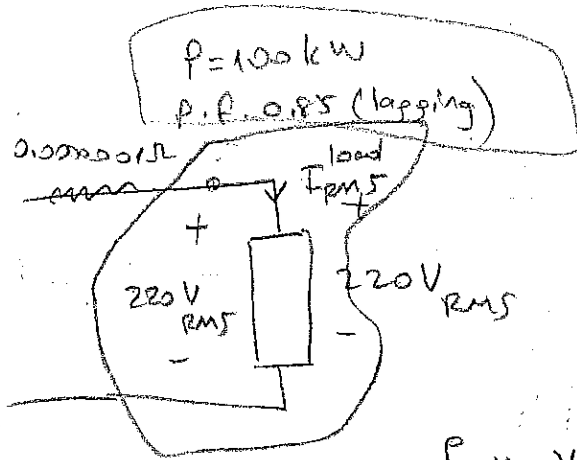- Find RMS current supplied by 220 V source to the mill.
- Find the current in RMS, if p.f. were 0.95 lagging.



$$\cos(\theta_L) = \text{p.f.} = 0.85$$

$$\begin{aligned} \text{a) } S_{\text{Load}} &= 100 + j100 \tan(\cos^{-1}(0.85)) \text{ kVA} \\ &= V_{\text{RMS}}^{\text{Load}} I_{\text{RMS}}^{\text{Load}} (\cos \theta_L + j \sin \theta_L) \end{aligned}$$


$$P_{\text{mill}} = V_{\text{RMS}}^{\text{Load}} I_{\text{RMS}}^{\text{Load}} \cos(\theta_L)$$

$$I_{\text{RMS}}^{\text{Load}} = \frac{P_{\text{mill}}}{V_{\text{RMS}}^{\text{Load}} \cos(\theta_L)} = 534.8 \text{ A}$$


100 kW
220 V RMS
0.85

$$\text{b) } I_{\text{RMS}}^{\text{Load}} = \frac{100 \text{ kW}}{220 \text{ V}_{\text{RMS}} \cdot (0.95)} = 478 \text{ A}$$

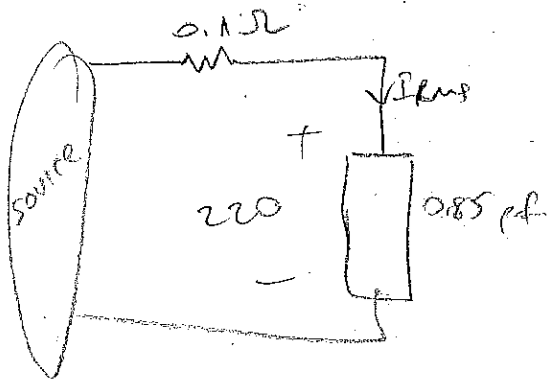- If there is a line (feeder) connecting load to the source and $R_{\text{line}} = 0.1 \Omega$, find the power loss over the line for both p.f. conditions


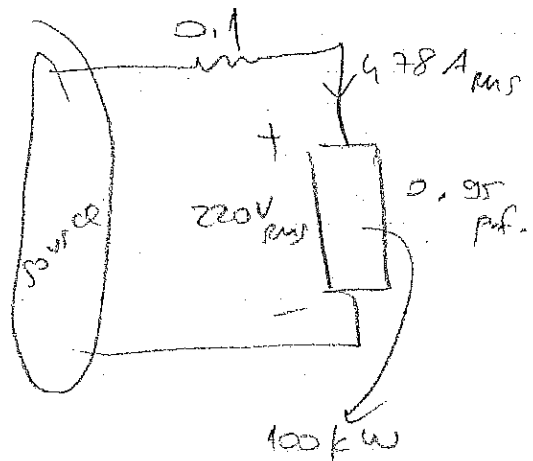
$$P = (I_{\text{RMS}})^2 \cdot 0.1 = 28.6 \text{ kW}$$



$$P_{\text{Line}} = (I_{\text{RMS}})^2 \cdot 0.1 = 22.9 \text{ kW}$$

↑
478

d) Define efficiency as $\frac{\text{Real Power delivered to the load (Watt)}}{\text{Real Power supplied by the source}}$ $\frac{W_{out}}{W_{in}}$



Find efficiency for both cases.

i) p.f. 0.85 $P_{load} = 100 \text{ kW}$
 $P_{supplied} = P_{load} + P_{line} = 128.6 \text{ kW}$
 $\eta = \frac{100 \text{ kWatt}}{128.6 \text{ kWatt}} \approx 77\%$


p.f. 0.95 $P_{load} = 100 \text{ kW}$
 $P_{supplied} = 100 + 22.9 \text{ kW} \rightarrow \eta = \frac{100}{122.9} \approx 82\%$

Almost always asked in exams!!!

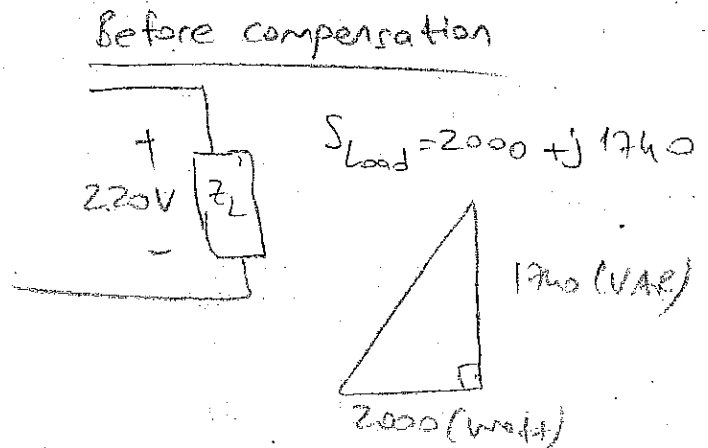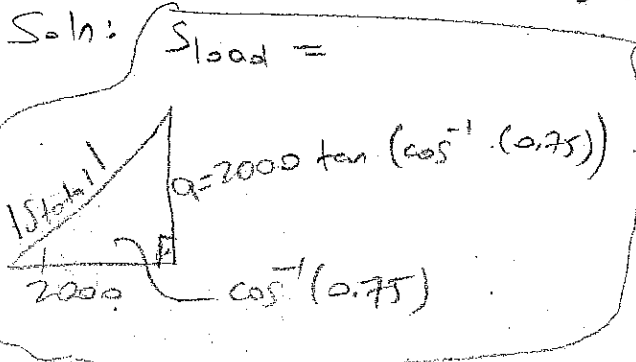
Ex: Load requires 2 kW at 0.75 p.f. lagging at 220 V rms. Calculate the reactive power supplied by the compensating capacitor to make p.f. 0.9 lagging. Find the impedance and the capacitance in Farads. (Assume 220 V rms, $f = 50 \text{ Hz}$)



After compensation:

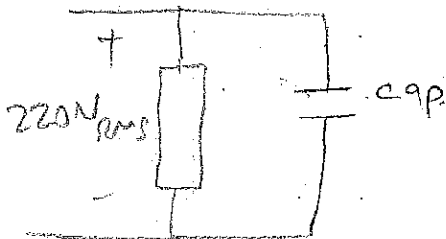

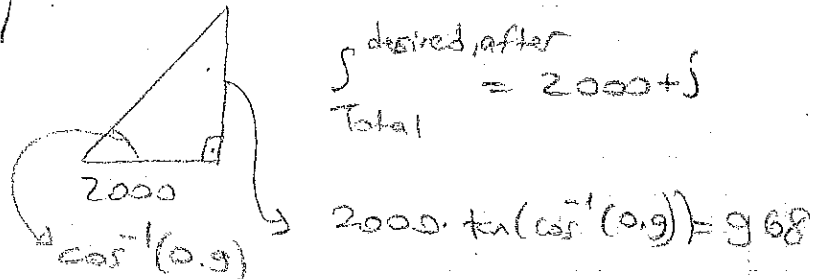$S_{cap} = -jX$
 $S_{Load} \text{ After} = 2000 + j(1740 - X)$



$S_{desired, after} = 2000 + j$
 Total

$S_{cap} = \frac{(V_{rms})^2}{Z_{cap}^*}$

$1740 - X = 968 \rightarrow X = 772$

$S_{cap} = -j772$

$Q_{cap} = -772 \text{ VARs}$

$\rightarrow -j772 = \frac{(220)^2}{Z_{cap}^*}$

$Z_{cap} = -j \frac{(220)^2}{772}$


$Z_{cap} = -j61.07 \Omega$

$Z_{cap} = \frac{1}{j\omega C} = -j61.07$

$\frac{1}{\omega C} = 61.07$

$\frac{1}{2\pi \times 50 \times C} = 61.07$
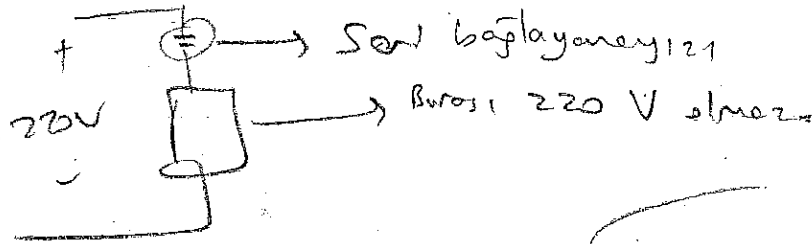
$$C = \frac{1}{100\pi \times 61.07} \quad F \approx 52 \mu F$$




★ check the example on the site.


Ex: Load consumer 10kW at 0.8 p.f. lagging.

P.59 The generator 2 supplies 5kW at 0.6 p.f. lagging.

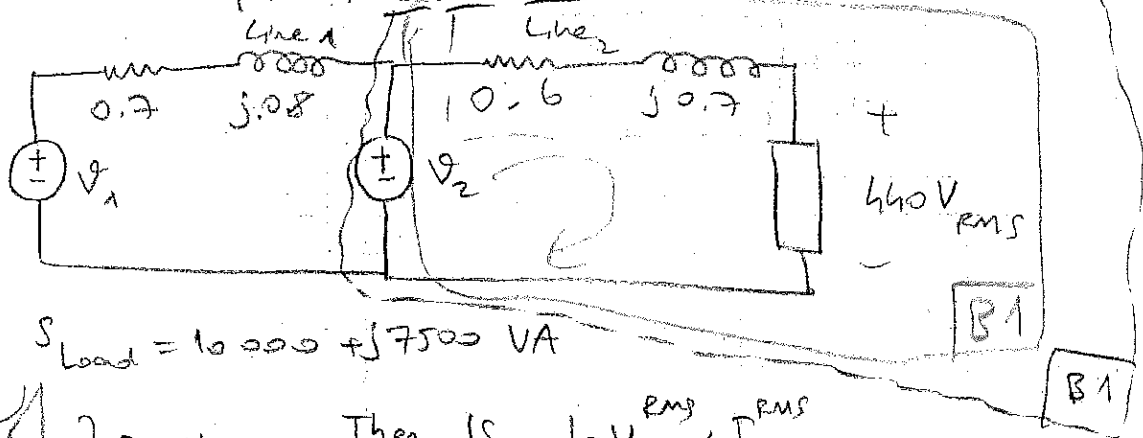Find V_1 and V_2 (in RMS), the apparent power of generator 1 and p.f. of generator 1.



A: $S_{Load} = 10000 + j7500 \text{ VA}$

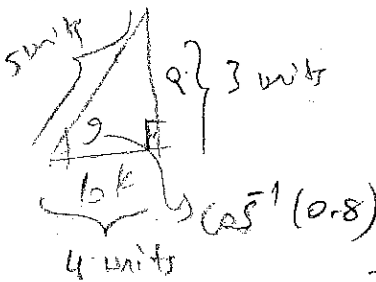


Then $|S_{Load}| = V_{Load} \cdot I_{Load}^{RMS}$
 $\rightarrow I_{Load}^{RMS} = \frac{10000/0.8}{440 (V_{RMS})} = 28.4 (A_{RMS})$

$S_{Line 2} = I_{Line, RMS}^2 \cdot Z_{Line 2} = 484 + j565$
 $(28.4)^2 \cdot 0.6 + j0.7$

$|S_{Line 2}| = V_{Line 2} \cdot I_{Line 2}^{RMS} \rightarrow V_{Line 2}^{RMS} = \frac{|484 + j565|}{28.4} = 2600 V_{RMS}$

Let's find V_2 in RMS.

Remember $V_2^{ph} = V_{Line 2}^{ph} + V_{Load}^{ph}$

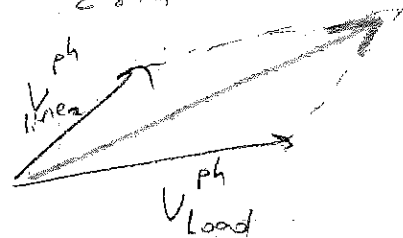

Method 1:

$S_{Load} = \frac{1}{2} V_{Load}^{ph} \cdot (I_{Load}^{ph})^*$
 $10000 + j7500 \rightarrow 440 \angle 16^\circ$
 $\rightarrow I_{Load}^{ph} = \dots$
 Find Z_{Load}


Reference Load phase angle

$V_2 = (Z_{Load} + Z_{Line 2}) I_{Load}^{ph}$

Method 2 (Recommended)

$$S_{B1} = S_{Line2} + S_{Load} = 10484 + j8065$$

$$|S_{B1}| = V_{B1}^{RMS} \cdot I_{B1}^{RMS} \rightarrow \frac{|10484 + j8065|}{28.4} = V_{B1}^{RMS} = 466 \text{ V}_{RMS}$$

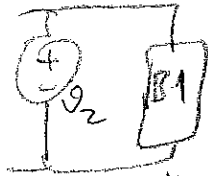


$$S_{\text{Supplied power } 2} = 5000 + j6666 \text{ VA}$$

2nd generator supplied power

$$S_{B2} = S_{B1} - S_{\text{Supplied } 2} = 5484 + j1400$$

$$|S_{B2}| = V_{B2}^{RMS} \cdot I_{B2}^{RMS} \rightarrow I_{B2}^{RMS} = \frac{|5484 + j1400|}{466} = 12.14 \text{ A}_{RMS}$$

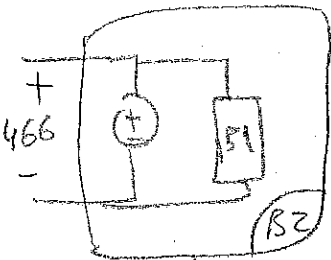

$$S_1^{\text{supplied}} = S_{Line1} + S_{B2} = 5587 + j1516$$

generator 1 supplied


$$V_1^{RMS} = \frac{|S_1|}{12.14 \text{ A}_{RMS}} = 477 \text{ V}_{RMS}$$

$$\text{Apparent power of Gen. 1} = V_1^{RMS} I_1^{RMS} = |S_1| = 5794 \text{ VA}$$

$$\text{p.f. of Gen. 1} \Rightarrow \frac{5587}{5794} \text{ lagging}$$


$$S_{Load} = \frac{1}{2} V_{Load}^{ph} (I_{Load}^{ph})^*$$

$\cos(\theta)$

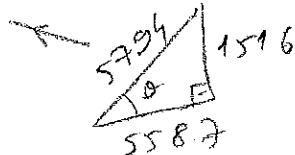

we can use this if we need angle

3 Phase Systems

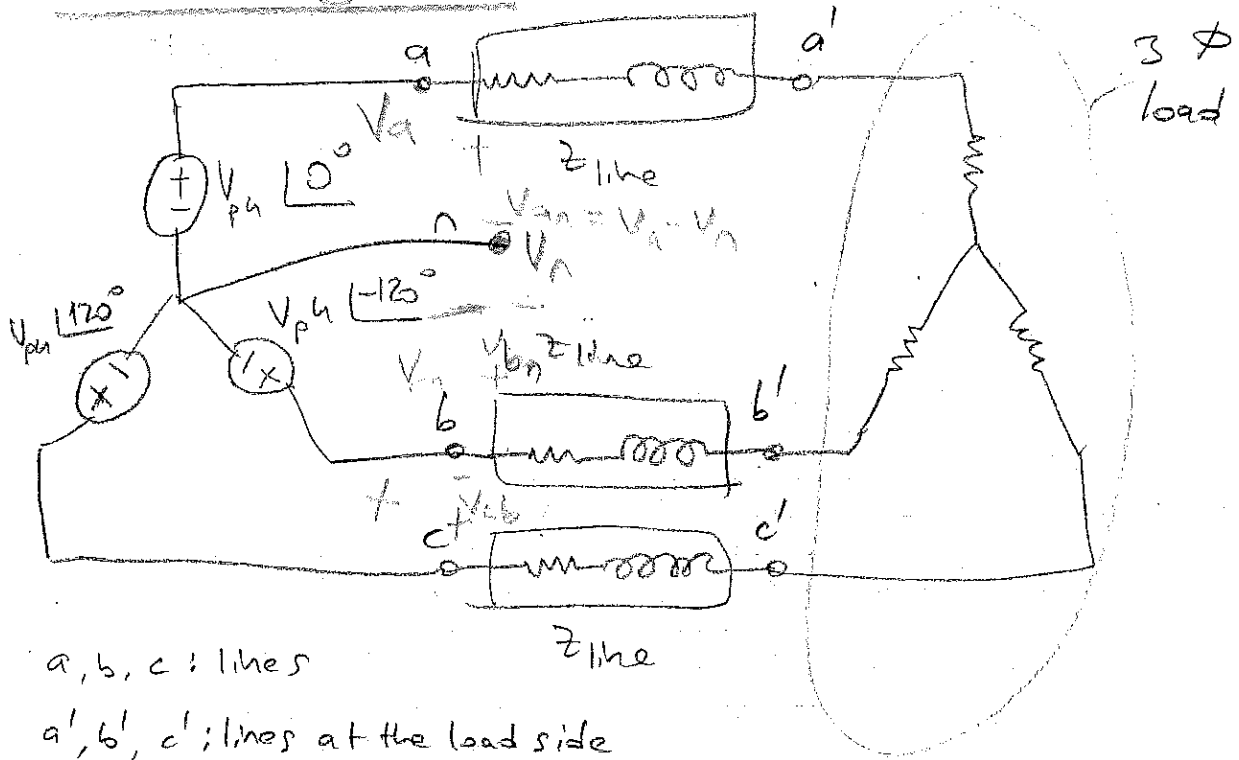

a, b, c : lines

Z_line

a', b', c' : lines at the load side

a, b, c : 3 lines powering the system

n : neutral line (common line)

$$\begin{cases} V_{an} = V_a - V_n = V_{ph} \angle 0^\circ \\ V_{bn} = V_b - V_n = V_{ph} \angle -120^\circ \\ V_{cn} = V_c - V_n = V_{ph} \angle 120^\circ \end{cases}$$


phase

voltages

line-to-line
voltages

$$\begin{cases} V_{ab} = V_a - V_b = V_{an} - V_{bn} \\ V_{ac} = V_a - V_c = V_{an} - V_{cn} \\ V_{cb} = V_c - V_b = V_{cn} - V_{bn} \end{cases}$$

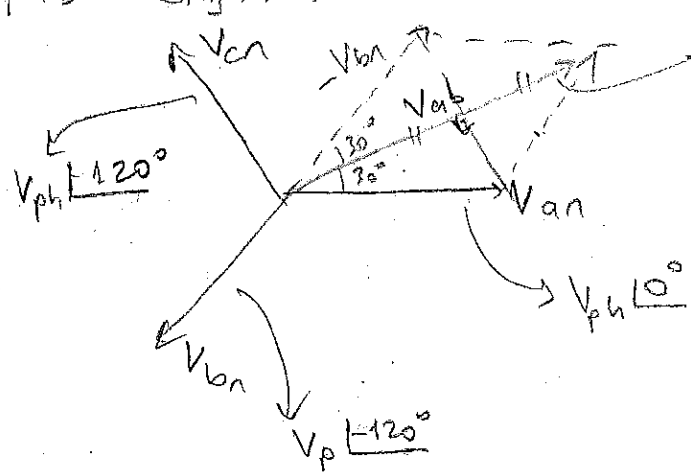Let's find the -to- line voltages V_{ab}, V_{ac}, V_{cb} using phasor diagram.





$$\begin{aligned} V_{ab} &= \sqrt{3} V_{ph} \angle 30^\circ \\ V_{ab} &= V_{an} - V_{bn} \\ &= (V_a - V_n) - (V_b - V_n) \\ &= V_a - V_b \\ V_{ab} &= V_{an} - V_{bn} \\ &= V_{an} + V_{nb} \end{aligned}$$


$$\begin{aligned}
 V_{ab} &= V_{an} - V_{bn} = V_{ph} \angle 0^\circ + (-1) V_{ph} \angle -120^\circ \rightarrow 1 \angle 180^\circ \\
 &= V_{ph} \angle 0^\circ + V_{ph} \angle 60^\circ = V_{ph} + V_{ph} \left(\frac{1}{2} + j \frac{\sqrt{3}}{2} \right) \\
 &= V_{ph} \left(\frac{3}{2} + j \frac{\sqrt{3}}{2} \right) \\
 &= \sqrt{3} V_{ph} \left(\frac{\sqrt{3}}{2} + j \frac{1}{2} \right) \\
 V_{ab} &= \sqrt{3} V_{ph} \angle 30^\circ
 \end{aligned}$$

$$\begin{aligned}
 V_{ac} &= \sqrt{3} V_{ph} \angle -30^\circ \\
 V_{cb} &= \sqrt{3} V_{ph} \angle 90^\circ
 \end{aligned}$$


Line Currents, Phase Currents

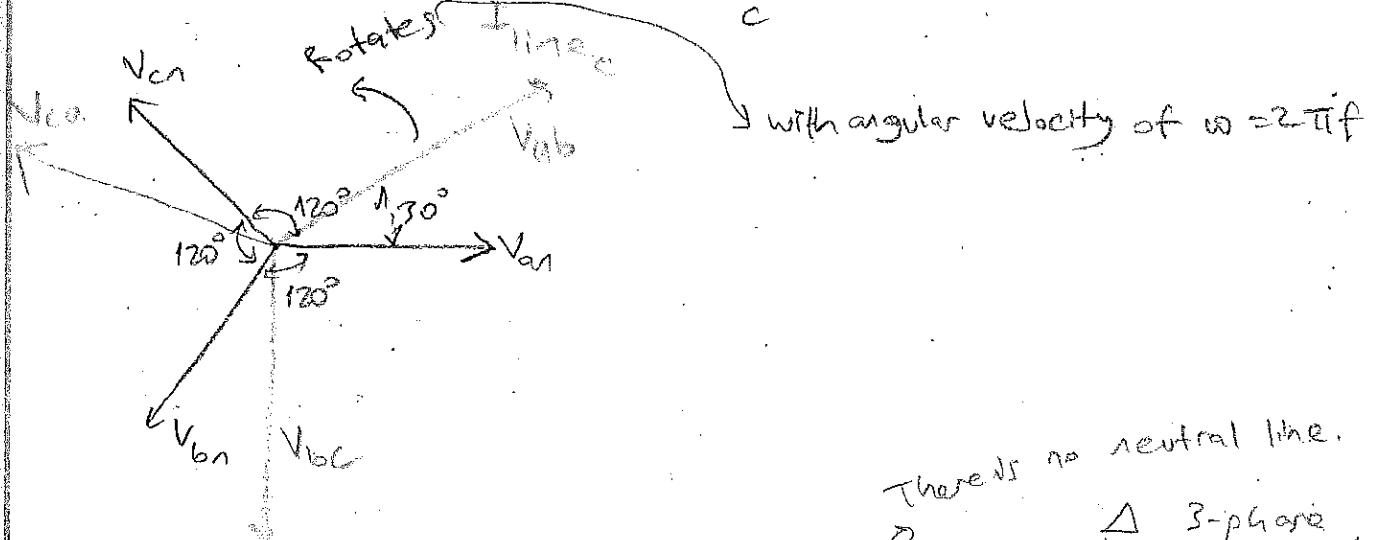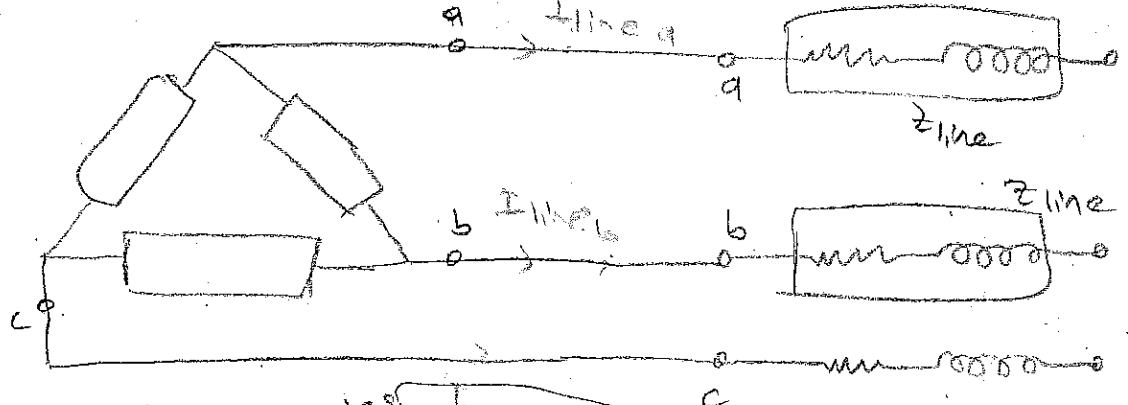


3-phase system (continued)

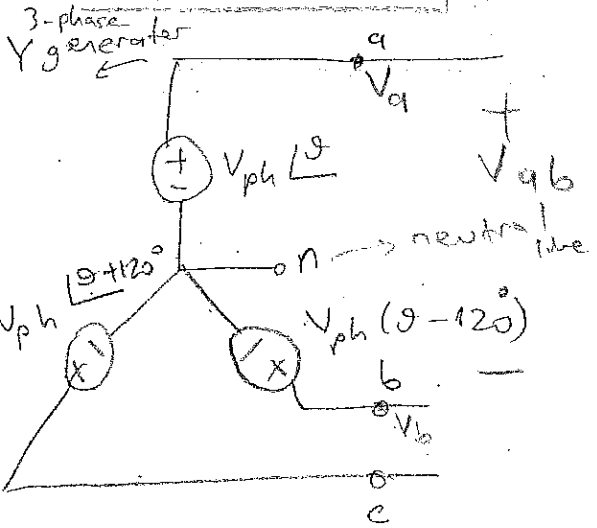

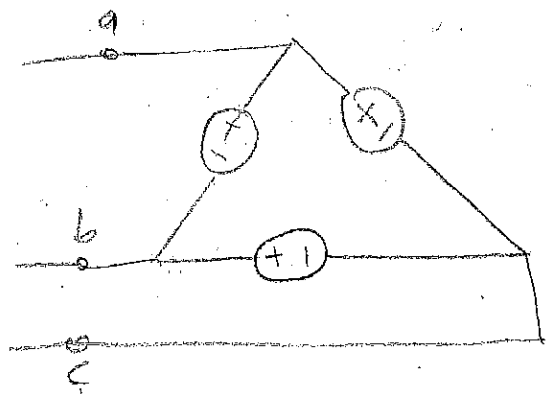There is no neutral line.
 3-phase generator




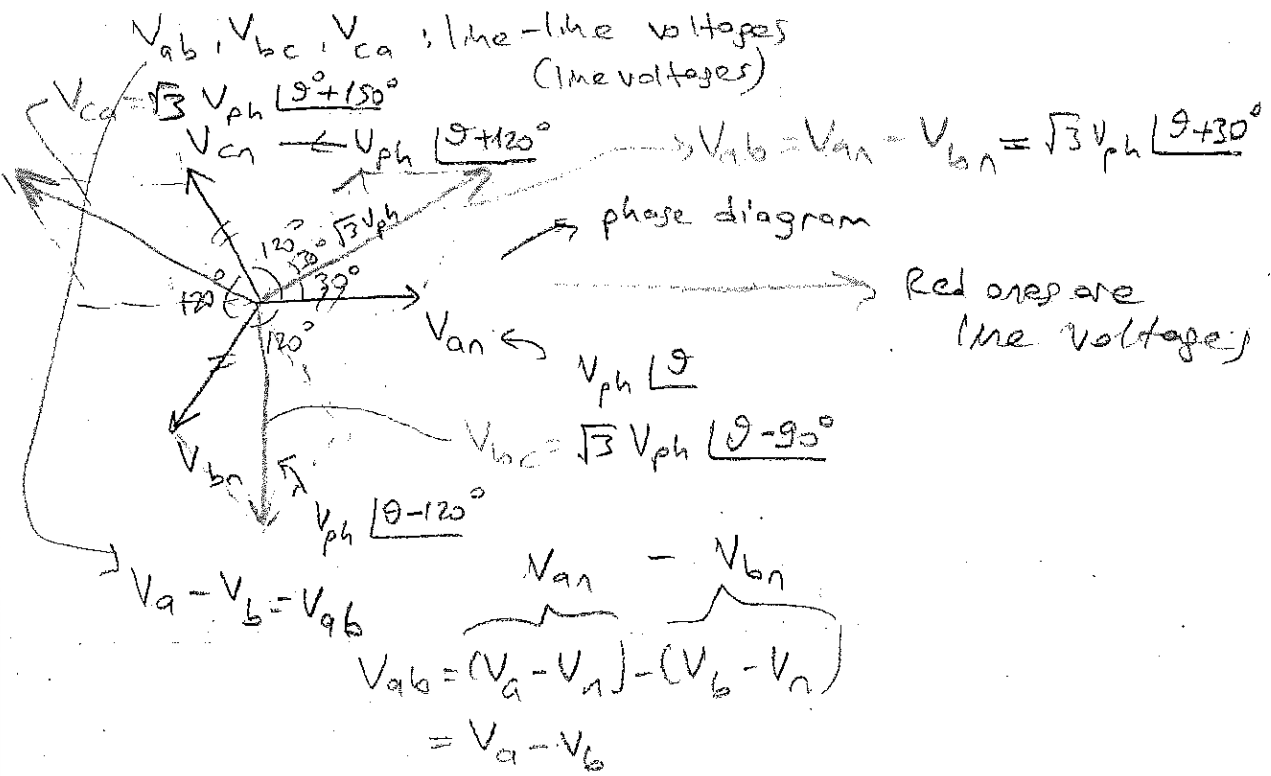a, b, c: lines
 n: neutral line
 $\{ \underbrace{V_{an}, V_{bn}, V_{cn}}_{\text{Phase voltages}} \}$
 $\{ \underbrace{V_{ph} \angle \theta, V_{ph} \angle \theta - 120^\circ, V_{ph} \angle \theta + 120^\circ} \}$



Positive Sequence

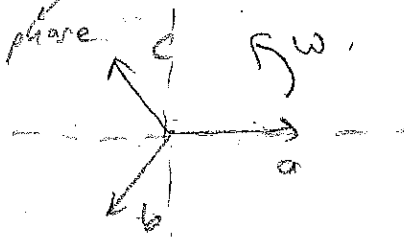
3 ϕ systems can be configured in two ways:



"a" leads "b" leads "c"

Config. 1

Positive sequence (abc sequence)

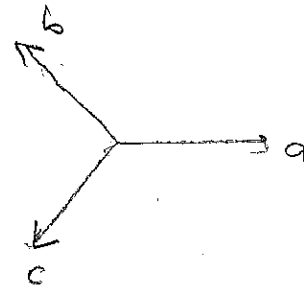

"a" leads "c" leads "b"


Config 2

Negative Sequence (acb sequence)


In EE202 we'll only use positive sequence for 3 ϕ systems.

Ex: $V_{an} = 10 \angle 45^\circ$ Volts (abc sequence)

Find V_{bc} .

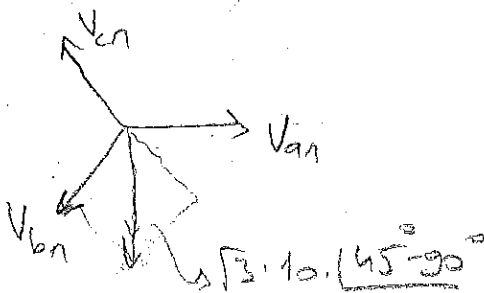

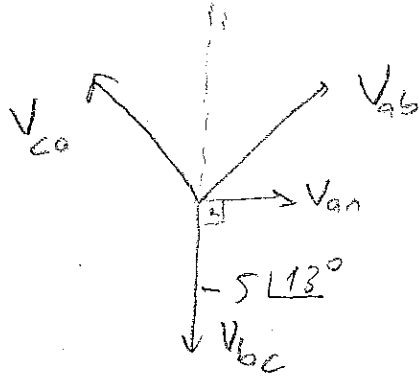
Ex: $V_{cb} = 5 \angle 13^\circ$ Volts $V_{an} = ?$



$$V_{an} = \frac{-5}{\sqrt{3}} \angle (13^\circ + 90^\circ) = \frac{5}{\sqrt{3}} \angle (13^\circ + 90^\circ - 180^\circ)$$

$$= \frac{5}{\sqrt{3}} \angle -77^\circ \text{ Volts.}$$

Line Current / Phase Current

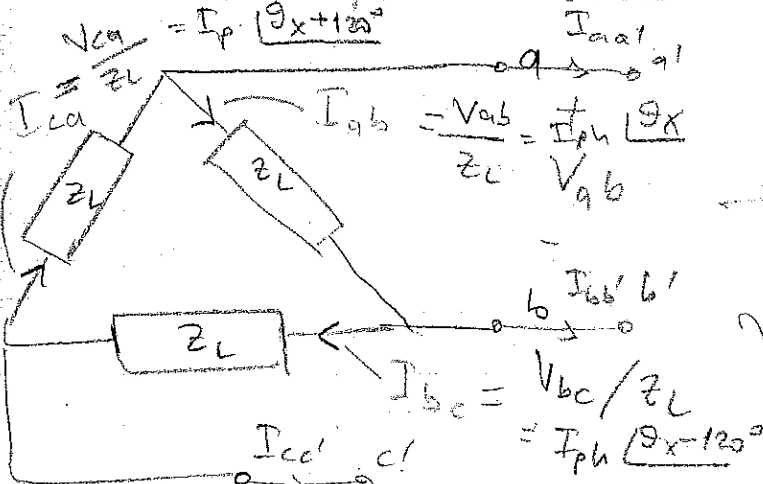

I_{ab}, I_{bc}, I_{ca} : phase currents
 $I_{aa'}, I_{bb'}, I_{cc'}$: Line current


$$I_{aa'} = ?$$

$$I_{aa'} = I_{ca} - I_{ab}$$

$$= \frac{V_{ca}}{Z_L} - \frac{V_{ab}}{Z_L}$$

$$= I_{ph} \angle (9x + 120^\circ) - I_{ph} \angle 9x$$
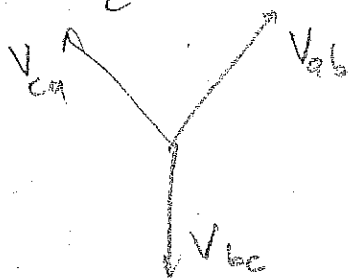
$$= \sqrt{3} I_{ph} \angle (9x + 150^\circ)$$



$$I_{bb'} = I_{ab} - I_{bc}$$


$$= I_{ph} \angle 9x - I_{ph} \angle (9x - 120^\circ)$$

$$= \sqrt{3} I_{ph} \angle (9x + 30^\circ)$$

$$I_{cc'} = \sqrt{3} I_{ph} \angle (9x - 90^\circ)$$

Note: The magnitude of line current is bigger by a power factor of $\sqrt{3}$ for a Δ connected 3ϕ Load/systems.

Y-connected Load

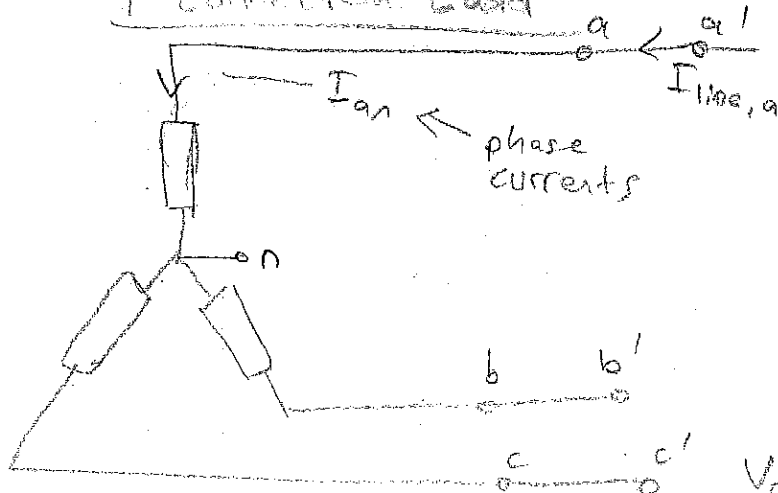


$I_{line,a} = I_{an}$
 $I_{line,b} = I_{bn}$
 $I_{line,c} = I_{cn}$

Y-connected Load phase current = Line current

V_{an}, V_{bn}, V_{cn} \leftarrow phase Load rms Voltages
 V_{ab}, V_{bc}, V_{ca} \leftarrow Line rms Voltages
 (Their angles also differ)

For a Δ connected Load:

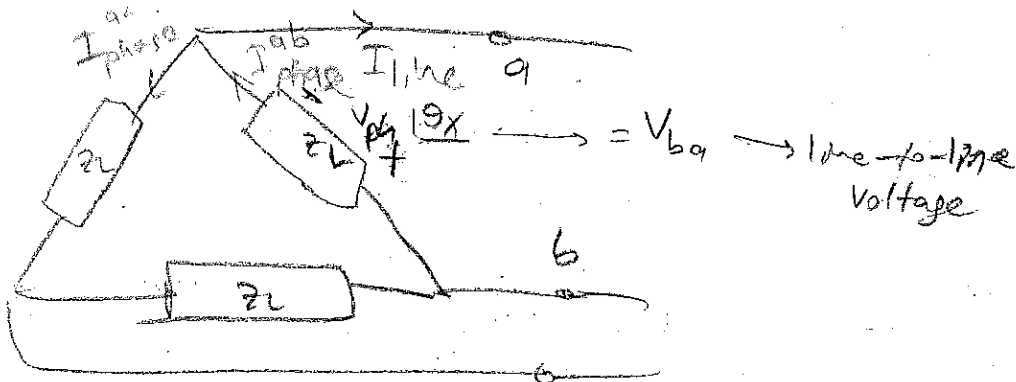
$V_{\text{phase voltage}} = V_{\text{line-line Voltage}}$
 $\sqrt{3} I_{\text{phase}} = I_{\text{line}}$



Analysis of Balanced 3 ϕ Systems

We are always using abc connected systems.


Balanced

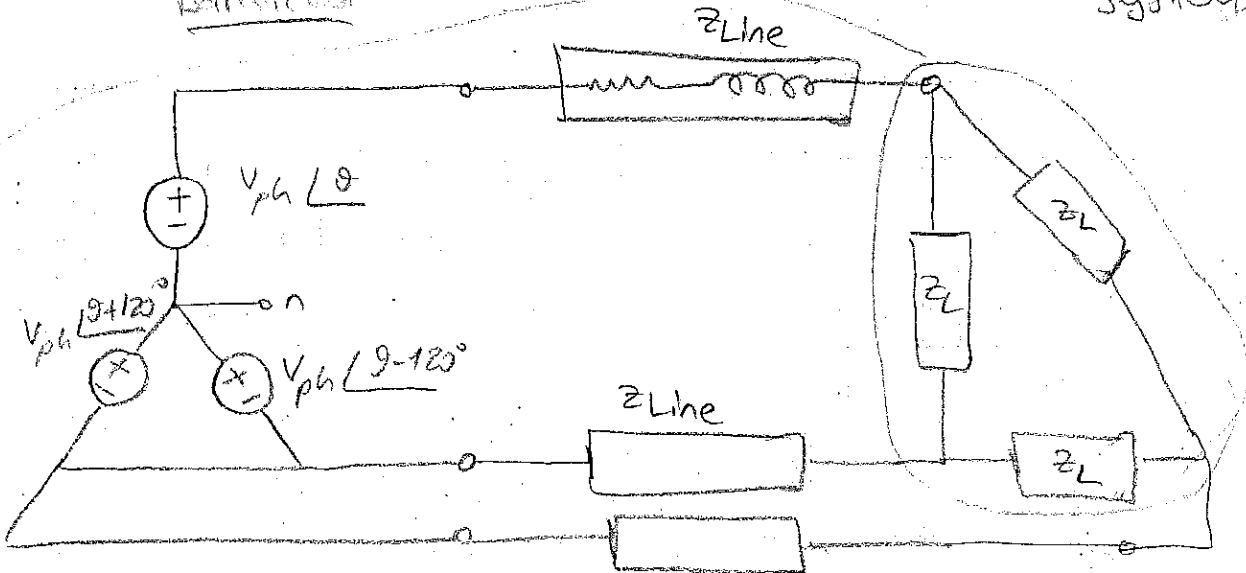

$Z_L = Z_{\text{Load}}$ \leftarrow Equivalent impedance of a 3 ϕ motor

In balanced 3 ϕ systems, the circuit in each phase is identical except the voltage source phase difference of $\pm 120^\circ$.


convert Δ to Y (first)

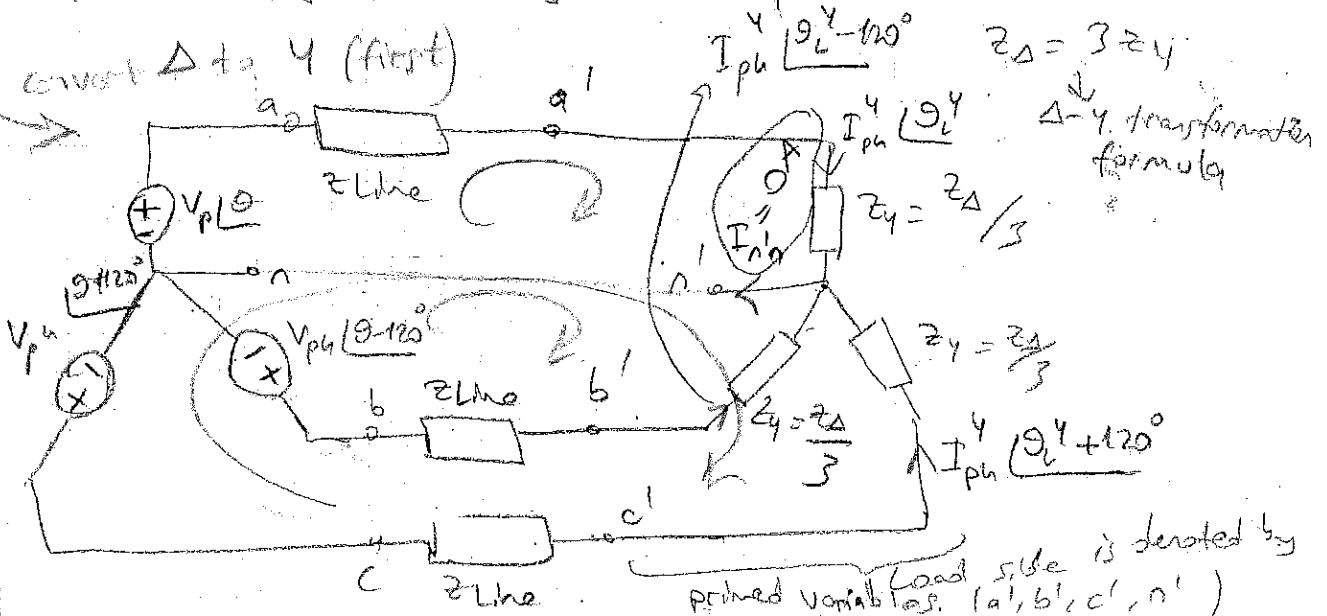

Load side is denoted by primed variables (a', b', c', n')

Single Phase Equivalent System

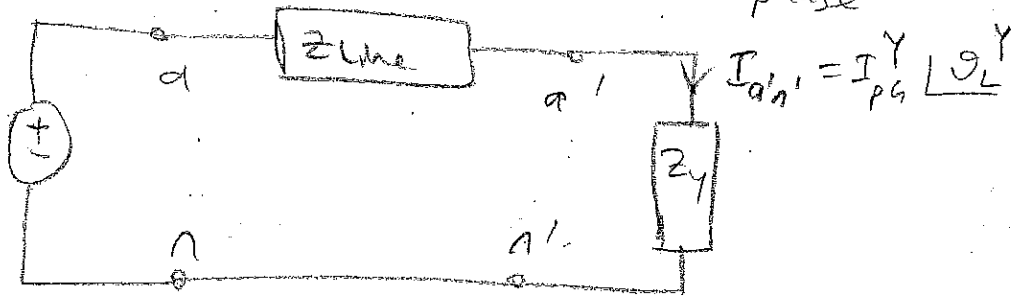We only sketch a single phase (say "a-n") phase



$$I_{a'n'} = I_{pg} \sqrt{3}$$


Note that $I_{n'} = 0$ A since we have a balanced three-phase system and currents $I_{a'n'}$ through each Y-connected load impedance are identical in RMS, but differ with $\pm 120^\circ$.

Therefore, the line from n to n' can be disconnected and totally removed for three phase balanced systems.

★ Also look at Sadiku's Textbook!!!

From these we understand it is P



Ex:

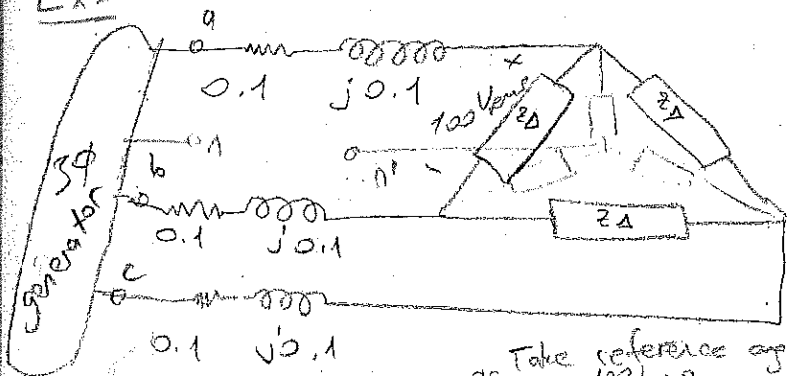

A 3 ϕ Load consumes 1200 Watts at p.f. of 0.8 lagging.
a) Find complex power generated by generator

b) Find V_{ph} (RMS) of generator
i) if generator is Δ connected
ii) " " " Y "

Soln.

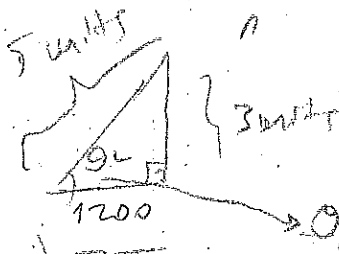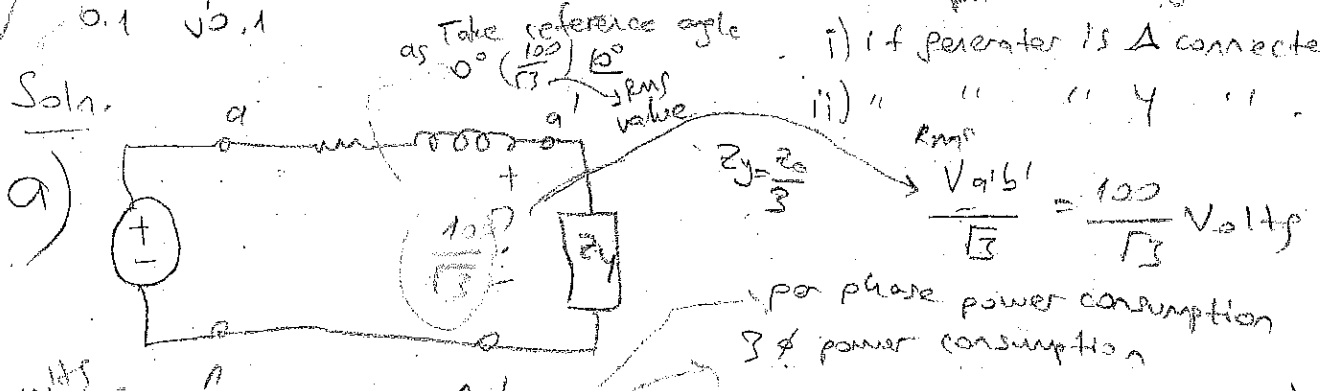

4 units

$$S_{load} = \frac{3\phi}{3} = 400 + j300 \text{ VA}$$

$$|S_{load}| = V_{load} I_{load} \Rightarrow I_{load} = 5\sqrt{3} \text{ A (rms)}$$

$$S_{line} = (I_{line}^{rms})^2 Z_{line} = (5\sqrt{3})^2 [0.1 + j0.1] = 7.5 + j7.5 \text{ VA}$$

$$Z_Y = \frac{Z_0}{3} \rightarrow \frac{V_{a'b'}}{\sqrt{3}} = \frac{100}{\sqrt{3}} \text{ Volts}$$

per phase power consumption
3 ϕ power consumption

$$S_{load}^{3\phi} = 1200 + j900 \text{ VA}$$

Total (3 ϕ) complex power

$$S_{\text{supplied}}^{\phi} = S_{\text{Load}}^{\phi} + S_{\text{Line}}^{\phi} = 407.5 + j302.5 \text{ VA}$$


$$S_{\text{supplied}}^{3\phi} = 3 S_{\text{supplied}}^{\phi} = 1222.5 + j922.5 \text{ VA}$$

b) From single phase equivalent, let's find V_x (RMS).

$$|S_{\text{supplied}}^{\phi}| = V_x^{\text{RMS}} I_{\text{line}}^{\text{RMS}} \rightarrow V_x^{\text{RMS}} = \frac{|407.5 + j302.5|}{5\sqrt{3}}$$

$$\downarrow 5\sqrt{3} \text{ Arms} \quad = 58.94 \text{ V}_{\text{RMS}}$$


$$\sqrt{(407.5)^2 + (302.5)^2}$$

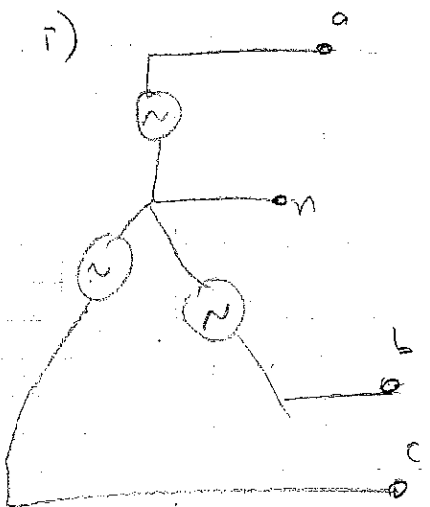

Y-Generator $V = 58.14 \text{ V}_{\text{RMS}}$

Δ -Generator $V_{\text{phase}} = \sqrt{3} V_x = 102.1 \text{ V}_{\text{RMS}}$


3 ϕ Power Calculations for Y- Δ Loads

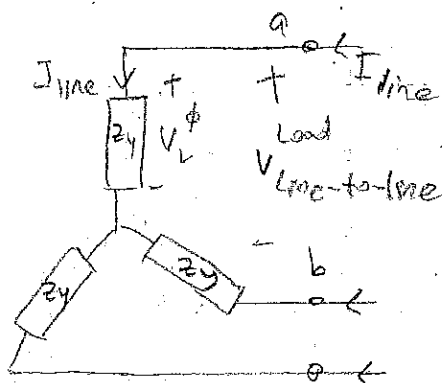

$$S_L^{3\phi} = 3 S_L^{\phi} = 3 (I_{\text{line}}^{\text{RMS}})^2 Z_Y$$

$$= 3 I_{\text{line}}^{\text{RMS}} \cdot I_{\text{line}}^{\text{RMS}} Z_Y$$
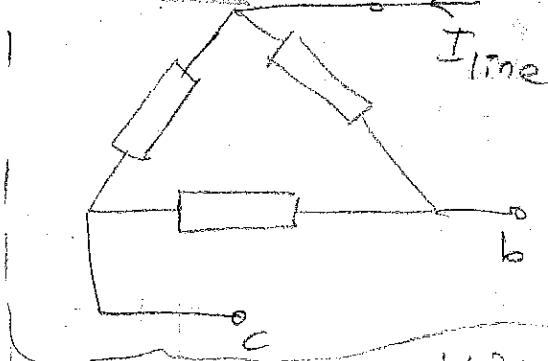
$$\downarrow \sqrt{3} I_{\text{line}}^{\text{RMS}} \cdot \sqrt{3} I_{\text{line}}^{\text{RMS}} Z_Y$$



$$= 3 I_{\text{line}}^{\text{RMS}} (I_{\text{line}}^{\text{RMS}} |Z_Y|) e^{j\Delta Z_Y}$$

$$= 3 I_{\text{line}}^{\text{RMS}} (V_{\text{Load}}^{\text{RMS}}) e^{j\Delta Z_Y}$$

$$= 3 I_{\text{line}}^{\text{RMS}} \frac{V_{\text{line-to-line}}^{\text{RMS}}}{\sqrt{3}} e^{j\Delta Z_Y}$$

$$S_L^{3\phi} = \sqrt{3} I_{\text{line}}^{\text{RMS}} V_{\text{line-to-line}}^{\text{RMS}} e^{j\Delta Z_Y}$$

For Δ connection:


$$\begin{aligned}
 S_L^{3\phi} &= 3 S_L^{\phi} = 3 (I_{Load}^{\phi, RMS})^2 Z_{\Delta} \\
 &= 3 I_{Load}^{\phi, RMS} I_{Load}^{\phi, RMS} Z_{\Delta} \leftarrow |Z_{\Delta}| e^{j\angle Z_{\Delta}} \\
 &= 3 I_{Load}^{\phi, RMS} V_{Load}^{\phi, RMS} e^{j\angle Z_{\Delta}} \\
 &= 3 I_{Load}^{\phi, RMS} V_{Load}^{\phi, RMS} e^{j\angle Z_{\Delta}} \\
 &\quad \swarrow \quad \searrow \\
 &\quad I_{Line}^{RMS} \quad V_{Line}^{RMS} \\
 \boxed{S_L^{3\phi} = \sqrt{3} I_{Line}^{RMS} V_{Line-to-Line}^{RMS} e^{j\angle Z_{\Delta}}}
 \end{aligned}$$

Note that, we have the same total 3 ϕ power formulas for both Δ and Y connected loads. That is

$$S_{Load}^{3\phi} = \sqrt{3} V_{Line-to-Line}^{Load, RMS} I_{Line}^{Load, RMS} e^{j\angle Z_L} = Q_{2L}$$

$$\begin{aligned}
 \text{Re} \{ \dots \} &\rightarrow P_{Load}^{3\phi} = \sqrt{3} V_{Line-to-Line}^{Load, RMS} I_{Line}^{Load, RMS} \cos(\theta_{2L}) \\
 \text{Im} \{ \dots \} &\rightarrow Q_{Load}^{3\phi} = \sqrt{3} V_{Line-to-Line}^{Load, RMS} I_{Line}^{Load, RMS} \sin(\theta_{2L}) \quad \text{power factor}
 \end{aligned}$$

Ex:

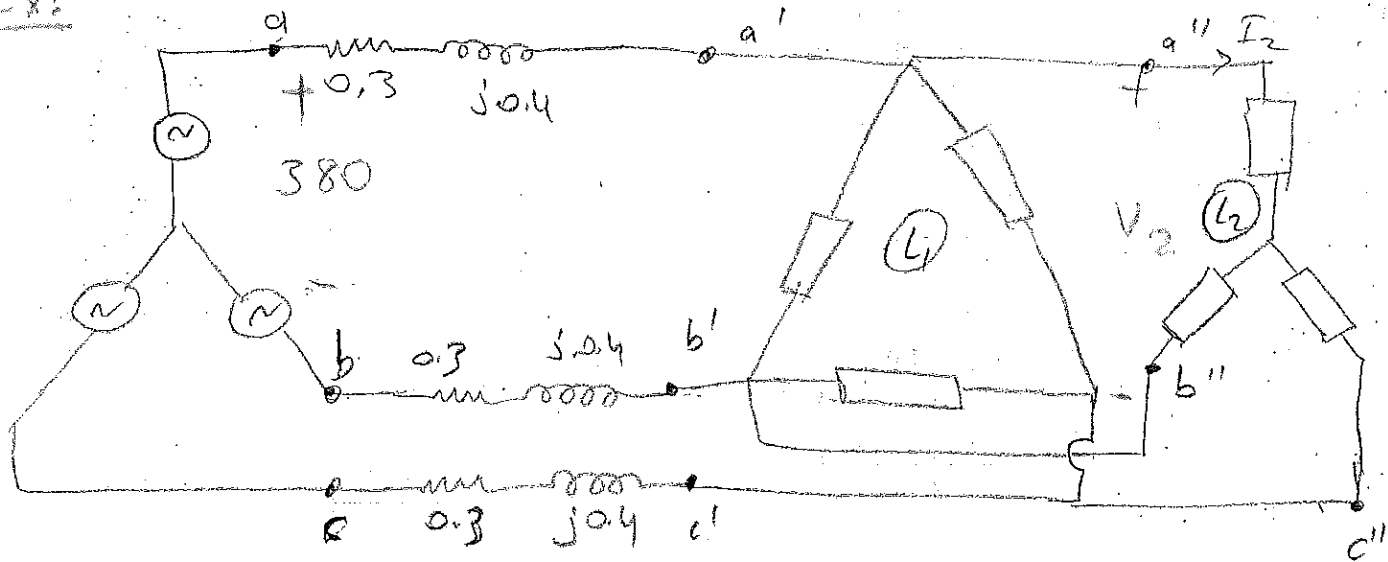


* Generator provides 380 V_{RMS} (line-to-line) at 9 kW and 9 kVAR


* L₁: 6 kW at 0.6 p.f. lagging

Find V₂, I₂ and power absorbed by L₂.

Sol. (1): (Single phase Equivalent)

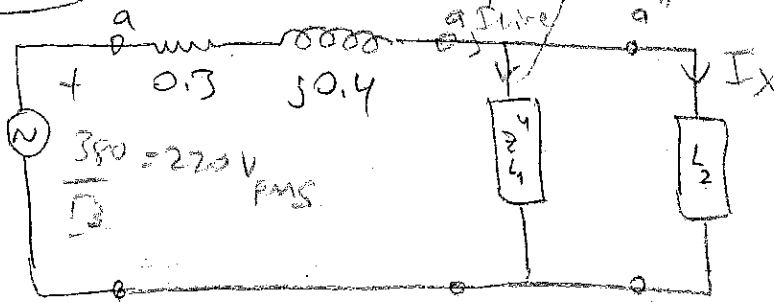

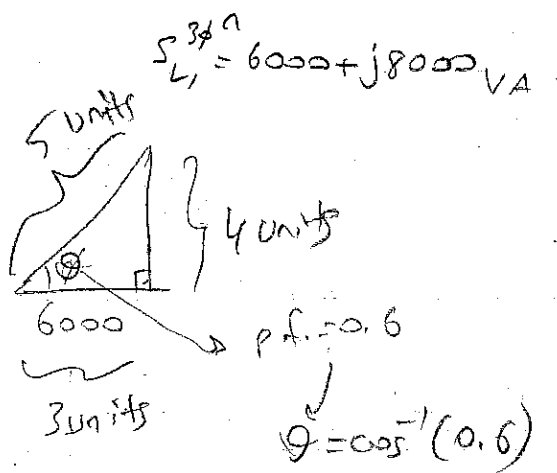★ This is not $I_{line}^{RMS} - I_x^{RMS}$!!!



$$S_{L1}^{3\phi} = 6000 + j8000 \text{ VA} \rightarrow S_{L1}^{\phi} = 2000 + j2666 \text{ VA}$$

$$S_{Source}^{\phi} = 3000 + j3000$$

$$|S_{Source}^{\phi}| = 220 V_{RMS} \cdot I_{Line}^{RMS} \rightarrow I_{Line}^{RMS} = 19.3 \text{ A}_{RMS}$$

$$3000\sqrt{2}$$

$$S_{Line}^{\phi} = (I_{Line}^{RMS})^2 Z_{Line} = (19.3)^2 (0.3 + j0.4) = 112 + j149$$

$$S_{L1+L2}^{\phi} = S_{supplied}^{\phi} - S_{Line}^{\phi} = (3000 + j3000) - (112 + j149) = 2888 + j2851$$

$$S_{L2}^{\phi} = S_{L1+L2}^{\phi} - S_{L1}^{\phi} = 888 + j187 \text{ VA}$$

$$|S_{L1+L2}^{\phi}| = V_x^{RMS} \cdot I_{Line}^{RMS} \rightarrow (2888 + j2851) = V_x^{RMS} \times (19.3)$$

$$\rightarrow V_x^{RMS} = 210.3 \text{ V}_{RMS}$$

$$|S_{L2}^{\phi}| = V_x^{RMS} \cdot I_x^{RMS}$$

$$\sqrt{888^2 + 187^2} = (210.3) I_x^{RMS}$$


$$I_x^{RMS} = 4.3 \text{ A}_{RMS}$$

Do not write KCL and KVC over RMS values.


$$V_2^{RMS} = \sqrt{3} V_x = 364 \text{ V}_{RMS}$$

$$I_2^{RMS} = I_x = 4.3 \text{ A}_{RMS}$$
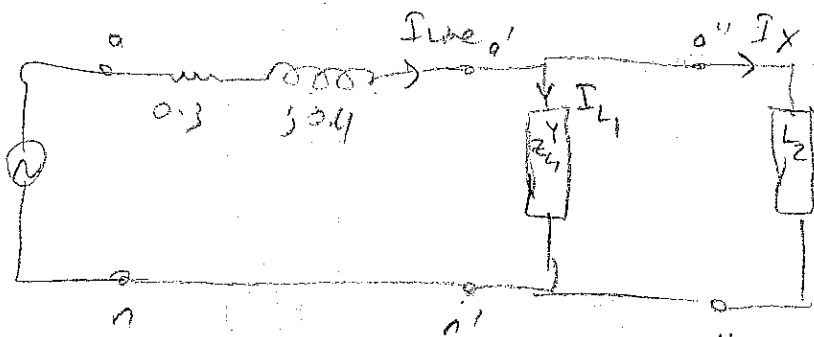
$$S_{L2}^{3\phi} = 3 S_{L2}^{\phi} = 3(888 + j187) \text{ VA}$$



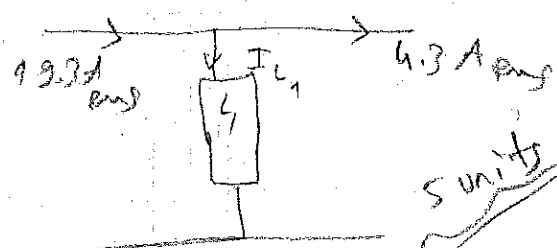Note: In the previous problem, let's find I_{L1} .




$S_L = 2000 + j2666$
 $|S_{L1}| = \frac{2000}{0.6} = 3333 \text{ VA}$
 $\cos(\theta_{L1}) = 0.6$
 $I_{L1} = 15.84 \text{ A RMS}$

Notes:
 Never write KVL or KCL equations for RMS quantities, it should be clear that RMS quantities by definition > 0 , so $V_1^{RMS} + V_2^{RMS} + V_3^{RMS} \neq 0$

Note that: $I_{L1}^{RMS} \neq 19.3 - 4.3$
 $15.84 \neq 15$

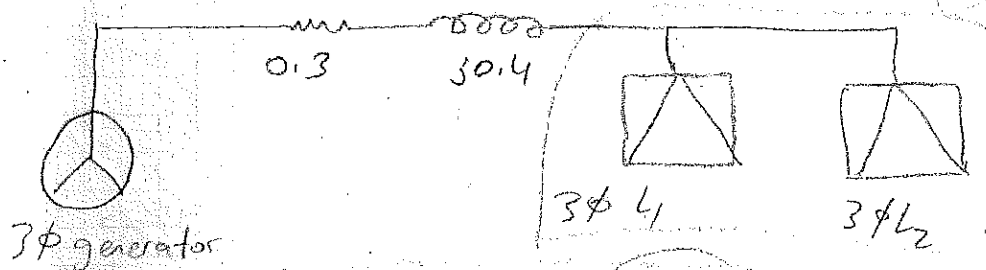Sol. (2): Schematic for a 3 ϕ system can never be equal to zero.



two loads are "hanging"
 we don't have any information about them being Y or Δ ;
 because this formula is valid for both cases

$S_{gen}^{3\phi} = \sqrt{3} V_{line-to-line}^{RMS} I_{line}^{RMS} e^{j\theta_{gen}}$
 $|S_{gen}^{3\phi}| = \sqrt{3} V_{line-to-line}^{RMS} I_{line}^{RMS} \rightarrow I_{line}^{RMS} = 19.3 \text{ A RMS}$
 $S_{line}^{3\phi} = 3(I_{line}^{RMS})^2 Z_{line} = 3(112 + j149) = 336 + j447$
 $S_{L1+L2}^{3\phi} = S_{gen}^{3\phi} - S_{line}^{3\phi} = 8664 + j8553 \text{ VA}$
 $|S_{L1+L2}^{3\phi}| = \sqrt{3} V_{L1+L2, line-to-line}^{RMS} I_{L1+L2}^{RMS} \rightarrow V_{L1+L2}^{RMS} = 364 \text{ V RMS}$


$$S_{L_2}^{3\phi} = S_{L_1+L_2}^{3\phi} - S_{L_1}^{3\phi} = 2664 + j561$$

Then $\rightarrow |S_{L_2}^{3\phi}| = \sqrt{3} V_{L_2, \text{line-to-line}}^{RMS} I_{L_2}^{RMS} \rightarrow I_{L_2}^{RMS} = 4.3 \text{ Amps}$

Pls. also check notes p.69 for solution of a 3 ϕ power compensation problem (A ZPS problem).
Check Sadiku's book for 3 ϕ definition and examples.

3 ϕ Power Measurement with 2 wattmeters:

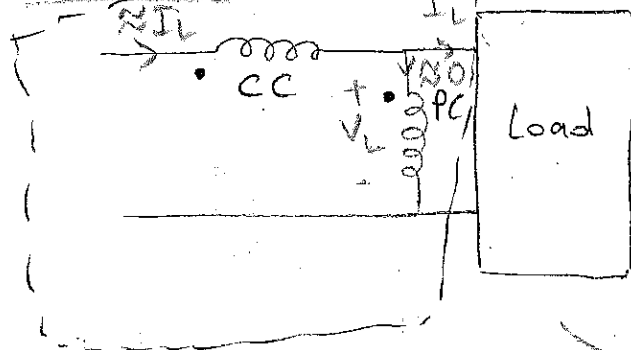Wattmeter: An equipment built for power measurement.



PC: potential coil

CC: current coil

High impedance

Low impedance


Watt meter

$$S = \frac{1}{2} V_L^{ph} I_L^{ph*}$$


1- ϕ Power measurement

Complex power of the load
Wattmeter gives the reading of:

$$\begin{aligned} P_{\text{Wattmeter}} &= \text{Re} \{ S \} \\ &= \text{Re} \left\{ \frac{1}{2} V_L^{ph} (I_L^{ph})^* \right\} \\ &= \frac{1}{2} |V_L^{ph}| \cdot |I_L^{ph}| \cos(\theta_{\text{Load}}) \\ &= V_L^{RMS} \cdot I_L^{RMS} \cos(\theta_{\text{Load}}) \end{aligned}$$

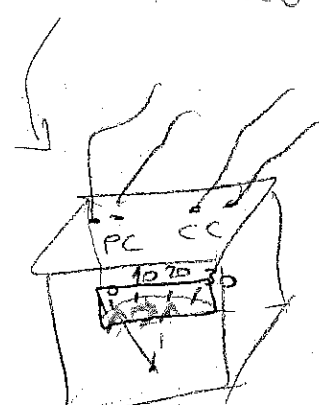

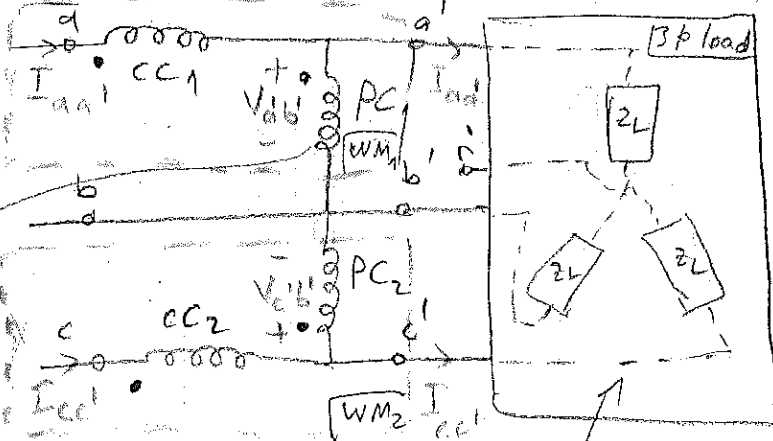
3 ϕ Power Measurement (with 2 wattmeters)



Power measured by WM's!

$$\begin{aligned} WM_1 &\Rightarrow \frac{1}{2} \text{Re} \{ V_{ab} I_{aa'}^* \} \\ WM_2 &\Rightarrow \frac{1}{2} \text{Re} \{ V_{cb} I_{cc'}^* \} \end{aligned}$$

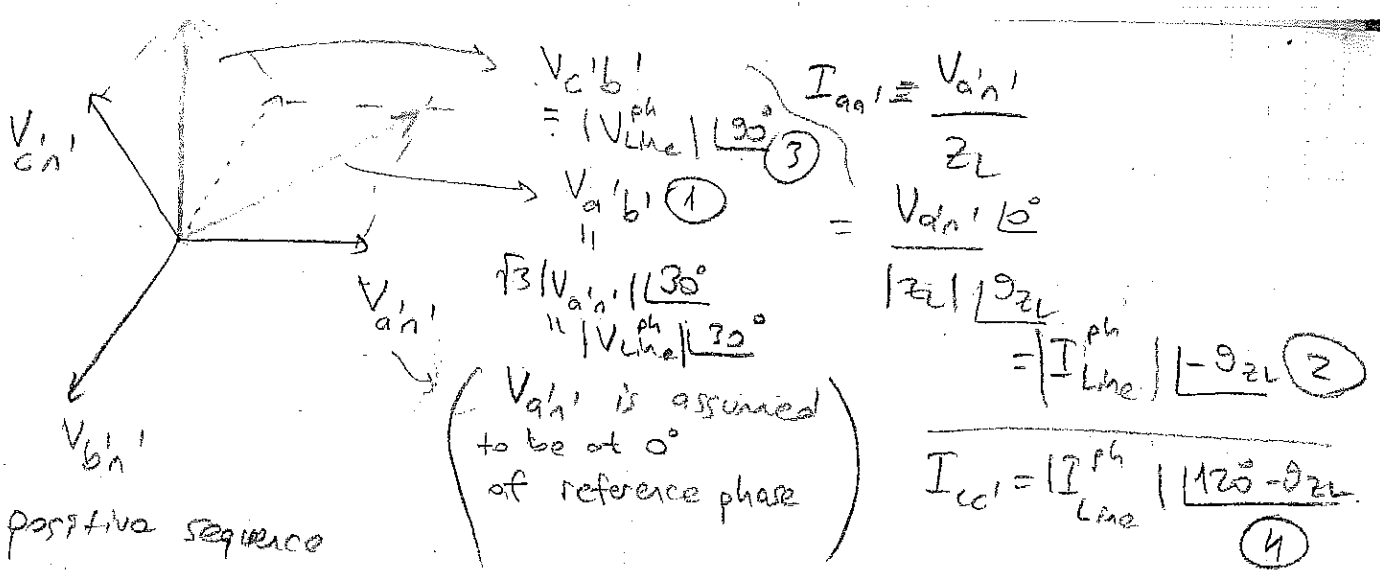Line-to-line voltage or line voltage V_{line}^{ph} balanced 3 ϕ Load



WM₁:

$$P_{WM_1} = \frac{1}{2} \operatorname{Re} \left\{ \underbrace{V_{a'b'}}_{(1)} \cdot \underbrace{I_{aa'}^*}_{(2)} \right\} = \frac{1}{2} \operatorname{Re} \left\{ |V_{Line}^{ph}| |I_{Line}^{ph}| \angle 30^\circ + \theta_{ZL} \right\}$$

WM₂:

$$P_{WM_2} = \frac{1}{2} \operatorname{Re} \left\{ \underbrace{V_{c'b'}}_{(3)} \cdot \underbrace{I_{cc'}^*}_{(4)} \right\} = \frac{1}{2} \operatorname{Re} \left\{ |V_{Line}^{ph}| |I_{Line}^{ph}| \angle -30^\circ + \theta_{ZL} \right\}$$

$$P_{WM_1} = \frac{1}{2} |V_{Line}^{ph}| |I_{Line}^{ph}| \cos(30^\circ + \theta_{ZL})$$

$$P_{WM_2} = \frac{1}{2} |V_{Line}^{ph}| |I_{Line}^{ph}| \cos(-30^\circ + \theta_{ZL})$$

$$P_{WM_1} + P_{WM_2} = \frac{1}{2} |V_{Line}^{ph}| |I_{Line}^{ph}| \cdot (2 \cos(\theta_{ZL}) \cos(30^\circ))$$

$$= \frac{\sqrt{3}}{2} |V_{Line}^{ph}| |I_{Line}^{ph}| \cos(\theta_{ZL})$$

$$= \sqrt{3} V_{Line}^{RMS} I_{Line}^{RMS} \cos(\theta_{ZL})$$

Remember that $P_{Load}^{3\phi} = \sqrt{3} V_{Line}^{RMS} I_{Line}^{RMS} \cos(\theta_{Load})$

Hence for the given wattmeter set-up, sum of watt-meter reading gives:

$$P_{WM_1} + P_{WM_2} = P_{Load}^{3\phi}$$

→ Sinusoidal
→ 4kabitivi

Similarly:

$$P_{W_1} - P_{W_2} = V_{Line}^{RMS} I_{Line}^{RMS} \sin(\theta_{Load})$$

$$= \frac{Q_{Load}^{3\phi}}{\sqrt{3}}$$


→ total reactive power of 3φ load

S-Domain (Laplace Domain) Circuit Analysis

Previously we've studied application of Laplace transform in the analysis of N^{th} order LTI circuits.

Now, we'll directly transform the circuit to Laplace domain and give the solution in the Laplace domain.

Component

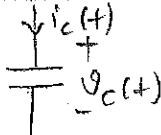C: 

Time-Domain

$i_c(t) = C \frac{d}{dt} v_c(t)$

$v_c(t) = v_c(t^-) + \frac{1}{C} \int_0^t i_c(\tau) d\tau$ ($t > 0$)

Laplace Transform


$I_c(s) = C [sV_c(s) - v_c(t^-)]$

Upper case letter \leftarrow Initial condition
Lower case letter \leftarrow


$V_c(s) = \frac{v_c(t^-)}{s} + \frac{1}{C} \frac{I_c(s)}{s}$

Initial condition models for capacitor

empty capacitor

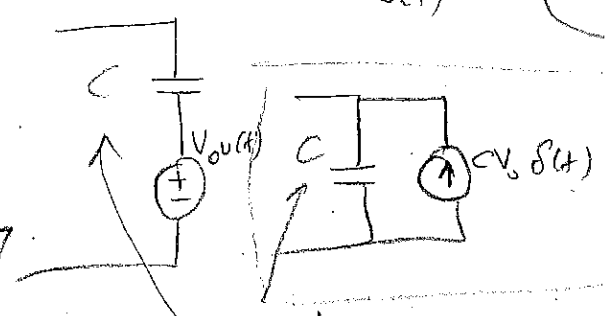


empty capacitor in Laplace domain

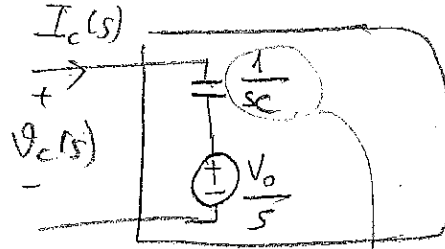

$\frac{V_c(s)}{\frac{1}{sC}} = sC V_c(s)$

$-eV_o$



Inductor:

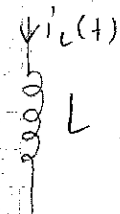



$i_L(0^-) = I_0$

empty inductors (unfluxed)

Time Domain Model:

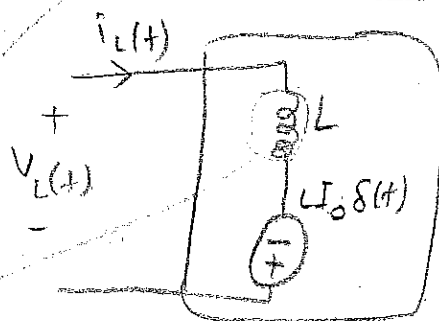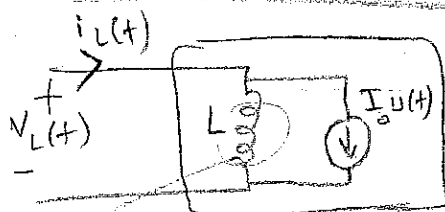


s-Domain Model:

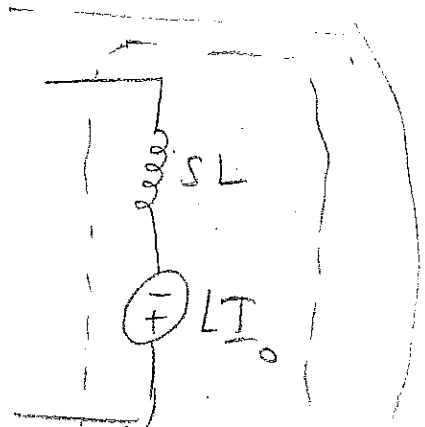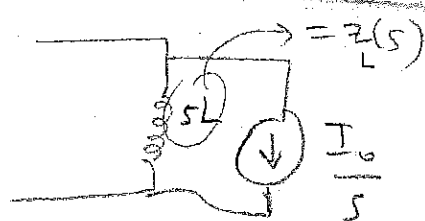


Source transformation of each other if sL is treated as an impedance with $z(s)$ definition.

Mesh Analysis in s-domain

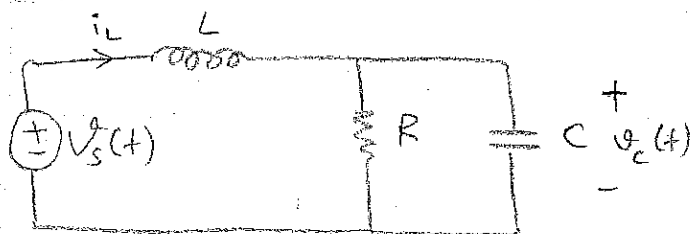

$i_L(0^-) = I_0$
 $v_C(0^-) = V_0$

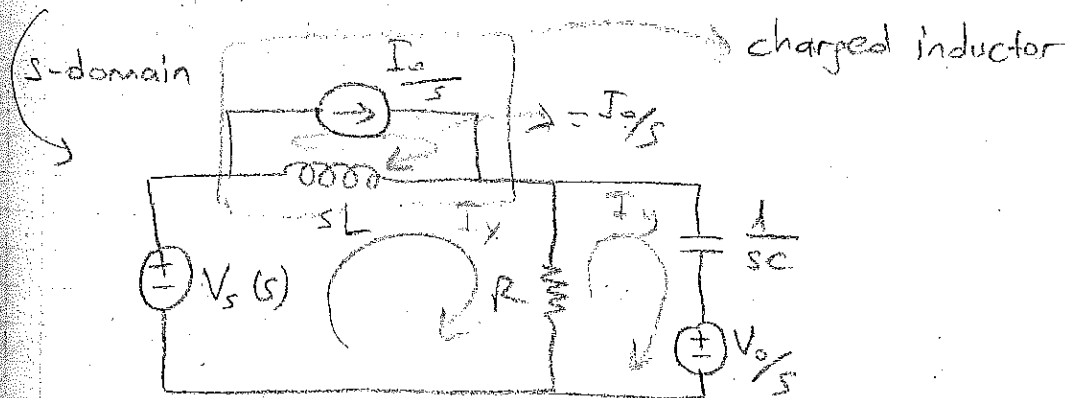

$$\begin{bmatrix} sL + R & -R \\ -R & R + \frac{1}{sC} \end{bmatrix} \begin{bmatrix} I_x(s) \\ I_y(s) \end{bmatrix} = \begin{bmatrix} V_s(s) + I_0 L \\ -\frac{V_0}{s} \end{bmatrix}$$

By calculating the inverse of matrix on LHS and applying from left to this equation, I can get

$$I_x(s) = \frac{\left(\frac{1}{RC} + \frac{s}{L}\right) V_s(s) + \frac{I_0}{RC} - \frac{V_0}{L} + sI_0}{s^2 + \frac{1}{RC}s + \frac{1}{LC}}$$


Solution in Laplace domain for zero-state solution

zero-input solution

Complete solution in Laplace domain

Note: $I_L(s) = I_x(s)$, that is charged inductor current is $I_x(s)$ in Laplace Domain.

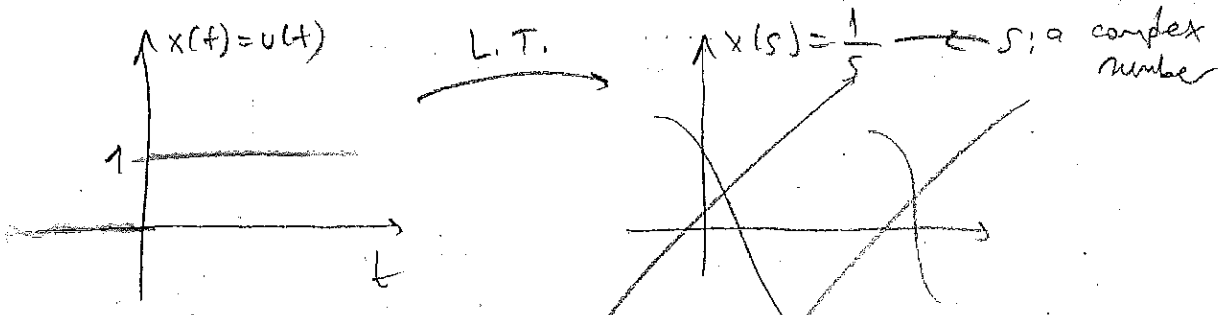Review: S-domain (Laplace Domain) Circuit Analysis!



$$x(s) = \frac{1}{s} = \frac{1}{\sigma + j\omega}$$

Upper-case "X"

↳ This can't be sketched

lower case signals

$$\text{Re}\{X(s)\} = \text{Re}\left\{\frac{1}{\sigma + j\omega}\right\} = \frac{\sigma}{\sigma^2 + \omega^2}$$

↳ function of two real variables

Laplace Transform


$$X(s) = \int_0^{\infty} x(t) e^{-st} dt$$

One-sided Laplace Transform (not two-sided)

There's a two-sided definition also.


$$x(t) = \frac{1}{2\pi j} \int_{\sigma - j\infty}^{\sigma + j\infty} X(s) e^{st} ds$$

Inverse Laplace Transform

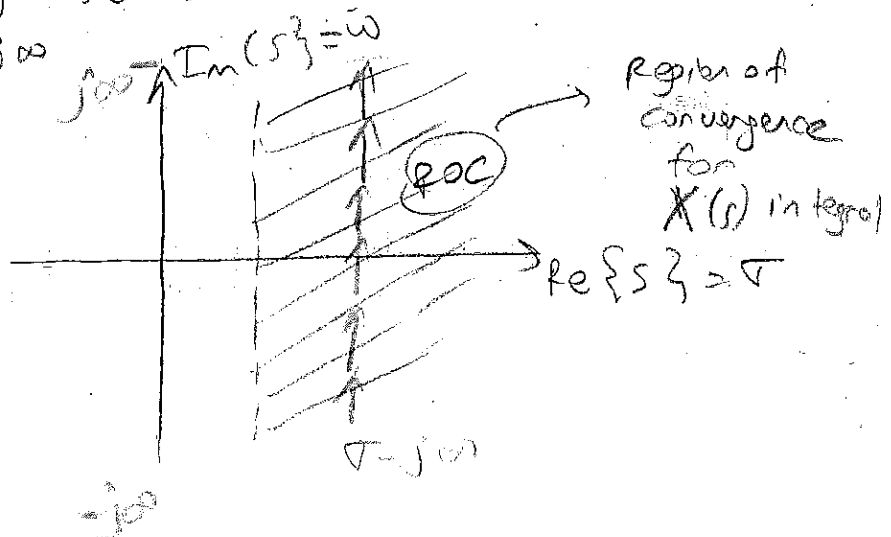

$$\mathcal{L}\left\{\frac{d}{dt}x(t)\right\} = sX(s) - \underbrace{x(0^-)}_{\text{Initial Condition}}$$

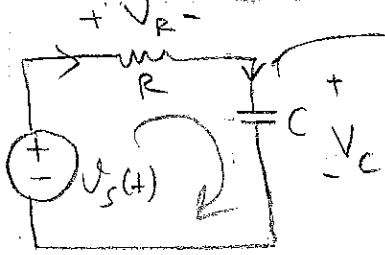Circuit Analysis with Laplace Transform / in s-domain



$$(v_c(0^-) = V_0)$$

Initial Condition

KVL:

$$-v_s(t) + v_R + v_c = 0$$

$$-v_s(t) + RC \dot{v}_c(t) + v_c(t) = 0$$

$$i_c = i_R$$

Lower case letters

$$\left(D + \frac{1}{RC}\right)v_c(t) = \frac{v_s(t)}{RC}, \quad v_c(0^-) = V_0$$

L.T.

$$\mathcal{L}\left\{\dot{v}_c(t) + \frac{v_c(t)}{RC}\right\} = \mathcal{L}\left\{\frac{v_s(t)}{RC}\right\}$$


$$(sV_c(s) - V_0) + \frac{V_c(s)}{RC} = \frac{V_s(s)}{RC}$$

$$V_c(s) = \frac{V_0}{s + \frac{1}{RC}} + \frac{1/RC}{s + 1/RC} \cdot V_s(s)$$


$$v_c^{z.i.}(s) = \frac{V_0}{s + \frac{1}{RC}}$$

$$v_c^{z.s.}(s) = \frac{1/RC}{s + 1/RC} V_s(s)$$

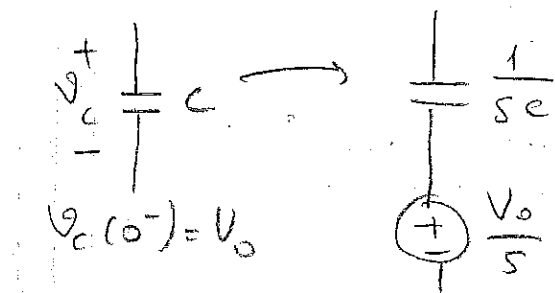
We'll further simplify the solution by transforming the circuit into Laplace domain.



time-domain

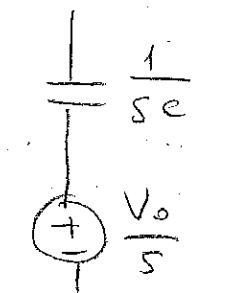


s-domain

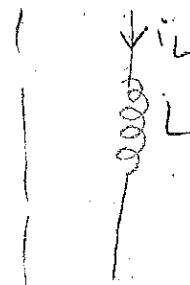

$i_L(0^-) = I_0$


time-domain

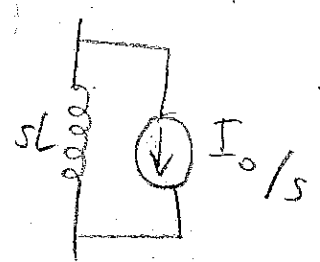


s-domain

Note: When $s = j\omega$, we have the phasor domain equivalents except the sources which are related with I.C.s.

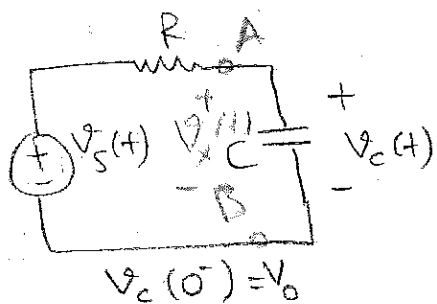(Remember, phasor domain gives s.s. (steady-state) solution; hence I.C.'s are not important in phasor domain.)



s-domain

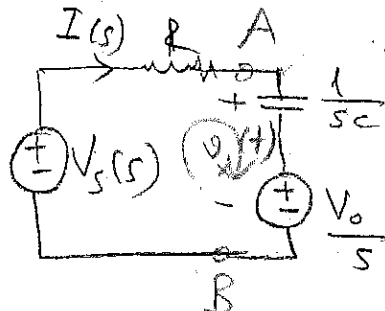

$$I(s) = \frac{V_s(s) - V_0/s}{R + \frac{1}{sC}}$$

$$V_c(s) = \frac{1}{sC} I(s) + \frac{V_0}{s}$$

$$= \frac{V_s(s) - V_0/s}{sCR + 1} + \frac{V_0}{s}$$

$$= \frac{V_s(s)}{sCR + 1} + V_0/s \left(1 - \frac{1}{sCR + 1}\right)$$

$$= \frac{V_s(s)/RC}{s + 1/RC} + \frac{V_0}{s} \left(\frac{sCR}{sCR + 1}\right)$$

Same with the result we have found.

$$\frac{V_0}{s + \frac{1}{RC}}$$

Some Important Laplace Transform Related Properties

(1) Initial Value Theorem

$$\lim_{t \rightarrow 0^+} f(t) = \lim_{s \rightarrow \infty} sF(s)$$

Initial value

(2) Final Value Theorem


$$\lim_{t \rightarrow \infty} f(t) = \lim_{s \rightarrow 0} sF(s)$$

Final value
 $f(\infty)$

Remark

① and ② is valid if all limits exist.

EX1

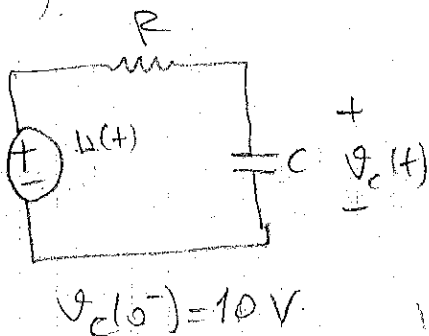

$$v_c(t) = 1 + 9e^{-\frac{t}{\tau}}, \quad t > 0 \quad (\tau = RC)$$

$$v_c(0^+) = 10V$$

$$v_c(\infty) = 1V$$


$$V_c(s) = \frac{V_s(s)/RC}{s + \frac{1}{RC}} + \frac{V_0}{s + \frac{1}{RC}}$$

$$\lim_{s \rightarrow \infty} sV_c(s) = 10 = V_c(0^+)$$

$$\lim_{s \rightarrow 0} sV_c(s) = 1 = V_c(\infty)$$

$$V_c(\infty) = 0$$

$$V_c(0^+) = 10 + \frac{1}{RC} V$$

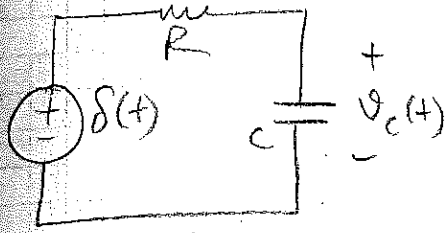

$$V_c(t) = \left(10 + \frac{1}{RC}\right) e^{-\frac{t}{RC}}, t > 0$$

$$V_c(0^-) = 10$$

$$V_c(s) = \frac{Vs(s)/RC}{s + \frac{1}{RC}} + \frac{V_0}{s + \frac{1}{RC}} = \frac{10 + \frac{1}{RC}}{s + \frac{1}{RC}}$$

$$1 = \int \delta(t) dt$$

$$\text{Initial value} = \lim_{s \rightarrow \infty} sV_c(s) = 10 + \frac{1}{RC}$$

$$\text{Final value} = \lim_{s \rightarrow 0} sV_c(s) = 0$$




Second MT \rightarrow It starts from AC analysis. HWs are on website. Check Sadiku for AC analysis, 3-phase systems, s-domain.

Additional Hours \rightarrow Friday 12:40 - 19:40 (in usual lecture room)

You can also check ZPS problems

Ex:

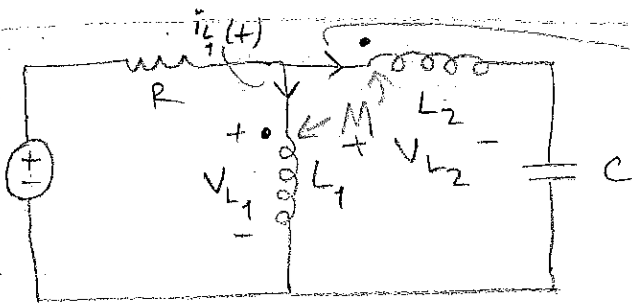

$$i_{L1}(0^-) = I_1$$

$$i_{L2}(0^-) = I_2$$


$$V_c(0^-) = V_0$$

L.T.

$$\begin{bmatrix} V_{L1}(t) \\ V_{L2}(t) \end{bmatrix} = \begin{bmatrix} L_1 & M \\ M & L_2 \end{bmatrix} \begin{bmatrix} \frac{d}{dt} i_{L1}(t) \\ \frac{d}{dt} i_{L2}(t) \end{bmatrix}$$

$$\begin{bmatrix} V_{L1}(s) \\ V_{L2}(s) \end{bmatrix} = \begin{bmatrix} L_1 & M \\ M & L_2 \end{bmatrix} \begin{bmatrix} sI_{L1}(s) - i_{L1}(0^-) \\ sI_{L2}(s) - i_{L2}(0^-) \end{bmatrix}$$
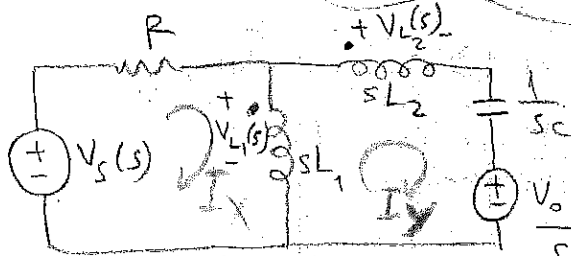
$$= \begin{bmatrix} sL_1 & sM \\ sM & sL_2 \end{bmatrix} \begin{bmatrix} I_{L1}(s) \\ I_{L2}(s) \end{bmatrix} - \begin{bmatrix} L_1 & M \\ M & L_2 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix} \rightarrow I_x(s) - I_y(s)$$



KVL (I_x):

$$-V_s(s) + RI_x + V_{L1}(s) = 0$$

KVL (I_y mesh):


$$-V_{L1}(s) + V_{L2}(s) + I_y \frac{1}{sC} + \frac{V_0}{s} = 0$$

2 equations with 2 mesh currents as unknowns

$$V_{L_1}(s) = sL_1(I_x - I_4) + sM I_4 - L_1 I_1 - M I_2$$

$$V_{L_2}(s) = sM(I_x - I_4) + sL_2 I_4 - M I_1 - L_2 I_2$$

For node analysis:

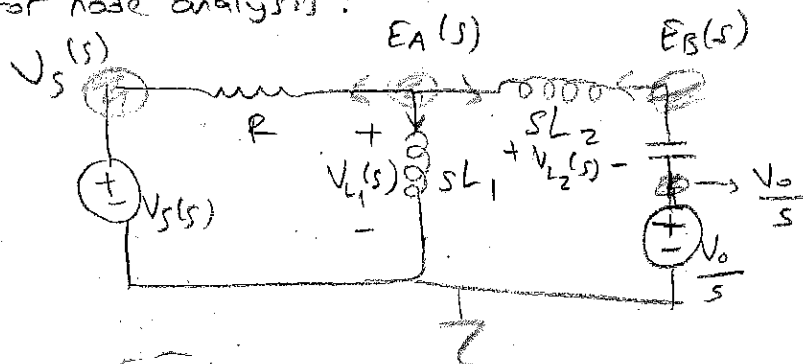

$$\begin{bmatrix} V_{L_1}(s) \\ V_{L_2}(s) \end{bmatrix} = \begin{bmatrix} sL_1 & sM \\ sM & sL_2 \end{bmatrix} \begin{bmatrix} I_{L_1}(s) \\ I_{L_2}(s) \end{bmatrix} - \begin{bmatrix} L_1 & M \\ M & L_2 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix}$$

\downarrow \downarrow \vdots
 $E_A(s)$ $E_A(s) - E_B(s)$ \vdots

Zero-state Responses in s-domain

Let's focus on zero-state response, that is the response when all I.C.'s are zero.

A typical solution is in the form

$$V_k^{z.s.}(s) = \frac{\text{num}(s)}{\text{denum}(s)} \cdot V_s(s)$$

↑ External input in Laplace domain

For 1st order RC circuit:

$$V_c^{z.s.}(s) = \frac{1/RC}{s + 1/RC} V_s(s)$$

Note that for different inputs the zero-state solution is simply the product of $\frac{\text{num}(s)}{\text{denum}(s)} = H(s)$ and

$V_s(s)$ in Laplace domain. That is, for any input $H(s)$ is fixed for a given system.


For example: $H(s) = \frac{1/RC}{s + 1/RC}$ ← 1st order R.C.

Case ① $V_s(t) = u(t) \rightarrow V_c^{z,s, step} = H(s) \cdot \{u(t)\} = \frac{1/RC}{s + 1/RC} \cdot \frac{1}{s}$

Case ② $V_s(t) = \delta(t) \rightarrow V_c^{z,s, impulse} = \frac{1/RC}{s + 1/RC} \cdot 1$
 $H(s)$


Case ③ $V_s(t) = 5 \cos(2t) \rightarrow V_c^{z,s, cosine}(s) = \frac{1/RC}{s + 1/RC} \cdot \frac{5s}{s^2 + 4}$
 $H(s)$

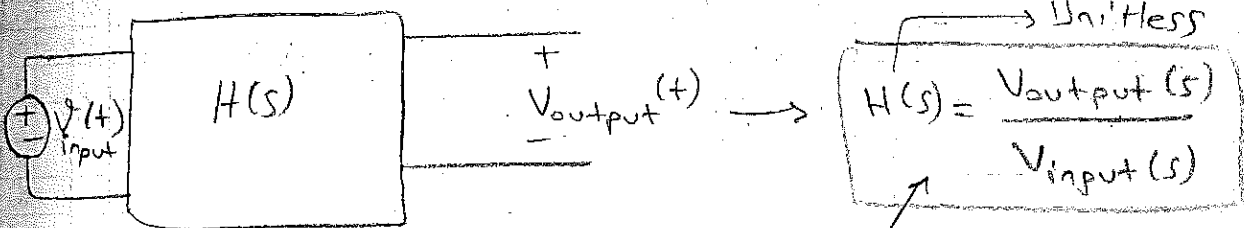$H(s)$ is called a transfer function and shown as:





Voltage transfer function
 input: voltage
 output: voltage

Current transfer function:

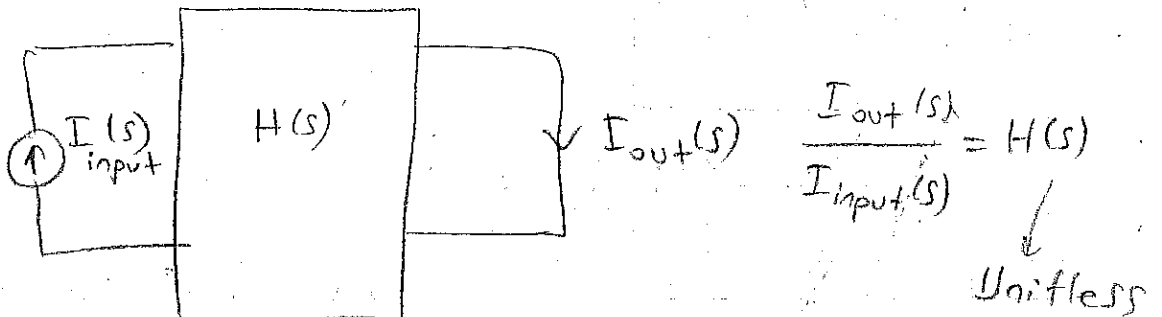

Transfer admittance

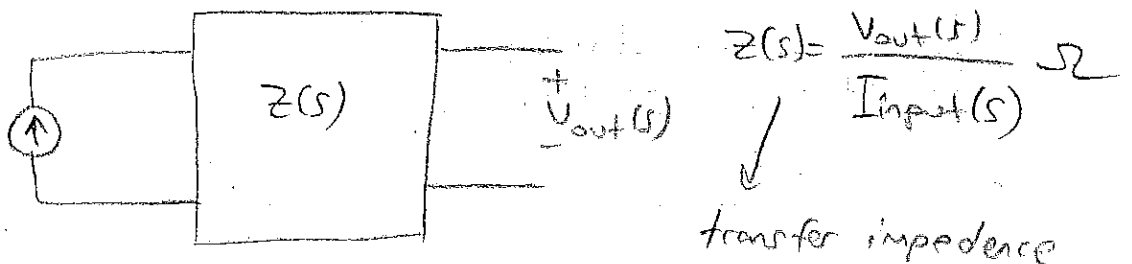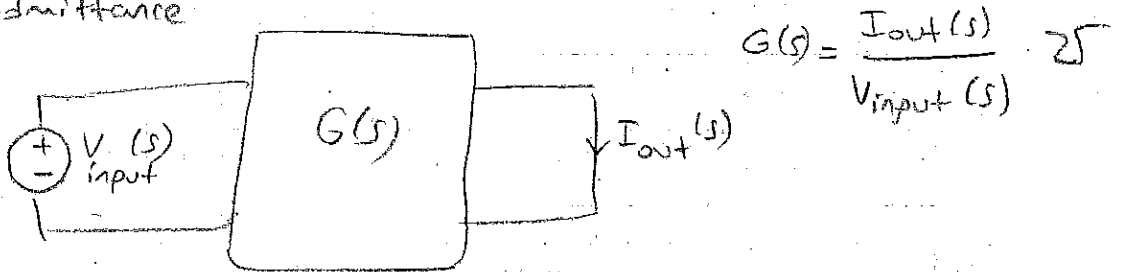

Note: All transfer functions are only valid for Z.S. circuits.

$$V_c(t) = 2 \cos(2t + 30^\circ) \text{ V (rms)}$$

$$V_c^{ph} = 2 \angle 30^\circ$$

$$V_c^{rms} = \frac{2}{\sqrt{2}} = \sqrt{2} \text{ V (rms)}$$

V_{rms}

Phasor
(Complex number)

$$V_c = \sqrt{2} \angle 30^\circ \text{ V (rms)}$$

$$I_{cap} = \frac{1}{Z_{cap}} \frac{(V_{cap}^{ph})^2}{Z_{cap}^*} = \frac{(V_{cap}^{ph, rms})^2}{Z_{cap}^*}$$

Magnitude of this phasor is in RMS!


$$X_{rms} = \sqrt{\langle x^2(t) \rangle}$$

$$\langle x^2(t) \rangle = \lim_{T \rightarrow \infty} \frac{1}{T} \int_{-T/2}^{T/2} x^2(t) dt$$

We can get rid of $\frac{1}{2}$ if we use

$$V_{cap}^{ph, rms}$$

Transfer Functions:

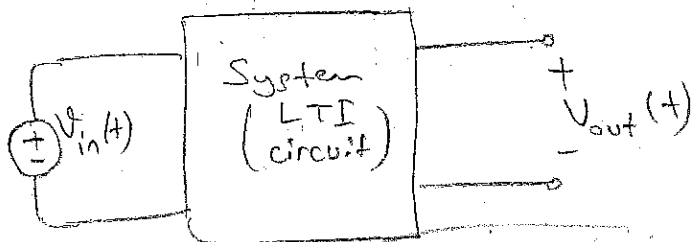

$$H(s) = \frac{V_{out}(s)}{V_{input}(s)}$$

transfer function


$$V_{out}(s) = H(s) V_{input}(s)$$

Important Fact

Note that

All transfer function related calculations assume that the initial conditions are all zero, that is they assume zero state conditions and transfer function is related with zero state input.

Ex:

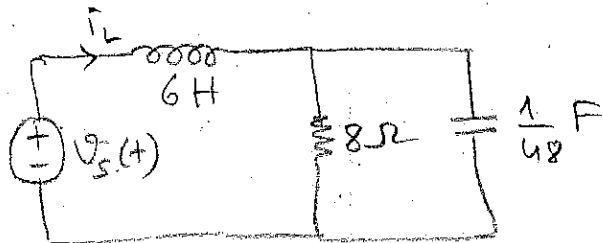


$$V_c(0^-) = V_0$$

$$I_L(0^-) = I_0$$

a) Find $i_L(t)$, $t > 0$.

Solution:

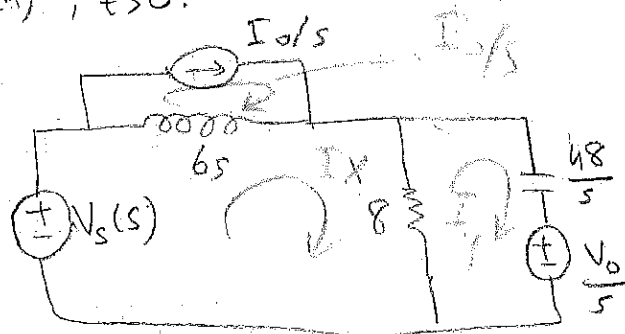

$$\frac{\text{KVL}}{I_x} \quad -V_s(s) + 6s(I_x - \frac{I_0}{s}) + 8(I_x - I_y) = 0$$

$$\frac{\text{KVL}}{I_y} \quad 8(I_y - I_x) + \frac{48}{s} \cdot I_y + \frac{V_0}{s} = 0$$

$$\begin{bmatrix} 6s+8 & -8 \\ -8 & \frac{48}{s}+8 \end{bmatrix} \begin{bmatrix} I_x(s) \\ I_y(s) \end{bmatrix} = \begin{bmatrix} 1 \\ 0 \end{bmatrix} V_s(s) + \begin{bmatrix} 6 \\ 0 \end{bmatrix} I_0 + \begin{bmatrix} 0 \\ -1 \end{bmatrix} \frac{V_0}{s}$$

$$\begin{bmatrix} I_x(s) \\ I_y(s) \end{bmatrix} = \underbrace{\begin{bmatrix} 6s+8 & -8 \\ -8 & \frac{48}{s}+8 \end{bmatrix}}_M^{-1} \begin{bmatrix} V_s(s) + 6I_0 \\ -\frac{V_0}{s} \end{bmatrix} = \frac{1}{\Delta} \begin{bmatrix} \frac{48}{s}+8 & 8 \\ 8 & 6s+8 \end{bmatrix} \begin{bmatrix} V_s(s) + 6I_0 \\ -\frac{V_0}{s} \end{bmatrix}$$

M

$$\begin{aligned} \Delta &= \det(M) = (6s+8)\left(\frac{48}{s}+8\right) - 64 \\ &= 16 \left[(3s+4)\left(\frac{6}{s}+1\right) - 4 \right] \\ &= 16 \left[18 + 3s + \frac{24}{s} \right] \\ &= \frac{16}{s} (3s^2 + 18s + 24) \\ &= \frac{48}{s} (s^2 + 6s + 8) \\ &= \frac{48}{s} (s+4)(s+2) \end{aligned}$$

$$\begin{bmatrix} I_x(s) \\ I_y(s) \end{bmatrix} = \frac{1}{\Delta} \begin{bmatrix} 8\left(\left(\frac{6}{s}+1\right)(V_s(s) + 6I_0) - \frac{V_0}{s}\right) \\ 8 \cdot 1 \cdot (V_s(s) + 6I_0) - (6s+8)\frac{V_0}{s} \end{bmatrix}$$

$$= \frac{s}{48(s+2)(s+4)}$$

$$\begin{aligned} I_x(s) &= \frac{s}{6(s+2)(s+4)} \left[\left(\frac{6}{s}+1\right)V_s(s) + \left(\frac{6}{s}+1\right)6I_0 - \frac{V_0}{s} \right] \\ &= \frac{1}{6(s+2)(s+4)} \left[(6+s)V_s(s) + (6+s)6I_0 - V_0 \right] \end{aligned}$$

$$\rightarrow i_x(t) = \mathcal{L}^{-1} \{ I_x(s) \}$$

complete solution

Let $v_s(t) = u(t) \rightarrow V_s(s) = \frac{1}{s}$

step, complete
 $I_x(s) = \frac{(s+6)}{6(s+2)(s+4)} \cdot \frac{1}{s} + \frac{(6+s)6I_0 - V_0}{6(s+2)(s+4)}$

$= \frac{A}{s} + \frac{B}{s+2} + \frac{C}{s+4}$

$A = \frac{6}{6 \cdot 2 \cdot 4}$ (Multiplied every side with $s=0$)

$B = \frac{4}{6 \cdot 2 \cdot (-2)} + \frac{24I_0 - V_0}{12}$

$A = \frac{1}{8}$

$= \frac{24I_0 - V_0 - 2}{12}$

(Multiplied every side with $s=-2$)

$C = \frac{-2}{6 \cdot (-2) \cdot (-4)} + \frac{12I_0 - V_0}{-12}$


(Multiplied both sides with $s=-4$)

$= \frac{-24I_0 + 2V_0 + 1}{24}$

complete, step
 $i_x(t) = A u(t) + B e^{-2t} u(t) + C e^{-4t} u(t)$


Note: (1) Natural frequencies of the system = $\{-2, -4\}$

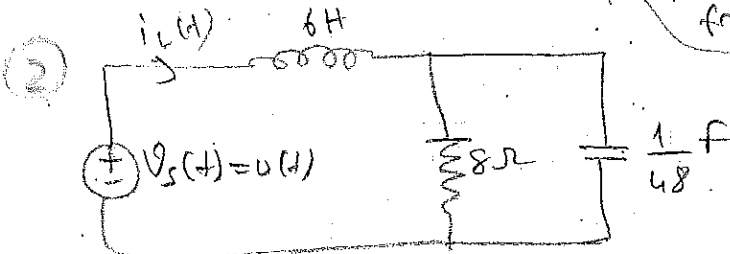\hookrightarrow zero (0). Don't a natural frequency; it comes from input ($v_s(t) = u(t)$)



$i_L(\infty) = \frac{1}{8}$ (Also $i_L(\infty) = \lim_{s \rightarrow 0} s I_x(s)$) Final Value Theorem

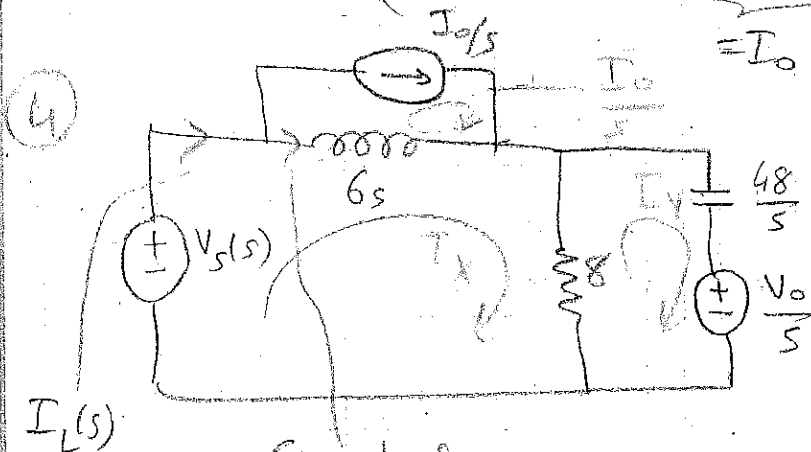$i_L(0^+) = I_0$ (Also $i_L(0^+) = \lim_{s \rightarrow \infty} s I_x(s)$) Initial Value Theorem



Current of the empty inductor that is the inductor without any initial charge.

5) The transfer function between $V_s(s)$ and $I_L(s)$ ($= I_x(s)$).

Then taken initial conditions as zero and look at the relation between input and output.

$$I_L(s) = \frac{s+6}{6(s+2)(s+4)} V_s(s)$$

$$I_x(s) = \frac{(s+6)V_s(s)}{6(s+2)(s+4)} + \frac{(6+s)6I_0 - V_0}{6(s+2)(s+4)}$$

Output in s-domain

Input in s-domain

$$G(s) = \frac{I_L(s)}{V_s(s)} = \frac{s+6}{6(s+2)(s+4)} \rightarrow \text{transfer function}$$

5.a) Find step response

$$V_s(t) = u(t) \rightarrow V_s(s) = \frac{1}{s}$$

$$I_L^{\text{step}}(s) = G(s) \cdot V_s(s) = G(s) \cdot \frac{1}{s}$$

$$I_L^{\text{step}}(s) = \frac{s+6}{6(s+2)(s+4)s}$$

$$i_L^{\text{step}}(t) = \frac{1}{8} - \frac{4}{24}e^{-2t} + \frac{1}{24}e^{-4t} \quad A, \quad t > 0$$

5.b) Find impulse response

$$V_s(t) = \delta(t) \rightarrow V_s(s) = 1$$

$$I_L^{\text{impulse}}(s) = G(s) \cdot V_s(s) = \frac{s+6}{6(s+2)(s+4)} = \frac{1/3}{s+2} + \frac{-1/6}{s+4}$$

$$i_L^{\text{impulse}}(t) = \left(\frac{1}{3}e^{-2t} - \frac{1}{6}e^{-4t} \right) u(t)$$

Remember

$$i_L^{\text{impulse}}(t) = \frac{d}{dt} i_L^{\text{step}}(t)$$

derivative of step response is the impulse response

or in Laplace domain

$$I_L^{\text{impulse resp.}}(s) = s I_L^{\text{step resp.}}(s) - i_L^{\text{step}}(0)$$

= 0 because step response calculation is done at zero I.C.'s or at zero-state.

From important fact

5.c) Find the zero-state response to the input

$$V_s(t) = \frac{d}{dt} \delta(t) = \dot{\delta}(t)$$

Doublet response

$$I_L(s) = G(s) V_s(s) = \mathcal{L}\{\dot{\delta}(t)\} = \mathcal{L}\left\{\frac{d}{dt} \delta(t)\right\}$$

$$= G(s) \cdot s$$

$$= \frac{(s+6) \cdot s}{6(s+2)(s+4)}$$

$$= s \mathcal{L}\{\delta(t)\} - \delta(0^+) = s$$

~~$$= \frac{-8/12}{s+2} + \frac{-8/12}{s+4}$$~~

$$= \frac{1}{6} + \frac{-8}{6(s+2)(s+4)}$$

They are not equal
(Wrong method)

Remember to do partial fraction expansion as usual

$$\deg(\text{num}(s)) < \deg(\text{denum}(s))$$

$$0 < 2$$

$$= \frac{1}{6} + \frac{-8/12}{s+2} + \frac{8/12}{s+4}$$

$$i_L(t) = \left(\frac{1}{6} \delta(t) - \frac{2}{3} e^{-2t} + \frac{2}{3} e^{-4t} \right) \quad A, t > 0$$

5.d) Find zero-state response for $V_s(t) = 6 \cos(2t)$

$$I_L(s) = G(s) \cdot \mathcal{L}\{V_s(t)\}$$

$$= \frac{s+6}{6(s+2)(s+4)} \cdot \frac{6s}{s^2+4}$$

$$= \frac{(s+6)s}{(s+2)(s+4)(s^2+4)} = \frac{(-2)}{(s+2)(s+4)} + \frac{(-4)}{(s+4)(s+2)} + \frac{As+B}{s^2+4}$$

$$-\frac{1}{2} + \frac{1}{5} + A = 0 \Rightarrow A = \frac{3}{10}$$

Coefficients of s^3

$$-\frac{1}{2} + \frac{1}{5} + B = 0 \Rightarrow B = \frac{4}{5}$$

Constant terms

$$i_L(t) = -\frac{1}{2} e^{-2t} + \frac{1}{5} e^{-4t} + \mathcal{L}^{-1}\left\{\frac{As+B}{s^2+4}\right\}$$

$$\cos(2t) u(t) \quad A \mathcal{L}^{-1}\left\{\frac{s}{s^2+4}\right\} + \frac{B}{2} \mathcal{L}^{-1}\left\{\frac{2}{s^2+4}\right\}$$

$\sin(2t) u(t)$

$$= \left(-\frac{1}{2} e^{-2t} + \frac{1}{5} e^{-4t} + \frac{3}{10} \cos(2t) + \frac{4}{10} \sin(2t) \right) u(t) \text{ A}$$

⑥ Let's find the differential equation between input $v_s(t)$ and output $i_L(t)$.

output $i_L(t)$

$$G(s) = \frac{s+6}{6(s+2)(s+4)}$$

input $v_s(t)$

$$I_L(s)(s+2)(s+4) = \frac{(s+6)}{6} V_s(s)$$

$$s^2 I_L(s) + 6s I_L(s) + 8 I_L(s) = \frac{s+6}{6} V_s(s)$$

$$-s I_L(0^-) - \frac{dI_L(0^-)}{dt} = 0$$

$$\frac{d^2 i_L(t)}{dt^2} + 6 \left[\frac{d}{dt} i_L(t) \right] + 8 i_L(t) = \frac{1}{6} \left[\frac{d}{dt} v_s(t) + 6 v_s(t) \right]$$


$$s^2 I_L(s) + 6s I_L(s) + 8 I_L(s) = \frac{1}{6} (s V_s(s) + 6 V_s(s))$$

Using the knowledge of the relation above is valid at zero-state, that is all I.C. at $t=0^-$ are zero!

$$(D^2 + 6D + 8) i_L(t) = \frac{1}{6} (D + 6) v_s(t)$$

Complete Solution via zero-state, zero-input Decomposition

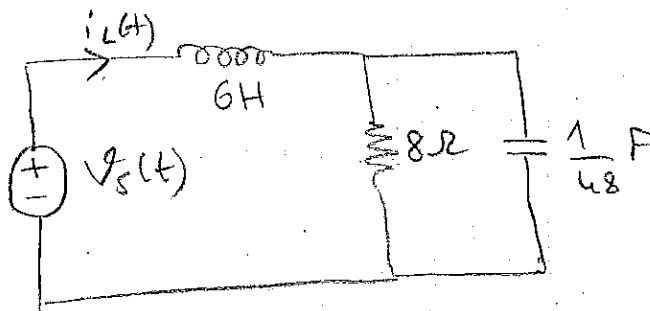Last lecture, we have studied the zero-state solution for LTI circuits in s-domain. We have studied transfer functions and established connection between transfer functions and zero-state responses such as step response, impulse response etc.



$v_c(0^-) = 0$
 $i_L(0^-) = 0$

Zero I.C.
 zero-state

$$H(s) = \frac{s+6}{6(s+2)(s+4)}$$

$$\frac{\mathcal{L}\{i_L(t)\}}{\mathcal{L}\{v_s(t)\}}$$

Then for any input $\mathcal{L}\{v_s(t)\}$
 $I_L^{zero-state}(s) = H(s) \cdot V_s(s)$

Case ① $v_s(t) = \delta(t)$
 $I_L^{zs, impulse}(s) = H(s) \cdot 1$

$$i_L^{impulse, zs}(t) = \mathcal{L}^{-1}\{H(s)\} = \left(\frac{1}{3}e^{-2t} - \frac{1}{6}e^{-4t}\right)u(t)$$


Special notation for impulse response
 (Also discussed in EE201)

Case ②: $v_s(t) = u(t)$

$$I_L^{step, zs}(s) = H(s) \cdot \frac{1}{s}$$


$$i_L^{step}(t) = \left(\frac{1}{8} - \frac{6}{24}e^{-2t} + \frac{1}{4}e^{-4t}\right)u(t)$$

Complete Solution:

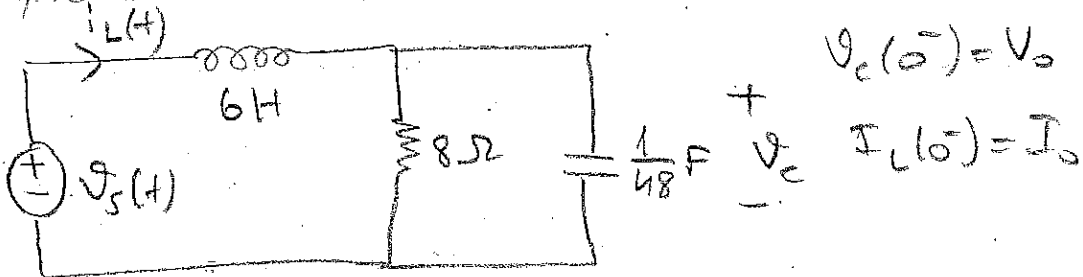


Find the complete solution for $i_L(t)$ in s -domain.

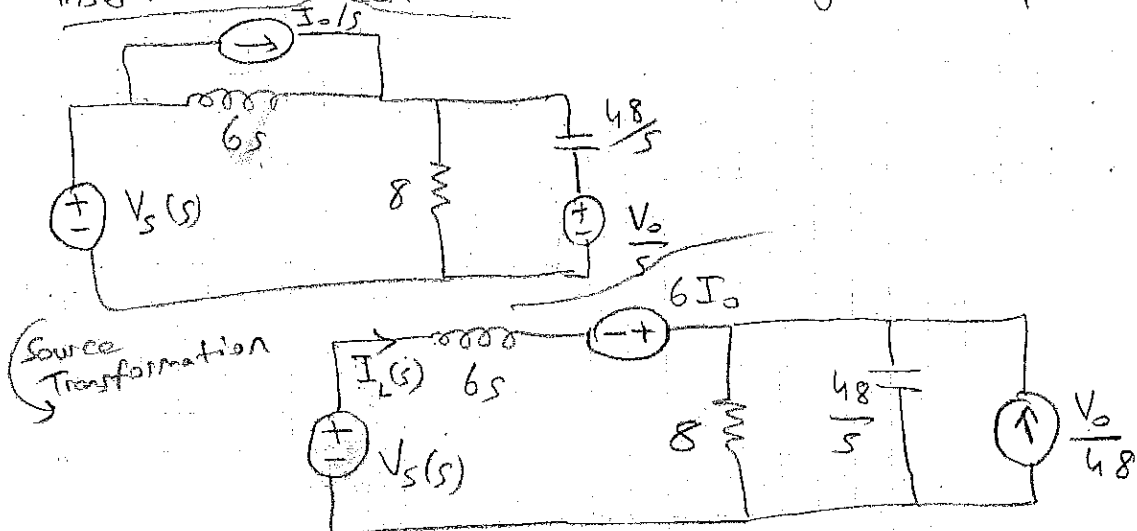Insert initial condition nodes for dynamic components.



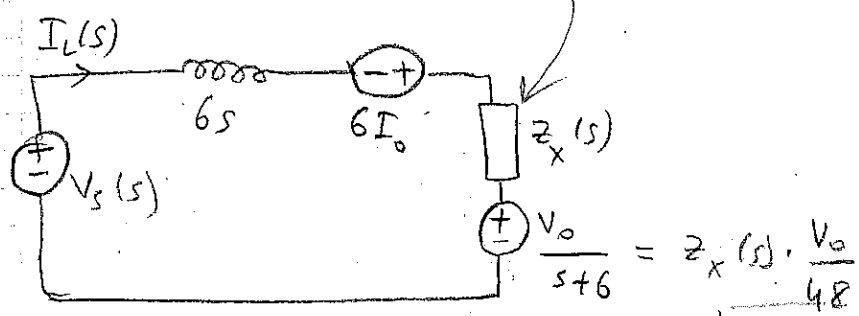
$$8 // \frac{48}{s} = \frac{8 \cdot \frac{48}{s}}{8 + \frac{48}{s}} = \frac{48}{s+6} = z_x(s)$$



$$H(s) = \frac{s+6}{6(s+2)(s+4)}$$
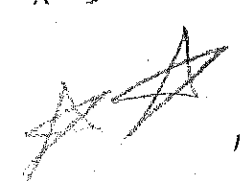
$$I_L(s) = \frac{V_s(s) + 6I_o - \frac{V_o}{s+6}}{z_x(s) + 6s} = I_L(s) = \underbrace{\frac{1}{z_x(s) + 6s}}_{\text{zero-state solution in s-domain}} V_s(s) + \underbrace{\frac{6I_o - \frac{V_o}{s+6}}{z_x(s) + 6s}}_{\text{zero-input solution in s-domain}}$$




complete solution in s-domain

zero-state solution in s-domain

zero-input solution in s-domain

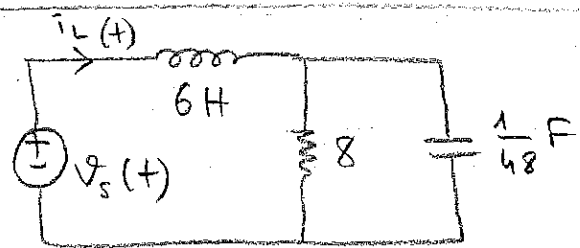Going back to zero-state responses are more time!



$$V_C(0^-) = 0$$

$$I_L(0^-) = 0$$

$$A = H(0)$$

$$H(s) = \frac{s+6}{6(s+2)(s+4)}$$

Case 1) $V_s(t) = u(t)$

$$I_L^{\text{step}}(s) = H(s) \cdot \frac{1}{s} = \frac{A}{s} + \frac{B}{s+2} + \frac{C}{s+4}$$

$$I_L^{\text{step}}(t) = (A + B e^{-2t} + C e^{-4t}) u(t)$$

$$\frac{I_L(s)}{V_s(s)}$$

Case 2: $V_s(t) = e^{s_0 t} u(t), s_0 \neq \{-2, -4\}$

$$I_L^{\text{case 2, z.s.}}(s) = H(s) \cdot \frac{1}{s-s_0}$$

$$= \frac{A}{s-s_0} + \frac{B}{s+2} + \frac{C}{s+4}$$

$L^{-1}\{s\}$

$$I_L^{\text{case 2, z.s.}}(t) = (A e^{s_0 t} + B e^{-2t} + C e^{-4t}) u(t)$$

$$A = H(s_0)$$

Case 3: $V_s(t) = e^{j\omega t} u(t)$

(Note: this is a special case ②, $s_0 = j\omega$)


case ③, z.s.
 $I_L(s) = H(s) \frac{1}{s-j\omega}$

$$= \frac{A}{s-j\omega} + \frac{B}{s+2} + \frac{C}{s+4}$$

case ③, z.s.
 $i_L(t) = A e^{j\omega t} + \dots e^{-2t} + \dots e^{-4t}$

$\rightarrow A = H(j\omega)$

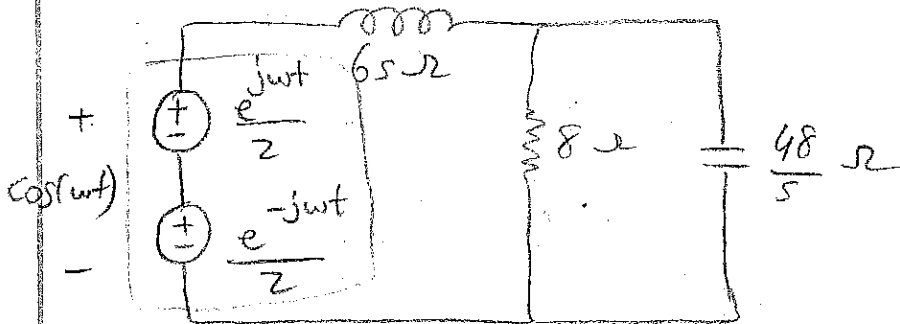Case ④ $V_s(t) = \cos(\omega t) u(t)$
 $= \left(\frac{e^{j\omega t} + e^{-j\omega t}}{2} \right) u(t)$



Zero-state circuit

When $\frac{e^{j\omega t}}{2}$ source is active (the other one is off):

$\rightarrow i_L^{z.s.} (t) = \frac{H(j\omega)}{2} e^{j\omega t} + \dots e^{-2t} + \dots e^{-4t}$

when $\frac{e^{-j\omega t}}{2}$ source is active (the other one is off):

$\rightarrow i_L^{z.s.} (t) = \frac{H(-j\omega)}{2} e^{-j\omega t} + \dots e^{-2t} + \dots e^{-4t}$

When both $\frac{e^{j\omega t}}{2}$ and $\frac{e^{-j\omega t}}{2}$ sources are ON at

the same time:

$i_L^{z.s.} (t) = i_L^{z.s.} (t)_{\text{A}} + i_L^{z.s.} (t)_{\text{B}}$

$$= \frac{H(j\omega)}{2} e^{j\omega t} + \frac{H(-j\omega)}{2} e^{-j\omega t} + \dots e^{-2t} + \dots e^{-4t}$$

Remember: $H(s) = \frac{s+6}{6(s+2)(s+4)}$

please note that

$$H(j\omega) = H^*(-j\omega)$$

$$H(s) = \frac{\text{num}(s)}{\text{denum}(s)}$$

This equality is also valid for all LTI circuits, since coefficients of num(s) polynomial and denum(s) polynomial are real valued.

$$\left(0 + \frac{1}{RC}\right) V_c(t) = \frac{V_s(t)}{RC} \rightarrow \frac{V_c(s)}{V_s(s)} = \frac{1/RC}{s + 1/RC}$$

$$i_L^{zs}(t) = \frac{H(j\omega)}{2} e^{j\omega t} + \left(\frac{H(j\omega)}{2} e^{j\omega t}\right)^* + \dots e^{-2t} + \dots e^{-4t}$$

$$= 2 \operatorname{Re} \left\{ \frac{H(j\omega)}{2} e^{j\omega t} \right\} + \dots e^{-2t} + \dots e^{-4t}$$

$$= \operatorname{Re} \left\{ H(j\omega) e^{j\omega t} \right\} + \dots e^{-2t} + \dots e^{-4t}$$

$\rightarrow |H(j\omega)| e^{j\angle H(j\omega)}$ } Polar coordinate representation of $H(j\omega)$

$$= |H(j\omega)| \cos(\omega t + \angle H(j\omega)) + \dots e^{-2t} + \dots e^{-4t} A$$

$$i_L^{zs}(t) \xrightarrow{t \rightarrow \infty} |H(j\omega)| \cos(\omega t + \angle H(j\omega)) A$$


Polar Coordinates:

steady-state ($t \rightarrow \infty$) of $i_L(t)$

$$z = 3 + j = \sqrt{10} e^{j \tan^{-1}(1/3)} = \sqrt{10} [\cos \theta + j \sin \theta]$$


$$= \sqrt{10} \left(\tan^{-1}\left(\frac{1}{3}\right) \right)$$


Phasor domain notation

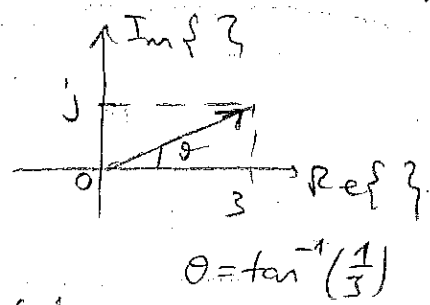

For $H(s) \Big|_{s=j\omega} = \frac{6+j\omega}{6(2+j\omega)(4+j\omega)} / H(j\omega) \Big|_{\omega=1} = \frac{6+j}{6(2+j)(4+j)}$
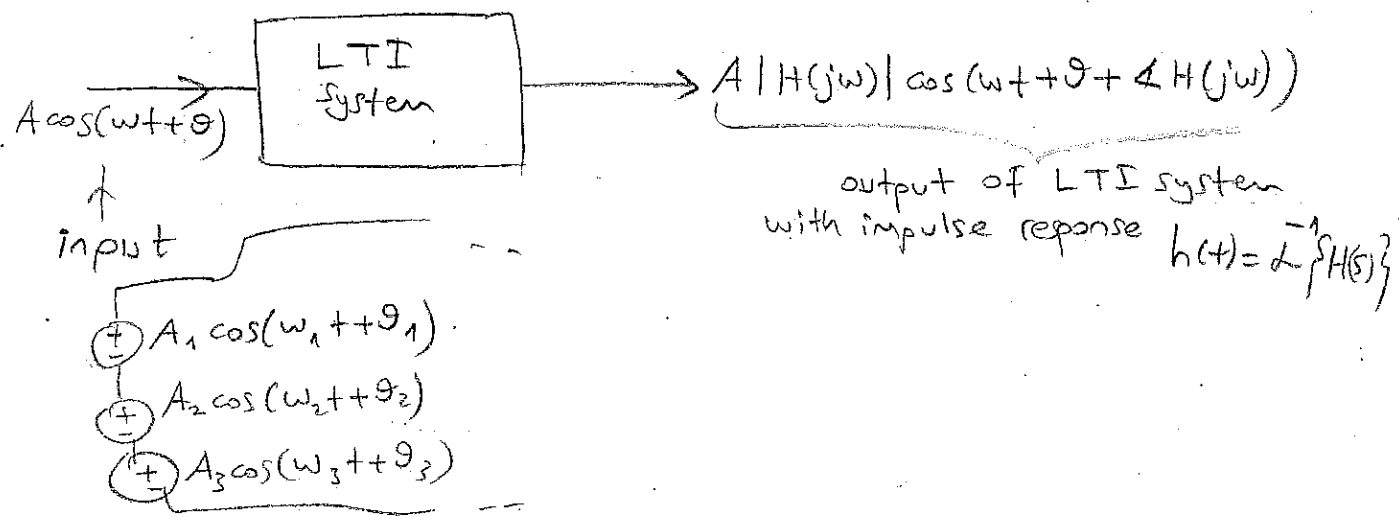
$$= \frac{\sqrt{37}}{6 \sqrt{17}} \left[\tan^{-1} \frac{1}{6} - \tan^{-1} \frac{1}{2} - \tan^{-1} \frac{1}{4} \right]$$



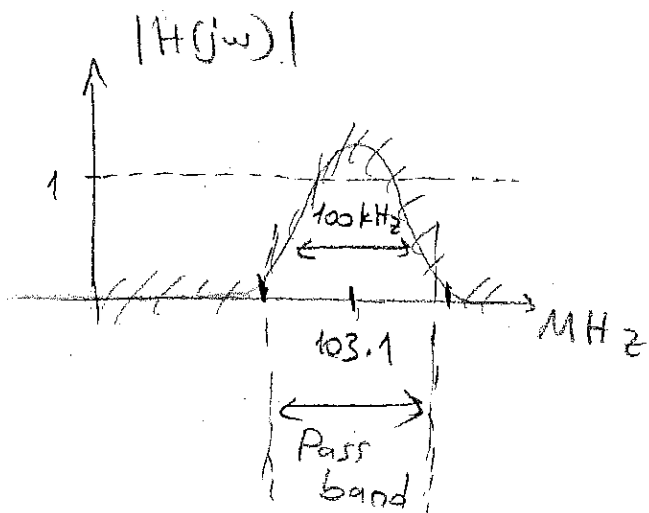

Pole-Zero Concept and $H(s)$

$$H(s) = K \frac{\prod_{k=1}^L (s - z_k)}{\prod_{k=1}^P (s - p_k)}$$

$\prod_{k=1}^3 k = 1 \cdot 2 \cdot 3 = 3!$
 Product symbol


Since for LTI systems of interest,

$H(s)$ is always ratio of two polynomials in "s" variable.

By fundamental theorem of algebra, \rightarrow num. and denom. polynomials can be factorized.


Then we may have a $H(s)$ in the form given:

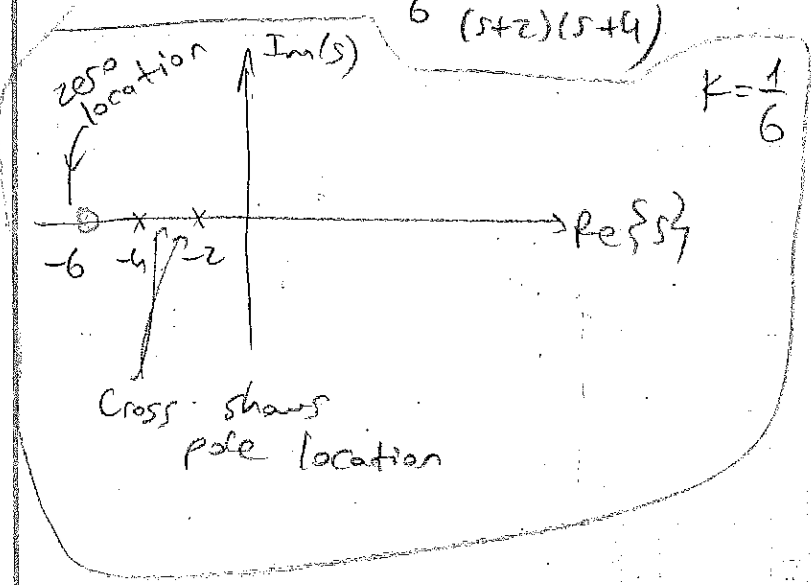For Ex 1 $H(s) = \frac{1}{6} \frac{s+6}{(s+2)(s+4)}$



$z_1 = -6$ } zero
 $p_1 = -2$ } poles
 $p_2 = -4$ }

Frequency Response

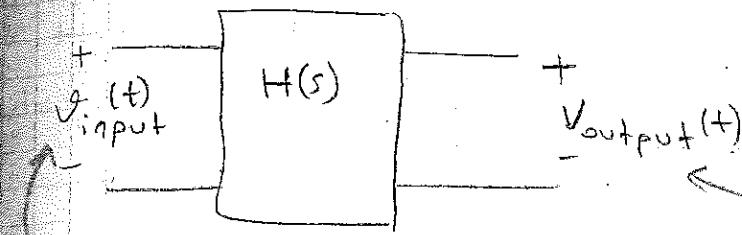

$A \cos(\omega t + \theta)$ Volts

$A |H(j\omega)| \cos(\omega t + \theta + \angle H(j\omega))$

$\angle H(j\omega)$ = angle of $H(j\omega)$

Response to cosine input at steady-state

$H(s)$: Transfer function

$V_{output}(s) = H(s) V_{input}(s)$



$H(s) = \frac{s + \frac{1}{RC}}{s^2 + \frac{R}{L}s + \frac{1}{LC}}$

$s = j\omega$

We consider:

$|H(j\omega)|$: Gain





$\angle H(j\omega)$: Added phase provided by the system denoted as $H(s)$.


$|H(j\omega)|$: Magnitude response

$\angle H(j\omega)$: Phase response


of the system.

Lowpass, Highpass and Bandpass Systems

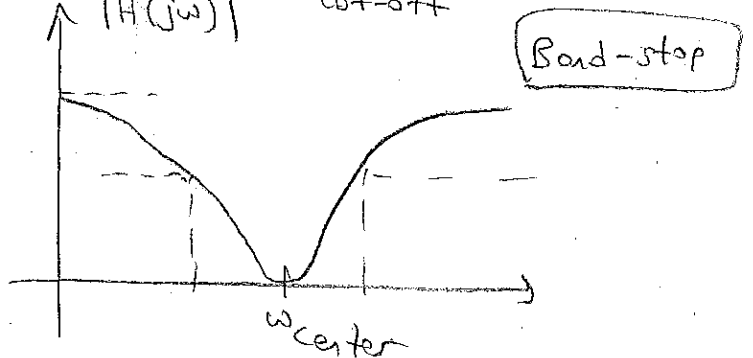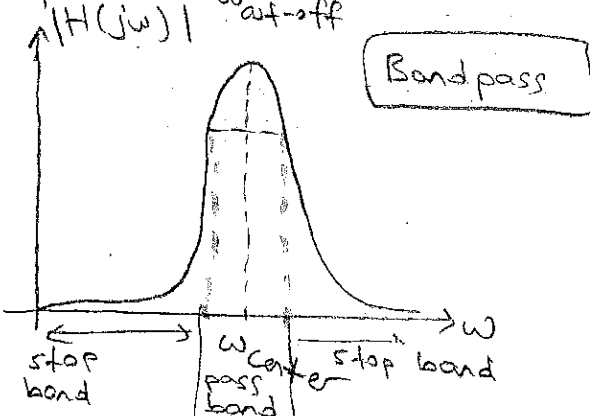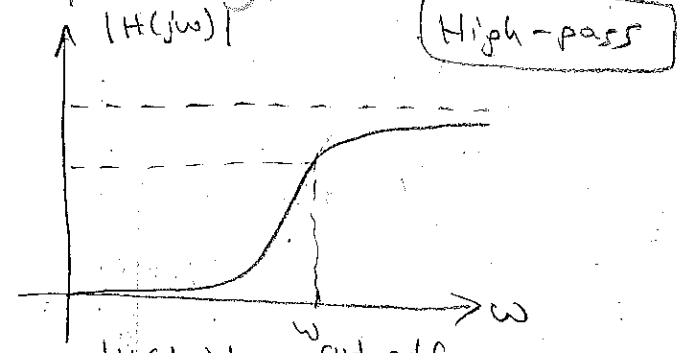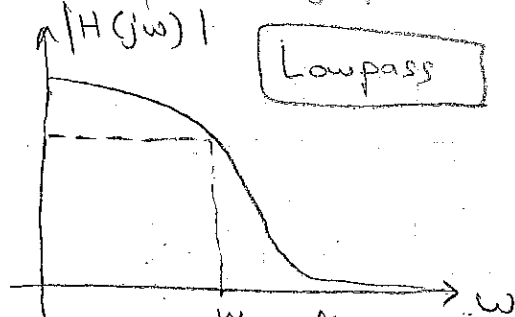


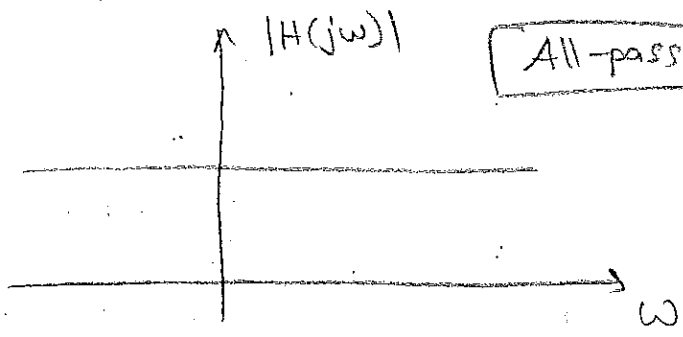

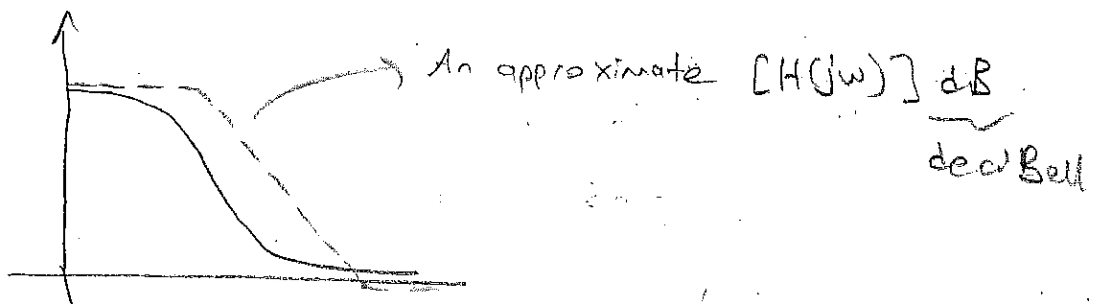
Used for phase correction of the signal at the input.
 (There is no amplification or attenuation).
 → ??



Decibell; Bell (Graham Bell)

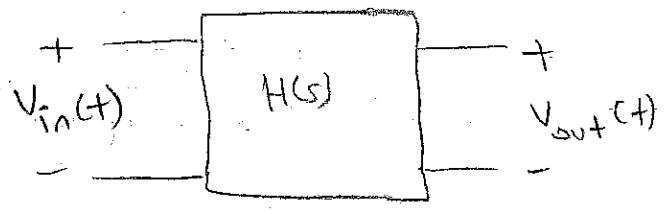

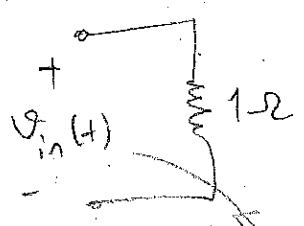Let's assume 1Ω resistance is connected to the V_{input}(t) and V_{output}(t):



$$P_{AV} = \frac{(V_{RMS}^{Input})^2}{R \rightarrow 1\Omega}$$

$$A \cos(\omega t + \theta) \text{ Volts} = \frac{A^2}{2R} \leftarrow 1\Omega$$

Decibell: $10 \log_{10} \frac{\text{Power at the output}}{\text{Power at the input}}$

$$= 10 \log_{10} |H(j\omega)|^2$$

power ratio of two signals
 $A \cos(\omega t + \theta)$
 $A |H(j\omega)| \cos(\omega t + \theta + \angle H(j\omega))$

$$\log(|H_1(j\omega)| |H_2(j\omega)|) = \log(|H_1(j\omega)|) + \log(|H_2(j\omega)|)$$

$$= 20 \log_{10} |H(j\omega)|$$

|H(jw)|: Gain in amplitude for the voltage signal.

Decibell Table

$ H(j\omega) ^2$	$10 \log_{10} H(j\omega) ^2$
1	0
2	3 dB
3	4.77 dB
4	6 dB
5	7 dB
6	7.77 dB
7	8.5
8	9 dB
9	9.54 dB
10	10

$$10 \log_{10}(2) = 3$$

$$10 \log_{10}(2^{10})$$



$$= 10 \log_{10}(1024)$$

$$\approx 10 \times 3$$

$$= 30$$


$10 \log(7^2)$
 $\approx 10 \log(\frac{100}{2})$
 $10 (\log 100 - \log 2)$
Ex: 20 - 3 = 17

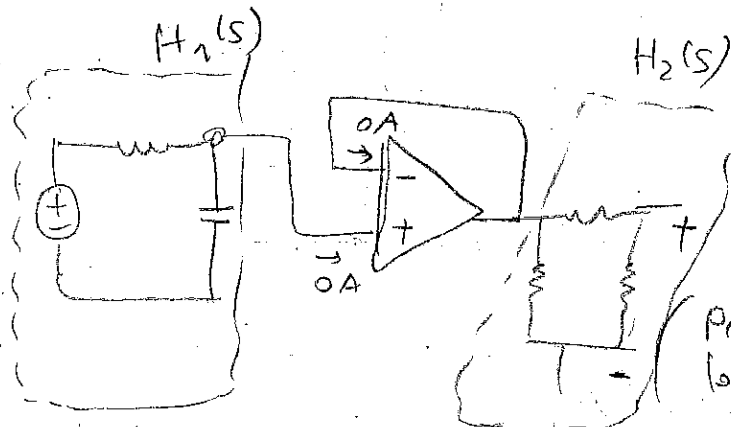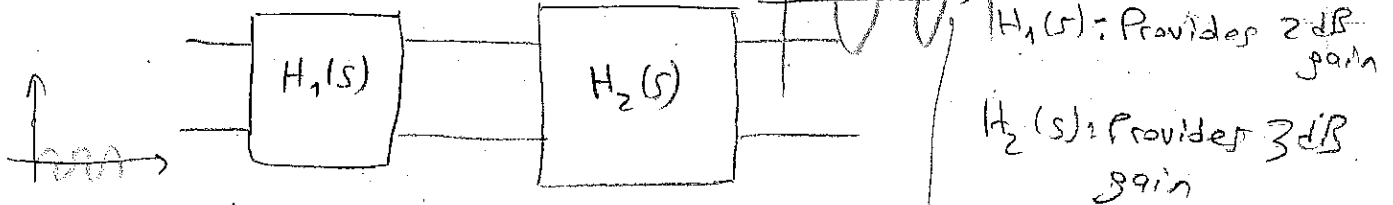Remember the values for 2 and 3 is helpful.



The overall system (the cascade application of $H_1(s)$ and $H_2(s)$) has a gain of 5 dB. Provided that $H_2(s)$ has no loading effect on $H_1(s)$.

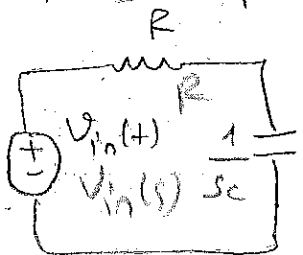Frequency Response Calculation for 1st order circuits



$V_{in}(s)$
 $V_{out}(s)$

$$H(s) = \frac{1/sC}{1 + R/sC} = \frac{1/RC}{s + 1/RC}$$


$$H(j\omega) = \frac{1/RC}{s + 1/RC} \Big|_{s=j\omega} = \frac{1/RC}{j\omega + 1/RC}$$

$$|H(j\omega)| = \frac{1/RC}{\sqrt{\omega^2 + (1/RC)^2}}$$

$$\angle H(j\omega) = -\tan^{-1}\left(\frac{\omega}{1/RC}\right) = -\tan^{-1}(\omega RC)$$

$$|H(j\omega)| = \frac{|K|}{\sqrt{\omega^2 + \alpha^2}}$$
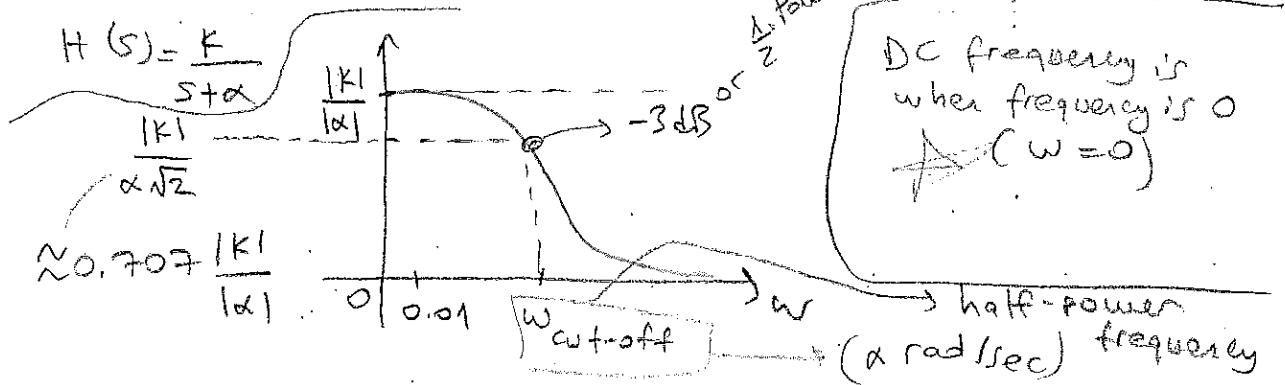
$$\angle H(j\omega) = -\tan^{-1}\left(\frac{\omega}{\alpha}\right)$$



Cut-off frequency is the frequency for which power gain is the half of the maximum value, also called as half-power frequency and also called as -3dB point.


$$|H(j\omega_{\text{cut-off}})| = \frac{\max |H(j\omega)|}{\sqrt{2}} = \frac{|K|}{|\alpha|\sqrt{2}}$$

$$\omega_{\text{cut-off}} = \alpha \text{ rad/sec}$$

Asymptotic Approximation and Sketches:

$$H(s) = \frac{K}{s + \alpha} \quad H(j\omega) = \frac{K}{j\omega + \alpha}$$


$$|H(j\omega)| = \frac{|K|}{\sqrt{\omega^2 + \alpha^2}} = \frac{|K|}{\sqrt{\alpha^2 \left(1 + \left(\frac{\omega}{\alpha}\right)^2\right)}} = \frac{|K|}{|\alpha| \sqrt{1 + \left(\frac{\omega}{\alpha}\right)^2}}$$

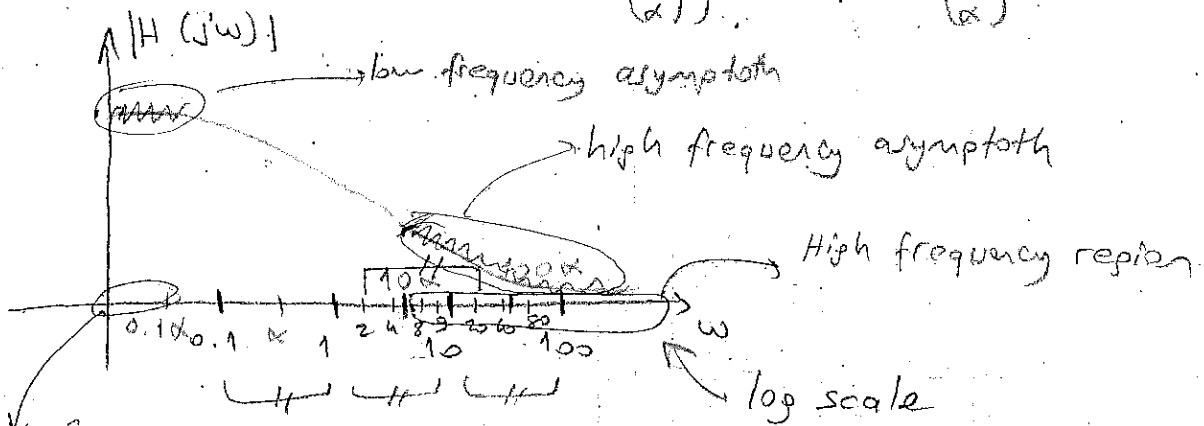

low frequency region

$$\omega \ll \alpha \left(1 + \left(\frac{\omega}{\alpha}\right)^2 \approx 1\right) \rightarrow |H(j\omega)| \approx \frac{|K|}{|\alpha|}$$

$$\omega \gg \alpha, \sqrt{1 + \left(\frac{\omega}{\alpha}\right)^2} = \frac{\omega}{\alpha} \rightarrow |H(j\omega)| = \frac{|K|}{\omega}$$

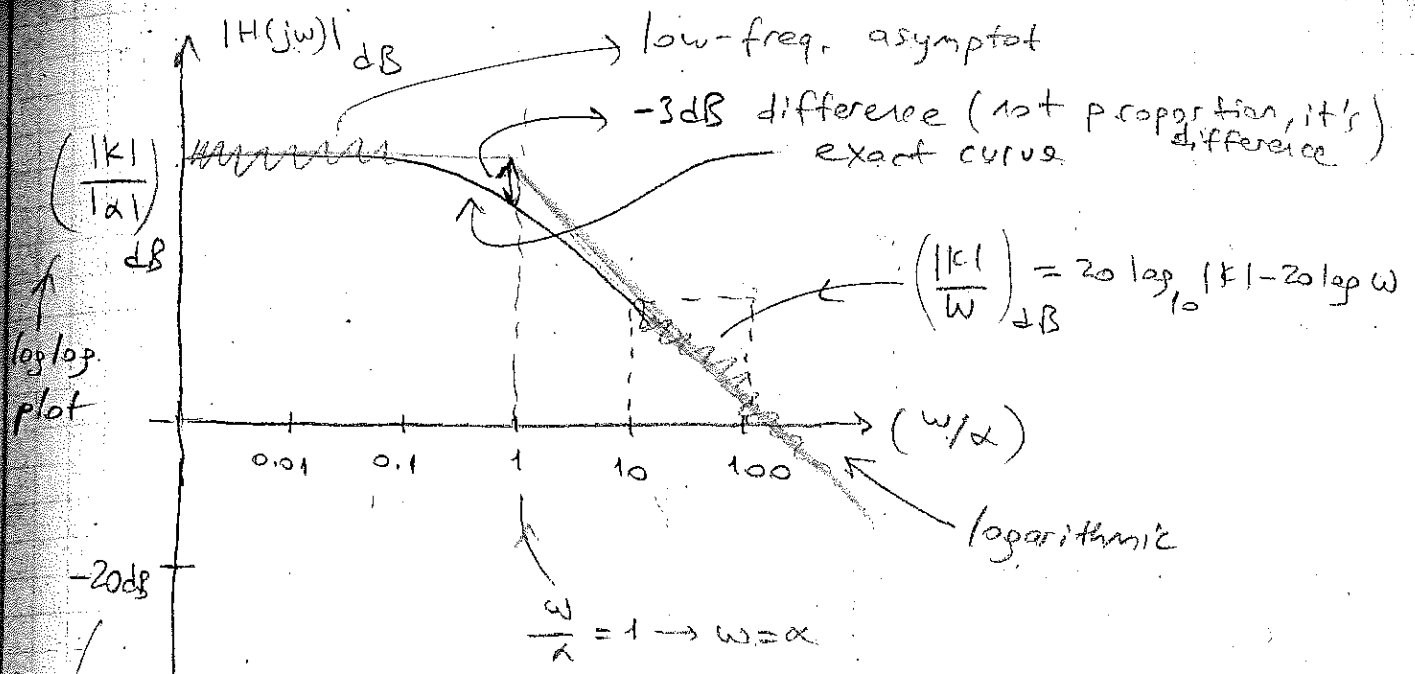



Note: We see straight lines as approximations to $|H(jw)|$ in log-log plot.

Let's find intersection point high/low freq. asymptots

$$\frac{|K|}{|\alpha|} = \frac{|K|}{w} \rightarrow w = \alpha$$

$$|H(jw)| = \frac{1}{10}$$

Frequency Response (cont'd)

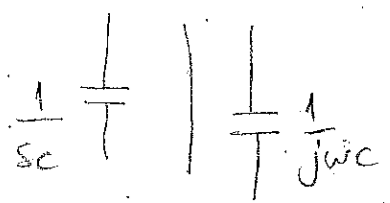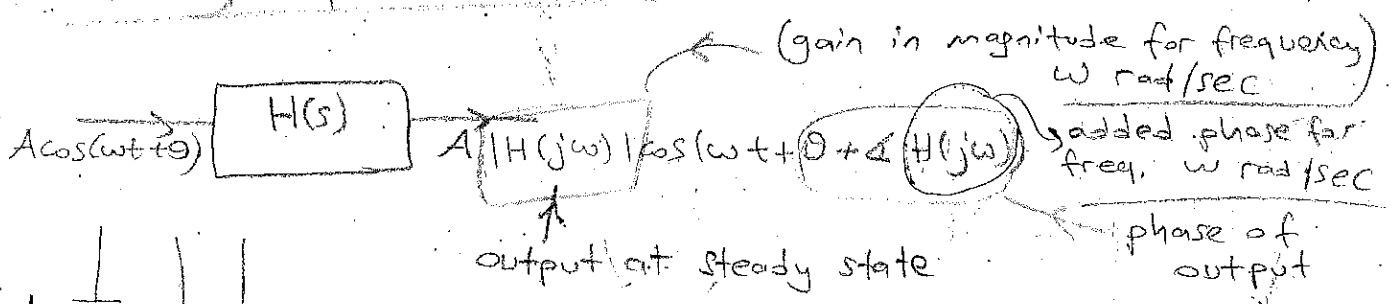

Low pass

$$H(s) = \frac{100}{s+20}$$

$$|H(jw)| = ?$$

$$\angle H(jw) = ?$$

magnitude response

phase response

$$H(s) \Big|_{s=jw} = \frac{100}{jw+20} \rightarrow |H(jw)| = \frac{100}{\sqrt{w^2+20^2}}$$

$$\angle H(jw) = -\tan^{-1}\left(\frac{w}{20}\right)$$

$$H(s) = \frac{100}{20\left(1 + \frac{s}{20}\right)} = \frac{5}{1 + \frac{s}{20}}$$


Standard form = $\frac{K(1 + \frac{s}{\alpha_1})(1 + \frac{s}{\alpha_2})}{(1 + \frac{s}{\beta_1})(1 + \frac{s}{\beta_2})}$

$$H(jw) = \frac{5}{1 + \frac{jw}{20}}$$

$w \ll 20 \rightarrow H(jw) \approx \frac{5}{1+0} = 5$

$w \gg 20 \rightarrow \frac{w}{20} \gg 1 \rightarrow H(jw) \approx \frac{5}{jw/20} = \frac{100}{jw}$

$K=5$
 $\beta_1=20$

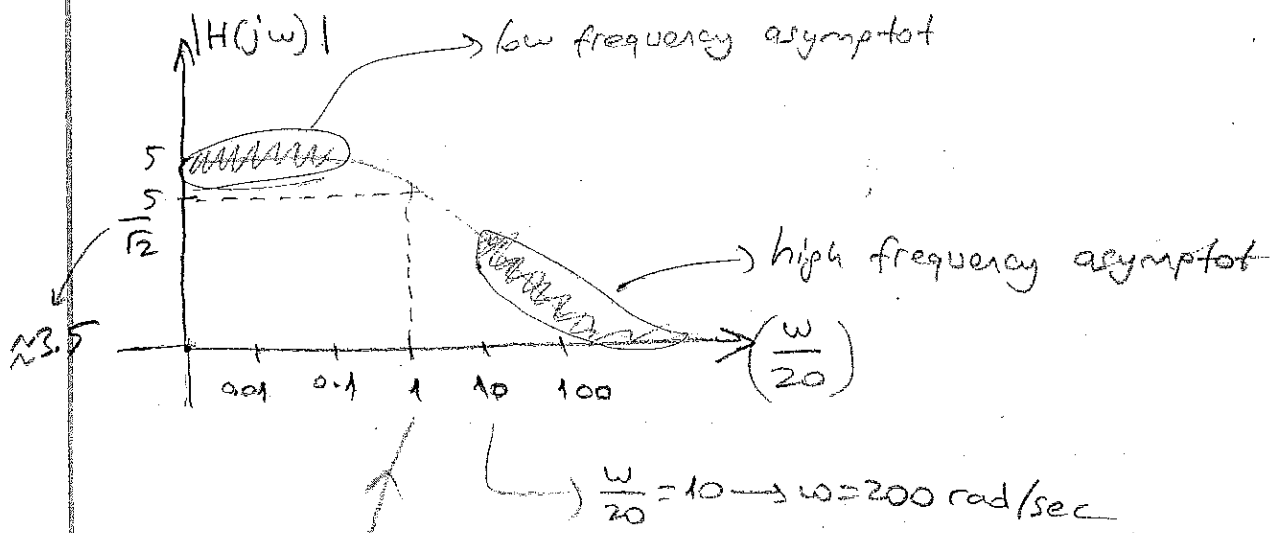


Cut-off freq.

$w_c = 20 \text{ rad/sec}$
is the frequency for which

$$|H(jw)| = \frac{\max(|H(jw)|)}{\sqrt{2}}$$

-3dB point


Half power frequency

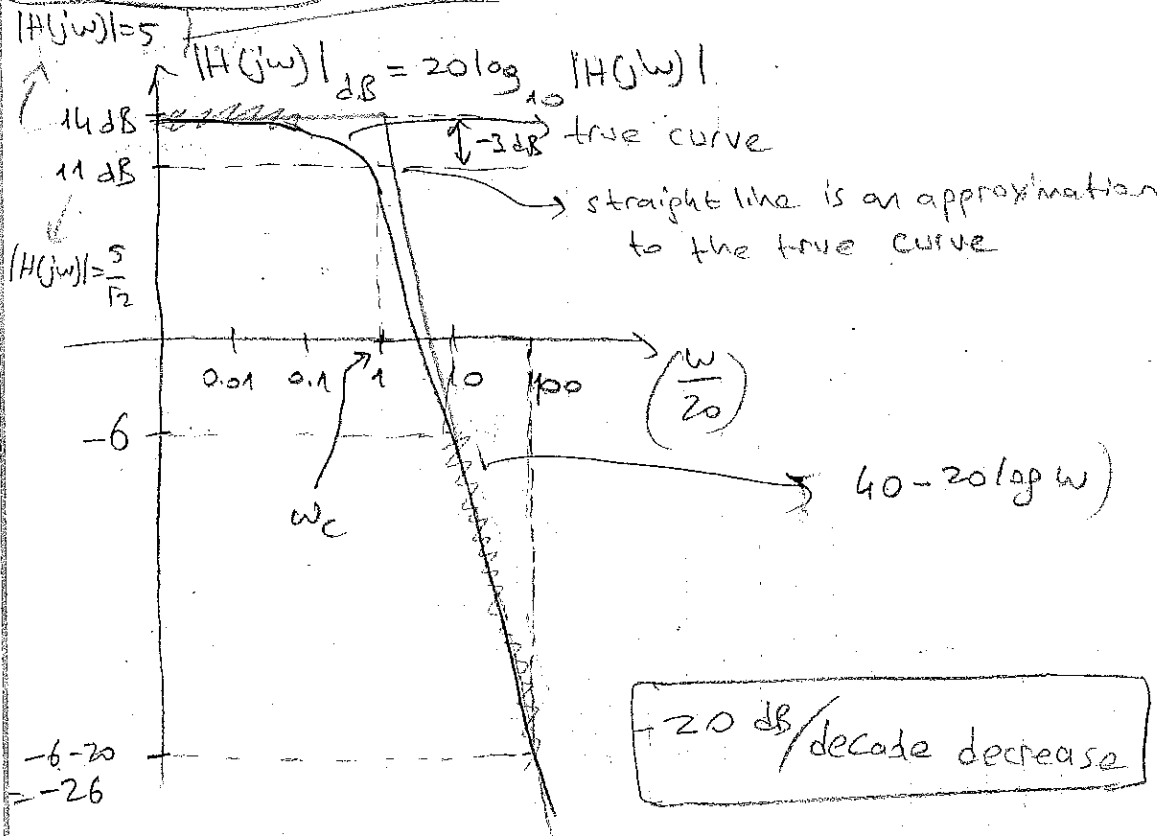

Phase Response

$$\angle H(j\omega) = -\tan^{-1}(\omega/20)$$
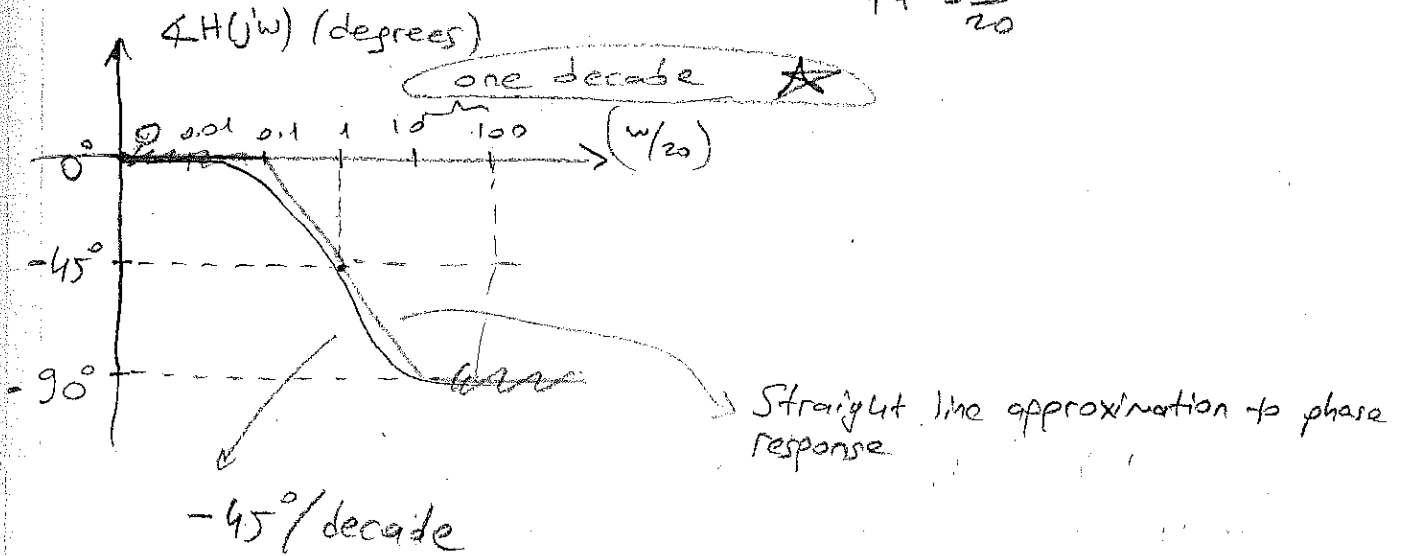
$$H(s) = \frac{5}{1 + \frac{j\omega}{20}}$$



High-pass

$$H(s) = K \frac{s}{s + \alpha}$$

$$|H(j\omega)| = ? \quad \angle H(j\omega) = ?$$


$$H(s) = \frac{K}{\alpha} \cdot \frac{s}{\left(1 + \frac{s}{\alpha}\right)} \rightarrow H(j\omega) = \frac{K}{\alpha} \cdot \frac{j\omega}{1 + \frac{j\omega}{\alpha}}$$

Low frequency
 $\omega \ll \alpha$


$$H(j\omega) \approx \frac{K}{\alpha} \cdot \frac{j\omega}{1}$$

High frequency
 $\frac{\omega}{\alpha} \gg 1$




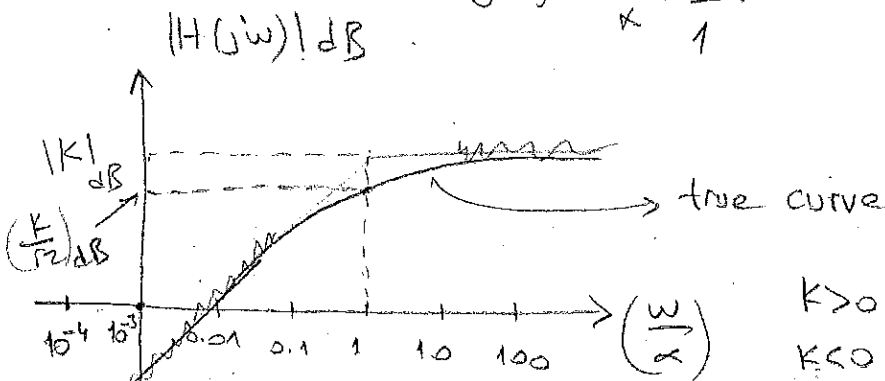
$$H(j\omega) \approx \frac{K}{\alpha} \cdot \frac{j\omega}{\frac{j\omega}{\alpha}} = K$$



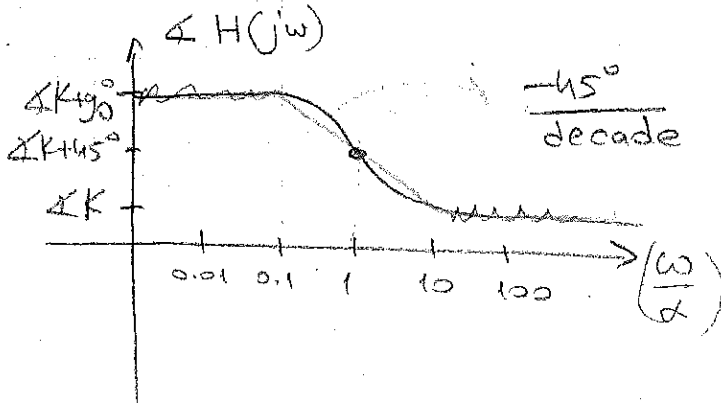
$K > 0$ ($K=3$)
 $K < 0$ ($K=4$)
 $\angle K = 0^\circ$
 $\angle K = \mp 180^\circ$



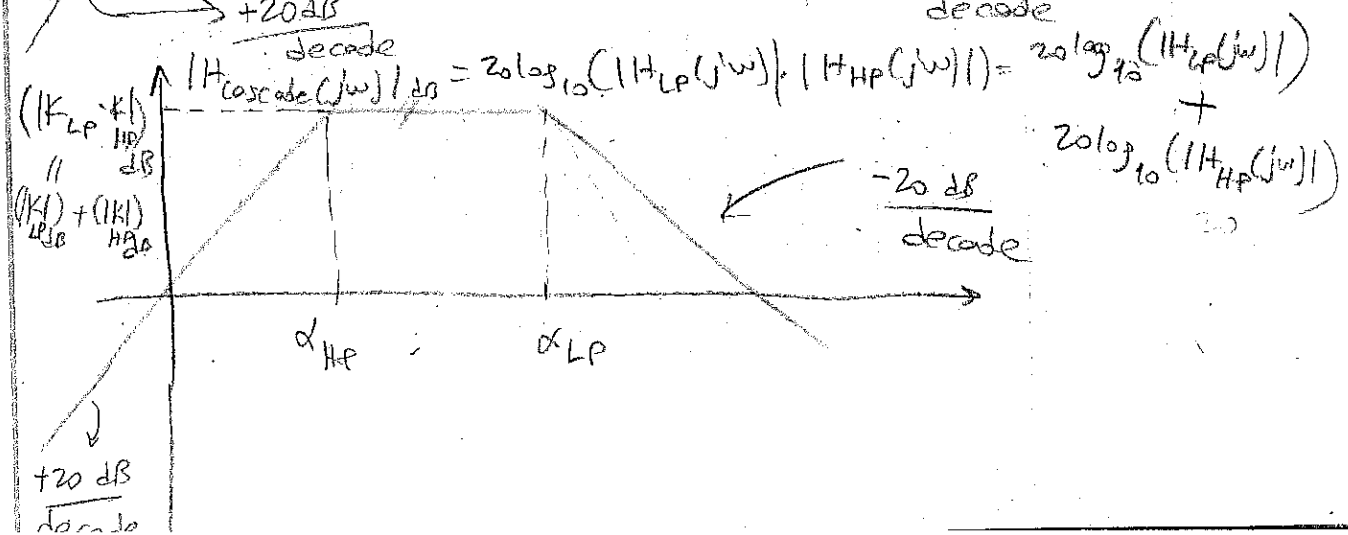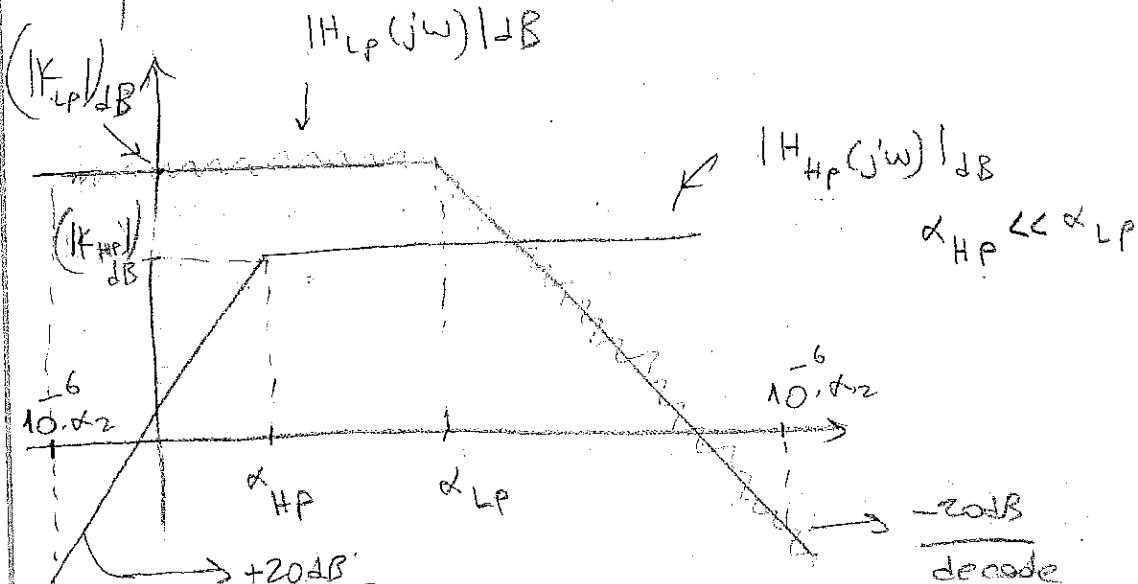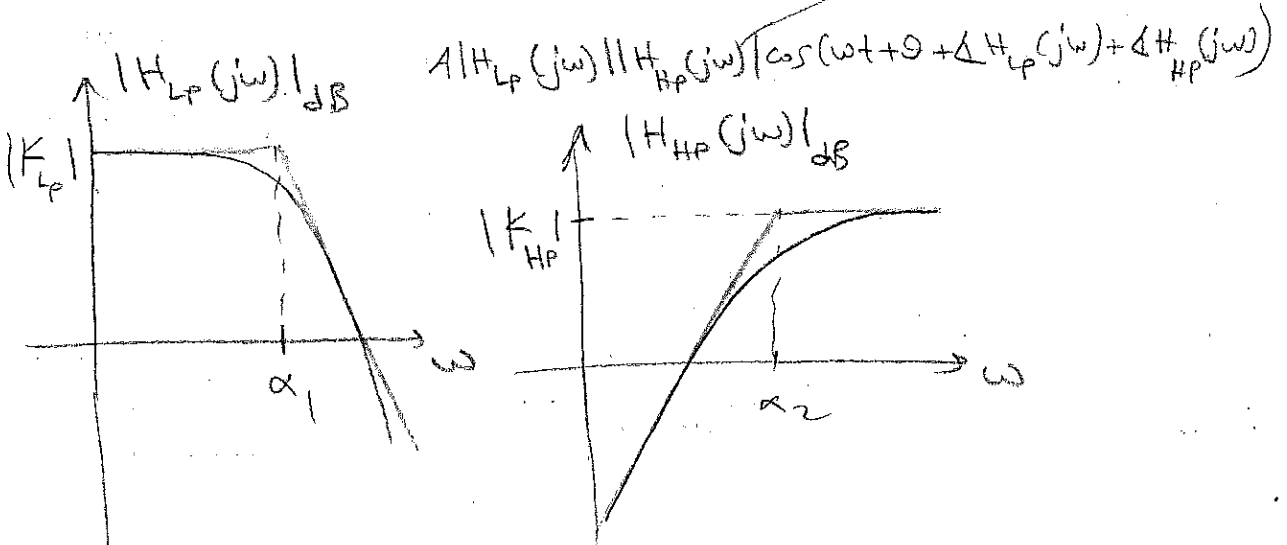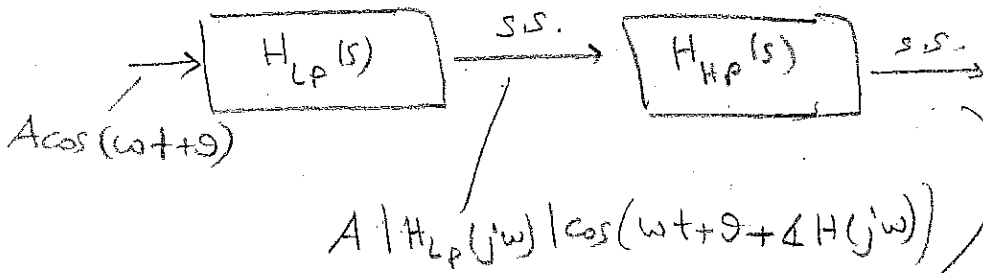
Band-pass Filter by Cascading Low-pass and High-pass Filter



Band-stop Filter

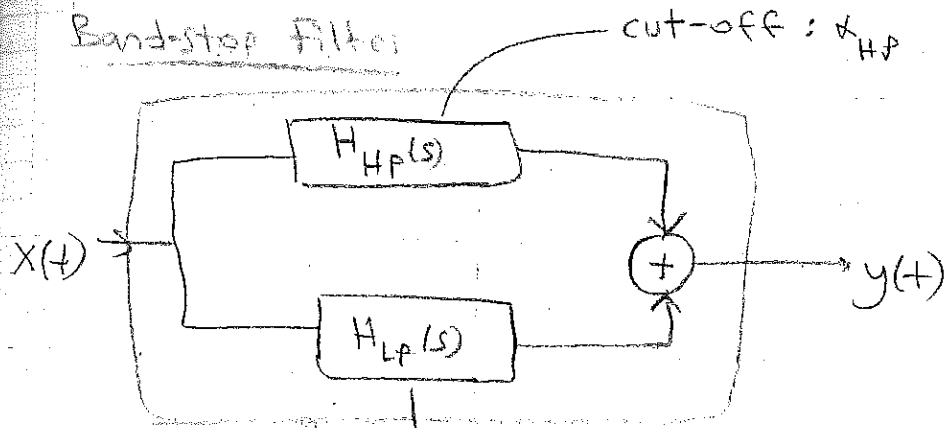


cut-off: ω_{HP}

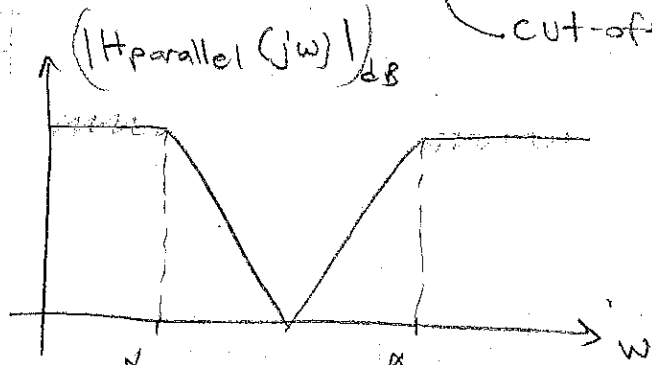


cut-off: ω_{LP}

$$H_{\text{parallel}}(s) = H_{HP}(s) + H_{LP}(s)$$
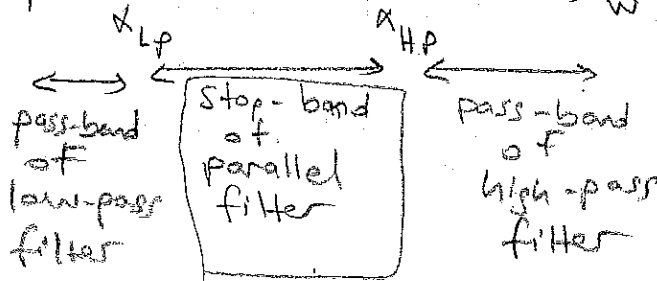
$$H_{\text{parallel}}(j\omega) = H_{HP}(j\omega) + H_{LP}(j\omega)$$




All-pass Filter

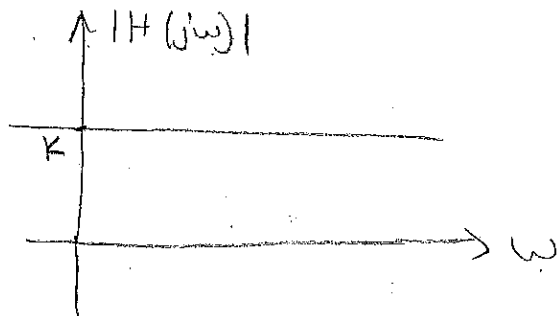

all-pass magnitude response

Ex)


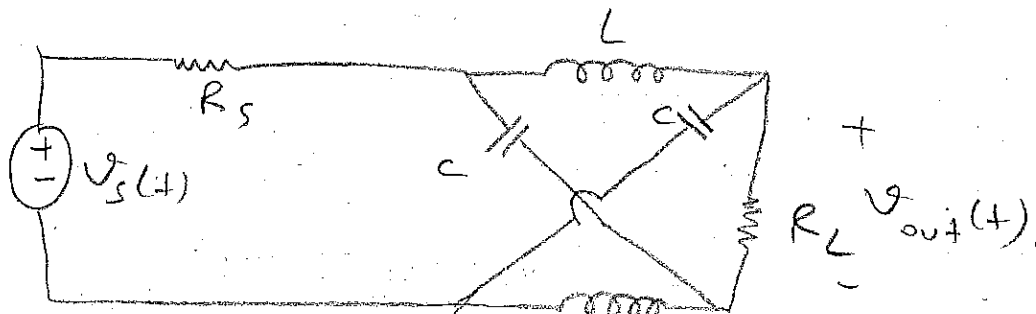


$$\text{If } \frac{L}{C} = R_L^2 \rightarrow H(j\omega) = \frac{R_L}{R_L + R_s} \cdot \frac{\sqrt{1 - j\omega C R_L}}{1 + j\omega C R_L}$$

$$\frac{V_{out}(s)}{V_s(s)} \Big|_{s=j\omega}$$

$$|H(j\omega)| = \frac{R_L}{R_L + R_S}$$

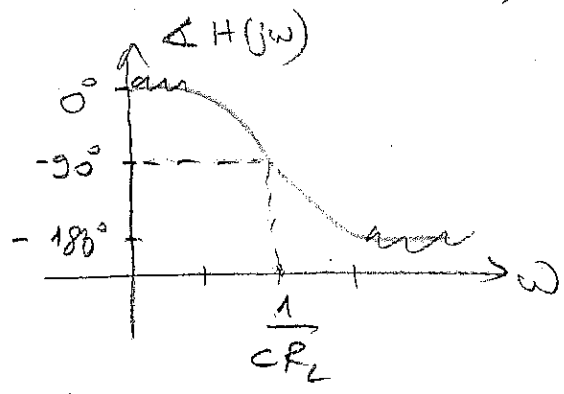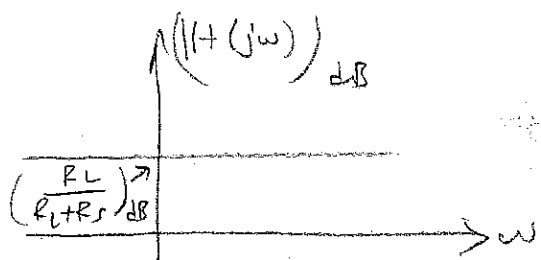
$$\angle H(j\omega) = -2 \tan^{-1}(\omega C R_L)$$



2nd Order Band-pass System:


→ most important system we'll study.
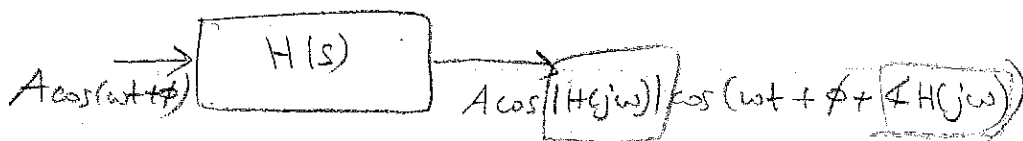
$$H(s) = \frac{Ks}{s^2 + 2\gamma\omega_0 s + \omega_0^2}$$



Gain: Magnitude response w.r.t. ω .

Phase response

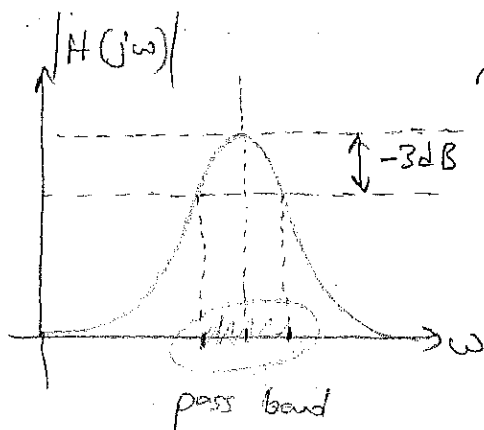

$$H(s) = \frac{Ks}{s^2 + 2\gamma\omega_0 s + \omega_0^2}$$

γ : damping factor

ω_0 : resonance frequency

Poles/Zeros of $H(s)$

Zeros: $s=0 \rightarrow H(s) \downarrow = 0$
 $s=0$

Poles: $s^2 + 2\gamma\omega_0 s + \omega_0^2 = 0$

$$s_{1,2} = \frac{-2\gamma\omega_0 \pm \sqrt{4\gamma^2\omega_0^2 - 4\omega_0^2}}{2}$$

$$s_{1,2} = -\gamma\omega_0 \pm \omega_0 \sqrt{\gamma^2 - 1}$$

→ pole locations!

γ , in general, considered as: $\gamma > 0$.

Observations:

① $\gamma = 1 \rightarrow s_{1,2} = -\gamma \omega_0 = -\omega_0$

Double pole at $s = -\omega_0$


critically damped
 $(s^2 + 2\gamma\omega_0 s + \omega_0^2 = 0 \mid \gamma=1)$

$(s^2 + 2\omega_0 s + \omega_0^2 = 0)$

② $\gamma > 1 \rightarrow s_{1,2}$ are real valued and distinct } overdamped
 $(s_1 \neq s_2)$

③ $\gamma < 1 \rightarrow s_{1,2}$ are complex valued and distinct } underdamped

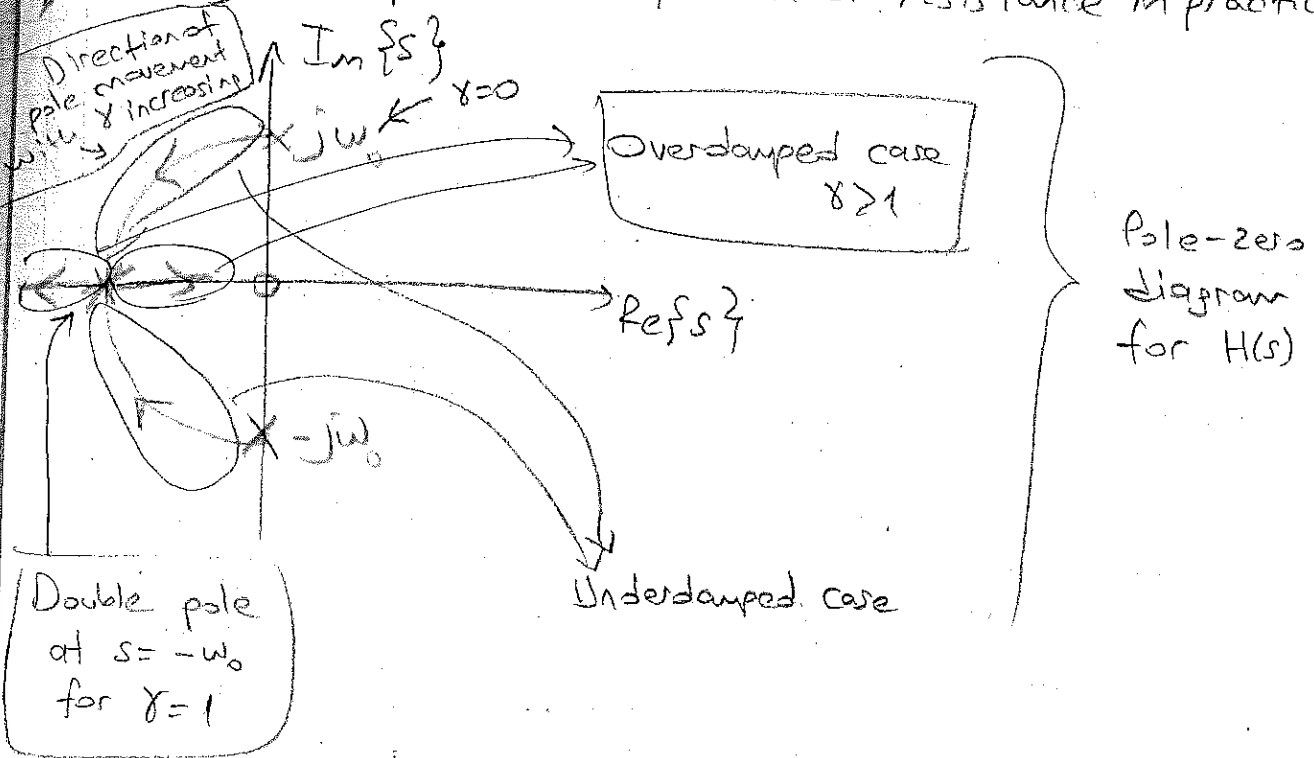* Damping corresponds to friction or resistance in practice.




Note: The case of overdamped band-pass is not of much interest since that case can be written as:


$$H(s) = \frac{Ks}{(s-p_1)(s-p_2)} \rightarrow$$

\uparrow \uparrow
 p_1, p_2 : real numbers

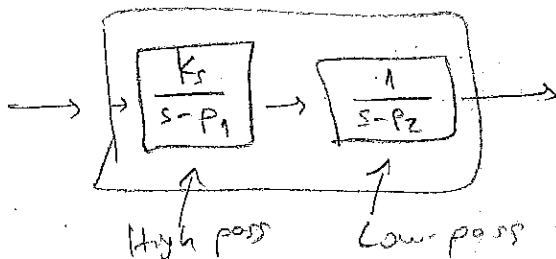This is simply the cascade of high-pass 1st order filter and low-pass 1st order filter.



Parallel RLC

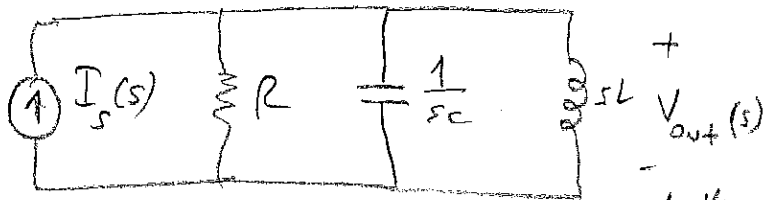

$$H(s) = \frac{V_{out}(s)}{I_s(s)} = \frac{s/L}{s^2 + \frac{1}{RC}s + \frac{1}{LC}}$$

Let's compare with

$$\frac{Ks}{s^2 + 2\gamma\omega_0 s + \omega_0^2}$$

$$H(s) = \frac{Ks}{s^2 + 2\gamma\omega_0 s + \omega_0^2}$$

$$K = \frac{1}{C} \quad \omega_0 = \sqrt{\frac{1}{LC}} \quad \gamma = \frac{1}{2} \sqrt{\frac{L}{R}}$$

$$H(j\omega) = \frac{Kj\omega}{- \omega^2 + j2\gamma\omega_0\omega + \omega_0^2} \cdot \frac{1/j\omega}{1/j\omega}$$

$$= \frac{K}{2\gamma\omega_0 + \frac{\omega_0^2 - \omega^2}{j\omega}} = \frac{K}{\omega_0(2\gamma - j[\frac{\omega_0}{\omega} - \frac{\omega}{\omega_0}])}$$

$$= \frac{K}{\omega_0(2\gamma + j[\frac{\omega}{\omega_0} - \frac{\omega_0}{\omega}])}$$

$$|H(j\omega)| = \frac{|K|}{\omega_0 \sqrt{4\gamma^2 + [\frac{\omega}{\omega_0} - \frac{\omega_0}{\omega}]^2}}$$

$$|H(j\omega)| = \frac{|K|}{\omega_0 \sqrt{4\gamma^2 + [\frac{\omega}{\omega_0} - \frac{\omega_0}{\omega}]^2}}$$

$$\omega_0 \sqrt{4\gamma^2 + [\frac{\omega}{\omega_0} - \frac{\omega_0}{\omega}]^2}$$

No need for absolute magnitude value response

Case ①: $\omega \ll \omega_0 \rightarrow |H(j\omega)| \approx \frac{|K|}{\omega_0 \frac{\omega_0}{\omega}} \approx \frac{|K|}{\omega_0^2} \cdot \omega$
 (Low frequency asymptote)

$$|H(j\omega)| = \frac{|K|}{\omega_0 \sqrt{4\gamma^2 + [\frac{\omega}{\omega_0} - \frac{\omega_0}{\omega}]^2}}$$


$$\omega_0 \sqrt{4\gamma^2 + [\frac{\omega}{\omega_0} - \frac{\omega_0}{\omega}]^2}$$

too small too small

Case (2): $\omega \gg \omega_0$
 (High frequency asymptote)

$$|H(j\omega)| \approx \frac{K}{\omega_0 \frac{\omega}{\omega_0}} = \frac{K}{\omega}$$

Case (3): $\omega = \omega_0 \rightarrow |H(j\omega)| = \frac{K}{2\gamma\omega_0}$

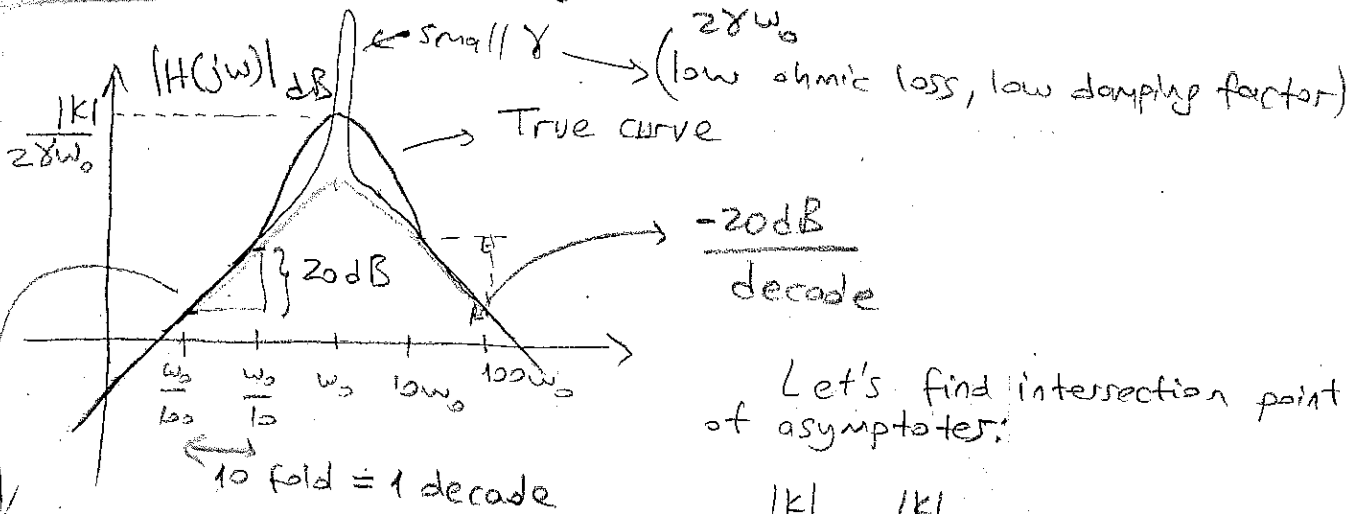

Let's find intersection point of asymptotes:

$$\frac{|K|}{\omega} = \frac{|K|}{\omega_0^2} \cdot \omega$$

$\omega = \omega_0$
 is the intersection point

High frequency
 Low frequency

the slope = $\frac{20 \text{ dB}}{\text{decade}}$

Note! (1) when $\gamma = \frac{1}{2} \rightarrow$ true curve passes from the intersection point of asymptotes.

(2) when $\gamma \ll \frac{1}{2} \rightarrow$ There is a high valued, much above the intersection point of asymptotes

(3) when $\gamma \gg \frac{1}{2} \rightarrow$ The peak location of true curve is below the intersection point of asymptotes.

Q1 Does the true curve really have its peak location (maxima) at $\omega = \omega_0$?

1: $|H(j\omega)| = \frac{|K|}{\omega_0 \sqrt{4\gamma^2 + \left[\frac{\omega}{\omega_0} - \frac{\omega_0}{\omega}\right]^2}}$

To maximize $|H(j\omega)|$

\rightarrow we need to


minimize $\sqrt{\dots}$

we need to minimize $\sqrt{\left(\frac{\omega}{\omega_0} - \frac{\omega_0}{\omega}\right)^2}$

Clearly $\omega = \omega_0$ minimizes \rightarrow

So indeed $\omega = \omega_0$ is the maxima of $|H(j\omega)|$.

Bandwidth:

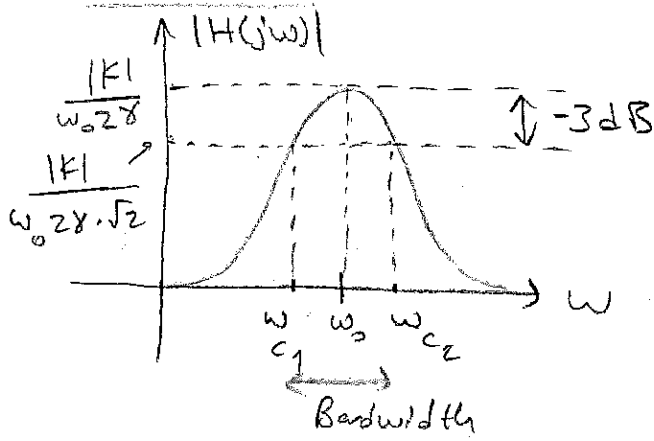

Bandwidth = $w_{c2} - w_{c1}$

We can find w_{c1} and w_{c2} by

$$|H(jw_{c1})| = \frac{|K|}{w_0 2\gamma} \cdot \frac{1}{\sqrt{2}}$$

$$\rightarrow \left(\frac{w}{w_0} - \frac{w_0}{w}\right)^2 = 4\gamma^2$$

By solving the quadratic equation:

$$w_{c2} = w_0 (\gamma + \sqrt{1 + \gamma^2})$$

$$w_{c1} = w_0 (-\gamma + \sqrt{1 + \gamma^2})$$

$$\text{B.W.} = w_{c2} - w_{c1} = 2\gamma w_0$$


Note: $H(s) = \frac{Ks}{s^2 + 2\gamma w_0 s + w_0^2}$

Resonant freq. (w_0)

B.W. = $2\gamma w_0$

Note that, $w_0 = \sqrt{w_{c1} \cdot w_{c2}}$

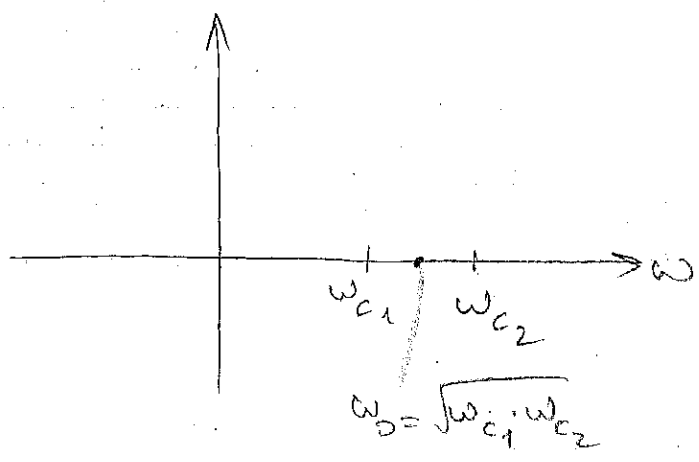Hence, w_0 is at the geometric mean of w_{c1} and w_{c2} .



But, if w axis is logarithmic

$$w_0 = \frac{\log((w_{c1} \cdot w_{c2})^{1/2})}{2}$$

$$= \frac{\log(w_{c1}) + \log(w_{c2})}{2}$$

Quality Factor

$$Q = \frac{\omega_0}{B.W.} \rightarrow Q = \frac{1}{2\delta}$$

$$B.W. = 2\delta\omega_0$$

Quality factor

So, a high Q filter has a high peak at $\omega = \omega_0$.

Quality factor indicates the bandwidth of the filter w.r.t. its expected operating frequency ω_0 .


$$Q = \frac{1}{2\delta} \quad \delta = \frac{1}{2Q}$$

Phase Response:

$$H(j\omega) = \frac{K}{\omega_0 (2\delta + j[\frac{\omega}{\omega_0} - \frac{\omega_0}{\omega}])}$$


$$\angle H(j\omega) = \angle K - \tan^{-1} \left(\left(\frac{\omega}{\omega_0} - \frac{\omega_0}{\omega} \right) \cdot \left(\frac{1}{2\delta} \right) \right) = \angle K - \tan^{-1} \left(\frac{1}{2\delta} \left(\frac{\omega}{\omega_0} - \frac{\omega_0}{\omega} \right) \right)$$

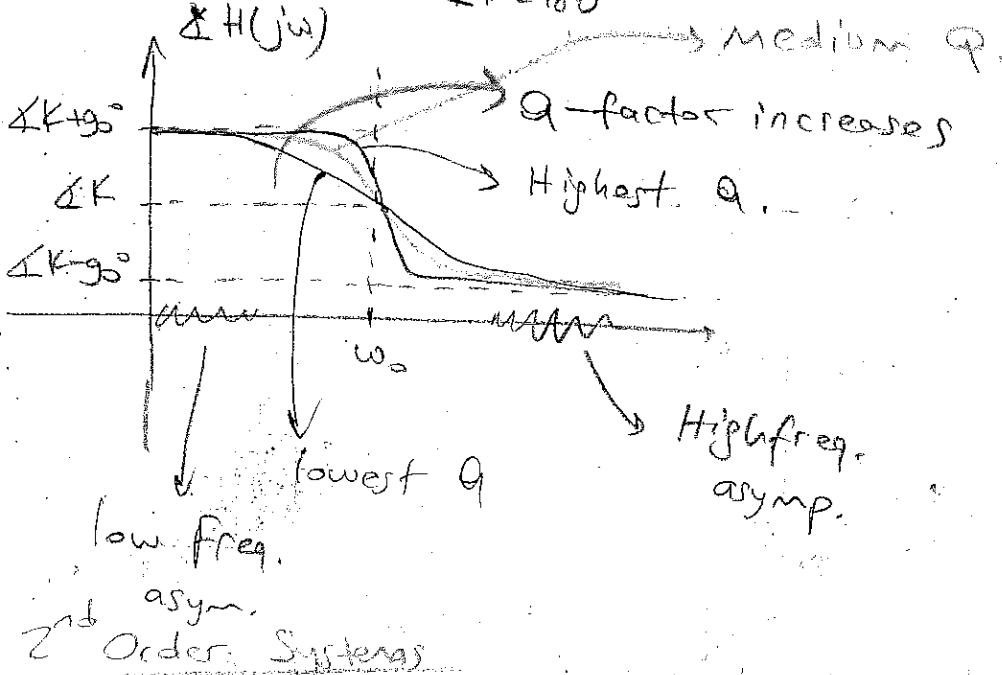$K > 0 \rightarrow \angle K = 0^\circ$
 $K < 0 \rightarrow \angle K = 180^\circ$



Last week's 2nd order Band-pass:

23.05.2016

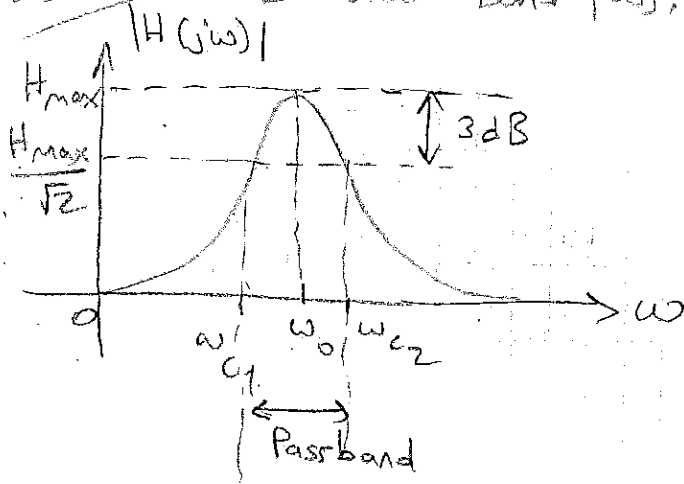


$$\frac{Ks}{s^2 + 2\delta\omega_0 s + \omega_0^2}$$

ω_0 : resonance frequency
 δ : Damping factor


2nd order low-pass:

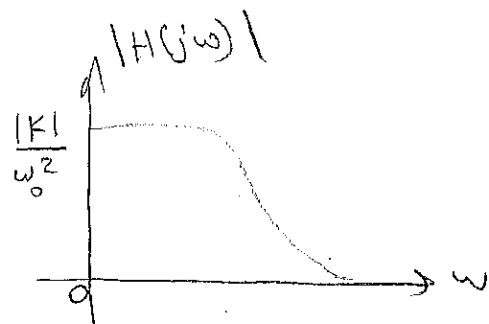Transfer function: $H(s) = \frac{K}{s^2 + 2\gamma\omega_0 s + \omega_0^2}$



Later 2nd order high-pass

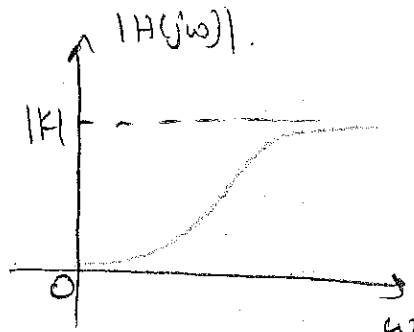Transfer function: $H(s) = \frac{Ks^2}{s^2 + 2\gamma\omega_0 s + \omega_0^2}$



2nd order low-pass

Substituting $s = j\omega$ into the transfer function: $H(s) \Big|_{s=j\omega} = \frac{K}{-\omega^2 + \omega_0^2 + j2\gamma\omega_0\omega} = \frac{K}{\omega_0^2 \left[1 - \left(\frac{\omega}{\omega_0}\right)^2 + j2\gamma\left(\frac{\omega}{\omega_0}\right) \right]}$

Low frequency approximation: $\omega \ll \omega_0 \left(\frac{\omega}{\omega_0} \ll 1 \right)$

Low frequency asymptote: $\approx \frac{K}{\omega_0^2}$


High frequency approximation: $\omega \gg \omega_0$

High frequency asymptote: $\approx \frac{K}{\omega_0^2} \left[-\frac{\omega^2}{\omega_0^2} \right] = \frac{-K}{\omega^2}$

At resonance $\omega = \omega_0$: $\rightarrow = \frac{K}{\omega_0^2 (j2\gamma)}$

Medium Q ($Q > 1$)

Low Q ($Q < 1$)

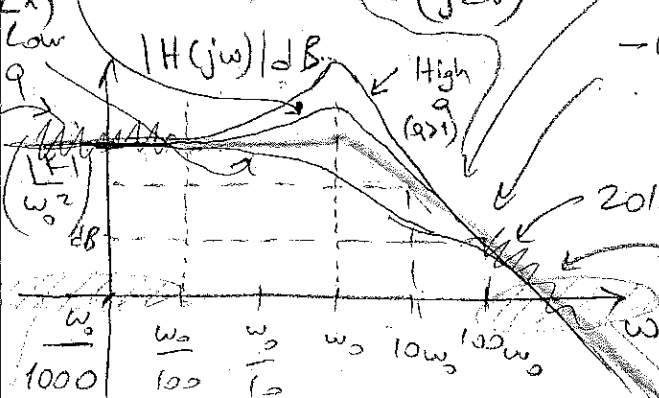

-12/octave

-40 dB/decade

Asymptotic approximation: $20 \log_{10} \left(\frac{|K|}{\omega^2} \right)$

High frequency asymptote

Low frequency region

High frequency region

Low frequency asymptote: $|H(j\omega)| = 20 \log_{10} \frac{|K|}{\omega^2}$

High frequency asymptote: $|H(j2\omega)| = 20 \log_{10} \frac{|K|}{4\omega^2}$
 $|H(j\omega)| = 20 \log_{10} 4$

Let's find the intersection point of Low and High frequency asymptotes:

$$\frac{|K|}{\omega_0^2} = \frac{|K|}{\omega^2} \rightarrow \omega = \omega_0$$


Intersection point of asymptotes

$$Q \triangleq \frac{1}{2\gamma}$$

Quality factor

$$-(1+j) \leftarrow -1-j \neq \sqrt{2} \tan^{-1}(-1/-1)$$

$$-1-\sqrt{2} \tan^{-1}(1/1)$$

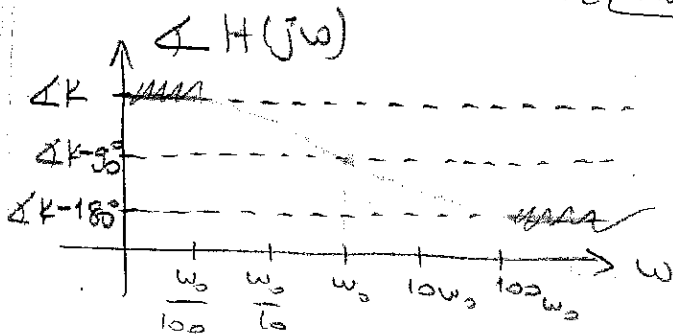

$$1+j \rightarrow \sqrt{2} \tan^{-1}(1)$$

$$-1-j \neq \sqrt{2} \tan^{-1}(-1/-1)$$

II	I
III	IV

\tan^{-1} is defined only in 1st and 4th quadrants.

Note: The maxima of $|H(j\omega)|$ of 2nd order low-pass filter is at:

$$\omega_m = \omega_0 \sqrt{1 - \frac{1}{2Q^2}}$$

Second Order High Pass system


(Page: 1.17)

$$H(s) = \frac{Ks^2}{s^2 + 2\gamma\omega_0 s + \omega_0^2}$$

$$H(j\omega) = \frac{K(-\omega^2)}{\omega_0^2 - \omega^2 + j2\gamma\omega_0\omega}$$

$$\rightarrow = -K \frac{(\omega/\omega_0)^2}{1 - (\frac{\omega}{\omega_0})^2 + j\gamma}$$

Ex 1:

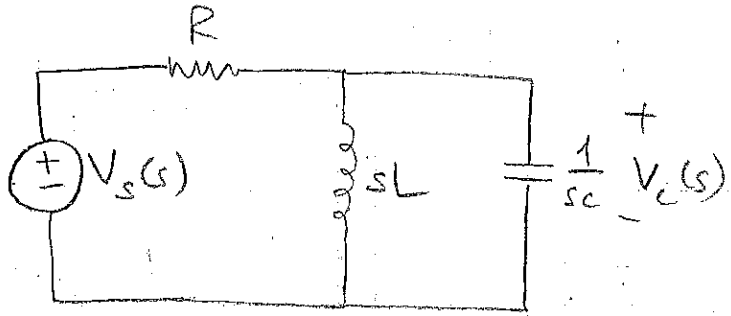

$$H(s) = \frac{V_c(s)}{V_s(s)} = \frac{s/RC}{s^2 + \frac{s}{RC} + \frac{1}{LC}}$$

$$H_2(s) = \frac{V_R(s)}{V_s(s)}$$

$$-V_s(s) + V_R(s) + V_c(s) = 0$$

$$H_2(s) = \frac{V_R(s)}{V_s(s)} = 1 - \frac{V_c(s)}{V_s(s)} = 1 - H(s)$$

$\rightarrow H_2(j\frac{1}{\sqrt{LC}}) = 0$; It is a band-stop filter.

$$H(s) = \frac{s/RC}{s^2 + \frac{1}{RC}s + \frac{1}{LC}} = k \frac{s}{s^2 + 2\gamma\omega_0 s + \omega_0^2}$$

$$L = \frac{1}{4} \text{ H}$$

$$R = 1 \text{ k}\Omega$$

$$C = 1 \text{ nF}$$


$$= \frac{s \cdot 1000}{s^2 + 1000s + (2000)^2}$$

$$\omega_0 = 2000$$

$$\gamma = \frac{1}{4} \rightarrow (Q = \frac{1}{2\gamma} = 2)$$

$$2\gamma\omega_0$$

Band-width = 1000 rad/sec

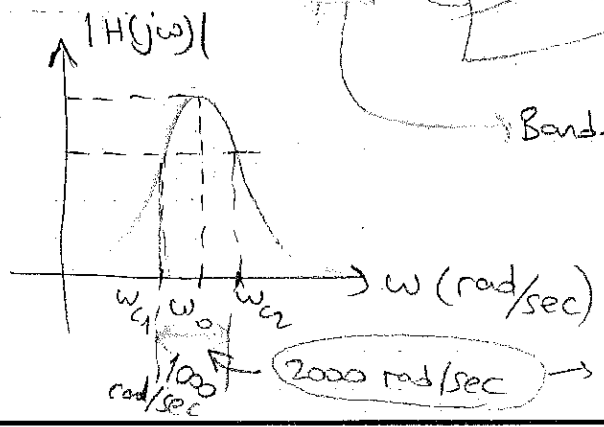

$$= 2\pi f_0 \rightarrow f_0 = \frac{1000}{\pi} \text{ Hz}$$

$$\omega_{c1} = \omega_0 \left(-\gamma + \sqrt{1 + \gamma^2} \right)$$

$$\omega_{c2} = \omega_0 \left(+\gamma + \sqrt{1 + \gamma^2} \right)$$

#1,28


$$\omega_0 = \sqrt{\omega_{c1} \cdot \omega_{c2}}$$

Geometric mean

Active Filters: Kinnari ★★

Filters constructed with R, L, C components (passive components) and op-amps (active components) are called active filters.

Ex:

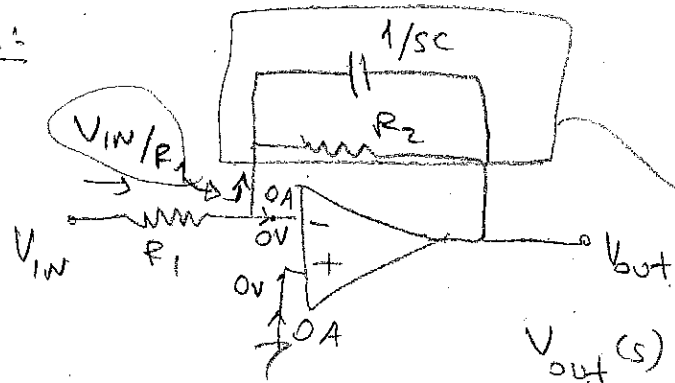

Assume ideal op-amp in linear region.

$$Z(s) = \frac{1}{sC} \parallel R_2$$

$$V_{out}(s) = -Z(s) \cdot \frac{V_{in}(s)}{R_1}$$

$$= -\frac{1}{R_1} \frac{\frac{1}{sC} \cdot R_2}{\frac{1}{sC} + R_2} V_{in}(s)$$

$$= \left[\frac{-R_2}{R_1} \right] \frac{1}{1 + sCR_2} V_{in}(s) = \frac{K}{s + \omega_c}$$


Note: ① $|K| > 1$ by selecting $R_1 \ll R_2$.

② $\angle K = 180^\circ$.

General Definition of Resonance:

The resonance frequency is the frequency for which input impedance $Z(j\omega)$ is purely real.

Ex:

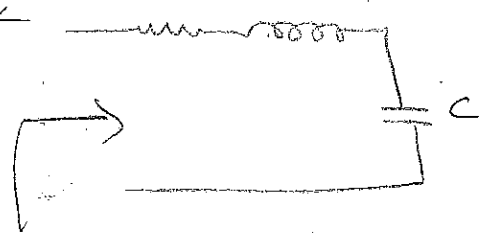


$$Z(s) = R + j\omega L - \frac{j}{\omega C} = R + j\left(\omega L - \frac{1}{\omega C}\right)$$

$$\Rightarrow Z_{in}(j\omega_0) = R \text{ when } \omega_0 L - \frac{1}{\omega_0 C}$$

$$\rightarrow \omega_0^2 = \frac{1}{LC} \rightarrow \omega_0 = \frac{1}{\sqrt{LC}}$$

$Z_{in}(j\omega)$

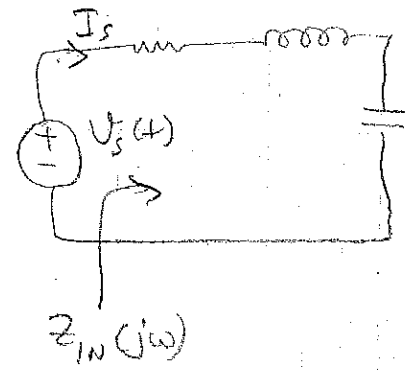


$$I_s^{RMS} = \frac{V_s^{RMS}}{|Z(j\omega)|}$$

$$P_{AVG}^{Resistor} = (I_R^{RMS})^2 \cdot R$$

$$= \left(\frac{V_s^{RMS}}{|Z(j\omega)|} \right)^2 \cdot R$$

$P_{AVG}^R(\omega)$ is maximum when $\omega = \omega_0$

resonance frequency.

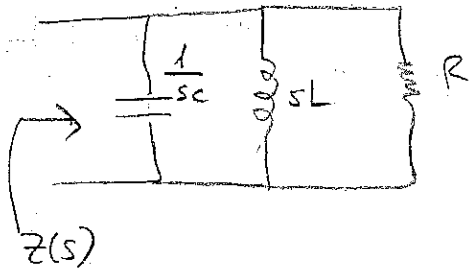

$$z(s) = \frac{1}{Y(s)} \rightarrow \text{admittance}$$

$$Y(s) = \frac{1}{R} + \frac{1}{sL} + sC$$

If $z(s)$ is real $Y(s)$ must be real too.


$$Y(j\omega_0) = \frac{1}{R} + j(\omega_0 C - \frac{1}{\omega_0 L})$$

has to be zero at resonance

$$\omega_0 = \frac{1}{\sqrt{LC}}$$

Magnitude/Frequency Scaling

Magnitude Scaling

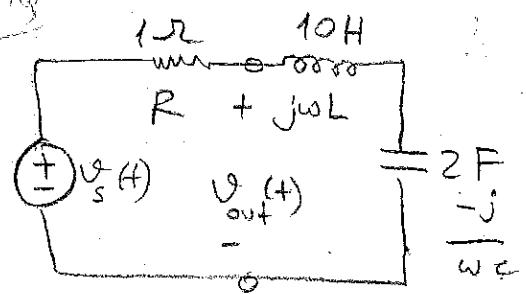

$$H(j\omega) = \frac{V_{out}(j\omega)}{V_s(j\omega)} = \frac{z_L(j\omega) + z_c(j\omega)}{R + z_L(j\omega) + z_c(j\omega)} = \frac{j\omega L - j/\omega C}{R + j\omega L - j/\omega C}$$


$$H(j\omega) = \frac{k_m}{k_m} H(j\omega) = \frac{j\omega k_m L - j \frac{1}{\omega C}}{R k_m + j\omega k_m L - j \frac{1}{\omega C}}$$

Magnitude Scaling:

- $R \rightarrow k_m R$
- $L \rightarrow k_m L$
- $C \rightarrow \frac{C}{k_m}$


Frequency Scaling

Prototype filter

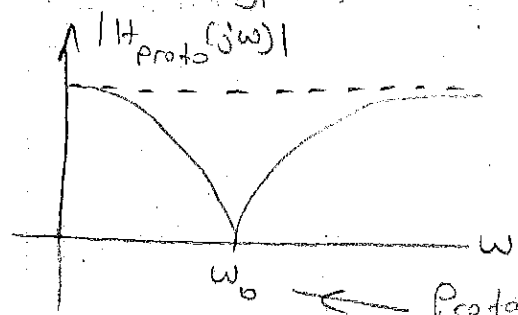


$$H(s) = \frac{s^2 + \omega_0^2}{s^2 + 2\zeta\omega_0 s + \omega_0^2}$$

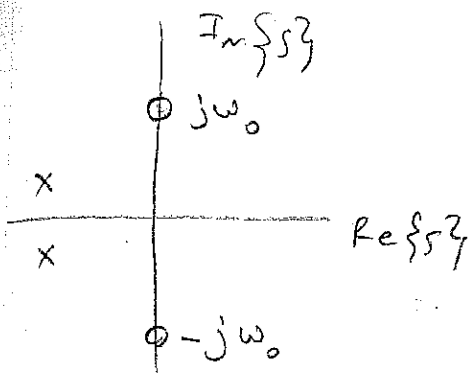Prototype filter has a zero at $s = \pm j\omega_0$



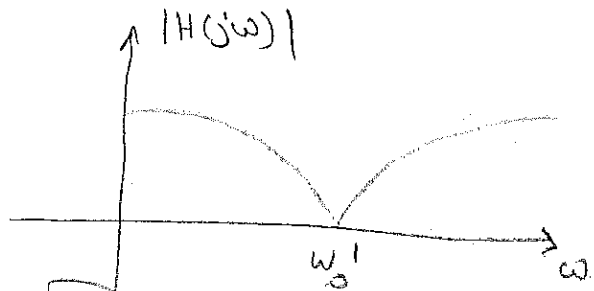Designed filter has a different band-stop frequency ω_0' .



$$H_{\text{desired}}(j\omega) = H_{\text{prototype}}\left(j\omega \frac{\omega_0}{\omega_0'}\right) = H_{\text{prototype}}\left(j\frac{\omega}{k_f}\right)$$

$$H_{\text{desired}}(j\omega_0') = H_{\text{prototype}}\left(j\omega_0' \cdot \frac{\omega_0}{\omega_0'}\right) = 0$$

$$H_{\text{prototype}}(j\omega) = \frac{j\omega L - \frac{j}{\omega C}}{R + j\omega L - \frac{j}{\omega C}}$$

$$H_{\text{prototype}}\left(\frac{j\omega}{k_f}\right) = \frac{j\omega \frac{L}{k_f} - \frac{j}{\omega \frac{C}{k_f}}}{R + j\omega \frac{L}{k_f} - \frac{j}{\omega \frac{C}{k_f}}}$$

Frequency Scaling

$$k_f = \frac{\omega_0'}{\omega_0} \leftarrow \text{new frequency}$$

$$R \rightarrow R$$

$$L \rightarrow \frac{L}{k_f}$$

$$C \rightarrow \frac{C}{k_f}$$

Bode Plots

1st Order Bode Plots:-

$$H(s) = 12500 \frac{s+10}{(s+50)(s+500)}$$

Step (1): Bring $H(s)$ into standard form,


$$H(s) = \frac{K \left(1 + \frac{s}{\alpha_1}\right) \left(1 + \frac{s}{\alpha_2}\right)}{\left(1 + \frac{s}{\beta_1}\right) \left(1 + \frac{s}{\beta_2}\right)}$$

$$H(s) = 12500 \frac{10 \left(1 + \frac{s}{10}\right)}{50 \left(1 + \frac{s}{50}\right) 500 \left(1 + \frac{s}{500}\right)} = 5 \frac{1 + \frac{s}{10}}{\left(1 + \frac{s}{50}\right) \left(1 + \frac{s}{500}\right)}$$

Step (2):

$$|H(j\omega)|_{\text{dB}} = 20 \log_{10} 5 + 20 \log_{10} \left|1 + \frac{j\omega}{10}\right| - 20 \log_{10} \left|1 + \frac{j\omega}{50}\right| - 20 \log_{10} \left|1 + \frac{j\omega}{500}\right|$$

Let's examine $20 \log_{10} \left|1 + \frac{j\omega}{\alpha_1}\right|$

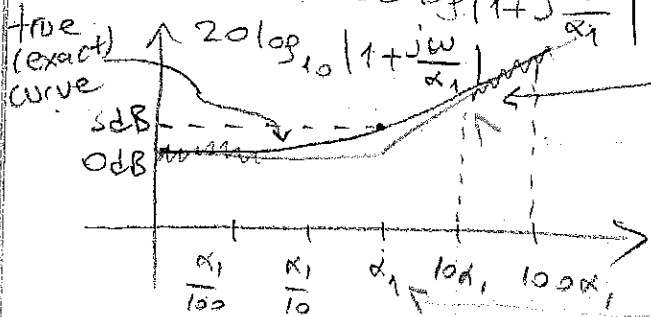


ω_c : ω cut-off



ω critical-frequency

ω corner-freq

Bode plot/straight line approximation

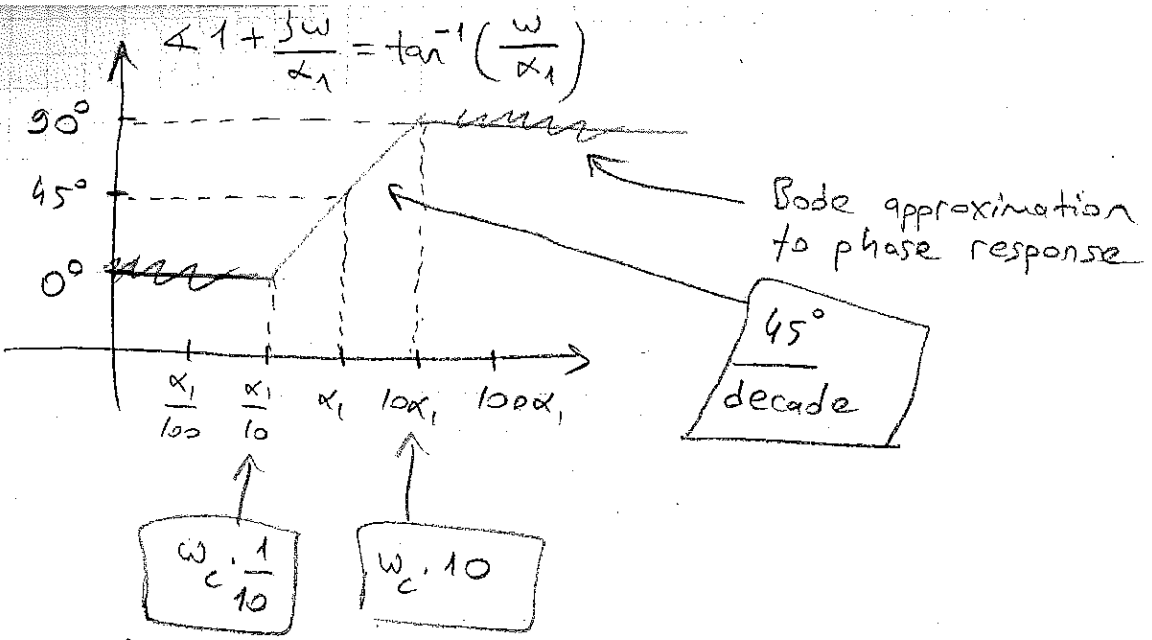

Do the plot

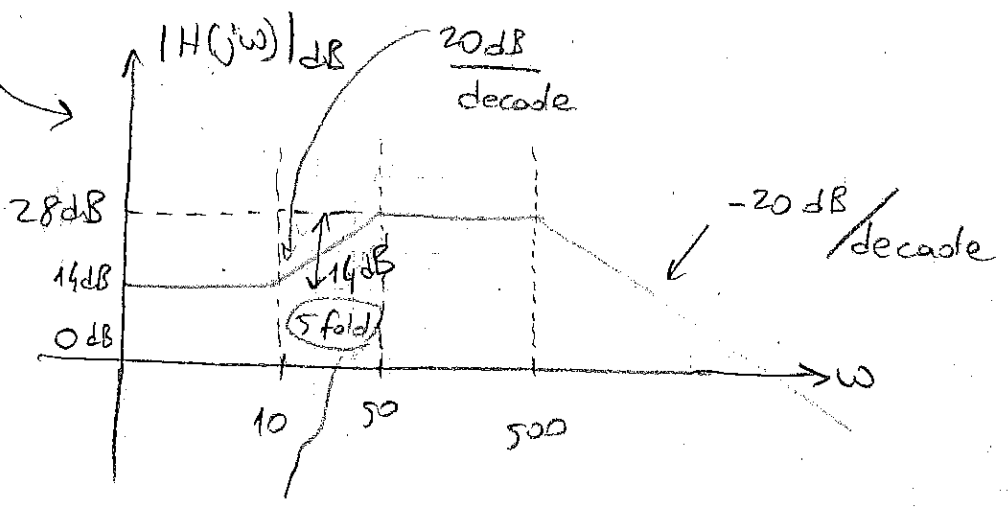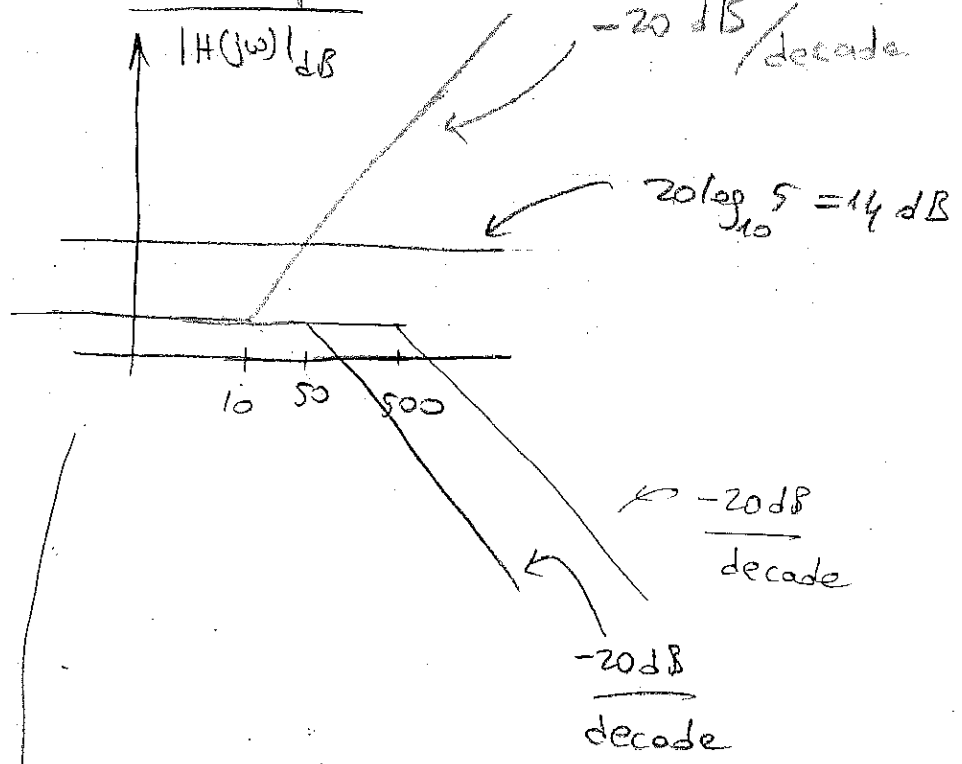

$20 \log_{10} (5) = 14 \text{ dB}$

